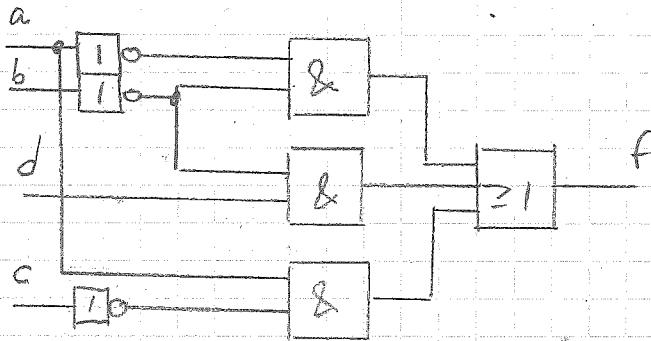


1/

| | | | | |
|----|----|----|----|----|
| | f | c | d | |
| | 00 | 01 | 11 | 10 |
| ab | 00 | 11 | 11 | 11 |
| | 01 | 00 | 00 | 00 |
| | 11 | 11 | 10 | 00 |
| | 10 | 11 | 11 | 00 |

3 2


$$f = \bar{a} \cdot \bar{b} + \bar{b} \cdot d + a \cdot \bar{c}$$



5 p

1b)
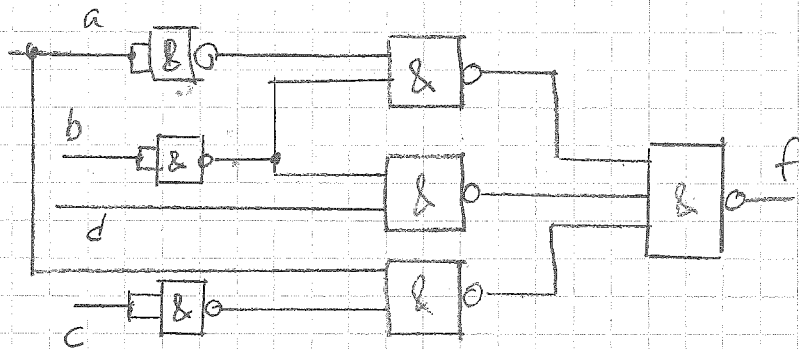
$$f = \bar{a} \cdot \bar{b} + \bar{b} \cdot d + a \cdot \bar{c} = \overline{\bar{a} \cdot \bar{b}} \cdot \overline{\bar{b} \cdot d} \cdot \overline{a \cdot \bar{c}}$$



3 p

2/

| x_1, x_0 | y_1, y_0 | z_1, z_0 | u |
|------------|------------|------------|-----|
| 00 | 01 | 10 | 1 |
| 00 | 01 | 11 | 1 |
| 00 | 10 | 11 | 1 |
| 01 | 10 | 11 | 1 |

| | | | | |
|------------|------------|------------|------------|-----|
| | x_1, x_0 | y_1, y_0 | z_1, z_0 | u |
| | 00 | 01 | 11 | 10 |
| x_1, x_0 | 00 | | | |
| | 01 | | | |
| | 11 | | | |
| | 10 | | | |

$z_1, z_0 = 00$

| | | | | |
|------------|------------|------------|------------|-----|
| | x_1, x_0 | y_1, y_0 | z_1, z_0 | u |
| | 00 | 01 | 11 | 10 |
| x_1, x_0 | 00 | | | |
| | 01 | | | |
| | 11 | | | |
| | 10 | | | |

$z_1, z_0 = 01$

| | | | | |
|------------|------------|------------|------------|-----|
| | x_1, x_0 | y_1, y_0 | z_1, z_0 | u |
| | 00 | 01 | 11 | 10 |
| x_1, x_0 | 00 | | | |
| | 01 | | | |
| | 11 | | | |
| | 10 | | | |

$z_1, z_0 = 10$

| | | | | |
|------------|------------|------------|------------|-----|
| | x_1, x_0 | y_1, y_0 | z_1, z_0 | u |
| | 00 | 01 | 11 | 10 |
| x_1, x_0 | 00 | | | |
| | 01 | | | |
| | 11 | | | |
| | 10 | | | |

$z_1, z_0 = 11$

$$u = \bar{x}_1 \cdot \bar{x}_0 \cdot \bar{y}_1 \cdot y_0 \cdot z_1 + \bar{x}_1 \cdot y_1 \cdot \bar{y}_0 \cdot z_1 \cdot z_0$$

Tentamen 14/12-12 blad 2

3) a) $93_{10} = 1 \cdot 64 + 0 \cdot 32 + 1 \cdot 16 + 1 \cdot 8 + 1 \cdot 4 + 0 \cdot 2 + 1 \cdot 1$

$$= 1011101_2$$

b) $93_{10} = 5 D_{16}$

c) $2 \quad 01011101 = 10100010$ *ORR! 8 bitar!*
 $\quad\quad\quad + \quad\quad\quad 1$
 $\quad\quad\quad \hline 10100011$

Svar: 10100011

d) $83_{10} = 01010011$

$$83_{10} - 93_{10} \Rightarrow \quad 01010011$$

$$+ \quad 10100011$$

$$\hline 11110110$$

*Negativt!
MSB tecken bit.*


$2 \quad 11110110 = 00001001$
 $\quad\quad\quad + \quad\quad\quad 1$
 $\quad\quad\quad \hline 00001010$

Svar: $-00001010_2 = -10$


5)

| | mod 8=0 | mod 8=1 | mod 8=0 | mod 8=1 |
|----------------------|----------------------|----------------------|----------------------|----------------------|
| q_3, q_2, q_1, q_0 | q_3, q_2, q_1, q_0 | q_3, q_2, q_1, q_0 | T_3, T_2, T_1, T_0 | T_3, T_2, T_1, T_0 |
| 0000 | 0001 | 0001 | 0001 | 0001 |
| 0001 | 0010 | 0010 | 0011 | 0011 |
| 0010 | 0011 | 0011 | 0001 | 0001 |
| 0011 | 0100 | 0100 | 0111 | 0111 |
| 0100 | 0101 | 0101 | 0001 | 0001 |
| 0101 | 0110 | 0110 | 0011 | 0011 |
| 0110 | 0111 | 0111 | 0001 | 0001 |
| 0111 | 1000 | 0000 | 1111 | 0111 |
| 1000 | 1001 | 1001 | 0001 | 0001 |
| 1001 | 1010 | 1010 | 0011 | 0011 |
| 1010 | 1011 | 1011 | 0001 | 0001 |
| 1011 | 1100 | 1100 | 0111 | 0111 |
| 1100 | 1101 | 1101 | 0001 | 0001 |
| 1101 | 1110 | 1110 | 0011 | 0011 |
| 1110 | 1111 | 1111 | 0001 | 0001 |
| 1111 | 0000 | 0000 | 1111 | 1111 |

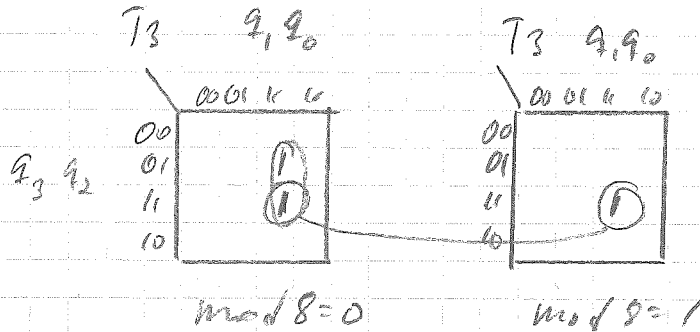5) Fourts! $T_0 = 1$ $T_1 = q_0$ $T_2 = q_2 \cdot q_1$


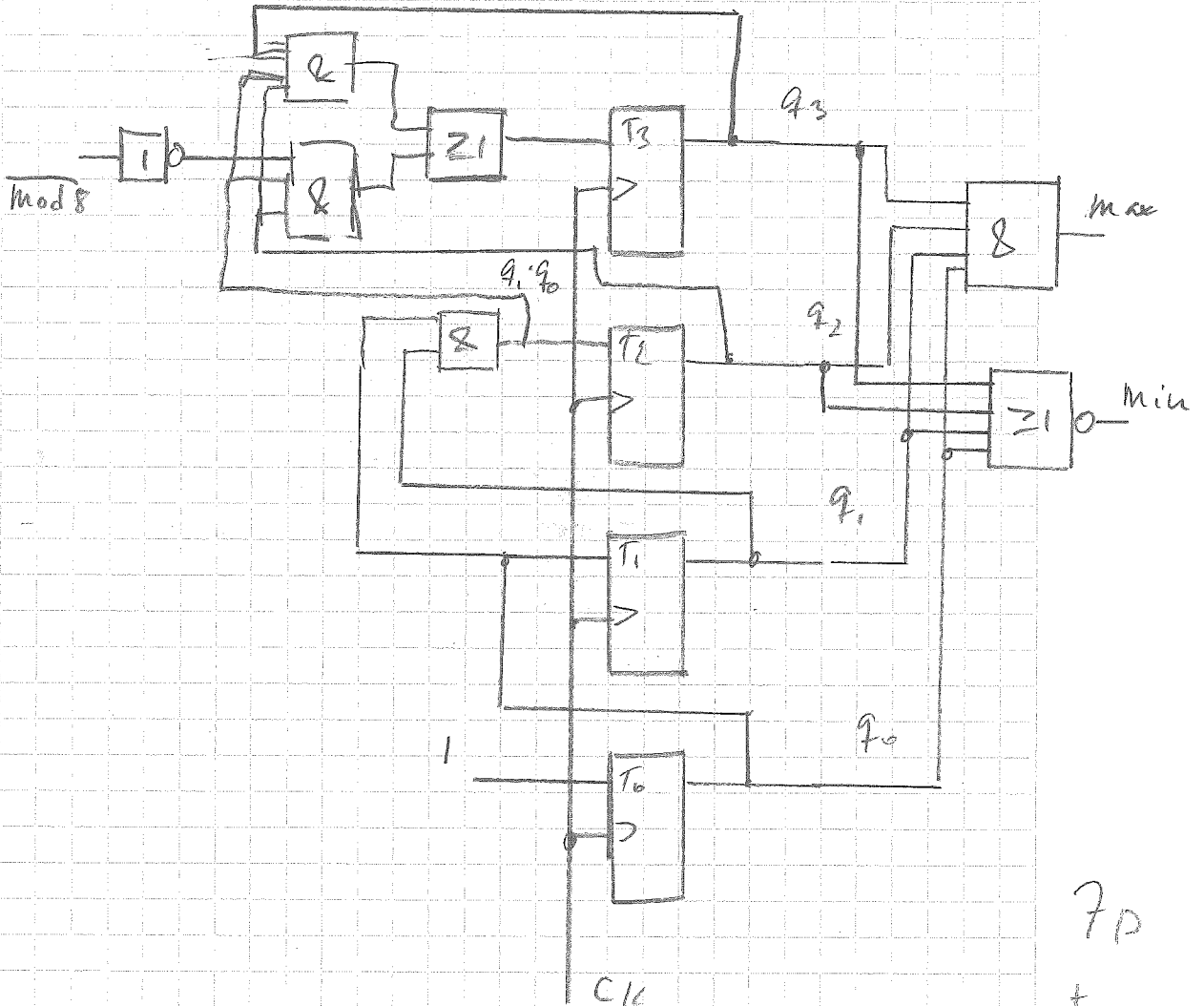
$$T_3 = \text{mod } 8 \cdot q_2 \cdot q_1 \cdot q_0 + q_3 \cdot q_2 \cdot q_1 \cdot q_0$$




$$\text{max} = q_3 \cdot q_2 \cdot q_1 \cdot q_0$$

$$\text{min} = \overline{q_3} \cdot \overline{q_2} \cdot \overline{q_1} \cdot \overline{q_0} = \overline{q_3 + q_2 + q_1 + q_0}$$




7p
+
3p

Tentamen 14/12-12 blad 4

7)

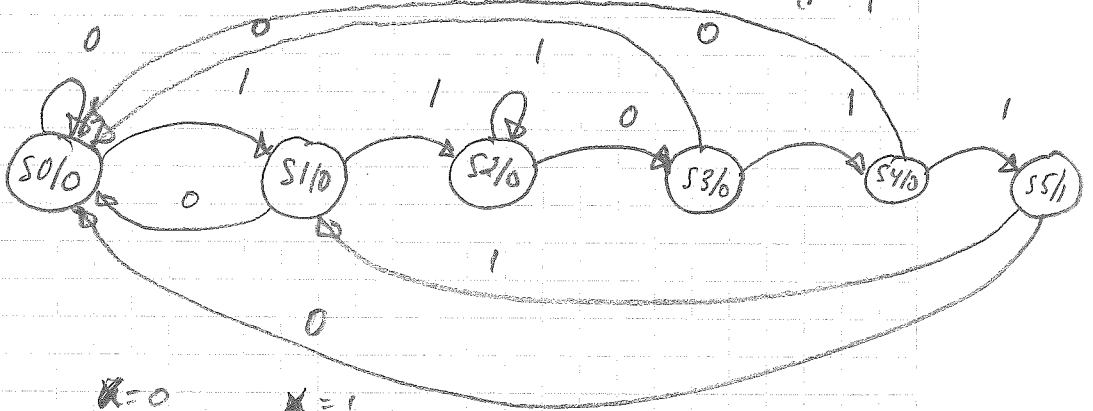

| q_2 q_1 q_0 | $x=0$ | $x=1$ | u |
|-------------------|-------|-------|-----|
| 000 | 000 | 001 | 0 |
| 001 | 000 | 010 | 0 |
| 010 | 011 | 010 | 0 |
| 011 | 000 | 100 | 0 |
| 100 | 000 | 101 | 0 |
| 101 | 000 | 001 | 1 |

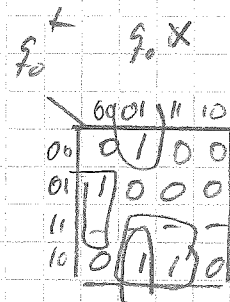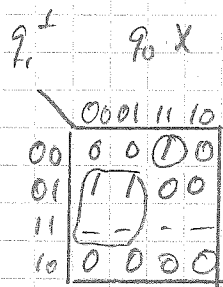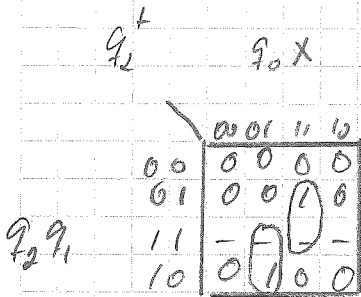


7+2 p

$$q_2^+ = q_2 \cdot \bar{q}_0 \cdot X + q_1 \cdot q_0 \cdot X$$

$$q_1^+ = q_1 \cdot \bar{q}_0 + \bar{q}_2 \cdot \bar{q}_1 \cdot q_0 \cdot X$$

$$q_0^+ = q_2 \cdot X + q_1 \cdot \bar{q}_0 \cdot \bar{X} + X$$

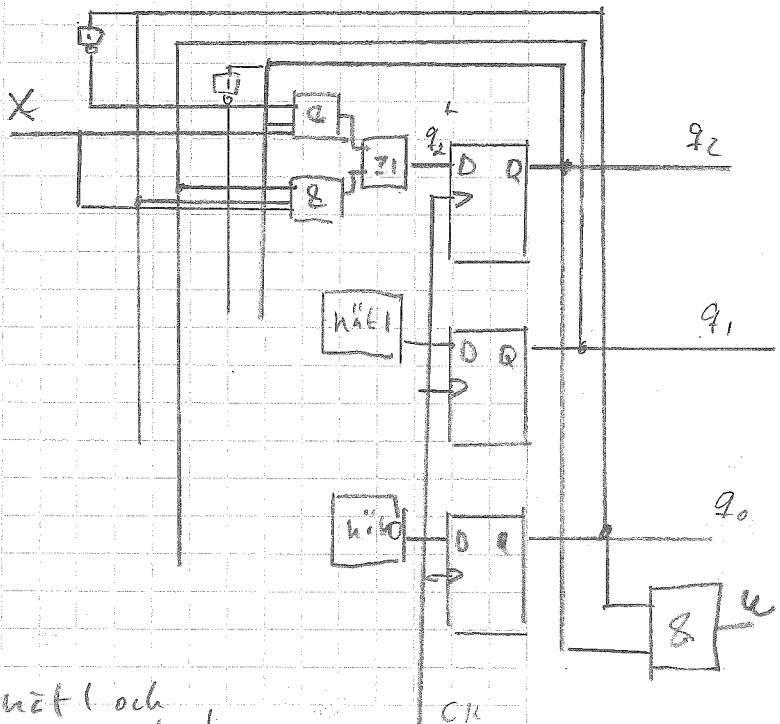
$$u = q_2 \cdot q_0 + \bar{q}_1 \cdot q_0 \cdot X$$



insignaler till nät 1 och nät 0 är q_2, q_1, q_0 och u .

7b)

blad 5.

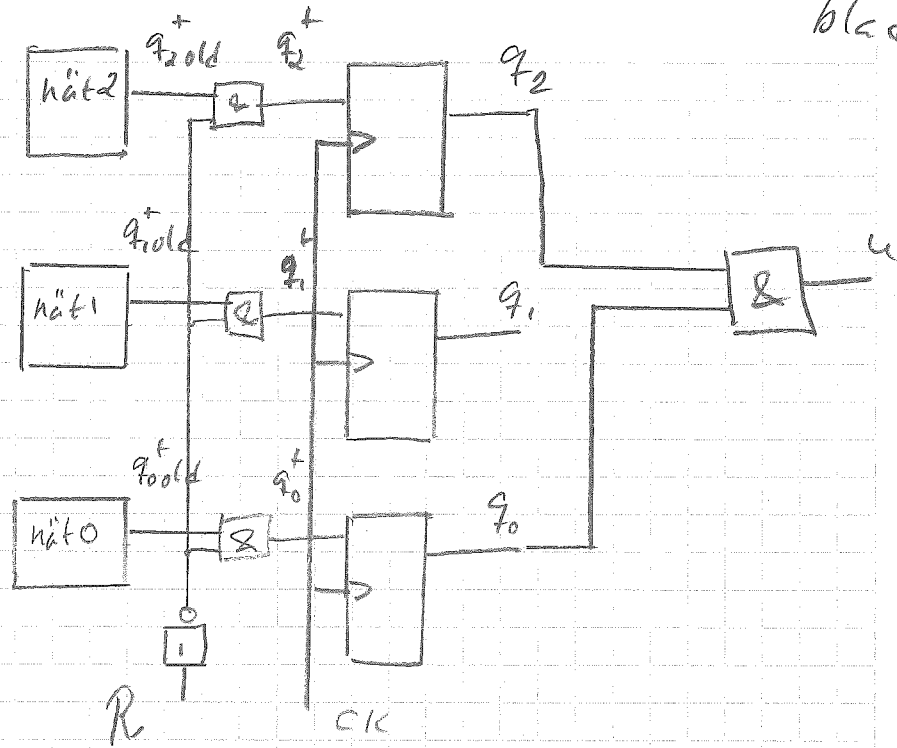

6)

ble 15

8P

