

Introduction to structured VLSI design

Design for Test (DfT) - Part 1

Erik Larsson
EIT, Lund University




Outline

- Electronics
- Manufacturing
- Test, diagnosis, and verification
- Test generation

Products with Electronics




Integrated Circuits (ICs)

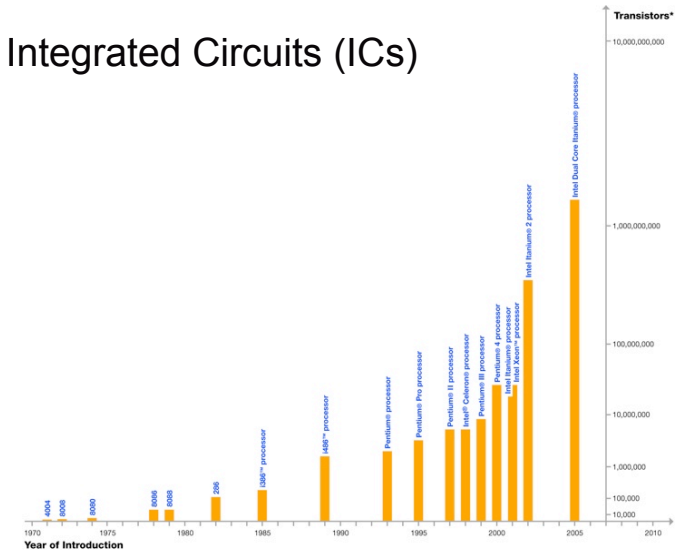

Integrated Circuits (ICs)


- Small Scale Integration (SSI), early 1960s
example, Philips TAA320 had two transistors
- Medium Scale Integration (MSI), late 1960s
example, Intel 4004 had 2300 transistors
- Large Scale Integration (LSI), mid-1970s
example, Intel 8008 had 4500 transistors
- Very-Large Scale Integration (VLSI), 1980s,
example, Intel 80286, 134000 transistors
- Ultra-Large Scale Integration (ULSI), now,
more than 1 million transistors
 - Wafer-scale integration (WSI)
 - System-on-a-chip
 - Three dimensional integrated circuits (3D-ICs)

Integrated Circuits (IC)

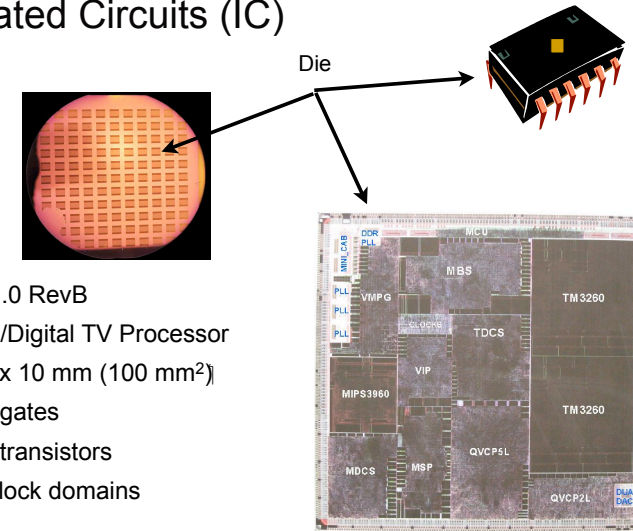


- Viper 2.0 RevB
- Analog/Digital TV Processor
- 10mm x 10 mm (100 mm²)
- ~10 M gates
- ~50 M transistors
- ~100 clock domains

Printed Circuit Board (PCB)

 


Multi-board System

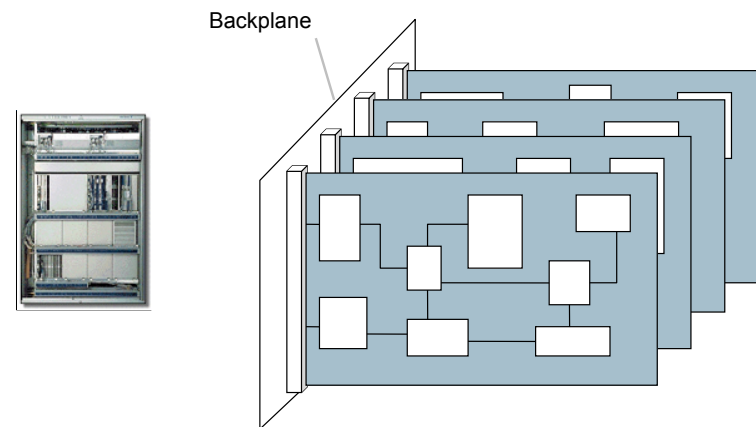


Outline

- Electronics
- Manufacturing
- Test, diagnosis, and verification
- Test generation


Making Electronic Products

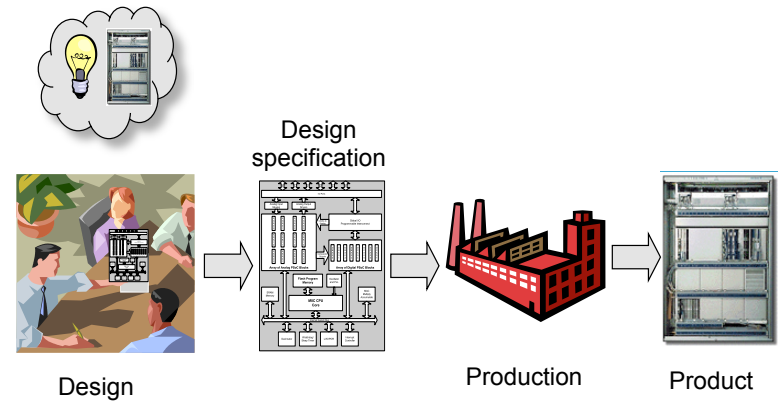



Electronics

 

AND-gate

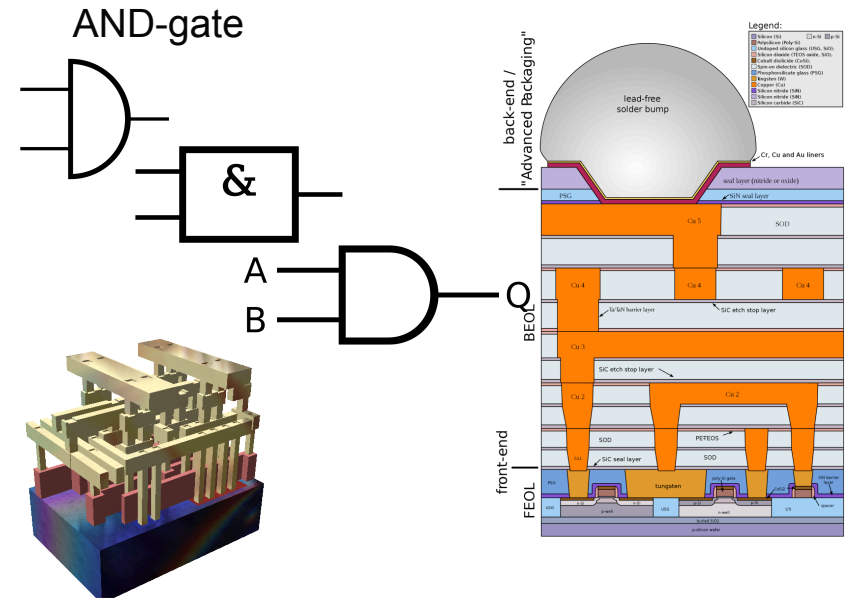


IC

  


- Viper 2.0 RevB
- Analog/Digital TV Processor
- 10mm x 10 mm (100 mm²)
- ~10 M gates
- ~50 M transistors
- ~100 clock domains

IC Manufacturing

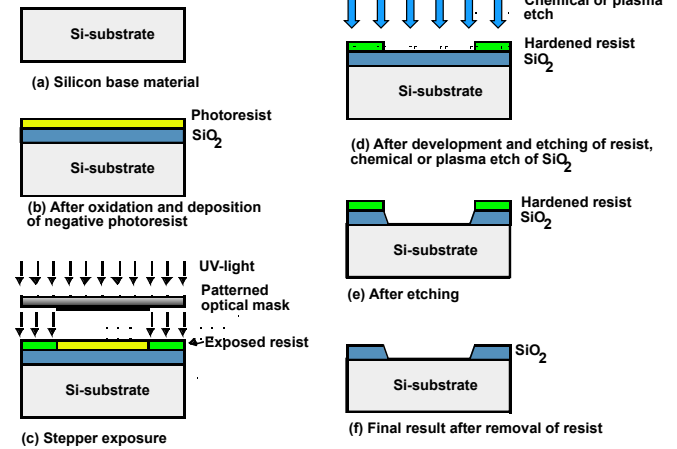



IC Manufacturing

 - The cost to set up a modern 45 nm process is \$200–500 million
- The purchase price of a photomask can range from \$1,000 to \$100,000 for a single mask.
- As many as 30 masks (of varying price) may be required to form a complete mask set.




Bonding Techniques


Wire Bonding

  


Flip-chip

 

Package-to-Board Interconnect

 

(a) Through-Hole Mounting

 



(b) Surface Mount

42


Outline

- Electronics
- Manufacturing
- Test, diagnosis, and verification
- Test generation



IC Defects

  

Salt

 

Seed

  

PCB Defects


Defect classes	Occurrence frequency (%)
Shorts	51
Opens	1
Missing components	6
Wrong components	13
Reversed components	6
Bent leads	8
Analog specifications	5
Digital logic	5
Performance (timing)	5

Ref.: J. Bateson, *In-Circuit Testing*, Van Nostrand Reinhold, 1985.

Fault Models

- Real defects too numerous and often not analyzable
- A fault model identifies targets for testing
- A fault model makes analysis possible
- Effectiveness measurable by experiments
- A defect manifests itself as a fault
- A fault is modeled by a fault model
- Example of fault models:
 - Stuck-at Fault, Bridging Fault, Shorts (Resistive shorts), Opens, Delay Faults, Transient Fault
- So far stuck-at fault model is the most used one:
- Motivations: Simple and covers quite well possible defects

Test

 

Stimulus: test vectors


Test pattern: test vector + expected test response (ordered n-tuple of binary values)
Produced test response is compared against expected test response

Design specification is correct. It means that tests can be generated from the design specification.

Verification, Test and Diagnosis

- Verification is to verify the correctness of the design. It is performed through simulation, hardware emulation, or formal methods. It is performed once prior to manufacturing. Responsible for quality of design.
- Test verifies the correctness of manufactured hardware. Test is a two-part process:
 - Test generation: software process executed once during design, and
 - Test application: electrical tests applied to hardware. Test application performed on every manufactured device. Responsible for quality of devices.
- Diagnosis: Identification of a specific fault that is present on DUT.

Diagnosis and Volume Production

 


Making Fault Free Electronic Products

Rule of ten: Finding a defect in one later step increases cost with a factor 10 compared to addressing the defect in current step.



Test Preparation

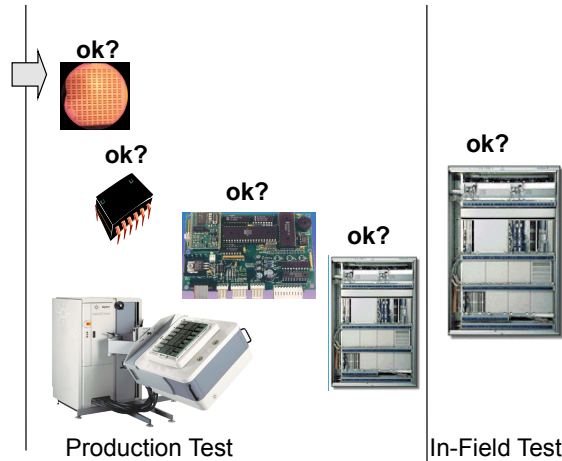

Types of Test

- Production
 - Wafer sort (or probe) Test of die on the wafer
 - Final test (package) Test of packaged chips
- Acceptance Test to demonstrate compliance with purchaser's requirements
- Sample Test some but not all parts
- Go/No-go Pass or fail test
- Characterization (performance) Test actual parameters
- Stress screening (burn-in) At high temperature to get wear-out
- Diagnostic (repair) Test to pinpoint defective part
- On-line Test while system is in operation

Types of Test

- Wafer sort - tests the logic of each die on the wafer



- Final test - tests the logic of each packaged IC



- Board test - tests interconnections (soldering errors)



Objective with Test

- Specify the test vector
- Determine correct response (expected response)
- Evaluate cost of test (# patterns related to cost)
- Evaluate quality of test

- Fault coverage = No of faults detected / No. faults modeled
- Yield = Number of good parts / Total number of tested parts

Tests

- Good IC that pass test -> OK
Bad IC that fail test -> OK
- Bad ICs that pass test -> test escape
Good ICs that fail test -> yield loss

		Outcome of test	
		Pass	Fail
IC	Good	OK	Yield loss
	Bad	Test esc.	OK

Automatic Test Equipment (ATE)


- Consists of:
 - Powerful computer
 - Powerful 32-bit Digital Signal Processor (DSP) for analog testing
 - Test Program (written in high-level language) running on the computer
 - Probe Head (actually touches the bare or packaged chip to perform fault detection experiments)
 - Probe Card or Membrane Probe (contains electronics to measure signals on chip pin or pad)



ATE






Automatic Test Equipment (ATE)

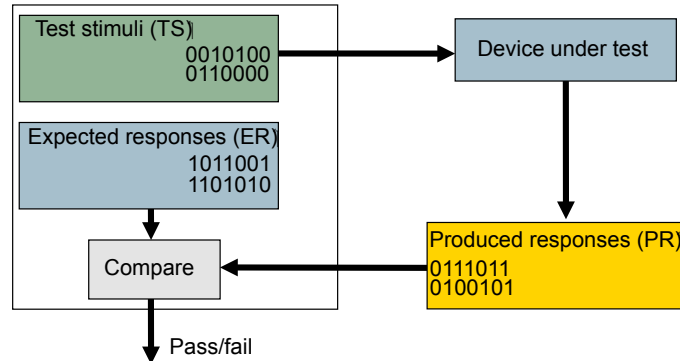

Outline

- Electronics
- Manufacturing
- Test, diagnosis, and verification
- Test generation


Test Generation

   

a	b	z
0	0	0
0	1	0
1	0	0
1	1	1

Test Generation

 
Example: Create test for output SA1 (Stuck-At 1)



Find test stimuli such that test responses are different in fault-free and faulty device

Stuck-at Fault (SAF) Model

 - A line is fixed to logic value 0 (stuck-at-0) or 1 (stuck-at-1)
- For the stuck-at fault model there are for a circuit with n lines 2*n possible faults




- Quality of a test is given by:
fault coverage = faults detected / total number of faults
- Example: 12 lines (24 faults) detect 15 faults: f.c.=15/24 (63%)

Single Stuck-at Fault


- Three properties define a single stuck-at fault
 - Only one line is faulty
 - The faulty line is permanently set to 0 or 1
 - The fault can be at an input or output of a gate
- Circuit has 12 fault sites (●) and 24 single stuck-at faults
- Find test for SA0 on h

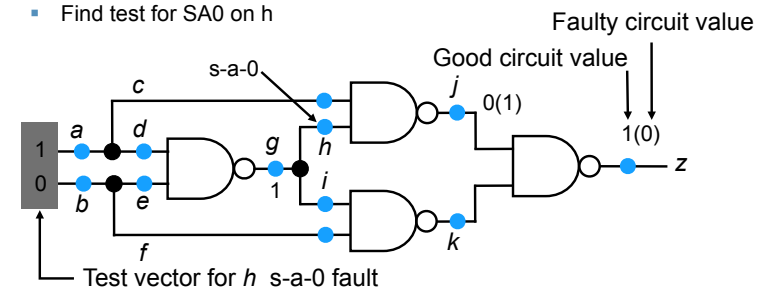To get test for SA0 on h:
1. fix e=1 -> good value on j to be 0 and defective value to be 1 (input reached - done)
2. fix k=0 -> set f=0 (input reached - done)




Single Stuck-at Fault

 - Let us generate a s-a-1 on the same line
- To get $c=0$, set $a=1$ and $b=1$
- To get fault effect on d (1/0), set $a=1$
- To get fault effect on z (0/1), set $e=0$
- To get $e=0$, set $b=1$ and $c=1$ (but $c=0$ - see above)



Stuck-at Faults

 

a	b	z
0	0	0
0	1	0
1	0	0
1	1	1


Minimize fault list through:
4 exhaustively generated vectors
but only 3 deterministic vectors
needed: Fault equivalence

Value fault free/faulty (v/v_f)


Stuck-at 0 on a: $a=1/0, b=1 \rightarrow z=1/0$	//vector (stimulus) 11
Stuck-at 0 on b: $b=1/0, a=1 \rightarrow z=1/0$	//vector (stimulus) 11
Stuck-at 0 on z: $b=1, a=1 \rightarrow z=1/0$	//vector (stimulus) 11
Stuck-at 1 on a: $a=0/1, b=1 \rightarrow z=0/1$	//vector (stimulus) 01
Stuck-at 1 on b: $b=0/1, a=1 \rightarrow z=0/1$	//vector (stimulus) 10
Stuck-at 1 on z: $a=0, b=x \rightarrow z=0/1$	//vector (stimulus) 0x or x0

Fault Equivalence

 
- Fault equivalence: Two faults f_1 and f_2 are equivalent if all tests that detect f_1 also detect f_2 .
- If faults f_1 and f_2 are equivalent then the corresponding faulty functions are identical.




Equivalence Rules

 

Equivalence Example

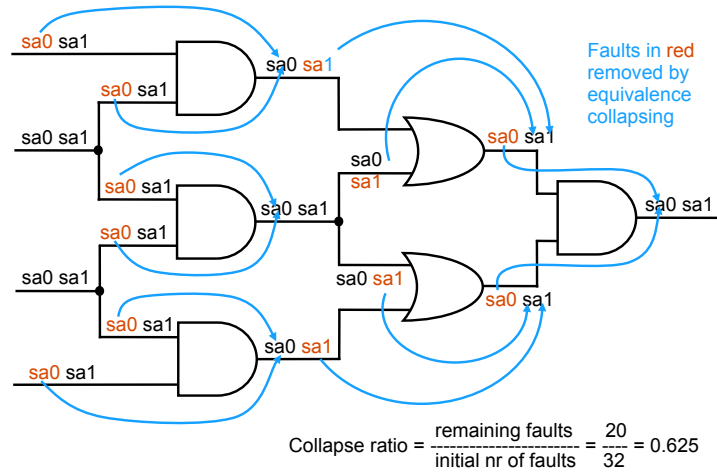


Redundant Faults

 

Cannot find a test for this fault.

Boolean Difference

 - Design (fault free): $z = a \text{ and } b$
- A stuck-at-1 fault on a , results in $z' = 1 \text{ and } b$.
- Make xor between z and z' to have different output in fault-free and faulty device.
- Hence, find a and b values such that: $z \text{ xor } z' = 1$.




Test Generation Schemes

- Exhaustive Test Generation
- Deterministic Test Generation
- Random Test Generation
- Pseudo-random Test Generation

Exhaustive Test Generation

 - Try all possible alternatives.
- For a 2-input design, 2^2 (4 vectors are needed).



a	b	z
0	0	0
0	1	0
1	0	0
1	1	1

- For a 30-input pin design, 2^{30} (1073741824 vectors are needed)
- 1 vectors per second and we know that there are $60 \cdot 60 \cdot 24 \cdot 365 = 31536000$ seconds in a year
- $2^{30} / 31536000 = 34$ years

Deterministic Test Generation

While fault coverage < desired limit {

Select an uncovered fault f

Generate test for the fault f

Evaluate fault coverage

}

- Needed functions to generate a test:
 - Excite (provoke) the fault
 - Sensitize (propagate) the results to primary outputs
 - Justify other values in the circuit
- ATPG:
 - D-algorithm
 - Path-Oriented Decision-Making (PODEM)
 - Fanout-oriented Test Generation (FAN)
 - Structure-oriented cost-reducing automatic test pattern generation (SOCRATES)


Deterministic Test Generation

A basic ATPG (automatic test-pattern generation) algorithm

- activate a fault. If stuck at 1, set the pin or node to '0' (the opposite value of the fault)
- work backward from the fault origin to the PIs (primary inputs) by recursively justifying signals at the output of logic cells
- work forward from the fault origin to a PO (primary output), setting inputs to gates on a sensitized path to their enabling values. Propagate the fault until the D-frontier reaches a PO.
- work backward from the PO to the PIs recursively justifying outputs to generate the sensitized path.

D-notation

 
- Five-valued algebra (0,1,X,D,D')
- $D=1/0$
- $D'=0/1$



- Stuck-at 0 on A ->
- Line A = D
- To propagate D (fault effect) to Z (check table) set B=1


OR	0	1	D	D'	X
0	0	1	D	D'	X
1	1	1	1	1	1
D	D	1	D	1	X
D'	D'	1	1	D'	X
X	X	1	X	X	X
AND	0	1	D	D'	X
0	0	0	0	0	0
1	0	1	D	D'	X
D	0	D	D	0	X
D'	0	D'	0	D'	X
X	0	X	X	X	X

D-Algorithm

 

- Initialize the circuit by placing X on each line
- For a SA0, $X=D$ and $A=B=0$ (for the selected fault)
- Propagate D through G2
- Select a sensitizing path (we select G3)
- To propagate through G3, we let $U=0$
- Propagate through G5
- Reached a primary output with D
- Justify values on H, Y, U, W. $H=0$ (ok). $F=0$? Conflict! Select $Y=0$

D-Algorithm

 


- $D=1/0$

1	Operation	Gate	A	B	X	Y	W	U	F	G	H	Z
2	Initialization		x	x	x	x	x	x	x	x	x	x
3	Provoke	G1	0	0	D	x	x	x	x	x	x	x
4	D-drive	G2	0	0	D	x	1	x	D	x	x	x
5	D-drive	G3	0	0	D	x	1	0	D	D'	x	x
6	D-drive	G5	0	0	D	x	1	0	D	D'	0	D'
7	Justification	$H=0$	0	0	D	x	1	0	!	D'	0	D'
8	Justification	$H=0$	0	0	D	0	1	0	D	D'	0	D'

Path-Oriented Decision-Making (PODEM)

- In the D-algorithm the search space is the entire circuit. Every internal gate can be a decision point.
- However, the end result for any ATPG algorithm are always the primary inputs.
- The number of primary inputs is in general much smaller than the number of gates
- The PODEM algorithm makes decisions only at primary inputs
- D-frontier is kept but the J-frontier is not needed

PODEM

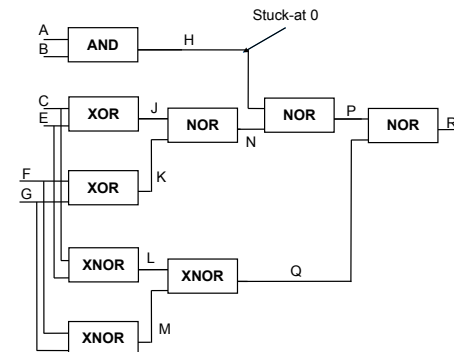

- Assign x to all inputs
- Assign $A=0$. Lead to $H=0$. Not good.
- Assign $A=1$. Good.
- Assign $B=0$. Lead to $H=0$. Not good.
- Assign $B=1$. Good
- Assign $C=0$.
- Assign $E=0$. Lead to $J=0$ and $L=1$
- As with C and E, assign $F=G=0$. Lead to $K=0$, $M=1$, $N=0$, and $Q=1$
- We can propagate D on P, and then D' on R

Hence: 110000 is the test stimulus for a stuck-at 0 on line H

Fanout-oriented Test Generation (FAN)

Fujiwara H. and Shimono T., On the acceleration of test generation algorithms, IEEE Transactions on Computers, Vol. C-31, No. 6, pages 555-560, 1983

Two major extensions to PODEM

- Backtracking may stop at internal lines
- Multiple backtrace-procedures attempts to simultaneously satisfy a set of objectives

Test generation time is reduced.

Structure-oriented Cost-reducing Automatic Test Pattern Generation (SOCRATES)

- Schultz, M. H, et al. SOCRATES: a highly efficient automatic test pattern generation system, IEEE Transactions on Computer-Aided Design, Vol. 7, No. 1, pages 126-137, 1988.
- Uses several heuristics to reduce test generation time and makes use of testability analysis to guidance.

Testability Analysis

- Objective:
 - Guide test generation algorithm
 - Predict hard to test areas in a circuit
- Example: Sandia Controllability/Observability Analysis Program (SCOAP)
 - Controllability: Effort to control a value at a line
 - CC0 - combinational 0-controllability
 - CC1 - combinational 1-controllability
 - SC0 - sequential 0-controllability
 - SC1 - sequential 1-controllability
 - Observability: Effort to observe a value
 - CO - observability controllability
 - SO - sequential observability

Fault Simulation

Problem and Motivation

Given

- A circuit
- A sequence of test vectors
- A fault model

Determine

- Fault coverage - fraction (or percentage) of modeled faults detected by test vectors
- Set of undetected faults


Motivation

- Determine test quality and in turn product quality
- Find undetected fault targets to improve tests

Fault Simulation

- Fault simulation consists of a fault free and a faulty circuit simulation.
- First, a fault free simulation takes place to find the fault free output responses for all patterns.
- Second, a series of simulations take place where. For each fault, fault injection is performed, the circuit is modified to become faulty. Then, the faulty circuit is simulated to find the faulty responses.

Pattern	Input			Internal			Output		
	A	B	C	E	F	H	K _{good}	K _{SA1_A}	K _{SA0_F}
P1	0	1	0	1	0	0	1	0	1
P2	0	0	1	1	0	0	1	0	1
P3	1	0	0	0	1	0	0	0	1

 

Fault Table - Analysis

- Fault simulator may provide fault table (fault dictionary)

Fault								
Pattern	1	2	3	4	5	6	7	8
1	x		x			x		
2		x	x	x				
3			x		x		x	
4			x				x	x

Test Set Compaction

- ATPG generates too many vectors; faults are covered by several vectors
- Test set compaction tries to reduce number of test vectors without compromising test quality
- Static test set compaction tries to remove vectors after the use of ATPG
- Dynamic test tries to remove vectors during ATPG


	f ₁	f ₂	f ₃	f ₄	f ₅	f ₆	f ₇
v ₁	x		x		x		
v ₂						x	x
v ₃	x				x		x
v ₄		x	x	x	x		

Commercial ATPG Tools

- Commercial ATPG tools are often for combinational circuits
- Commercial tools usually make use of a random test generation for 60-80% of the faults (easy to detect) and deterministic test generation for the remaining part (hard to detect)
- Examples of commercial ATPG tools:
 - Encounter Test - Cadence
 - TetraMax - Synopsis
 - FastScan, FlexTest - Mentor Graphics


Test Generation for Sequential Circuits

 - Most real circuits are sequential
- A major problem is that the output depends not only on inputs but also on current state



Test Generation for Sequential Circuits

 - Keep track on time frames (unroll design)



Summery

- Electronics
- Manufacturing
- Test, diagnosis, and verification
- Cost, defects, fault models, and quality of test
- Test generation Test Generation
 - Exhaustive Test Generation
 - Deterministic Test Generation
 - Random Test Generation
 - (Pseudo-random Test Generation)
- Fault Simulation and test set compaction
- On next lecture we will answer the question: How is it possible to use combinational ATPG when real circuits are sequential.

Introduction to structured VLSI design Design for Test (DfT) - Part 1

Erik Larsson
EIT, Lund University

