



LUND  
UNIVERSITY

# EITF35: Introduction to Structured VLSI Design

Part 2.1.1: Combinational circuit

Liang Liu  
liang.liu@eit.lth.se




# Why Called “Combinational” Circuits?

## □ Combination

- In mathematics a combination is a way of selecting several things out of a larger group
- Select two fruits out of APPLE, PEAR, and ORANGE
- In a combination the **order** of elements is **irrelevant**
 
## □ Combinational Circuits

- **time-independent logic**, where the output is a pure function of the present input only.
- the **order** of inputs doesn't matter for the outputs.




# Overview

- Fixed-Point Representation
- Add/Subtract
- Multiplication
- Timing & Techniques to Reduce Delay



# 'Digital'- quantization

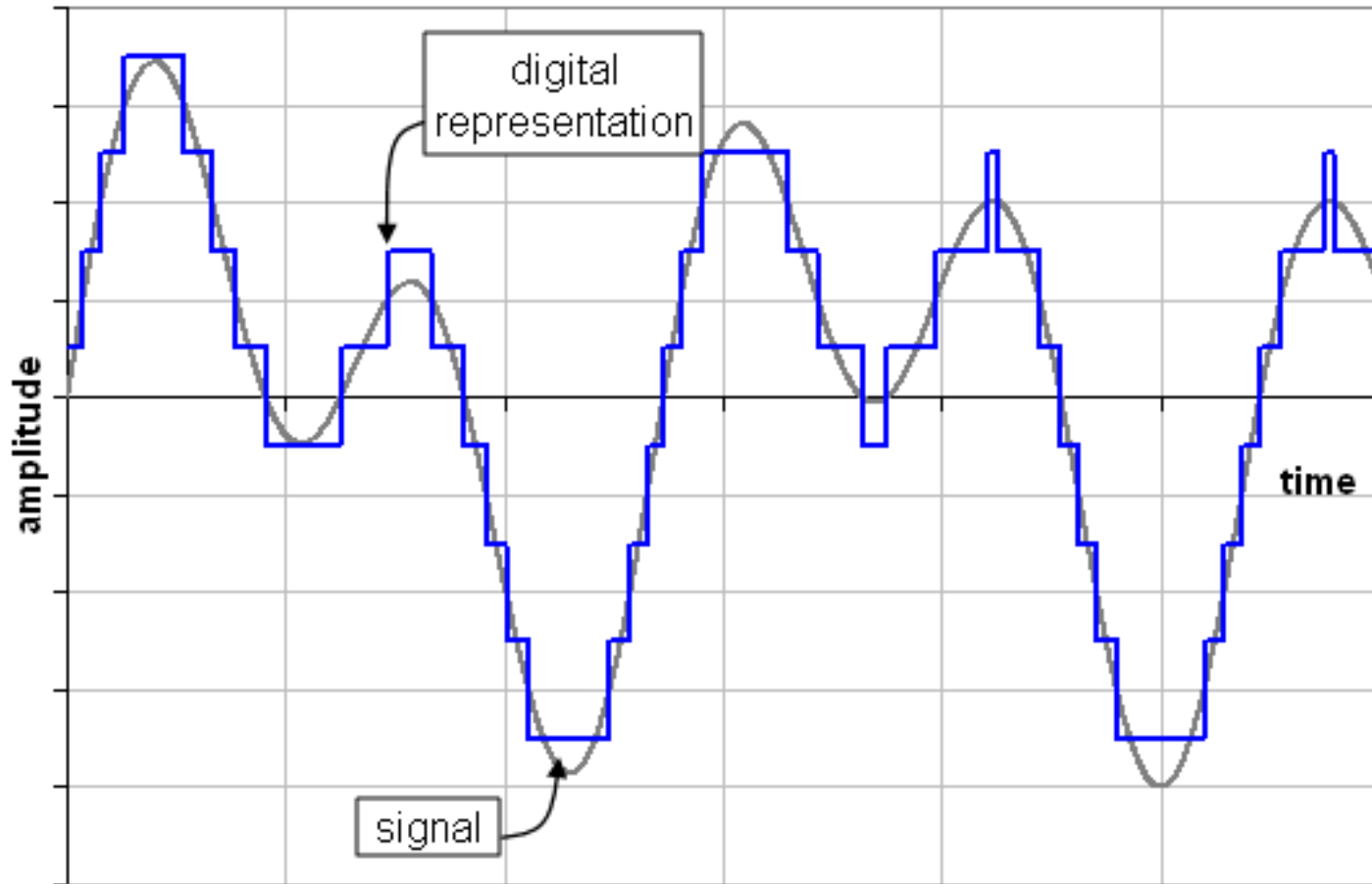

# Data Representation

## □ Unsigned

- Uses the two numbers from 0 to 1
- Every column represents a power of 2
- Unsigned integer:

$$\sum_{i=0}^{n-1} \text{bit}_i 2^i$$

## □ Signed (Two's complement)

- $N$ -bit number is defined as the complement with respect to  $2^N$ , in other words the result of **subtracting the number from  $2^N$**
- 2's complement of a binary number involves inverting all bits and **adding 1**

$$\text{bit}_{n-1} (-2^{n-1}) + \sum_{i=0}^{n-2} \text{bit}_i 2^i$$

$$\underline{11110100}_2 = -12_{10}$$

Sign bit

2's complement



# 8-bit Signed/Unsigned Integers

Signed overflow ↑	-128	1000 0000	
	-127	1000 0001	
	...	...	
		1111 1100	
		1111 1101	
		1111 1110	
		1111 1111	
		0000 0000	0
		0000 0001	1
		0000 0010	2
	0000 0011	3	
	...	...	
Signed integers	0	0000 0000	0
	1	0000 0001	1
	2	0000 0010	2
	3	0000 0011	3
	...	...	...
	126	0111 1110	126
	127	0111 1111	127
		1000 0000	128
		1000 0001	129
		...	...
		1111 1110	254
		1111 1111	255
Signed overflow ↓			Unsigned overflow ↓

MSB defines sign



# General Fixed-Point Representation

## □ $Qm.n$ notation


- $m$  bits for integer portion,  $n$  bits for fractional portion
- Total number of bits  $N = m + n + 1$ , for signed numbers

## □ Example: 16-bit number (N=16) and Q2.13 format

- 2 bits for integer portion, 13 bits for fractional portion, 1 signed bit (MSB)
 
## □ Special cases:

- 16-bit integer number (N=16)  $\Rightarrow$  Q15.0 format
- 16-bit fractional number (N = 16)  $\Rightarrow$  Q0.15 format





# Finite Word-Length Effect

## □ Overflow

- Saturation

## □ Quantization error

- Round
- Truncation

  

$$\mathit{round}(0.51)=1$$

$$\mathit{floor}(0.51)=0$$

$$\mathit{ceil}(0.49)=1$$





# Exercise (1 min)

- 1.234, only 3 bits for the fraction part
- Do Round Truncation
- Do Floor Truncation

$$\mathit{round}(1.234 * 2^3) / 2^3 = 1.25$$

$$\mathit{floor}(1.234 * 2^3) / 2^3 = 1.125$$




# Fixed-Point Design

## □ Digital signal processing algorithms

- Often developed in floating point
- Later mapped into **fixed point** for digital hardware realization
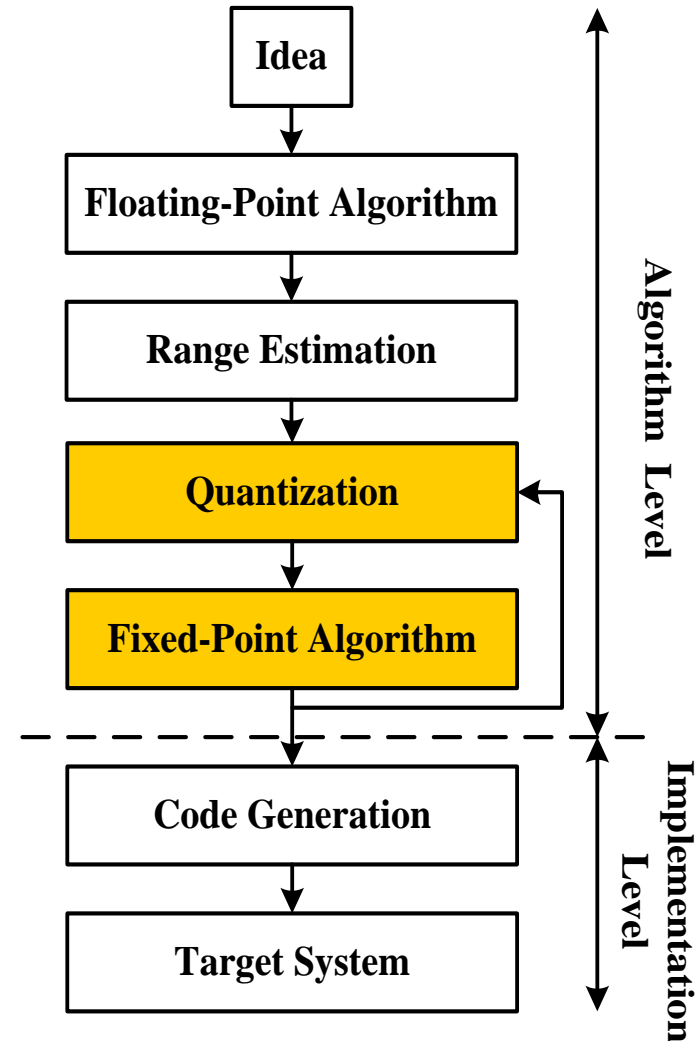
## □ Fixed-point digital hardware

- Lower area
- Lower power
- Higher quantization error



# Design Trade-off

Implement the best HW realization. **Best??**



Flexibility  
Complexity




- Processors
- FPGAs



Low power  
Low cost  
Flexibility



- Processors
- Dedicated HW

 

Lower power  
Lower cost



- Dedicated HW
- Processors



# Design Trade-off

Implement the best HW realization. **Best??**

Different applications, different demands...  
Thus, "*just good enough*" is the best in engineering.


Try to find a balance between effort and cost!



# Optimum Word-Length

□ Range Analysis

□ Fixed-point Simulation

 

**Will learn more in DSP-Design course**



# QoS requirements of different applications



High-Quality  
Voice



$$\text{BER} \leq 2 \times 10^{-3}$$



Video  
Program



$$\text{BER} \leq 2 \times 10^{-4}$$



File  
Transfer



$$\text{BER} < 10^{-6}$$




# Overview

- Fixed-Point Representation
- **Add/Subtract**
- Multiplication
- Timing & Techniques to Reduce Delay



# Add/Subtract

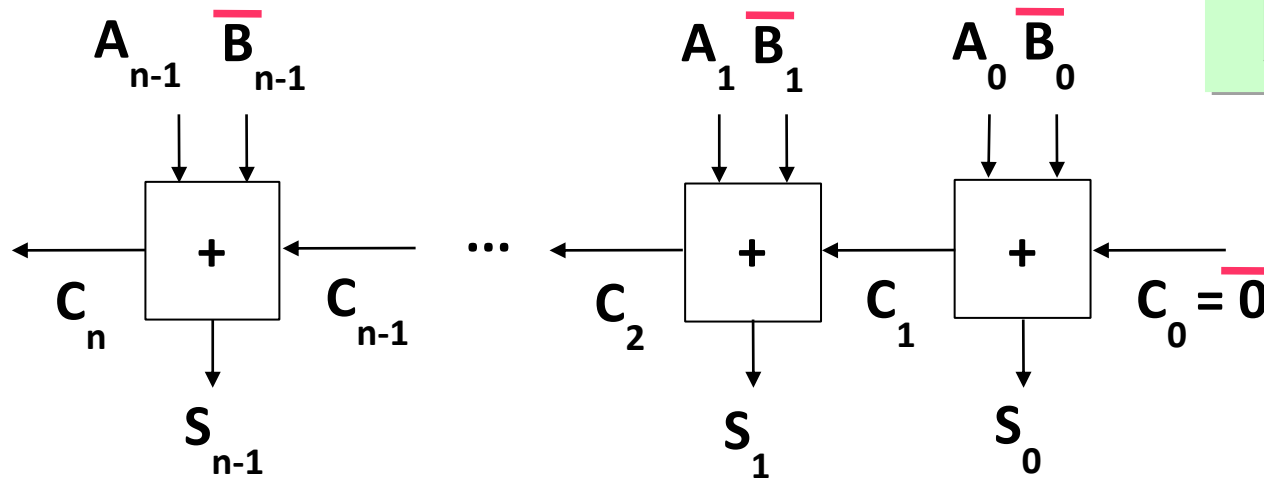

□ The HW for sum/difference (S) does not care about signed/unsigned

□ Unsigned overflow = Carry-out & add

□ Signed overflow =  $C_n \oplus C_{n-1}$

□ True sign =  $S_{n-1} \oplus \text{signed overflow} = (A_{n-1} \oplus B_{n-1} \oplus C_{n-1}) \oplus (C_n \oplus C_{n-1}) = A_{n-1} \oplus B_{n-1} \oplus C_n$





# Unsigned Overflow Examples

## 4-Bit unsigned addition

10+6 = 16, outside [0..15]

$$\begin{array}{r} 1010 \\ +0110 \\ \hline C_4=1 \quad 0000 \end{array}$$

$C_n = C_4 = 1$  & add  $\Leftrightarrow$  Unsigned overflow

Carry-out & add  $\Leftrightarrow$  Unsigned overflow



# Signed Overflow Example

## 4-Bit signed addition

6+7 = 13, outside [-8..7]

$$\begin{array}{r} 0110 \\ +0111 \\ \hline 1101 \end{array}$$

$C_4 = 0$   
 $C_3 = 1$

$$C_n \oplus C_{n-1} = C_4 \oplus C_3 = 0 \oplus 1 = 1 \Leftrightarrow$$

Carry-outs different  $\Leftrightarrow$  **Signed overflow**


$$S_{n-1} \oplus \text{signed overflow} =$$
$$A_{n-1} \oplus B_{n-1} \oplus C_n = A_3 \oplus B_3 \oplus C_4 = 0 \oplus 0 \oplus 0 = 0 \Leftrightarrow \text{True sign} = \text{Positive/zero}$$




# Overflow in Hardware

## Hardware does not take care of the overflow for you

- Unsigned

 

- Signed

 

# Two's Complement Signed Extension

□ To add two numbers, we must represent them with the **same number of bits**: **0100+11100**

- If we just pad with zeroes on the left:

4-bit

**0100** (4)

**1100** (-4)

8-bit

**00000100** (still 4)

**00001100** (12, not -4)

- Instead, replicate the MS bit -- **the sign bit**:

4-bit

**0100** (4)

**1100** (-4)

8-bit

**00000100** (still 4)

**11111100** (still -4)

□ **Extend one sign-bit to protect overflow**



# Decimal Mark in Hardware

- Matlab aligns the decimal mark automatically

$$1.32+100.2343= 101.5543$$

- Hardware **does NOT**

- Decimal mark is just a concept

$$01.100+001.01=?$$

$$10001$$

- You need to align the decimal mark manually

$$001.100+001.010=010.110$$



# Overview

- Fixed-Point Representation
- Add/Subtract
- **Multiplication**
- Timing & Techniques to Reduce Delay




# Array Multiplier (unsigned)

```

1011 * 1110
-----
0000 (*0 = zero)
+1011. (*1 = copy)
+1011.. (*1 = copy)
+1011... (*1 = copy)
-----
10011010
    
```
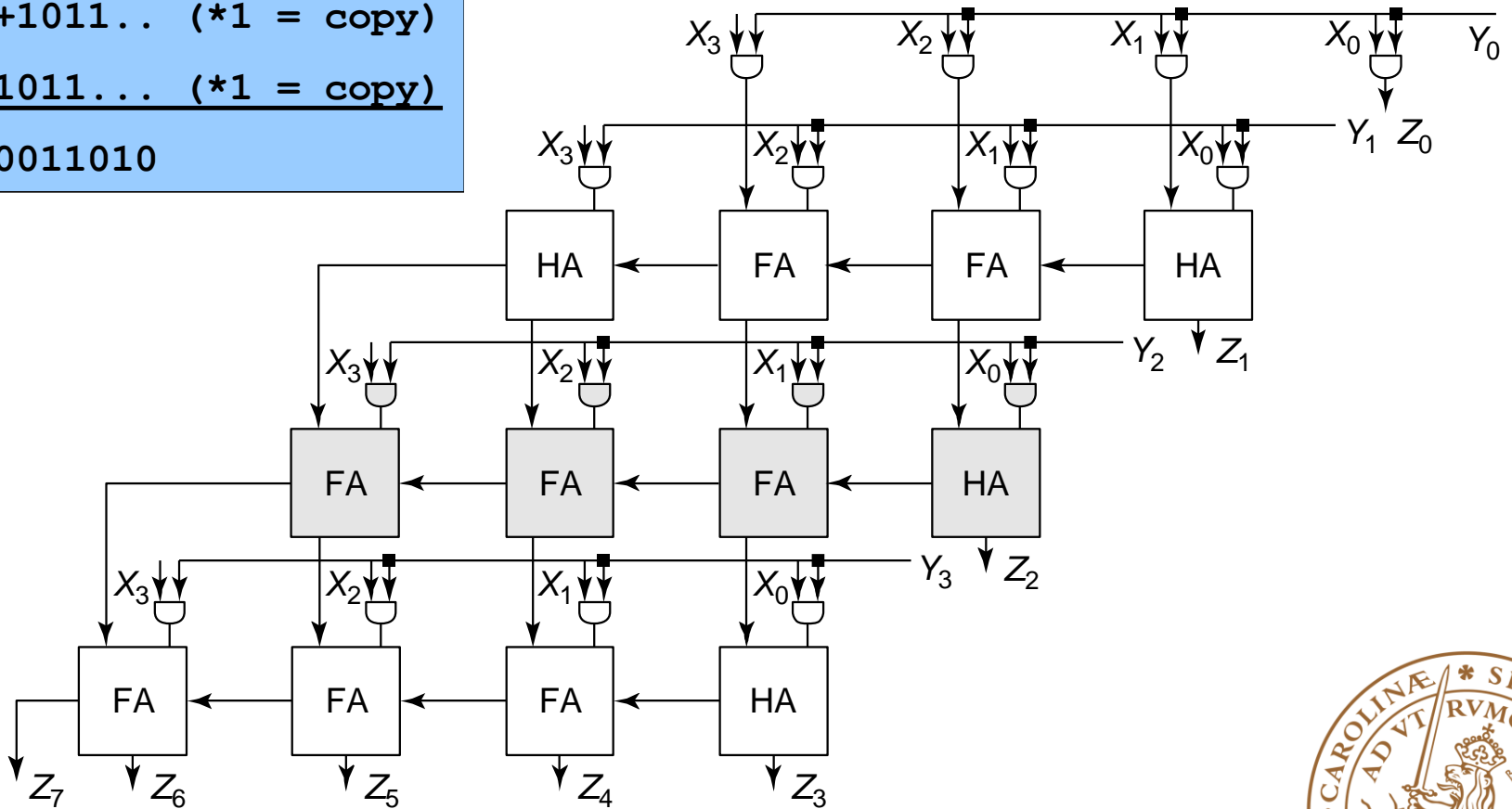
## Direct Mapping

- Horizontal** : partial product using AND
- Vertical** : shift-add of partial product



# Don't Forget ... Signed Multiplication

$$\begin{array}{r} 1\ 0\ 1\ 1 \\ \underline{0\ 0\ 1\ 1} \end{array} \begin{array}{l} -5x \\ +3 \end{array}$$

?

$$\underline{1\ 1\ 1\ 1\ 0\ 0\ 0\ 1} \quad -15$$









# Signed Multiplication


## □ Or directly perform signed multiplication:

- Multiplier & Multiplicand: positive or negative
- Sign extend the partial products when adding up
- Subtract instead of adding last partial product

Ex:

- 5		1011	multiplicand
x - 3	x	1101	multiplier
15		00000	partial product
		11011	shifted multiplicand
	→	111011	partial product
		00000	shifted multiplicand
	→	1111011	partial product
		11011	shifted multiplicand
	→	11100111	partial product
		00101	shifted and negated multiplicand
		00001111	product

Added bit using  
sign extension


 


# Multiplier in Xilinx FPGA
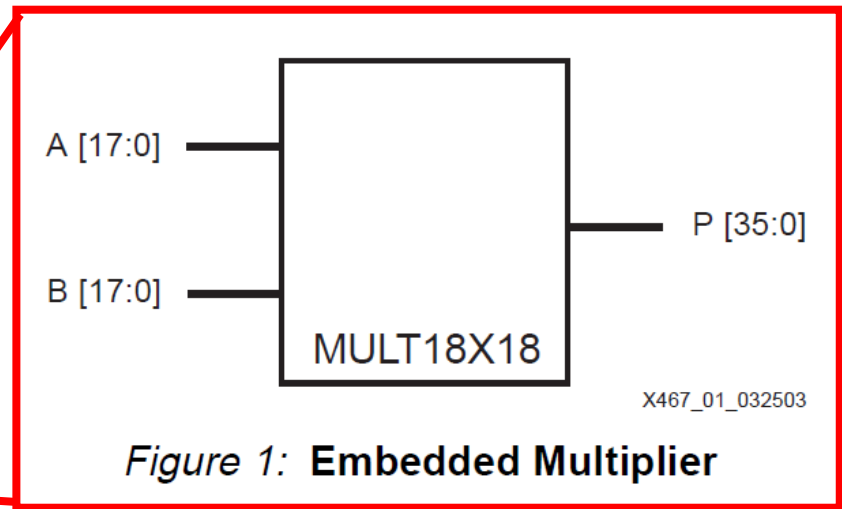 
## Embedded Multipliers

- 18-bit embedded multipliers (signed and unsigned)
- Using Embedded Multipliers in Spartan-3 FPGAs

[http://www.xilinx.com/support/documentation/application\\_notes/xapp467.pdf](http://www.xilinx.com/support/documentation/application_notes/xapp467.pdf)




# Multiplier in Xilinx FPGA
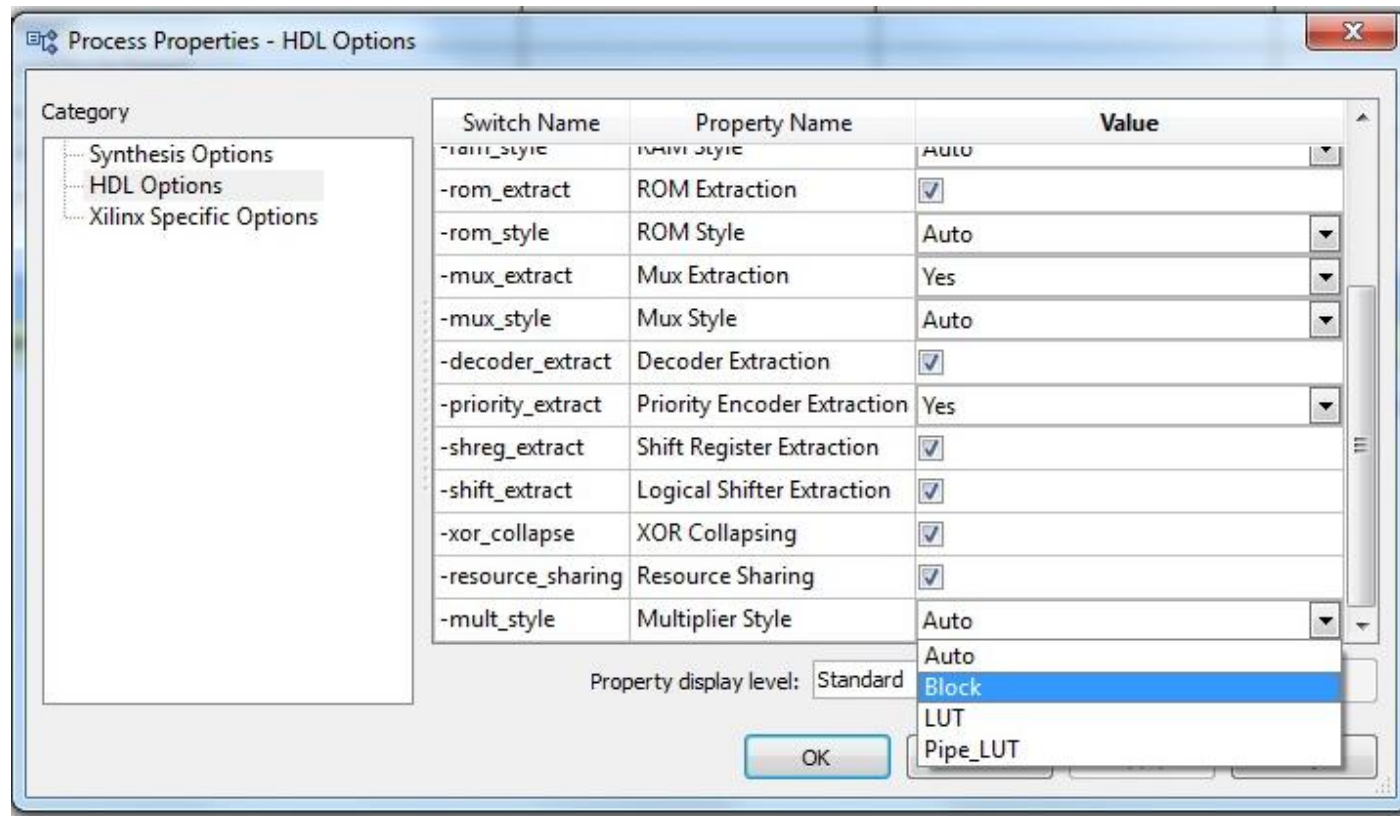
## □ Embedded Multipliers

- 18-bit embedded multipliers (signed and unsigned)
- Using Embedded Multipliers in Spartan-3 FPGAs

[http://www.xilinx.com/support/documentation/application\\_notes/xapp467.pdf](http://www.xilinx.com/support/documentation/application_notes/xapp467.pdf)




# Multiplication by a Constant
 
## Examples:

- **Twiddle factor** in FFTs
- **Constellation points** in wireless communication

$$y_j = \sum_{k=0}^{n-1} e^{-\frac{2\pi i}{n}jk} x_k$$



□ The synthesis engine may be not smart enough to do some evident optimizations.

□ As a designer you need to assure that multiplications with a small constant is accomplished by a number of **shifts & adds**

Some numerical examples:

\*2 (\*10<sub>2</sub>): multiplicand << 1

\*3 (\*11<sub>2</sub>): multiplicand << 1 + multiplicand

\*5 (\*101<sub>2</sub>): multiplicand << 2 + multiplicand

\*255 (\*11111111<sub>2</sub>): ?

**multiplicand << 8 – multiplicand**




# Overview

- Fixed-Point Representation
- Add/Subtract
- Multiplication
- **Timing & Techniques to Reduce Delay**




# Combinational Circuit Timing

□ Path delay = cell delay + net delay

 

 
$$\text{Path Delay} = 0.5 + 0.4 + 0.62 + 0.21 + 1.28 + 0.12 + 0.82 = 3.95 \text{ ns}$$






# Combinational Circuit Timing

□ Path delay = cell delay + net delay

 

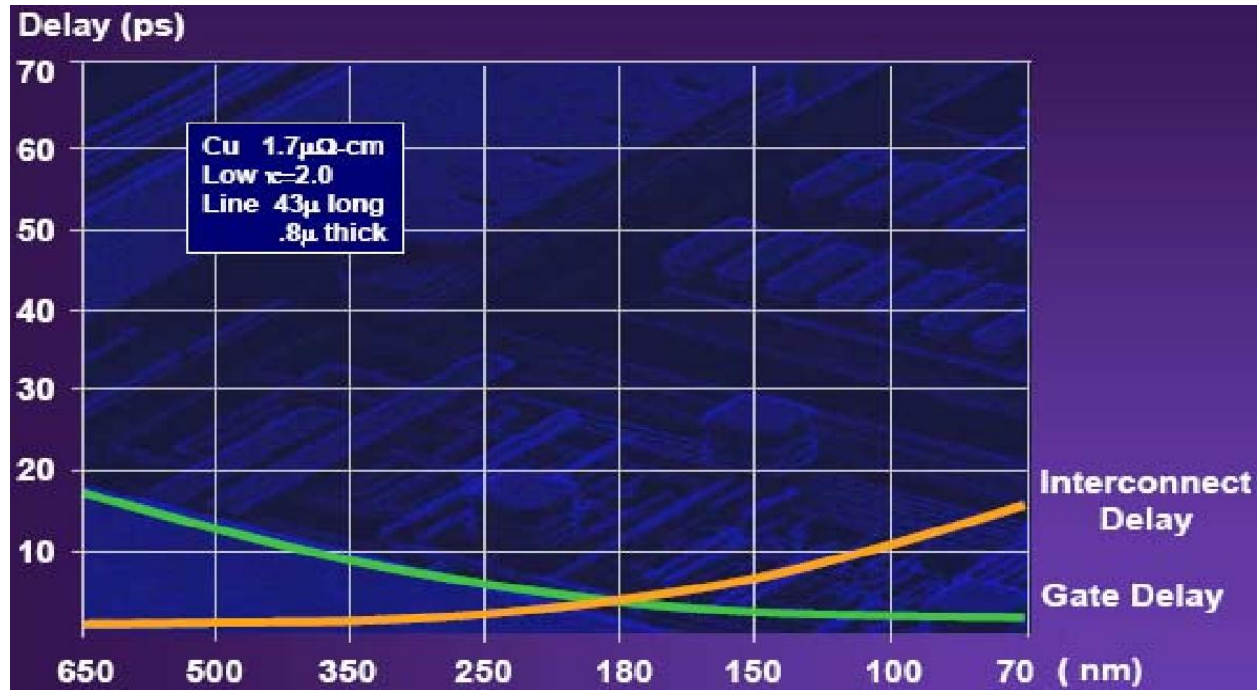
$$\text{Path Delay} = 0.5 + 0.4 + 0.62 + 0.21 + 1.28 + 0.12 + 0.82 = 3.95 \text{ ns}$$



# Combinational Circuit Timing

□ Path delay = cell delay + net delay

 

$$\text{Path Delay} = 0.5 + 0.4 + 0.62 + 0.21 + 1.28 + 0.12 + 0.82 = 3.95 \text{ ns}$$


□ How to reduce processing delay

- Reduce cell delay? Standard-cell library
- Reduce net delay? Place & Route
- Or we can change the architecture


 
# Example1: Higher-Level Adder Chain

□ Calculate:  $B = A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8$




Cascaded-Chain


 
# Higher-Level

$$B = [(A_1 + A_2) + (A_3 + A_4)] + [(A_5 + A_6) + (A_7 + A_8)]$$



Tree



# Cascade vs. Tree

## □ Comparison of n-input adder

- Cascading chain:
  - Area:  $(n-1)$  full adder
  - Delay:  $(n-1)$
  - Flexibility: easy to modify (scale)
- Tree:
  - Area:  $(n-1)$  full adder
  - Delay:  $\log_2 n$
  - Flexibility: not so easy to modify
- Software should be able to do the conversion automatically



# Thanks!

