



LUND
UNIVERSITY

EITF35: Introduction to Structured VLSI Design

Lab assignment 3 Arithmetic Logic Unit (ALU)

Chenxin Zhang

Chenxin.Zhang@eit.lth.se



ALU is the heart of any computing



- Supercomputer (TOP500)
- Unveiled in 2007
- 250K processors
- Optical network
- petaFLOPS (10^{15})
- Low power

Every processor needs at least one ALU!




This assignment



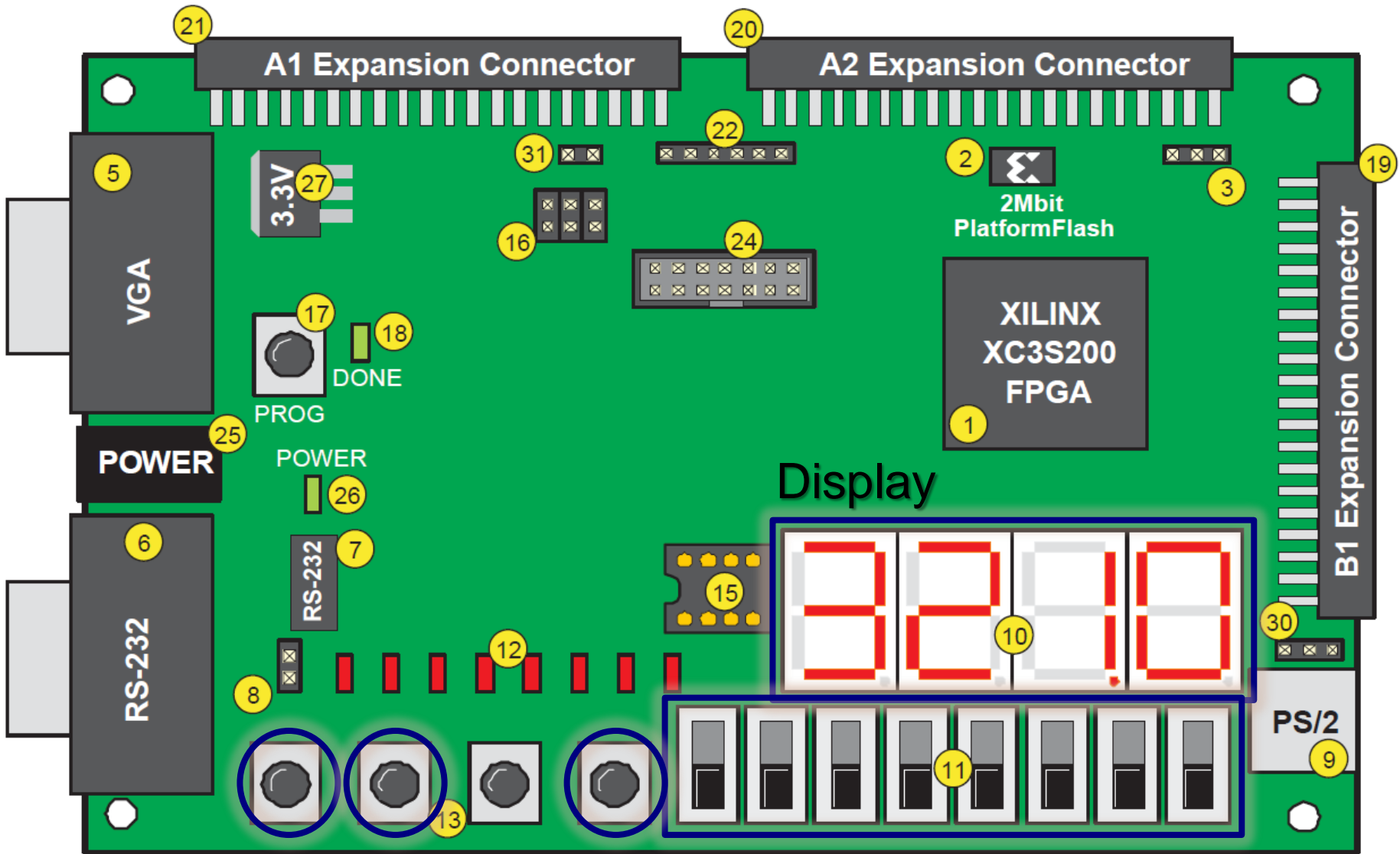- 8-bit calculator
- Sign/unsigned
- +/- and mod-3
- Overflow detection
- Switch inputs
- 7-segment display






Reset Sign

Enter

Numeric keypad



ALU structure

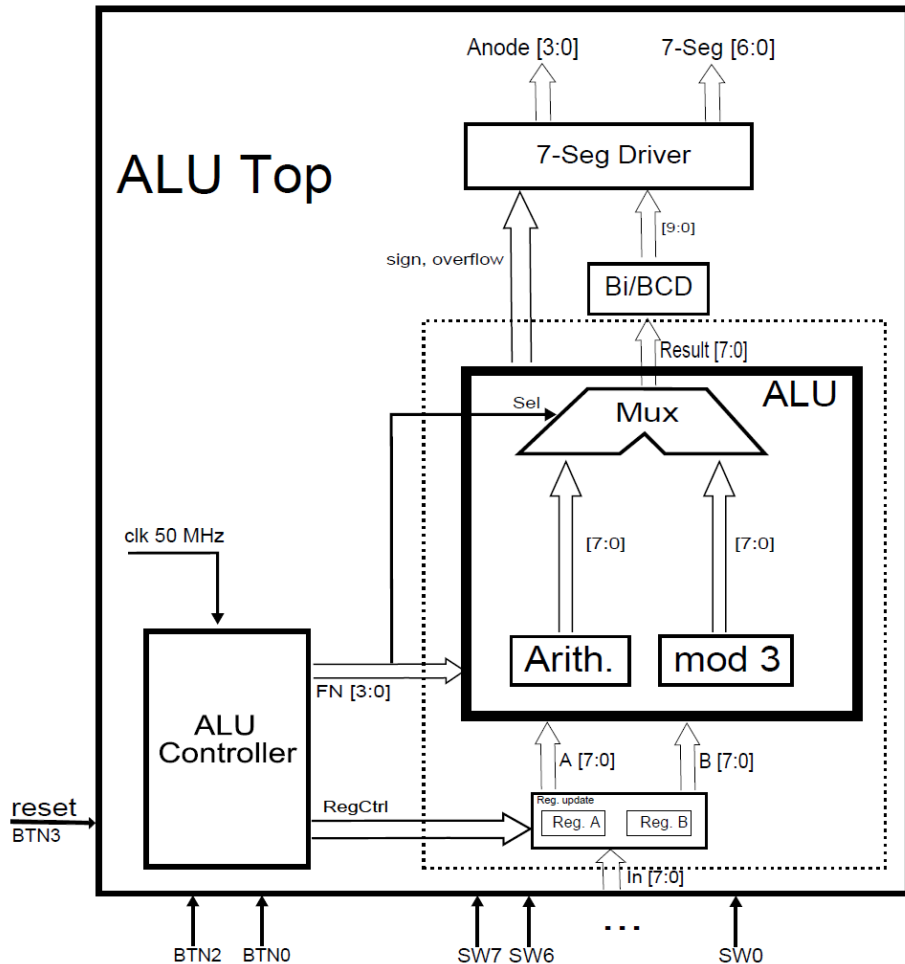

- ALU
- Operand registers
- ALU controller
- Bi/BCD (Binary-Coded-Decimal) converter
- 7-segment driver (Lab 2)



Lab preparation

- Thoroughly read through the lab manual to understand all the detailed requirements.
- Draw a reasonably detailed FSM for ALU controller.
- Search on or come up with **HARDWARE-FRIENDLY** algorithms for:
 - Modulo-3 operation
 - Bi/BCD conversion



Modulo operation

- Definition: $x \bmod n = x - n \cdot \text{floor}(x/n)$
- We only look at the case of **n = 3** in this assignment.
- e.g., $7 \bmod 3 = 7 - 3 \cdot \text{floor}(7/3) = 7 - 3 \cdot \text{floor}(2.33)$
 $= 7 - 3 \cdot 2 = 7 - 6 = 1$
- **IMPORTANT** to find a good algorithm to compute mod-3!
- **Be careful** with the signed modulo operations!



Some comments

- **Start early!**
- **Think before coding!**
- Thorough tests & **extensibility!**
- **Balanced workload!** Both group members should be able to do small changes individually during approval time.

