 


Introduction to structured VLSI design

Design for Test (DfT) - Part 2

Erik Larsson


EIT, Lund University



Outline

- Electronics
- Manufacturing
- Test, diagnosis, and verification
- Test generation
- Test points and Scan
- Test Compression
- Built-In Self-Test (BIST)
- Systems-on-chip test
- Boundary scan (IEEE 1149.1)

Test

 


Stimulus: test vectors

Test pattern: test vector + expected test response (ordered n-tuple of binary values)
Produced test response is compared against expected test response

Test application




Automatic Test Equipment (ATE)

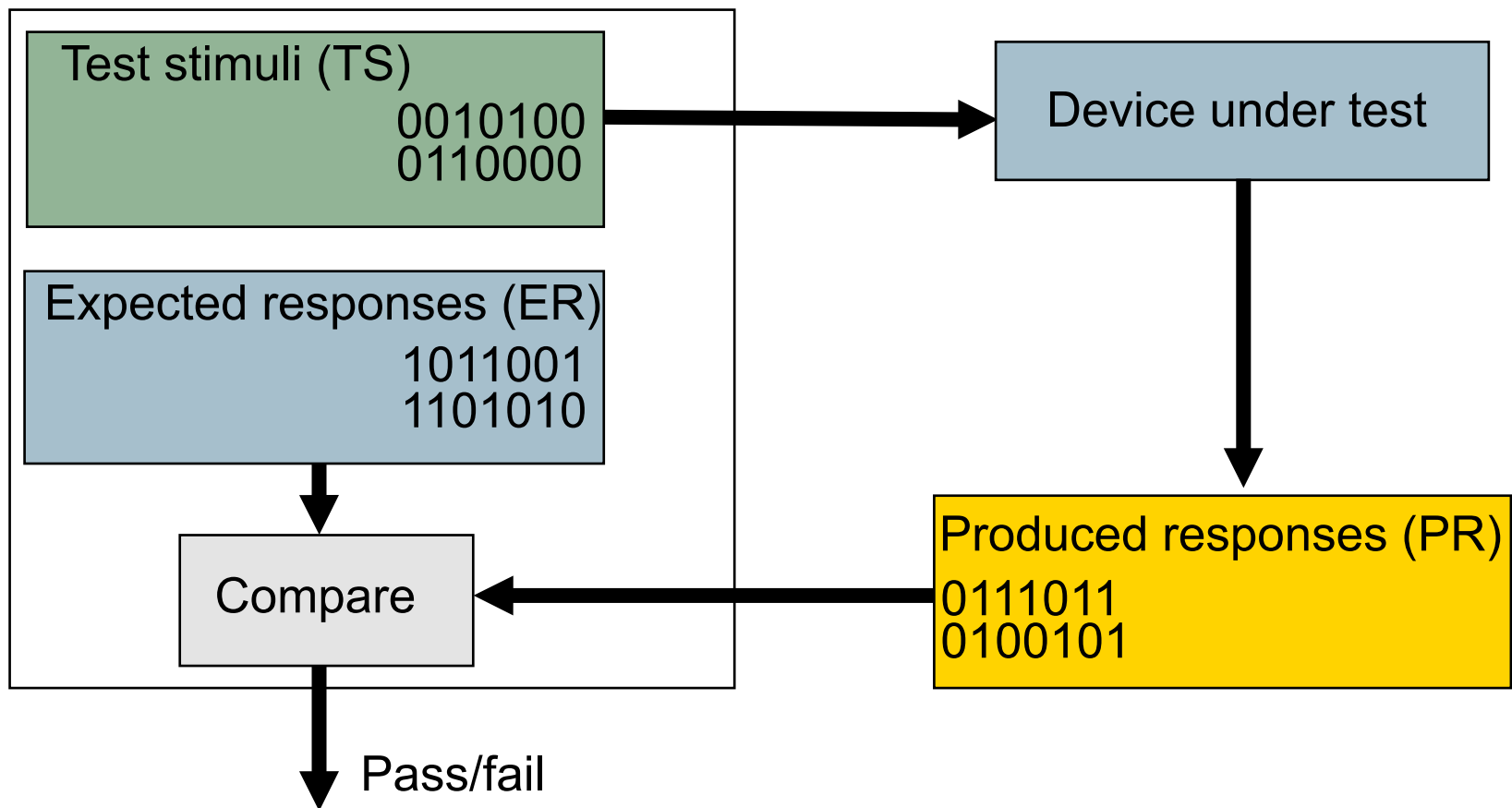

Stuck-at Fault (SAF) Model

 - A line is fixed to logic value 0 (stuck-at-0) or 1 (stuck-at-1)
- For the stuck-at fault model there are for a circuit with n lines 2^n possible faults




- Quality of a test is given by:
fault coverage = faults detected / total number of faults
- Example: 12 lines (24 faults) detect 15 faults: f.c.=15/24 (63%)

Commercial ATPG Tools

- Commercial ATPG tools are often for combinational circuits
- Commercial tools usually make use of a random test generation for 60-80% of the faults (easy to detect) and deterministic test generation for the remaining part (hard to detect)
- Examples of commercial ATPG tools:
 - Encounter Test - Cadence
 - TetraMax - Synopsys
 - FastScan, FlexTest - Mentor Graphics

Test Generation for Sequential Circuits


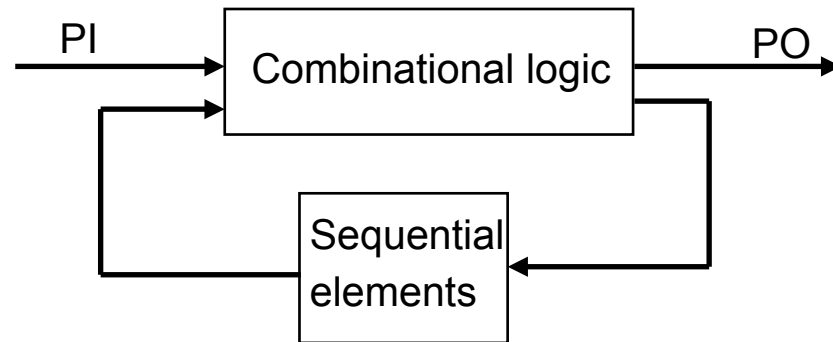
- Most real circuits are sequential
- A major problem is that the output depends not only on inputs but also on current state




Outline

- Electronics
- Manufacturing
- Test, diagnosis, and verification
- Test generation
- Test points and Scan
- Test Compression
- Built-In Self-Test (BIST)
- Systems-on-chip test
- Boundary scan (IEEE 1149.1)


Test Point Insertion

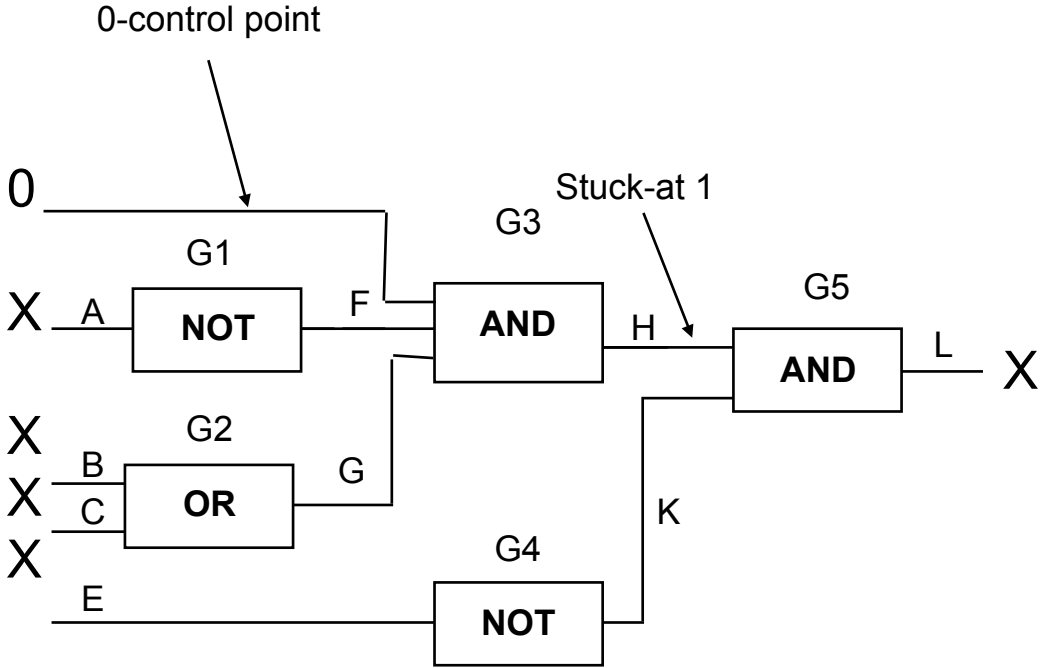 


Test Point Insertion

 


Original

 


Observation

 

0-controllability

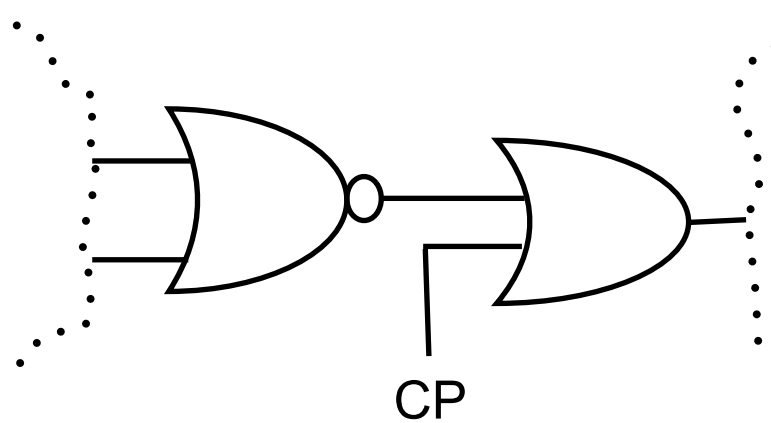


1-controllability

 


1/0-controllability

Sequential -> Combinational

 - Problem: ATPG works for combinational logic while most ICs are sequential
- Solution: Provide a test mode in which flip flops can be accessed directly
- Register provide virtual primary inputs/primary outputs





Flip flops

 

1. Write flip flops
2. Stimulus at inputs
3. Normal cycle launch/capture
4. Observe output
5. Read flip flops

Scan Design Concept

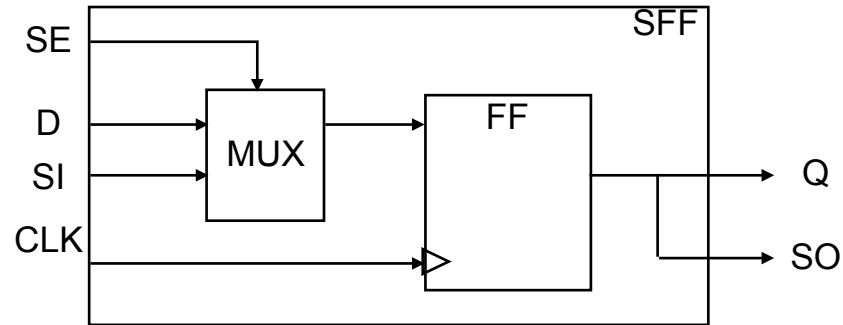
 


SE: Scan enable
SI: Scan input
SO: Scan output

- Replace flip flop (FF) with scan flip flop (SFF): extra multiplexer on data input
- Connect SFFs to form one or more scan chains
- Connect multiplexer control signal to scan enable

Sequential -> Combinational

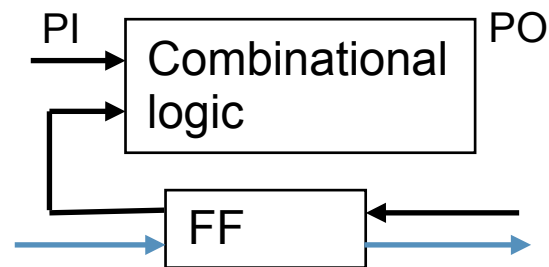 - Circuit can be in two modes: Functional mode and Test mode
- In Test mode test data can be shifted in and shifted out
- Test mode adds virtual PI and PO such that test data can be directly applied to combinational logic
- ATPG for combinational logic works also for sequential




1. Write flip flops
2. Stimulus at inputs
3. Normal cycle launch/capture
4. Observe output
5. Read flip flops


Test application




Automatic Test Equipment (ATE)

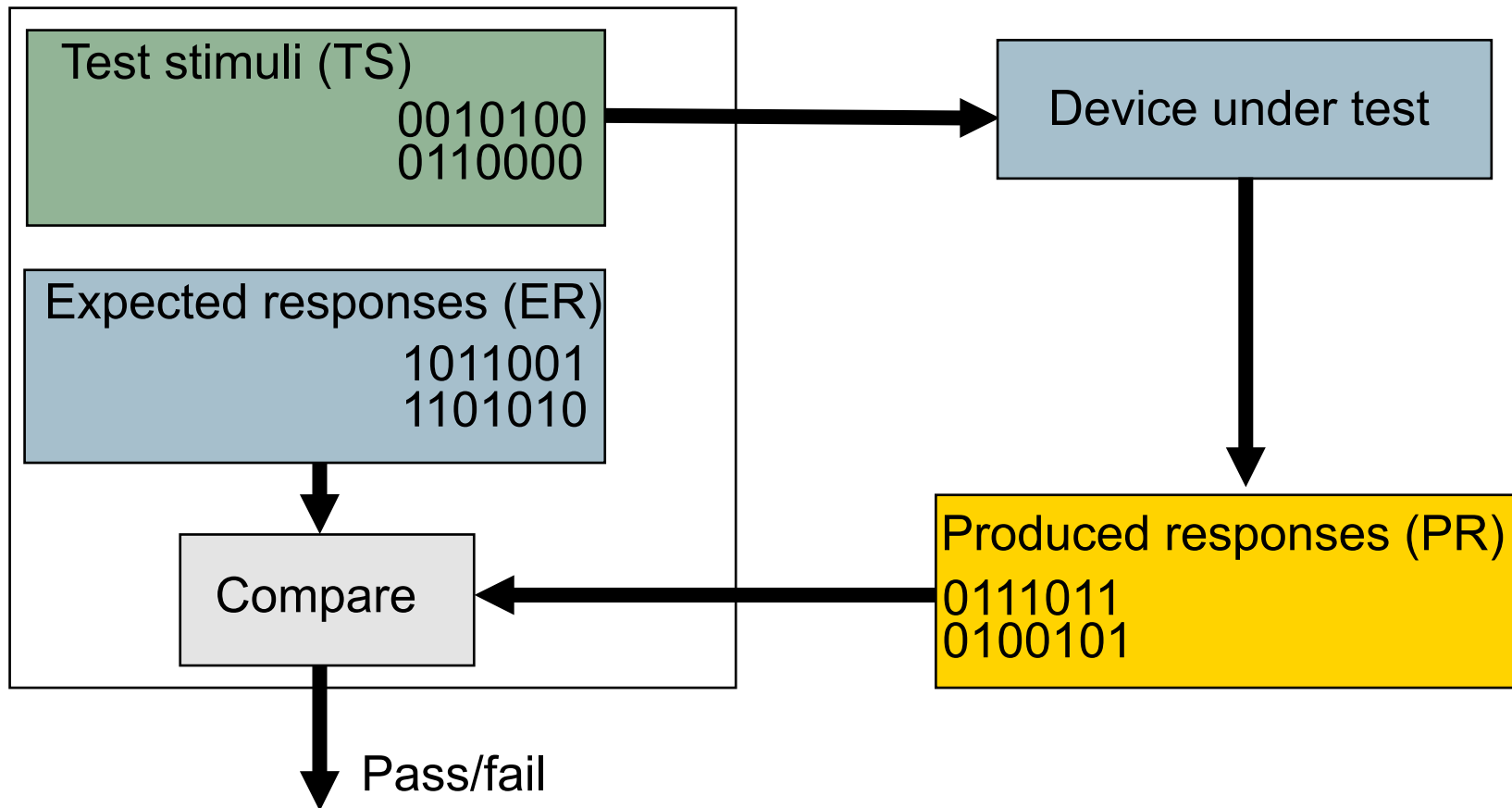


Test Application

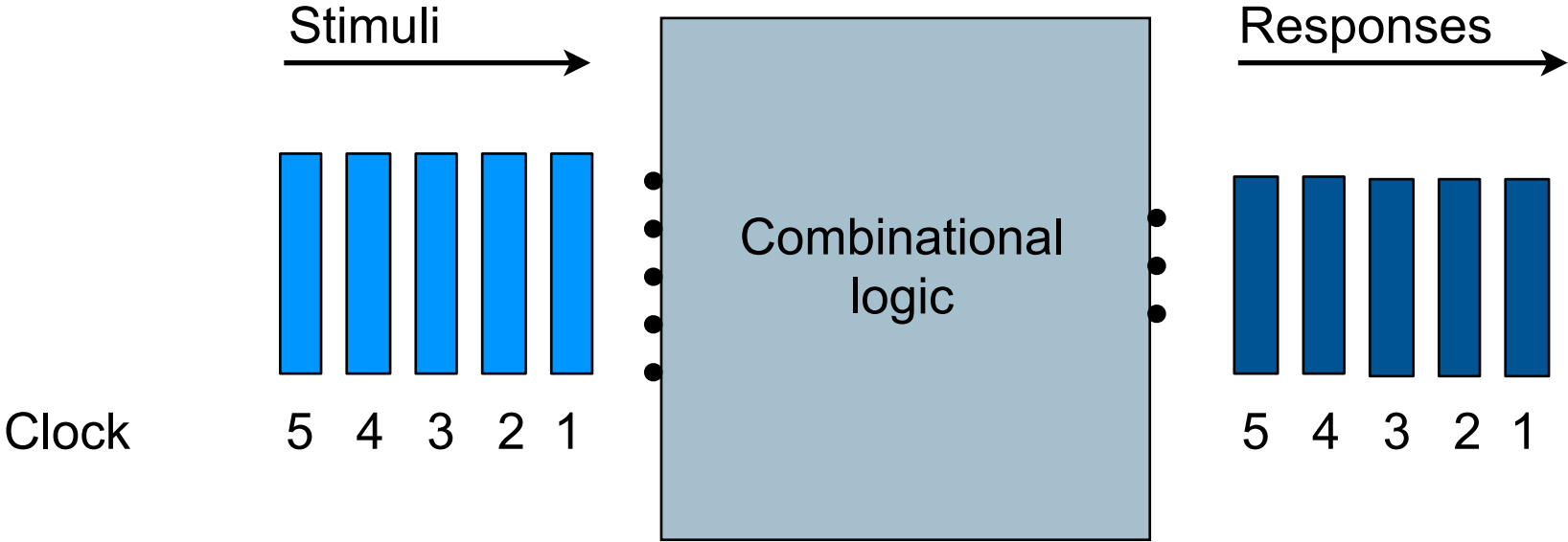


Scan Test Application - first attempt

 

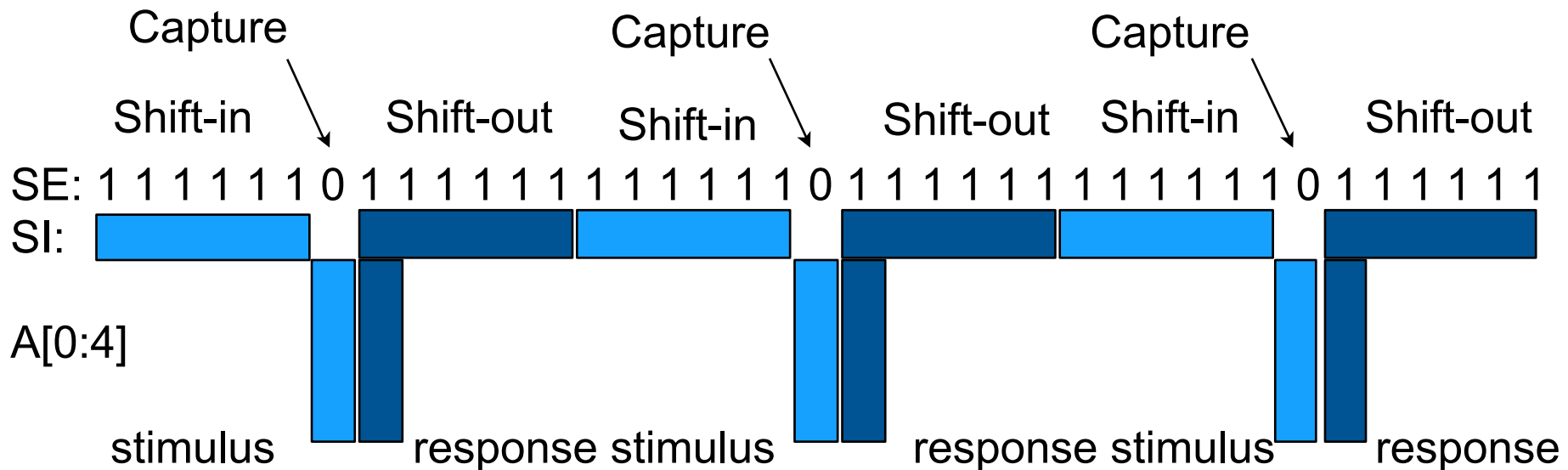
Test time=number of patterns
 *(shift-in + capture + shift-out)=
 $3*(6+1+6)=39$



Scan Test Application - second attempt

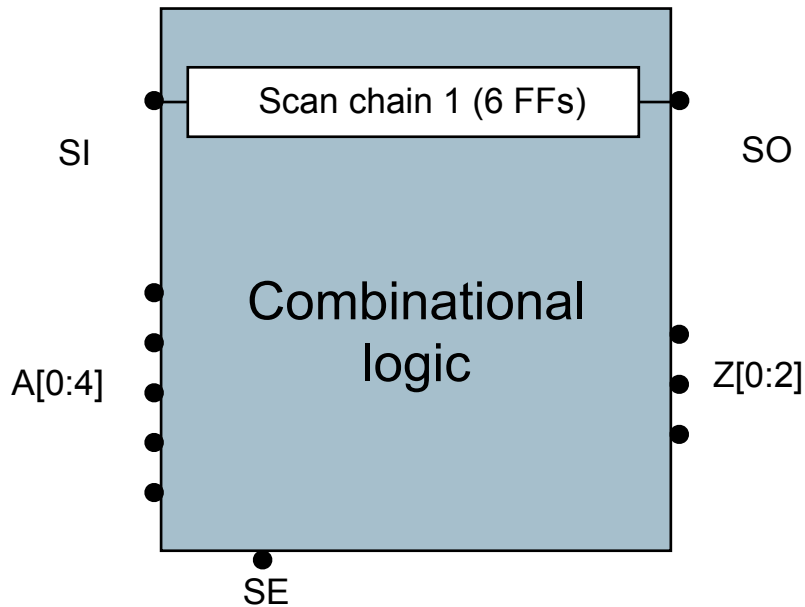

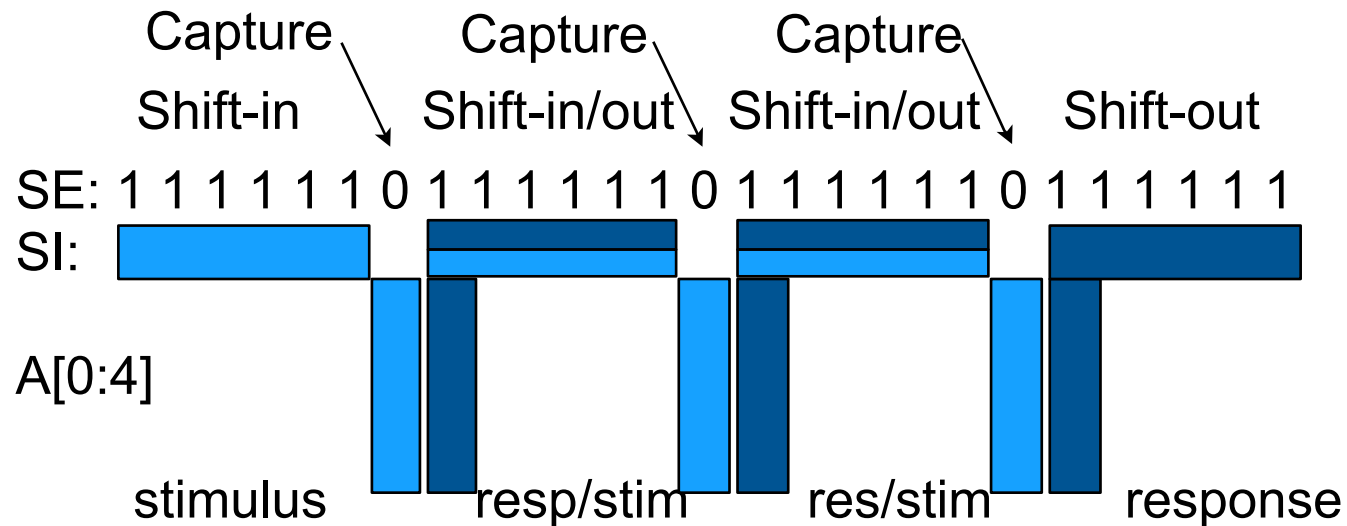Test time = number of patterns
 * (shift-in + capture) + shift-out =
 $3 * (6 + 1) + 6 = 27$



Scan Benefits and Costs

Scan Benefits

- Automatic scan insertion
- ATPG
- High fault coverage
- Short test development time

EDA tools

- For scan insertion (converting flip flops to scan flip flops)
- Connection
- Partial scan selection
- Scan stitching

Scan Costs

- Silicon area - Mux, scan chain, scan enable
- Performance reduction - Multiplexer in time-critical path
- IC pins - Scan-in (SI), scan-out (SO), scan_enable (SE)
- Test time - Serial shifting is slow

Delay Test

- Stuck-at-fault test consist of one vector. Each vector applied at slow speed (DC-scan).
- Timing related faults need two vectors and they are to be applied on consecutive clock cycles (at normal clock speed) (AC-scan)
- At speed test:
 - Vector V1 is applied to set the circuit in its state
 - Vector V2 is applied
 - Response is captured
- Three approaches:
 - Launch-on-capture
 - Launch-on-shift
 - Enhanced scan

Launch on shift (LOS) and launch on capture (LOC)

- Launch on capture (broadside or double capture)
 - shift in test stimuli (usually at low speed). For an n-bit shift register, shift in n bits.
 - apply a capture to create transition
 - apply another capture cycle to capture the response
- Launch on shift (skewed load)
 - shift in test stimuli (usually at low speed). For an n-bit shift register, shift in n-1 bits at low speed.
 - The final bit is shifted at high speed and then a capture is applied in high speed.

Outline

- Electronics
- Manufacturing
- Test, diagnosis, and verification
- Test generation
- Test points and Scan
- Test Compression
- Built-In Self-Test (BIST)
- Systems-on-chip test
- Boundary scan (IEEE 1149.1)

ATE-based testing


- Advantages with ATE-based testing
 - High quality test
 - Diagnosis possible
- Disadvantages with ATE-based testing
 - ATEs are expensive
 - Interface between ATE and device-under-test
 - Low throughput due to:
 - Long scan-chains
 - Low test shift speed
 - Limited number of channels
 - Limited tester memory
 - Only possible to test at manufacturing

Alternatives


- Test data compression
- Built-In Self-Test
 - Logic BIST and Memory BIST
- Important aspects:
 - Test stimuli
 - Test responses

Test generation

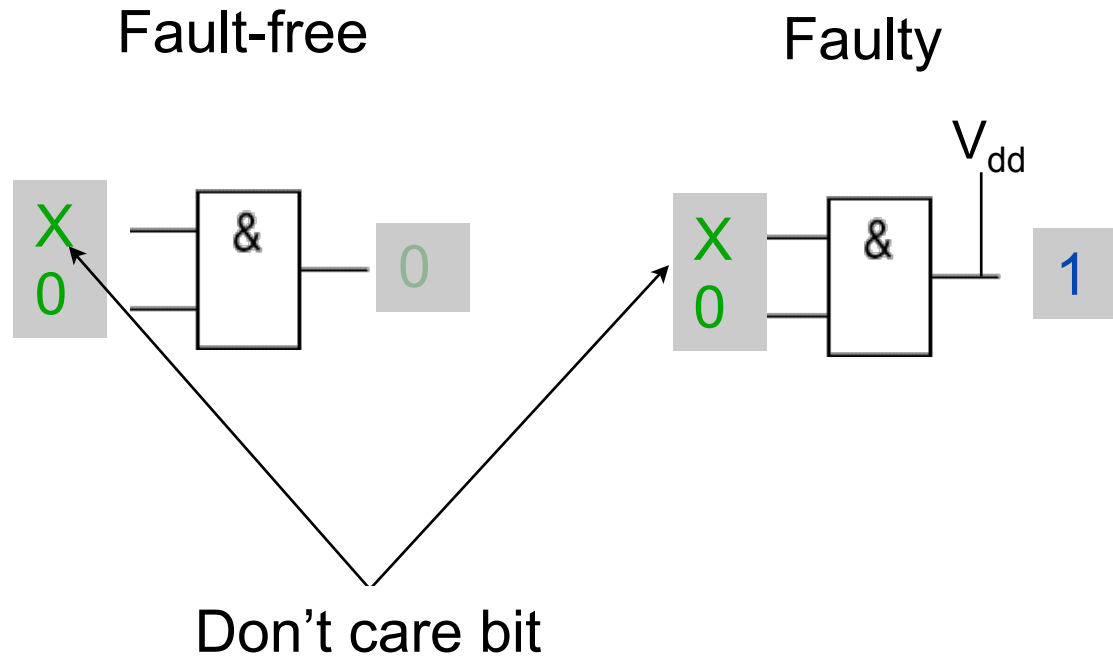Example: Create test for output connected to V_{dd}




D-Algorithm

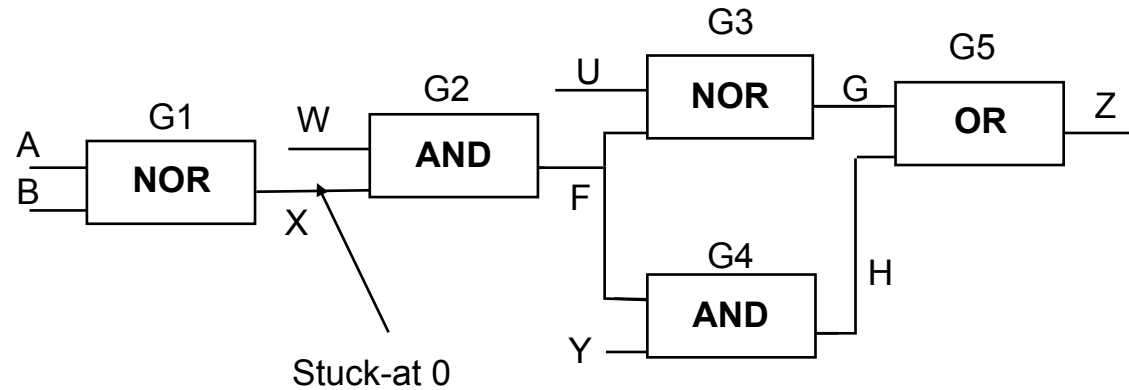

- Initialize the circuit by placing X on each line
- For a SA0, $X=D$ and $A=B=0$ (for the selected fault)
- Propagate D through G2
- Select a sensitizing path (we select G3)
- To propagate through G3, we let $U=0$
- Propagate through G5
- Reached a primary output with D
- Justify values on H, Y, U, W. $H=0$ (ok). $F=0$? Conflict! Select $Y=0$


Analysis of Scan Test

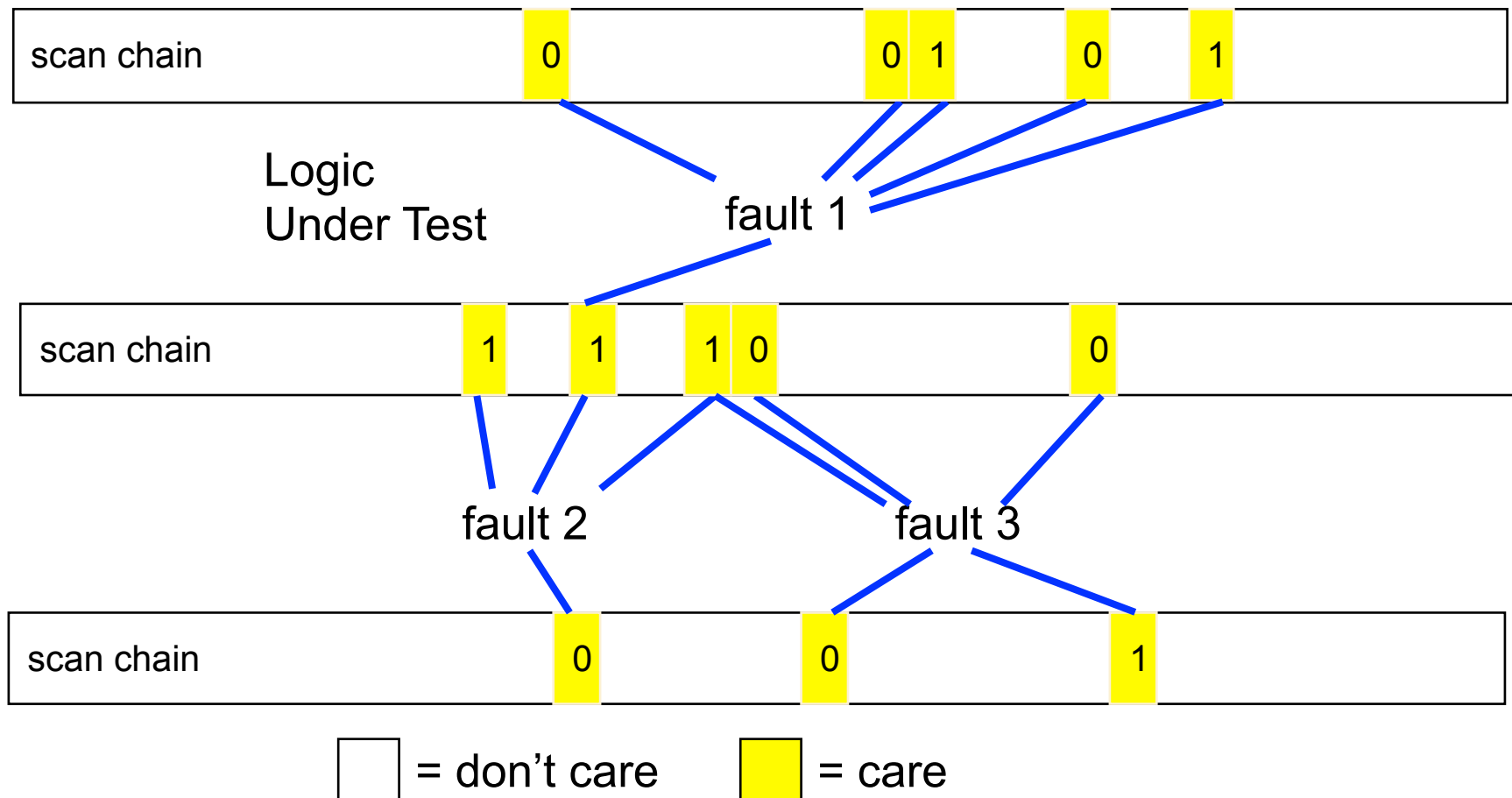- ATPG first creates test cubes
 - Merged for several faults; many unspecified don't care values




Analysis of Scan Test

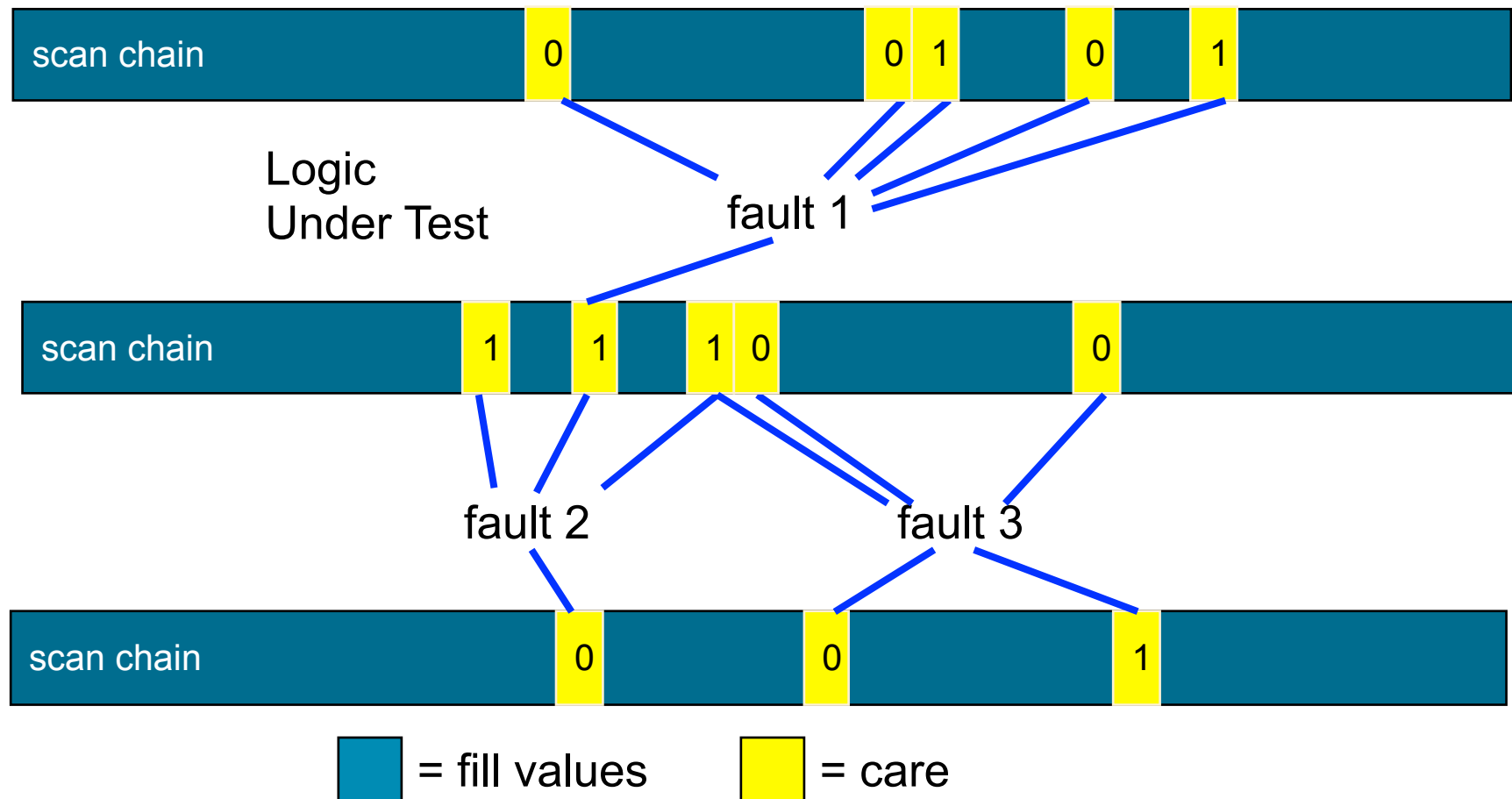- Then, convert cubes to vectors by filling don't cares
 - Fault simulate vectors to mark off additional faults




Test data compression

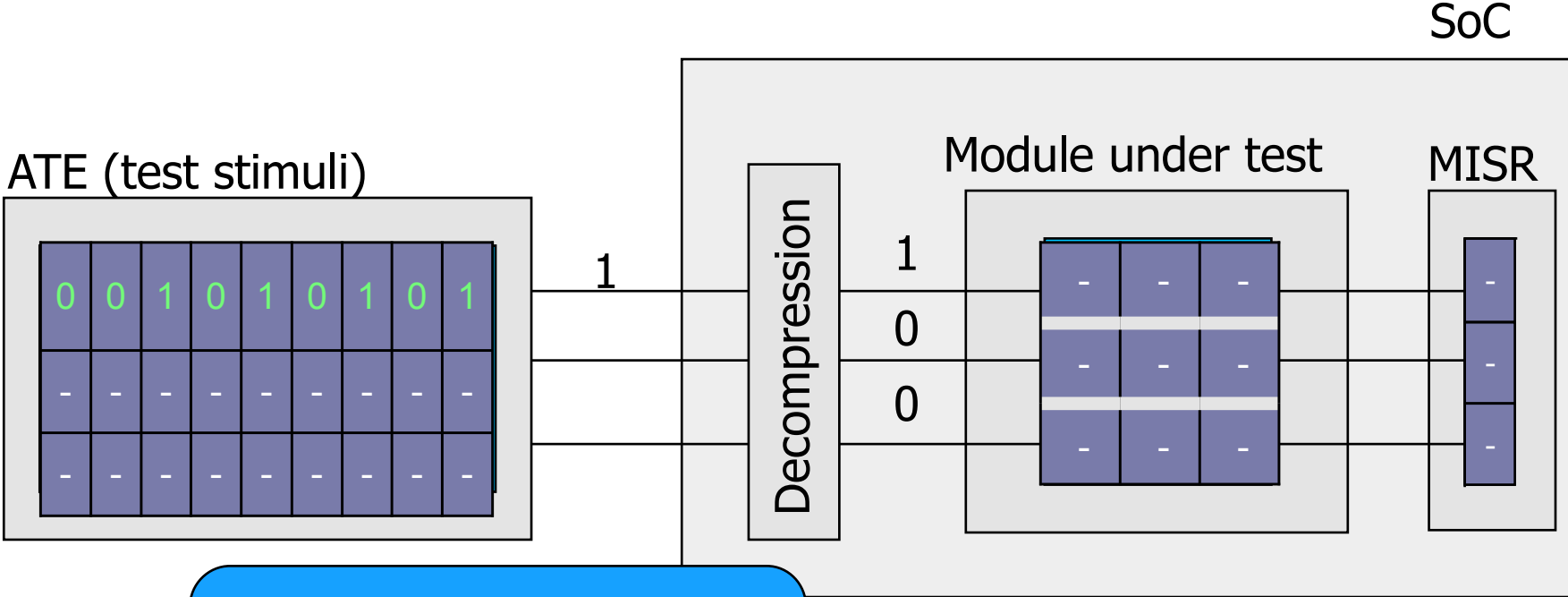





Few ATE channels and many (short) scan-chains lead to shorter test times

Test data compression

MISR (produced)

 

MISR (expected)

   
 


Faulty module!

Outline

- Electronics
- Manufacturing
- Test, diagnosis, and verification
- Test generation
- Test points and Scan
- Test compression
- Built-In Self-Test
- Systems-on-chip test
- Boundary scan (IEEE 1149.1)

On-chip/off-chip

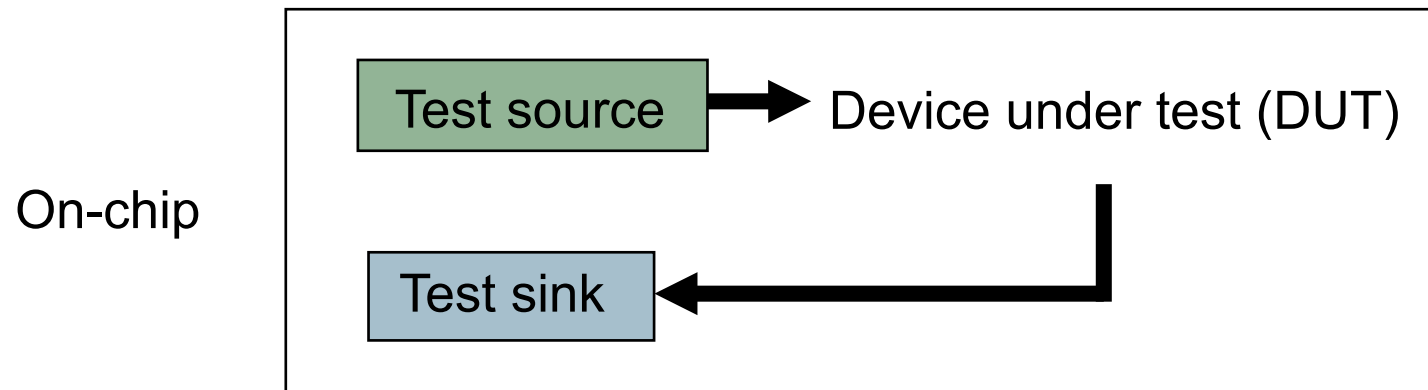 


Test Pattern Generation


- How store/generate test patterns on-chip?
- Deterministic test patterns
- Exhaustive test patterns
- Pseudo-exhaustive/random test patterns
- Random test patterns
- Commercial tools usually make use of a random test generation for 60-80% of the faults (easy to detect) and deterministic test generation for the remaining part (hard to detect)

Test generations

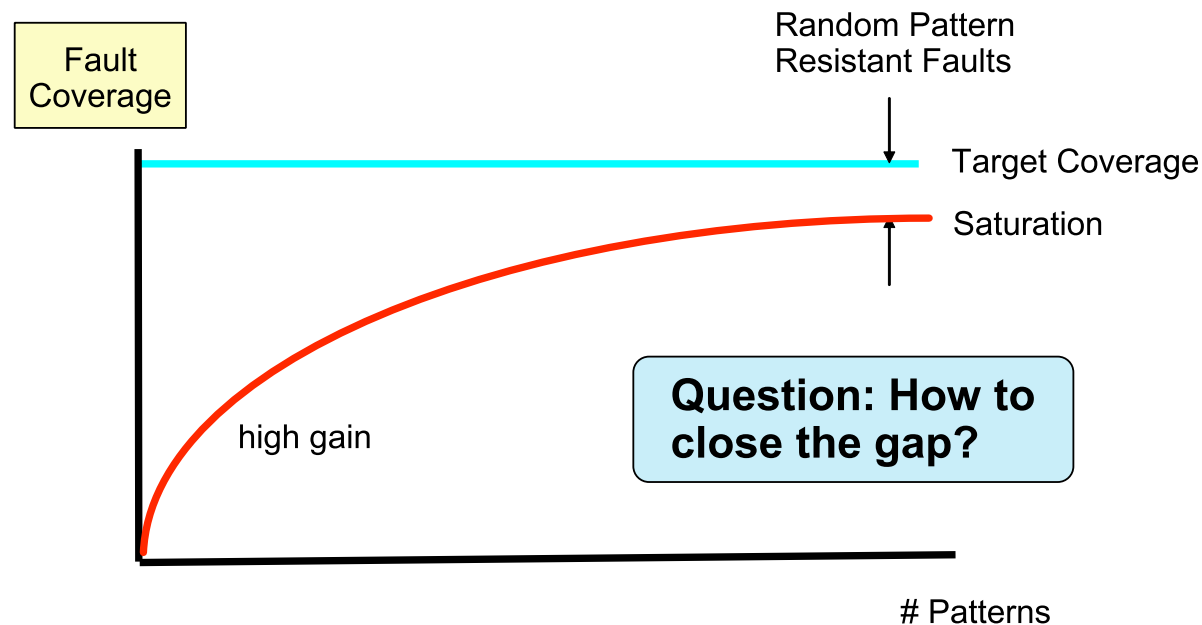- Some logic takes too long to test with pseudo-random patterns
 - Too many specific input bit values are required
 - Too many pseudo-random trials needed to achieve the required value combination



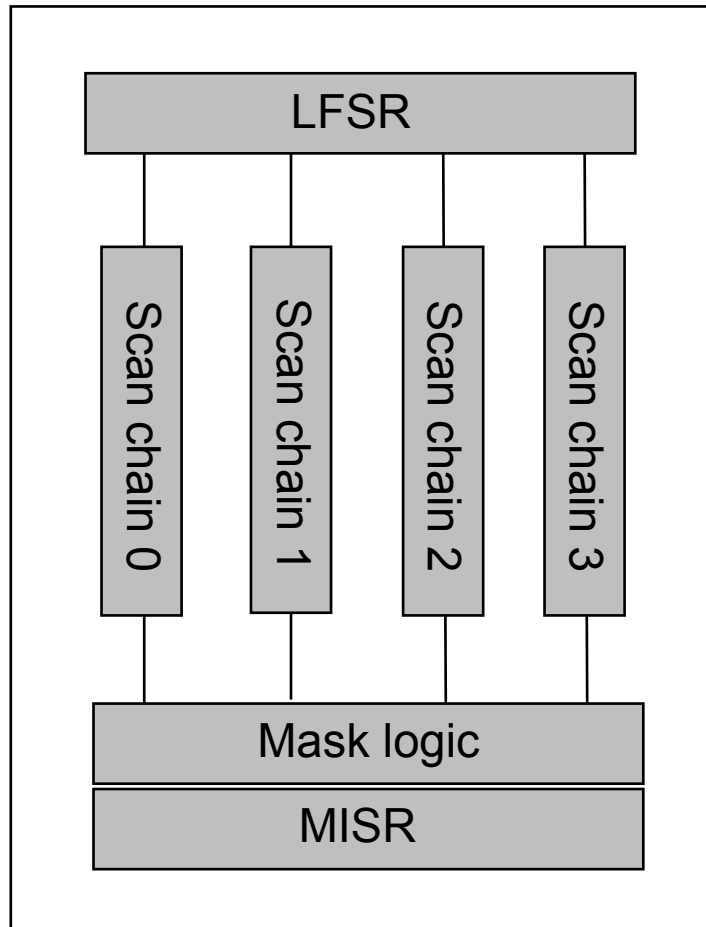STUMPS: Self-testing using MISR and parallel shift register sequence generator




Test source: **L**inear **F**eedback
Shift **R**egister (LFSR)
Test sink: **M**ultiple Input
Signature **R**egister (MISR)


Outline

- Electronics
- Manufacturing
- Test, diagnosis, and verification
- Test generation
- Test points and Scan
- Test compression
- Built-In Self-Test (BIST)
- Systems-on-chip test
- Boundary scan (IEEE 1149.1)


System-on-Chip

 


Die

 

 - Viper 2.0 RevB
- Analog/Digital TV Processor
- 10mm x 10 mm (100 mm²)
- ~10 M gates
- ~50 M transistors
- ~100 clock domains




Generic Test Access Architecture


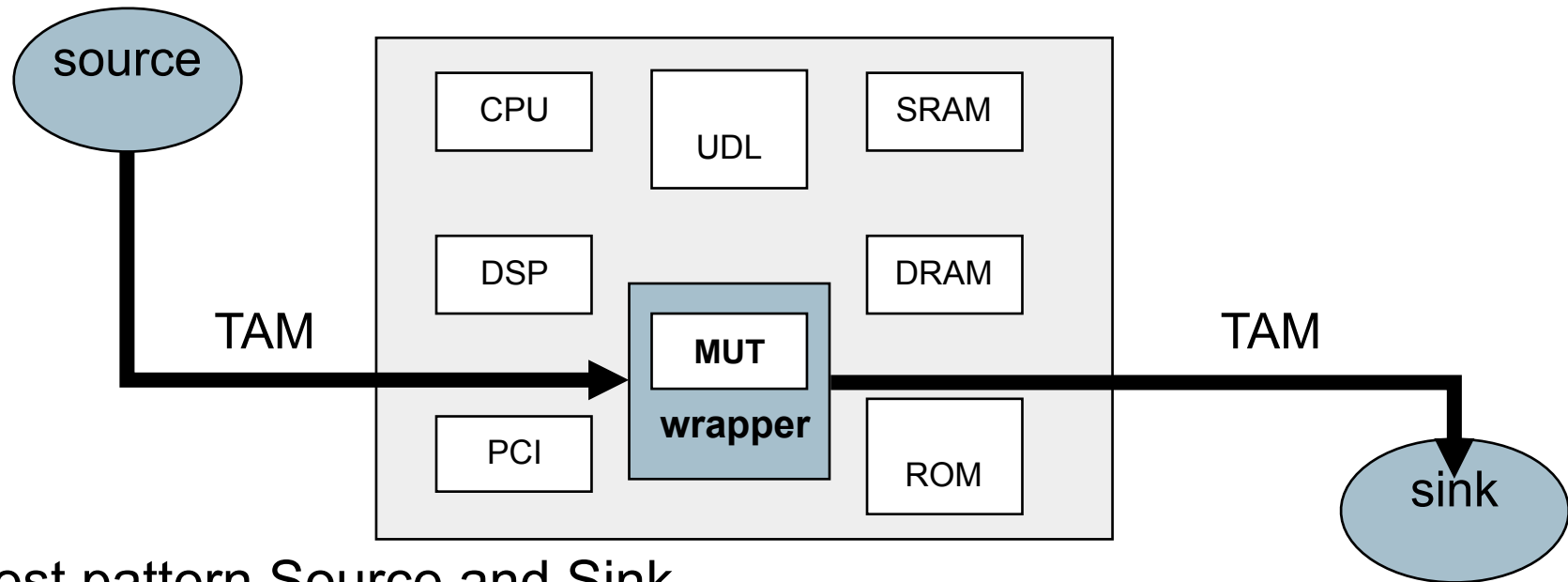


- Test pattern Source and Sink
 - Store/generate test stimuli and store/evaluate test responses
- Test Access Mechanism (TAM)
 - Transports test patterns to/from module under test (MUT)
- Test Wrapper
 - Provides test access to MUT
 - Isolates MUT at test


Architecture Design

 

Wrapper Design

 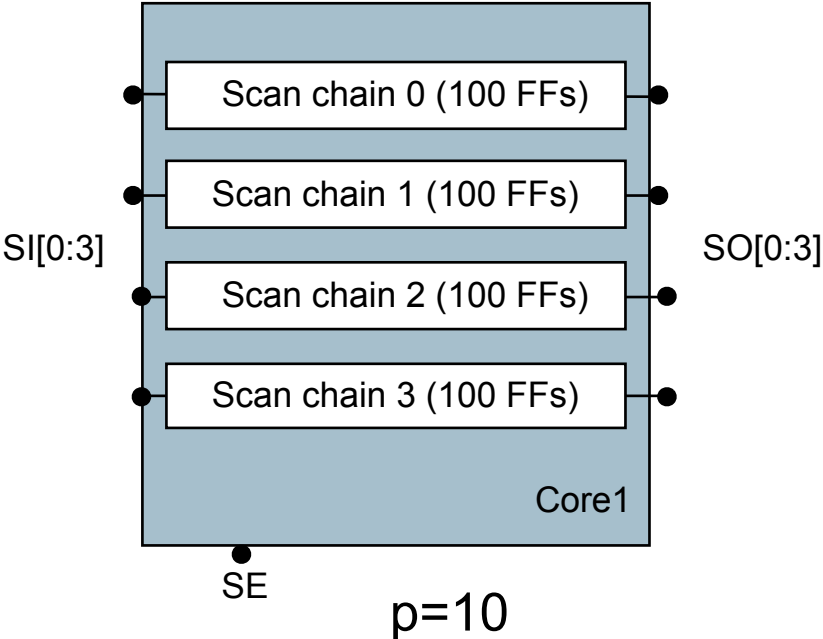

$$T = (200 + 1) * 10 + 200 = 2210$$

 



$$T = (200 + 1) * 10 + 200 = 2210$$

$$\text{Test time } (T) = (sc + 1) * p + sc$$



$$T = (400 + 1) * 10 + 400 = 4410$$


Core To TAM Assignment

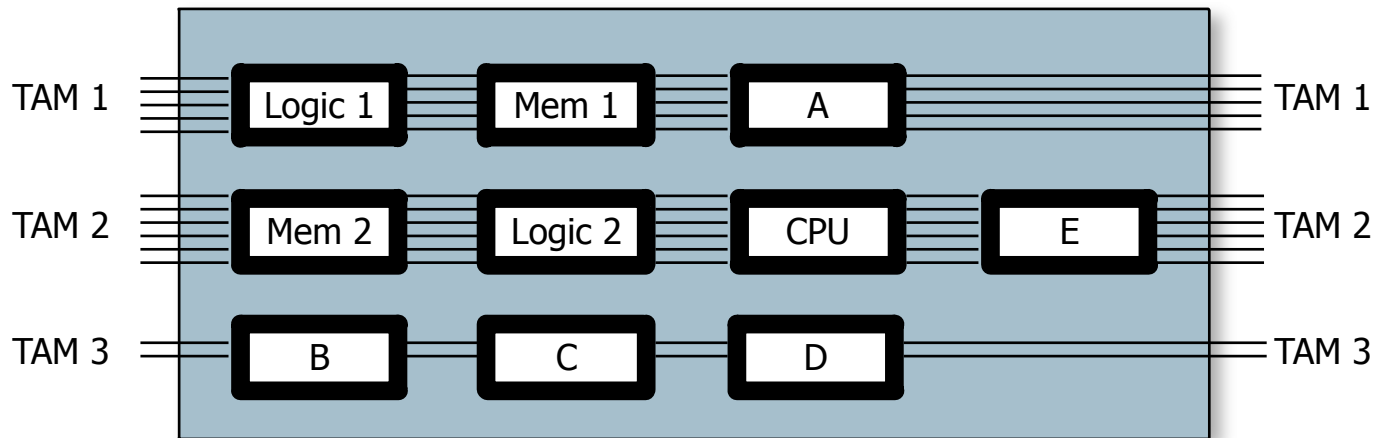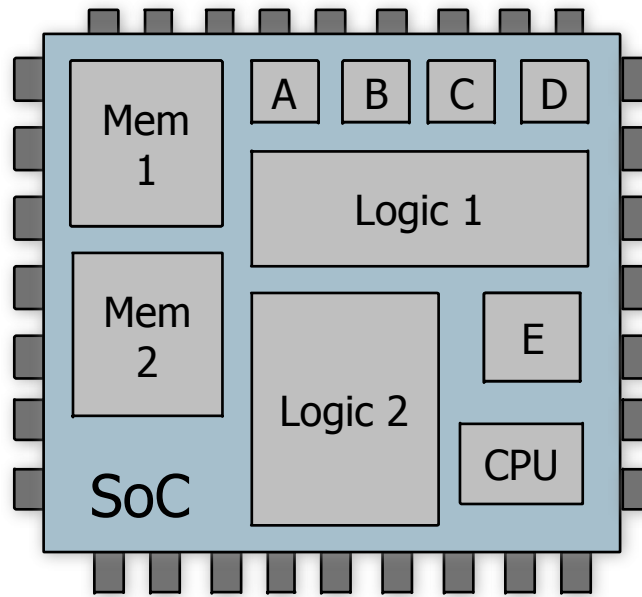

Outline

- Electronics
- Manufacturing
- Test, diagnosis, and verification
- Test generation
- Test points and Scan
- Test Compression
- Built-In Self-Test (BIST)
- Systems-on-chip test
- Boundary scan (IEEE 1149.1)

Probing for Test

 



Test Objectives

- Given a Printed Circuit Board (PCB) composed of a set of components (ICs) where each component is tested good.
- The main objectives are to ensure that all components are:
 - correct (the desired ICs are selected)
 - mounted correctly at the right place on the board and
 - ensuring that interconnections are functioning according to specification
- Problems that may occur:
 - A component does not contain logic
 - A component is not placed where it should be,
 - A component is at its place but turned wrongly,
 - A component is correct but the interconnection is not correct, for example due to bad soldering.


Boundary Scan (IEEE std. 1149.1)

- The Joint European Test Action Group (JETAG), formed in mid-80, became Joint Test Action Group (JTAG) in 1988 and formed the IEEE std 1149.1. The standard consists of:
 - Test Access Port (TAP)
 - TAP Controller (TAPC),
 - Instruction Register (IR), and
 - Data Registers (DR)

Boundary Scan

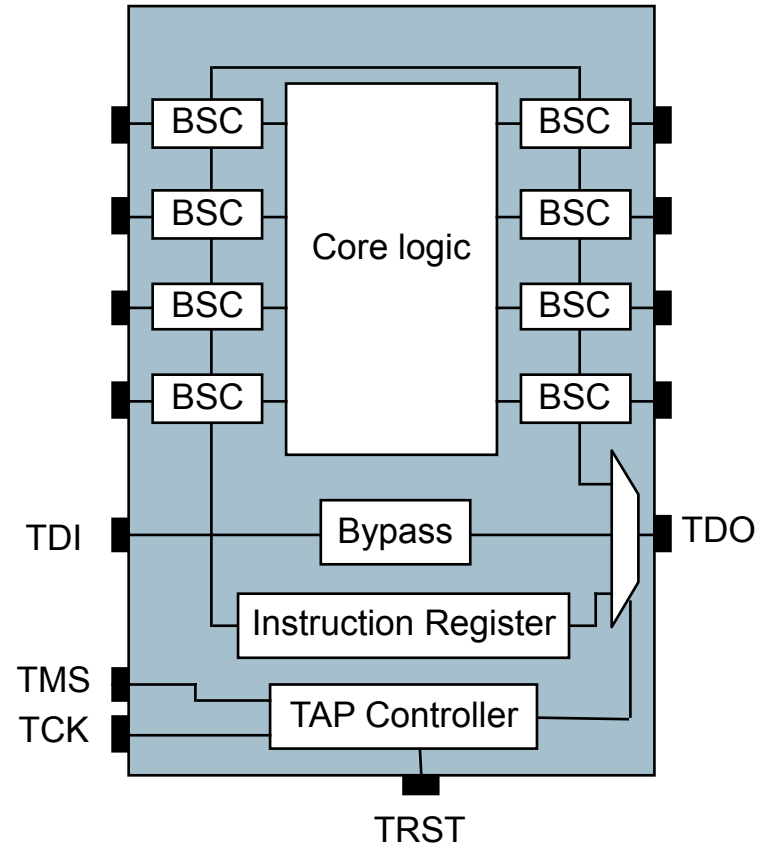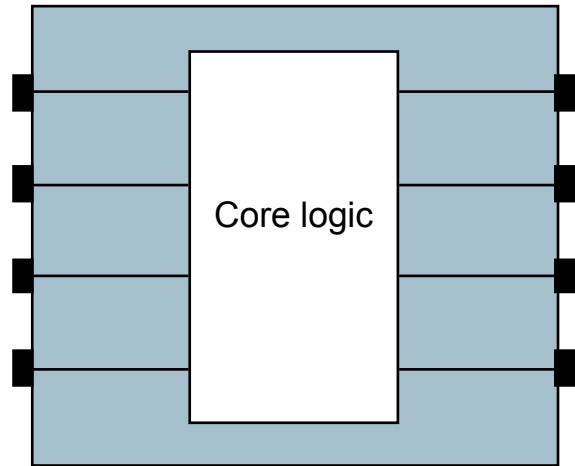

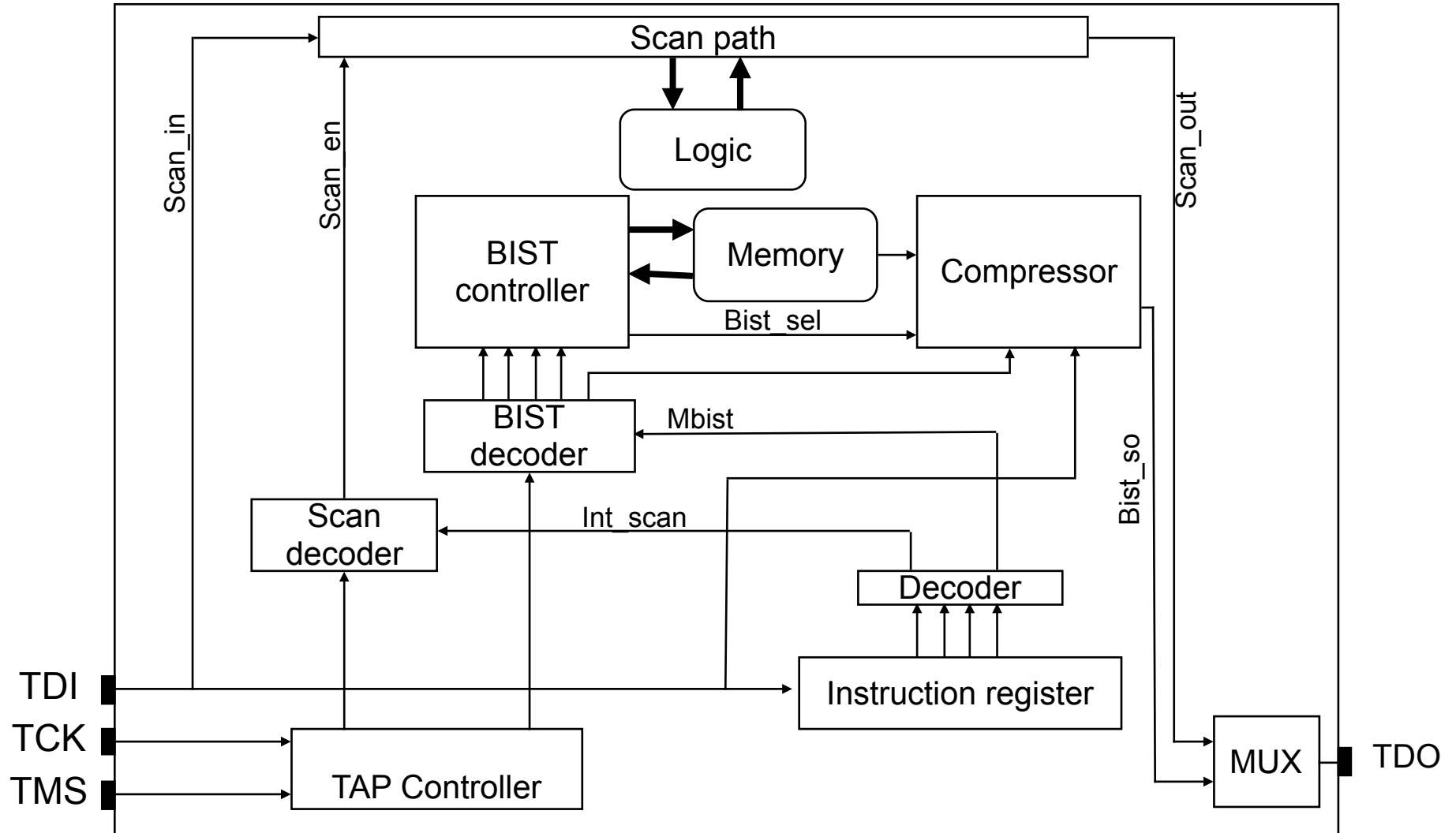Scan and MBIST support with Boundary Scan



Introduction to structured VLSI design

Design for Test (DfT) - Part 2

Erik Larsson

EIT, Lund University

