



LUND  
UNIVERSITY

# EITF35: Introduction to Structured VLSI Design

Part 2.2.1: Sequential circuit

Liang Liu  
liang.liu@eit.lth.se



# Outline

- **Sequential vs. Combinational**
- **Synchronous vs. Asynchronous**
- **Basic Storage Elements**
- **Timing**
- **Folding & Pipeline**



# Sequential vs. Combinational

## □ A combinational circuit:



## □ At any time, outputs depend only on present inputs

- Changing inputs changes outputs

## □ No regard for previous inputs

- No memory (history)


## □ Time is “ignored” !

- Time-independent circuit



# Sequential vs. Combinational

## □ A sequential circuit:

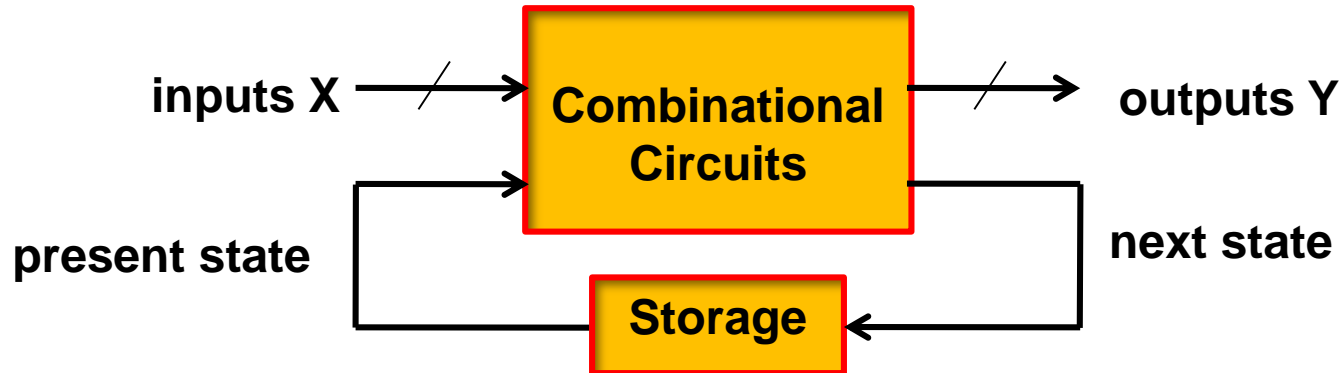

## □ Outputs depends on inputs and **past history** of inputs

- Previous inputs can be stored into **storage elements**
- **Input order matters**




# Sequential vs. Combinational: adders

□ Calculate  $A_3A_2A_1A_0 + B_3B_2B_1B_0$


□ Combinational adder

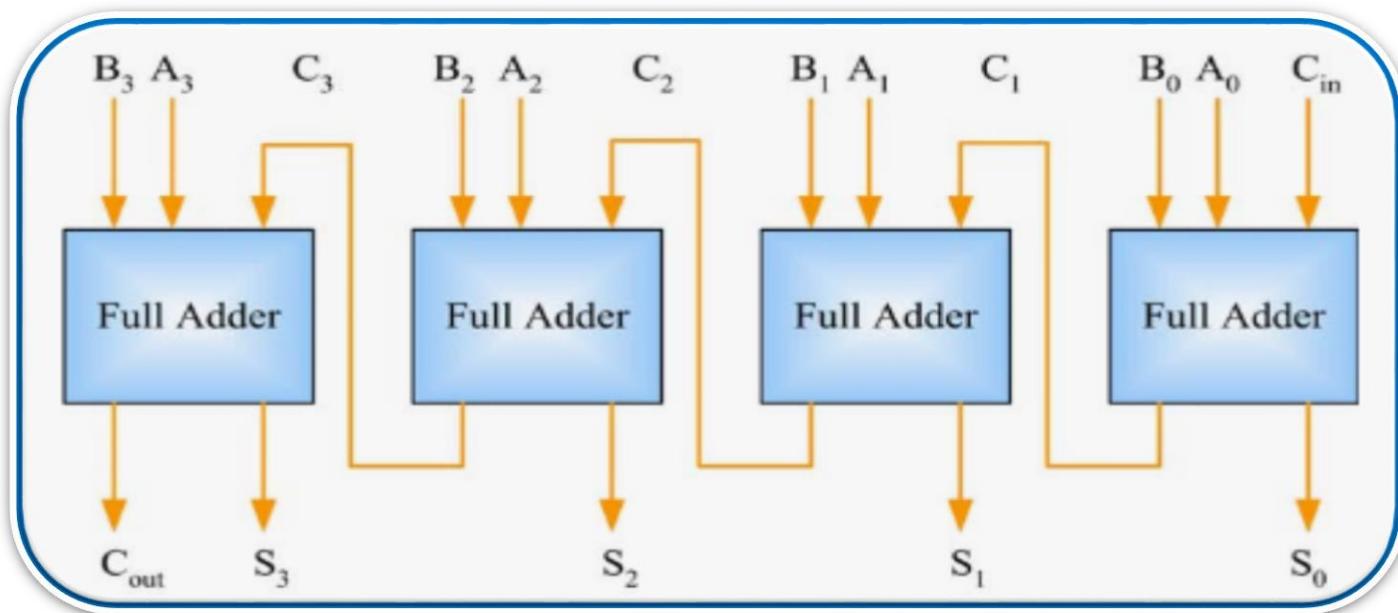- 4 full adders are required
- One adder is active at a time slot



# What we can do with memory?

## □ Sequential Adder

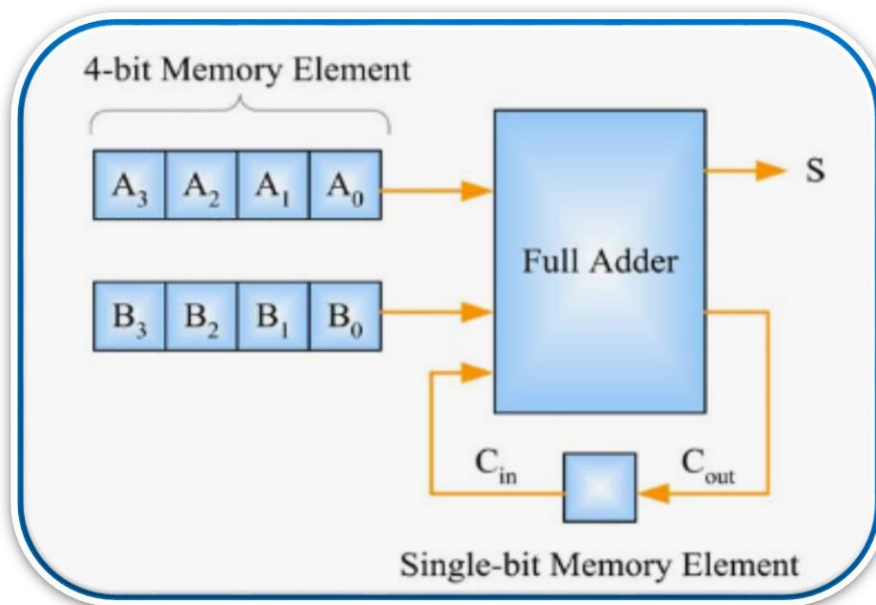

## □ Folding!

- One full adder
- 1-bit memory for carry
- Two 4-bit memory for operators

## □ 4 clock cycles to get the output



# Outline


- Sequential vs. Combinational
- **Synchronous vs. Asynchronous**
- Basic Storage Elements
- Timing
- Folding & Pipeline




# Synchronous vs. Asynchronous
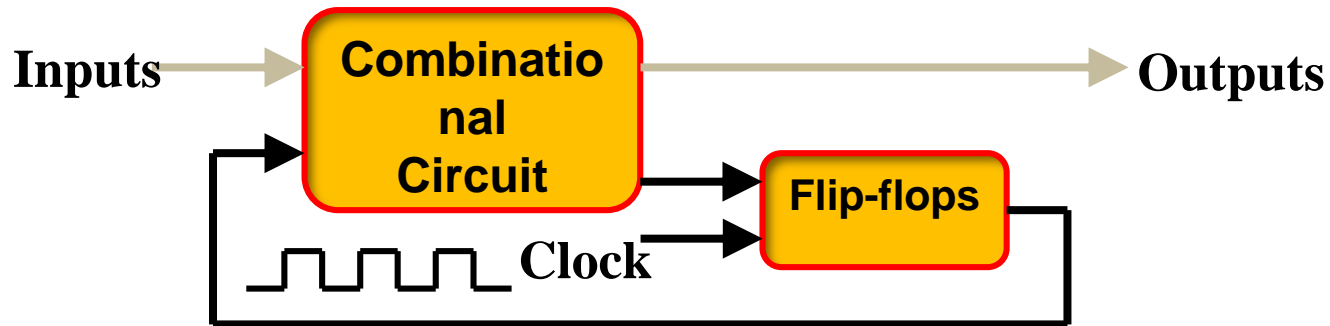
## Two types of sequential circuits:

- **Synchronous**: The behavior of the circuit depends on the input signal at discrete instances of time (also called **clocked**)



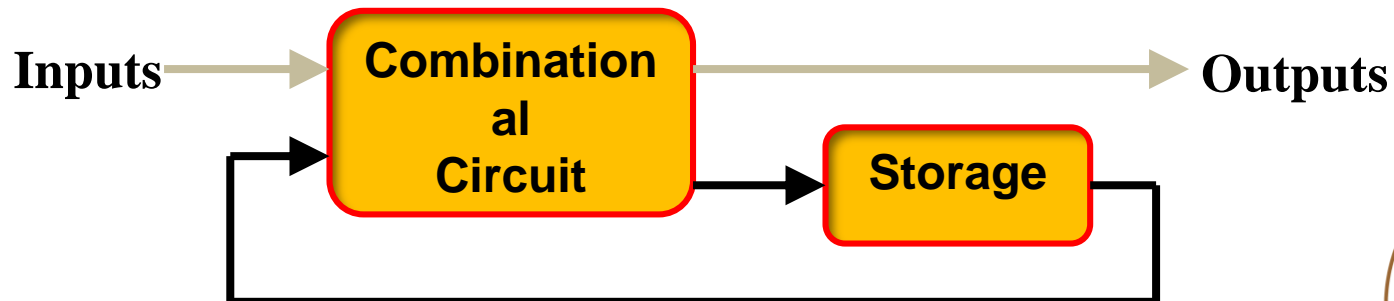- **Asynchronous**: The behavior of the circuit depends on the input signals at **any instance of time**







# Synchronous vs. Asynchronous

- ❑ When you have a clock
- ❑ You know that washer takes 1 hour
- ❑ You put the laundry in the washer and leave
- ❑ Dry 1 hour later



# Synchronous vs. Asynchronous

□ What if you don't have a clock ...

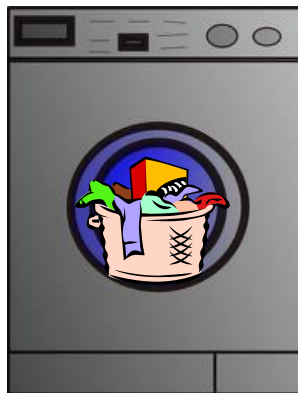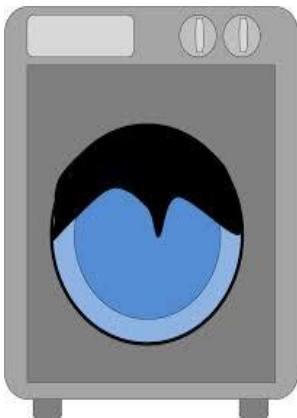

# Synchronous or Asynchronous?

## □ Sync. Advantages: Simplicity to design, debug, and test

- Timing is controlled by one simple clock
- No hand-shake circuits
- Well supported by EDA tools
- Clock-gating to save power
- Recommended for **VLSI**

## □ Sync. Disadvantages:

- Performance constrained by worst-case: critical path
- Overhead for clock network
- Less power efficient

***We will focus on synchronous circuits in this course***



# Power Example

Power Group	Internal Power	Switching Power	Leakage Power	Total Power ( %)	Attrs
io_pad	0.0000	0.0000	0.0000	0.0000 ( 0.00%)	
memory	0.0000	0.0000	0.0000	0.0000 ( 0.00%)	
black_box	0.0000	0.0000	0.0000	0.0000 ( 0.00%)	
clock_network	0.0137	4.982e-03	3.116e-05	0.0187 (13.76%)	
register	3.029e-03	1.298e-03	8.082e-04	5.136e-03 ( 3.79%)	
combinational	0.0518	0.0557	4.337e-03	0.1118 (82.45%)	



# Outline

- Sequential vs. Combinational
- Synchronous vs. Asynchronous
- **Basic Storage Elements**
- Timing
- Folding & Pipeline




# Basic storage element

- D latch: level sensitive
- D flip-flop (D-FF): edge sensitive



c	q*
0	q
1	d

*D latch*

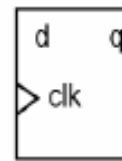


clk	q*
0	q
1	q
$\uparrow$	d

*pos-edge triggered D-FF*



clk	q*
0	q
1	q
$\downarrow$	d

*neg-edge triggered D-FF*

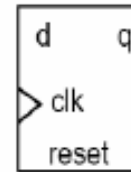



reset	clk	q*
1	-	0
0	0	q
0	1	q
0	$\uparrow$	d

*D-FF with reset*


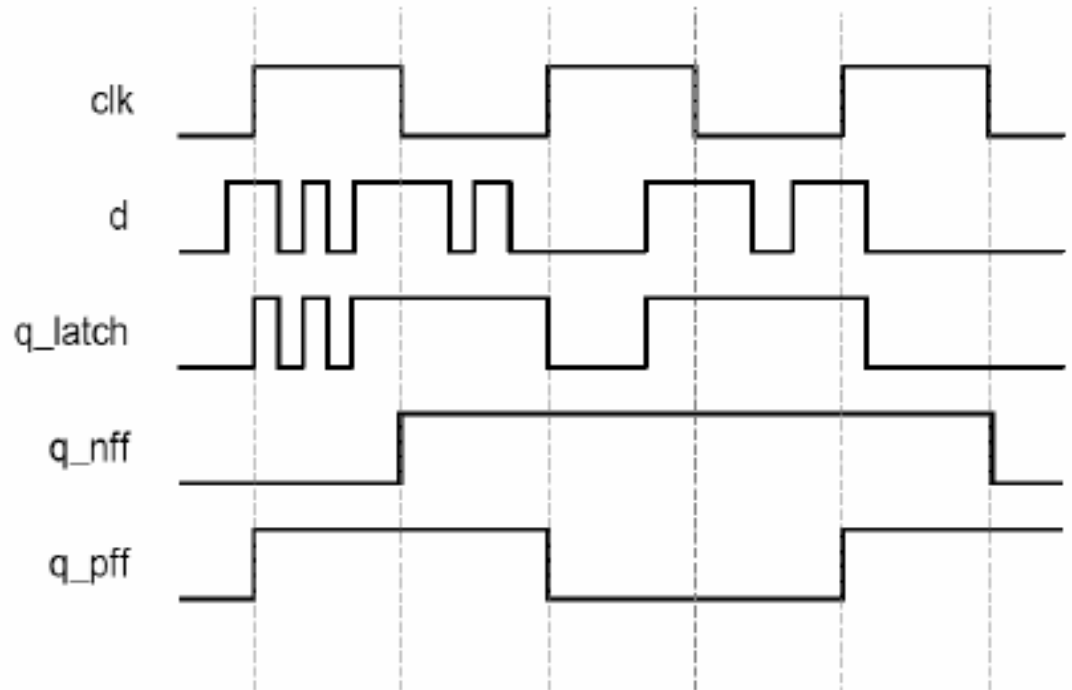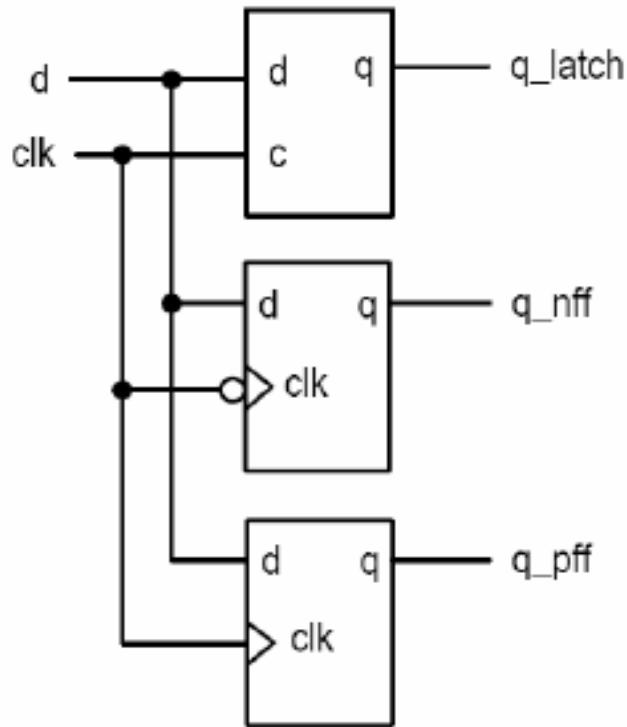
# Basic storage element


- D latch: level sensitive
- D flip-flop (D-FF): edge sensitive



# Problem with Latches

- ❑ **Problem:** A latch is transparent; state keep changing as long as the clock remains active
- ❑ **Due to this uncertainty, latches can not be reliably used as storage elements.**
- ❑ **What happens if Clock=1? What will be the value of Q when Clock goes to 0?**

## Example

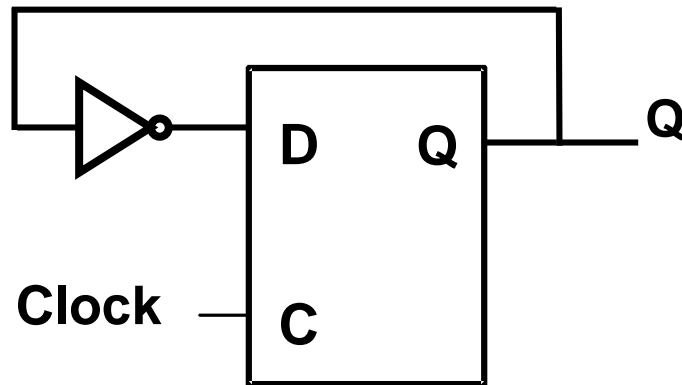



# Outline

- Sequential vs. Combinational
- Synchronous vs. Asynchronous
- Basic Storage Elements
- Timing**
- Folding & Pipeline




# Flip Flops Timing

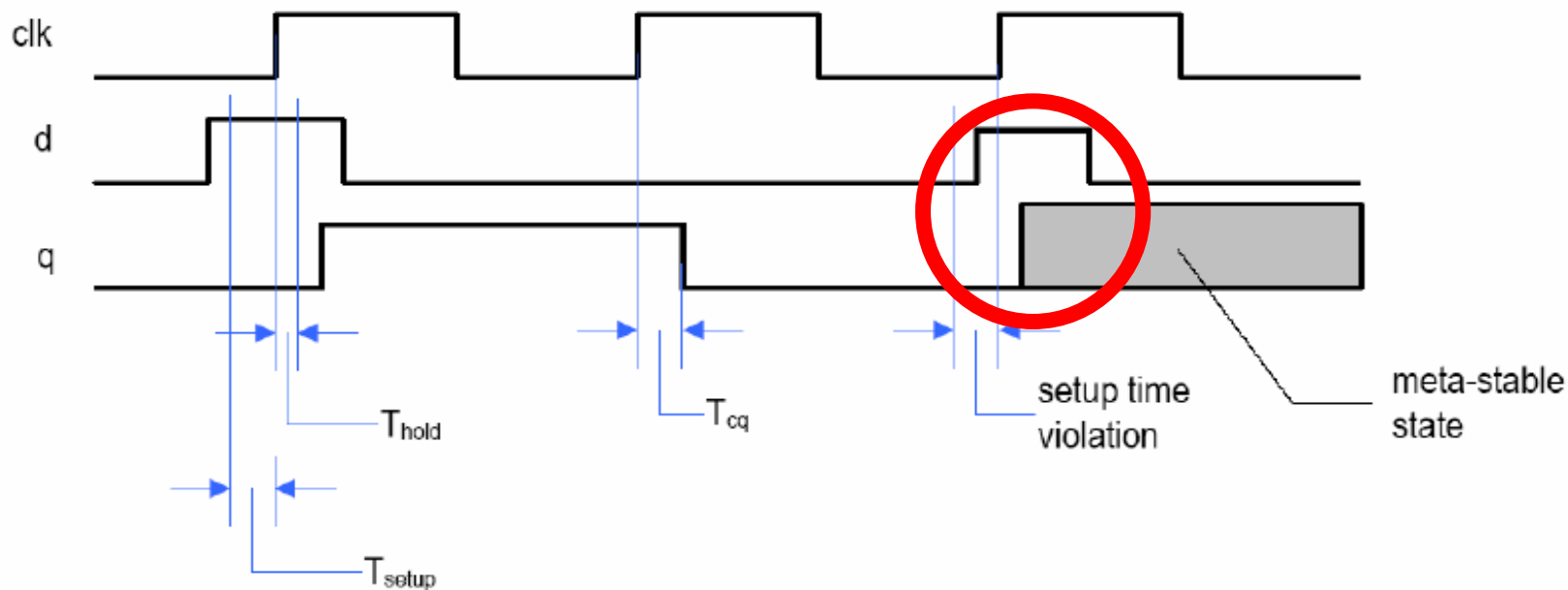
## *Very Important Timing Considerations!*

□ **Setup Time** ( $T_s$ ): The minimum time during which D input must be maintained **before** the clock transition occurs.

□ **Hold Time** ( $T_h$ ): The minimum time during which D input must not be changed **after** the clock transition occurs.




# Metastability in Digital Logic

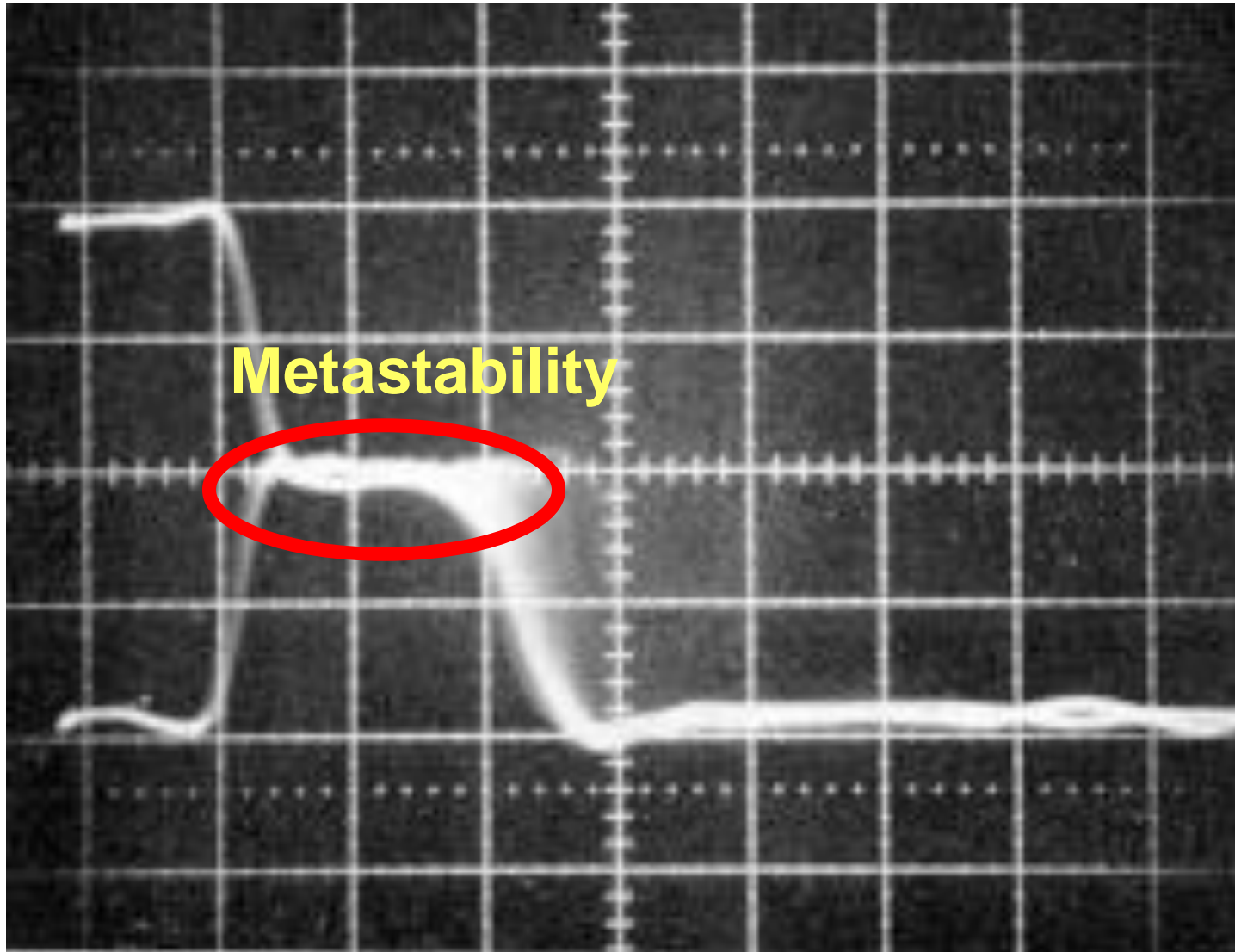

# How fast can a synchronous circuit run?

## □ RTL (Register Transfer Level)

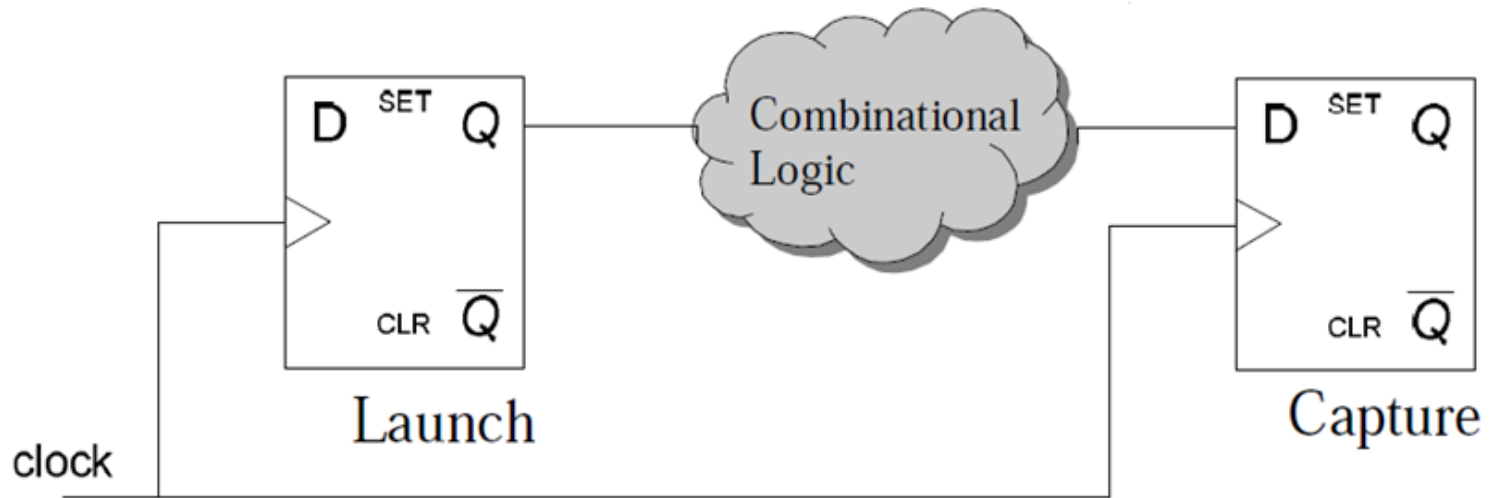

## □ Timing analysis:


- Starting with the clock rising edge at the launch FF, end with the clock rising edge (**next period or same period**) of the capture FF



# Setup Time
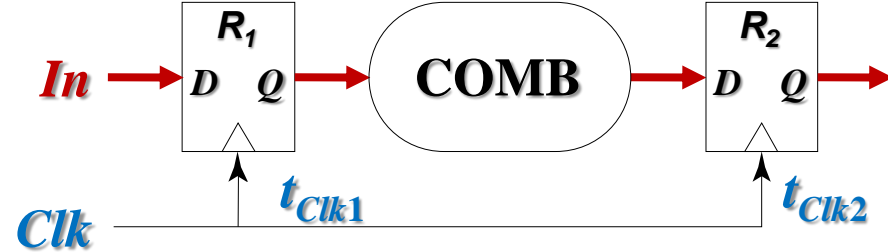
## □ Setup Timing analysis:


- Starting with the clock rising edge at the launch FF, end with the clock rising edge (**next period**) of the capture FF



□ **Data-Path (arrive time):**  $T_{\text{Combinational logic}} + FF_{\text{launch}}(\text{clk} \rightarrow Q)$

□ **Clock-Path (required time):** Clock Period -  $FF_{\text{capture}} t_{\text{Setup}}$

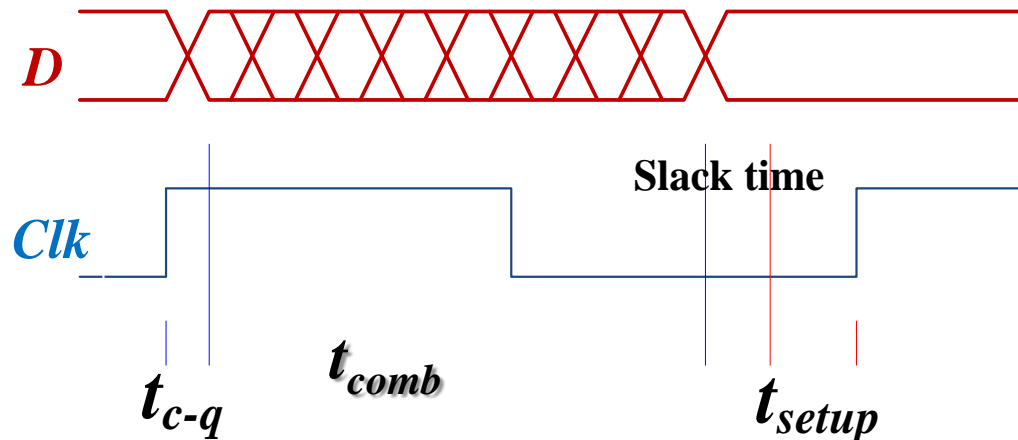
□ **Timing constraint :**  $T_{\text{Combinational logic}} + FF_{\text{launch}}(\text{clk} \rightarrow Q) < \text{Clock Period} - FF_{\text{capture}} t_{\text{Setup}}$



# Hold Time
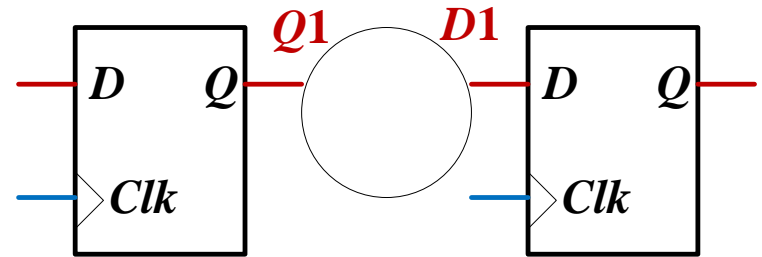
## Hold Timing analysis:


- Starting with the clock rising edge at the launch FF, end with the clock rising edge (same period) of the capture FF



**Data-Path (arrive time):**  $T_{\text{Combinational logic}} + FF_{\text{launch}}(\text{clk} \rightarrow Q)$

**Clock-Path (required time):**  $FF_{t\text{Hold}}$

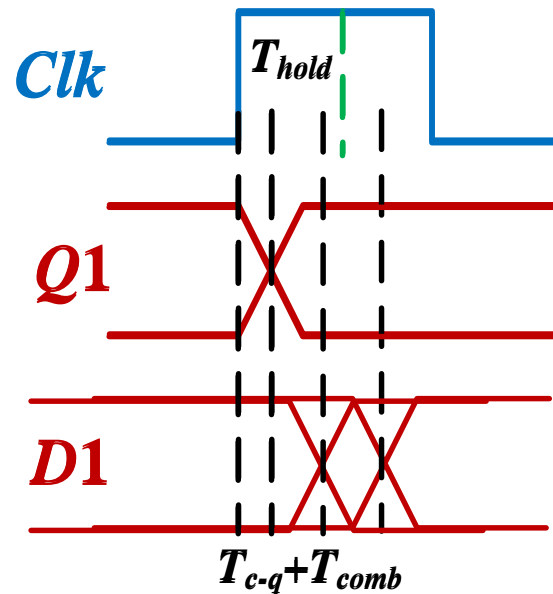**Timing constraint :**  $T_{\text{Combinational logic}} + FF_{\text{launch}}(\text{clk} \rightarrow Q) > FF_{t\text{Hold}}$



# Outline

- Sequential vs. Combinational
- Synchronous vs. Asynchronous
- Basic Storage Elements
- Timing
- **Folding & Pipeline**



# Pipeline

## □ Acknowledgement:


- The following slides have been provided by Prof. Ward in September 2004.
- Reformatting of PowerPoint and addition of two more slide done September 2007 by Jens Sparsø.
- Slides are used in DTU course 02154 Digital Systems Engineering (fall 2008).
- Due to Joachim Rodrigues' position at DTU, I used some of the slides in EITF35.





# Pipelining

## □ Start again from laundry room

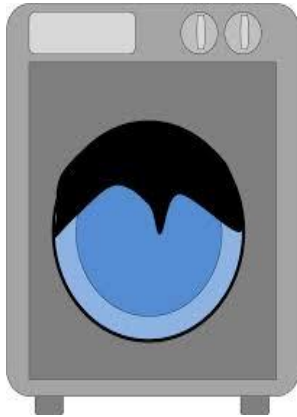

## □ Small laundry has one washer, one dryer and one folder, it takes 110 minutes to finish one load:


- Washer takes 40 minutes
- Dryer takes 50 minutes
- “Folding” takes 20 minutes



## □ Need to do 4 laundries




# Not very smart way...

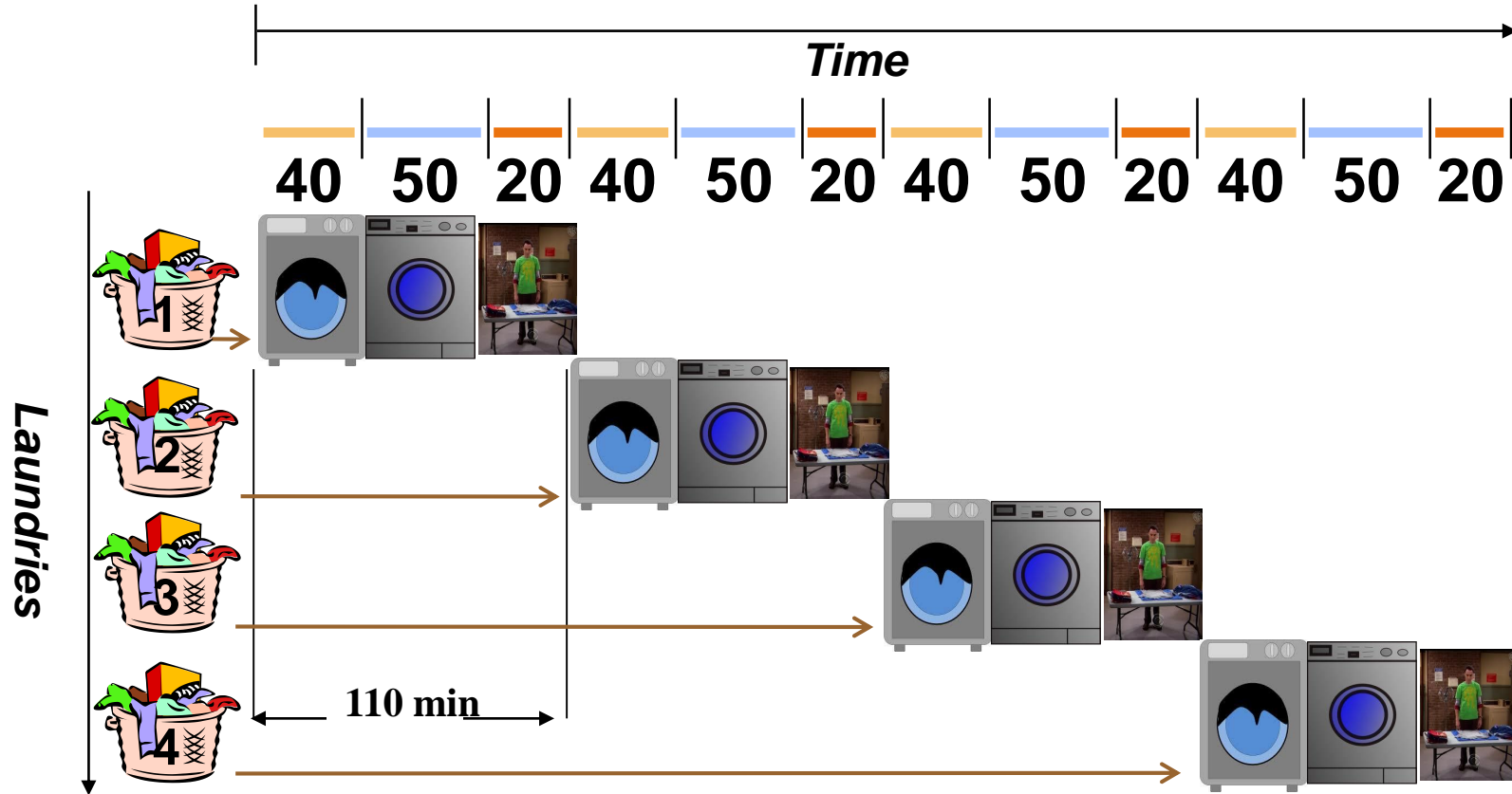

$$\begin{aligned} \text{Total} &= N * (\text{Washer} + \text{Dryer} + \text{Folder}) \\ &= \underline{\quad 440 \quad} \text{ mins} \end{aligned}$$



# If we pipelining

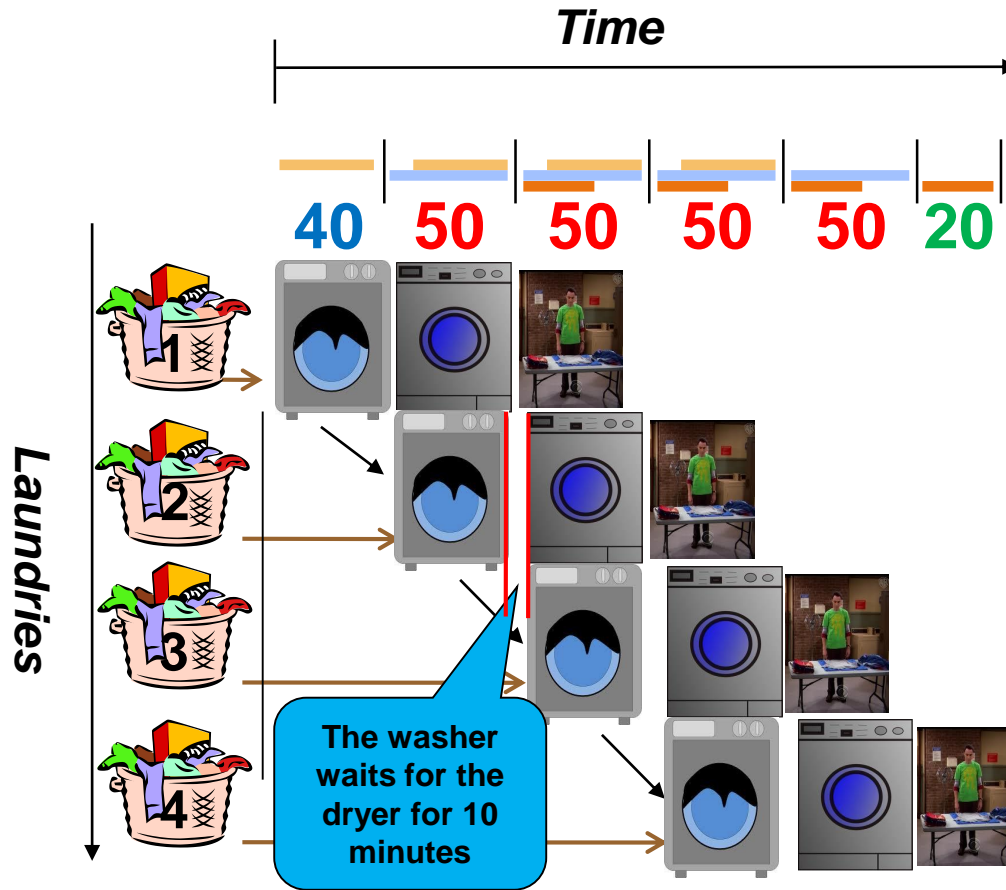


$$\text{Total} = \text{Washer} + N * \text{Max}(\text{Washer}, \text{Dryer}, \text{Folder}) + \text{Folder}$$

$$= \underline{\quad 260 \quad} \text{ mins}$$



# Pipeline Facts

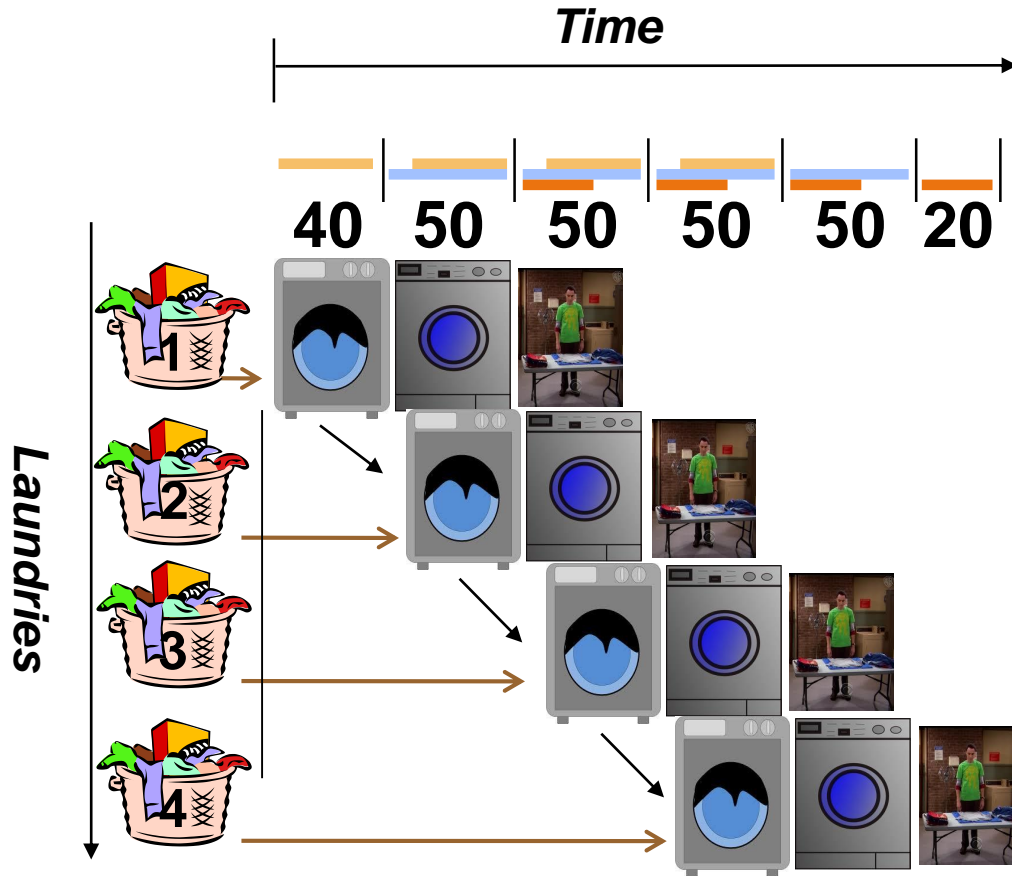

- Multiple tasks operating simultaneously
- Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- Pipeline rate limited by slowest pipeline stage**
- Unbalanced** lengths of pipe stages reduces speedup
- Potential speedup  $\propto$  **Number of pipe stages**




# Some definitions

# Very Important!

- **Latency**: The delay from when an input is established until the output associated with **that input** becomes valid.

(non-pipeline Laundry = 110 mins)

( pipeline Laundry = 120 mins)

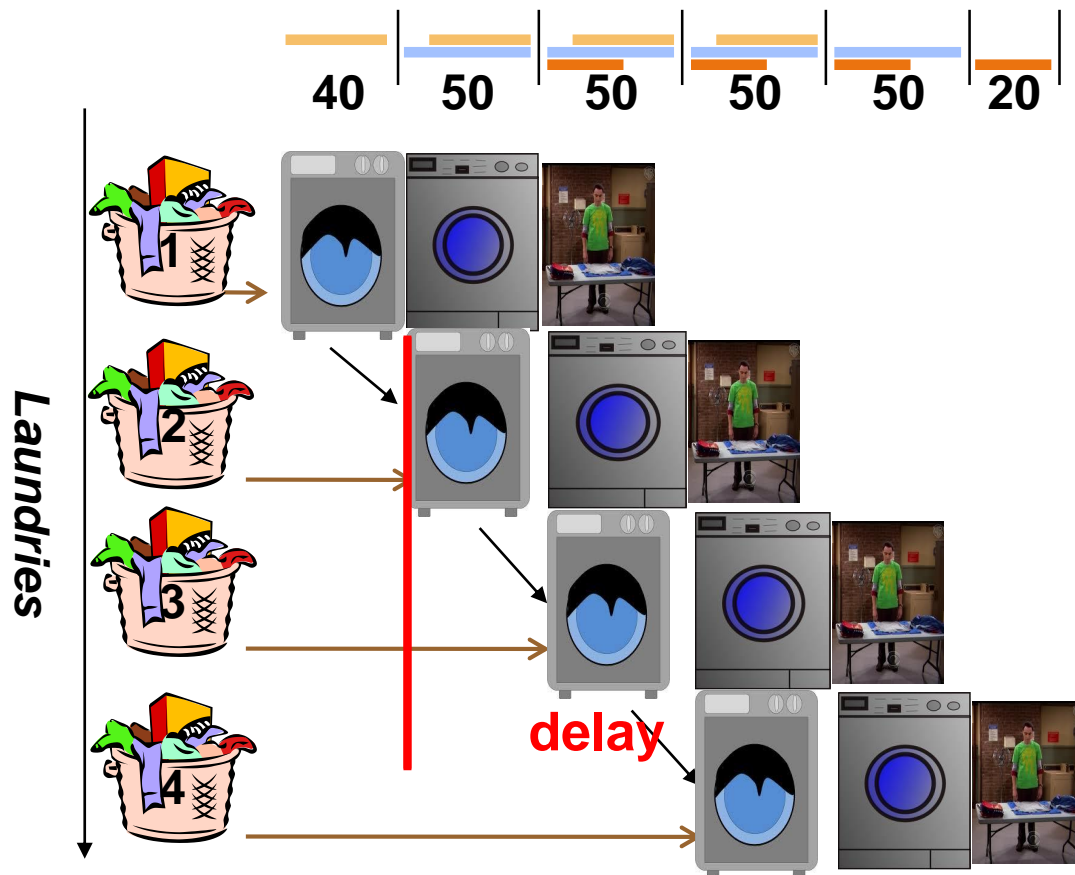


# Some definitions

# Very Important!

- **Throughput:** The rate of which **inputs** or **outputs** are processed or **how frequently** a laundry can be loaded

(non-pipeline Laundry =  $\frac{1}{110}$  outputs/min)

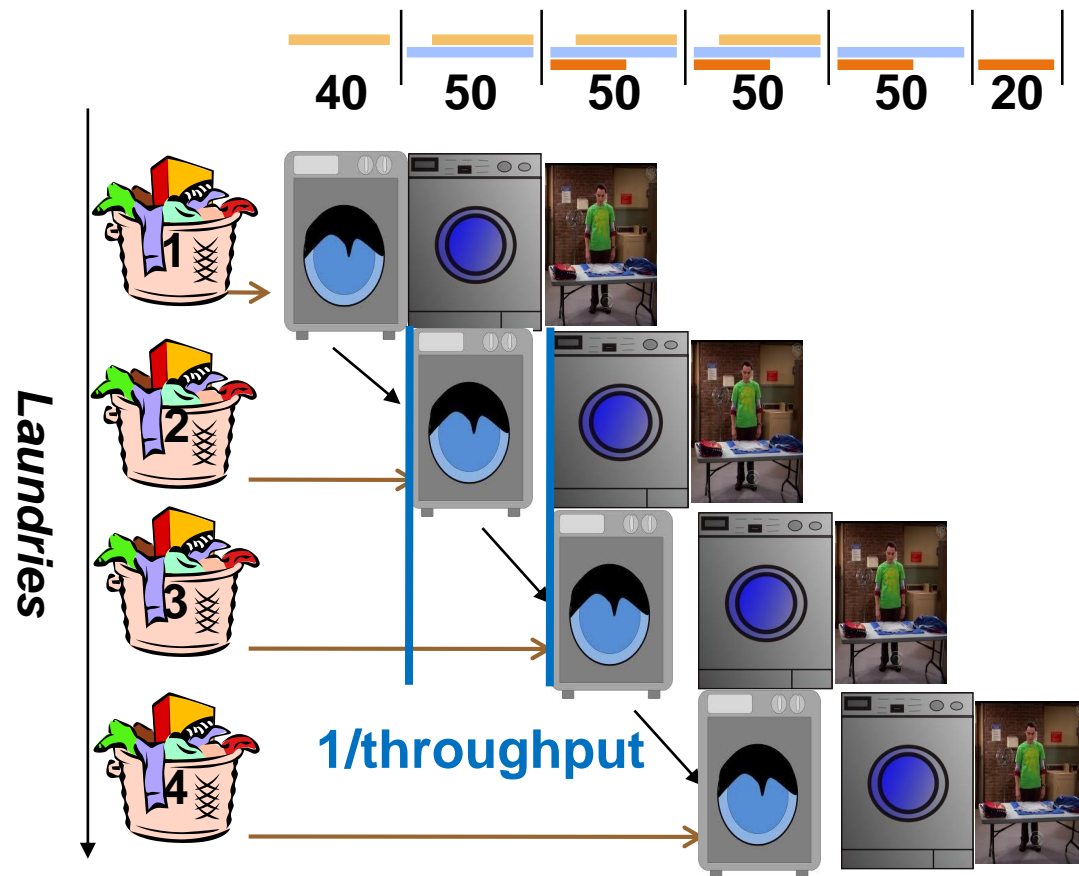(pipeline Laundry =  $\frac{1}{50}$  outputs/min)



# Combinational, Folding and Pipelined

## □ Combinational Circuits

- **Advantage:** low latency
- **Disadvantage:** low throughput, more hardware, low utilization

## □ Folding

- **Advantage:** less hardware, high utilization
- **Disadvantage:** high latency, limited application

## □ Pipeline

- **Advantage:** very high throughput
- **Disadvantages:** pipeline latency, more hardware



# Thanks!

