



LUND  
UNIVERSITY

# EITF35: Introduction to Structured VLSI Design

Part 2.2.2: VHDL-3

Liang Liu  
liang.liu@eit.lth.se



# Outline

- **Inference of Basic Storage Element**
- **Some Design Examples**
  - DFF with enable
  - Counter
- **Coding Style: Segment**
- **Variables in Sequential Circuit**
- **Poor Design Examples**




# Inference of Basic Storage Elements

## □ VHDL code should be clear so that the pre-designed cells can be inferred

- As an architecture designer, you need to be very familiar with the available elements
 
## □ VHDL code of storage elements


- Positive edge-triggered D FF
- Negative edge-triggered D FF
- D FF with asynchronous reset
- D Latch (***DON'T USE***)


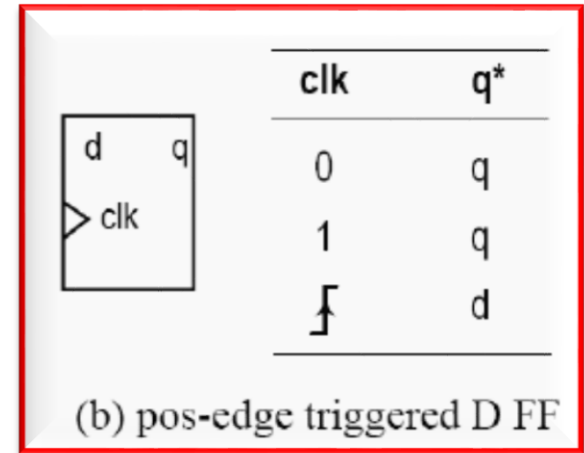
# Positive edge-Triggered D FF

- ❑ No else branch
- ❑ Note the sensitivity list (*only clk*)

```
library ieee;
use ieee.std_logic_1164.all;
entity dff is
  port(
    clk: in std_logic;
    d: in std_logic;
    q: out std_logic
  );
end dff;
architecture arch of dff is
begin
  process (clk)
  begin
    if (clk'event and clk='1') then
      q <= d;
    end if;
  end process;
end arch;
```




**rising\_edge(clk)**


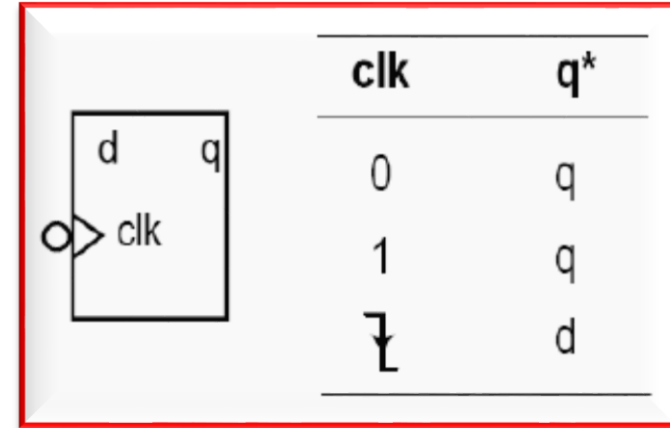
# Negative edge-Triggered D FF

```
library ieee;
use ieee.std_logic_1164.all;
entity dff is
  port(
    clk: in std_logic;
    d: in std_logic;
    q: out std_logic
  );
end dff;
architecture arch of dff is
begin
  process (clk)
  begin
    if (clk'event and clk='0') then
      q <= d;
    end if;
  end process;
end arch;
```





```
falling_edge(clk
)
```


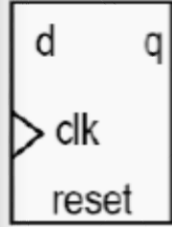
# D FF with Async. Reset

```
entity dffr is
  port(
    clk: in std_logic;
    reset: in std_logic;
    d: in std_logic;
    q: out std_logic
  );
end dffr;
architecture arch of dffr is
begin
  process (clk, reset)
  begin
    if (reset='1') then
      q <= '0';
    elsif (clk'event and clk='1') then
      q <= d;
    end if;
  end process;
end arch;
```



	reset	clk	q*
	1	-	0
	0	0	q
	0	1	q
	0		d




# D Latch (Learn How to Avoid)

```
Bad1:  
process (sA, sB, a, b)  
begin  
    if sA='1' then  
        z<=a;  
    elsif sB='1' then  
        z<=b;  
    end if;  
end process Bad1;
```

	c	q*
d	0	q
c	1	d
 
```
Bad2:  
process (sA, a, b)  
begin  
    if sA='1' then  
        f<=a;  
    end if;  
end process Bad2;
```



```
Bad3: process (I3, I2, I1, I0, S)  
begin -- use case statement  
    case S is  
        when "00" => O <= I0;  
        when "01" => O <= I1;  
        when "10" => O <= I2;  
    end case;  
end process Bad3;
```






# Exercise

```
c1: process (clk)
begin
  if (clk 'event
and clk = '1') then
    q <= '1';
  end if;
end process c1;
```

```
c2: process (clk)
begin
  if (clk
= '1') then
    q <= '1';
  end if;
end process c2;
```

```
c3: process (clk)
begin
  if (clk
= '1') then
    q <= '1';
  else
    q <= '0';
  end if;
end process c3;
```

What is the corresponding circuits?

   



# Outline

- Inference of Basic Storage Element
- **Some Design Examples**
  - DFF with enable
  - Counter
- Coding Style: Segment
- Variables in Sequential Circuit
- Poor Design Examples




# Design Examples: D FF with sync enable

## □ Sync Enable

- Means the enable signal is controlled by clock

reset	clk	en	q*
1	-	-	0
0	0	-	q
0	1	-	q
0	f	0	q
0	f	1	d

function

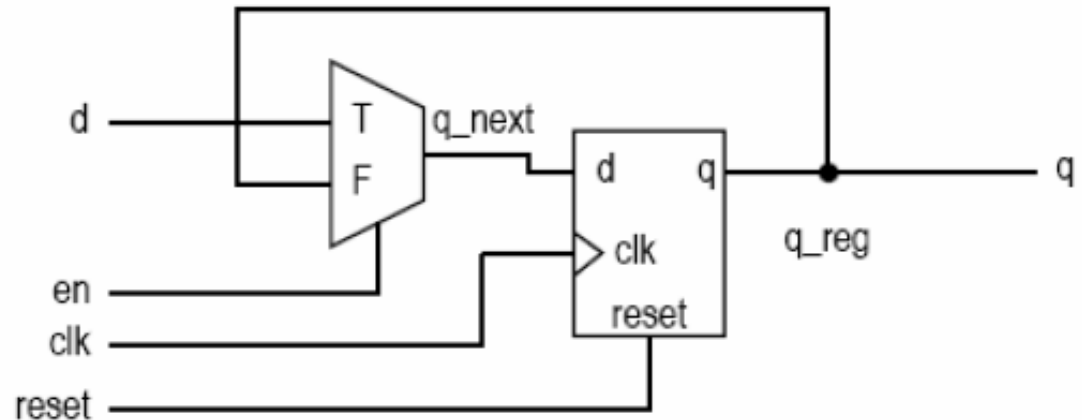

circuit



# Design Examples: D FF with sync enable

architecture two\_seg\_arch of dff\_en is

```
signal q_reg:std_logic;
```

```
signal q_next:std_logic;
```

```
begin
```

```
-- D FF
```

```
process (clk, reset)
```

```
begin
```

```
if (reset='1') then
```

```
q_reg <= '0';
```

```
elsif (clk'event and clk='1') then
```

```
q_reg <= q_next;
```

```
end if ;
```

```
end process;
```

```
-- next-state logic
```


```
q_next <= d when en ='1' else
```

```
q_reg;
```

```
-- output logic
```

```
q <= q_reg;
```

```
end two_seg_arch;
```

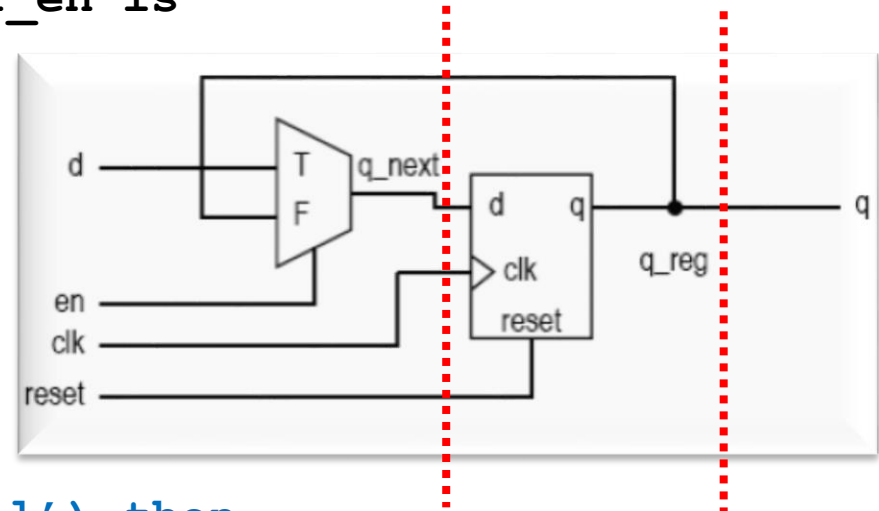


**Multi-Segment  
Recommended!**



# Design Examples: Binary Counter
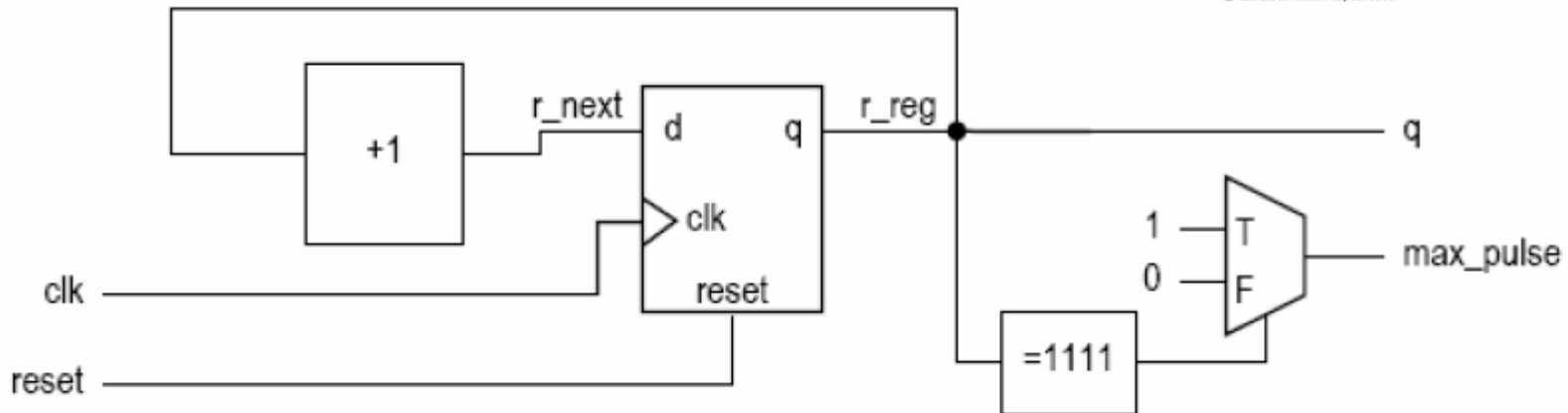
## Binary Counter

- Circulates through a sequence that resembles the unsigned binary number
- Count from 0 to 15 and repeat
- Set a flag when counting to 15



# Design Examples: Binary Counter

```
entity binary_counter4_pulse is
port( clk, reset: in std_logic;
max_pulse: out std_logic;
q: out std_logic_vector (3 downto 0) );
end binary_counter4_pulse ;
architecture two_seg_arch of binary_counter4_pulse is
signal r_reg : unsigned (3 downto 0) ;
signal r_next : unsigned (3 downto 0) ;
    process (clk, reset)
        begin
            if (reset='1') then r_reg <= ( others=> '0') ;
            elsif (clk'event and clk='1') then r_reg <= r_next;
            end if;
        end process;
    r_next <= r_reg + 1; -- incrementor
    q <= std_logic_vector(r_reg) ;
    max_pulse <= '1' when r_reg= "1111" else '0'; -- output
end two_seg_arch;
```



# Design Examples: Binary Counter

## □ How to wrap around: 1111->0000

- Poor code ('Wrong' code)

```
bad:r_next <= (r_reg + 1) mod 16
```

□ In the IEEE `numeric_std` package, "+" on the **unsigned** data type is modeled after a **hardware adder**

□ Wrap around **automatically** when the addition result exceeds the range.

□ **Mod** operation may cannot be synthesized

```
Good:r_next <= (r_reg + 1)
```

How to wrap if we count from 0 to 9?



# Outline

□ Inference of Basic Storage Element

□ Some Design Examples

- DFF with enable
- Register shifter
- Counter

□ **Coding Style: Segment**

□ Variables in Sequential Circuit

□ Poor Design Examples



# Coding Style: Segment

## □ One-segment

- Describe storage and combinational logic in one process
- May appear compact for certain simple circuit
- But it can be error-prone




*Is integration  
always better???*




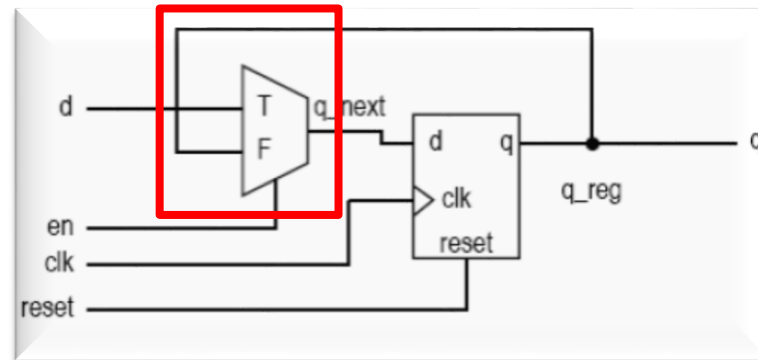
# Segment: D FF with sync enable

```
architecture one_seg_arch of dff_en is
begin
  process (clk,reset)
  begin
    if (reset='1') then
      q <= '0' ;
    elsif (clk'event and clk='1') then
      if (en='1') then
        q <= d;
      end if;
    end if ;
  end process;
end one_seg_arch;
```




# Segment: Binary Counter

```
architecture not_work_one_seg_glitch_arch
    of binary_counter4_pulse is
    signal r_reg: unsigned(3 downto 0);
begin
    process (clk, reset)
    begin
        if (reset='1') then
            r_reg <= (others=>'0');
        elsif (clk'event and clk='1') then
            r_reg <= r_reg + 1;
            if r_reg="1111" then
                max_pulse <= '1';
            else
                max_pulse <= '0';
            end if;
        end if;
    end process;
```

*What will be  
the circuit?*



# Segment: Binary Counter

 

- A 1-bit register is inferred for the `max_pulse` signal.
- The register works as a buffer and *delays the output by one clock cycle*,
- and thus the `max_pulse` signal will be asserted when `r_reg="0000"`.



# Segment: Summary

## □ Two-segment code


- Separate storage segment from the rest
- Has a clear mapping to hardware component
- *Is preferred and recommended*

## □ One-segment code

- Mix memory segment and next-state logic/output logic
- Can sometimes be more compact
- No clear hardware mapping
- Error prone



# Segment: Summary

 

□ Keep the *hardware and the corresponding coding rule* in mind and then go ahead!

- Signals inside the `clk'event` and `clk='1'` branch are referred as registers



# Outline

□ Inference of Basic Storage Element

□ Some Design Examples

- DFF with enable
- Register shifter
- Counter

□ Coding Style: Segment

□ **Variables in Sequential Circuit**

□ Poor Design Examples




# Variables in Sequential Circuit

- ❑ Signals **always imply an FF** under `clk'event` and `clk='1'` condition
- ❑ When you don't want to infer an FF in a **one-segment** process
- ❑ Variable is **local** in a process and is not needed outside
- ❑ Variable may imply differently
  - Variable is used **after** it is assigned: get a value every time when the process is invoked
    - ❑ ***no register is inferred***
  - Variable is used **before** it is assigned: use the value from the previous process execution
    - ❑ ***FF or register need to be inferred***


 
# Variables in Sequential Circuit: Example

```
architecture arch of variable_ff_demo is
  signal tmp_sig1: std_logic;
begin
  process (clk)
  begin
    if (clk'event and clk='1') then
      tmp_sig1 <= a and b;
      q1 <= tmp_sig1;
    end if ;
  end process;
end architecture;
```



- Registers are inferred
- $q1$  is one clock later than  $tmp\_sig1$





# Variables in Sequential Circuit: Example

architecture arch of variable\_ff\_demo is

begin

```
process (clk)
```

```
    variable tmp_var2: std_logic; -- declare in process
```

```
begin
```


```
    if (clk'event and clk='1') then
```

```
        tmp_var2 := a and b; -- notice assignment format
```

```
        q1 <= tmp_var2;
```

```
    end if ;
```

```
end process;
```

 

□ Use variable

□ *tmp\_sig2* is used after it is assigned

□ Just a hard wire, no Reg. is inferred



# Variables in Sequential Circuit: Example

architecture arch of variable\_ff\_demo is

begin

  process (clk)

    variable tmp\_var2: std\_logic; -- declare in process

  begin


    if (clk'event and clk='1') then

      q1 <= tmp\_var2;

      tmp\_var2 := a and b; -- change the assignment order

    end if ;

  end process;

 

**2min: Draw the corresponding circuits**

**No Variables!**



# Outline

## □ Inference of Basic Storage Element

## □ Some Design Examples

- DFF with enable
- Register shifter
- Counter

## □ Coding Style: Segment


## □ Variables in Sequential Circuit

## □ Poor Design Examples



# Poor Design 1: Misuse of asynchronous reset

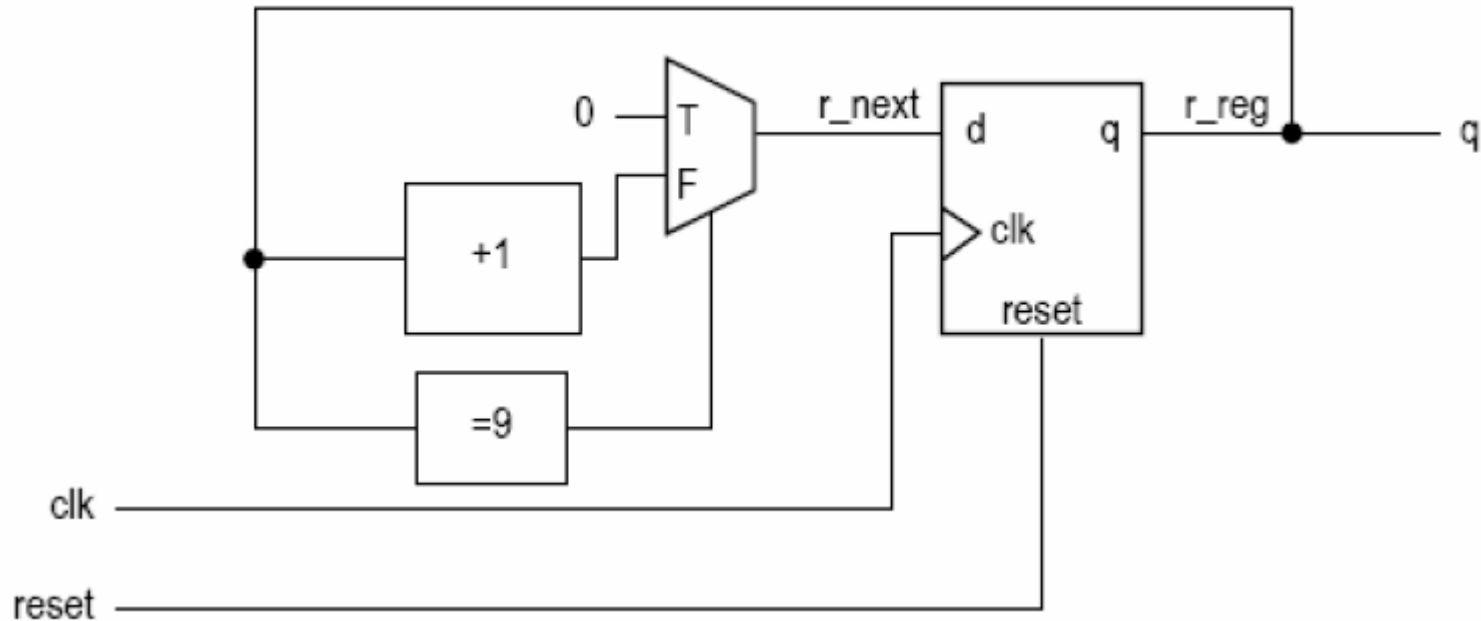Example: a mod-10 counter: 0,1,2 ...,7,8,9, 0,1,2..., 7,8,9,0



How to wrap from 9 to 0?





# Poor Design 1: Misuse of asynchronous reset

```
entity mod10_counter is
  port(clk,reset: in std_logic; q:out std_logic_vector (3 downto 0));
end mod10_counter;
architecture poor_async_arch of mod10_counter is
  signal r_reg: unsigned (3 downto 0) ;
  signal r_next: unsigned (3 downto 0) ;
  signal async_clr: std_logic;
begin
  process (clk,async_clr)
    begin
      if (async_clr='1') then
        r_reg <= (others=>'0');
      elsif(clk'event and clk='1') then
        r_reg<=r_next;
      end if ;
    end process;
    async_clr <='1' when (reset='1' or r_reg="1010") else '0';
    r_next <= r_reg + 1;
    q <= std_logic_vector(r_reg);
  end poor_async_arch;
```



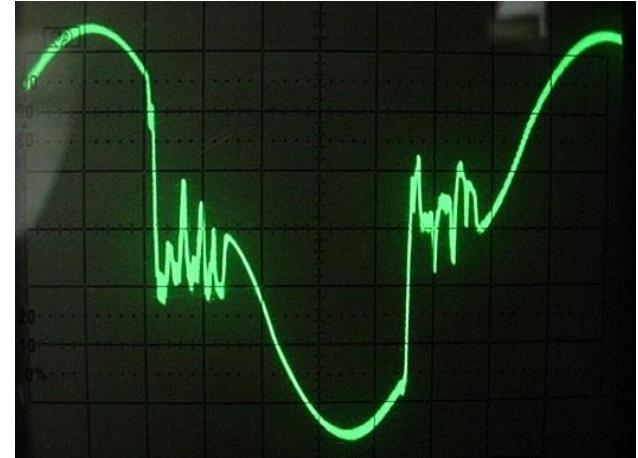 
# Poor Design 1: Misuse of asynchronous reset


 
## Problems

- Glitch in counter: r\_req goes to 10 and then reset, due to the delay of comparator
- **Glitches** in aync\_clr can reset the counter mistakenly



# Poor Design 1: Misuse of asynchronous reset

## □ Remedy

architecture two\_seg of mod10\_counter is

```
signal r_reg: unsigned (3 downto 0) ;
```

```
signal r_next: unsigned (3 downto 0) ;
```

```
begin
```

```
  process (clk, reset)
```

```
  begin
```

```
    if (reset = '1') then r_reg <= (others=>'0');
```

```
    elsif (clk'event and clk='1') then r_reg<=r_next;
```

```
  end if ;
```


```
end process;
```

```
r_next <= (others=>'0') when (r_reg=9) else r_reg+1;
```

```
q <= std_logic_vector(r_reg);
```

```
end two_seg;
```

 **asynchronous reset should  
ONLY be used for initialization!**



# Something to remember

- ❑ Strictly follow the synchronous design methodology; i.e., all registers in a system should be ***synchronized by a common global clock signal*** (otherwise special circuits are needed)
- ❑ The memory components should be coded clearly so that a predesigned cell can be ***inferred from the device library***.
- ❑ Isolate the memory components from the VHDL description and code them in a ***separate segment***. One-segment coding style is not advisable.
- ❑ ***Asynchronous reset***, if used, should be only for system initialization. It should not be used to clear the registers during regular operation
- ❑ Unless there is a compelling reason, a ***variable should not be used*** to infer a memory component.





# Reading advice

**RTL Hardware Design Using VHDL: P213-P254**



# Thanks

