



LUND
UNIVERSITY

EITF35: Introduction to Structured VLSI Design

Part 3.2.1: Memories & Advanced Timing

Liang Liu
liang.liu@eit.lth.se



Outline

□ Overview of Memory

- Application, history, trend
- Different memory type
- Overall architecture


□ Registers as Storage Element

- Register File
- FIFO

□ Xilinx Storage Elements




Memory is Everywhere

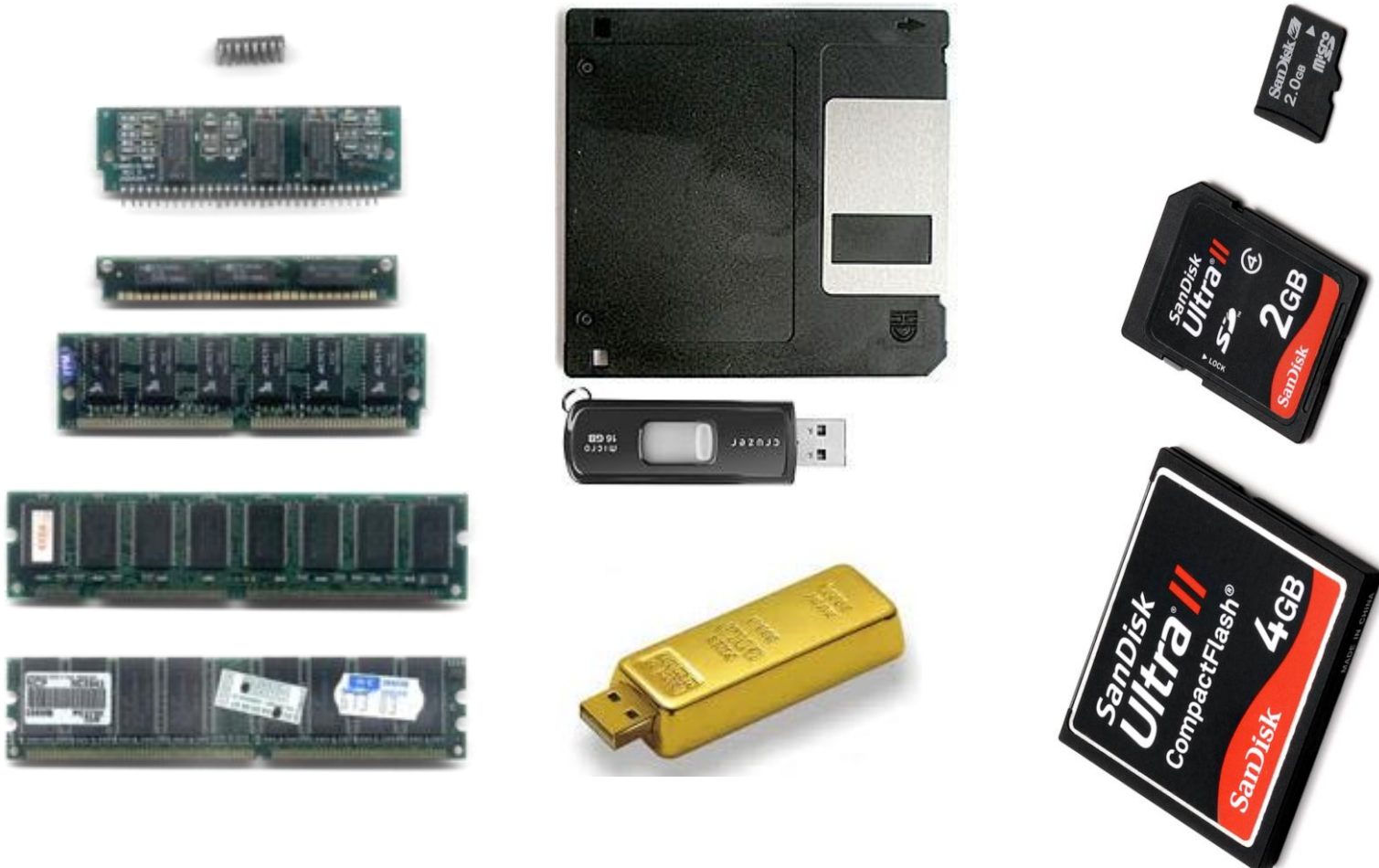

Memory Wafer Shipments Forecast

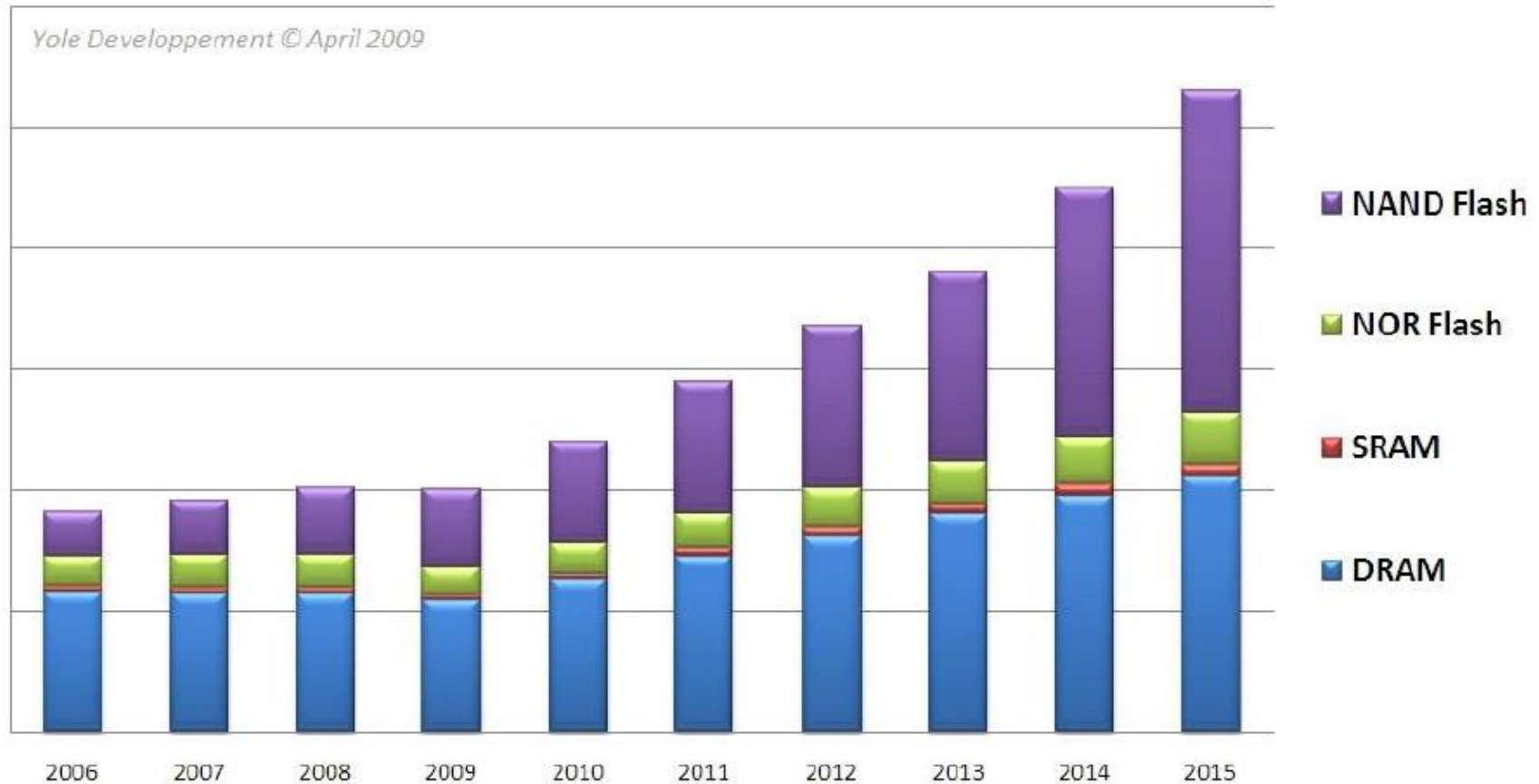Overall Memory wafer shipments forecast (12" eq. wspy)



Faster-Than-Moore?

Bits shipped routinely doubles-to-triples year-over-year



Memory Size



*In 1991, a 65MegaByte
Seagate hard disk
storage cost around
\$350*



**Seagate Barracuda 1 TB HDD SA
Drive ST1000DM003** by Seagate

~~\$114.99~~ **\$52.92** ✓Prime

Get it by **Monday, Aug 11**

More Buying Choices

\$47.00 new (102 offers)

\$42.00 used (20 offers)




\$5,595,000 USD


Los Angeles (City), CA
United States



Bandwidth

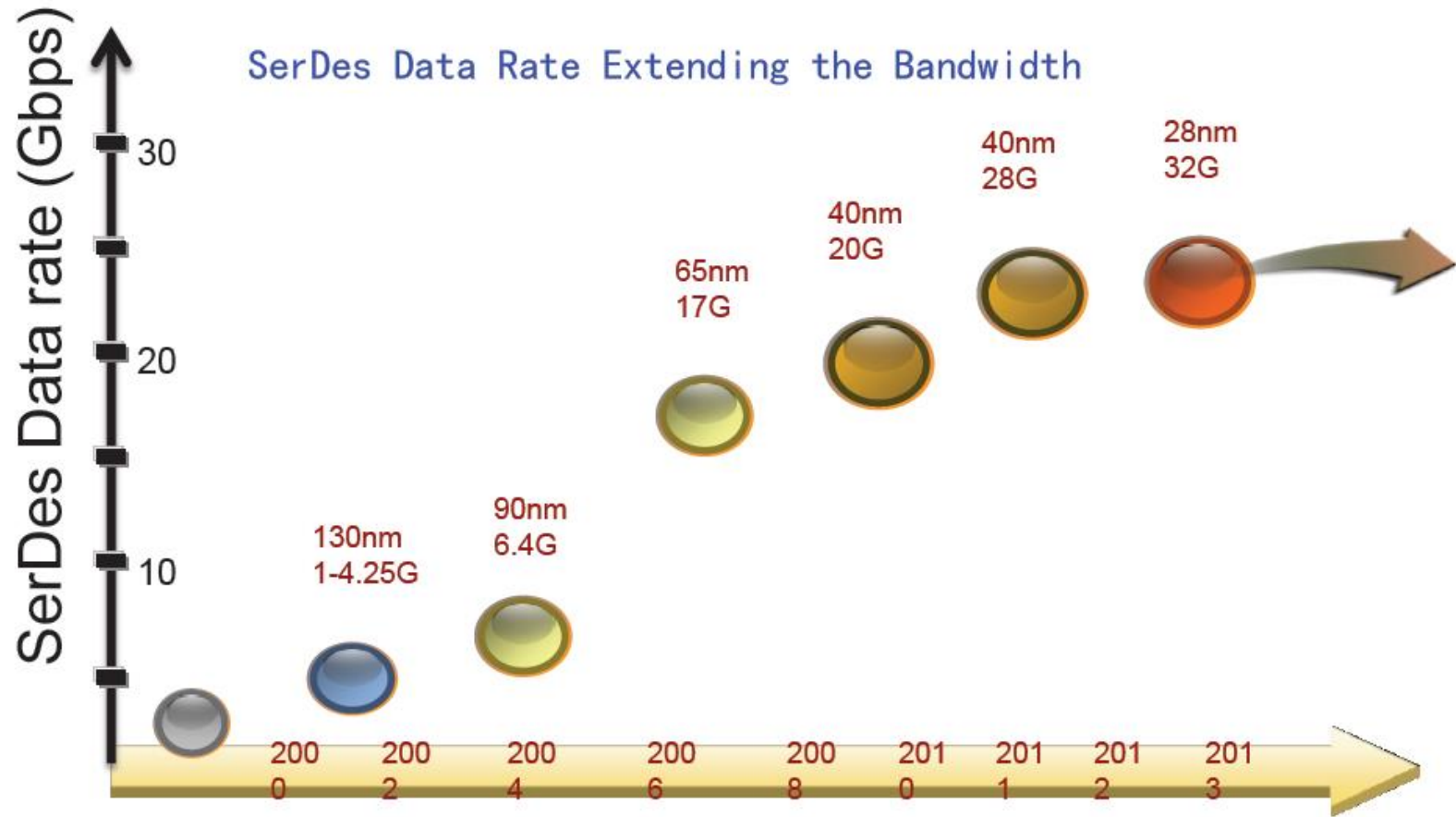

Bandwidth (cont'd.)

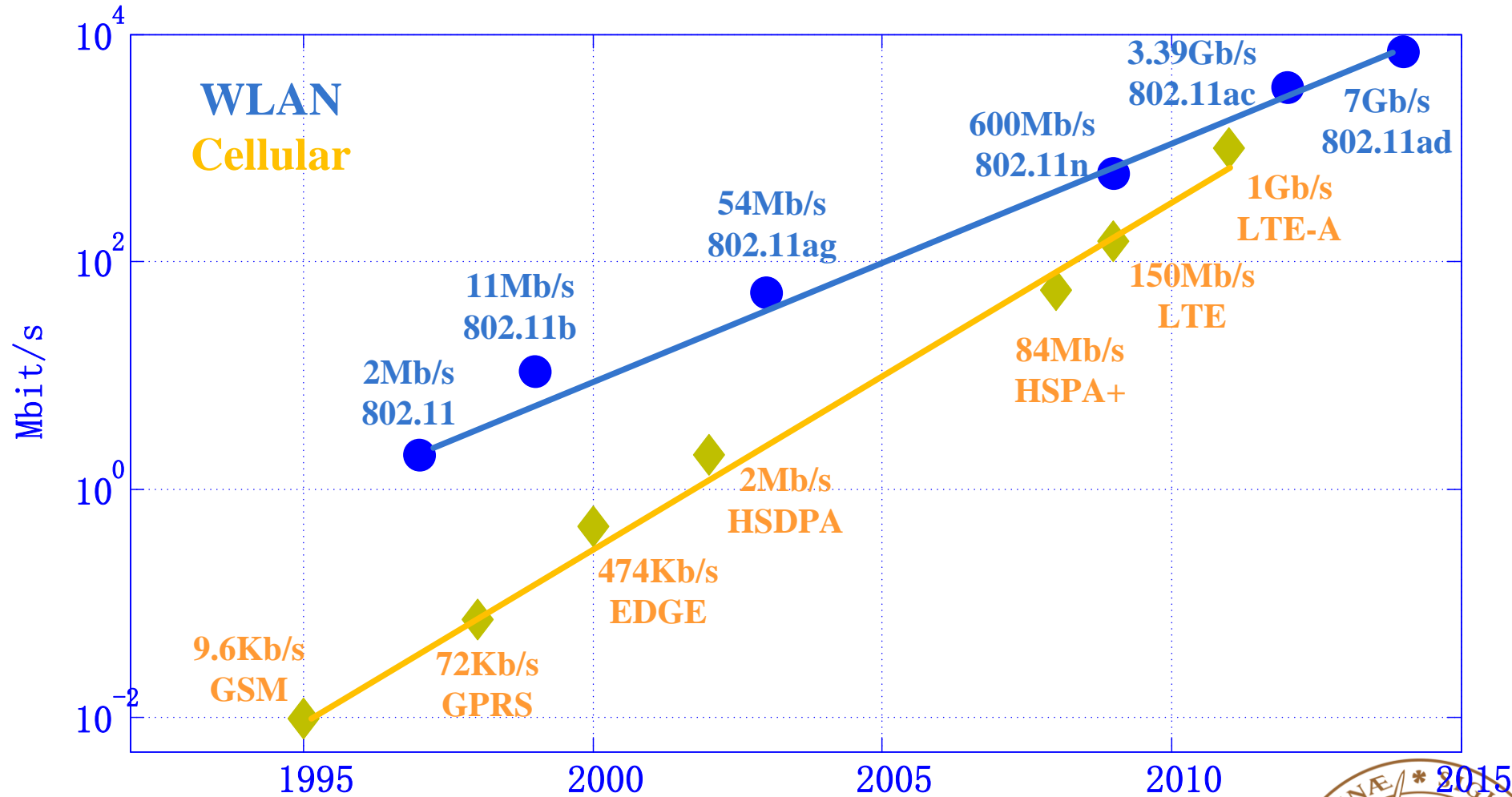

Memory Bandwidth: 1TB/s by 2017




2015


Memories, on chip

- ❑ **Power** and **Bandwidth** becomes bottleneck
- ❑ Everything is pointing to more and more “local” memory/storage at the device level

Nvidia Tegra 2

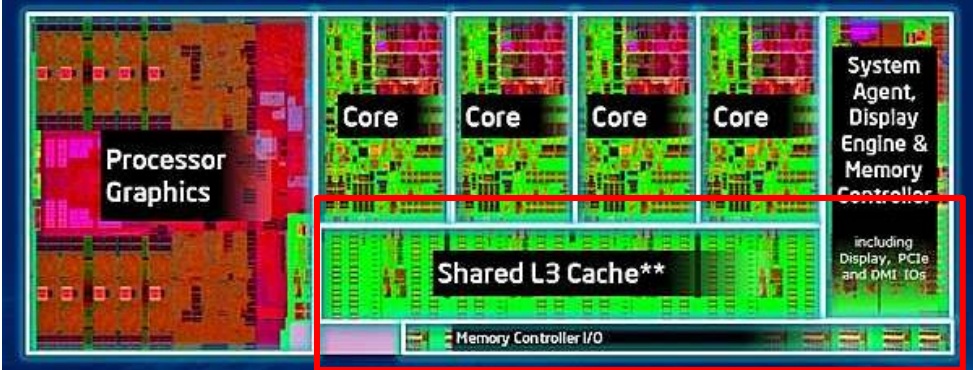

Intel Haswell


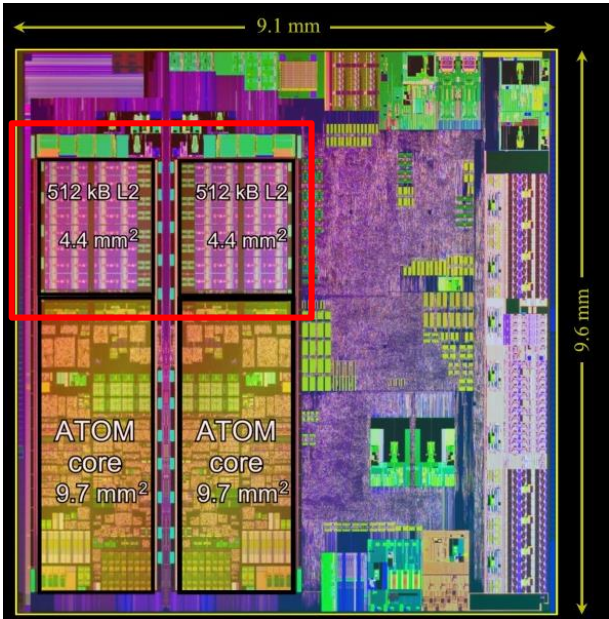


Intel ATOM




Memories, on chip

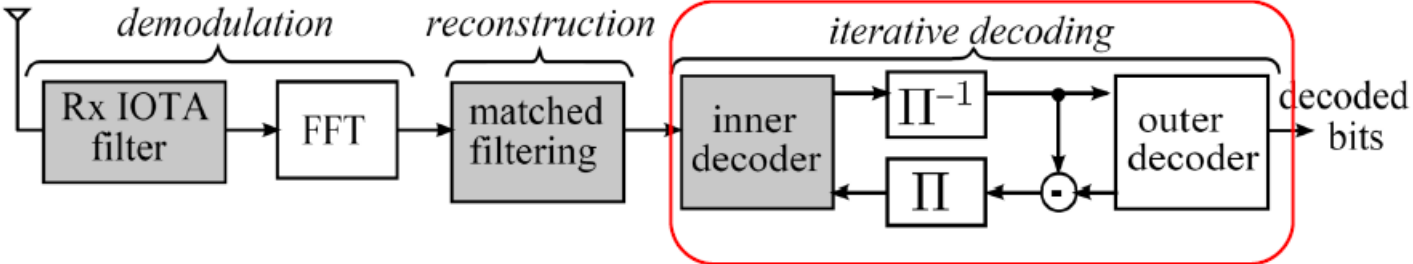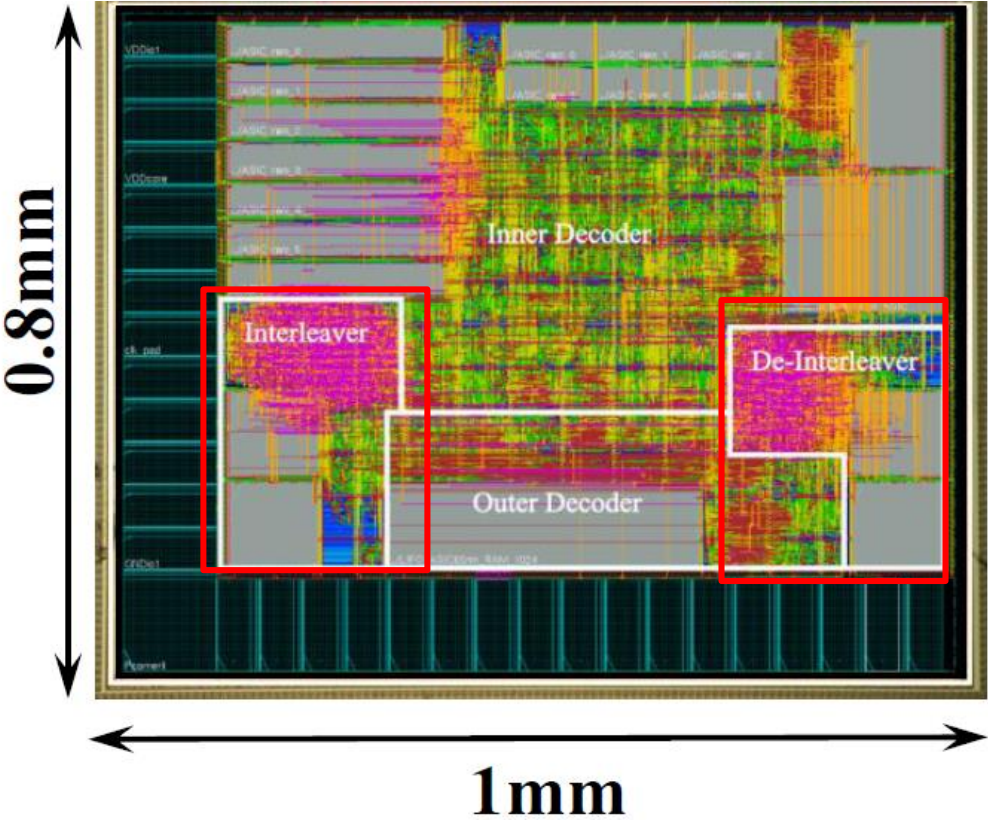One of our chip for wireless communication system (iterative decoder+interleaver)




Memories, History

□ First Storage?

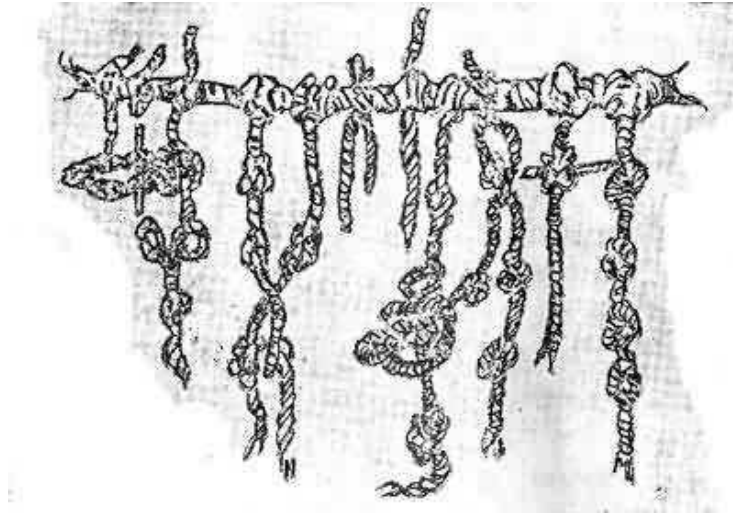

□ Early Memory

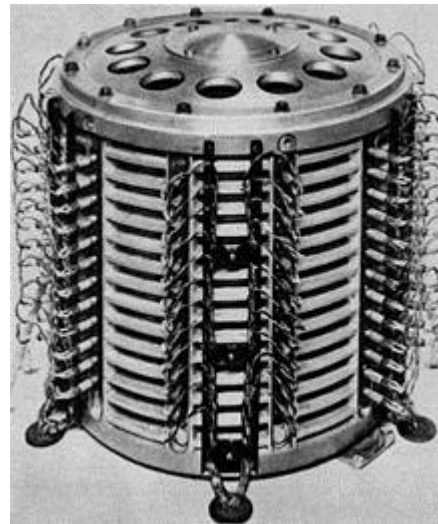- Drum memory: magnetic data storage device.
- Gustav Tauschek (1932)
- Widely used in the 1950s and into the 1960s as computer memory




Memory, current state

□ Yesterday:

- RAM memories are historically driven by computing applications
- NOR/NAND Flash is used in most of consumer devices (cell-phone, digital camera, USB stick ...)


□ Today:

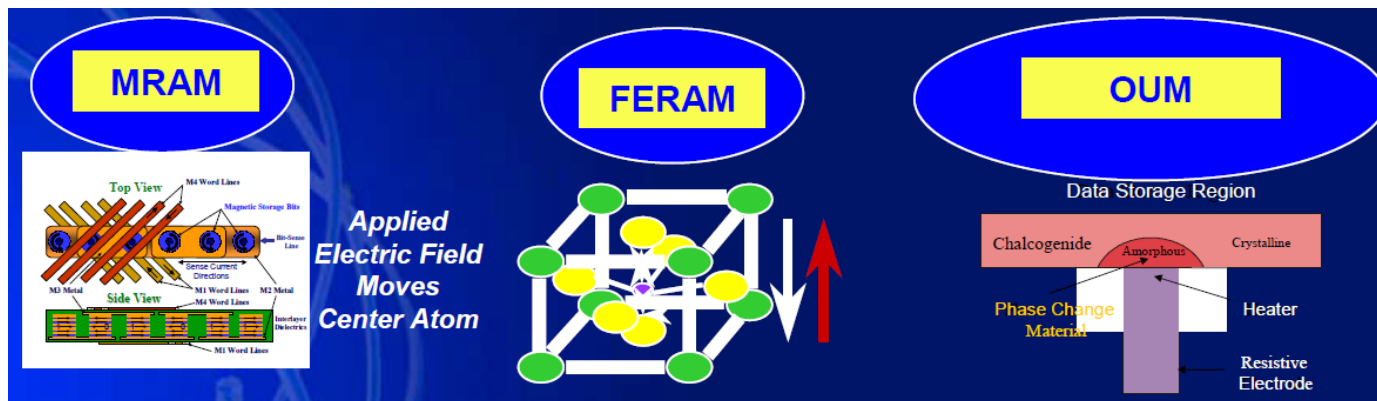- New generation memories
 - PRAM, FeRAM, MRAM..
- “Solid State” memory is the killer application for NAND Flash in volume:
 - SSDs to replace HDD (hard disk magnetic drives)
- RAM (SRAM / DRAM)
 - DDR3 / DDR4 / GDDR5/GDDR6



Memory, leading the semiconductor tech.

NAND Memory Product Roadmap

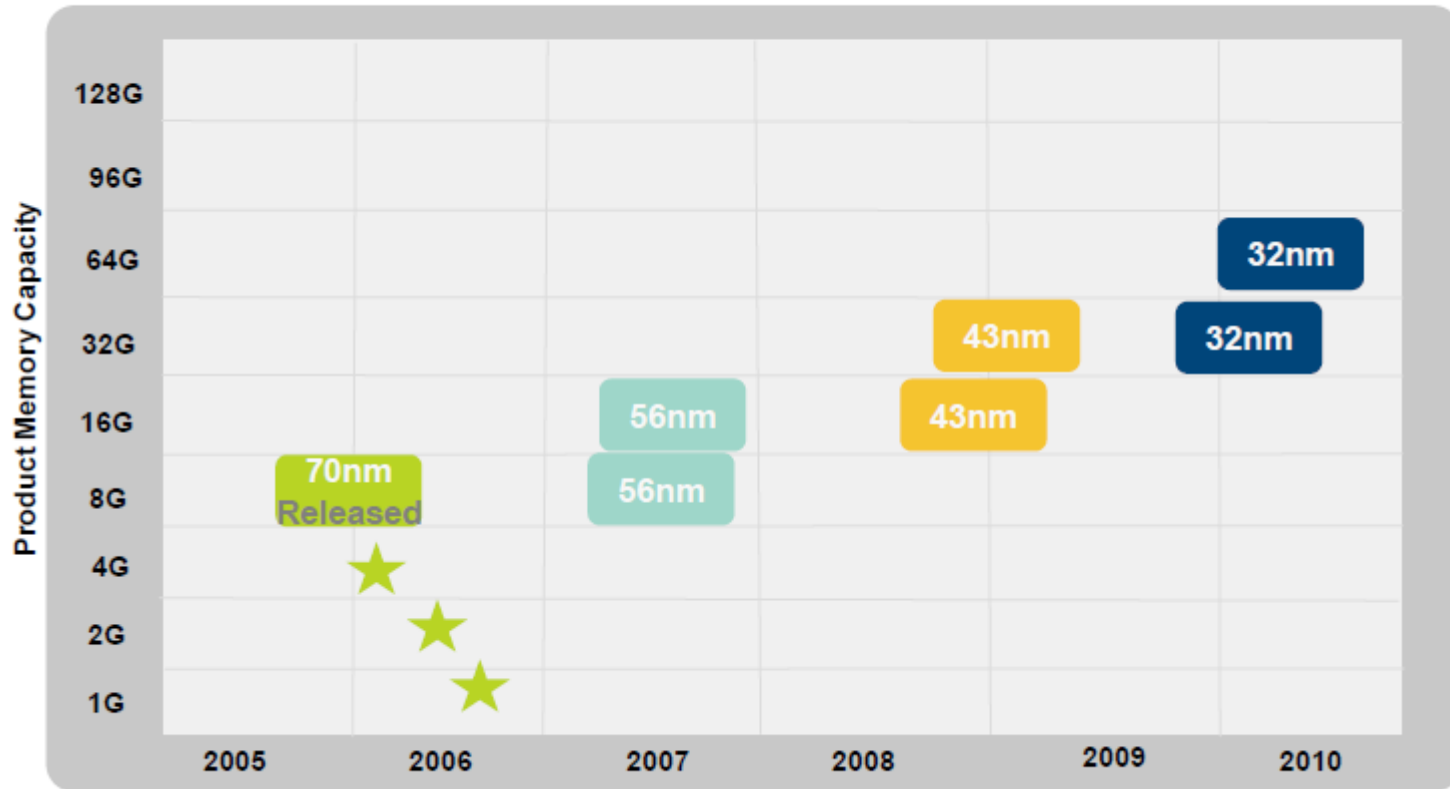


Source: SanDisk

First 32nm NAND Flash memory, **2009**, Toshiba


First 32nm CPU released, **2010**, Intel Core i3



Memory, leading the semiconductor tech.

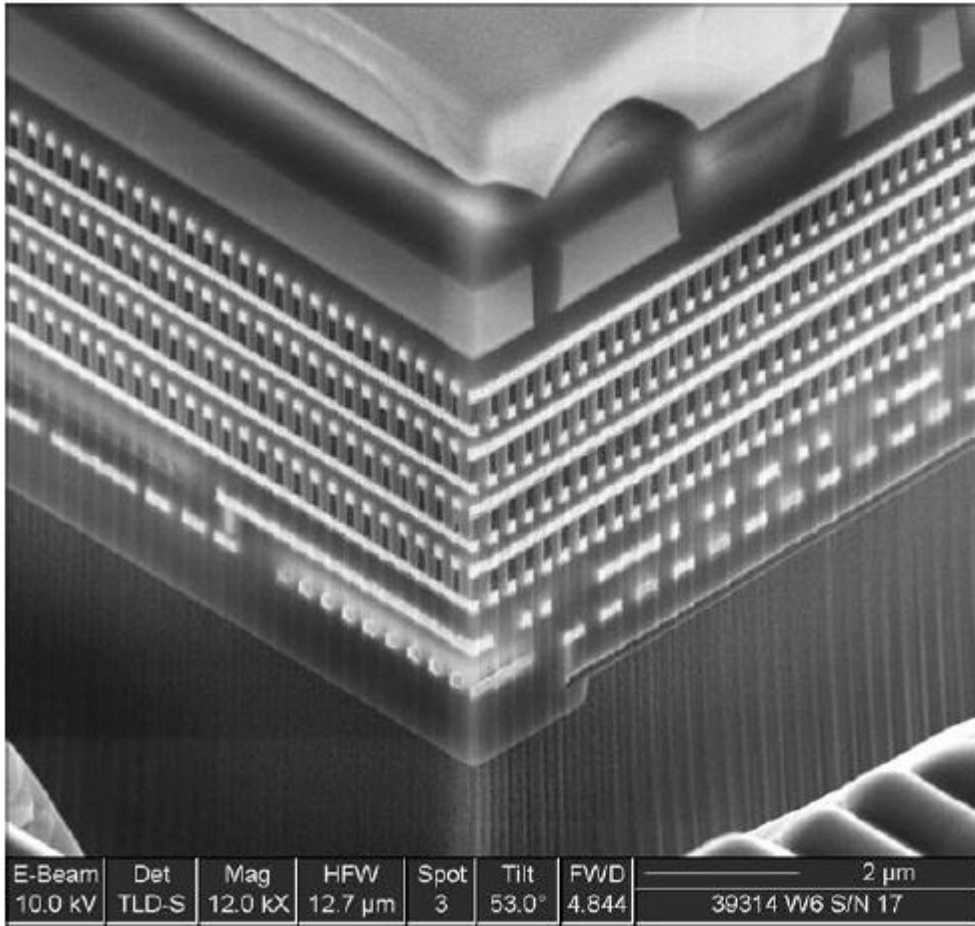

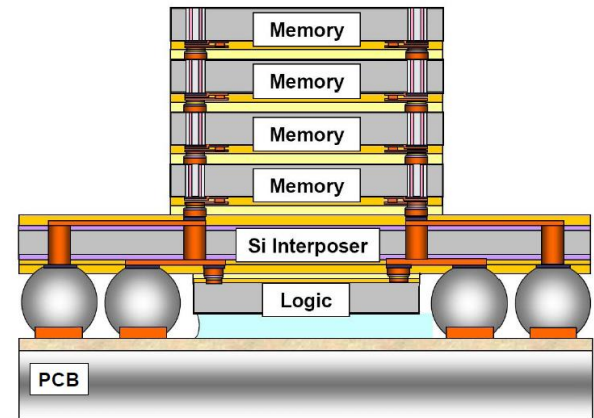- Al top metal
- 4 layers of memory cells + tungsten interconnect
- 2 levels of tungsten routing
- LV + HV CMOS logic



Example of 3-D integrated construction (Image courtesy of DuPont Electronics)


First 22-nm SRAMs using Tri-Gate transistors, in Sept. **2009**
First 22-nm Tri-Gate microprocessor (Ivy Bridge), released in **2013**



3D Processors for Massive Parallel Computing

Centip3De: University of Michigan

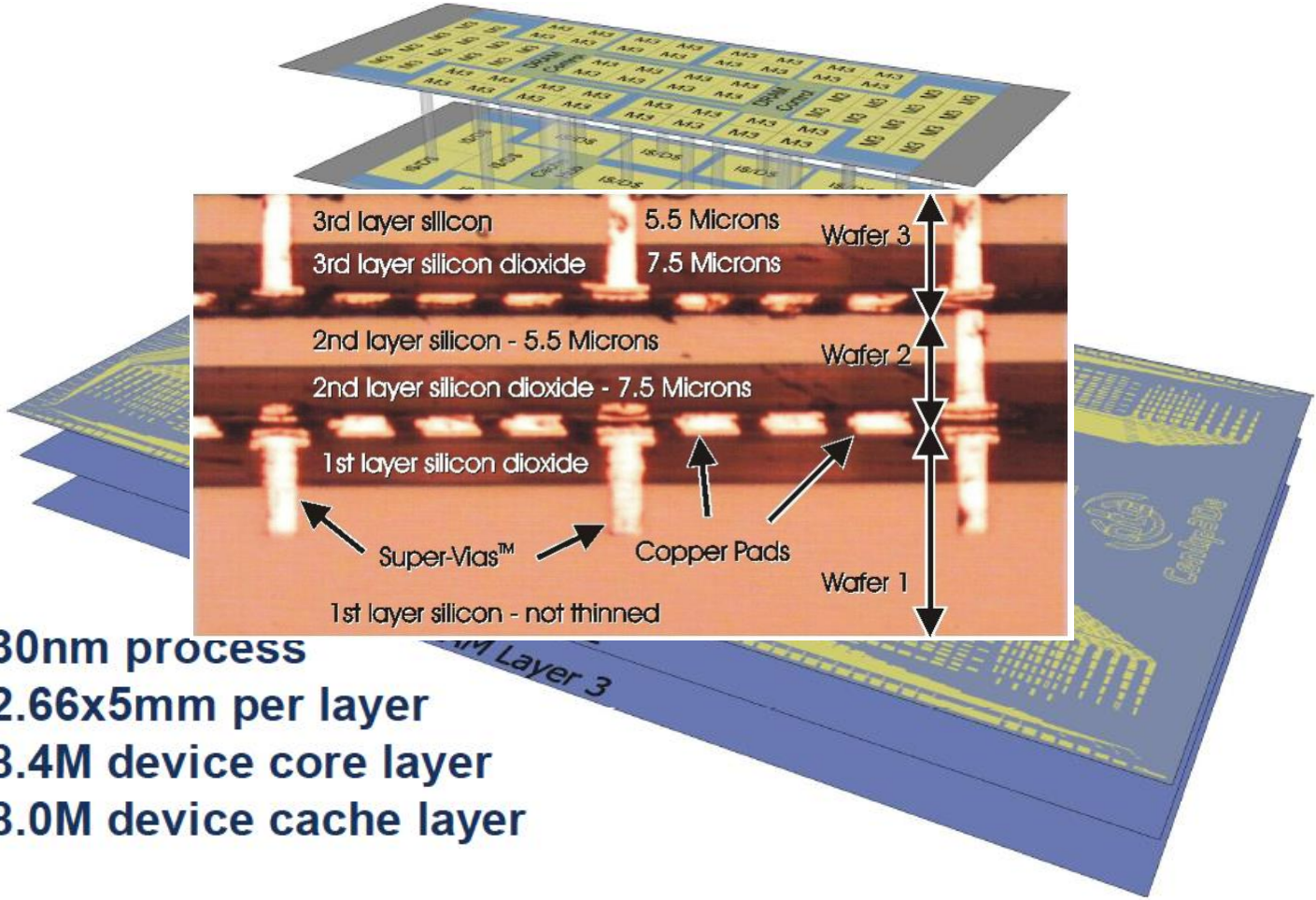


- Configurable 3D stacked system with 64 ARM Cortex-M3 cores
- 7-layer system (2 core layers, 2 cache layers, 3 DRAM layers)



130nm process
12.66x5mm per layer
28.4M device core layer
18.0M device cache layer




Memory Classification

Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E²PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM		
			



Memory Classification

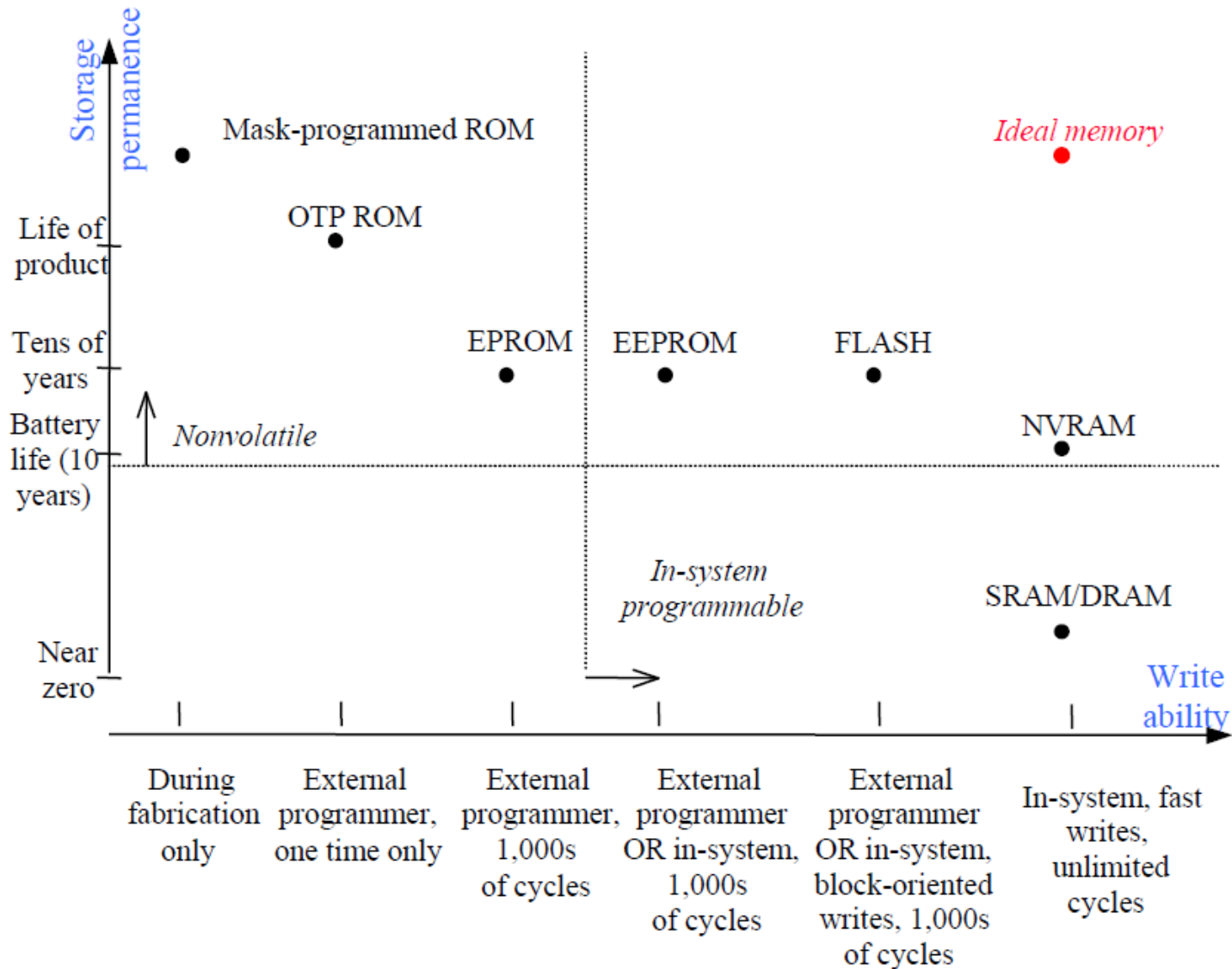


Picture from *Embedded Systems Design: A Unified Hardware/Software Introduction*



Memory Hierarchy

Speed (ns):	.1's	1's	10's	100's	1,000's
Size (bytes):	100's	K's	10K's	M's	T's
Cost:	highest				lowest

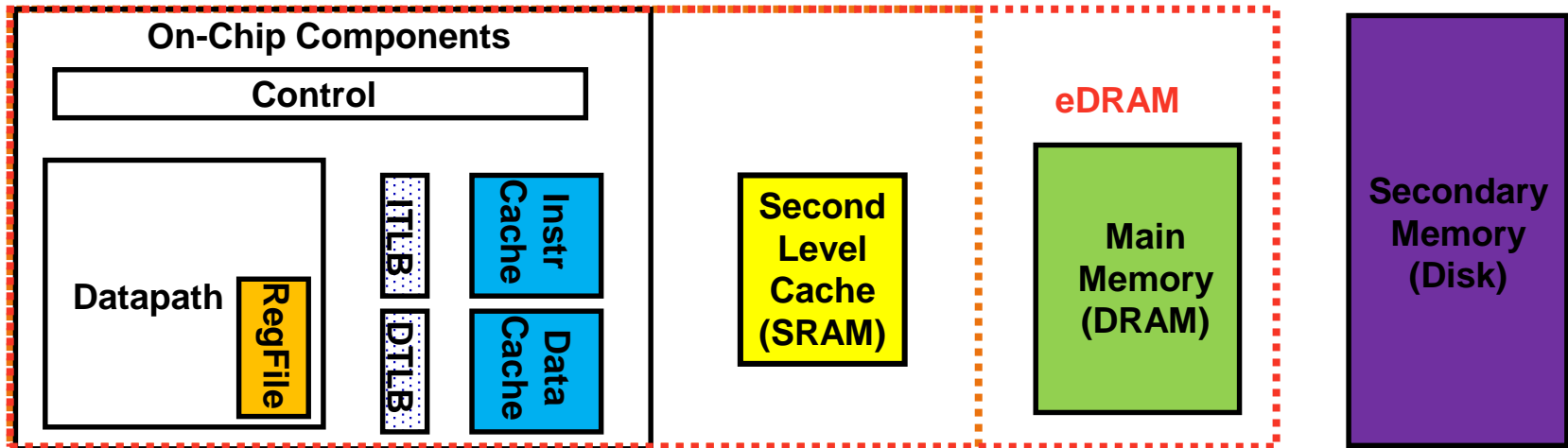

Heterogeneous is important

The concept of "most suitable"





Memory Basic Concept

□ Stores large number of bits

- $m \times n$: m words of n bits each
- $k = \text{Log}_2(m)$ address input signals
- or $m = 2^k$ words
- e.g., 4096 x 8 memory:
 - 32,768 bits
 - 12 address input signals
 - 8 input/output data signals

□ Memory access

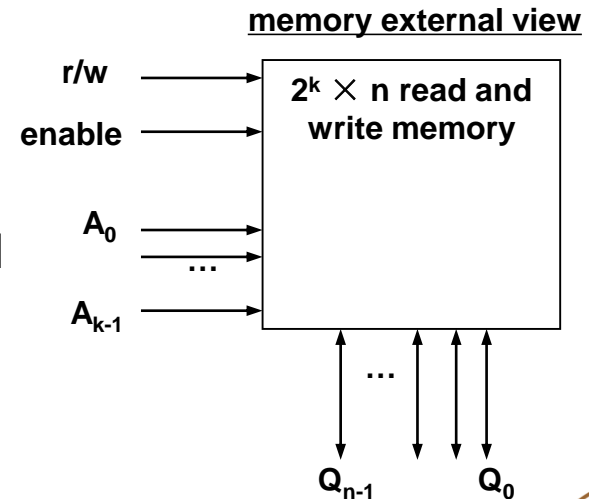
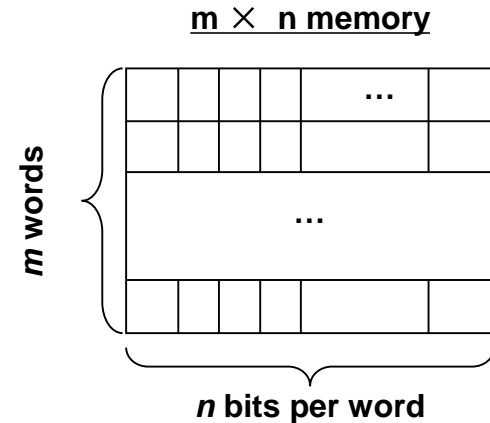
- r/w: selects read or write
- enable: read or write only when asserted
- Address
- Data-port



We stay at higher-level, gate-level view of memory will be taught at Digital IC Design



Memory Architecture

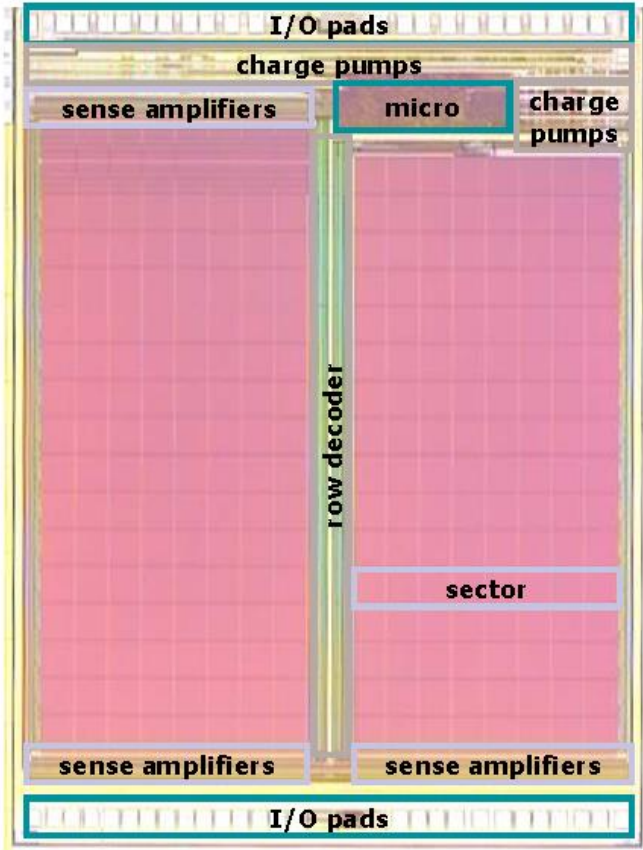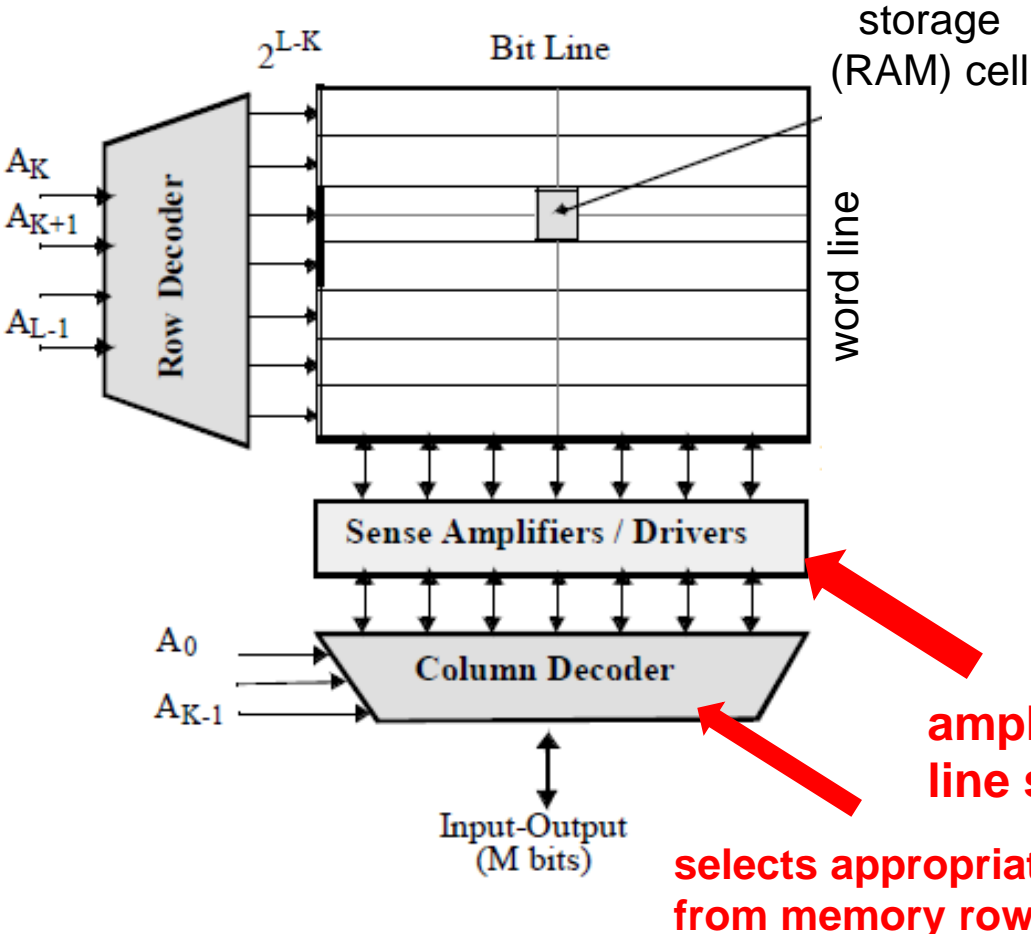

Outline

□ Overview of Memory

- Application, history, trend
- Different memory type
- Overall architecture

□ Registers as Storage Element

- Register File
- FIFO



□ Xilinx Storage Elements



Storage Examples 1

□ Register File

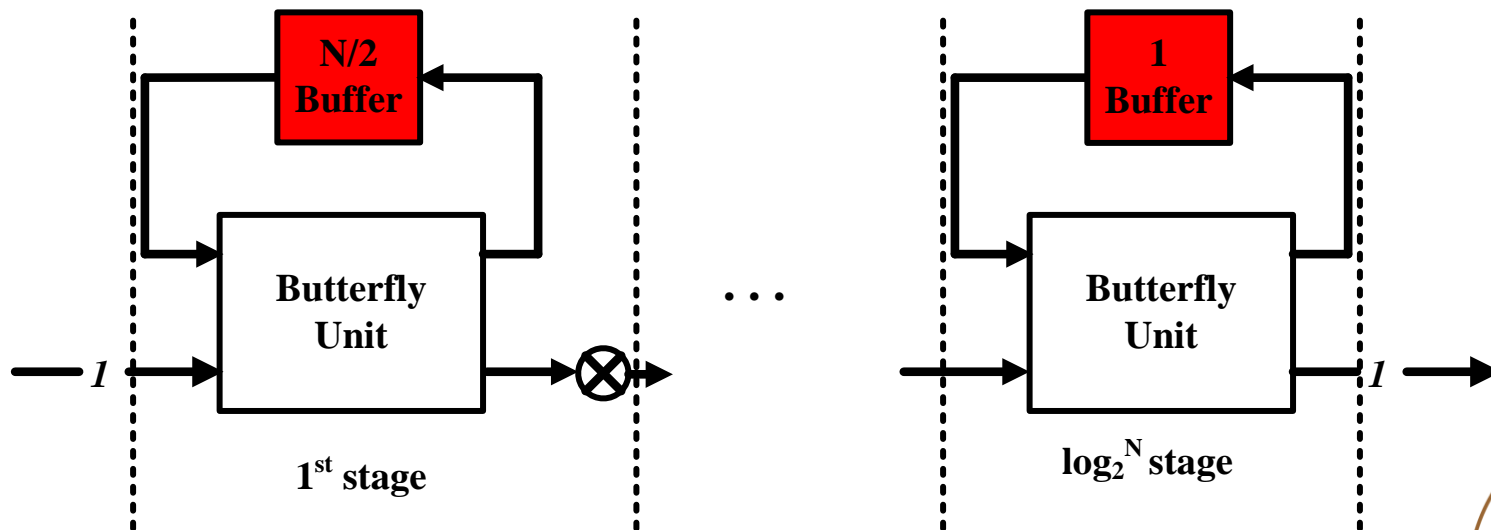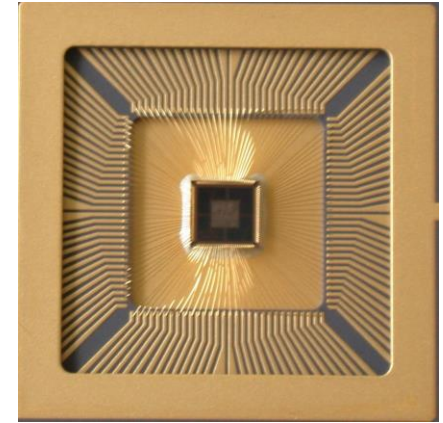- Used as *fast temporary* storage
- Registers arranged as *array*
- Each register is identified with an address
- Normally has 1 write port (with write enable signal)
- Can has multiple read ports



Register File

□ **Example:** 4-word register file with 1 write port and two read ports

□ **Register array:**


- 4*16bit registers
- Each register has an enable signal

□ **Write decoding circuit:**

- 0000 if wr_en is 0
- 1 bit asserted according to w_addr if wr_en is 1

□ **Read circuit:**

- A mux for each read port

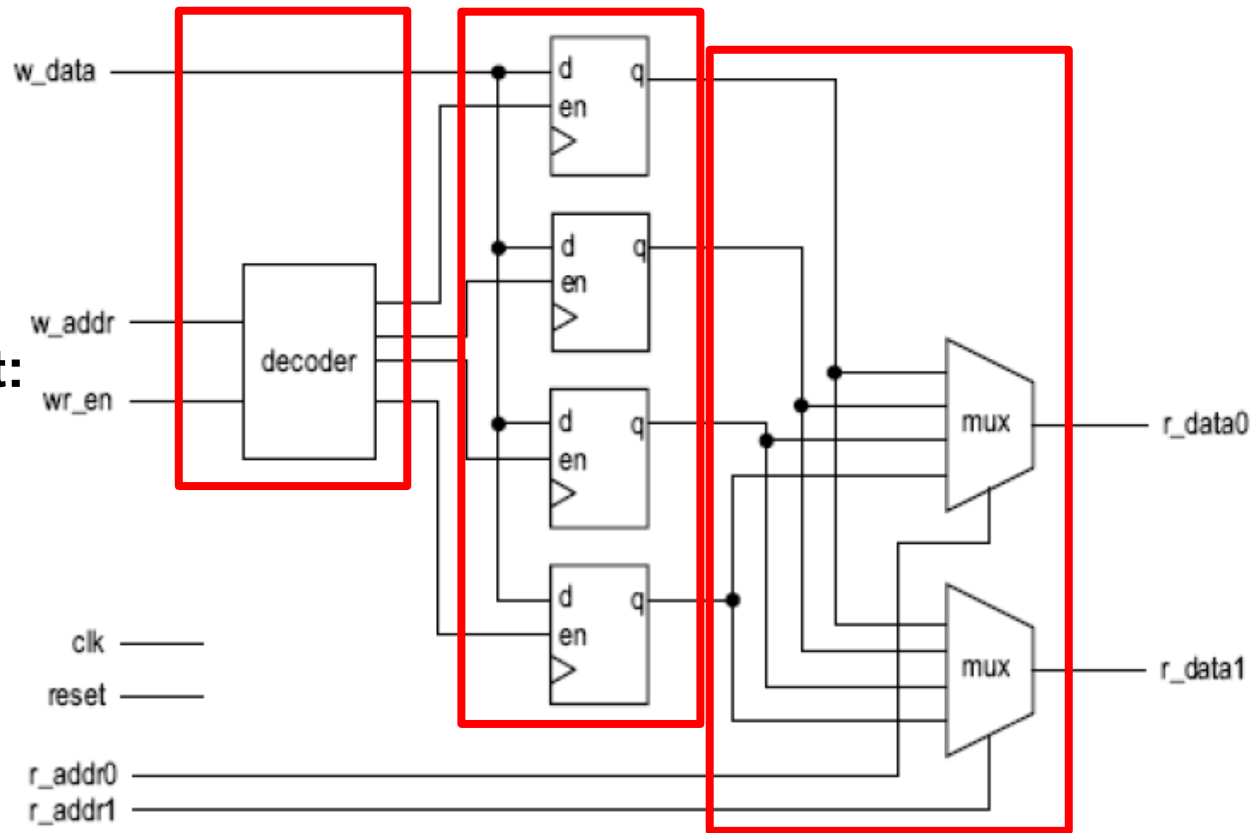

VHDL: a parameterized 2^W -by-B register file


```
library ieee;
use ieee.std_logic_1164.all;
entity reg_file is
  port(
    clk, reset: in std_logic;
    wr_en: in std_logic;
    w_addr: in std_logic_vector(1 downto 0);
    w_data: in std_logic_vector(15 downto 0);
    r_addr0, r_addr1: in std_logic_vector(1 downto 0);
    r_data0, r_data1: out std_logic_vector(15 downto 0)
  );
end reg_file;

architecture no_loop_arch of reg_file is
  constant W: natural:=2; -- number of bits in address
  constant B: natural:=16; -- number of bits in data
  type reg_file_type is array (2**W-1 downto 0) of
    std_logic_vector(B-1 downto 0);
  signal array_reg: reg_file_type;
  signal array_next: reg_file_type;
  signal en: std_logic_vector(2**W-1 downto 0);
```

A user-defined array-of-array data type is introduced



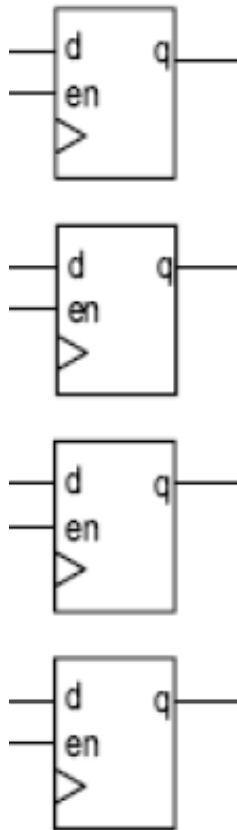VHDL: a parameterized 2^W -by-B register file



```
process (clk, reset)
begin
    if (reset='1') then
        array_reg(3) <= (others=>'0');
        array_reg(2) <= (others=>'0');
        array_reg(1) <= (others=>'0');
        array_reg(0) <= (others=>'0');
    elsif (clk'event and clk='1') then
        array_reg(3) <= array_next(3);
        array_reg(2) <= array_next(2);
        array_reg(1) <= array_next(1);
        array_reg(0) <= array_next(0);
    end if;
end process;
```


□ Index to access an element in the array

- $s(i)$ to access the i th row of the array s
- $S(i)(j)$ to access the j th element of i th row in the array



VHDL: a parameterized 2^W -by-B register file

Enable logic for register

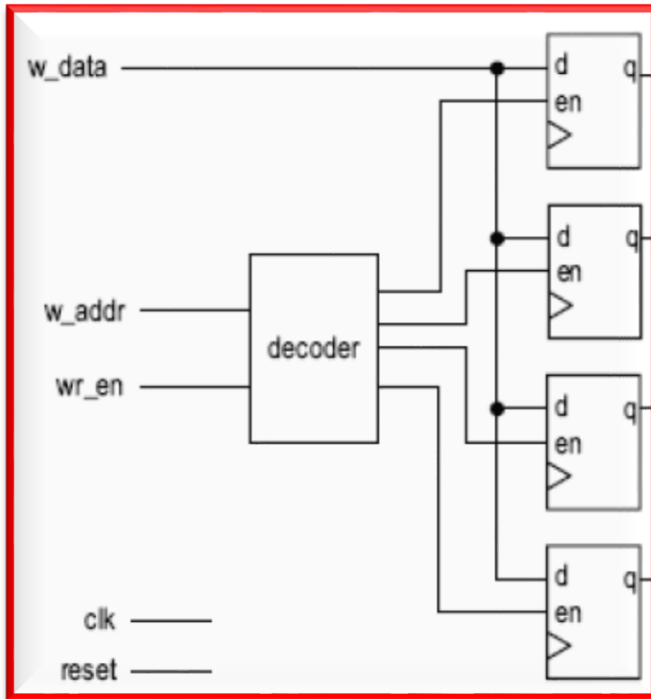


```
process(array_reg, en, w_data)
begin
    array_next(3) <= array_reg(3);
    array_next(2) <= array_reg(2);
    array_next(1) <= array_reg(1);
    array_next(0) <= array_reg(0);
    if en(3)='1' then
        array_next(3) <= w_data;
    end if;
    if en(2)='1' then
        array_next(2) <= w_data;
    end if;
    if en(1)='1' then
        array_next(1) <= w_data;
    end if;
    if en(0)='1' then
        array_next(0) <= w_data;
    end if;
end process;
```



VHDL: a parameterized 2^W -by-B register file

Enable logic for register (Cont.)

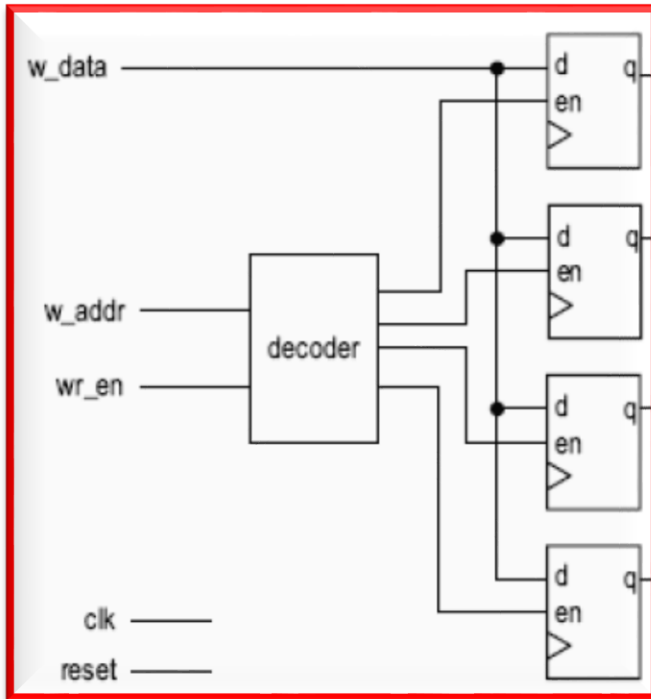


```
process (wr_en, w_addr)
begin
  if (wr_en='0') then
    en <= (others=>'0');
  else
    case w_addr is
      when "00" => en <= "0001";
      when "01" => en <= "0010";
      when "10" => en <= "0100";
      when others => en <= "1000";
    end case;
  end if;
end process;
```



VHDL: a parameterized 2^W -by-B register file

Read Multiplexing

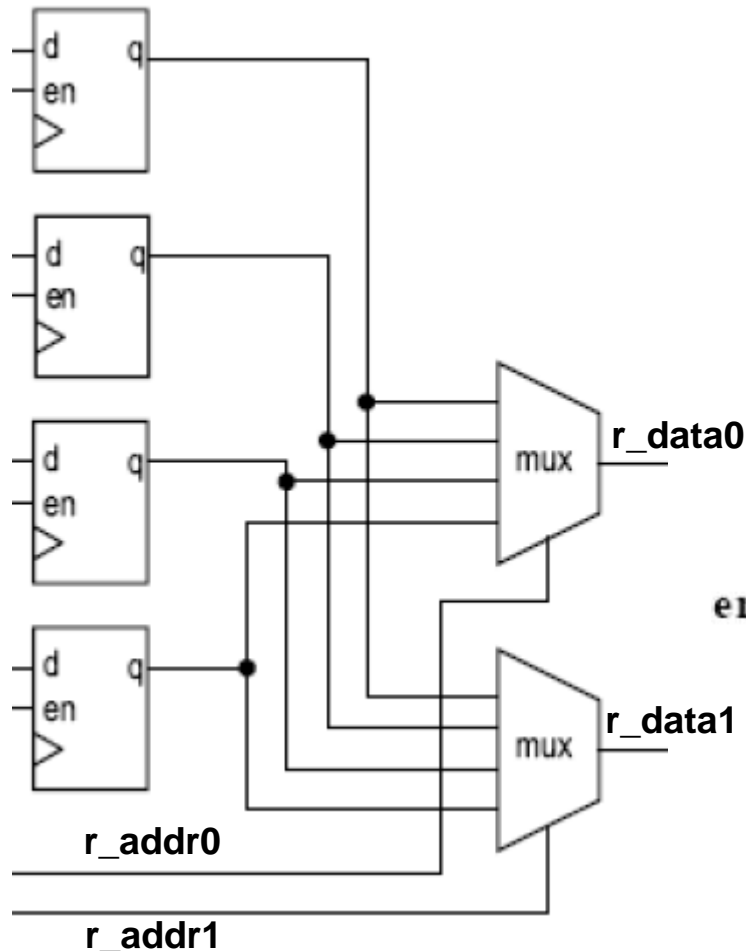

```
with r_addr0 select
    r_data0 <= array_reg(0) when "00",
              array_reg(1) when "01",
              array_reg(2) when "10",
              array_reg(3) when others;

with r_addr1 select
    r_data1 <= array_reg(0) when "00",
              array_reg(1) when "01",
              array_reg(2) when "10",
              array_reg(3) when others;


end no_loop_arch;
```



Storage Examples 2

□ FIFO (first in first out) Buffer

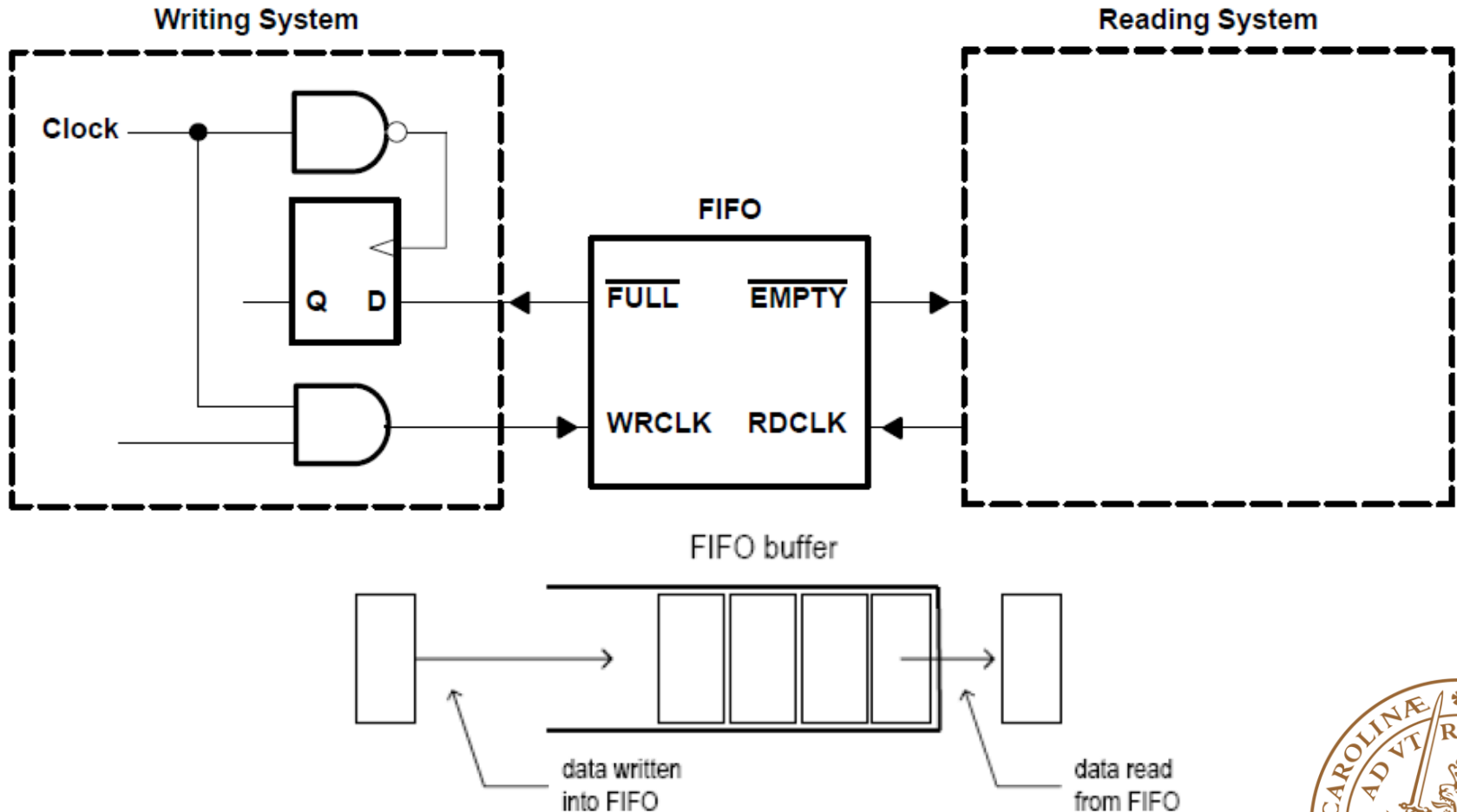- “Elastic” storage between two subsystems




Circular FIFO

□ How to Implement a FIFO?


- Circular queue implementation
- Use two pointers and a “generic storage”
 - **Write pointer:** point to the empty slot before the **head** of the queue
 - **Read pointer:** point to the **tail** of the queue



"First in? First out!"

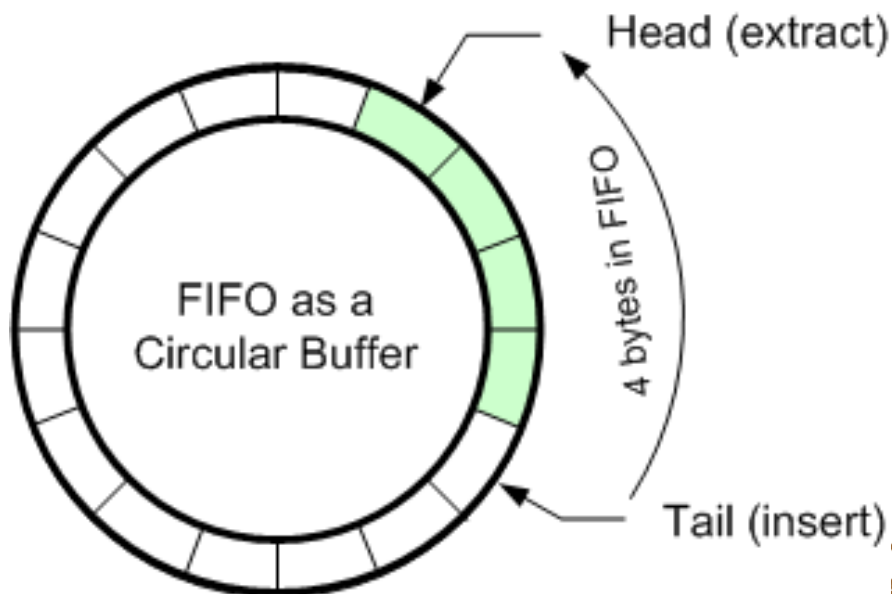

Circular FIFO

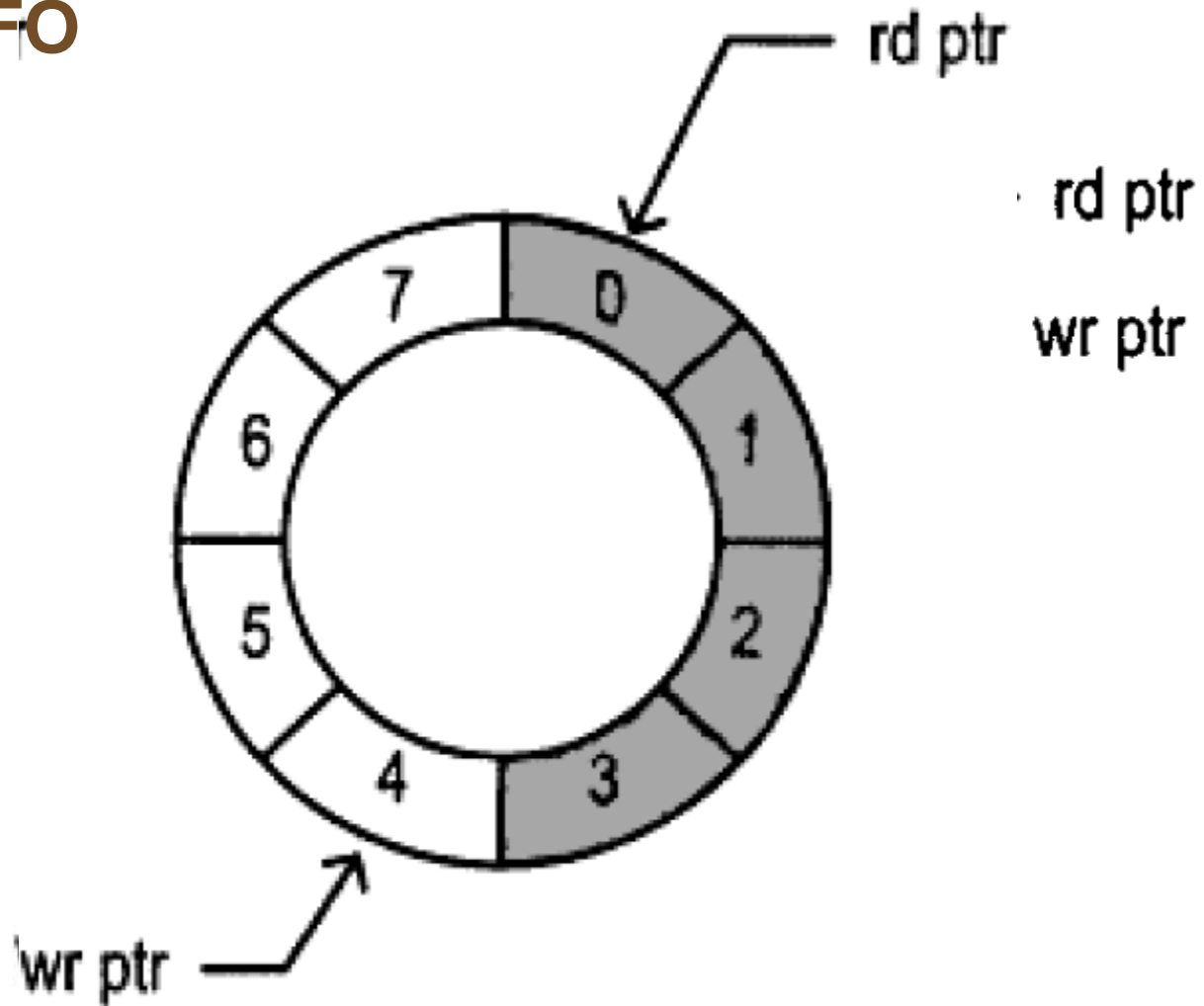

(c). 4 more writes



FIFO Implementation

Overall Architecture


- Storage Elements

 - Reg. file

- FIFO Controller**

 - Read and write pointers: 2 counters

 - Status circuit: *full, empty*

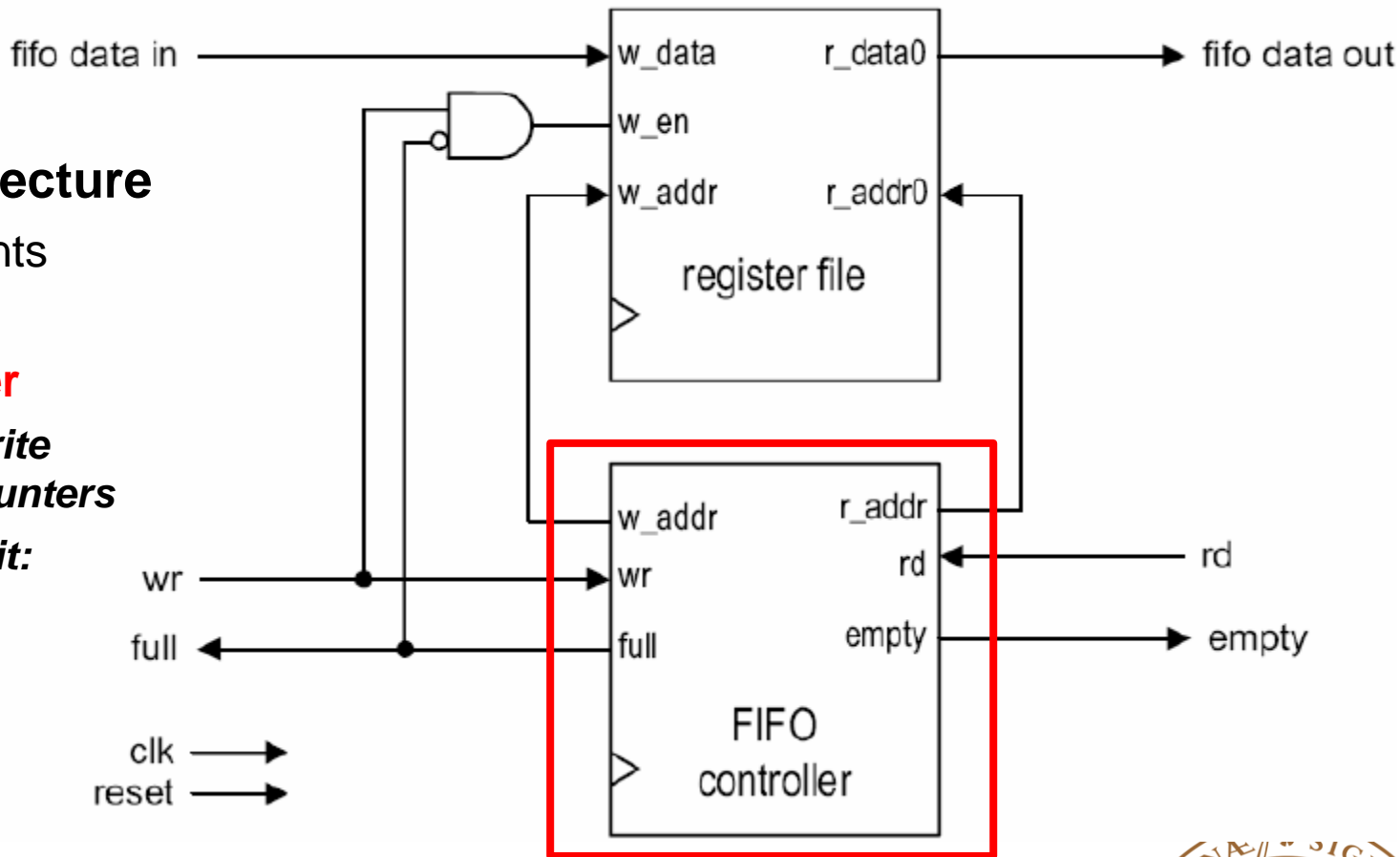

FIFO Implementation: Controller

□ Augmented binary counter:

- Increase the counter by 1 bits
- Use LSBs for as register address
- Use **MSB** to distinguish full or empty

Write pointer	Read pointer	Operation	Status
0 000	0 000	initialization	empty
0 111	0 000	after 7 writes	
1 000	0 000	after 1 write	full
1 000	0 100	after 4 reads	
1 100	0 100	after 4 writes	full
1 100	1 011	after 7 reads	
1 100	1 100	after 1 read	empty
0 011	1 100	after 7 writes	
0 100	1 100	after 1 write	full
0 100	0 100	after 8 reads	empty



Outline

□ Overview of Memory

- Application, history, trend
- Different memory type
- Overall architecture

□ Registers as Storage Element

- Register File
- FIFO

□ Xilinx Storage Elements

□ Memory Generator




Storage Components in a Spartan-3 Device

□ Distributed RAM



- Fast, localized
- ideal for small data buffers, FIFOs, or register files

□ Block RAM

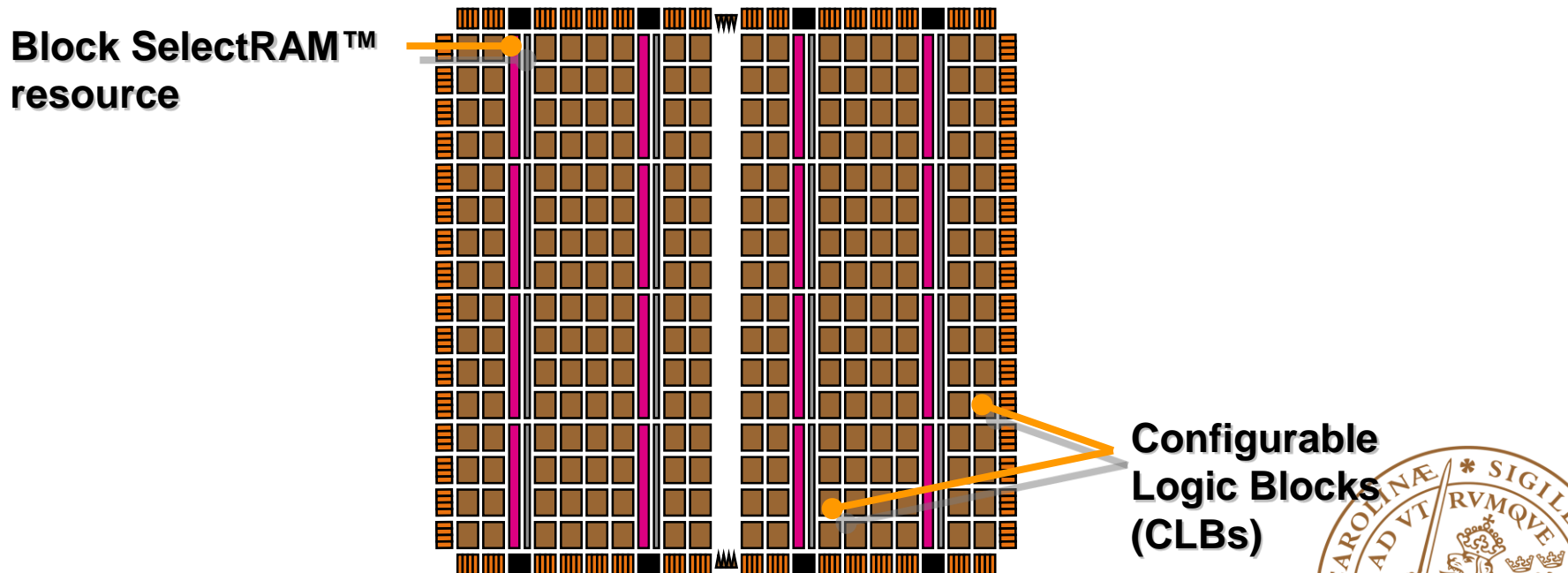- For applications requiring large, on-chip memories



Spartan-3 Distributed Memory

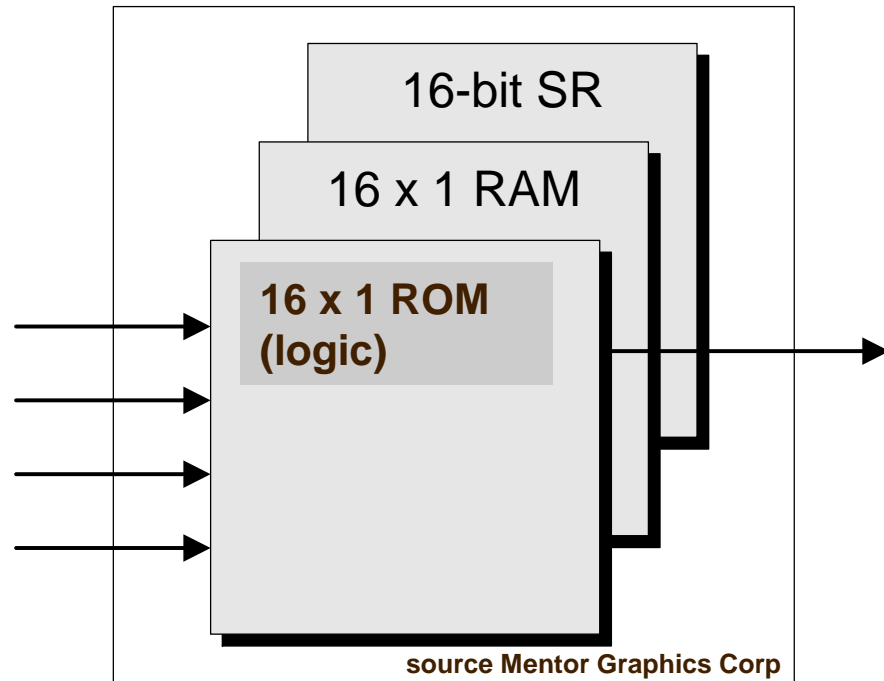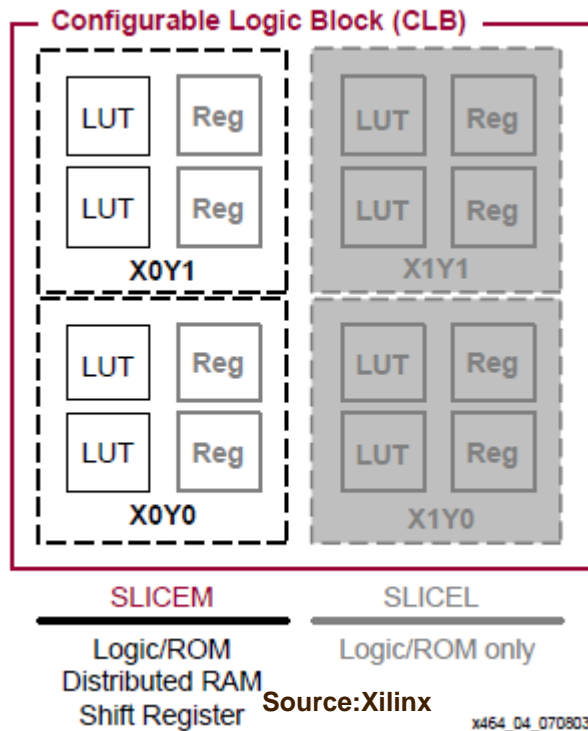

- ❑ One CLB has four slices: SLICEM & SLICEL
- ❑ Each LUT in SLICEM has RAM 16×1 S



Spartan-3 Distributed Memory

❑ Uses a LUT in a slice as memory

- An LUT equals 16x1 RAM
- Cascade LUTs to increase RAM size


❑ Two LUTs can make

- 32 x 1 single-port RAM
- 16 x 2 single-port RAM
- 16 x 1 dual-port RAM

❑ Synchronous write

❑ Asynchronous read

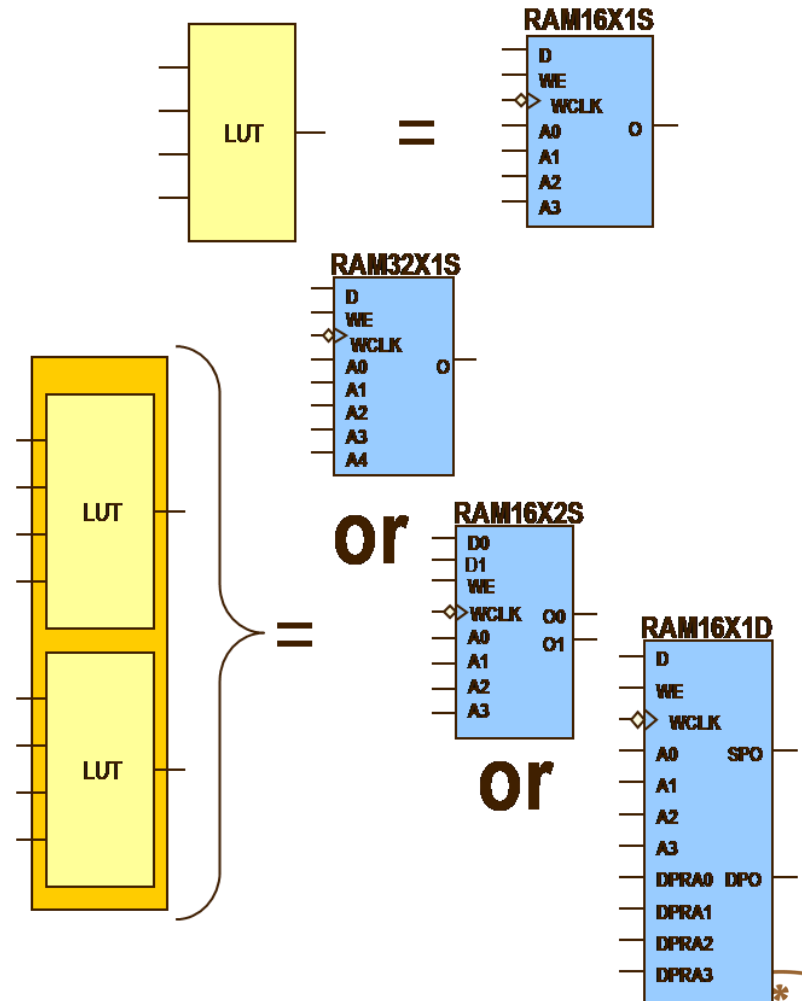
- Accompanying flip-flops can be used to create synchronous read



Spartan-3 Distributed Memory

□ Timing


- Synchronous write
- Asynchronous read

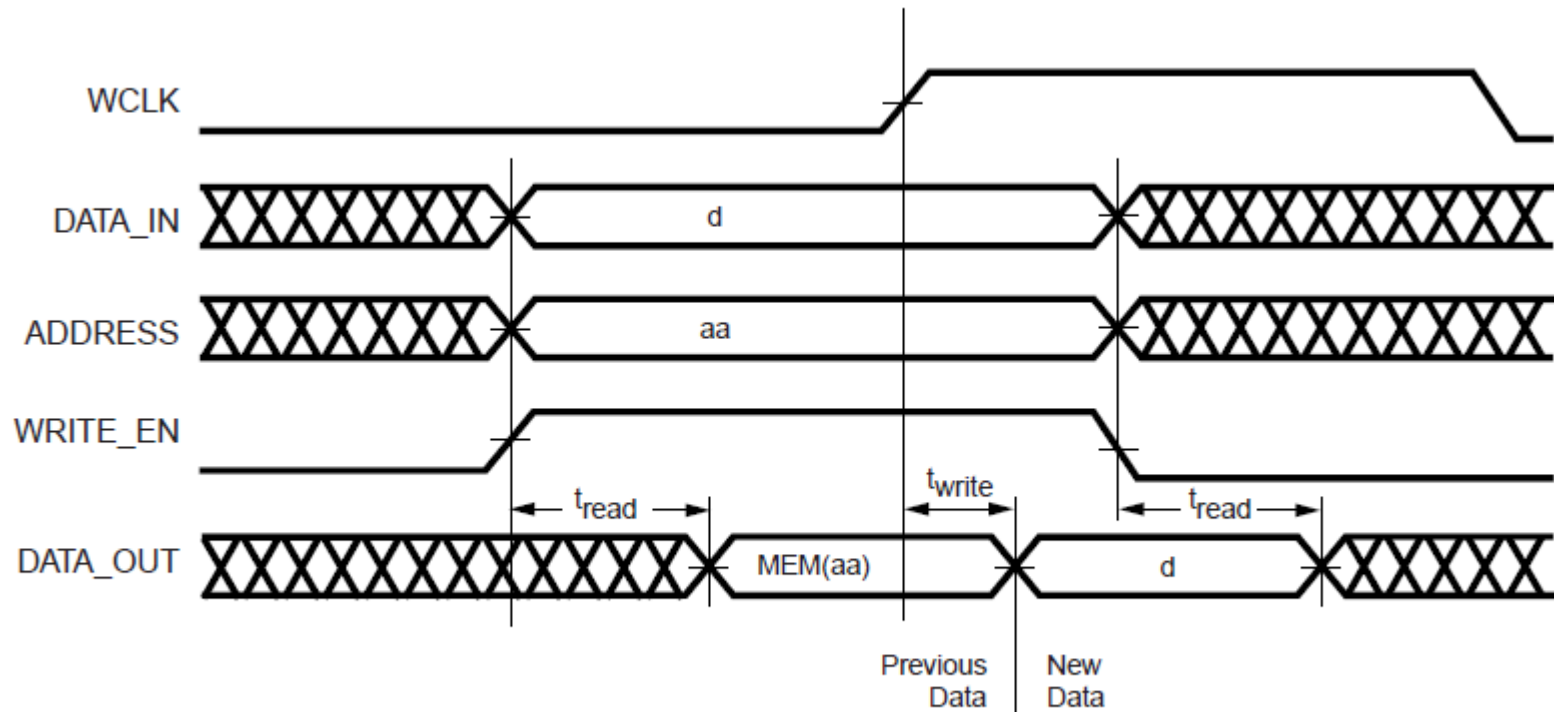

x464_02_070303



Spartan-3 Block Memory

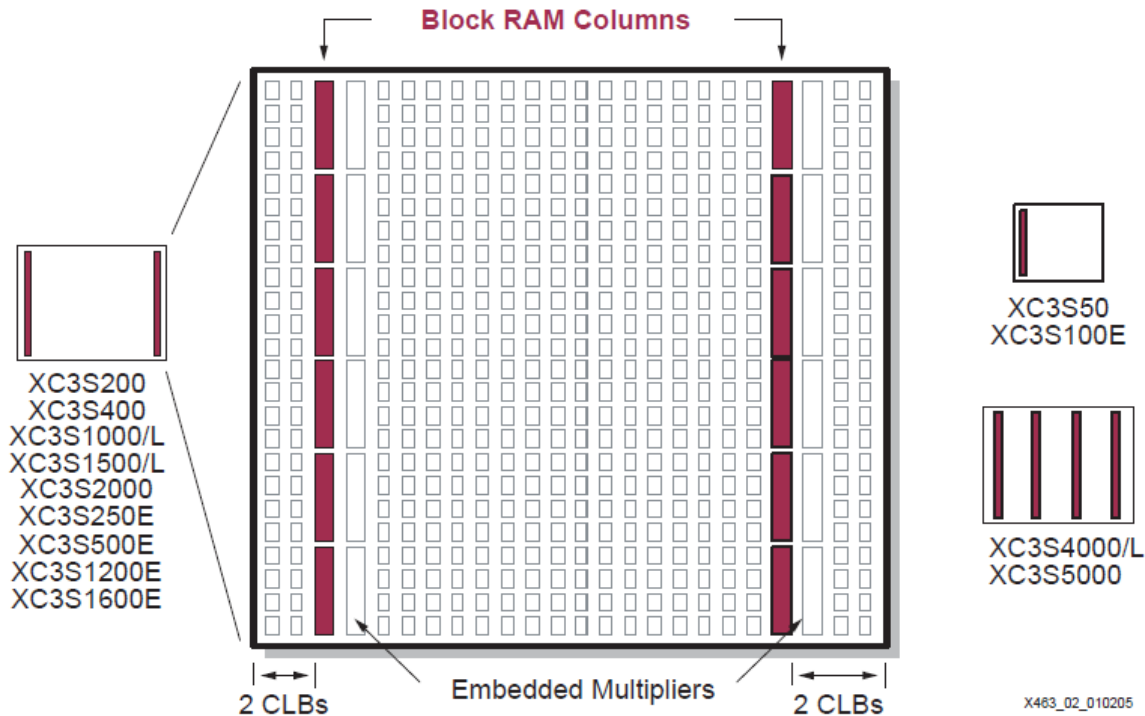

Most efficient memory implementation


- Dedicated blocks of memory
- 18 kbits = 18,432 bits per block (16 k without parity bits)

Builds both single and true dual-port RAMs


Synchronous write and read (different from distributed RAM)



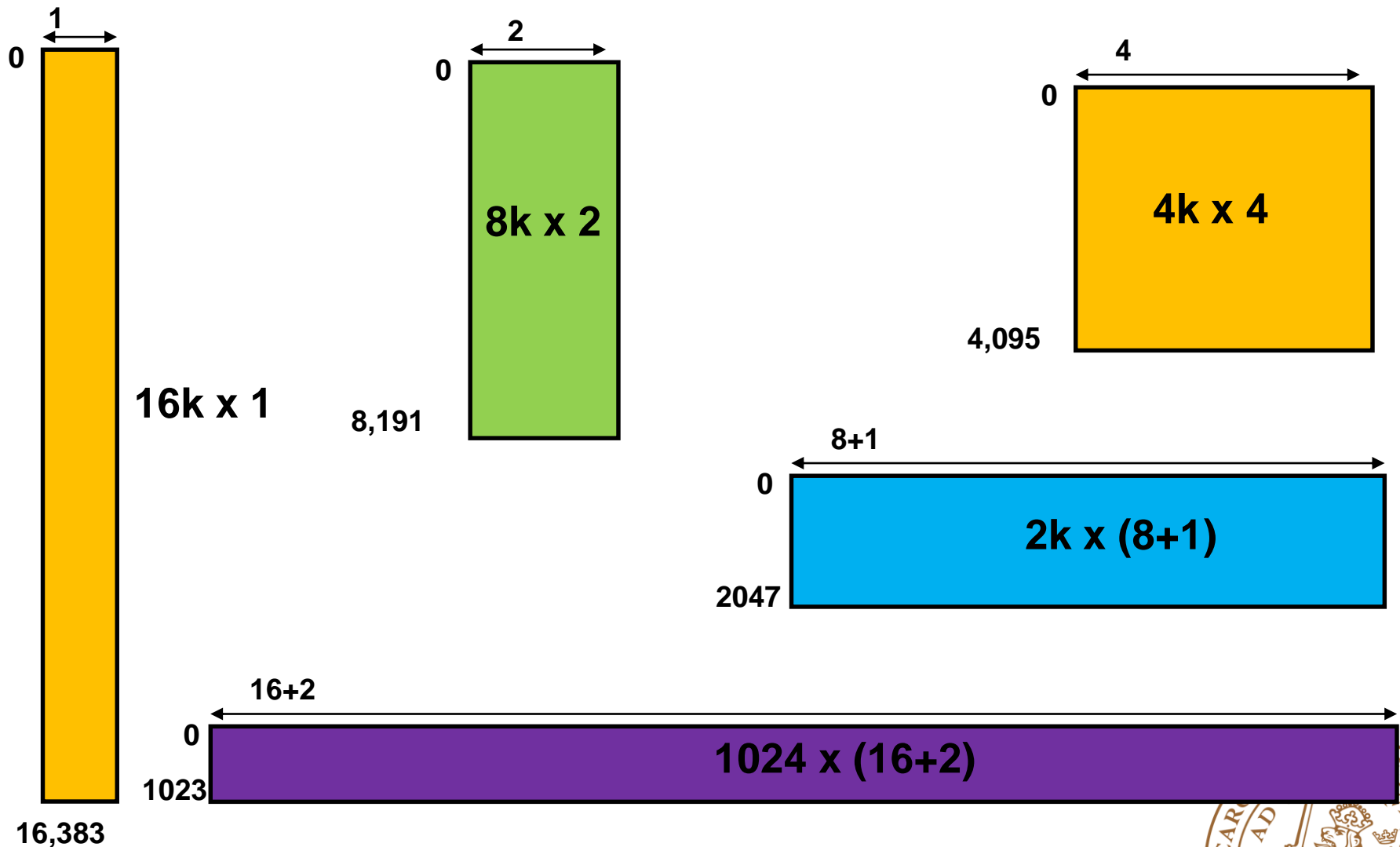Block RAM Configuration (port aspect ratios)



Block RAM Ports

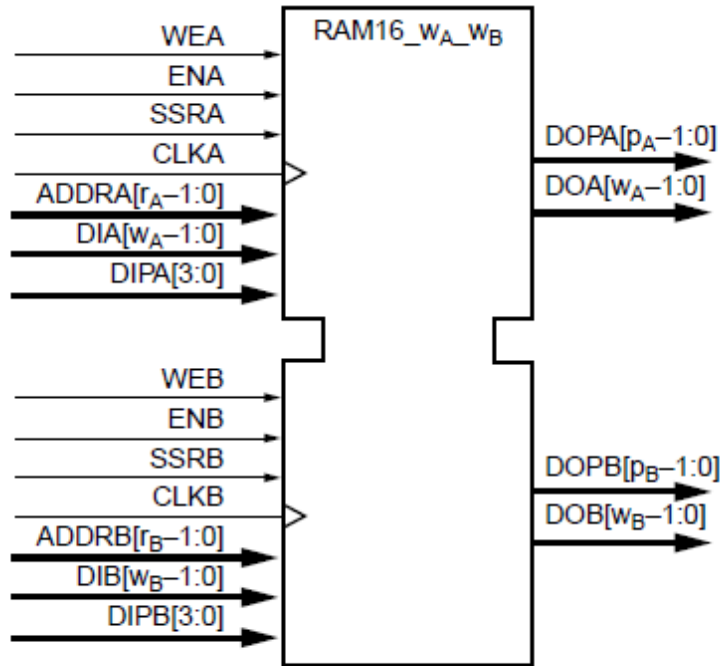

(a) Dual-Port

Table 4: Block RAM Interface Signals

Signal Description	Single Port	Dual Port		Direction
		Port A	Port B	
Data Input Bus	DI	DIA	DIB	Input
Parity Data Input Bus (available only for byte-wide and wider organizations)	DIP	DIPA	DIPB	Input
Data Output Bus	DO	DOA	DOB	Output
Parity Data Output (available only for byte-wide and wider organizations)	DOP	DOPA	DOPB	Output
Address Bus	ADDR	ADDRA	ADDRB	Input
Write Enable	WE	WEA	WEB	Input
Clock Enable	EN	ENA	ENB	Input
Synchronous Set/Reset	SSR	SSRA	SSRB	Input
Clock	CLK	CLKA	CLKB	Input

- $w_{A,B}$: the data path width at ports A,B.
- $r_{A,B}$: the address bus width at ports A, B
- The control signals CLK, WE, EN, and **SSR** on both ports have the option of inverted polarity.
- **Reset signal does NOT affect memory cells**




Block RAM: Operation Modes

Write Mode	Effect on Same Port	Effect on Opposite Port (dual-port mode only, same address)
WRITE_FIRST Read After Write (Default)	Data on DI, DIP inputs written into specified RAM location and simultaneously appears on DO, DOP outputs.	Invalidates data on DO, DOP outputs.
READ_FIRST Read Before Write (Recommended)	Data from specified RAM location appears on DO, DOP outputs. Data on DI, DIP inputs written into specified location.	Data from specified RAM location appears on DO, DOP outputs.
NO_CHANGE No Read on Write	Data on DO, DOP outputs remains unchanged. Data on DI, DIP inputs written into specified location.	Invalidates data on DO, DOP outputs.




Block RAM: WRITE_FIRST

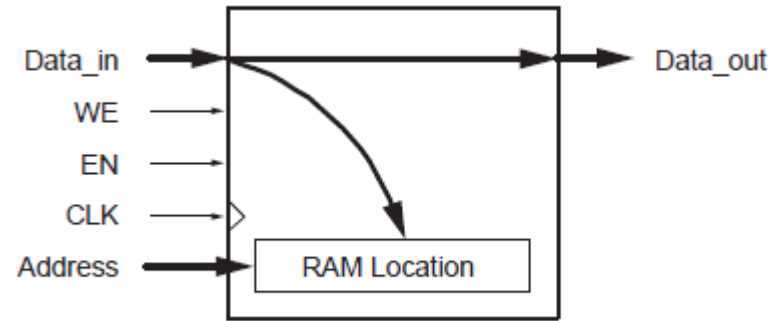

WRITE_MODE = WRITE_FIRST


X463_11_062503

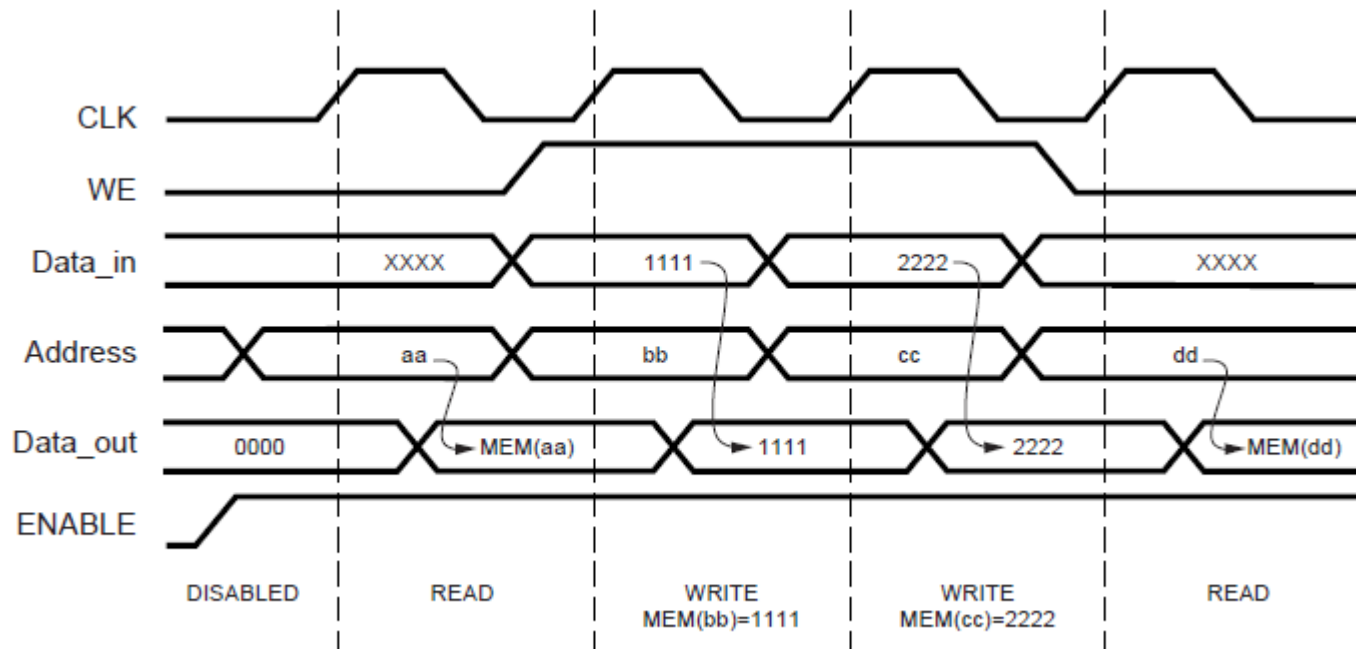


X463_12_020503



Block RAM: NO_CHANGE

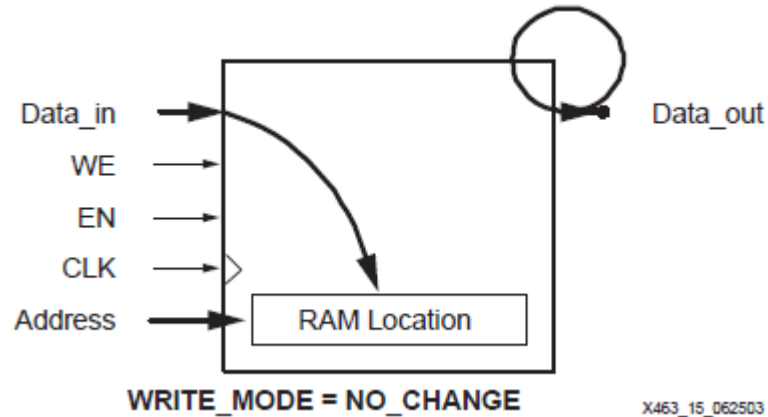



X463_15_062503

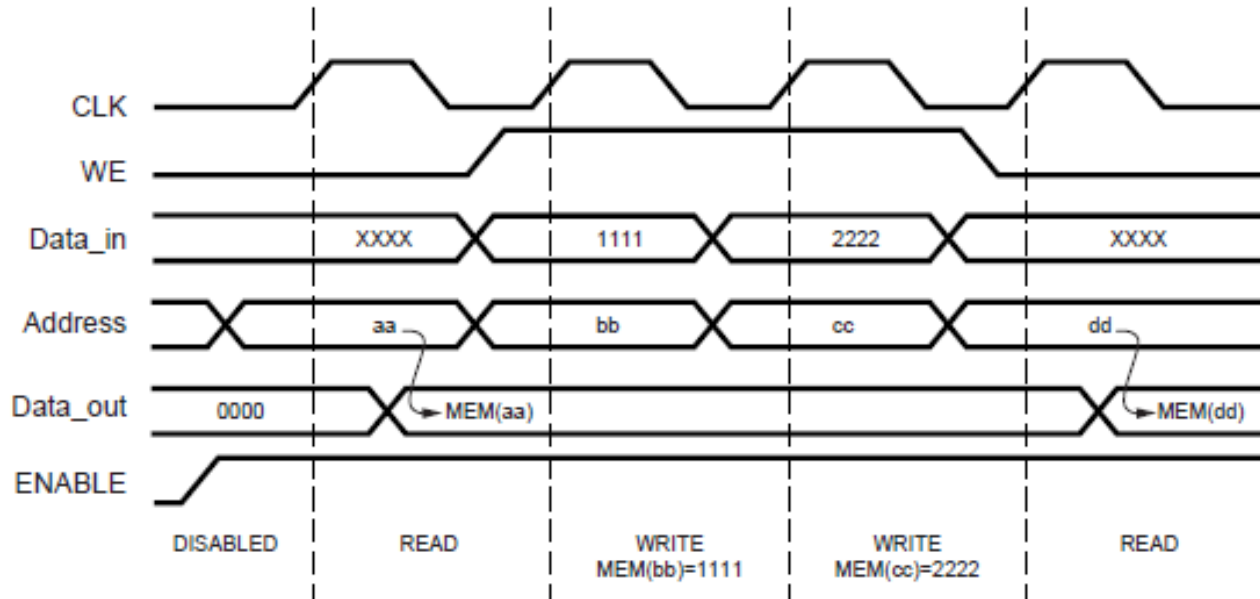

X463_16_020503



Block RAM: READ_FIRST (Recomm.)

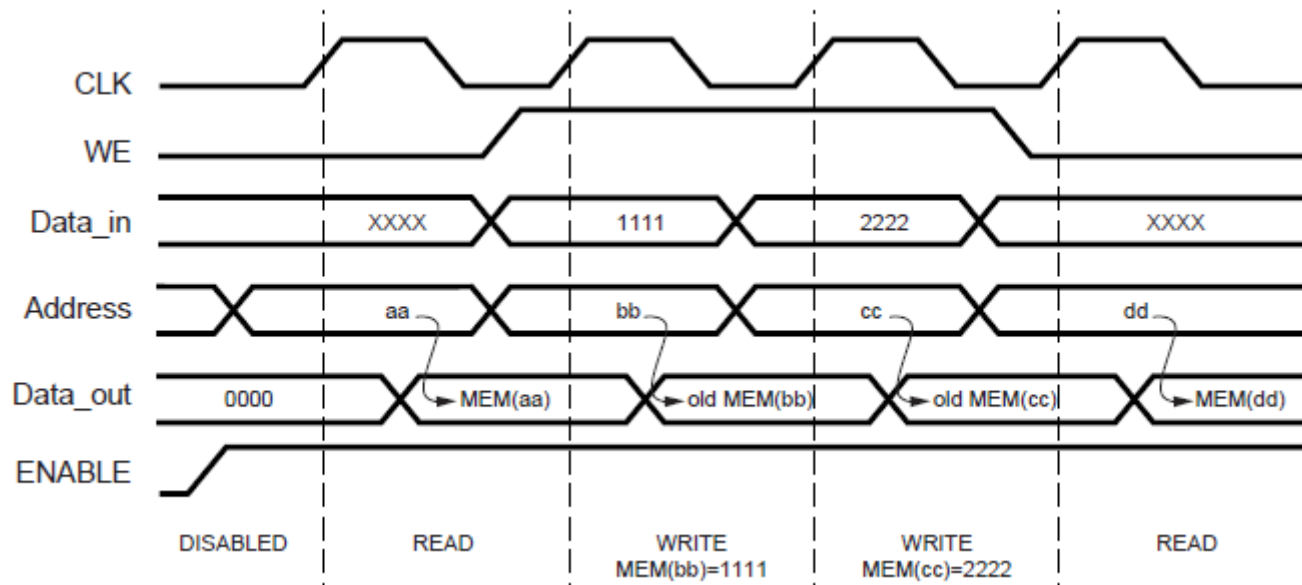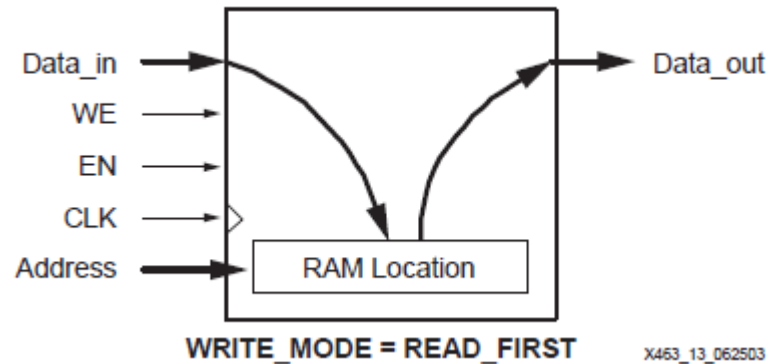

Reading Advice

- RTL Hardware Design Using VHDL: P276-P292
- XAPP463 Using Block RAM in Spartan-3 Generation FPGAs (*Google search: XAPP463*)
- XAPP464 Using Look-Up Tables as Distributed RAM in Spartan-3 Generation FPGAs (*Google search: XAPP464*)
- XST User Guide, Section: RAMs and ROMs HDL Coding Techniques (*Google search: XST User Guide (PDF)*)
- ISE In-Depth Tutorial, Section: Creating a CORE Generator Software Module (*Google search: ISE In-Depth Tutorial*)




□ Why two DFFs?



Crossing clock domain

□ Multiple clock is needed in case:

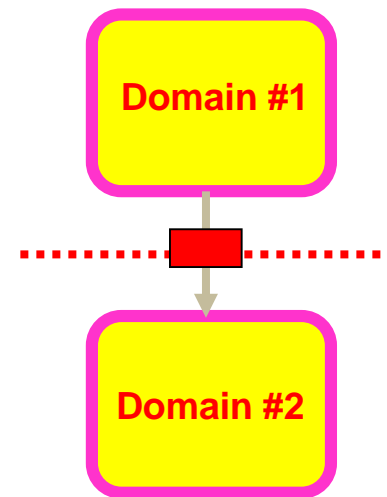
- Inherent system requirement
 - ***Different clocks for sampling and processing***
- Chip size limitation
 - ***Clock skew increases with the # FFs in a system***
 - ***Current technology can support up to 10^4 FFs***




Multiple Clocks: Problems

□ We have been setting very strict rules to make our digital circuits safe: using a forbidden zone in both voltage and time dimensions

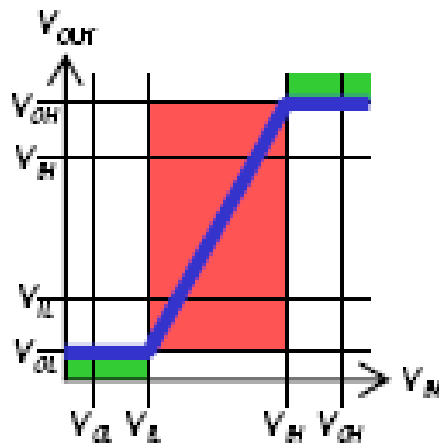Digital Values: distinguishing voltages representing “1” from “0”




Digital Time: setup and hold time rules

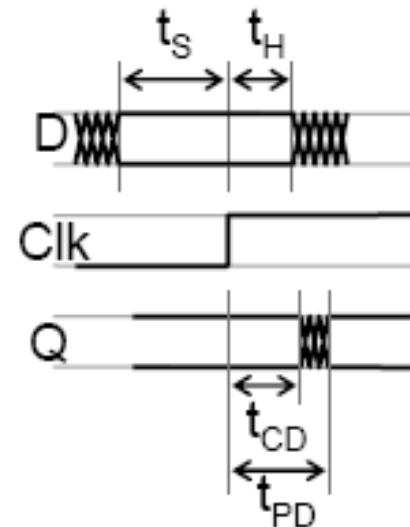

Metastability

□ With asynchronous inputs, we have to break the rules: ***we cannot guarantee that setup and hold time requirements are met at the inputs!***

□ What happens after timing violation?

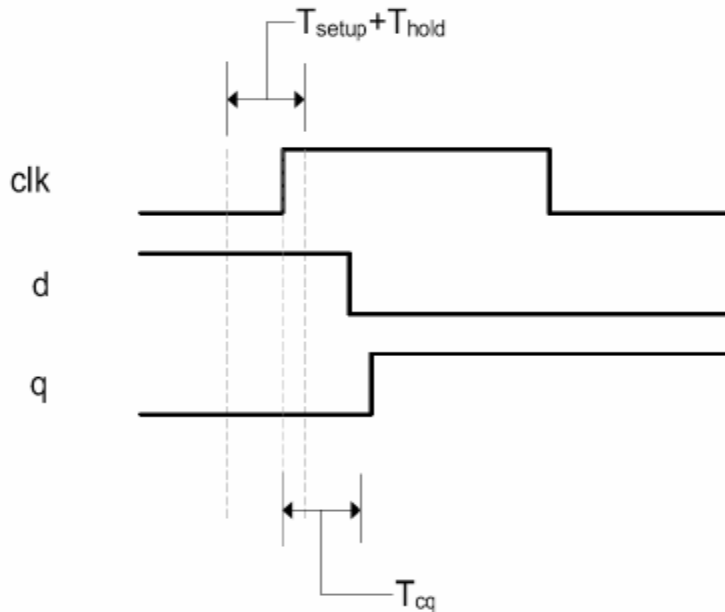

clk


D

Q

setup hold



Metastability in Digital Logic

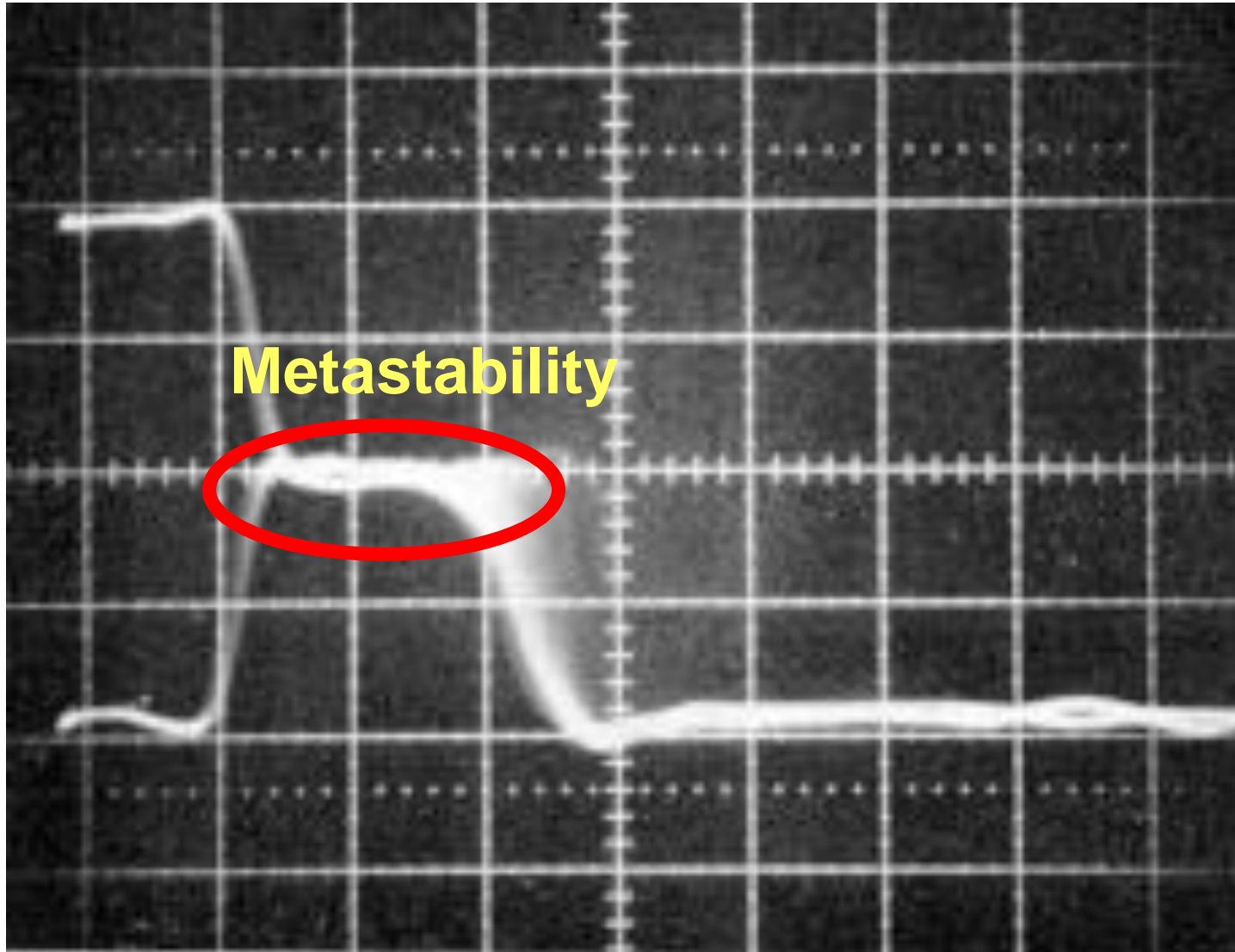


Mechanical Metastability



□ Launch a golf up a hill, 3 possible outcomes:

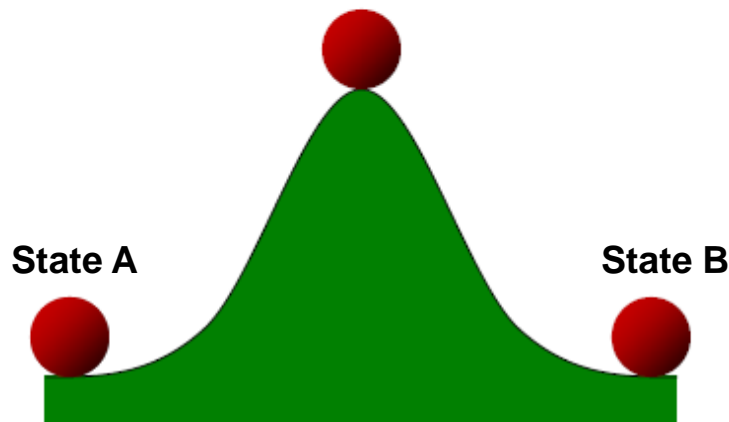- Hit lightly: Rolls back
- Hit hard: Goes over
- Or: Stalls at the apex



□ That last outcome is not stable:

- A gust of wind
- Brownian motion
- *Can you tell the eventual state?*




Metastability in Digital Logic



□ Our hill is related to the VTC (Voltage Transfer Curve).

- The higher the gain thru the transition region
- The steeper the peak of the hill
- The harder to get into a metastable state.

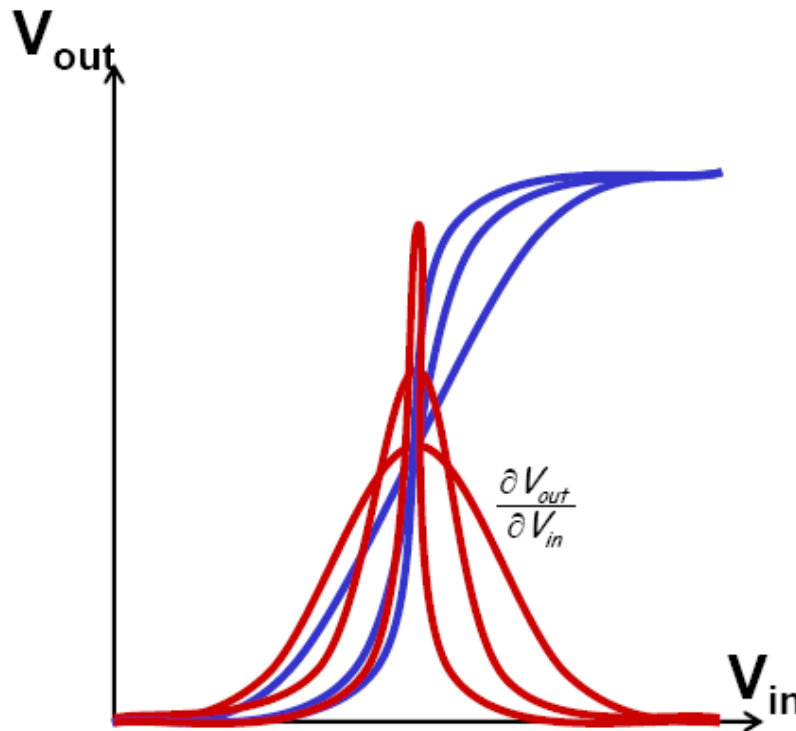□ We can decrease the probability of getting into the metastable state, but we can't eliminate it...



Metastability in Digital Logic

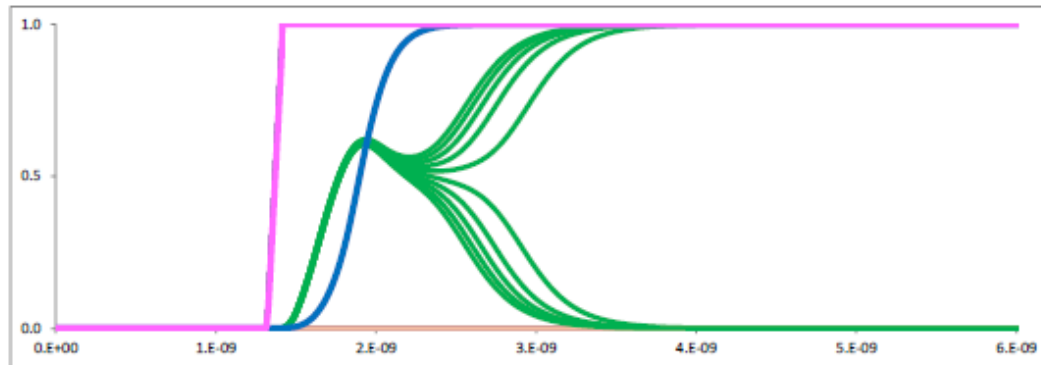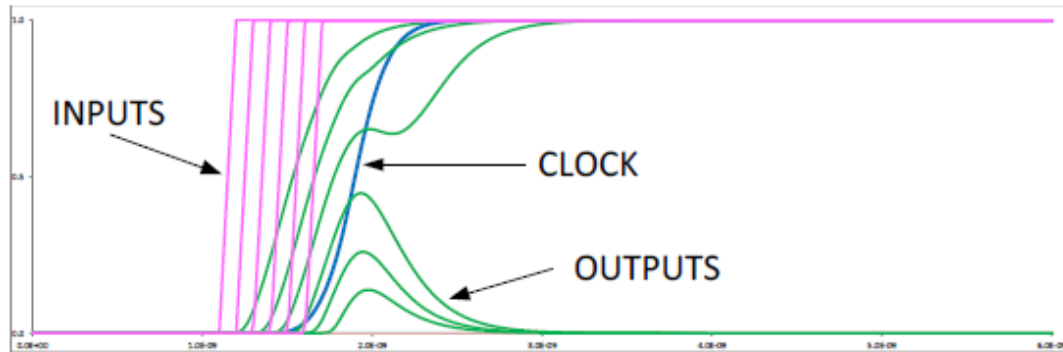


- ❑ Fixed clock edge
- ❑ Change the edge of inputs
- ❑ The input edge is moved in steps of 100ps and 1ps
- ❑ The behavior of outputs
 - ‘Three’ possible states
 - Will exit metastability

How long it takes to exit Metastability?




Exit Metastability

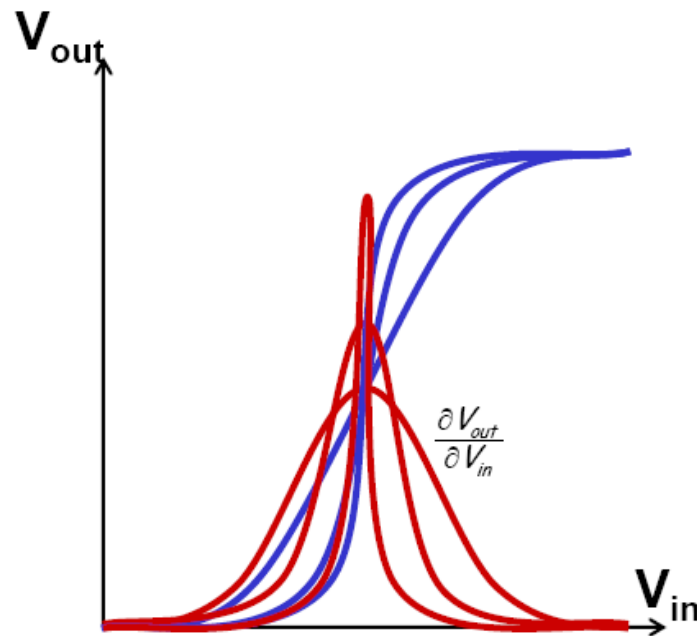- Define a fixed-point voltage, V_M , (always have) such that $V_{IN} = V_M$ implies $V_{OUT} = V_M$
- Assume the device is sampling at some voltage V_0 near V_M
- The time to settle to a stable value depends on $(V_0 - V_M)$; its theoretically infinite for $V_0 = V_M$



Exit Metastability

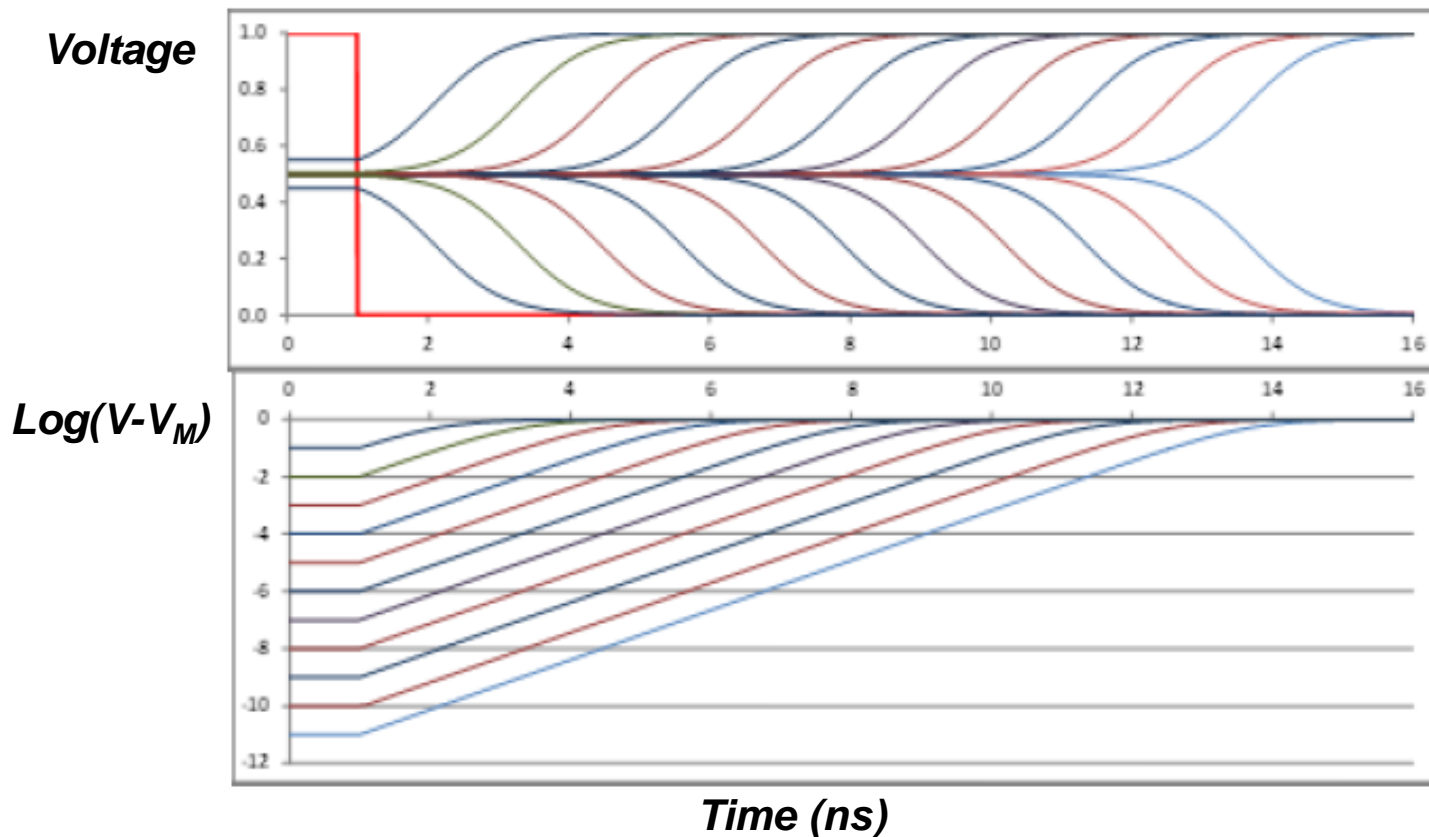- The time to exit metastability depends *logarithmically on* $(V_0 - V_M)$
- The *probability* of remaining metastable at time T is $e^{-T/\tau}$



MTBF: The probability of being metastable at time S ?

□ Two conditions have to be met concurrently

- An FF enters the metastable state
- An FF cannot resolve the metastable condition within S

□ The rate of failure $p(\text{failure}) = p(\text{enter MS}) \times p(\text{time to exit} > S)$

$$\text{Rate}(\text{failures}) = T_W F_C F_D \times e^{-S/\tau}$$

- T_W : time window around sampling edge incurring metastability
- F_C : clock rate (assuming data change is uniformly distributed)
- F_D : input change rate (input may not change every cycle)

□ Mean time between failures (MTBF)

$$\text{MTBF} = \frac{e^{S/\tau}}{T_W F_C F_D}$$



MTBF (Mean Time Between Failure)

□ Let's calculate an ASIC for 28nm CMOS process

- τ : 10ps (different FFs have different τ)
- $T_W=20\text{ps}$, $F_C=1\text{GHz}$
- Data changes every ten clock cycles
- Allow 1 clock cycle to resolve metastability, $S=T_C$

$$\text{MTBF} = 4 \times 10^{29} \text{ year !}$$


[For comparison:

Age of oldest hominid fossil: 5×10^6 years

Age of earth: 5×10^9 years]



The Two-Flip-Flop Synchronizer


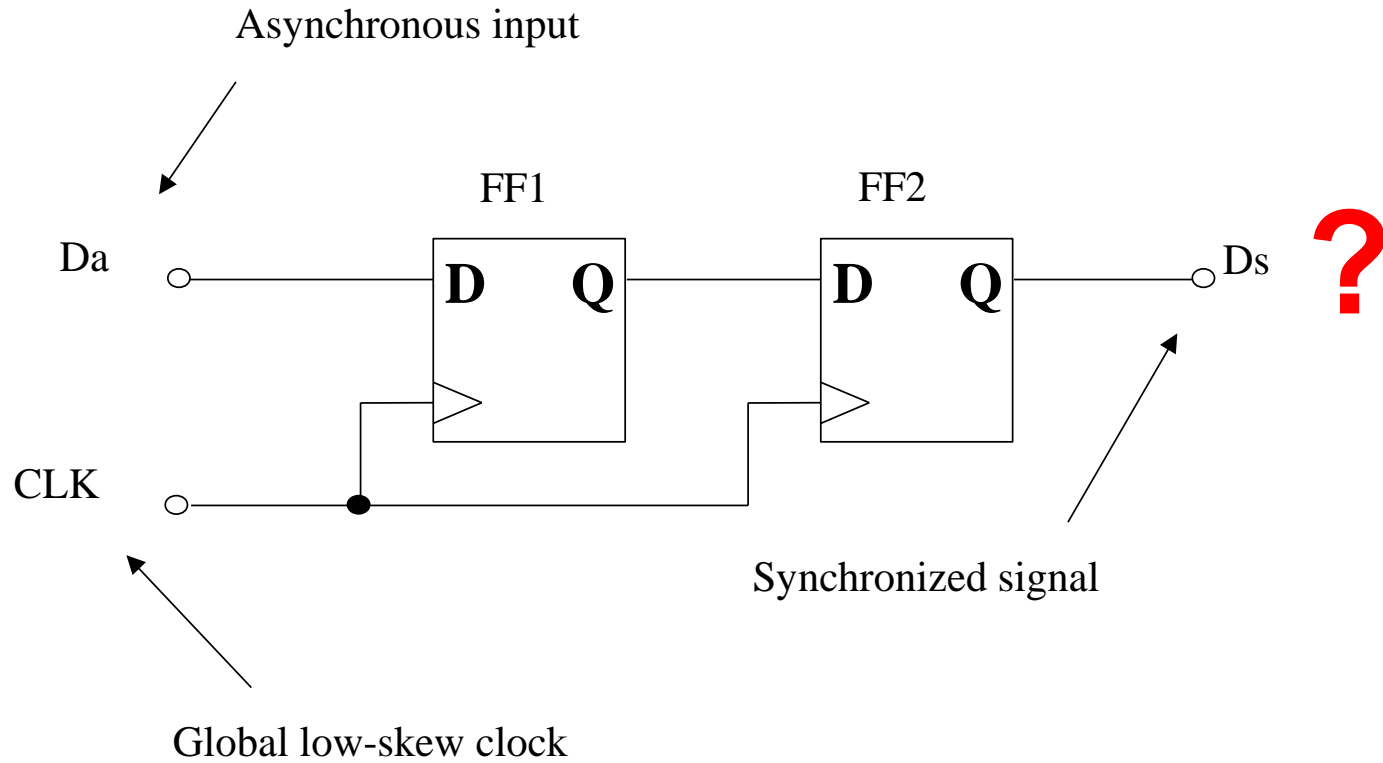


$$S = T_c$$





The Two-Flip-Flop Synchronizer

□ Possible Outcomes

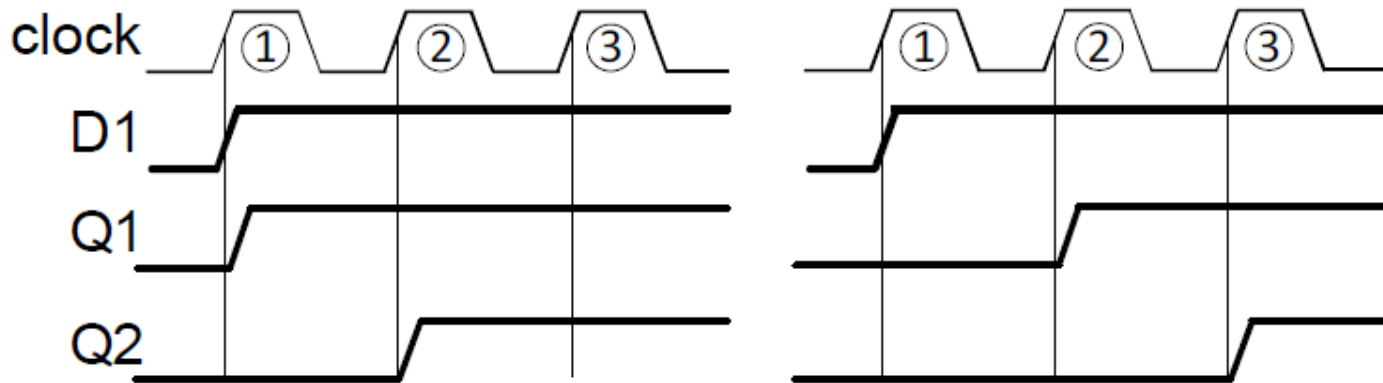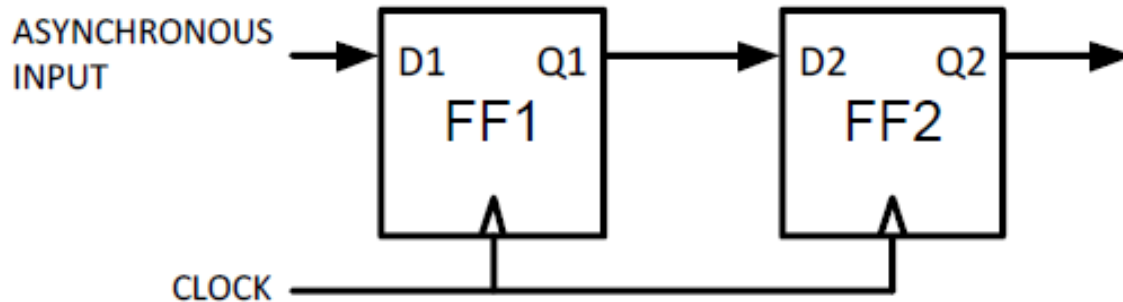

The Two-Flip-Flop Synchronizer

□ Possible Outcomes

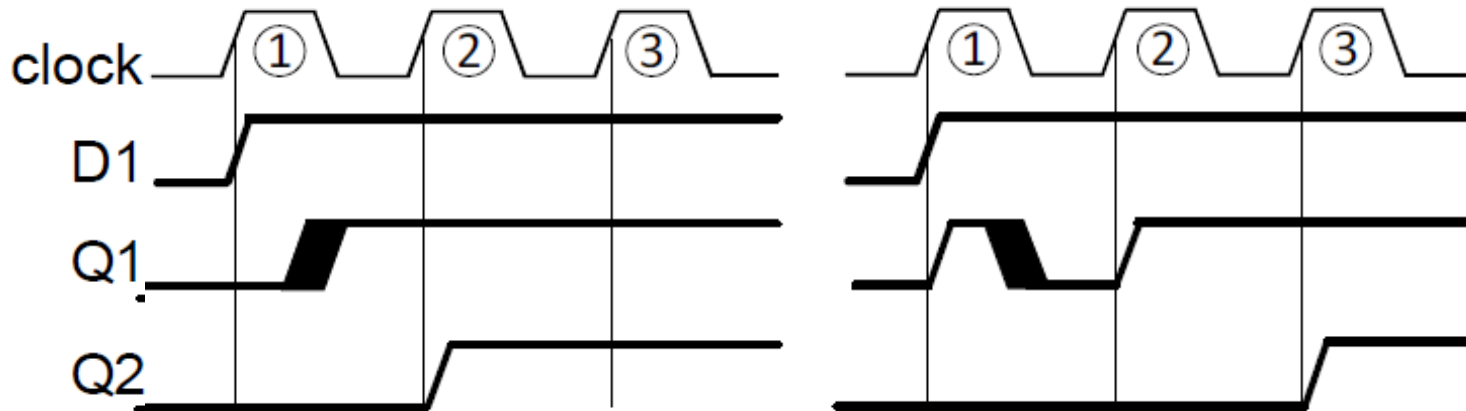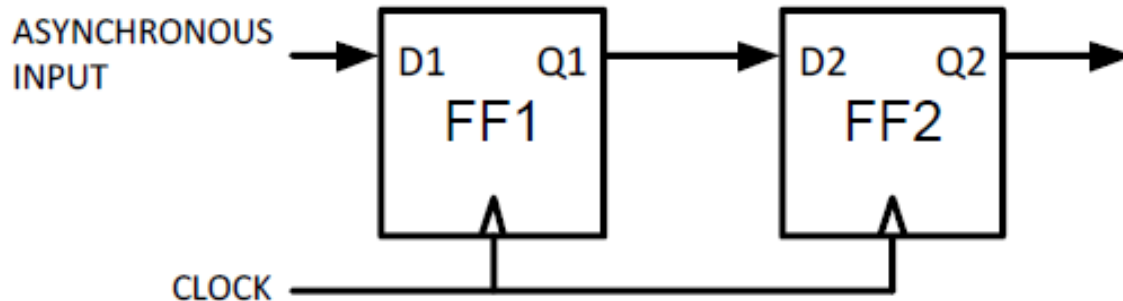

Open Question: What is the limitation?



Reading Advice

**“Metastability and Synchronizers: A Tutorial”, Ran Ginosar,
VLSI Systems Research Center, Israel Institute of Technology**



Lectures next week



Design for Test (DFT)

Erik Larsson
Associate Professor

DFT1: Monday (Sept. 22th), 10.15-12.00, E2311

DFT2: Tuesday (Sept. 23th), 9.00-10.00, EC

