



LUND  
UNIVERSITY

# EITF35: Introduction to Structured VLSI Design


## Part 1.2.1: Finite State Machines

Liang Liu  
liang.liu@eit.lth.se



# Two Basic Digital Components (What)

## Combinational Logic

 


Always:

```
z <= F(a, b, c);
```

i.e. a function that is always evaluated when an input changes.  
Can be expressed by a truth table.

## Register

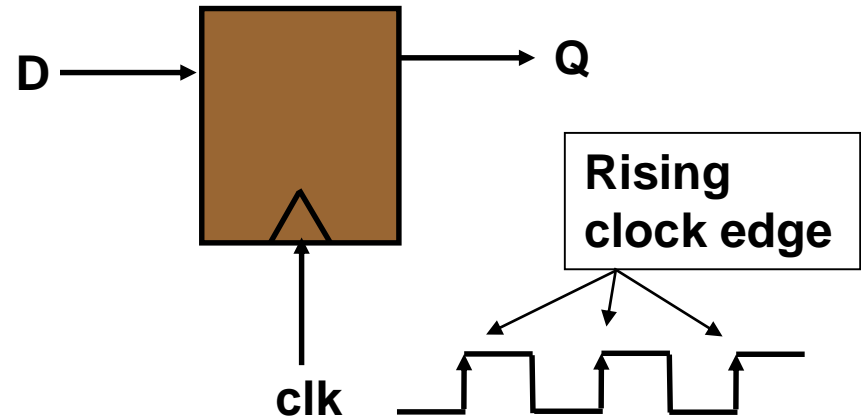


```
if clk' event and clk= '1' then  
  Q <= D;
```


i.e. a stored variable,  
Edge triggered D Flip-Flop  
with enable.





# Combinational Logic Timing

 

 - **Propagation delay:**  
After presenting new inputs  
Worst case delay before  
producing correct output



# Register timing

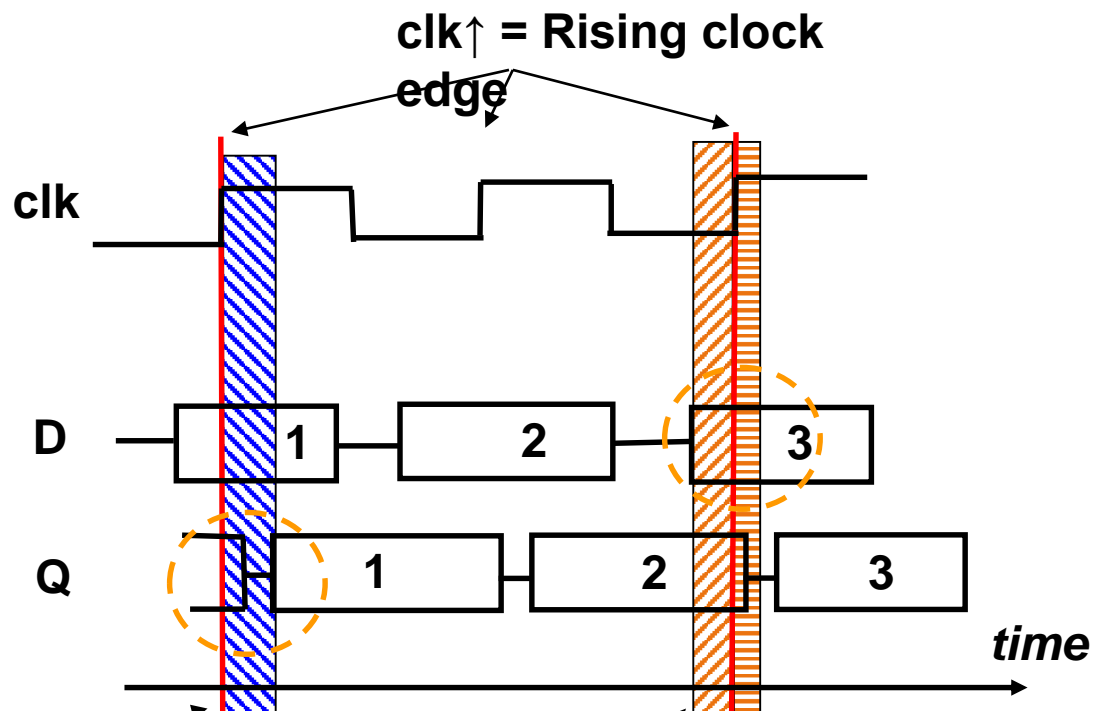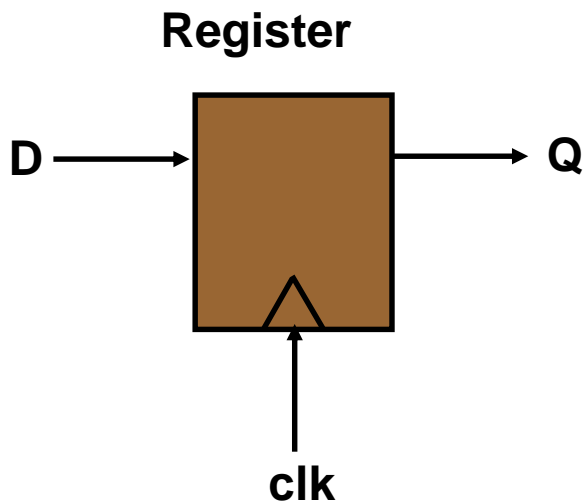

**Propagation delay (clk\_to\_Q):**  
Worst case (maximum) delay after  $\text{clk}\uparrow$  before new output data is valid on Q.

**Setup time:** Minimum time input must be stable before  $\text{clk}\uparrow$

**Hold time:** Minimum time input must be stable after  $\text{clk}\uparrow$



# Outline

## □ FSM Overview

## □ FSM Representation

- examples


## □ Moore vs. Mealy Machine

- from **circuits** perspective



 
# FSM Overview

- It has at most **a finite number** of states
- Models for representing **sequential** circuits
- Used mainly as a **controller** in a large system
- Moore vs. Mealy machines



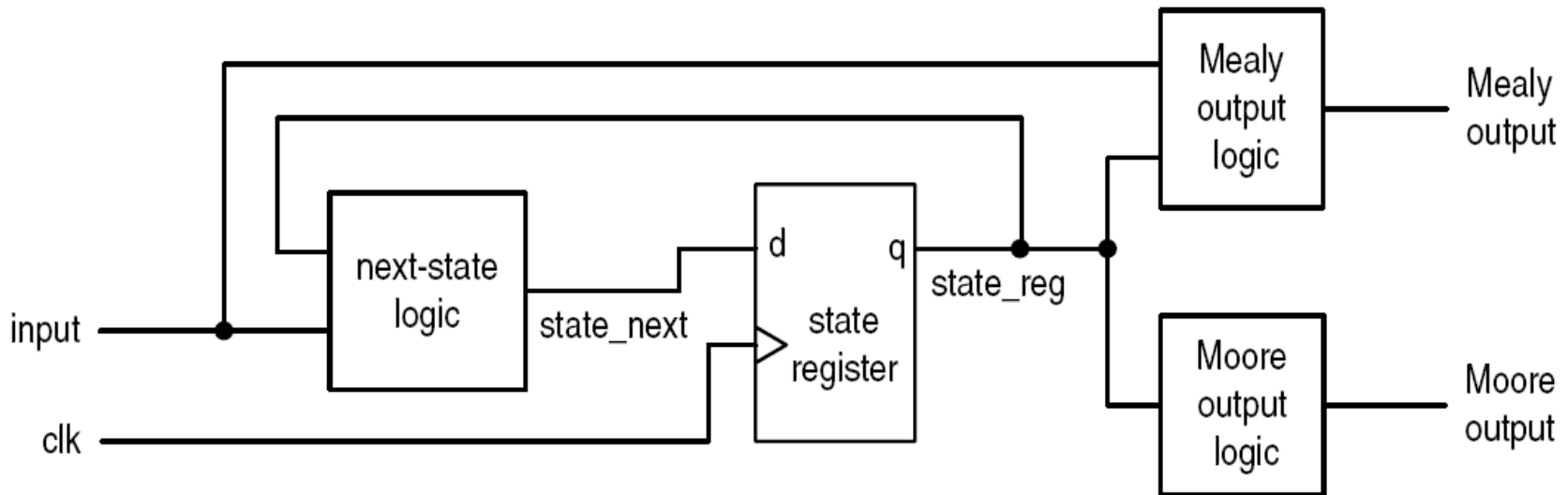
# Abstraction of state elements

- A FSM consists of several **states**. **Inputs** into the machine are combined with the **current state** of the machine to determine the new state or **next state** of the machine.
- Depending on the state of the machine, **outputs** are generated based on either the state or the state and inputs of the machine.


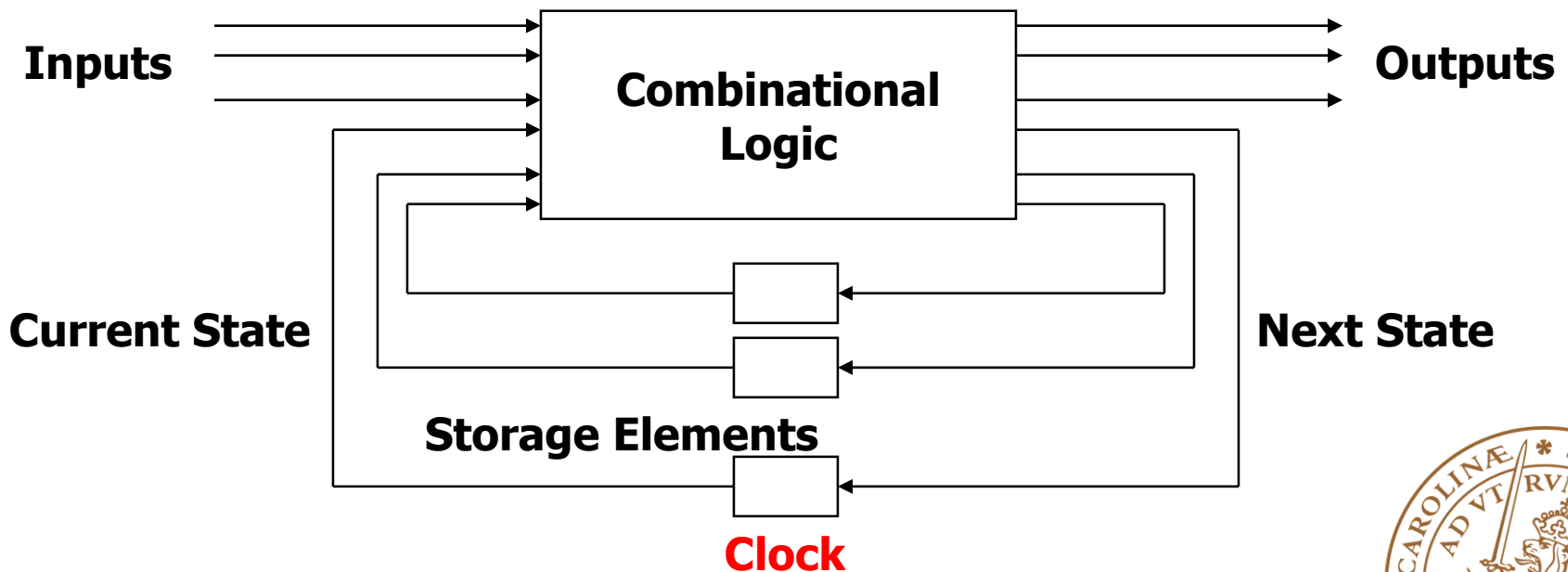
# Abstraction of state elements

- A FSM consists of several **states**. **Inputs** into the machine are combined with the **current state** of the machine to determine the new state or **next state** of the machine.
- Depending on the state of the machine, **outputs** are generated based on either the state or the state and inputs of the machine.
- Divide circuit into combinational logic and state





# Outline

- FSM Overview
- FSM Representation**
- Moore vs. Mealy Outputs
- Exercise



# FSM Representation

- Can be represented using a state transition table which shows the *current state*, *input*, any *outputs*, and the *next state*.

Input	Input <sub>0</sub>	Input <sub>1</sub>	...	Input <sub>n</sub>
Current State				
State <sub>0</sub>	Next State / Output	...	Next State / Output	
State <sub>1</sub>	....	....	....	
....	....	....	....	
State <sub>n</sub>	....	....	....	



# FSM Representation

- It can also be represented using a *state diagram* which has the same information as the state transition table.

- Mealy Output**


$Outputs = F(Inputs, Current\ state)$

$Next\ state = F(Inputs, Current\ state)$

- Moore Output**

$Outputs = F(Current\ state)$

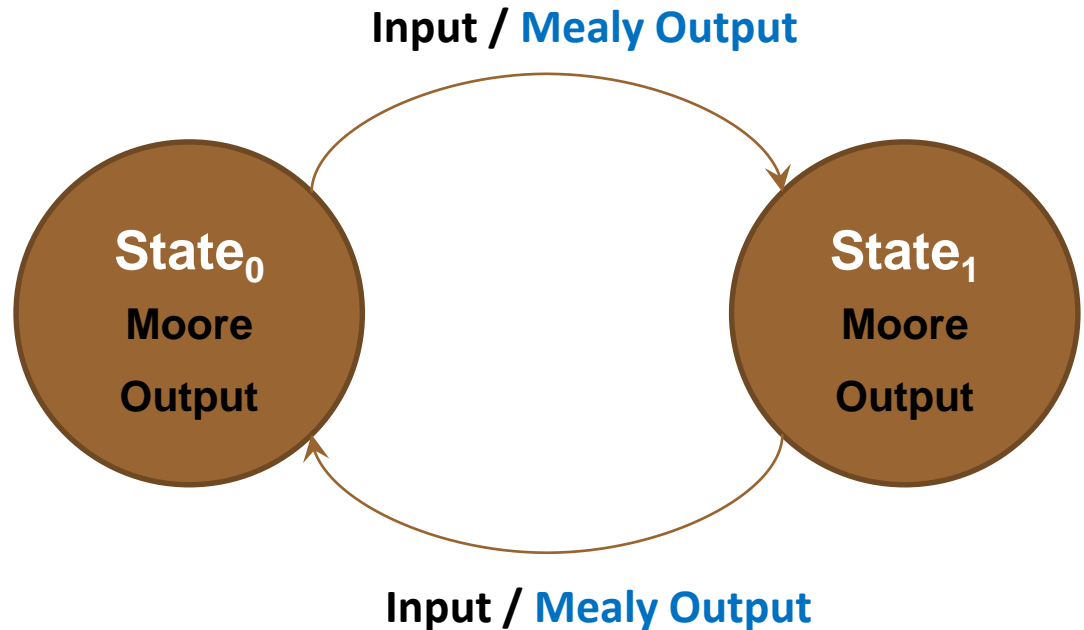$Next\ state = F(Inputs, current\ state)$



# Example 1: A mod-4 synchronous counter

- ❑ **Function:** Counts from 0 to 3 and then repeats; Reset signal reset the counter to 0.
- ❑ It has a clock (*CLK*) and a *RESET* input.
- ❑ **Outputs** appear as a sequence of values of 2 bits (*q1 q0*)
- ❑ As the outputs are generated, a **new state** (*s1 s0*) is generated which takes on values of 00, 01, 10, and 11.



# State Transition Table of Mod-4 Counter

Present state ( $S_t$ ) \ Input	<i>RESET</i>	
	0	1
<i>A</i> :00	01/01	00/00
<i>B</i> :01	10/10	00/00
<i>C</i> :10	11/11	00/00
<i>D</i> :11	00/00	00/00


Next State

Output

**One input is missing!**


 
# State Transition Diagram for the Mod-4 Counter



**Use meaningful names for states**




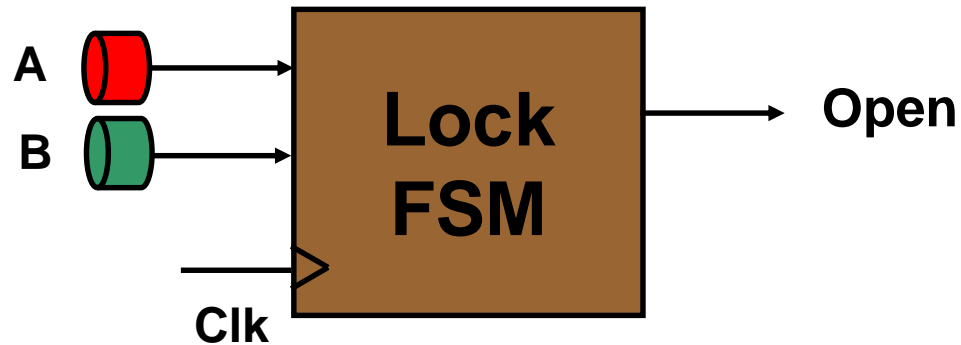 
# Example 2: Lock



□ Pushing: \* { A; B; B; A } => Open


- A & B never push at the same time
- Have to release the button before next pushing


 
# State Diagram for lock-FSM

{A;B;B;A}

- A and B are never pressed at the same time ...
- Debounce before next pushing




Finish the state graph for the Lock-FSM  
(5min)




 
# State Diagram for lock-FSM

- A and B are never pressed at the same time ...
- Debounce before next pushing



Consider all the input possibilities at each state



# Outline

- FSM Overview
- FSM Representation
- **Moore vs. Mealy Outputs**
- Exercise



# Mealy and Moore FSM

## A Method for Synthesizing Sequential Circuits

By GEORGE H. MEALY

(Manuscript received May 6, 1955)

*The theoretical basis of sequential circuit synthesis is developed, with particular reference to the work of D. A. Huffman and E. F. Moore. A new method of synthesis is developed which emphasizes formal procedures rather than the more familiar intuitive ones. Familiarity is assumed with the use of switching algebra in the synthesis of combinational circuits.*

### CONTENTS

1. Introduction .....	1045
1.1 Foreword .....	1045
1.2 Introductory Remarks .....	1046
2. A Model for Sequential Circuits .....	1049
2.1 The Model .....	1049
2.2 State Diagrams .....	1051
3. Circuit Equivalence .....	1053
3.1 Moore's Theory .....	1053
3.2 First Reduction Process .....	1056
4. Development of the Method for Synchronous Circuits .....	1059
4.1 Introductory Remarks .....	1059
4.2 Modification of First Reduction Process .....	1062
4.3 Second Reduction Process .....	1063
4.4 Blank Entries; Uniqueness of Reduction .....	1065
4.5 Final Remarks; Summary of Method .....	1065
5. The Method Applied to Asynchronous Circuits .....	1067
5.1 Introductory Remarks .....	1067
5.2 Interpretation of the Model .....	1067
5.3 Race Conditions; Coding of States .....	1069
5.4 Huffman's Method .....	1072
5.5 Summary of Method .....	1072
6. Discussion .....	1077
7. Acknowledgements .....	1078
8. Selected Bibliography .....	1078

### 1. INTRODUCTION

### GEDANKEN-EXPERIMENTS ON SEQUENTIAL MACHINES

Edward F. Moore

### INTRODUCTION

This paper is concerned with finite automata<sup>1</sup> from the experimental point of view. This does not mean that it reports the results of any experimentation on actual physical models, but rather it is concerned with what kinds of conclusions about the internal conditions of a finite machine it is possible to draw from external experiments. To emphasize the conceptual nature of these experiments, the word "gedanken-experiments" has been borrowed from the physicists for the title.

The sequential machines considered have a finite number of states, a finite number of possible input symbols, and a finite number of possible output symbols. The behavior of these machines is strictly deterministic (i.e., no random elements are permitted in the machines) in that the present state of a machine depends only on its previous input and previous state, and the present output depends only on the present state.

The point of view of this paper might also be extended to probabilistic machines (such as the noisy discrete channel of communication theory<sup>2</sup>), but this will not be attempted here.

### EXPERIMENTS


There will be two kinds of experiments considered in this paper. The first of these, called a simple experiment, is depicted in Figure 1.

<sup>1</sup>The term "finite" is used to distinguish these automata from Turing machines [considered in Turing's "On Computable Numbers, with an Application to the Entscheidungsproblem", Proc. Lond. Math. Soc., (1936) Vol. 24, pp. 230-265] which have an infinite tape, permitting them to have more complicated behavior than these automata.

<sup>2</sup>Defined in Shannon's "A Mathematical Theory of Communication", B.S.T.J. Vol. 27, p. 406.




# Output Timing: Moore

 

- ... a Moore machine is not able to produce  $A \rightarrow 1$  until the **next clock** when it enters s1





# Output Timing: Mealy

 

- When in s0, a Mealy machine may produce A->1 **immediately** in response to R->1



# Output Timing: Moore and Mealy

  

# Moore vs. Mealy (summary)

- **A Moore machine produces glitch free outputs**
  - Output change at the clock edge only
- **A Moore machine produces outputs depending only on states, and this may allow using a higher-frequency clock**
  - Less gate delay for the output logic
- **A Mealy machine can be specified using less states**
  - Because it is capable of producing different outputs in a given state, (nm) possible outputs v.s. (n)
- **A Mealy machine can be faster**
  - because an output may be produced immediately instead of at the next clock tick



# Moore vs. Mealy (summary)

## □ Which one is better?

- Edge sensitive control
  - *E.g., enable signal of counter*
  - *Both can be used but **Mealy** is faster*
- Level sensitive control
  - *E.g., write enable signal of SRAM*
  - ***Moore** is preferred for glitch free*

**Suggestion: do NOT mix Mealy and Moore in one design (before getting experienced)**





?

