



LUND
UNIVERSITY

EITF35: Introduction to Structured VLSI Design

Part 4.2.1: Learn More ...

Liang Liu
liang.liu@eit.lth.se



Outline

□ Crossing clock domain

□ Reset, synchronous or asynchronous?




□ Why two DFFs?



Crossing clock domain

□ Multiple clock is needed in case:

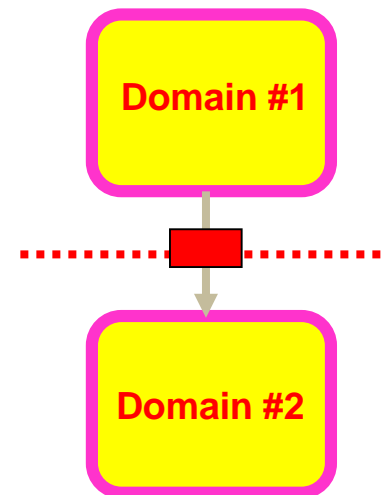
- Inherent system requirement
 - ***Different clocks for sampling and processing***
- Chip size limitation
 - ***Clock skew increases with the # FFs in a system***




Multiple Clocks: Problems

□ We have been setting very strict rules to make our digital circuits safe: using a forbidden zone in both voltage and time dimensions

 Digital Values: distinguishing voltages representing “1” from “0”





Digital Time: setup and hold time rules

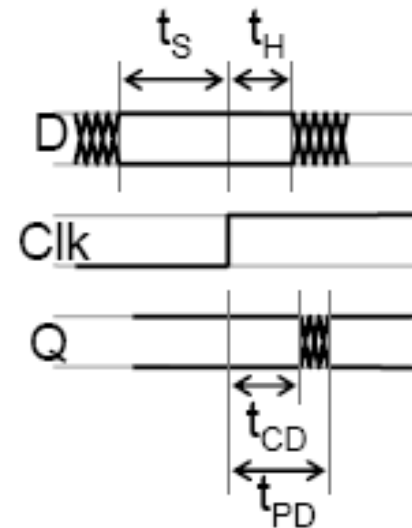


Metastability

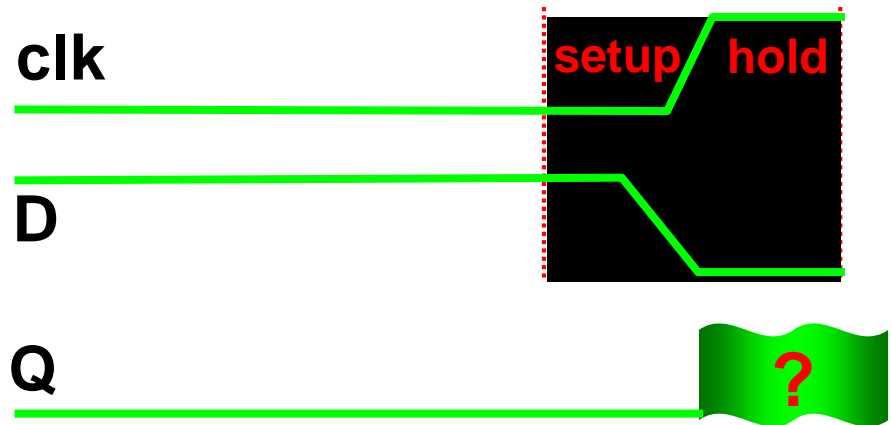 - With asynchronous inputs, we have to break the rules: ***we cannot guarantee that setup and hold time requirements are met at the inputs!***
- What happens after timing violation?



Metastability in Digital Logic

 


Mechanical Metastability



□ Launch a golf up a hill, 3 possible outcomes:

 - Hit lightly: Rolls back
- Hit hard: Goes over
- Or: Stalls at the apex



□ That last outcome is not stable:

- A gust of wind
- Brownian motion
- *Can you tell the eventual state?*




Metastability in Digital Logic



□ Our hill is related to the VTC (Voltage Transfer Curve).

- The higher the gain thru the transition region
- The steeper the peak of the hill
- The harder to get into a metastable state.

 □ We can decrease the probability of getting into the metastable state, but we can't eliminate it...



Metastability in Digital Logic

  


- ❑ Fixed clock edge
- ❑ Change the edge of inputs
- ❑ The input edge is moved in steps of 100ps and 1ps
- ❑ The behavior of outputs
 - ‘Three’ possible states
 - Will exit metastability

How long it takes to exit Metastability?




Exit Metastability

 - Define a fixed-point voltage, V_M , (always have) such that $V_{IN} = V_M$ implies $V_{OUT} = V_M$
- Assume the device is sampling at some voltage V_0 near V_M
- The time to settle to a stable value depends on $(V_0 - V_M)$; its theoretically infinite for $V_0 = V_M$



Exit Metastability

 - The time to exit metastability depends *logarithmically on* $(V_0 - V_M)$
- The *probability* of remaining metastable at time T is $e^{-T/\tau}$



MTBF: The probability of being metastable at time S ?

□ Two conditions have to be met concurrently

- An FF enters the metastable state
- An FF cannot resolve the metastable condition within S

□ The rate of failure $p(\text{failure}) = p(\text{enter MS}) \times p(\text{time to exit} > S)$

$$\text{Rate}(\text{failures}) = T_W F_C F_D \times e^{-S/\tau}$$

- T_W : time window around sampling edge incurring metastability
- F_C : clock rate (assuming data change is uniformly distributed)
- F_D : input change rate (input may not change every cycle)

□ Mean time between failures (MTBF)

$$\text{MTBF} = \frac{e^{S/\tau}}{T_W F_C F_D}$$



MTBF (Mean Time Between Failure)

□ Let's calculate an ASIC for 28nm CMOS process

- τ : 10ps (different FFs have different τ)
- $T_W=20\text{ps}$, $F_C=1\text{GHz}$
- Data changes every ten clock cycles
- Allow 1 clock cycle to resolve metastability, $S=T_C$

$$\text{MTBF} = 4 \times 10^{29} \text{ year !}$$


[For comparison:

Age of oldest hominid fossil: 5×10^6 years

Age of earth: 5×10^9 years]



The Two-Flip-Flop Synchronizer


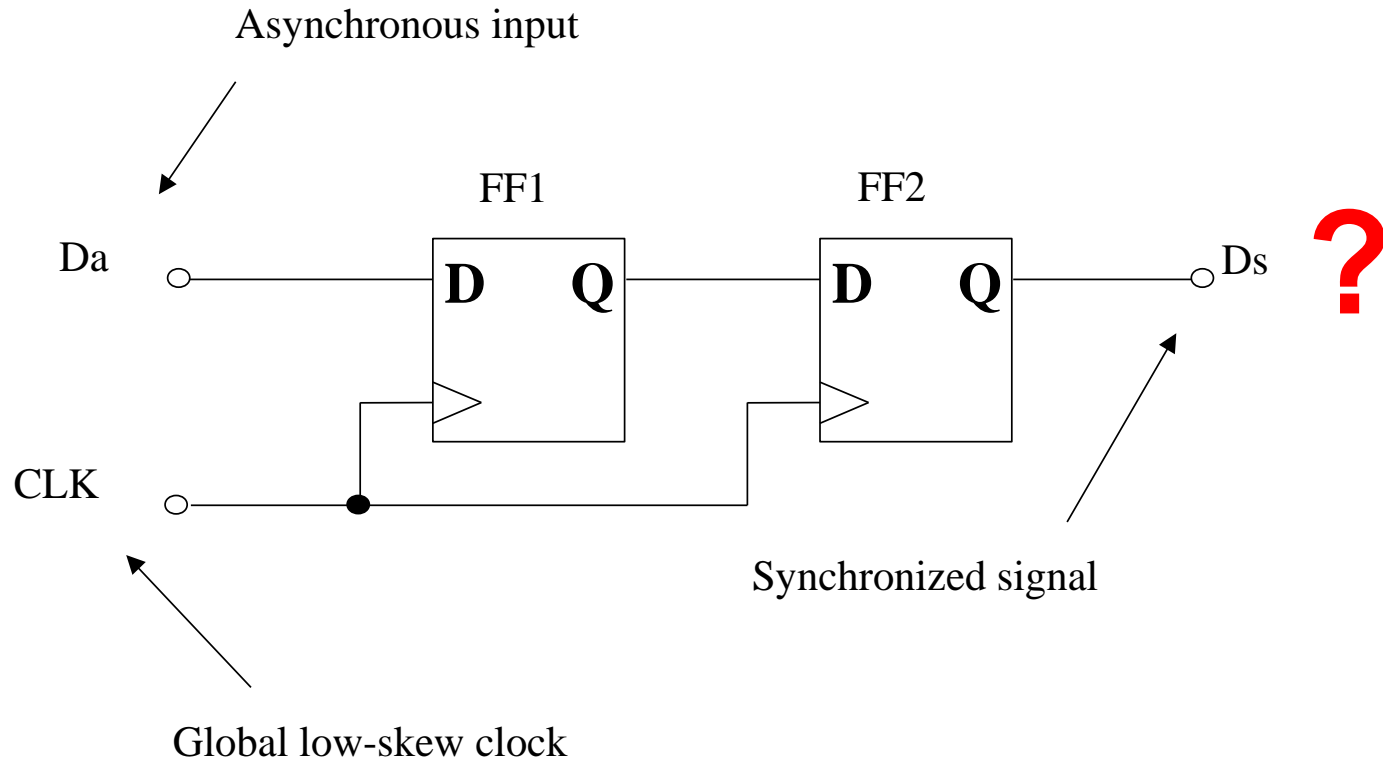


$$S = T_c$$





The Two-Flip-Flop Synchronizer

Possible Outcomes

  

The Two-Flip-Flop Synchronizer

□ Possible Outcomes

  


Open Question: What is the limitation?




The Two-Flip-Flop Synchronizer

□ Problems

- Just ensures that the receiving system does not enter a metastable state
- Not guarantee the **“function”** of the received signal
 - **Uncertainty Remains: Q2 goes high either *one or two* cycles later than the input**
- D1 must stay high for at *least two cycles*.
- How about data bus (**multiple bits**) crossing clock domain?
 - **Some bits may pass through the synchronizer after one cycle while others may take two cycles.**

 

A Complete Synchronizer

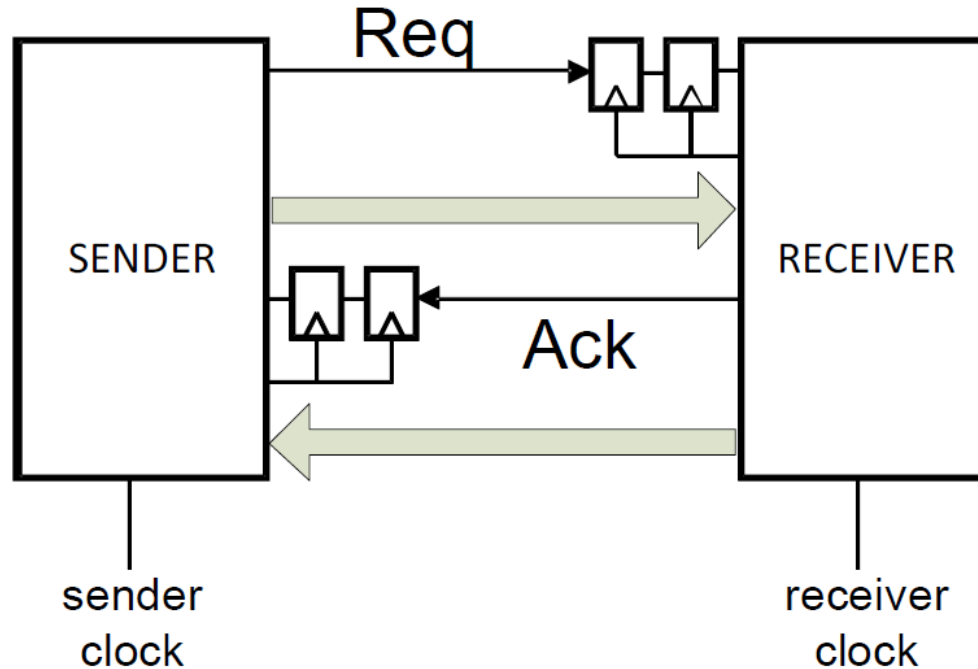


- ❑ The sender place data on the bus
- ❑ The sender sends Req, Req gets synchronized by the top synchronization circuits
- ❑ The receiver gets data and sends back ACK
- ❑ Ack gets synchronized by the sender, and only then is the sender allowed to start a new cycle again.



FIFO

□ FIFO (first in first out) Buffer

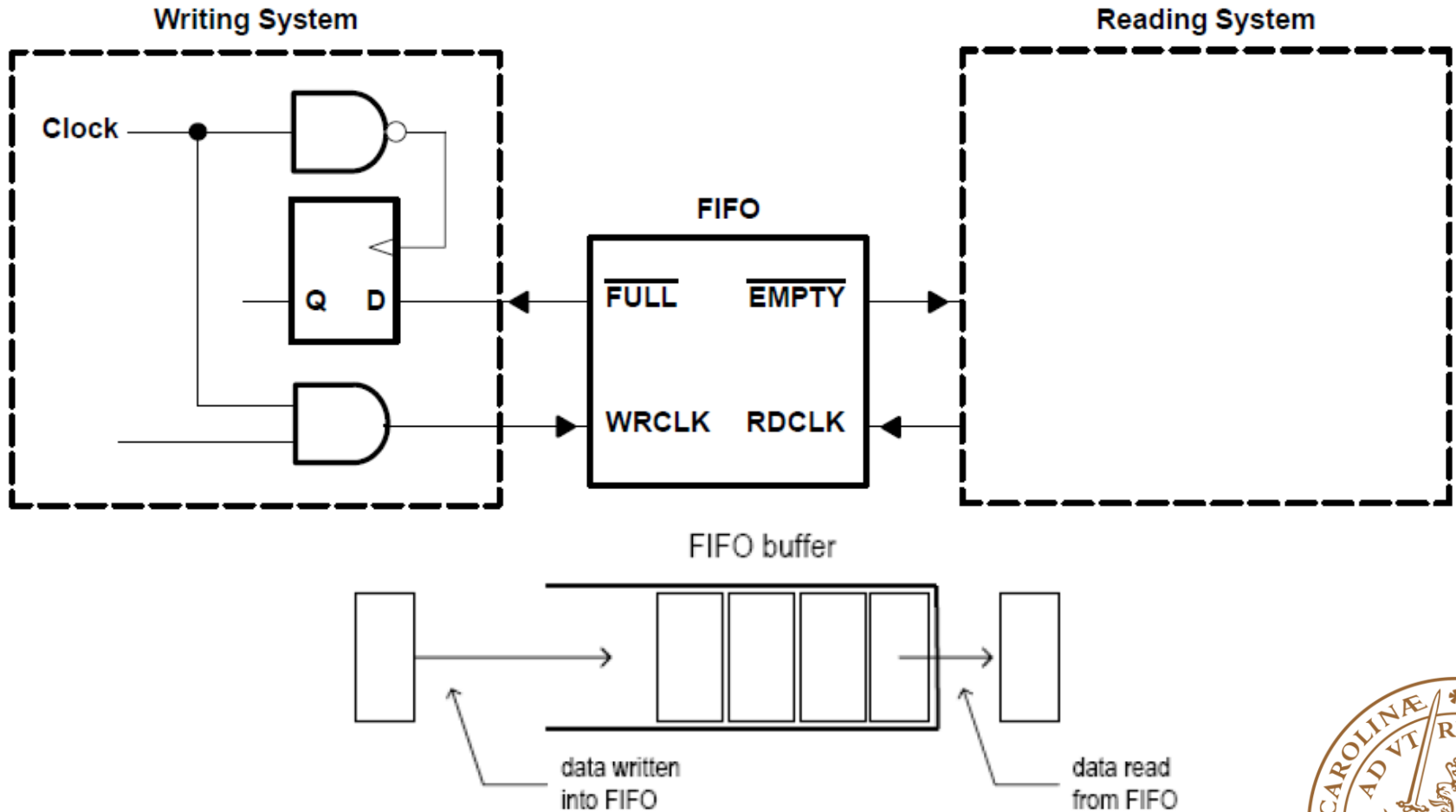- “Elastic” storage between two subsystems




Circular FIFO

□ How to Implement a FIFO?


- Circular queue implementation
- Use two pointers and a “generic storage”
 - **Write pointer:** point to the empty slot before the **head** of the queue
 - **Read pointer:** point to the **tail** of the queue



"First in? First out!"

 

Circular FIFO

 

(c). 4 more writes



FIFO Implementation

Overall Architecture


- Storage Elements

 - Reg. file

- FIFO Controller**

 - Read and write pointers: 2 counters

 - Status circuit: *full, empty*

 

FIFO Implementation: Controller

□ Augmented binary counter:


- Increase the counter by 1 bits
- Use LSBs for as register address
- Use **MSB** to distinguish full or empty

Write pointer	Read pointer	Operation	Status
0 000	0 000	initialization	empty
0 111	0 000	after 7 writes	
1 000	0 000	after 1 write	full
1 000	0 100	after 4 reads	
1 100	0 100	after 4 writes	full
1 100	1 011	after 7 reads	
1 100	1 100	after 1 read	empty
0 011	1 100	after 7 writes	
0 100	1 100	after 1 write	full
0 100	0 100	after 8 reads	empty

0000
0001
0011
0010
0110
0111
0101
0100
1100
1101
1111
1110
1010
1011
1001
1000



A Complete Synchronizer

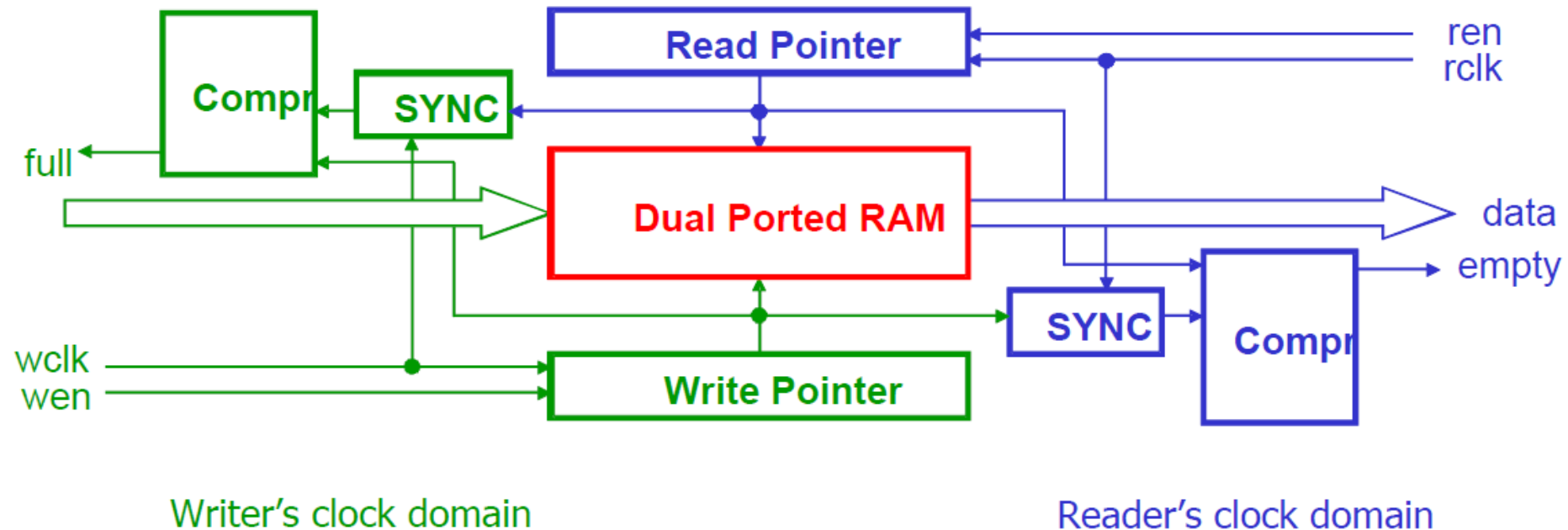

- ❑ **Control signals** are 'synchronized', **data** pass through storage elements
- ❑ Assertion delay, it takes **two clock** cycles for the control signal passing through synchronizer
- ❑ Usually available in libraries
- ❑ The key question, **how large the RAM should be?**
- ❑ "When in doubt, double it"



Outline

□ Crossing clock domain

□ **Reset, synchronous or asynchronous?**



Reset Design Strategy

- ❑ Force the SoC into a known state for stable operations
- ❑ In general, every flip-flop in an SoC (ASIC) should be resettable whether or not it is required by the system
- ❑ Reset might be eliminated for high-performance pipeline FFs
- ❑ Many design issues must be considered before choosing a reset strategy for an ASIC design

Synchronous or Asynchronous?



General Coding Style: FFs

□ Coding for synchronous and asynchronous reset

architecture rtl of goodFFstyle is


```
    signal q1 : std_logic;
begin
    process (clk, rst_n)
    begin
        if (clk'event and clk = '1') then
            if (rst_n = '0') then
                q1 <= '0';
            else
                q1 <= d;
            end if;
        end if;
    end process;
end rtl;
```

architecture rtl of goodFFstyle is

```
    signal q1 : std_logic;
begin
    process (clk)
    begin
        if (clk'event and clk = '1') then
            if (rst_n = '0') then
                q1 <= '0';
            else
                q1 <= d;
            end if;
        end if;
    end process;
end rtl;
```



Synchronous vs. Asynchronous Reset

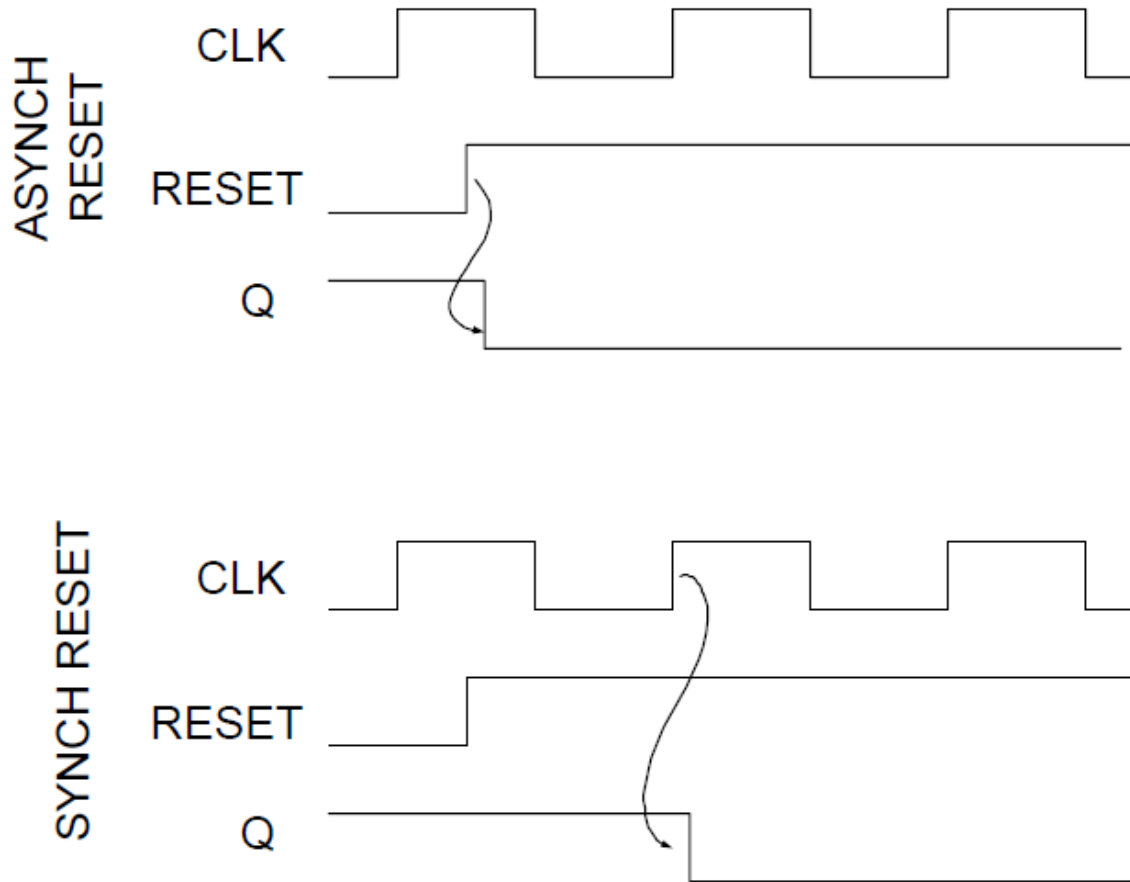

Synchronous vs. Asynchronous Reset

- ❑ 80% designs using synchronous reset (investigation by *Sunburst Design, Inc*)
- ❑ “we all know that the best way to do resets in an ASIC is to strictly use synchronous resets”
- ❑ “asynchronous resets are bad and should be avoided”

- ❑ There are *both advantages and disadvantages* to using either synchronous or asynchronous resets.
- ❑ The designer must use an approach that is appropriate for the design.




Synchronous Reset

reset is not part of the sensitivity list.

```
architecture rtl of ctr8sr is
    signal count : std_logic_vector(8 downto 0);
begin
    co <= count(8);
    q <= count(7 downto 0);

    process (clk)
    begin
        if (clk'event and clk = '1') then
            if (rst_n = '0') then
                count <= (others => '0');
            elsif (ld = '1') then
                count <= '0' & d;
            else
                count <= count + 1;
            end if;
        end if;
    end process;
end rtl;
```

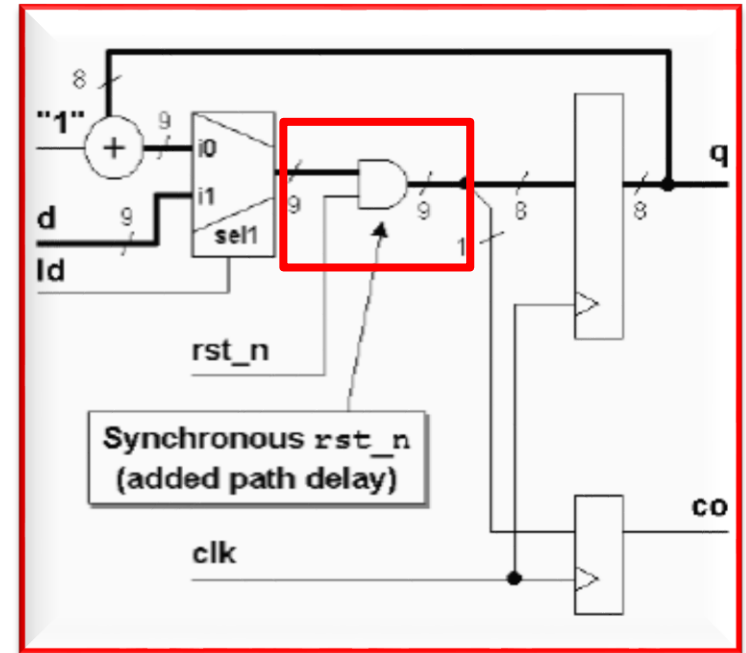-- sync reset
-- sync load
-- sync increment





reset is part of the input path



Synchronous Reset: one problem

 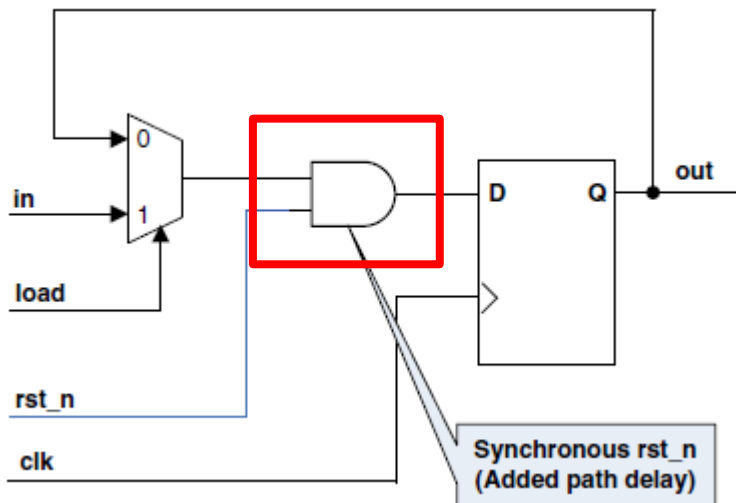- ❑ Synthesis tool may not easily distinguish the reset signal from any other data signal
- ❑ The synthesis tool could alternatively have produced the circuit
- ❑ If synthesis tool can distinguish reset, it will put reset as close to FFs as possible



What ... If 'load=X'
Only a problem in simulation



Synchronous Reset

□ Advantage

- Generally insure that the *circuit is 100% synchronous*.
- Will synthesize to *smaller flip-flops*
- Ensure that reset can only occur at an active clock edge. The clock works as a filter for *small reset glitches*.


□ Disadvantage

- May need a pulse stretcher to guarantee a reset *pulse width* wide enough to ensure reset is present during an active edge of the clock
- Will require a clock in order to reset the circuit, e.g., if you have a gated clock to save power, the *clock may be disabled*



Asynchronous Reset

reset is part of the sensitivity list.

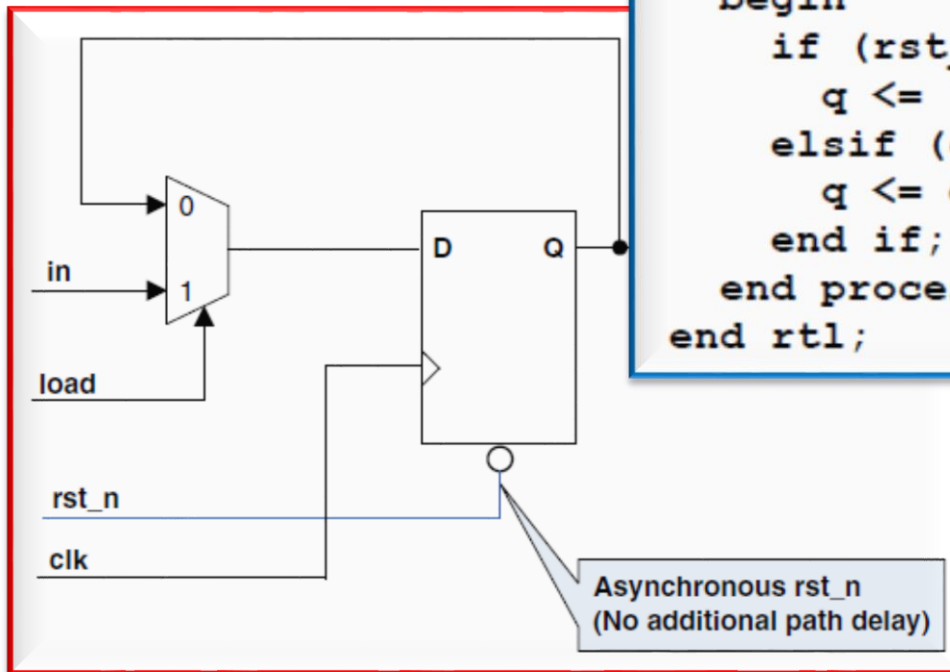

```
architecture rtl of asynresetFFstyle is
begin
  process (clk, rst_n)
  begin
    if (rst_n = '0') then
      q <= '0';
    elsif (clk'event and clk = '1') then
      q <= d;
    end if;
  end process;
end rtl;
```

reset is not part of the input path




Asynchronous Reset

□ Advantage

- The **data path** is guaranteed to be **clean**
 - designs that are pushing the limit for data path timing, cannot afford to have added gates and additional net delays in the data path due to synchronous resets
- The most obvious advantage favoring asynchronous resets is that the circuit can be reset with or **without a clock** present

□ Disadvantage

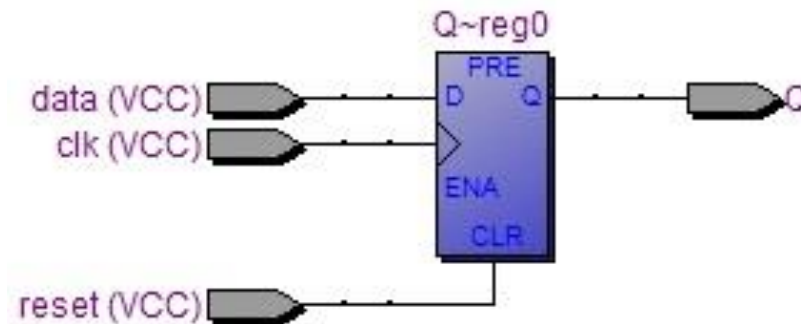- If the asynchronous reset is **released at or near the active clock edge** of a flip-flop, the output of the flip-flop could go **metastable** and thus the reset state of the SoC could be lost.
- **Spurious resets** due to noise or glitches on the board or system reset




Reset Timing



Reset Removal Problem

Reset recovery time:

 - Time between when *reset is de-asserted* and the time that the *clock signal goes high* again.
- Synchronous reset, *both the leading and trailing edges* of the reset must be away from the active edge of the clock.




Active high reset



Reset Removal Problem

Reset removal traversing different clock cycles

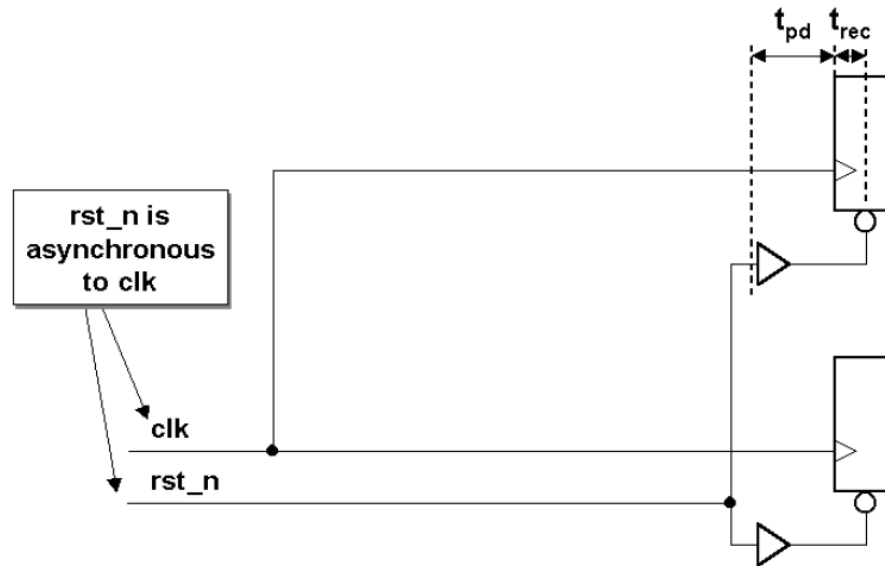- Cause some registers or flip-flops to exit the reset state *before others*
- Reset Buffer Tree



Reset Removal Problem

❑ Reset removal traversing different clock cycles

- ❑ Cause some registers or flip-flops to exit the reset state *before others*
- ❑ Especially for high-rate clock and big chip
- ❑ Reset Buffer Tree

 


Figure 3: Reset Timing Diagram - High Clock Rate

Active high reset



But... Does it really matter?

□ Single pipeline stage?

- After a few cycles, the entire pipeline will be operational
- Any incorrect data will be flushed out of the system
- In fact, there is little point in having a reset at all


 


Figure 4: Reset for a Pipeline

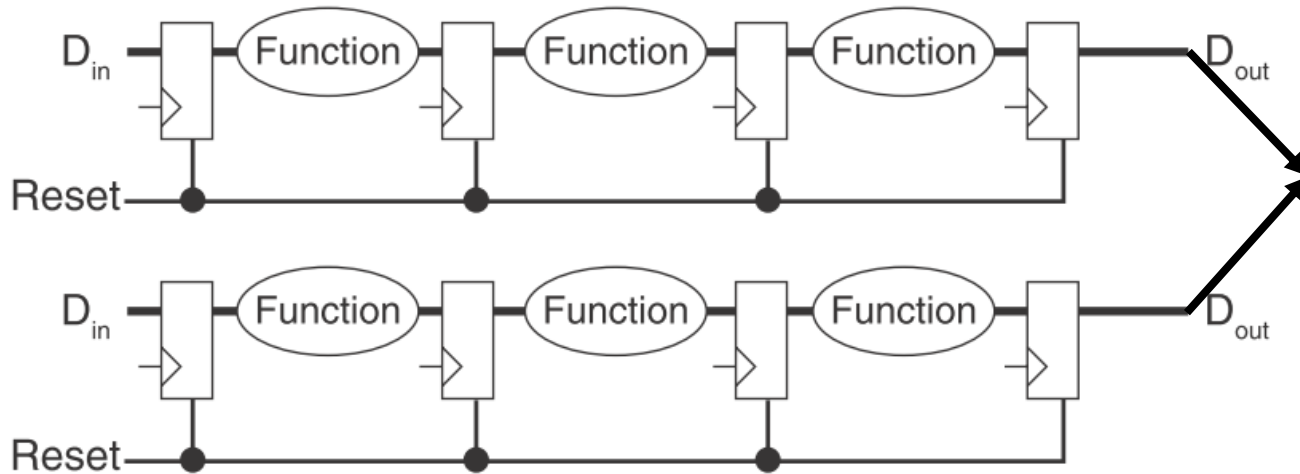


But... Does it really matter?

Parallel pipeline



Pipeline with feedback

 


WP272_05_010708




Reset Synchronizer

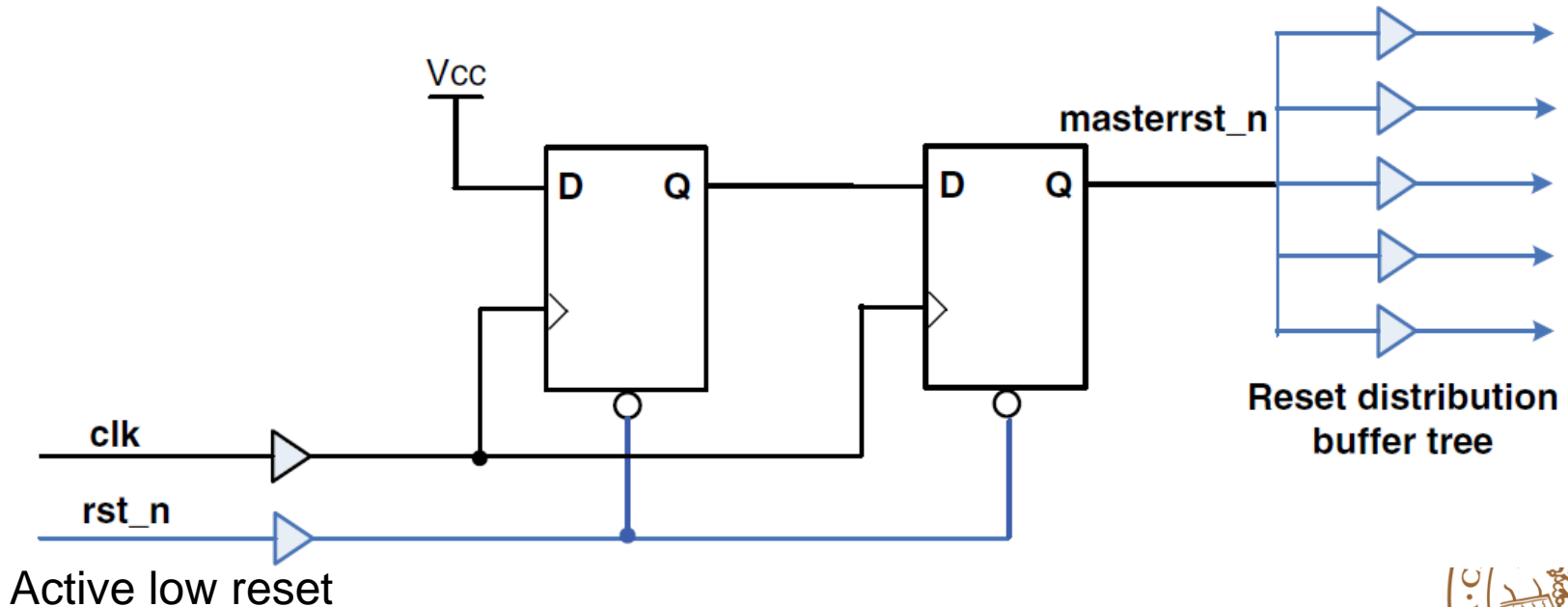- An external reset signal asynchronously resets *a pair of master reset flip-flops*, which in turn drive the master reset signal *asynchronously*
- Take advantage of the best of both asynchronous and synchronous reset styles.
- Takes *two rising clock edges* after reset removal to synchronize removal of the master reset.
- *No metastability problems* on the second flip-flop when reset is removed



Reset Glitch Filter

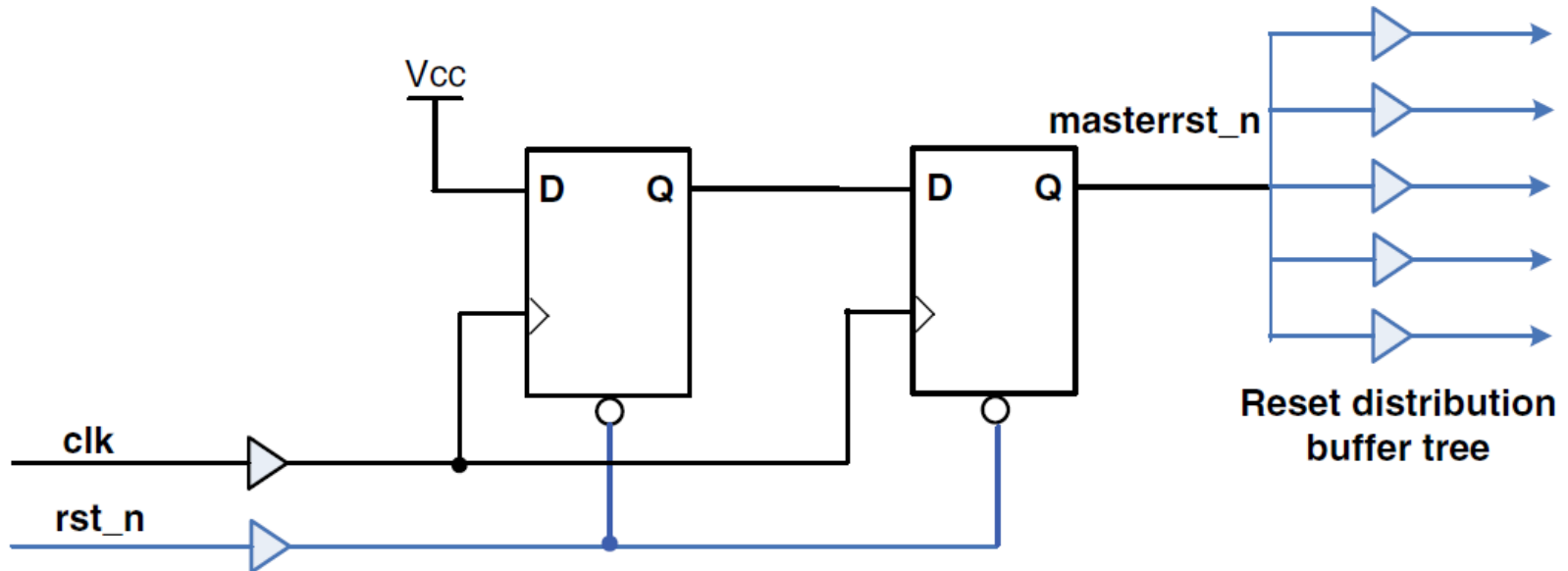Any input wide enough to meet the minimum reset pulse width for a flip-flop will cause the flip-flop to reset



Active low reset




Reset Glitch Filter

Any input wide enough to meet the minimum reset pulse width for a flip-flop will cause the flip-flop to reset

Delay line:

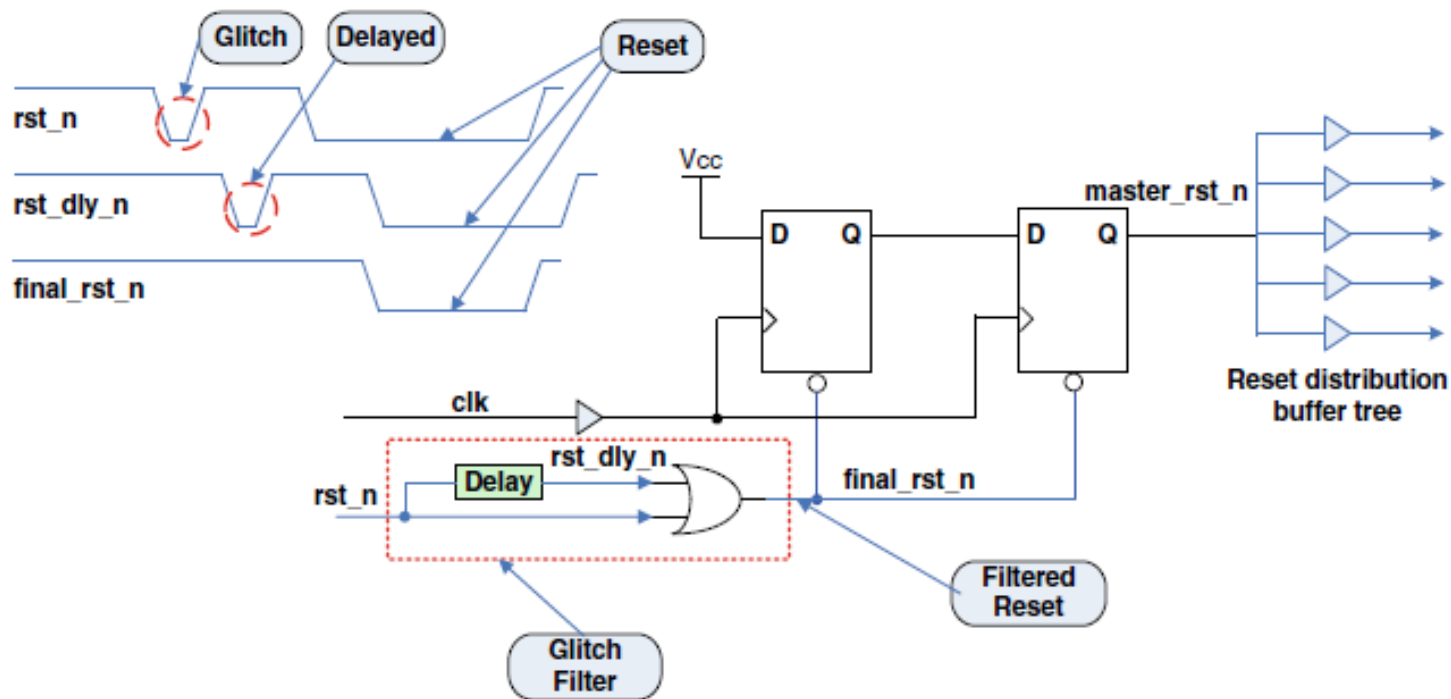- Vendors provide a delay hard macro that can be hand instantiated
- Instantiate a slow buffer in a module



Active low reset



Xilinx Reset

One of the commandments of digital design states, "Thou shalt have a master reset for all flip-flops so that the test engineer will love you, and your simulations will not remain undefined for time eternal."

So, some may be surprised to learn that applying a global reset to your FPGA designs is not a very good idea and should be avoided. Clearly, this is a controversial issue, so let's take a look at the reasons why such a design policy should be considered.



Xilinx Reset: covering 99.99% of cases

Initialization after configuration (power-on reset)

- Has the same effect as a global reset
- It also initializes all RAM cells
- All program and data areas are defined even before the processor executes the first instruction


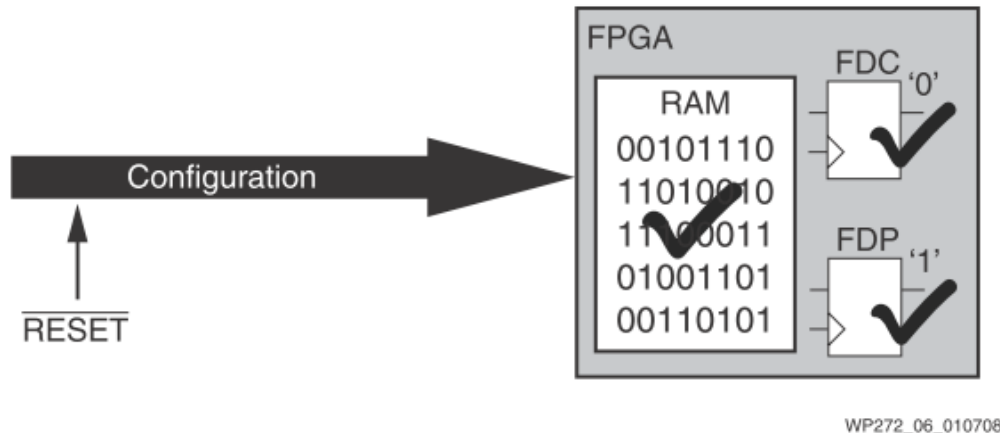


Figure 6: FPGA Configuration

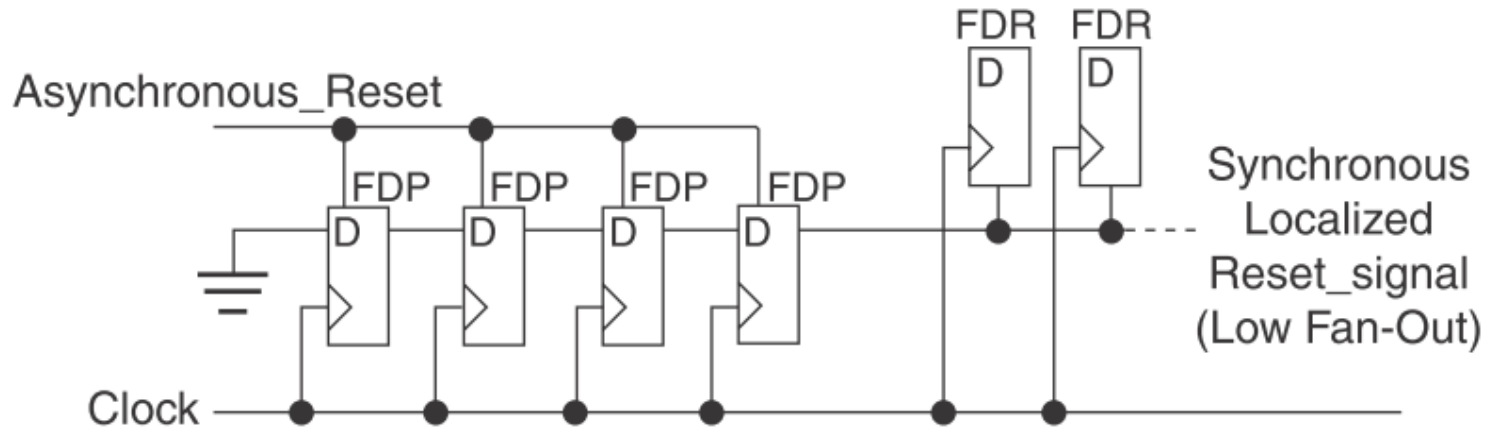

Xilinx Reset: Strategy for the 0.01% of Cases



WP272_07_010708



Reference Readings

Simulation and Synthesis Techniques for Asynchronous FIFO Design

“Synchronous Resets? Asynchronous Resets? I am so confused! How will I ever know which to use?”

Get Smart About Reset: Think Local, Not Global

http://www.xilinx.com/support/documentation/white_papers/wp272.pdf

Get your Priorities Right – Make your Design Up to 50% Smaller

http://www.xilinx.com/support/documentation/white_papers/wp275.pdf



Lecture

- ❑ No lecture tomorrow
- ❑ Sept. 28th Monday (8.15-10.00)



Design for Test (DFT)

Erik Larsson

Associate Professor

- ❑ Sept. 29th Tuesday (8.30-10.00)



Igor Tasevski

