

Lab Assignment 2



Interfacing Keyboard with FPGA Board

Siyu Tan

Room - 2335

siyu.tan@eit.lth.se

Keyboard Clk and Data



- Interface the USB keyboard.
- It uses two signals (keyboard data and clock)
- Interface protocol (LSB first)

 


Figure 1: Key Board interface waveform



Make code & Break code


- When key pressed, a make code is generated.
- When key is released a break code is generated.

key	make	break
A	'1C'h	'F0'h '1C'h
B	'32'h	'F0'h '32'h
C	'21'h	'F0'h '21'h



Scan codes

 
- Each key is assigned a unique scan code.



FPGA



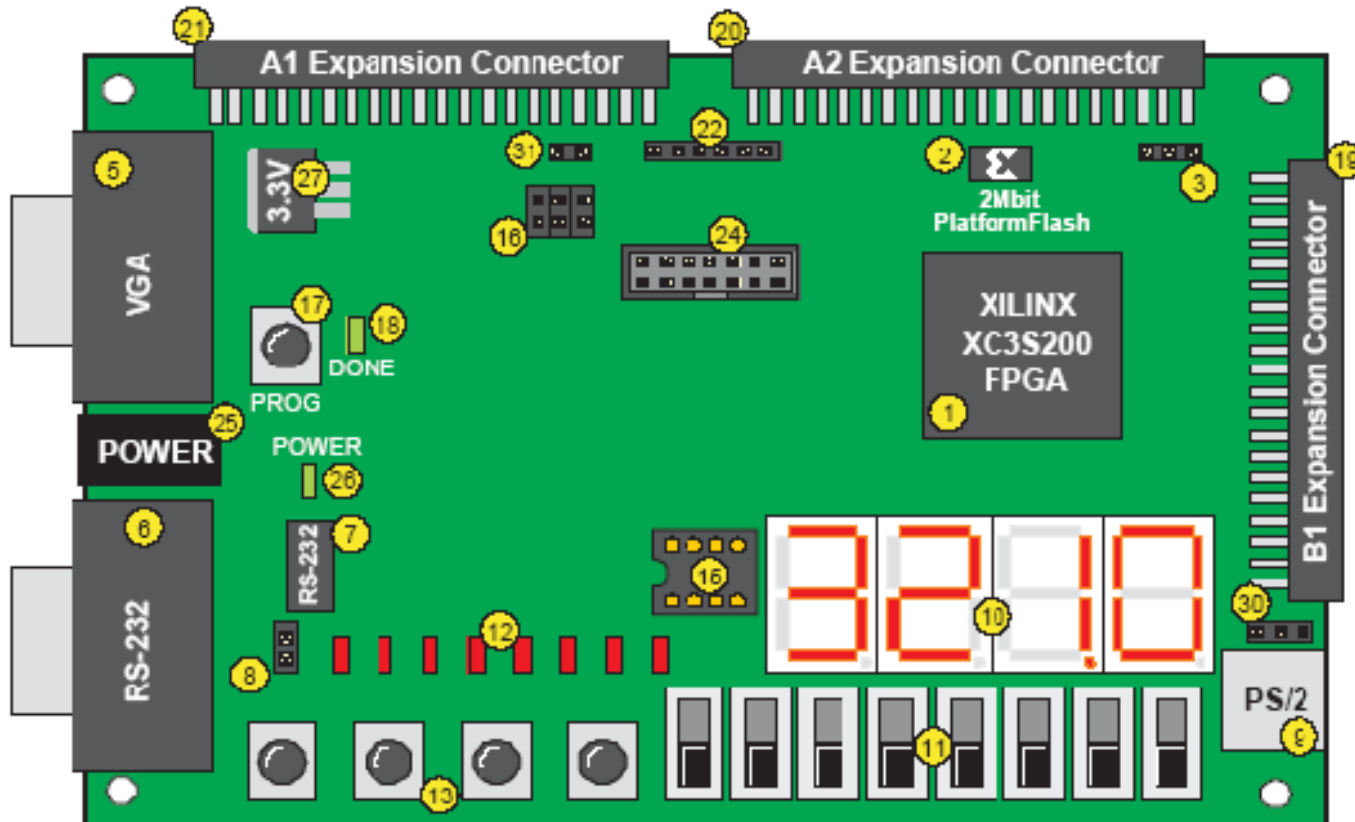- Pressed key shows on FPGA -- 7 SEGEMENT DISPLAY



Demostration



- Check the reset condition, all display should be switched off at reset.
- Pressing "123456" one by one, the display should look the following:

Seven Segement Display

DISPLAY OFF			
			1
		1	2
	1	2	3
1	2	3	4
2	3	4	5
3	4	5	6

press (sw0) reset

press 1

press 2

press 3

press 4

press 5


press 6

Main Processes



- **Synchronizing Keyboard with FPGA.**
- **Detection of falling edge of keyboard Clock.**
- **Storing of relevant Data (Scan Code).**
- **Display of 'numbers' keys on Seven Segment.**
- **Shift the previous key left and display the current number when the next number key is pressed.**

Tasks

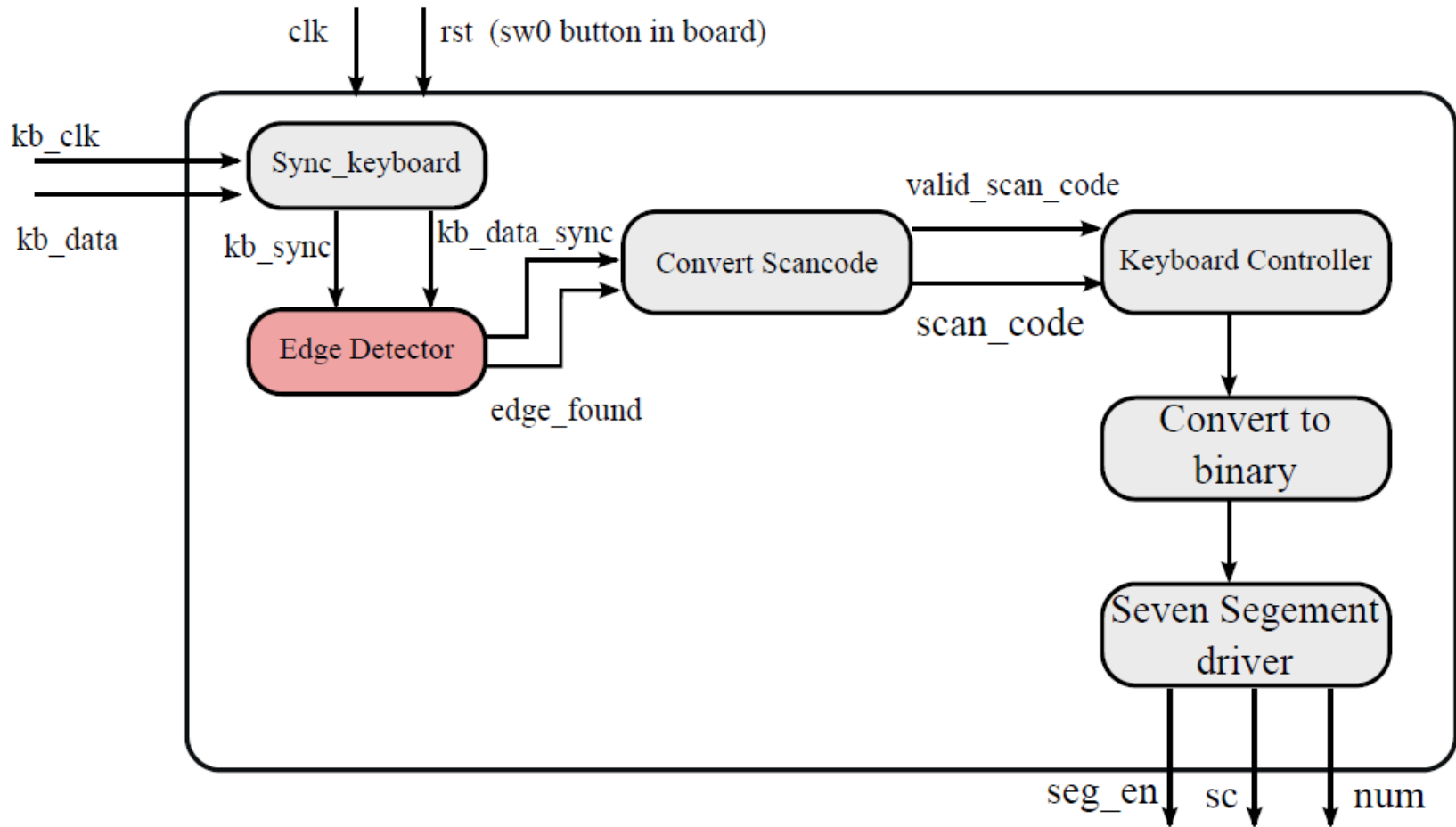

VHDL File Lists



File Name

keyboard_top.vhd

sync_keyboard.vhd

edge_detector.vhd

convert_scancode.vhd

keybaord_ctrl.vhd

convert_to_binary.vhd

binary_to_sg.vhd

keyboard_top.xdc

tb_pkg.vhd

tb_keyboard.vhd

input.txt

Function

Top level integration file

Synchronize keyboard data

Edge detection circuit

Convert serial data to parallel

Keyboard controller

Convert scan code to binary

Seven segment driver

Pin mapping to FPGA board.

Required for some functions in testbench

test bench to drive stimulus

Keys to be sent to design via testbench.