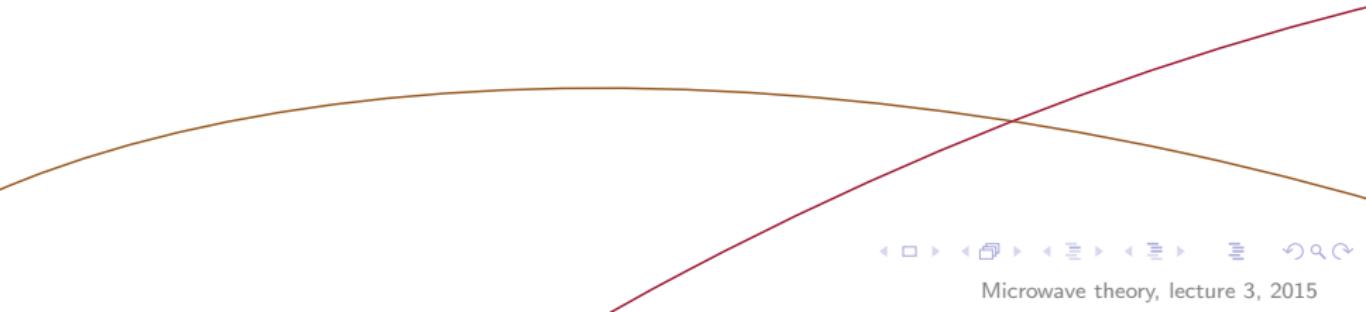




Microwave theory, lecture 3, 2015

Anders Karlsson, anders.karlsson@eit.lth.se

Electrical and information technology




Last lecture

- ▶ Standing wave ratio (SWR)
- ▶ Lossy line

Today

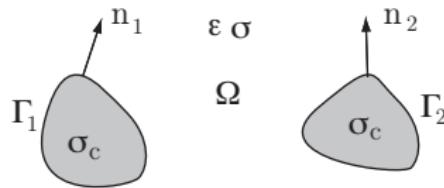- ▶ Determination of R, L, G, C
- ▶ COMSOL example
- ▶ S -parameters
- ▶ Smith chart
- ▶ Introduction to hollow waveguides



Solve Laplace equation $\nabla^2 \Phi(x, y)$ in Ω .

$$\nabla^2 \Phi(x, y) = 0$$

$$\Phi(x, y) = \begin{cases} V/2 & \text{on } \Gamma_1 \\ -V/2 & \text{on } \Gamma_2 \end{cases}$$

$$C = \frac{Q}{V} = \frac{\oint_{\Gamma_1} \rho_S d\ell}{V}$$

or

$$C = 2 \frac{W_e}{V^2}$$


$$L = \frac{\mu_0 \epsilon_0 \epsilon}{C} \text{ (if losses are small)}$$

$$G = \frac{C\sigma}{\epsilon_0 \epsilon}$$

$$R = R_s \frac{\int_{\Gamma_1 + \Gamma_2} (\rho_S)^2 d\ell}{\left(\int_{\Gamma_1} \rho_S d\ell \right)^2}$$

$$R_S = \sqrt{\frac{\omega \mu_0}{2\sigma_c}} = \text{surface resistance.}$$

Smith chart

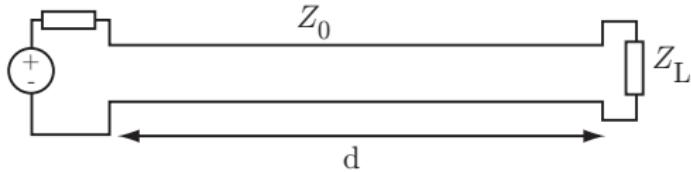


$$\Gamma(0) = \frac{Z(0) - Z_0}{Z(0) + Z_0} = \frac{Z_L - Z_0}{Z_L + Z_0} e^{-2j\beta d} = \Gamma_d e^{-2j\beta d}$$

Normalize with Z_0

$$z(0) = \frac{Z(0)}{Z_0} = \frac{R(0) + jX(0)}{Z_0} = r(0) + jx(0)$$

$$z_L = \frac{Z_L}{Z_0}$$



Smith chart

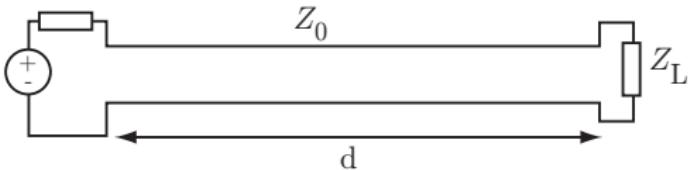


$$\Gamma(0) = \frac{z(0) - 1}{z(0) + 1} = \frac{z_L - 1}{z_L + 1} e^{-2j\beta d}$$

Plot $\Gamma(0)$, $r(0)$, $x(0)$ in the same diagram \Rightarrow Smith chart!


Smith chart

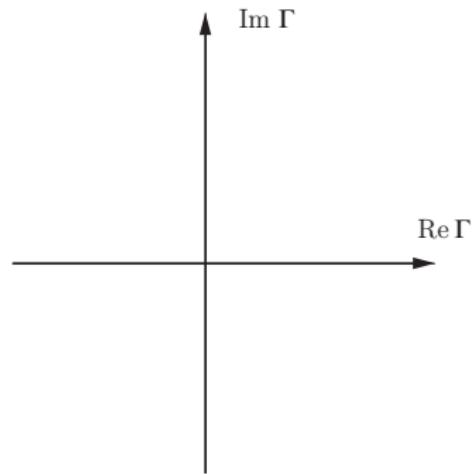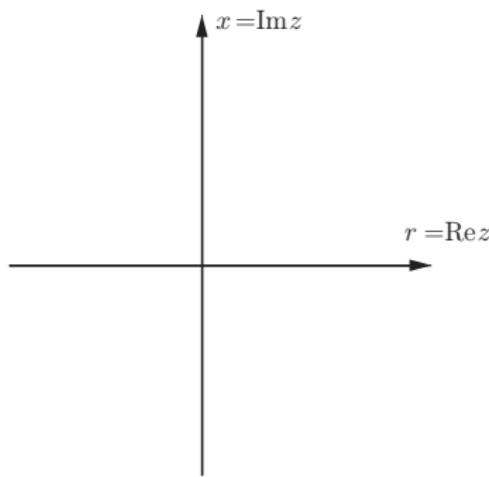


Smith chart

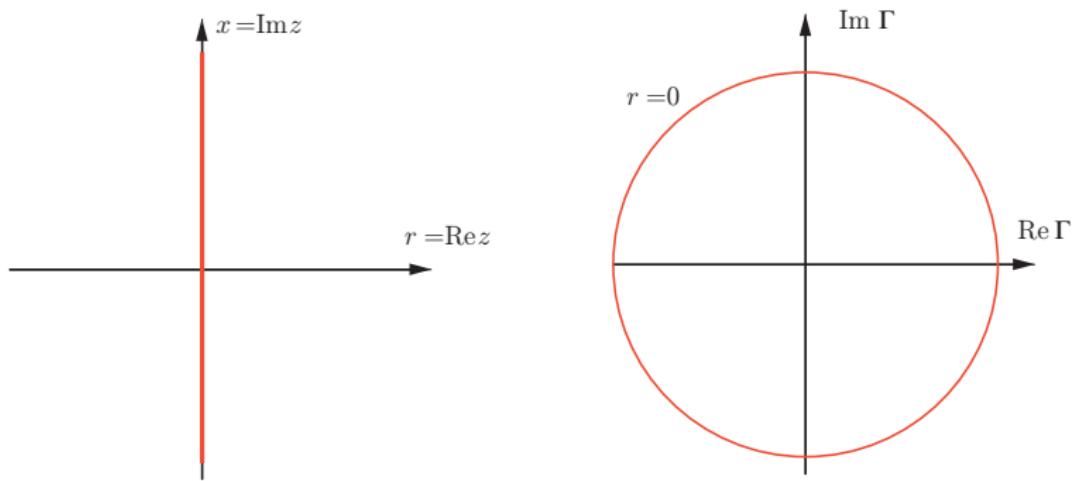



Smith chart

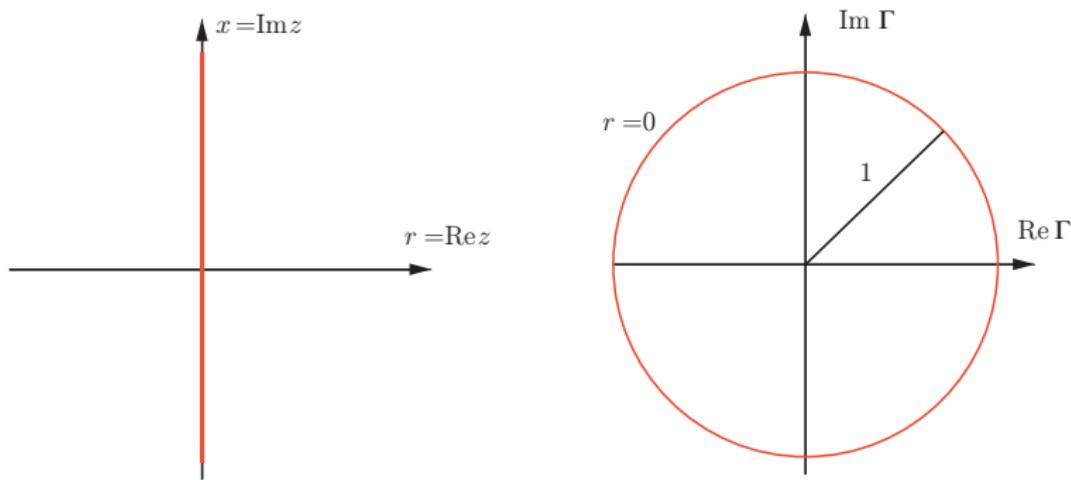



Smith chart

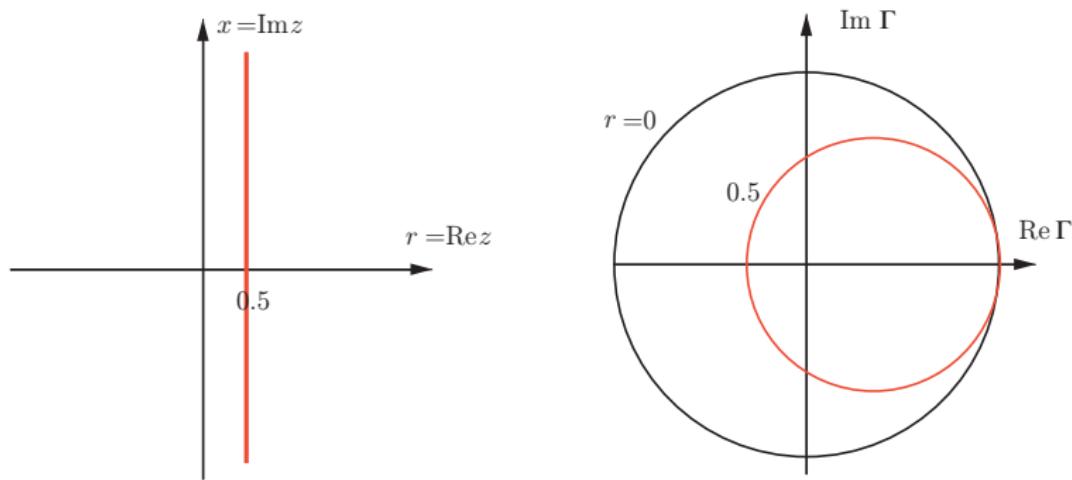


Smith chart

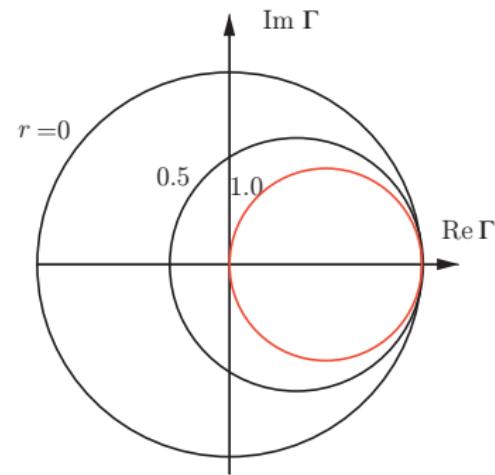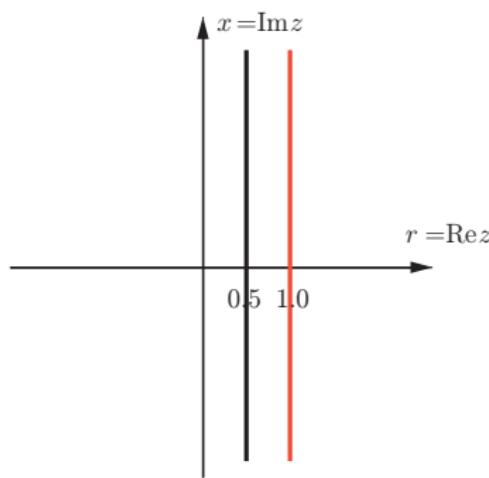


Smith chart

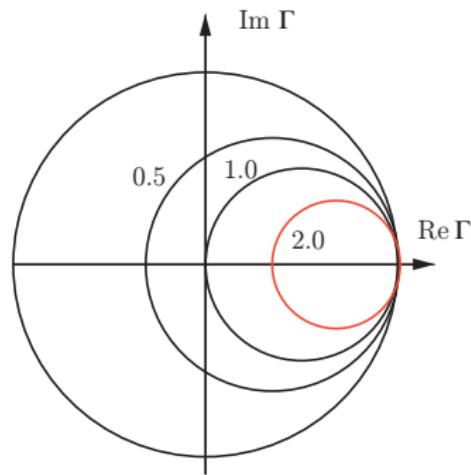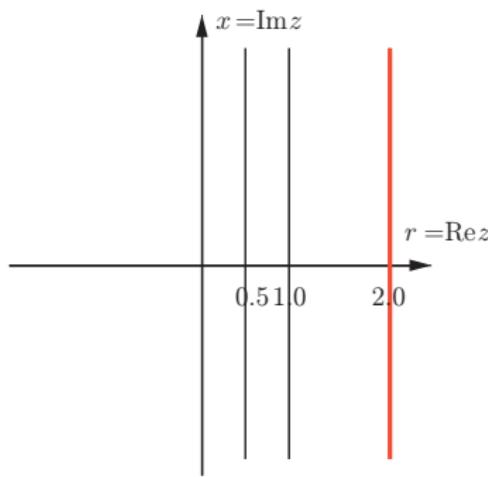


Smith chart

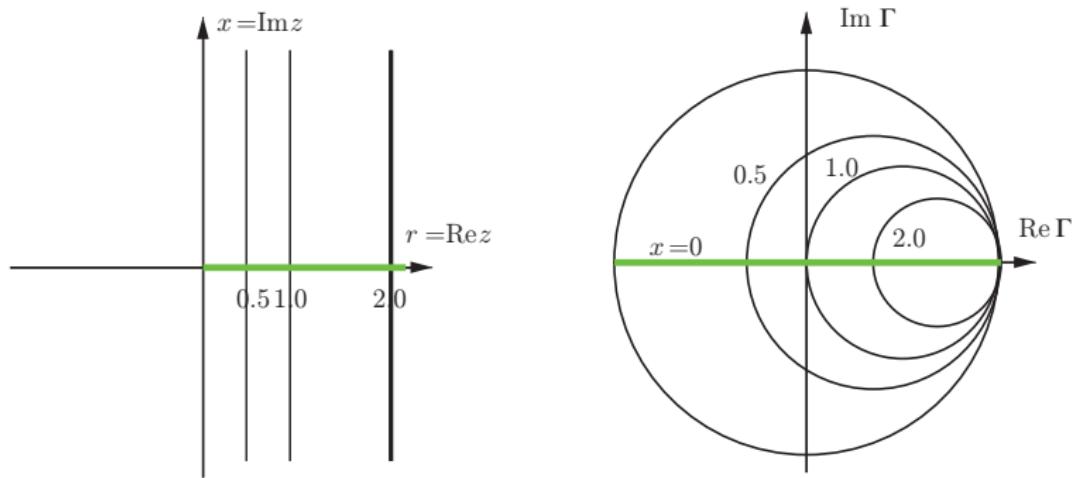

Smith chart

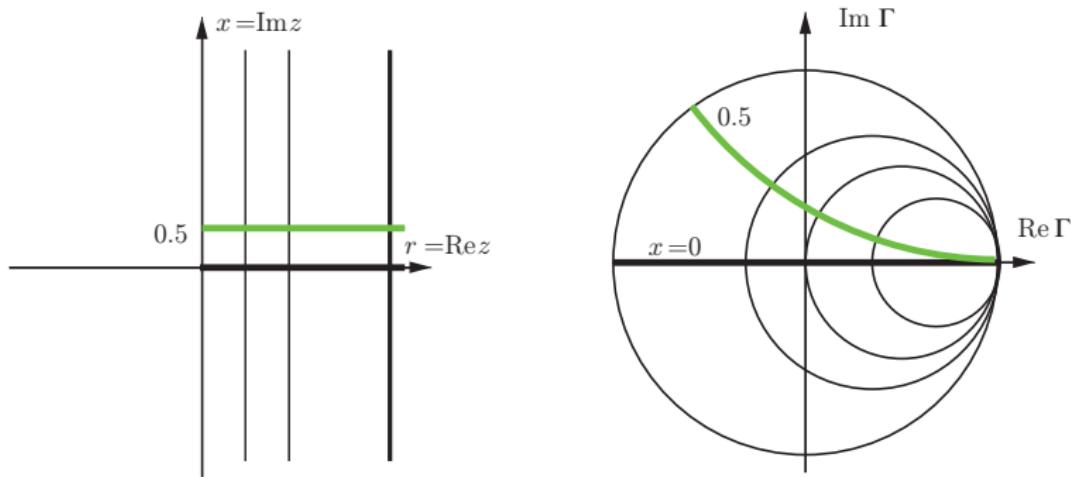


Smith chart

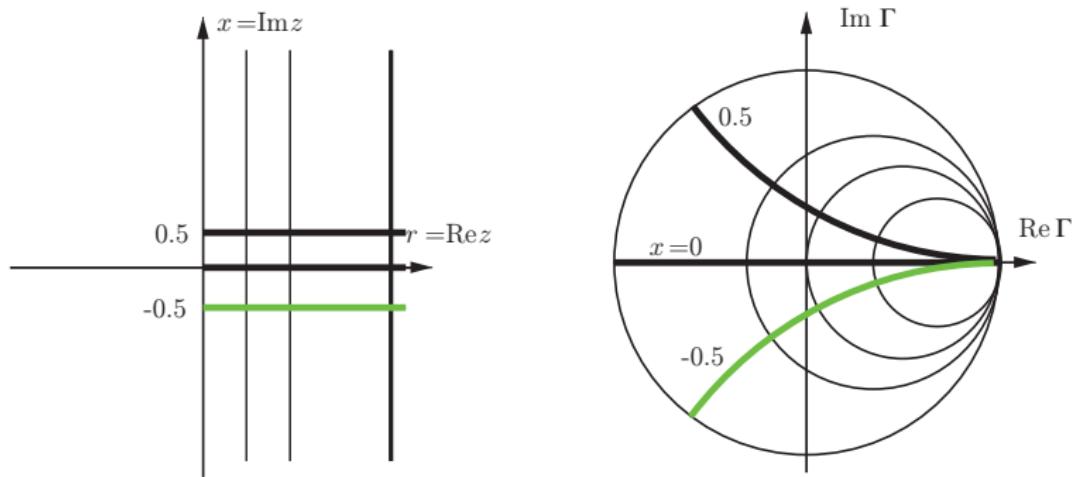



Smith chart

The Complete Smith Chart

Black Magic Design

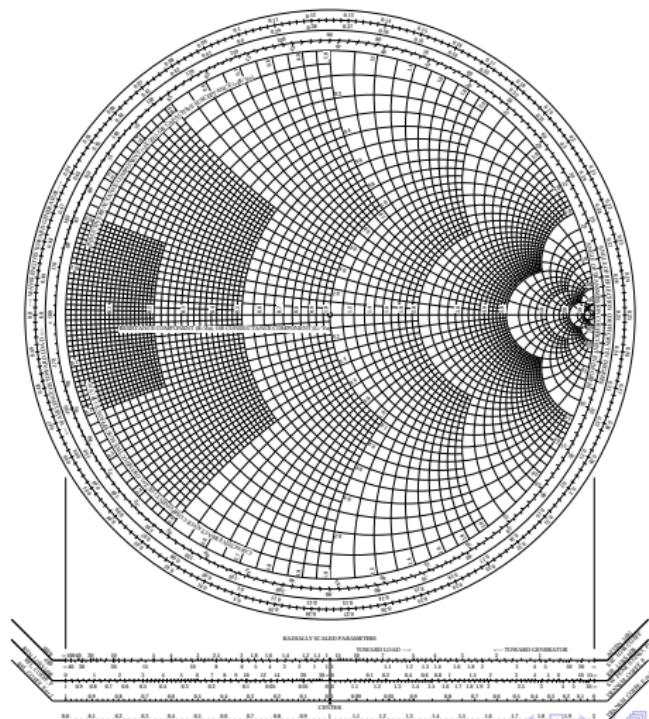


Smith chart: example 1

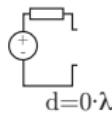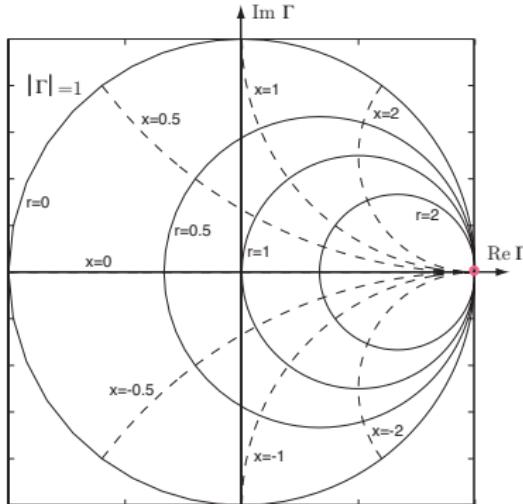


$$\beta d = 0 \Rightarrow \Gamma(0) = \Gamma_d = 1$$

Smith chart: example 1

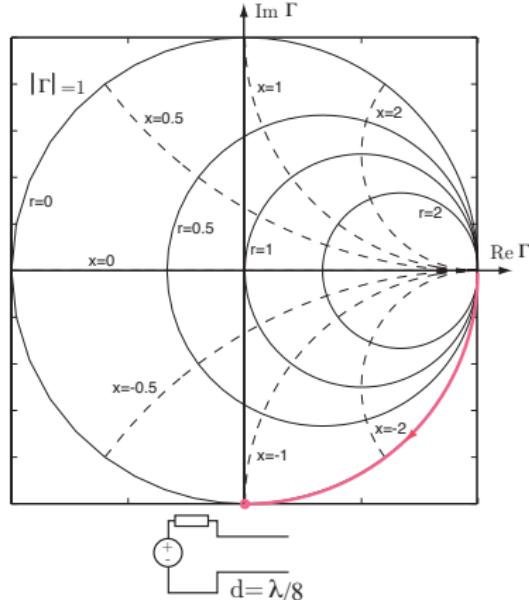


$$\beta d = \pi/4 \Rightarrow \Gamma(0) = -i$$

Smith chart: example 1

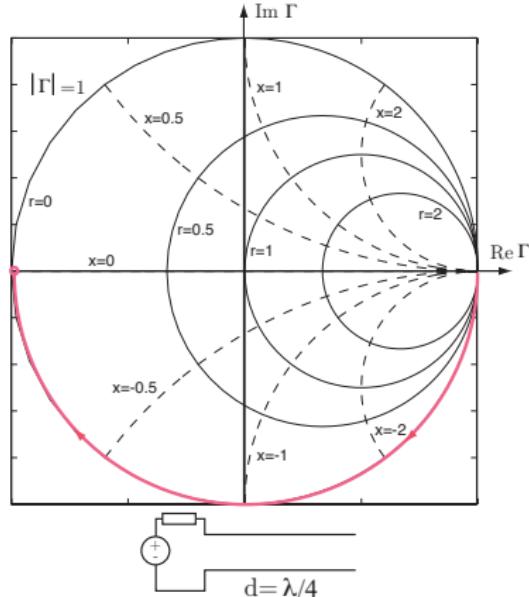


$$\beta d = \pi/2 \Rightarrow \Gamma(0) = -1$$

Smith chart: example 1

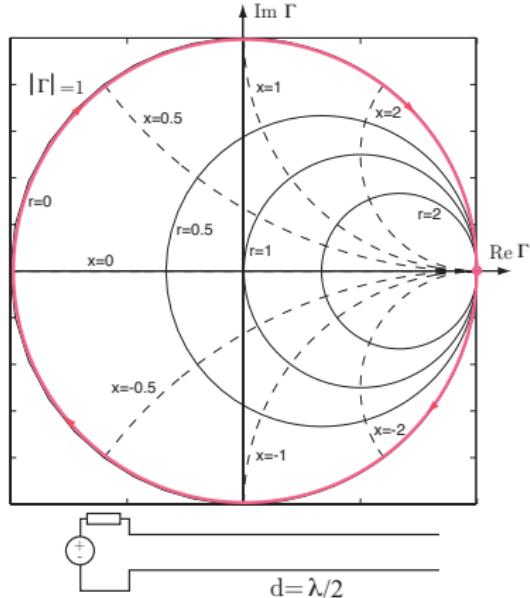


$$\beta d = \pi \Rightarrow \Gamma(0) = \Gamma_d = 1$$

Smith chart: example 2

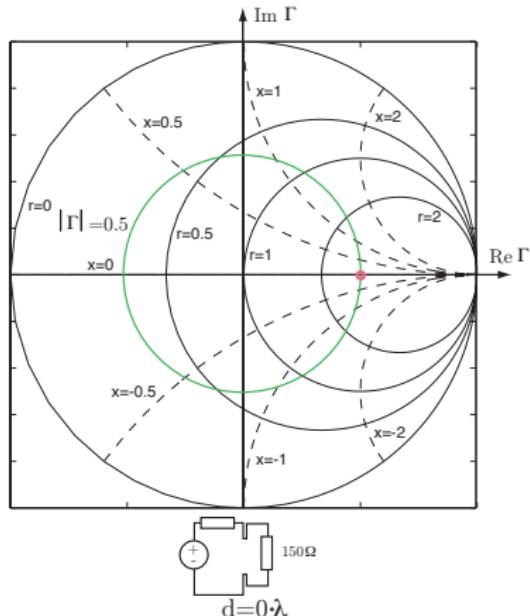


$$\beta d = 0 \Rightarrow \Gamma(0) = \Gamma_d = \frac{150 - 50}{150 + 50} = 0.5$$

Smith chart: example 2

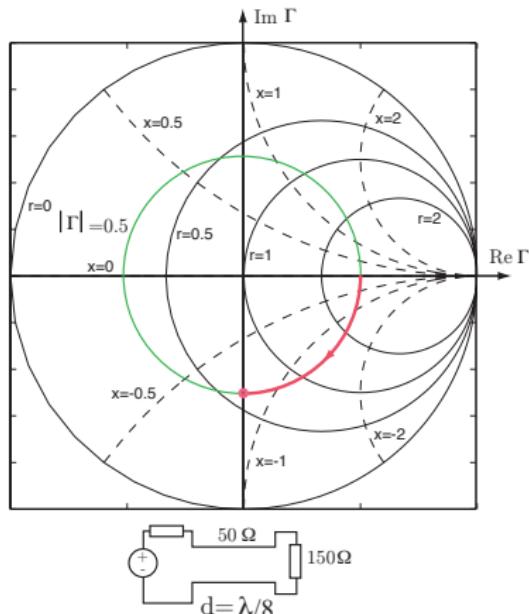


$$\beta d = \pi/4 \Rightarrow \Gamma(0) = -0.5i$$

Smith chart: example 2

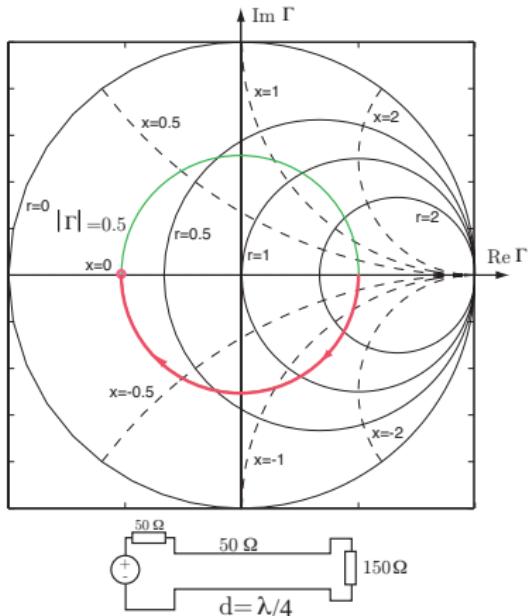

$$\beta d = \pi/2 \Rightarrow \Gamma(0) = -0.5$$

Smith chart: example 2

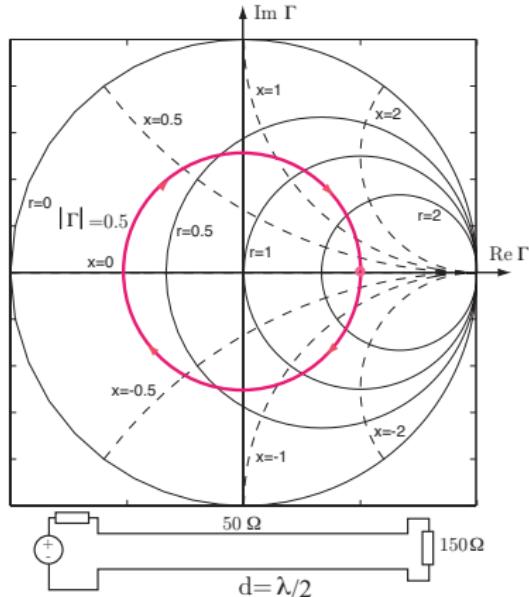

$$\beta d = \pi \Rightarrow \Gamma(0) = \Gamma_d = 0.5$$

Smith chart

The admittance diagram


$$Y = \frac{1}{Z} = G + jB = \text{admittance}$$

G = conductance, B = susceptance.

$$\Gamma(0) = \frac{z(0) - 1}{z(0) + 1} = \frac{1 - y(0)}{1 + y(0)} = -\frac{y(0) - 1}{y(0) + 1}$$

Go to $-\Gamma$ in Smith chart and exchange g for r and b for x .


Smith chart

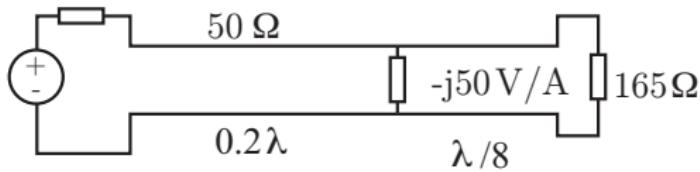

Smith chart

The Complete Smith Chart

Black Magic Design

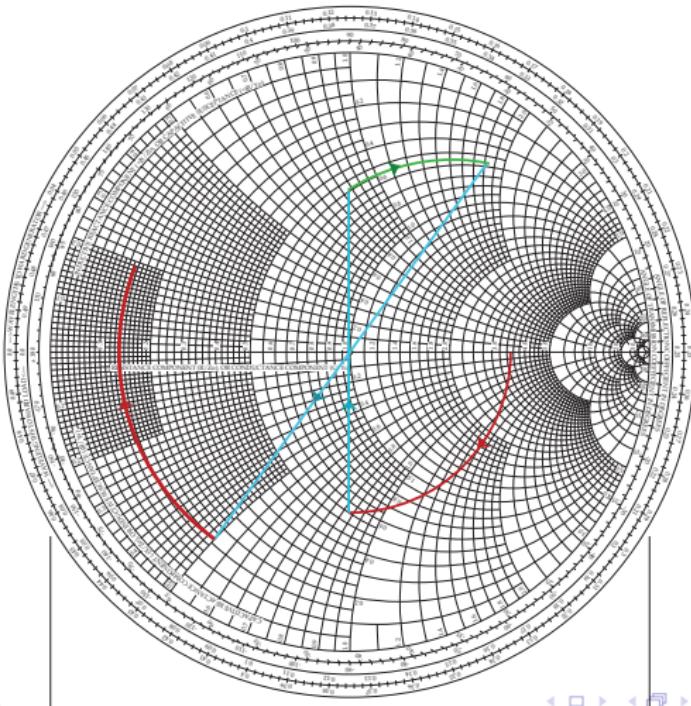

Impedance match by Smith chart


Goal: Try to reach $z = 1 \Rightarrow \Gamma = 0$.

Rules:

- ▶ You cannot add resistance, only reactive components.
- ▶ You are allowed to move along the transmission line.
- ▶ You are allowed to go to admittance diagram and add susceptance.

Impedance match by Smith chart example

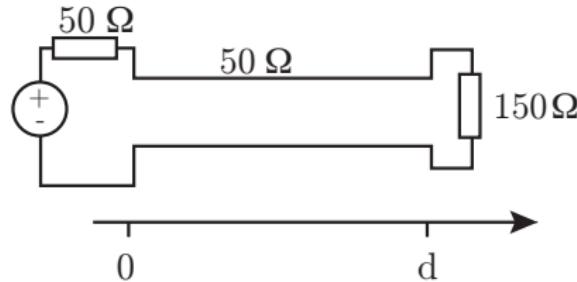
Goal: Match with two reactive components at $z = d$.




Impedance match by Smith chart example

The Complete Smith Chart

Black Magic Design

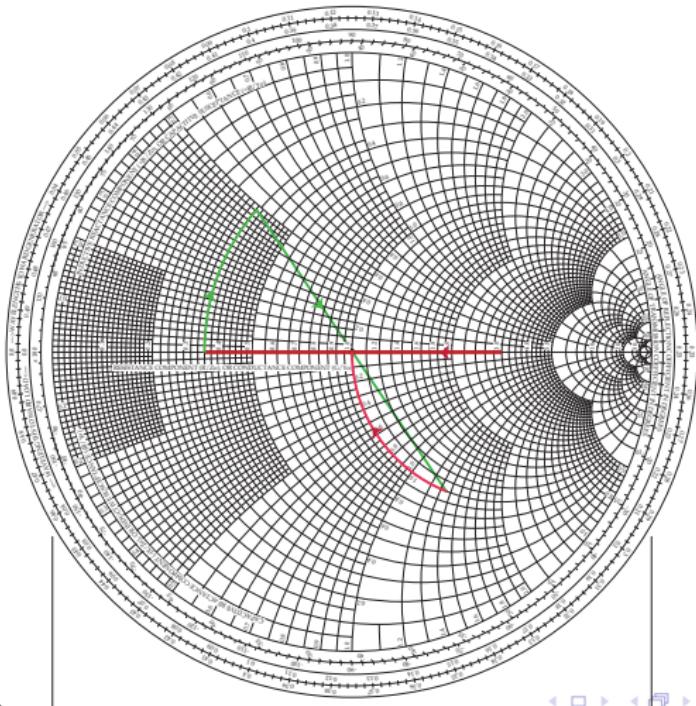

Impedance match by Smith chart example

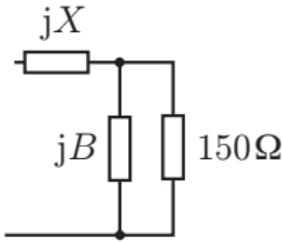

$$B = \frac{0.475}{50} = 9.5 \text{ mA/V} \text{ and } X = 1.38 \cdot 50 = 69 \text{ V/A.}$$

$$Z = j69 + \frac{1}{\frac{1}{150} + j\frac{0.475}{50}} \approx 49.5 \Omega - j1.5 \text{ V/A}$$