



# Microwave theory, lecture 3, 2016

Anders Karlsson, anders.karlsson@eit.lth.se

Electrical and information technology

# Last lecture

---

- ▶ Standing wave ratio (SWR)
- ▶ Lossy line


# Today

---

- ▶ Determination of  $R$ ,  $L$ ,  $G$ ,  $C$
- ▶ COMSOL example
- ▶  $S$ -parameters
- ▶ Smith chart
- ▶ Introduction to hollow waveguides

# $R, L, G, C$

---

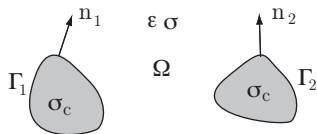

Solve Laplace equation  $\nabla^2 \Phi(x, y)$  in  $\Omega$ .

$$\nabla^2 \Phi(x, y) = 0$$

$$\Phi(x, y) = \begin{cases} V/2 & \text{on } \Gamma_1 \\ -V/2 & \text{on } \Gamma_2 \end{cases}$$

$C$

---

$$C = \frac{Q}{V} = \frac{\oint_{\Gamma_1} \rho_S dl}{V}$$

or

$$C = 2 \frac{W_e}{V^2}$$

# $L, G, R$

---


$$L = \frac{\mu_0 \epsilon_0 \epsilon}{C} \text{ (if losses are small)}$$

$$G = \frac{C \sigma}{\epsilon_0 \epsilon}$$

$$R = R_s \frac{\int_{\Gamma_1 + \Gamma_2} (\rho_S)^2 dl}{\left( \int_{\Gamma_1} \rho_S dl \right)^2}$$

$$R_s = \sqrt{\frac{\omega \mu_0}{2 \sigma_c}} = \text{surface resistance.}$$

# Smith chart

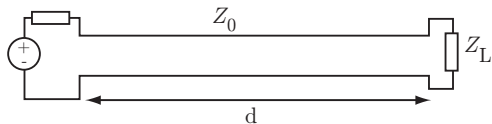

$$\Gamma(0) = \frac{Z(0) - Z_0}{Z(0) + Z_0} = \frac{Z_L - Z_0}{Z_L + Z_0} e^{-2j\beta d} = \Gamma_d e^{-2j\beta d}$$


Normalize with  $Z_0$

$$z(0) = \frac{Z(0)}{Z_0} = \frac{R(0) + jX(0)}{Z_0} = r(0) + jx(0)$$

$$z_L = \frac{Z_L}{Z_0}$$

# Smith chart

---

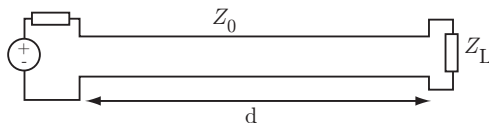



$$\Gamma(0) = \frac{z(0) - 1}{z(0) + 1} = \frac{z_L - 1}{z_L + 1} e^{-2j\beta d}$$

Plot  $\Gamma(0)$ ,  $r(0)$ ,  $x(0)$  in the same diagram  $\Rightarrow$  Smith chart!





# Smith chart

---

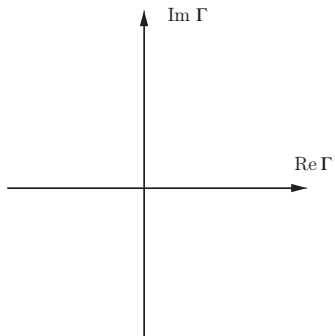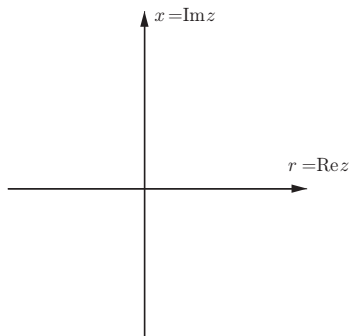



# Smith chart

---

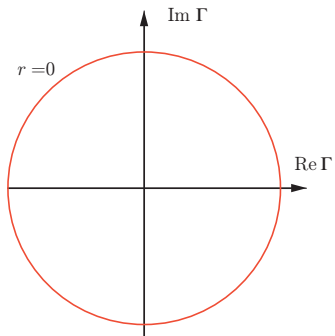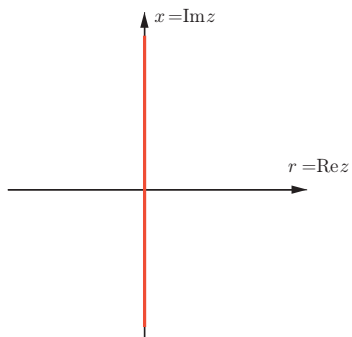



# Smith chart

---

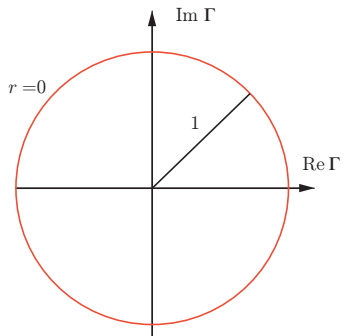
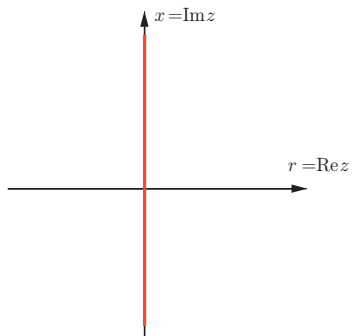


# Smith chart



---

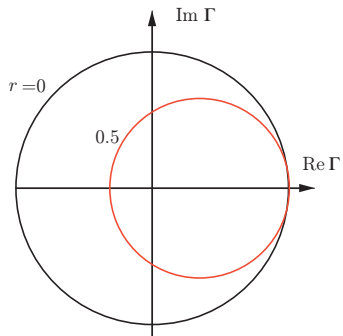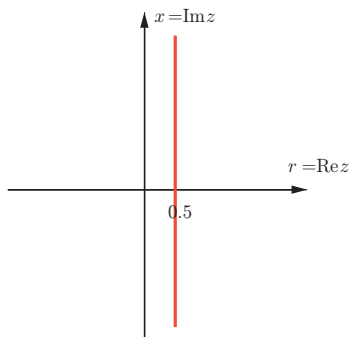



# Smith chart

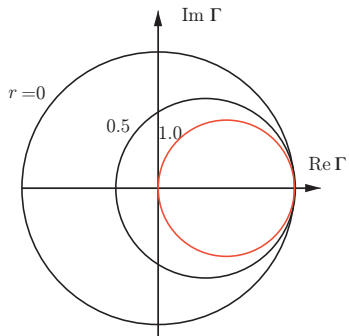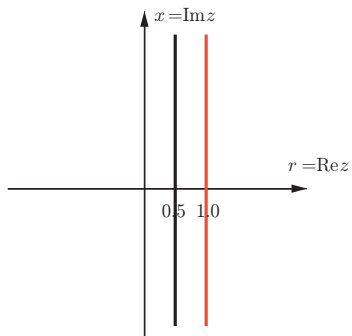



# Smith chart

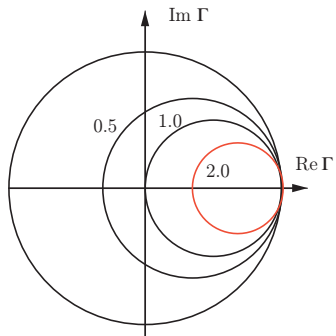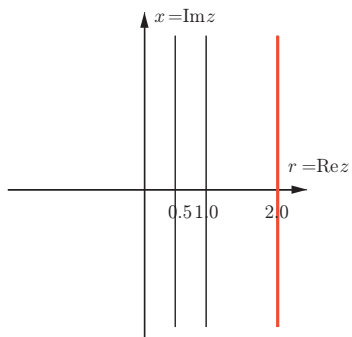

# Smith chart

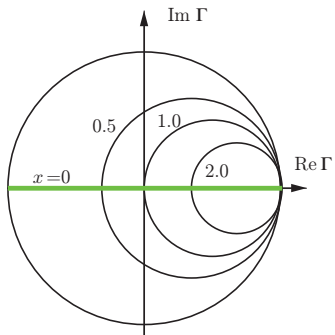
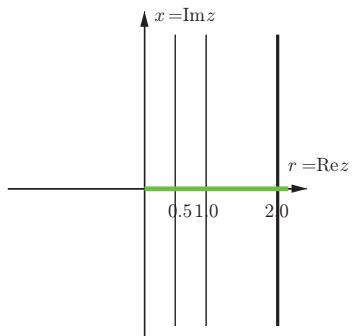


# Smith chart

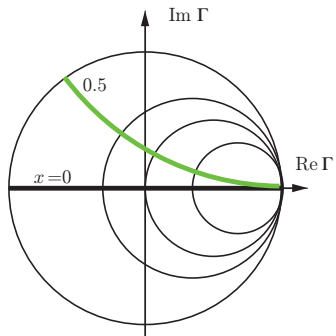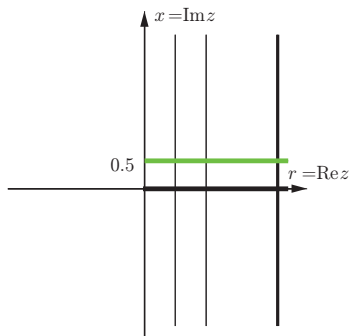




# Smith chart

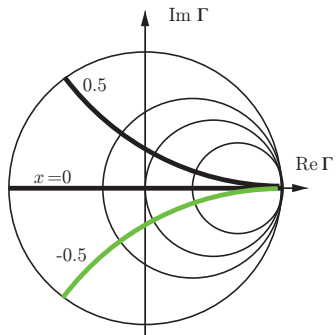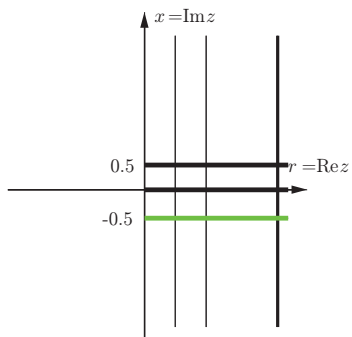


# Smith chart
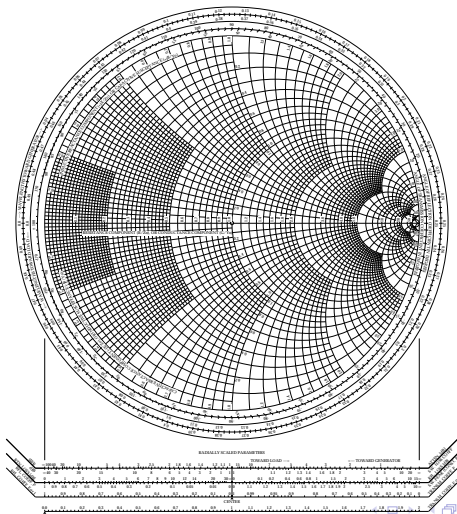
## The Complete Smith Chart Black Magic Design




# Smith chart: example 1

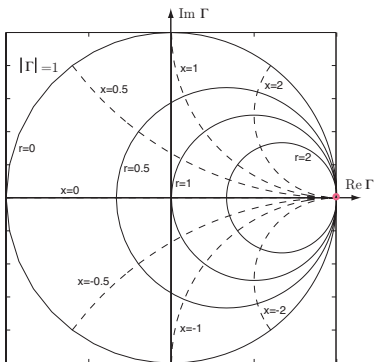


$$\beta d = 0 \Rightarrow \Gamma(0) = \Gamma_d = 1$$

# Smith chart: example 1

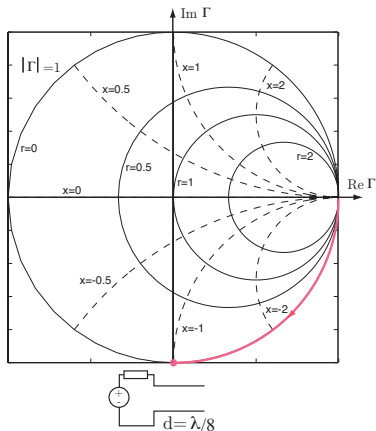


$$\beta d = \pi/4 \Rightarrow \Gamma(0) = -i$$

# Smith chart: example 1

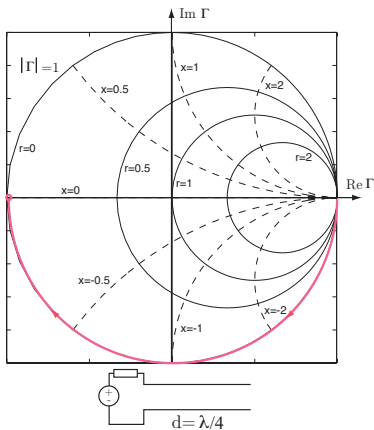


$$\beta d = \pi/2 \Rightarrow \Gamma(0) = -1$$

# Smith chart: example 1

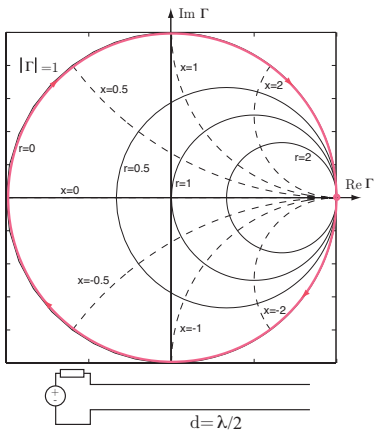


$$\beta d = \pi \Rightarrow \Gamma(0) = \Gamma_d = 1$$

## Smith chart: example 2

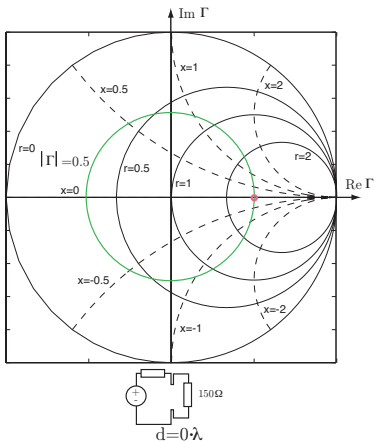

$$\beta d = 0 \Rightarrow \Gamma(0) = \Gamma_d = \frac{150 - 50}{150 + 50} = 0.5$$


## Smith chart: example 2

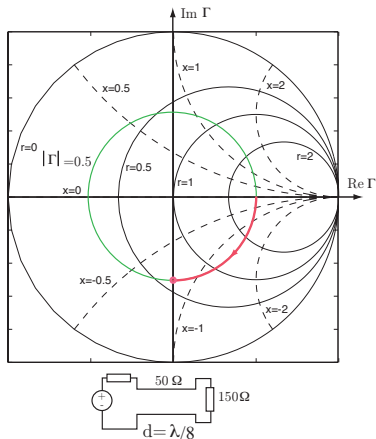

$$\beta d = \pi/4 \Rightarrow \Gamma(0) = -0.5i$$




## Smith chart: example 2

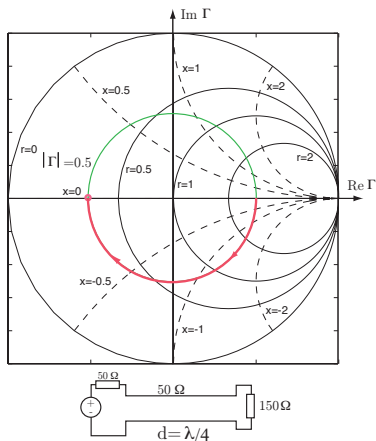

$$\beta d = \pi/2 \Rightarrow \Gamma(0) = -0.5$$

## Smith chart: example 2

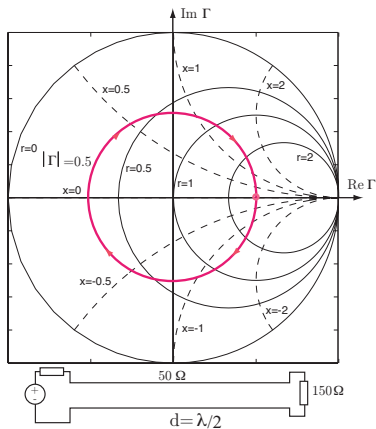

$$\beta d = \pi \Rightarrow \Gamma(0) = \Gamma_d = 0.5$$

# Smith chart

---

The admittance diagram

$$Y = \frac{1}{Z} = G + jB = \text{admittance}$$


$G$  =conductance,  $B$  =susceptance.

$$\Gamma(0) = \frac{z(0) - 1}{z(0) + 1} = \frac{1 - y(0)}{1 + y(0)} = -\frac{y(0) - 1}{y(0) + 1}$$

Go to  $-\Gamma$  in Smith chart and exchange  $g$  for  $r$  and  $b$  for  $x$ .

# Smith chart

---

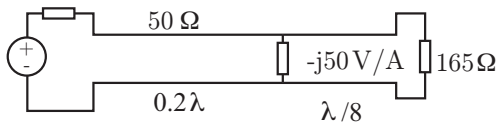


# Smith chart

---

## The Complete Smith Chart

Black Magic Design

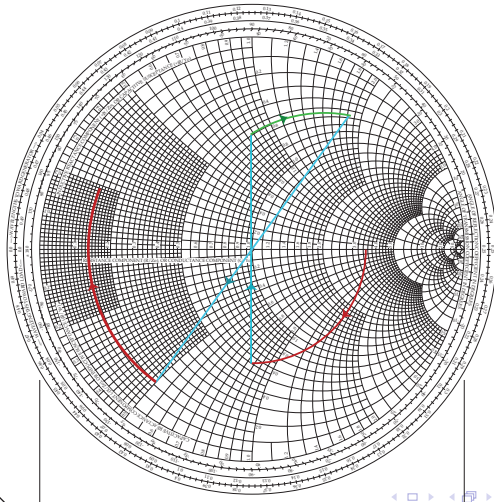

# Impedance match by Smith chart

---


Goal: Try to reach  $z = 1 \Rightarrow \Gamma = 0$ .

Rules:

- ▶ You cannot add resistance, only reactive components.
- ▶ You are allowed to move along the transmission line.
- ▶ You are allowed to go to admittance diagram and add susceptance.
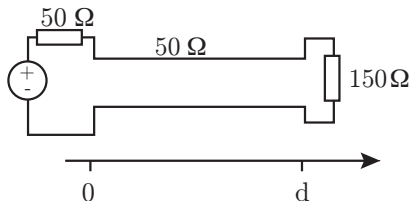
# Impedance match by Smith chart example

Goal: Match with two reactive components at  $z = d$ .




# Impedance match by Smith chart example

---

## The Complete Smith Chart


Black Magic Design

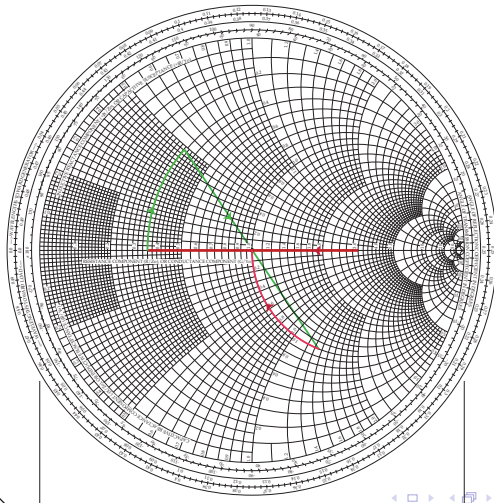



## Impedance match by Smith chart example

---

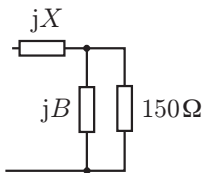

$$B = \frac{0.475}{50} = 9.5 \text{ mA/V and } X = 1.38 \cdot 50 = 69 \text{ V/A.}$$

$$Z = j69 + \frac{1}{\frac{1}{150} + j\frac{0.475}{50}} \approx 49.5 \Omega - j1.5 \text{ V/A}$$