


Clock oscillators

There are, basically, two categories of oscillators that are of interest to the electronics engineers: Harmonic and relaxation. The former produce sinusoidal waveforms and contains at least one active component that supplies power constantly to the passive components, whereas relaxation oscillators produce non-sinusoidal waveform, such as rectangular pulses.

An oscillator is generally an amplifier operating with positive feedback in a manner whereby an output is produced without any input signal. To achieve the desired frequency every oscillator contains a frequency-determining part, which may be an LC circuit, a phase-shifting RC network or a quartz crystal.

Requirements of a clock oscillator


Clock oscillators must be reliable, easily reproducible and simple. An example of such an oscillator is shown in figure 1.

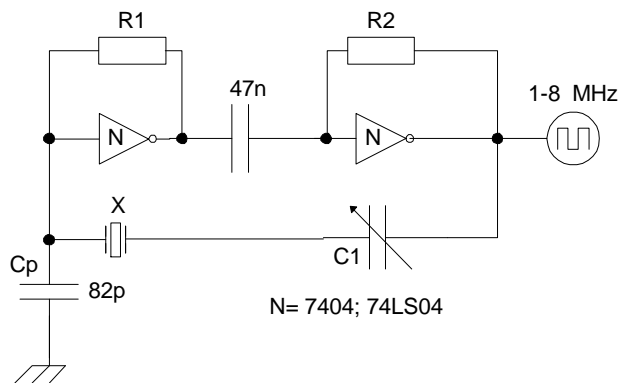

figur1.

This series-mode circuit is suitable for operation between 1 and 8 MHz. Fine adjustment of the frequency is provided by the trimmer C_1 . If the required frequency accuracy is not important the trimmer may be omitted. Capacitor C_p prevents operation on a harmonic frequency. The value of R_1 is 2k Ω for operation below 2 MHz. The value of R_2 is calculated from $R_2 = 3000/f_c$ where f_c is in MHz.

A better oscillator using inverter gates is given in figure 2.

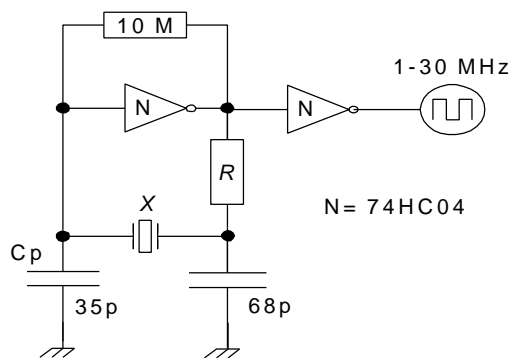

figur 2

It operates in parallel mode. Resistor R serves to limit the current through the crystal. If fine frequency adjustment is not required, C_1 may be omitted and C_p increased to 56pF. This circuit is suitable for use between 1 and 30 MHz. The value of R is calculated from $R = 10^4/f_c - 300$ where f_c is the crystal frequency in MHz.