
 


P1 P2 P3 P4	L1 L2 L3
0 0 0 0	0 0 1
0 0 0 1	0 0 1
0 0 1 0	0 0 1
0 0 1 1	0 1 0
0 1 0 0	0 0 1
0 1 0 1	0 1 0
0 1 1 0	0 1 0
0 1 1 1	1 0 0
1 0 0 0	0 0 1
1 0 0 1	0 1 0
1 0 1 0	0 1 0
1 0 1 1	1 0 0
1 1 0 0	0 1 0
1 1 0 1	1 0 0
1 1 1 0	1 0 0
1 1 1 1	1 0 0

 

$$L1 = P1 \cdot P2 \cdot P3 + P2 \cdot P3 \cdot P4 + P1 \cdot P2 \cdot P4 + P1 \cdot P2 \cdot P3$$



$$P1 \cdot P4 (P2 \oplus P3)$$

$$L2 = \overline{P1} \cdot \overline{P2} \cdot P3 \cdot P4 + \overline{P1} \cdot P2 \cdot P3 \cdot P4 + \overline{P1} \cdot P2 \cdot P3 \cdot \overline{P4} + \overline{P1} \cdot P2 \cdot \overline{P3} \cdot \overline{P4} +$$

$$+ P1 \cdot \overline{P2} \cdot \overline{P3} \cdot P4 + P1 \cdot \overline{P2} \cdot P3 \cdot \overline{P4} \quad (P1 \oplus P2) \cdot (P3 \oplus P4)$$

$$P1 \cdot P2 (P3 \oplus P4)$$

$$L2 = (P1 \oplus P4) \cdot (P2 \oplus P3) + (P1 \oplus P2) \cdot (P3 \oplus P4) + (P1 \oplus P3) \cdot (P2 \oplus P4)$$

Ur tabelle f₀₃ ⇒ L3 = L1 • L2


(9p)

2) Ur schema:

$$f = \overline{a} \cdot \overline{c} \cdot \overline{d} + b \cdot \overline{c} \cdot \overline{d} + a \cdot \overline{c} \cdot \overline{d} + b \cdot c \cdot d + \overline{a} \cdot c \cdot \overline{d} + a \cdot c \cdot \overline{d}$$

f cd

$$f = \overline{d} + b \cdot c$$

 

$$\overline{f} = \overline{c} \cdot d + \overline{b} \cdot d$$

(4p)



$$f = \overline{c} \cdot d + \overline{b} \cdot d$$

$$f = \overline{c} \cdot d + \overline{b} \cdot d$$

$$f = (c + d) \cdot (b + d)$$

vänd!

2 for to

 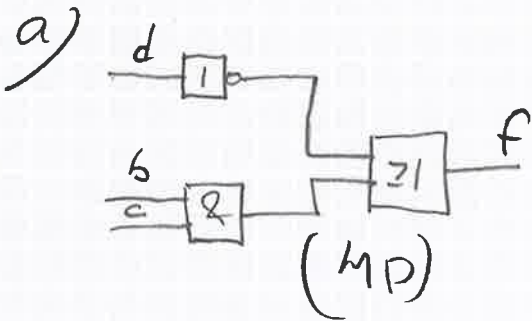

3)

1	0	
2	0	
4	1	92
8	1	88
16	1	80
32	0	64
64	1	64
128	0	

a) $92_{10} = 01 \overset{1}{|} 01 \overset{3}{|} 1100 \overset{4}{|} 0_2$

b) $92 = 5C_{16}$

c) $92 = 134_8$

d) $201011100_2 = 101000 \overset{1}{|} \overset{1}{|} 11$
 $\underline{10100100}$

e) $80 = 64 + 16 = 01010000_2$

$80 - 92 = 01010000 + 10100100$

$$\begin{array}{r} 01010000 \\ + 10100100 \\ \hline 11110100 \end{array} \quad \text{neg!}$$

$211110100 = 0000 \overset{1}{|} \overset{1}{|} 11$
 $\underline{00001100} = 12_{10}$

Svar: -12

f)

$C = 10 - 13 = -3$

0	00000000	0
-1	11111111	255
-2	11111110	254
-3	11111101	253

Svar: 253

8P


4)

$$u_{ta} = \overline{a \cdot b + c \cdot d}$$

$$u_{tb} = a \cdot b \oplus c \cdot d$$


$$u_{tc} = \overline{a \cdot b \cdot c \cdot d} = a \cdot b + c \cdot d$$

a	b	c	d	a·b	c·d	u _{ta}	u _{tb}	u _{tc}
0	0	0	0	0	0	1	0	0
0	0	0	1	0	0	1	0	0
0	0	1	0	0	0	1	0	0
0	0	1	1	0	1	0	1	1
0	1	0	0	0	0	1	0	0
0	1	0	1	0	0	1	0	0
0	1	1	0	0	0	1	0	0
0	1	1	1	0	1	0	1	1
1	0	0	0	0	0	1	0	0
1	0	0	1	0	0	1	0	0
1	0	1	0	0	0	1	0	0
1	0	1	1	0	1	0	1	1
1	1	0	0	1	0	0	1	1
1	1	0	1	1	0	0	1	1
1	1	1	0	1	0	0	1	1
1	1	1	1	1	1	0	0	1

 

(6 p)

5)

 

$q_2 q_1 q_0$	$u_{PP}=0$	$u_{PP}=1$
000	101	001
001	000	010
010	001	011
011	010	100
100	011	101
101	100	000

$q_2^+ q_1^+ q_0^+ u_{PP}$

	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	-	-	-	-
10	0	1	0	1

$q_1^+ q_0^+ u_{PP}$

	00	01	11	10
00	0	0	1	0
01	0	1	0	1
11	-	-	-	-
10	1	0	0	0

$q_0^+ q_0^+ u_{PP}$


	00	01	11	10
00	1	1	0	0
01	1	1	0	0
11	-	-	-	-
10	1	1	0	0

$q_2 q_1$

$$q_0^+ = \overline{q_0}$$

$$q_1^+ = q_1 \cdot \overline{q_0} \cdot u_{PP} + q_1 \cdot \overline{q_0} \cdot \overline{u_{PP}} + \overline{q_0} \cdot \overline{q_1} \cdot q_0 \cdot u_{PP} + q_2 \cdot \overline{q_1} \cdot \overline{q_0} \cdot u_{PP}$$
 
$$q_2^+ = q_2 \cdot \overline{q_0} \cdot u_{PP} + q_2 \cdot \overline{q_0} \cdot \overline{u_{PP}} + q_0 \cdot \overline{q_0} \cdot \overline{u_{PP}} + \overline{q_2} \cdot \overline{q_1} \cdot \overline{q_0} \cdot \overline{u_{PP}}$$




värt 1 och värt 2 är de som har erhållits
 ur Karnaughdiagrammen

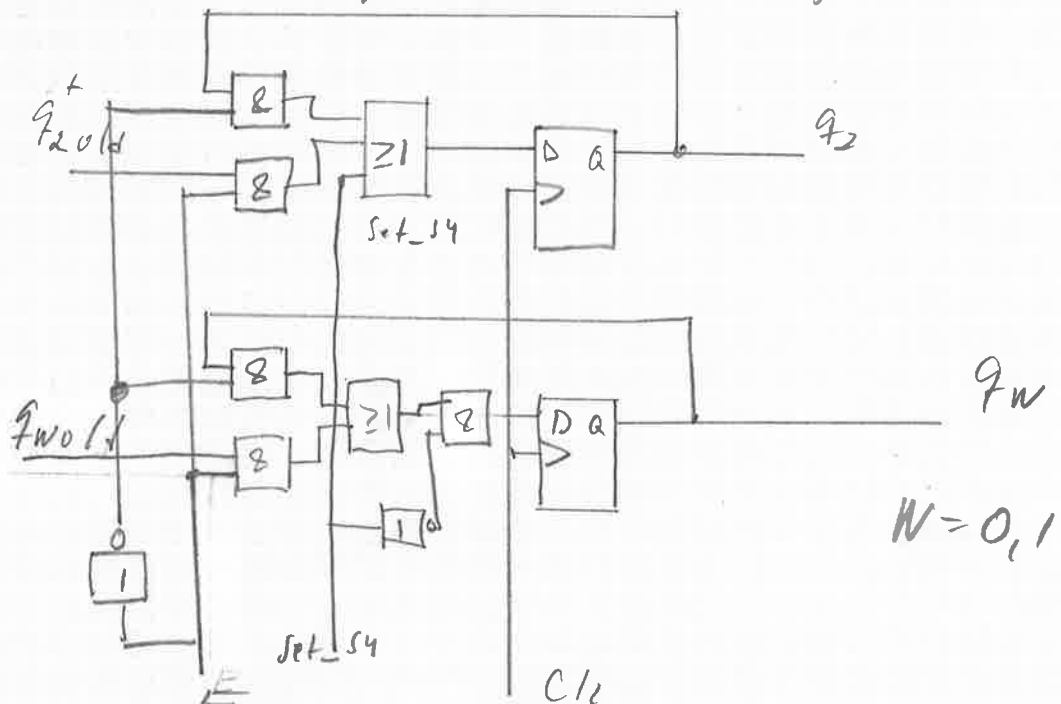6)

$$\text{Vippa 2: } q_2^+ = E \cdot q_{2old} + \overline{E} \cdot q_2 + \text{set}_{S4}$$

$$\text{Vippa 0 och 1: } q_N^+ = (E \cdot q_{Nold} + \overline{E} \cdot q_N) \cdot \overline{\text{set}_{S4}}$$



$N=0,1$

8) Se läroboken

4 pp9. 7.

```
1  -- enkel modula 6 räknare med upp/nedfunktion
2  library IEEE;
3  use IEEE.std_logic_1164.all;
4
5  entity mod6 is
6      port(upp, clock, enable, set_S4:in std_logic;
7           q: out std_logic_vector(2 downto 0));
8  end entity mod6;
9
10 architecture beteende of mod6 is
11     type state_type is (s0,s1,s2,s3 ,s4, s5);
12     signal present_state, next_state:state_type;
13 begin
14     process(present_state, upp)
15     begin
16         case present_state is
17             when s0 => if upp='1' then
18                 next_state<=s1;
19             else
20                 next_state<=s5;
21             end if;
22             when s1 => if upp='1' then
23                 next_state<=s2;
24             else
25                 next_state<=s0;
26             end if;
27             when s2 => if upp='1' then
28                 next_state<=s3;
29             else
30                 next_state<=s1;
31             end if;
32             when s3 => if upp='1' then
33                 next_state<=s4;
34             else
35                 next_state<=s2;
36             end if;
37             when s4 => if upp='1' then
38                 next_state<=s5;
39             else
40                 next_state<=s3;
41             end if;
42             when s5 => if upp='1' then
43                 next_state<=s0;
44             else
45                 next_state<=s4;
46             end if;
47         end case;
48     end process;
49
50     process(present_state)
51     begin
52         case (present_state) is
53             when s0 => q<="000";
54             when s1 => q<="001";
55             when s2 => q<="010";
56             when s3 => q<="011";
```

```
57         when s4 => q<="100";
58         when s5 => q<="101";
59     end case;
60 end process;
61
62 process(clock,enable, set_S4)
63 begin
64     if rising_edge(clock) then
65         if set_S4='1' then
66             present_state<=s4;
67         elsif
68             enable='0' then
69             present_state<=present_state;
70         else
71             present_state<=next_state;
72         end if;
73     end if;
74 end process;
75 end architecture beteende;
76
77
```