
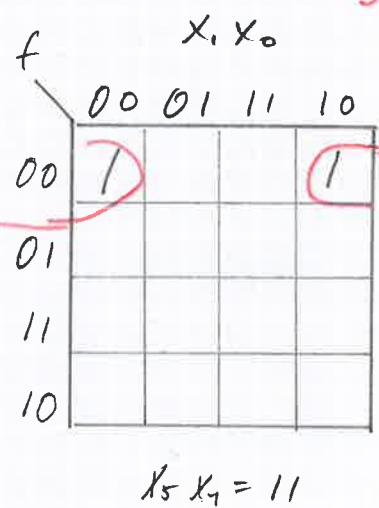
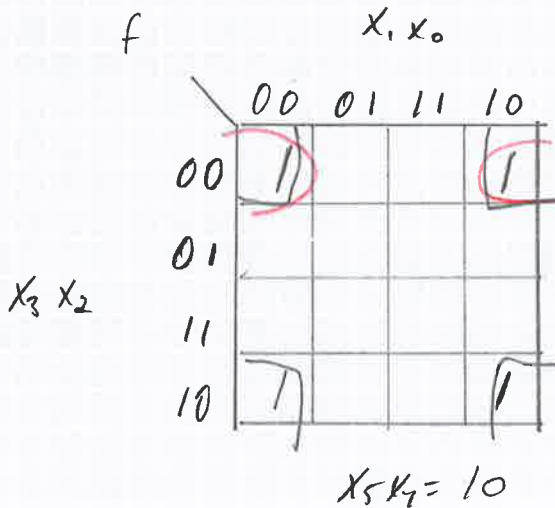
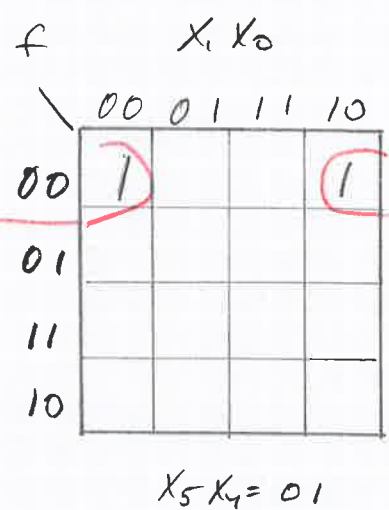


Karnaugh diagram 6-variabler.

Ö. Tag fram ett minimalt SP-nät för

$$f = \sum(0, 1, 2, 3, 16, 18, 32, 34, 40, 42, 48, 50)$$

32	16	8	4	2	1	
x_5	x_4	x_3	x_2	x_1	x_0	f
0	0	0	0	0	0	1
1	0	0	0	0	1	1
2	0	0	0	1	0	1
3	0	0	0	1	1	1
16	0	1	0	0	0	1
18	0	1	0	0	1	1
32	1	0	0	0	0	1
34	1	0	0	1	0	1
40	1	0	1	0	0	1
42	1	0	1	0	1	1
48	1	1	0	0	0	1
50	1	1	0	0	1	1

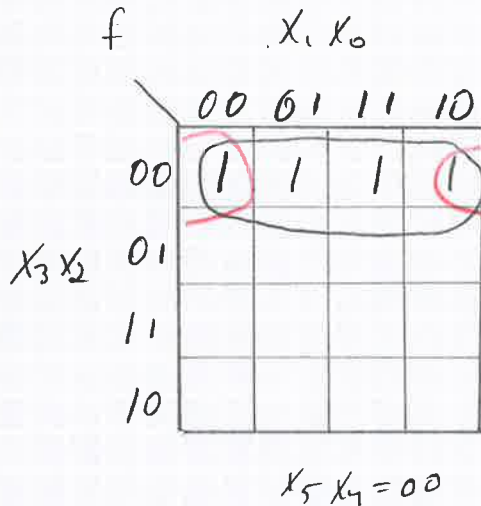


$$f = \overline{x_5} \cdot \overline{x_4} \cdot \overline{x_3} \cdot \overline{x_2} + x_5 \cdot \overline{x_4} \cdot \overline{x_2} \cdot \overline{x_0} + \overline{x_5} \cdot \overline{x_4} \cdot \overline{x_0}$$

NAND-NAND nät sid 139.

Realisera $f = a \cdot b + c \cdot d$ med enbart NAND-skivor.

$$a \cdot b + c \cdot d = (a \cdot b + c \cdot d)'' = ((a \cdot b)' \cdot (c \cdot d)')'$$

de Morgan

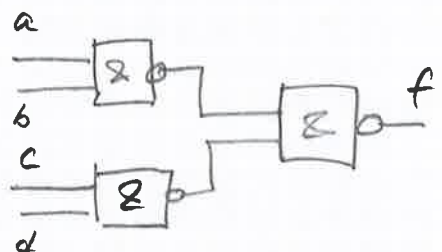

ex. på NAND-net:


Realisera en XOR-grind med enbart 2-ingångars NAND grindar (7400)

XOR-grindens sanningstabell:

a	b	u
0	0	0
0	1	1
1	0	1
1	1	0

d.v.s. $u = \overline{a} \cdot b + a \cdot \overline{b}$
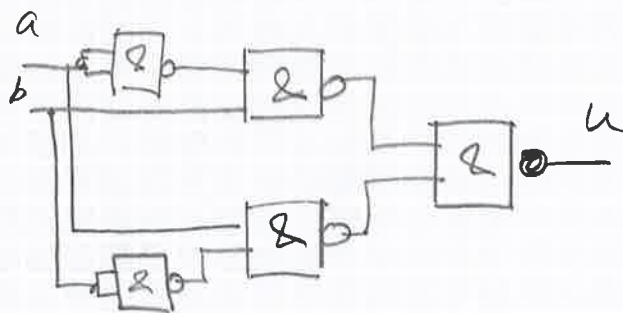
$$u = \overline{\overline{\overline{a} \cdot b} + \overline{a \cdot \overline{b}}} = \overline{\overline{a} \cdot b + a \cdot \overline{b}}$$



anm: inversfunktion realiseras med


ex. på NOR-net

Realisera en XOR-grind med enbart 2-ingångars NOR-grindar (7402)

tas fram villkoren för $u = 0$ (i tabellen ovan)

$$\overline{u} = \overline{a} \cdot b + a \cdot \overline{b} \Rightarrow u = \overline{\overline{\overline{a} \cdot b} + \overline{a \cdot \overline{b}}} = \overline{a + b + \overline{a} + \overline{b}}$$
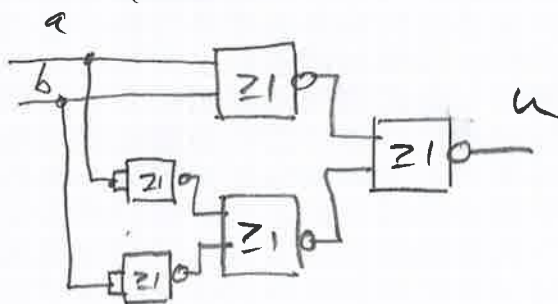
$$\overline{\overline{a} \cdot b} = \overline{a} + b$$



anm: inversfunktion realiseras med