



LUND  
UNIVERSITY


# Information Transmission

## Appendix B, Circuit theory

---

OVE EDFORS

ELECTRICAL AND INFORMATION TECHNOLOGY

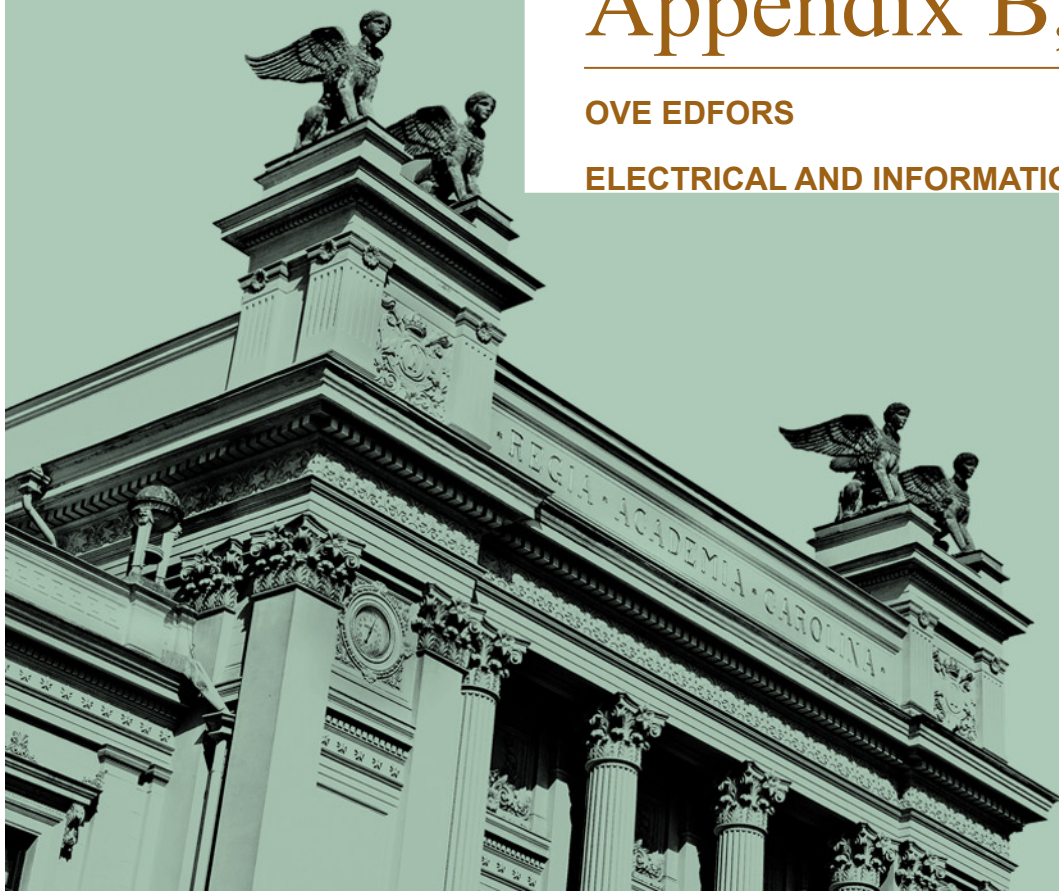

# Learning outcomes

---




After this lecture the student should

- Know the properties of, and be able to perform basic calculations with, resistors, inductors and capacitors
- Know how resistors, inductors, and capacitors, behave when sinusoidal signals are applied.
- Know Kirchhoff's voltage and current laws and understand how they are applied to perform basic calculations on electronic circuits.
- Understand the impedance concept and how to calculate the total impedance of impedances connected in serial or parallel



# Resistors, Inductors, Capacitors

---

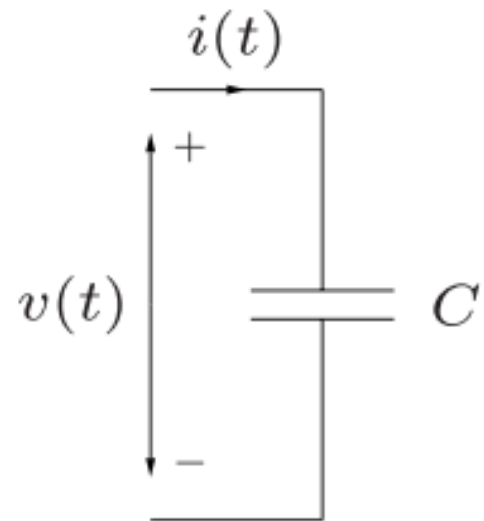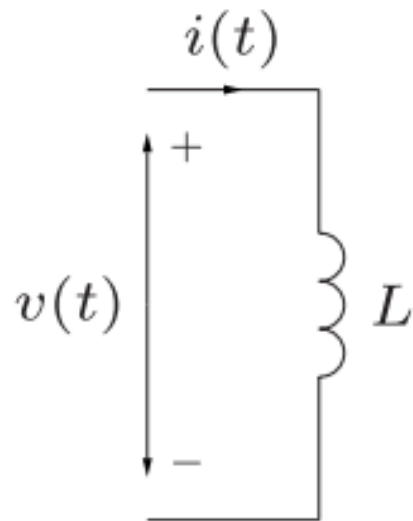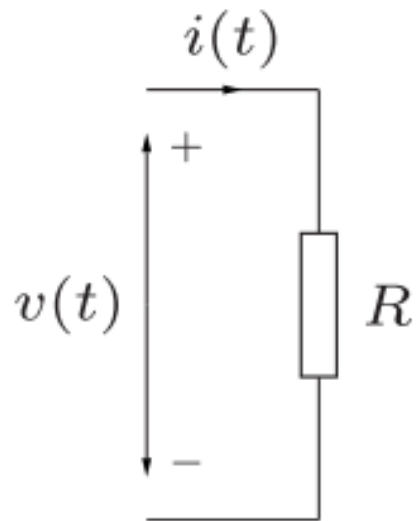



# Resistors

---


Ohm's law: the voltage  $v(t)$  volt [V] across a resistor with resistance  $R$  ohm [ $\Omega$ ] is proportional to the current  $i(t)$  ampère [A] through the resistance.

$$v(t) = Ri(t) \quad (\text{B.1})$$

For  $i(t) = e^{j\omega_0 t}$  we have
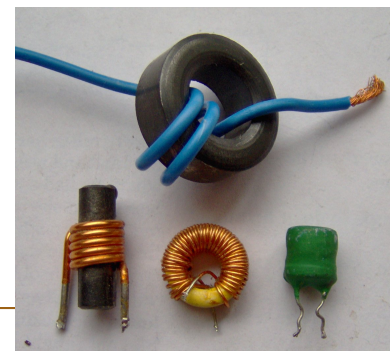
$$v(t) = \underbrace{R}_{\text{Does not depend on frequency.}} e^{j\omega_0 t} \quad (\text{B.2})$$





# Inductors

The voltage across an inductor with inductance  $L$  henry [H] is proportional to the derivative of the current  $i(t)$  through the inductor.


$$v(t) = L \frac{di(t)}{dt} \quad (\text{B.3})$$

For  $i(t) = e^{j\omega_0 t}$  we have

$$v(t) = j\omega_0 L e^{j\omega_0 t} \quad (\text{B.4})$$

Depends (increases)  
with frequency.



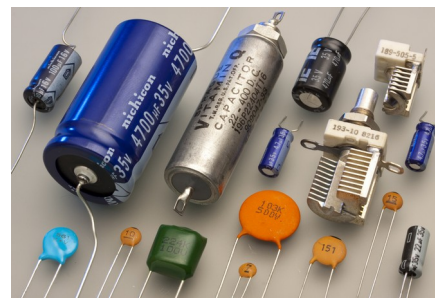

# Capacitors

The charge  $q(t)$  coulombs [C] of a capacitor with capacitance  $C$  farad [F] is proportional to the voltage across the capacitor:

$$q(t) = Cv(t)$$

Since  $q(t) = \int_{-\infty}^t i(\tau) d\tau$ , we have

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

For  $i(t) = e^{j\omega_0 t}$  we have

$$v(t) = \frac{1}{C} \int_{-\infty}^t e^{j\omega_0 \tau} d\tau = \frac{1}{j\omega_0 C} e^{j\omega_0 t}$$

Depends on  
(decreases with)  
frequency.




# Impedance

---

The one-port shown in Fig. B.2 is a network consisting of resistors, inductors, and capacitors. The voltage across the one-port is  $v(t) = e^{j\omega_0 t}$ .

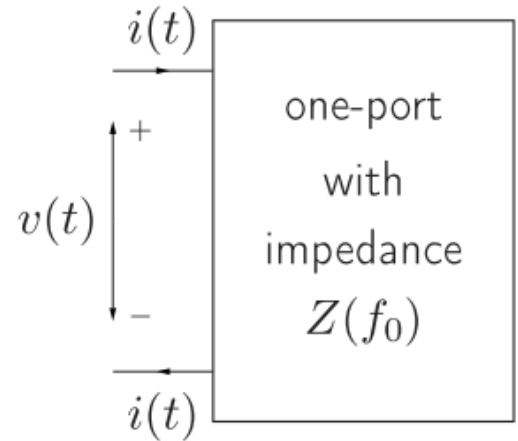The current  $i(t)$  will also be a complex exponential signal; but, in general, with different amplitude and phase.



We have

$$v(t) = Z(f_0)i(t)$$

where  $Z(f_0)$  is called the impedance.



# Impedance

---

*The impedance is in general complex and dependent on the frequency  $f_0$ , but if the one-port consists only of resistors, then its impedance will always be real and independent of the frequency  $f_0$ ; that is, it is a resistance.*

*Ohm's law for alternating current holds only for stationary sinusoidal voltages and currents (including the special case when  $f_0 = 0$ ).*





# Kirchhoff's current law

---

Kirchhoff's current law (KCL): *The algebraic sum of the currents entering any node is identically zero for all instants of time.*

*KCL: Sum of currents flowing into a node  
= sum of currents leaving the node*



# Kirchhoff's voltage law


---

*Kirchhoff's voltage law (KVL): The algebraic sum of the voltages around any closed path, or loop, in a circuit is identically zero for all instants of time.*



# Example 1

---

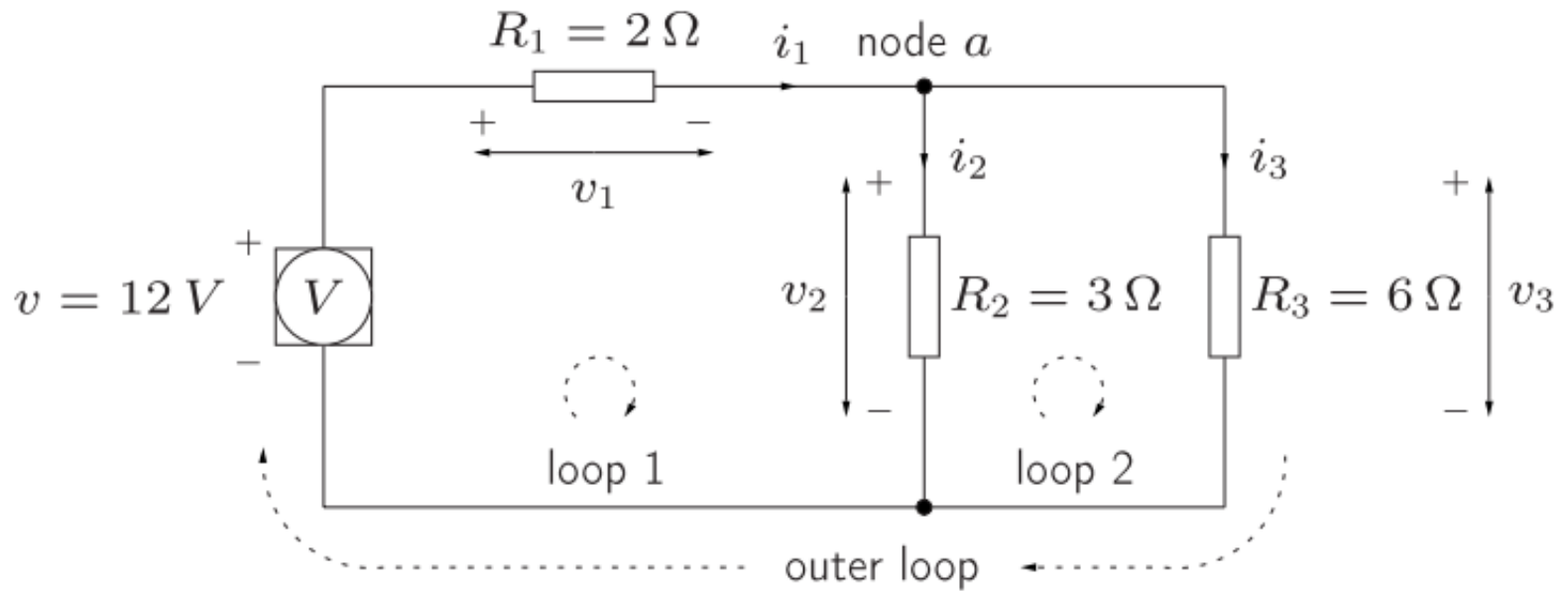

What is  $i_1$ ,  $i_2$ ,  $i_3$ ,  $v_1$ ,  $v_2$ ,  $v_3$ ?




# Serial impedance

Consider three impedances connected in a serial manner.

Assuming that the current  $i(t)$  is sinusoidal with frequency  $f_0$ , let  $Z_s(f_0)$  denote the impedance of this serial circuit.

$$v(t) = Z_s(f_0)i(t)$$

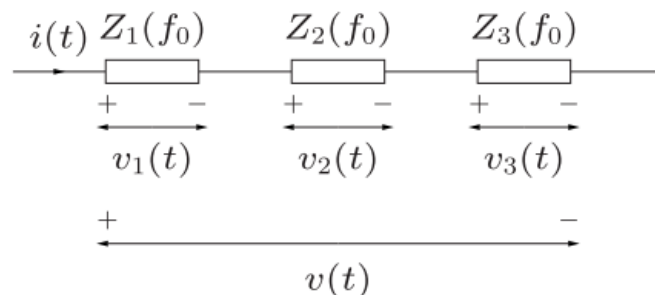

The impedance for the serial circuit is


$$Z(f_0) = Z_1(f_0) + Z_2(f_0) + Z_3(f_0)$$



## Example 2

---

Consider the circuit

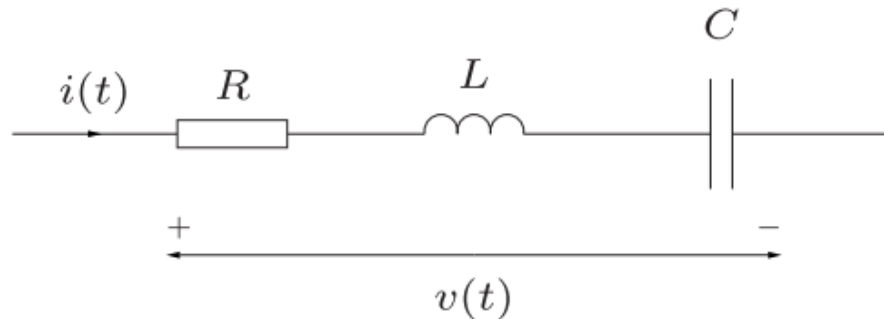

The current  $i(t)$  is a sinusoid of frequency  $f_0$  Hz.


What is  $v(t)$ ?


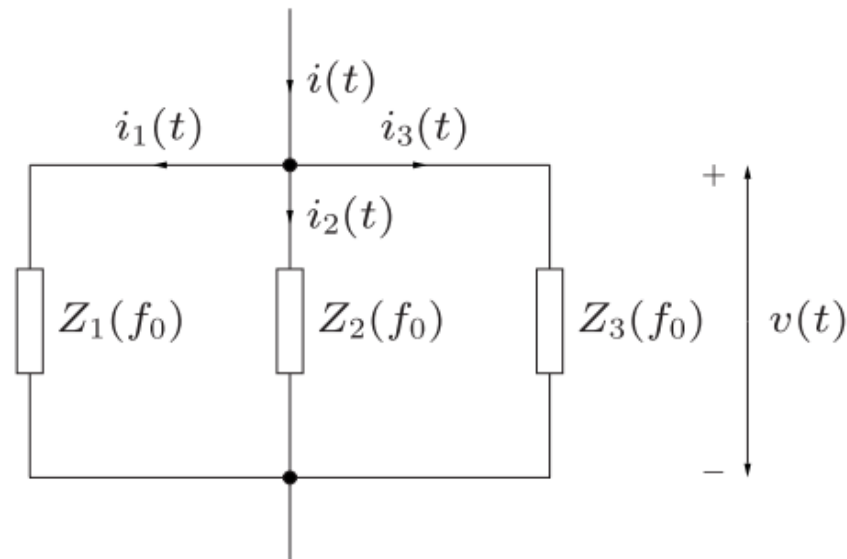
# Parallel impedances

---

*Consider three impedances connected in parallel:*



What is the equivalent parallel impedance?



# Parallel impedances

---

*The impedance for the parallel circuit is written*


$$\frac{1}{Z_p(f_0)} = \frac{1}{Z_1(f_0)} + \frac{1}{Z_2(f_0)} + \frac{1}{Z_3(f_0)}$$

Often we have only two impedances in parallel


$$Z_p(f_0) = \frac{Z_1(f_0)Z_2(f_0)}{Z_1(f_0) + Z_2(f_0)}$$



# Split of voltage and current

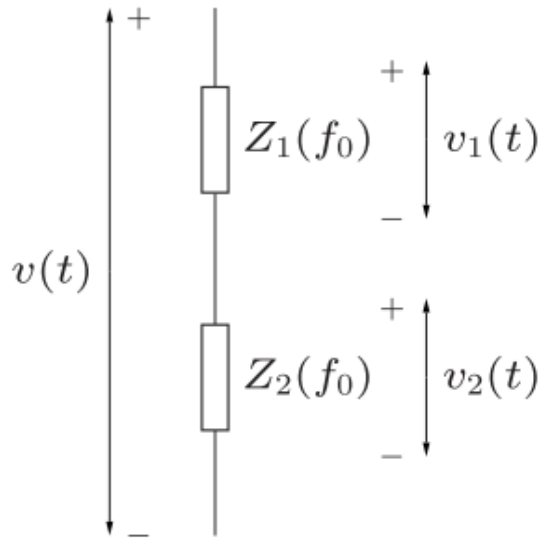
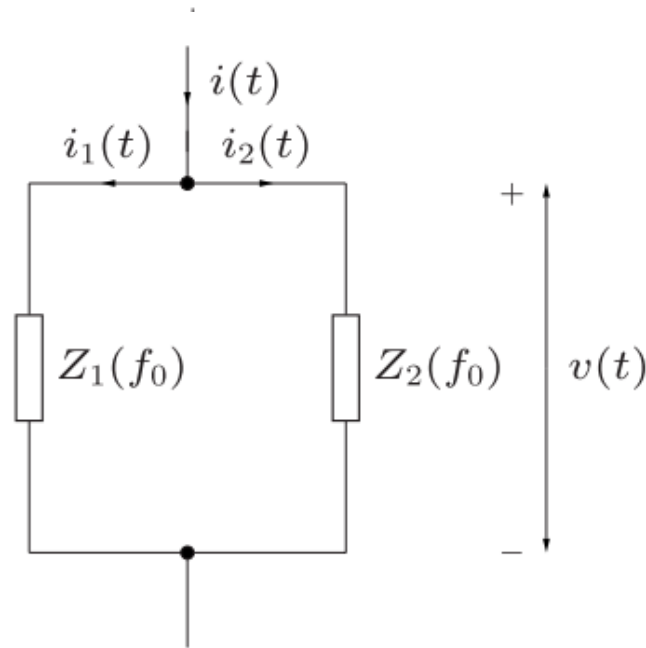
$$v_1(t) = \frac{Z_1(f_0)}{Z_1(f_0) + Z_2(f_0)} v(t)$$



$$i_1(t) = \frac{Z_2(f_0)}{Z_1(f_0) + Z_2(f_0)} i(t)$$





# Summary

---

- Resistors, inductors & capacitors
  - We can apply Ohm's law, also for inductors and capacitors, by using  $j\omega_0 L$  and  $1/j\omega_0 C$  in place of "resistance".
  - Impedance is the relation between voltage and current (often from a combination of resistors, inductors and capacitors).
- Kirchoff's laws (general)
  - **Current law:** At all times, the sum of all currents into a node must equal the sum of currents leaving the node. (Charge can't accumulate in a node.)
  - **Voltage law:** At all times, the sum of voltages around any closed loop in a circuit must be zero.
- Typical circuits (special cases)
  - Serial and parallel impedance
  - Split of voltage and current



**LUND**  
**UNIVERSITY**