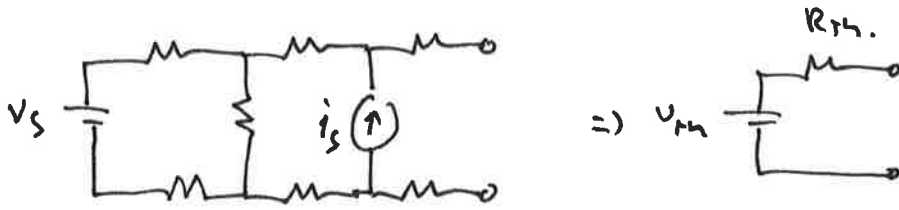

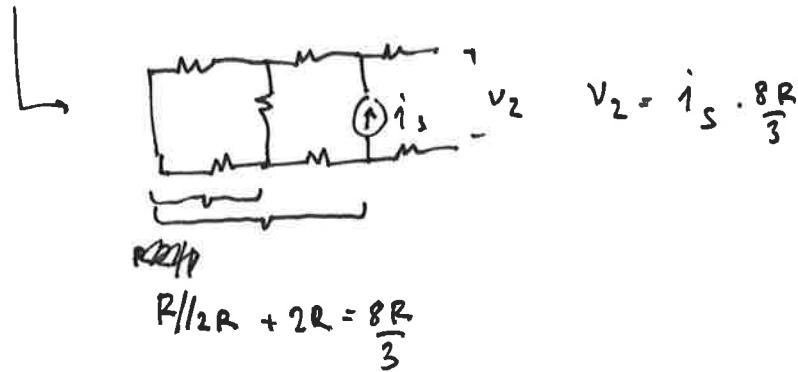


1)




V_{th} : Superposition: $\rightarrow V_s$  Sp. delung: $V_1 = \frac{R}{R+2R} \cdot V_s = \frac{V_s}{3}$



$$V_{th} = \frac{V_s}{3} + \frac{8R}{3} \cdot i_s$$


$8R/3$

R_{th} : Nullstell Keller:

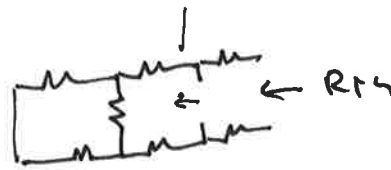

$$R_{th} = \frac{8R}{3} \cdot 2R = \frac{14R}{3}$$

2)

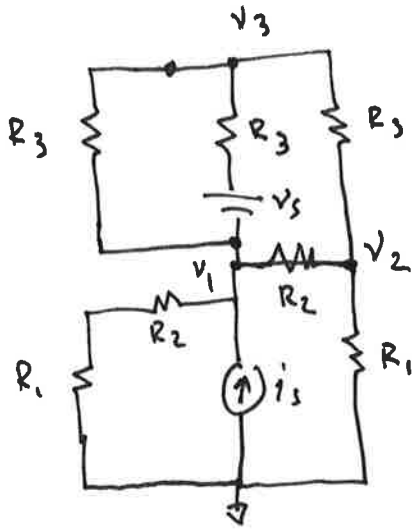

$$1) \frac{V_1}{R_1+R_2} + \frac{V_1-V_2}{R_2} + \frac{V_1-V_3}{R_3} + \frac{V_1+V_s-V_3}{R_3} - i_s = 0$$

$$2) \frac{V_2-V_1}{R_2} + \frac{V_2}{R_1} + \frac{V_2-V_3}{R_3} = 0$$

$$3) \frac{V_3-V_1}{R_3} + \frac{V_3-V_s-V_2}{R_3} + \frac{V_3-V_2}{R_3} = 0$$



$$1) V_1 \left(\frac{1}{R_1+R_2} + \frac{1}{R_2} + \frac{2}{R_3} \right) + V_2 \left(-\frac{1}{R_2} \right) + V_3 \left(-\frac{2}{R_3} \right) = i_s - \frac{V_s}{R_3}$$

$$2) V_1 \left(-\frac{1}{R_2} \right) + V_2 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) + V_3 \left(-\frac{1}{R_3} \right) = 0$$


$$3) V_1 \left(-\frac{2}{R_3} \right) + V_2 \left(-\frac{1}{R_3} \right) + V_3 \left(\frac{3}{R_3} \right) = \frac{V_s}{R_3}$$

3) a) $|H(\omega)|_{dB} = -40dB \Rightarrow \omega_c = 100 \cdot \omega_b \Rightarrow \omega_b = 10^3 \text{ rad/s}$

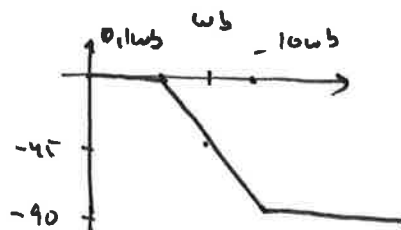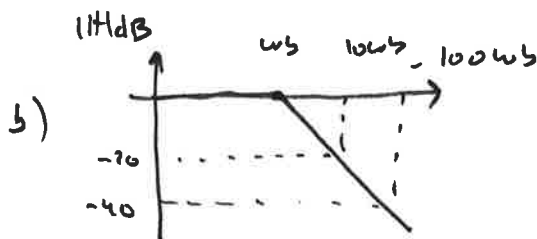
$$\omega_b = \frac{1}{RC} \Rightarrow C = \frac{1}{\omega_b \cdot R} = \frac{1}{10^3 \cdot 10^3} = 10^{-6} = \underline{\underline{1 \mu F}}$$



c)

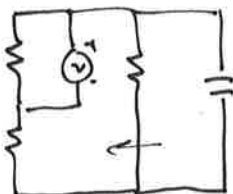
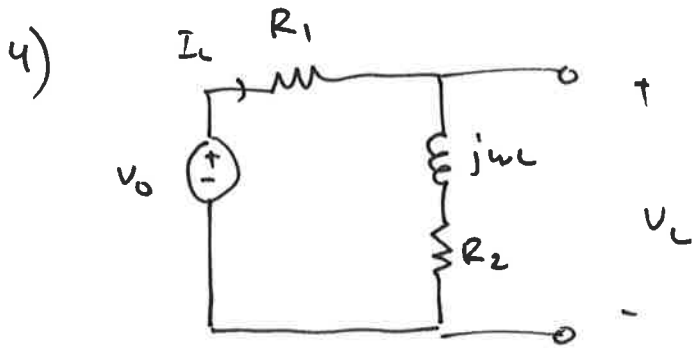
$$R_{Th} = R // R = \frac{R}{2} \Rightarrow \omega_b = \underline{\underline{\frac{2}{RC}}}$$




$$a) \quad I_L = \frac{V_0}{Z_L + R_1} = \frac{V_0}{R_1 + R_2 + j\omega L} = \frac{V_0 (R_1 + R_2 - j\omega L)}{\cancel{(R_1 + R_2)^2 + (\omega L)^2} \sqrt{(R_1 + R_2)^2 + (\omega L)^2}}$$

$$b) \quad V_L = I_2 \cdot Z_L = V_0 \cdot \frac{R_2 + j\omega L}{R_1 + R_2 + j\omega L} = \frac{\sqrt{R_2^2 + (\omega L)^2}}{\sqrt{(R_1 + R_2)^2 + (\omega L)^2}} \cdot e^{j\left(\frac{\omega L}{R_2} - \frac{\omega L}{R_1 + R_2}\right)} \cdot V_0$$


$$c) \quad v(t) = V_0 \cdot \frac{\sqrt{R_2^2 + (\omega L)^2}}{\sqrt{(R_1 + R_2)^2 + (\omega L)^2}} \cdot \cos\left(\omega t + \frac{\omega L R_1}{R_2 (R_1 + R_2)}\right)$$

$$d) \quad S = \frac{1}{2} V I^* = \frac{1}{2} V_0^2 \cdot \frac{R_2 + j\omega L}{(R_1 + R_2)^2 + (\omega L)^2} \quad ; \quad P = \operatorname{Re}(S) = \frac{V_0^2}{2} \cdot \frac{R_2}{(R_1 + R_2)^2 + (\omega L)^2}$$

5)

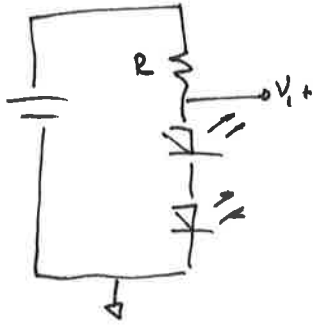

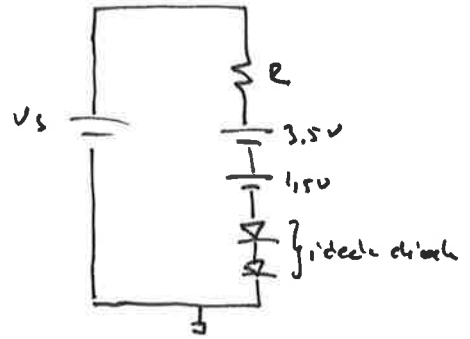
\Rightarrow ideale dioder med knipspänning.



a) Backspända till $V_s \geq 3.5 + 1.5 = 5.0V$




$i = 0$ (KCL!)

$V_1 = V_s$

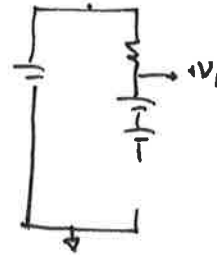


Franspända då $V_s > 5$
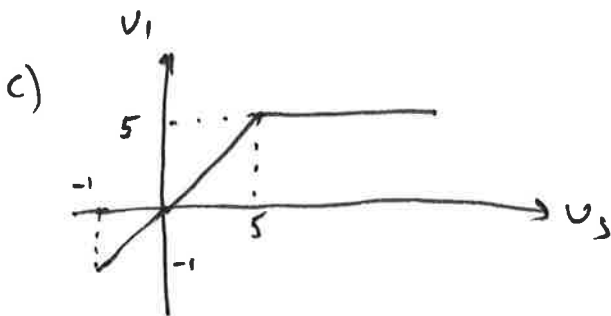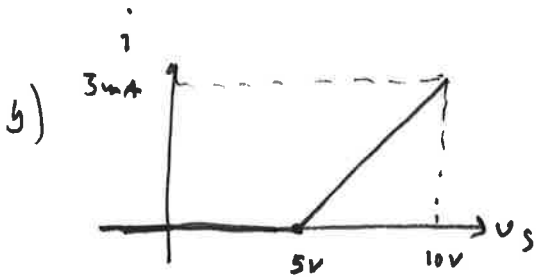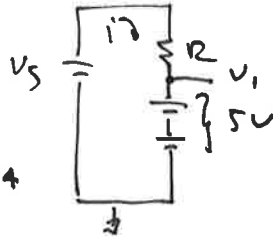
$$i = \frac{V_s - 5}{R} = \frac{V_s - 5}{10^3} \text{ A} = (V_s - 5) \text{ mA}$$



b) a)

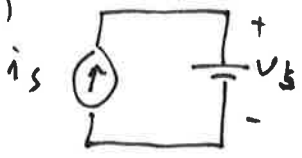


Ja, går att realisera!

Strömkälla: ger strömmen i_s oavsett spänning

Spänningskälla: ger spänningen U_b -||- ström!

b)

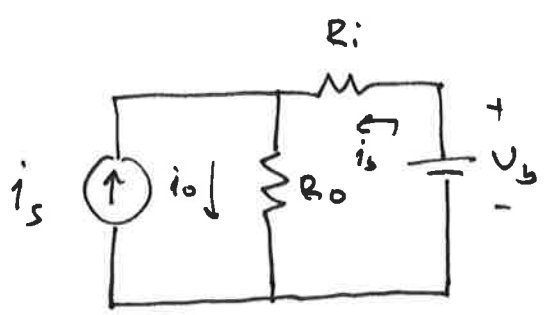

Superposition:

$$i_b = -\frac{R_o}{R_i + R_o} \cdot i_s + \frac{U_b}{R_i + R_o}$$

$$i_o = \frac{R_i}{R_i + R_o} \cdot i_s + \frac{U_b}{R_i + R_o}$$

b) effekt i batteriet: $P_b = -i_b \cdot U_b = \frac{+R_o \cdot i_s \cdot U_b}{R_i + R_o} + \frac{-U_b^2}{R_i + R_o}$

Om $P_b > 0$: batteriet laddas upp!

c) Förluster: effekt förbrukning i resistanserna.

$$P_F = i_o^2 \cdot R_o + i_b^2 \cdot R_i = \frac{1}{(R_i + R_o)^2} \left(R_o \left((R_i \cdot i_s) + U_b \right)^2 + R_i \left(-R_o \cdot i_s + U_b \right)^2 \right)$$

$P_F \geq 0$