


1a)



$$R_{th} = 2R // R + R = \frac{5R}{3}$$

$$v_{Lth} = v_s \cdot \frac{R}{3R} = \underline{\underline{\frac{v_s}{3}}}$$

b)

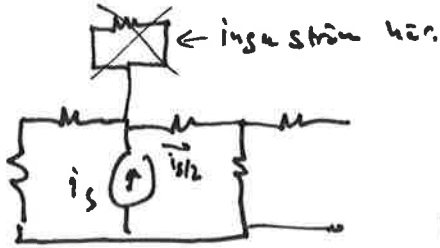

$$R_{th} = 3R // R + R = \frac{7R}{4}$$



$$v_{Lth} = \frac{i_s \cdot R}{2} = \underline{\underline{i_s \cdot R/2}}$$

$$2. \quad \frac{v_1}{2R_1} + \frac{v_1 - v_2}{R_2} + \frac{v_1 + v_3 - v_3}{R_2 + R_3} = 0 \Rightarrow v_1 \left(\frac{1}{2R_1} + \frac{1}{R_2} + \frac{1}{R_2 + R_3} \right) + v_2 \left(-\frac{1}{R_2} \right) + v_3 \left(\frac{-1}{R_2 + R_3} \right) = -\frac{v_s}{R_2 + R_3}$$

$$\frac{v_2}{R_1} + \frac{v_2 - v_1}{R_2} + i_s = 0 \Rightarrow v_1 \left(-\frac{1}{R_2} \right) + v_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = -i_s$$

$$\frac{v_3}{R_2} - i_s + \frac{v_3 - (v_1 + v_3)}{R_2 + R_3} = 0 \Rightarrow v_1 \left(-\frac{1}{R_2 + R_3} \right) + v_3 \left(\frac{1}{R_2} + \frac{1}{R_2 + R_3} \right) = i_s + \frac{v_s}{R_2 + R_3}$$
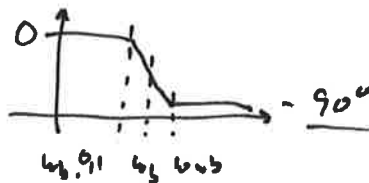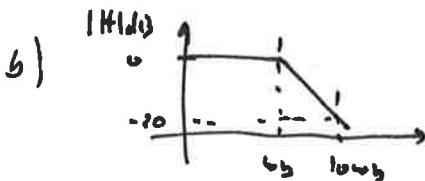
$$3. \quad a) \quad \omega_b = \frac{1}{RC} = 10^3 \text{ rad/s} \Rightarrow R = \frac{1}{10^3 \cdot 10^{-6}} = \underline{\underline{1k\Omega}}$$



$$c) \quad R_{th} = 2R // R = \frac{2R}{3} \Rightarrow \omega_b = \underline{\underline{\frac{3}{2RC}}}$$

$$4a) \quad V_L = V_S \cdot \frac{R + \frac{1}{j\omega C}}{2R + \frac{1}{j\omega C}} = \frac{1 + j\omega RC}{1 + 2j\omega RC} \cdot V_S$$

$$b) \quad V_L = \frac{\sqrt{1 + (\omega RC)^2}}{\sqrt{1 + (2\omega RC)^2}} \cdot e^{j(\arctan(\omega RC) - \arctan(2\omega RC))}$$


$$\Rightarrow V_L(t) = \frac{\sqrt{1 + (\omega RC)^2}}{\sqrt{1 + (2\omega RC)^2}} \cdot \cos(\omega t + \arctan(\omega RC) - \arctan(2\omega RC))$$

$$c) \quad I_L = \frac{V_S}{2R + \frac{1}{j\omega C}} = \frac{j\omega C}{1 + 2j\omega RC} \cdot V_S$$

$$d) \quad S = \frac{V \cdot I^*}{2} = \frac{|V_S|^2}{2} \cdot \frac{-j\omega C \cdot (1 + j\omega RC)}{1 + (2\omega RC)^2} = \frac{|V_S|^2}{2} \cdot \frac{\omega^2 RC^2 - j\omega C}{1 + (2\omega RC)^2}$$

$$P = \operatorname{Re}(S) = \frac{V_S^2}{2} \cdot \frac{\omega^2 RC^2}{1 + (2\omega RC)^2}$$

5. Gissa backspänd.

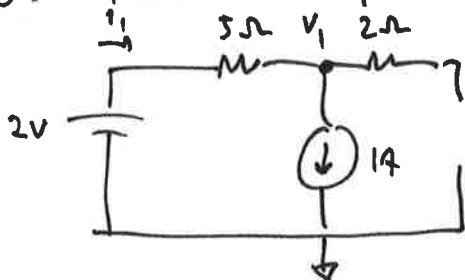


$$V_1 = \frac{V_1 - 2}{5} = -1 \Rightarrow \underline{V_1 = -3V}$$

D Oh! → D, backspänd.

$$\Rightarrow \underline{I_1 = 1A}$$


6)

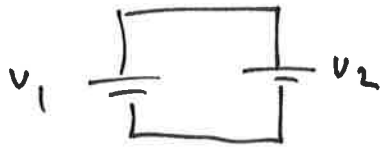

a) Nej! Bryter mot KVL då:

KVL: $V_1 - V_2 = 0 \Rightarrow V_1 = V_2$. Men enligt uppgift: $V_1 > V_2$ Kan alltså ej realiseras med ideala komponenter!

b)

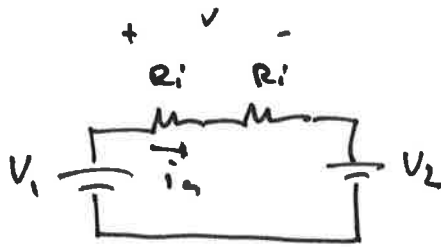

$$i_a = \frac{V_1 - V_2}{2R_i}$$

$$c) P_{R_i} = i_a \cdot V = \frac{V_1 - V_2}{2R_i} \cdot (V_1 - V_2) = \frac{(V_1 - V_2)^2}{2 \cdot R_i}$$

$$d) P_{V_2} = -i_a \cdot V_2 = -\frac{(V_1 - V_2)^2}{2 \cdot R_i} \cdot V_2$$

El-energi \rightarrow Kemisk energi!

$$E = P_{V_2} \cdot t_0 = \frac{(V_1 - V_2)^2 \cdot V_2}{2 \cdot R_i} \cdot t_0 \quad (\text{energi effektivitet!})$$