

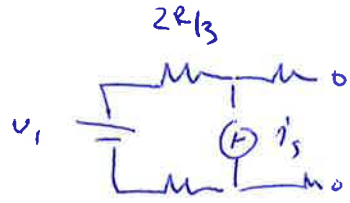
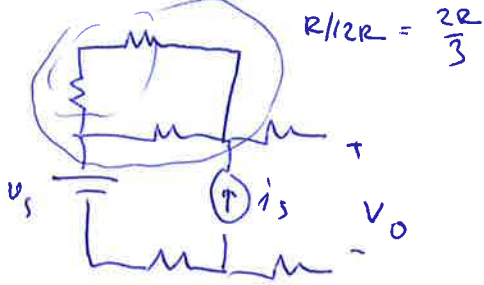


28/10-2019


1).

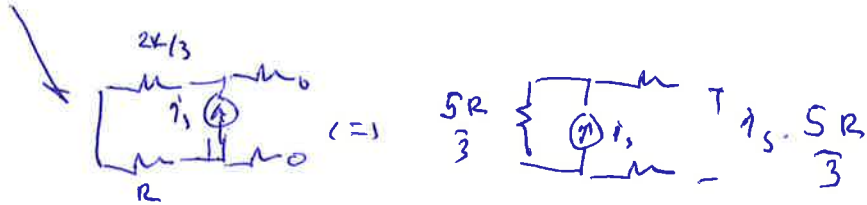

$V_{TK}$ : Superposition:

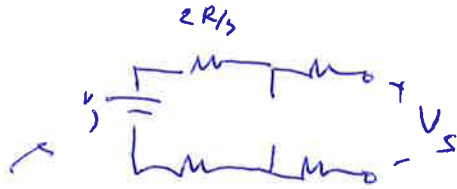
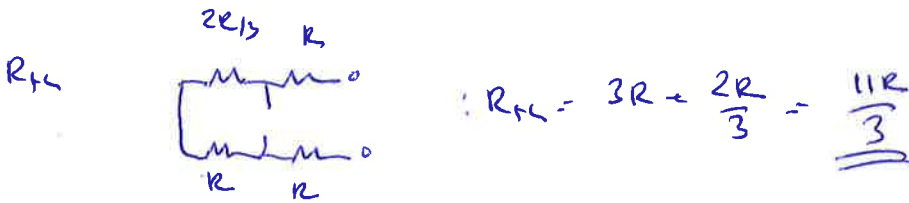
$$\Rightarrow \underline{V_{TK}} = v_s + i_s \cdot \frac{5R}{3}$$



2) (v1)  $V_1 = v_a$





(v2)  $\frac{V_2 - V_1}{2R} + \frac{V_2 - V_3}{R} + \frac{V_2 - V_4 - v_c}{2R} = 0 \Rightarrow V_1 \left( -\frac{1}{2R} \right) + V_2 \left( \frac{3}{R} \right) + V_3 \left( -\frac{1}{R} \right) + V_4 \left( -\frac{1}{2R} \right) + \frac{v_c}{2R}$

(v3)  $\frac{V_3 - V_1}{R} + \frac{V_3 - V_2}{R} - i_s + \frac{V_3 - V_4}{R} = 0 \Rightarrow V_1 \left( -\frac{1}{R} \right) + V_2 \left( -\frac{1}{R} \right) + V_3 \left( \frac{3}{R} \right) + V_4 \left( -\frac{1}{R} \right) = i_s$


(v4)  $\frac{V_4 - v_b}{2R} + \frac{V_4 - V_3}{R} + \frac{V_4 + v_c - v_d}{2R} = 0 \Rightarrow V_2 \left( -\frac{1}{2R} \right) + V_3 \left( -\frac{1}{R} \right) + V_4 \left( \frac{2}{R} \right) = \frac{v_b}{2R} - \frac{v_c}{2R}$

3) a)  $\omega_b = -20\text{dB}$  ( $|H(\omega)| = -40\text{dB} @ 10^5 \text{ rad/s.}$ )
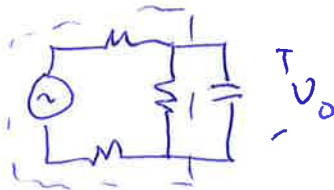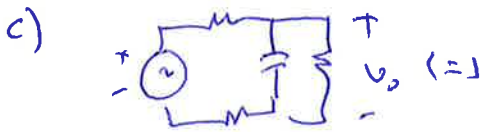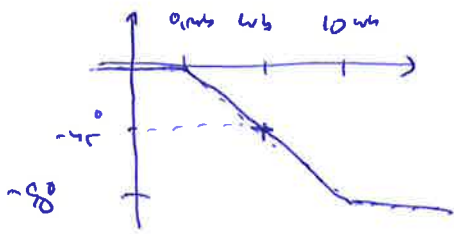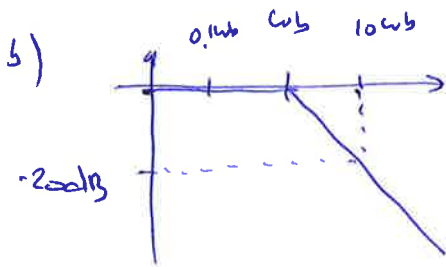
$$\omega_b = \frac{1}{RC} \Rightarrow R = \frac{1}{C} \cdot \frac{1}{\omega_b} = 10^3 \Omega = \underline{\underline{1\text{k}\Omega}}$$


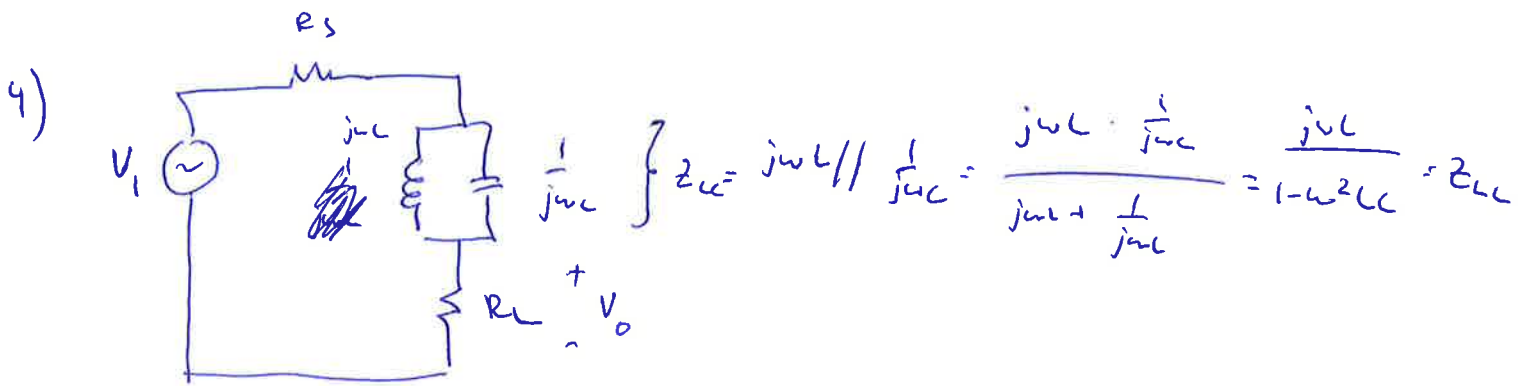
$$R_{th} = R // R = \frac{2R}{3} \Rightarrow \omega_b = \underline{\underline{\frac{3}{2RC}}}$$




a) Sp. delning:  $V_o = \frac{R_L}{R_s + R_L + Z_{LL}} \cdot V_1 = \frac{R_L}{R_s + R_L + \frac{j\omega L}{1 - \omega^2 LC}} \cdot V_1$

b)  $V_o(t) = \frac{R_L}{\sqrt{(R_s + R_L)^2 + \left(\frac{\omega L}{1 - \omega^2 LC}\right)^2}} \cdot \cos(\omega t - \arctan \frac{\omega L}{(1 - \omega^2 LC)(R_s + R_L)})$

c)  $Z_{LL} \rightarrow \infty$  då  $\omega^2 = \frac{1}{LC} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$

↳ ger att  $V_o \rightarrow 0!$

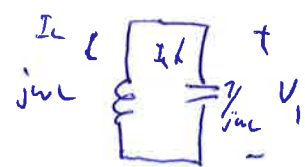d) Då  $Z_{LL} \rightarrow \infty \Rightarrow$  all spänning  $V_1$  faller över  $Z_{LL}$ .




$$I_C = \frac{V_1}{j\omega C} = V_1 \cdot j\omega C \quad I_C^* = -V_1^* \cdot j\omega C$$

$$I_C = \frac{V_1}{j\omega L} \quad I_C^* = \frac{V_1^*}{\omega L}$$


$$S_C = \frac{V_1 \cdot I_C^*}{2} = -\frac{|V_1|^2}{2} \cdot \omega C \cdot j \Rightarrow Q_C = \text{Im}(S_C) = -\frac{|V_1|^2}{2} \cdot \omega C$$

$$S_L = \frac{V_1 \cdot I_C^*}{2} = \frac{|V_1|^2}{2} \cdot \frac{1}{\omega L} \Rightarrow Q_L = \text{Im}(S_L) = \frac{|V_1|^2}{2} \cdot \frac{1}{\omega L}$$

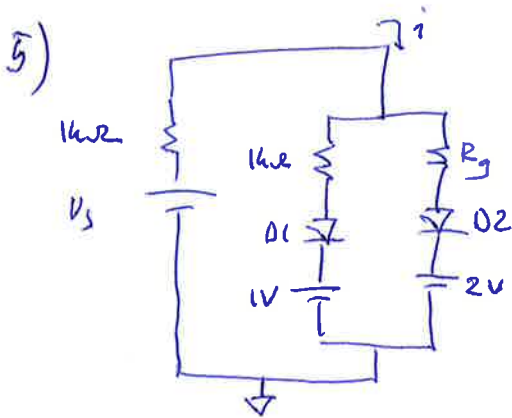

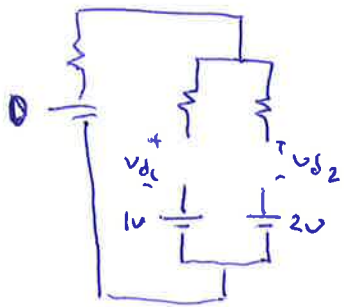a)  $V_S = 0V \Rightarrow i = 0A$ : D1 och D2 backspända.


$$\Rightarrow \underline{i_r = i_g = 0A}$$



Kontroll:  $V_{D1} = 0 - 1 = -1 \leq 0$  ok!

$$V_{D2} = 0 - 2 = -2 < 0 \quad \underline{\underline{ok!}}$$

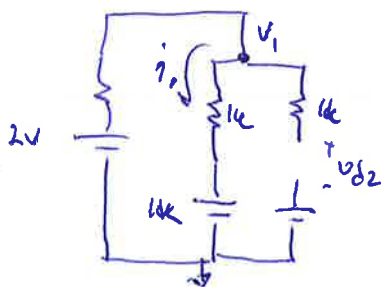b)  $V_S = 2V$ :  $\rightarrow$  D1 framspänd, D2 backspänd.



$$\text{KCL på } V_1: \frac{V_1 - 2}{10^3} + \frac{V_1 - 1}{10^3} = 0 \Rightarrow \underline{\underline{V_1 = 1,5V}}$$


$$i_r = \frac{1,5 - 1}{10^3} = 0,5 \mu A$$

$$i_g = 0A$$

Kontroll:  $i_r > 0$  ok!

$$V_{D2} = 1,5 - 2 = -0,5V \quad \underline{\underline{ok!}}$$

c)  $V_s = 4V$  D1 och D2 framspända.

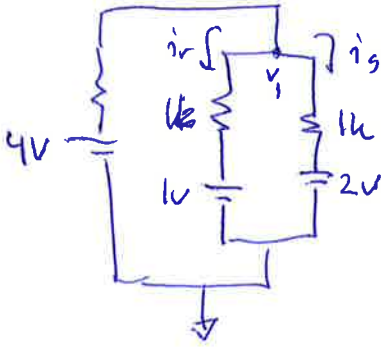


KCL på  $V_1$   $\frac{V_1 - 4}{10^3} + \frac{V_1 - 1}{10^3} + \frac{V_1 - 2}{10^3} = 0$

$\Rightarrow V_1 = \frac{7}{3}V$

$i_r = \frac{\frac{7}{3} - 1}{10^3} = \frac{4}{3} \text{ mA}$

$i_g = \frac{\frac{7}{3} - 2}{10^3} = \frac{1}{3} \text{ mA}$

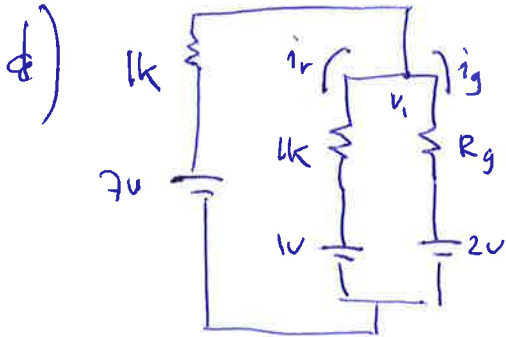Kontroll:  $i_r > 0$  ok!  
 $i_g > 0$  ok!



Både D1 och D2 ska vara framspända.

$i_r = i_g$


$\frac{V_1 - 7}{10^3} + \frac{V_1 - 1}{10^3} + \frac{V_1 - 2}{R_g} = 0$

Om  $i_r = i_g$ :  $\frac{V_1 - 7}{10^3} - 2 \cdot \frac{(V_1 - 1)}{10^3} = 0 \Rightarrow \underline{\underline{V_1 = 3V}}$

$i_r = \frac{3 - 1}{10^3} = 2 \text{ mA} \Rightarrow i_g = 2 \cdot 10^{-3} = \frac{3 - 2}{R_g}$

$\Rightarrow R_g = \frac{1}{2 \cdot 10^{-3}} = \underline{\underline{0,5 \text{ k}\Omega}}$


Kontroll:  $i_r = i_g > 0!$

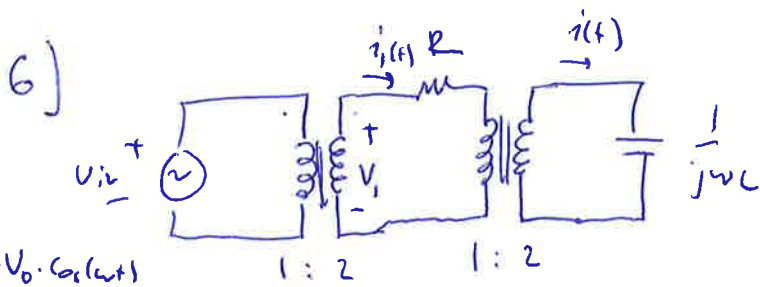

$j\omega$

$$V_1 = \frac{N_2}{N_1} \cdot V_0 = 2 \cdot V_0$$

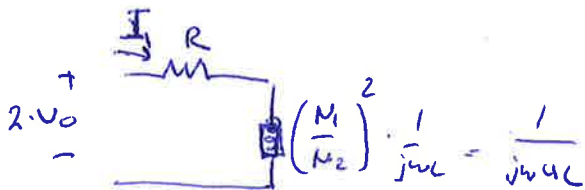$\frac{1}{j\omega C}$  impedans transformeras



$$I_1 = \frac{2 \cdot V_0}{R + \frac{1}{j\omega 4C}} = \frac{2 \cdot j\omega 4C}{1 + j\omega 4RC} \cdot V_0 = \frac{8 \cdot j\omega C}{1 + j\omega 4RC} \cdot V_0$$

$I_1$  är den (komplexa) ström som flyter in på primärsidan i Transformator 2.

$$\Rightarrow I = \frac{N_1}{N_2} \cdot I_1 = \frac{I_1}{2} = \frac{4 \cdot j\omega C}{1 + j\omega 4RC} \cdot V_0$$

$$\Rightarrow i(t) = \frac{4\omega C \cdot V_0}{\sqrt{(1 + (\omega 4RC)^2)}} \cdot \cos\left(\omega t + \frac{\pi}{2} - \arctan(\omega 4RC)\right)$$


---