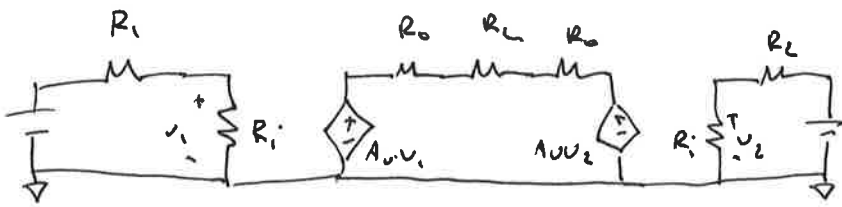



1)



a) 
$$V_L = \frac{R_0 + R_L}{2R_0 + R_L} \left( \frac{R_i}{R_i + R_1} \cdot U_1 - \frac{R_i}{R_i + R_2} \cdot U_2 \right)$$

b) 
$$R_i \rightarrow \infty, R_0 \rightarrow 0 \Rightarrow V_L = A_v (U_1 - U_2)$$


2)

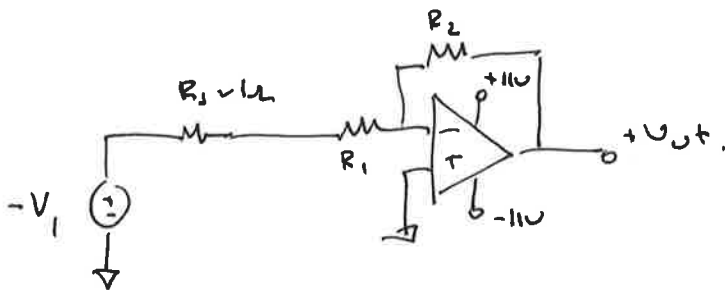

Da  $R_1 \gg R_s$  (ex  $R_1 = 1k\Omega$ ) bleibt  $R_s$  fortwahr!


$$\rightarrow U_{out} = -\frac{R_2}{R_1} \cdot U_1 \quad \begin{matrix} R_2 = 10k\Omega \\ R_1 = 1k\Omega \end{matrix}$$

act.

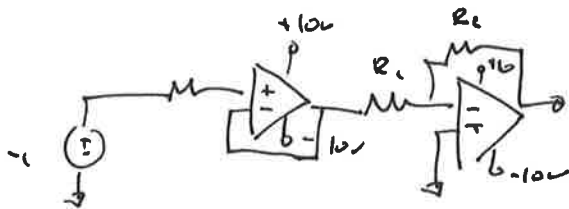

mit  $R_1 = 1k\Omega, R_2 = 10k\Omega$

3)

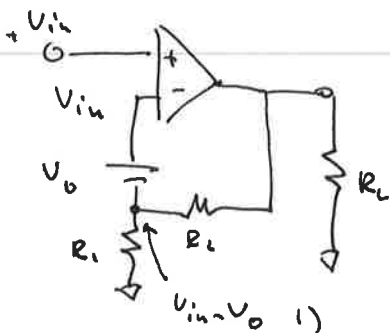


$$\begin{matrix} V_u = V_p \\ i_n = i_p = 0 \end{matrix}$$

KCL p1 1) 
$$\frac{U_{in} - U_0}{R_1} + \frac{(U_{in} - U_0) - U_L}{R_2} = 0$$

$$U_{in} - U_0 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{U_L}{R_2}$$

$$\Rightarrow U_L = U_{in} \cdot U_0 \left( 1 + \frac{R_2}{R_1} \right)$$

4) I mättnadsområdet

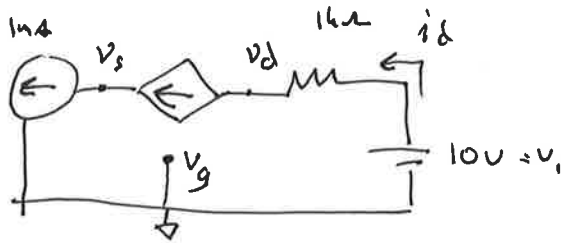

$$a) \quad V_d = 10 - i_d \cdot 10^3 = \underline{\underline{9V}}$$

Från kcl:  $i_d = 1mA$

$$b) \quad i_d = K(V_g - V_s - V_T) \Rightarrow 10^{-3} = 10^{-3}(-V_s - 2) \Rightarrow \underline{\underline{V_s = -3V}}$$

$V_g = 0V, V_T = 2V$

$$c) \quad \text{Mättnadsområdet: } V_{ds} \geq V_{gs} - V_T = 0 - (-3) = 2 = 1V$$


$$\Rightarrow V_d - V_s \geq 1V \Rightarrow V_d \geq 1 + V_s = \underline{\underline{-2V}}$$

$$V_d = V_1 - i_d \cdot 10^3 = V_1 - 1 \Rightarrow \underline{\underline{V_1 \geq -1V}}$$


5)

$$a) \quad \begin{array}{c|c|c|c} A & B & C' & C \\ \hline 0 & 0 & 1 & 0 \\ 1 & 0 & 1 & 0 \\ 0 & 1 & 1 & 0 \\ 1 & 1 & 0 & 1 \end{array}$$

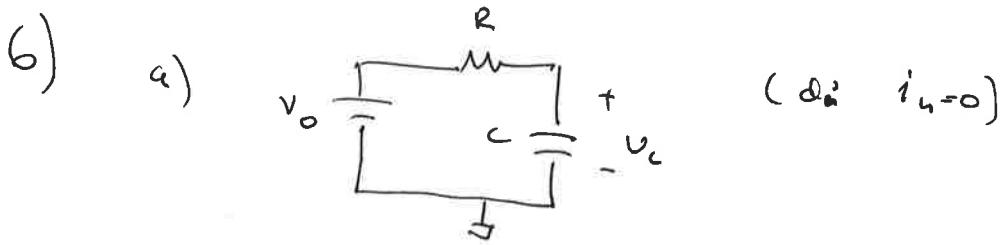b) Om  $V_{dd} = 0V \rightarrow \underline{\underline{V_c = 0V}}$


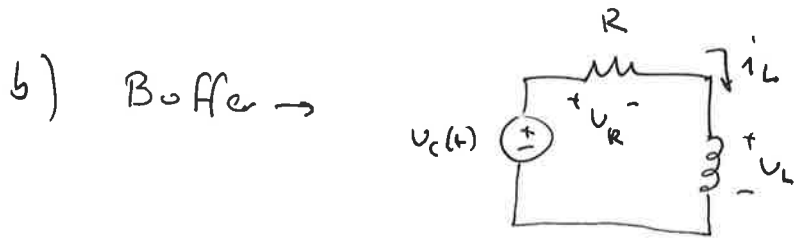
$$v_c = v_0 (1 - e^{-t/\tau}), \quad \tau = RC \quad (\text{Vandig RC-oppknytning})$$



$$\text{KVL: } v_R + v_L = v_c \Rightarrow R i_L(t) + L \frac{di}{dt} = v_c \Rightarrow i_L + \frac{i_L}{\tau} = \frac{v_c(t)}{L}, \quad \tau = \frac{L}{R} (= RC)$$

$$(i(t) \cdot e^{t/\tau})' = \frac{v_c(t)}{L} \cdot e^{t/\tau} = \frac{v_0}{L} (1 - e^{-t/\tau}) \cdot e^{t/\tau} = \frac{v_0}{L} (e^{t/\tau} - 1)$$

$$\rightarrow \text{Integrer: } \int_0^t [i(t) e^{t/\tau}]' dt = \frac{v_0}{L} \int_0^t (e^{t/\tau} - 1) dt =$$

$$= i(t) e^{t/\tau} - i(0) = \frac{v_0}{L} (\tau e^{t/\tau} - t - \tau) \Rightarrow i(t) = \frac{v_0}{L} (\tau - (t + \tau) \cdot e^{-t/\tau})$$

$$v_L(t) = L \cdot \frac{di}{dt} = v_0 \cdot \frac{d}{dt} (\tau - (t + \tau) \cdot e^{-t/\tau}) = v_0 \left( -e^{-t/\tau} - \frac{t}{\tau} e^{-t/\tau} + e^{-t/\tau} \right) =$$

$$= \underline{\underline{v_0 \cdot \frac{t}{\tau} \cdot e^{-t/\tau}}}$$

c)  $t \rightarrow \infty$ :  $\frac{1}{s} \rightarrow 1$ ,  $\frac{1}{s} \rightarrow 1$   $\Rightarrow v_c \rightarrow v_0$   
 $v_L \rightarrow 0$  (åker från a och b)