



LUND  
UNIVERSITY

# EITF35: Introduction to Structured VLSI Design

Part 2.2.1: Sequential circuit

Liang Liu  
liang.liu@eit.lth.se



# Outline

- **Sequential vs. Combinational**
- **Synchronous vs. Asynchronous**
- **Basic Storage Elements**
- **Timing**
- **Folding & Pipeline**



# Sequential vs. Combinational

## □ A combinational circuit:



## □ At any time, outputs depend only on present inputs

- Changing inputs changes outputs

## □ No regard for previous inputs

- No memory (history)


## □ Time is “ignored” !

- Time-independent circuit



# Sequential vs. Combinational

## □ A sequential circuit:

 

## □ Outputs depends on inputs and **past history** of inputs

- Previous inputs can be stored into **storage elements**
- **Input order matters**




# Sequential vs. Combinational: adders

□ Calculate  $A_3A_2A_1A_0 + B_3B_2B_1B_0$


□ Combinational adder

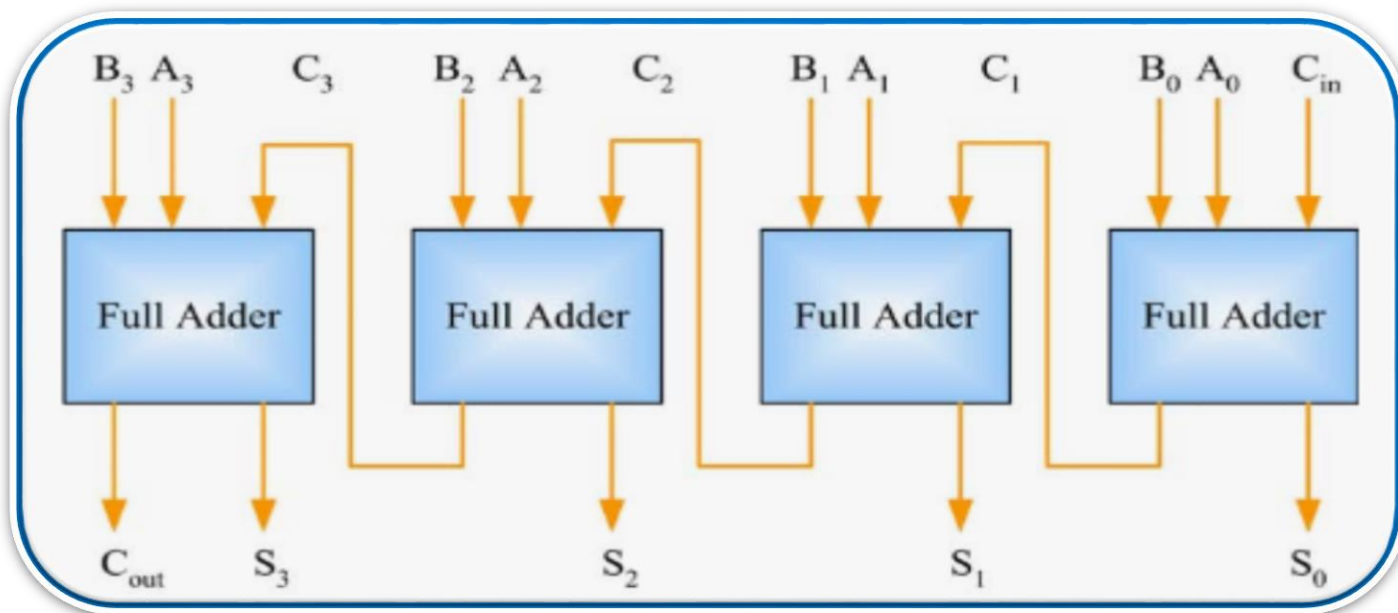- 4 full adders are required
- One adder is active at a time slot



# What we can do with storage elements?

## □ Sequential Adder

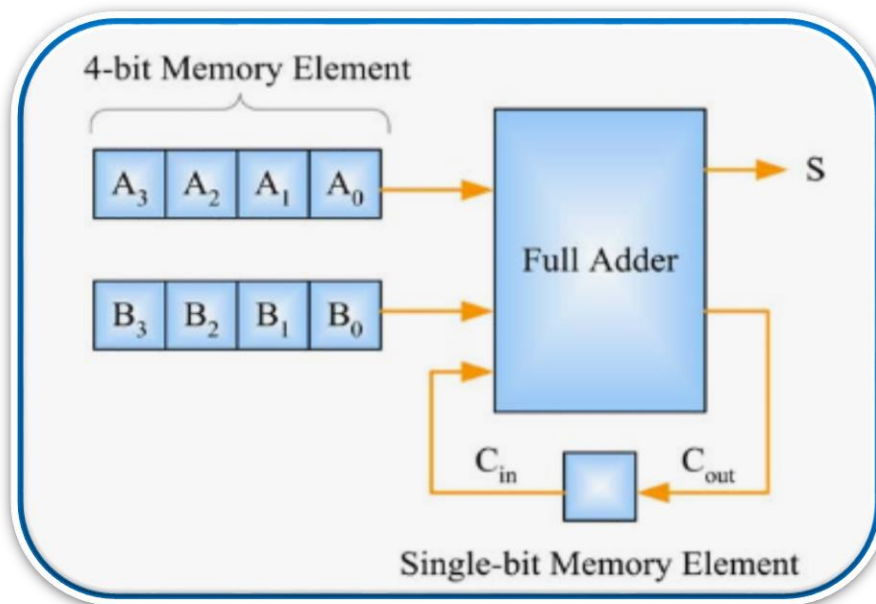

## □ Folding!

- One full adder
- 1-bit memory for carry
- Two 4-bit memory for operators

## □ 4 clock cycles to get the output



# Outline


- Sequential vs. Combinational
- **Synchronous vs. Asynchronous**
- Basic Storage Elements
- Timing
- Folding & Pipeline




# Synchronous vs. Asynchronous
 
## Two types of sequential circuits:

- **Synchronous**: The behavior of the circuit depends on the input signal at discrete instances of time (also called **clocked**)



 - **Asynchronous**: The behavior of the circuit depends on the input signals at **any instance of time**






# Synchronous vs. Asynchronous

- ❑ When you have a clock
- ❑ You know that washer takes 1 hour
- ❑ You put the laundry in the washer and leave
- ❑ Dry 1 hour later



# Synchronous vs. Asynchronous

□ What if you don't have a clock ...

 

# Synchronous or Asynchronous?

## □ Sync. Advantages: Simplicity to design, debug, and test

- Timing is controlled by one simple clock
- No hand-shake circuits
- Well supported by EDA tools
- Recommended for **VLSI**

## □ Sync. Disadvantages:

- Performance constrained by worst-case: critical path
- Overhead for clock network
- Less power efficient

***We will focus on synchronous circuits in this course***



# Power Example

Power Group	Internal Power	Switching Power	Leakage Power	Total Power ( %)	Attrs
io_pad	0.0000	0.0000	0.0000	0.0000 ( 0.00%)	
memory	0.0000	0.0000	0.0000	0.0000 ( 0.00%)	
black_box	0.0000	0.0000	0.0000	0.0000 ( 0.00%)	
clock_network	0.0137	4.982e-03	3.116e-05	0.0187 (13.76%)	
register	3.029e-03	1.298e-03	8.082e-04	5.136e-03 ( 3.79%)	
combinational	0.0518	0.0557	4.337e-03	0.1118 (82.45%)	



# Outline

- Sequential vs. Combinational
- Synchronous vs. Asynchronous
- **Basic Storage Elements**
- Timing
- Folding & Pipeline




# Basic storage element

- D latch: level sensitive
- D flip-flop (D-FF): edge sensitive



c	q*
0	q
1	d

*D latch*

 


clk	q*
0	q
1	q
$\uparrow$	d

*pos-edge triggered D-FF*



clk	q*
0	q
1	q
$\downarrow$	d

*neg-edge triggered D-FF*

 

reset	clk	q*
1	-	0
0	0	q
0	1	q
0	$\uparrow$	d

*D-FF with reset*



# Why Reset?

## □ Initial State



## □ Some Hints

- Efficient sync. design for complicated system
- The importance of sync initial state
- A good clock is crucial
- No timing violation


  
# Basic storage element

- D latch: level sensitive
- D flip-flop (D-FF): edge sensitive






# Problem with Latches

- ❑ Problem: A latch is transparent; state keep changing as long as the clock remains active
- ❑ Due to this uncertainty, latches can not be reliably used as storage elements.
- ❑ What happens if Clock=1? What will be the value of Q when Clock goes to 0?

Latch Example

 

**Most EDA software tools have difficulty with latches.**



# Outline

- Sequential vs. Combinational
- Synchronous vs. Asynchronous
- Basic Storage Elements
- Timing**
- Folding & Pipeline




# Flip Flops Timing

 
## *Very Important Timing Considerations!*

□ **Setup Time** ( $T_s$ ): The minimum time during which D input must be maintained **before** the clock transition occurs.

□ **Hold Time** ( $T_h$ ): The minimum time during which D input must not be changed **after** the clock transition occurs.




# Metastability in Digital Logic

 

# How fast can a synchronous circuit run?

## □ RTL (Register Transfer Level)

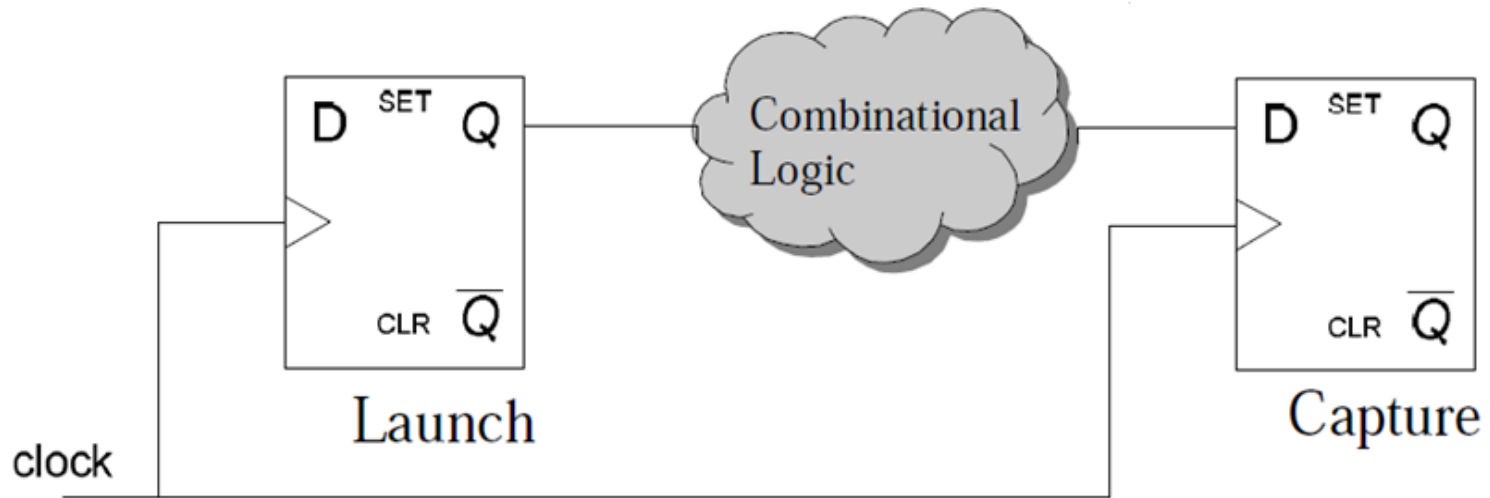

## □ Timing analysis:


- Starting with the clock rising edge at the launch FF, end with the clock rising edge (**next period or same period**) of the capture FF



# Setup Time
 
## □ Setup Timing analysis:


- Starting with the clock rising edge at the launch FF, end with the clock rising edge (**next period**) of the capture FF



□ **Data-Path (arrive time):**  $T_{\text{Combinational logic}} + FF_{\text{launch}}(\text{clk} \rightarrow Q)$

□ **Clock-Path (required time):** Clock Period -  $FF_{\text{capture}} t_{\text{Setup}}$

 
□ **Timing constraint :**  $T_{\text{Combinational logic}} + FF_{\text{launch}}(\text{clk} \rightarrow Q) < \text{Clock Period} - FF_{\text{capture}} t_{\text{Setup}}$



# Hold Time
 
## Hold Timing analysis:


- Starting with the clock rising edge at the launch FF, end with the clock rising edge (same period) of the capture FF



**Data-Path (arrive time):**  $T_{\text{Combinational logic}} + FF_{\text{launch}}(\text{clk} \rightarrow Q)$

**Clock-Path (required time):**  $FF_{t\text{Hold}}$

 **Timing constraint :**  $T_{\text{Combinational logic}} + FF_{\text{launch}}(\text{clk} \rightarrow Q) > FF_{t\text{Hold}}$



# Clock uncertainty

□ Clock uncertainty = skew ± jitter


□ Clock skew

- The (knowable) difference in clock arrival times at each flip-flop
- Caused mainly by imperfect balancing of clock tree/mesh

□ Clock jitter

- The random (unknowable) difference in clock arrival times at each flip-flop
- Caused by on-die process,  $V_{dd}$ , temperature variation, PLL jitter, crosstalk.

 
□ Clock tree to minimize clock uncertainty





 
# Clock uncertainty

□ Clock uncertainty = skew  $\pm$  jitter





□ Timing analysis with clock uncertainty

 


$$T_{\text{Combinational logic}} + FF_{\text{launch}}(\text{clk} \rightarrow \text{Q}) < \text{Clock Period} - FF_{\text{tSetup}} - \text{Clock Uncertainty}$$



# Clock tree

  

**Clock-tree Asic**

 


**Global clock network in Xilinx FPGA**


DS001\_08\_002100



# Time borrow

 

# Time borrow

 

# Outline

- Sequential vs. Combinational
- Synchronous vs. Asynchronous
- Basic Storage Elements
- Timing
- **Folding & Pipeline**



# Pipeline


## □ Acknowledgement:

- The following slides have been provided by Prof. Ward in September 2004.
- Reformatting of PowerPoint and addition of two more slide done September 2007 by Jens Sparsø.
- Slides are used in DTU course 02154 Digital Systems Engineering (fall 2008).
- Due to Joachim Rodrigues' position at DTU, I used some of the slides in EITF35.



# Pipelining

## □ Start again from laundry room

 

## □ Small laundry has one washer, one dryer and one folder, it takes 110 minutes to finish one load:


- Washer takes 40 minutes
- Dryer takes 50 minutes
- “Folding” takes 20 minutes



## □ Need to do 4 laundries



# Not very smart way...

 


$$\begin{aligned} \text{Total} &= N * (\text{Washer} + \text{Dryer} + \text{Folder}) \\ &= \underline{\quad 440 \quad} \text{ mins} \end{aligned}$$





# If we pipelining

 


$$\text{Total} = \text{Washer} + N * \text{Max}(\text{Washer}, \text{Dryer}, \text{Folder}) + \text{Folder}$$

$$= \underline{\quad 260 \quad} \text{ mins}$$



# Pipeline Facts

 

- Multiple tasks operating simultaneously
- Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- Pipeline rate limited by slowest pipeline stage**
- Unbalanced** lengths of pipe stages reduces speedup
- Potential speedup  $\propto$  **Number of pipe stages**




# Some definitions

# Very Important!

- **Latency**: The delay from when an input is established until the output associated with **that input** becomes valid.

(non-pipeline Laundry = 110 mins)

( pipeline Laundry = 120 mins)

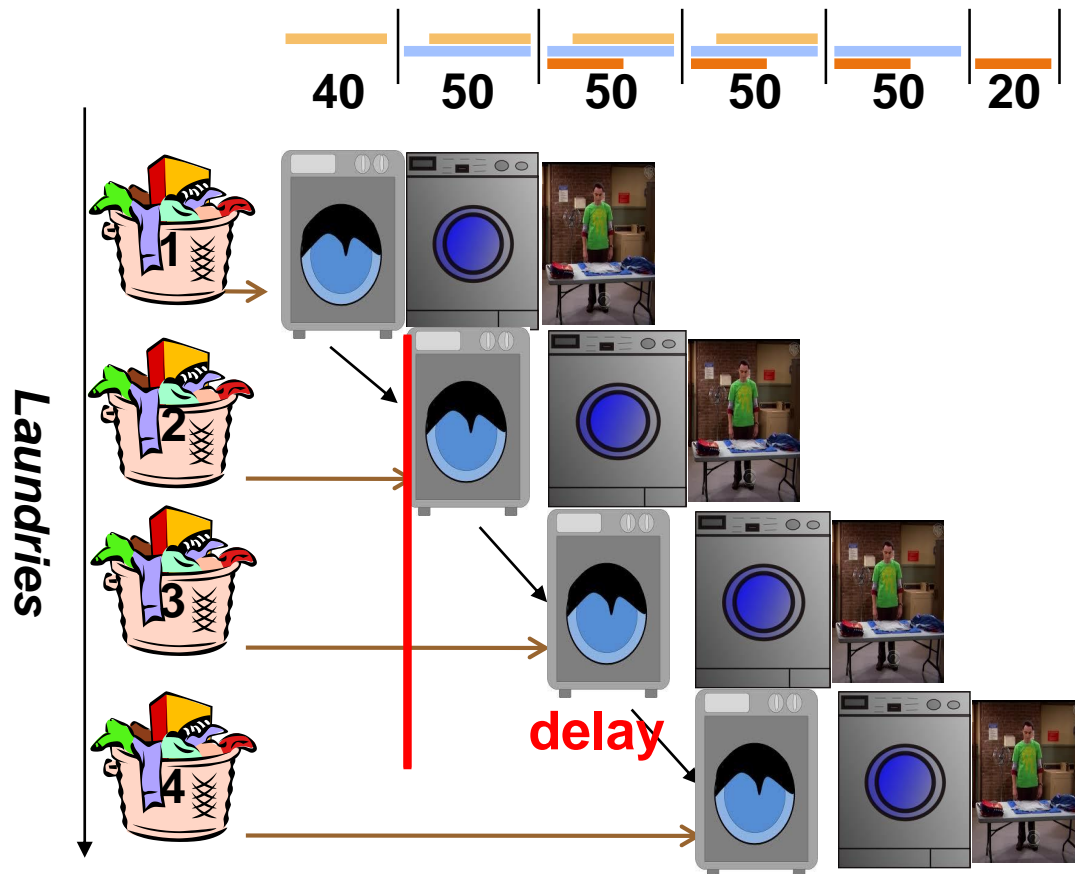


# Some definitions

# Very Important!


- **Throughput:** The rate of which **inputs** or **outputs** are processed or **how frequently** a laundry can be loaded

(non-pipeline Laundry =  $\frac{1}{110}$  outputs/min)

 (pipeline Laundry =  $\frac{1}{50}$  outputs/min)




# Okay, back to circuits...

 

□ **Combinational logic:**

*latency =  $t_{PD}$ ,*  
*throughput =  $1/t_{PD}$ .*

 □ **Can we use the hardware more efficiently?**




*F & G are “idle”, just holding their outputs stable while H performs its computation*


 
# Pipelined Circuits

use registers to hold  $H$ 's input stable!



## □ Pipelined circuit:



- 2-stage *pipeline*: if we have a valid input  $X$  during clock cycle  $j$ ,  $P(X)$  is valid during clock  $j+2$ .
- Now  $F$  &  $G$  can be working on input  $X_{i+1}$  while  $H$  is performing its computation on  $X_i$ .

Suppose  $F$ ,  $G$ ,  $H$  have propagation delays of 15, 20, 25 ns and we are using ideal zero-delay registers:

	<u>latency</u>	<u>throughput</u>
un-pipelined	45	1/45
2-stage pipelined	<u>50</u>	<u>1/25</u>
	worse	better




# Pipeline timing diagrams

  

# Ill-formed pipelines

Consider a BAD job of pipelining:

 

Problem:

Some paths from inputs to outputs had 2 registers, and some had only 1!

**Make sure every paths have been pipelined with same stages**





# Combinational, Folding and Pipelined

## □ Combinational Circuits

- **Advantage:** low latency
- **Disadvantage:** low throughput, more hardware, low utilization

## □ Folding

- **Advantage:** less hardware, high utilization
- **Disadvantage:** high latency, limited application

## □ Pipeline

- **Advantage:** very high throughput
- **Disadvantages:** pipeline latency, more hardware



# Thanks!

