



LUND
UNIVERSITY

EITF35: Introduction to Structured VLSI Design

Part 2.2.2: VHDL-3

Liang Liu
liang.liu@eit.lth.se



Outline

□ Inference of Basic Storage Element

□ Some Design Examples

- DFF with enable
- Counter

□ Coding Style: Segment

□ Variables in Sequential Circuit

□ Poor Design Examples




Inference of Basic Storage Elements

❑ VHDL code should be clear so that the pre-designed cells can be inferred

- As an architecture designer, you need to be very familiar with the available elements

❑ VHDL code of storage elements

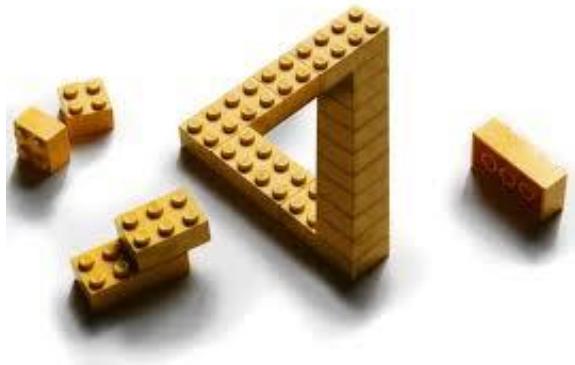
- Positive edge-triggered D FF
- Negative edge-triggered D FF
- D FF with asynchronous reset
- D Latch (**DON'T USE**)



Positive edge-Triggered D FF

- ❑ No else branch
- ❑ Note the sensitivity list (*only clk*)
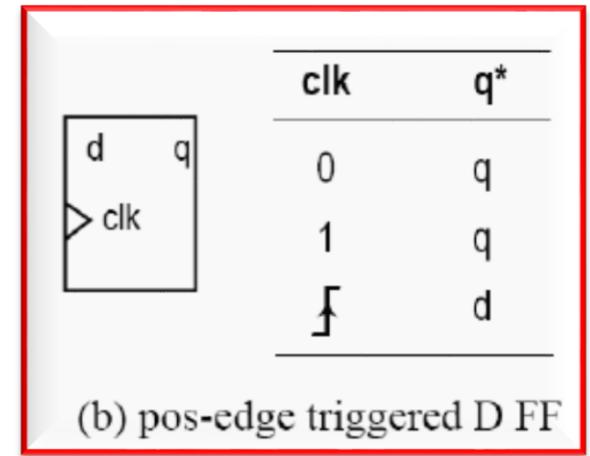
```
library ieee;
use ieee.std_logic_1164.all;
entity dff is
  port(
    clk: in std_logic;
    d: in std_logic;
    q: out std_logic
  );
end dff;
architecture arch of dff is
begin
  process (clk)
  begin
    if (clk'event and clk='1') then
      q <= d;
    end if;
  end process;
end arch;
```




rising_edge(clk)



Negative edge-Triggered D FF
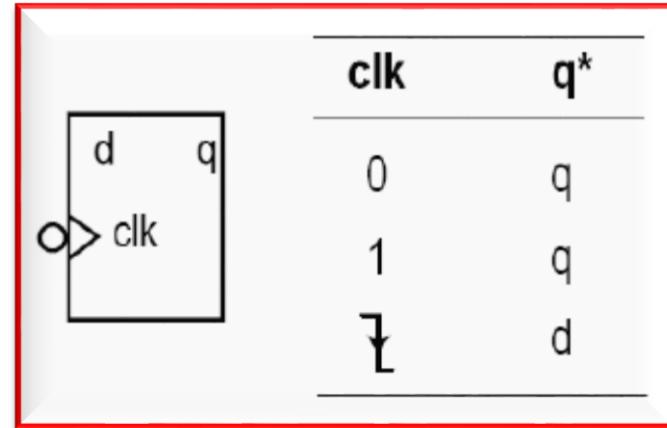
```
library ieee;
use ieee.std_logic_1164.all;
entity dff is
  port(
    clk: in std_logic;
    d: in std_logic;
    q: out std_logic
  );
end dff;
architecture arch of dff is
begin
  process (clk)
  begin
    if (clk'event and clk='0') then
      q <= a;
    end if;
  end process;
end arch;
```



falling_edge(clk)




D FF with Async. Reset

```
entity dffr is
  port(
    clk: in std_logic;
    reset: in std_logic;
    d: in std_logic;
    q: out std_logic
  );
end dffr;
architecture arch of dffr is
begin
  process (clk,reset)
  begin
    if (reset='1') then
      q <= '0';
    elsif (clk'event and clk='1') then
      q <= d;
    end if;
  end process;
end arch;
```

reset	clk	q*
d	q	0
> clk	0	0
reset	0	1
	0	d
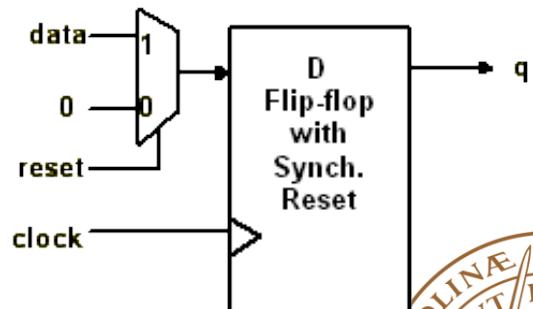
```
process (clk)
begin
  if rising_edge(clk) then
    if rst = '1' then
      Q <= '0';
    ...
  end if;
end process;
```



D FF in Xilinx FPGA

Flip-Flops, Registers, and Latches

Vivado synthesis recognizes Flip-Flops, Registers with the following control signals:

- Rising or falling-edge clocks
- Asynchronous Set/Reset
- Synchronous Set/Reset
- Clock Enable

Coding Guidelines


- Do not set or reset Registers asynchronously.
 - Control set remapping becomes impossible.
 - Sequential functionality in device resources such as block RAM components and DSP blocks can be set or reset synchronously only.
 - You will be unable to leverage device resources, or they will be configured sub-optimally.
- Avoid operational set/reset logic whenever possible. There may be other, less expensive, ways to achieve the desired effect, such as taking advantage of the circuit global reset by defining an initial content.
- Always describe the clock enable, set, and reset control inputs of Flip-Flop primitives as active-High. If they are described as active-Low, the resulting inverter logic will penalize circuit performance.



D Latch (Learn How to Avoid)

Bad1:
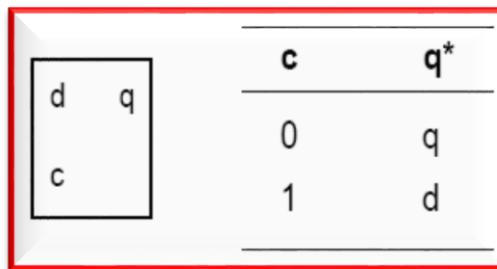
```
process (sA,sB,a,b)
begin
    if sA='1' then
        z<=a;
    elsif sB='1' then
        z<=b;
    end if;
end
```




A timing diagram illustrating a D latch. It shows four signals: d, q, c, and q*. The d signal is high for the first half of the period. The q signal is high during the second half. The c signal is high during the first half. The q* signal is high during the second half.

c	q*
0	q
1	d

Bad2:

```
process (sA,a,b)
begin
    if sA='1' then
        f<=a;
    end if;
end process Bad2;
```

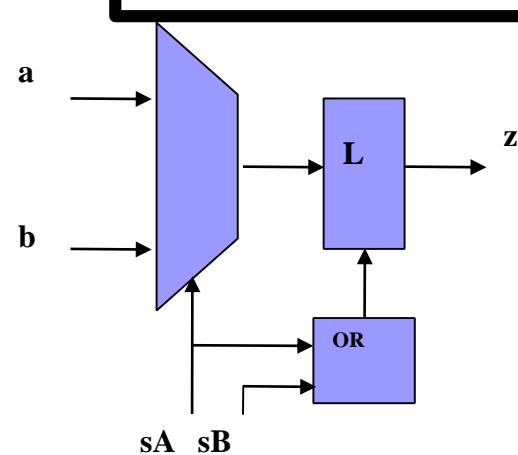

Bad3: process (sA,sB,a,b,z)

```
begin -- use case statement
    case S is
        when "00" => O <= I0;
        when "01" => O <= I1;
        when "10" => O <= I2;
    end case;
end process Bad3;
```






Exercise

```
c1: process(clk)
begin
  if (clk 'event
and clk = '1') then
    q<='1';
  end if;
end process c1;
```

```
c2: process(clk)
begin
  if (clk='1') then
    q<='1';
  end if;
end process c2;
```

```
c3: process(clk)
begin
  if (clk='1') then
    q<='1';
  else
    q<='0';
  end if;
end process c3;
```

What is the corresponding circuits?

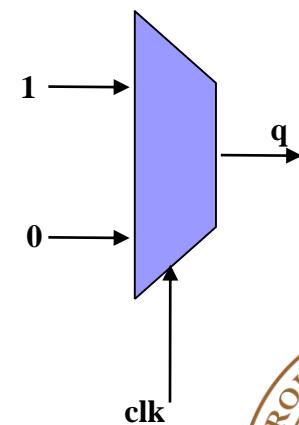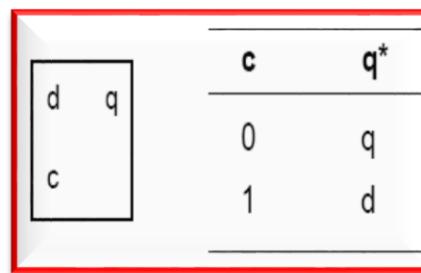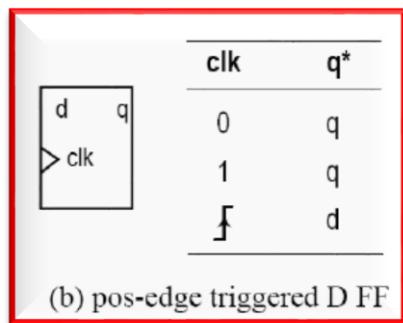

Outline

□ Inference of Basic Storage Element

□ Some Design Examples

- DFF with enable
- Counter

□ Coding Style: Segment

□ Variables in Sequential Circuit

□ Poor Design Examples




Design Examples: D FF with sync enable

□ Sync Enable

- Means the enable signal is controlled by clock

reset	clk	en	q*
1	-	-	0
0	0	-	q
0	1	-	q
0	↑	0	q
0	↑	1	d

function

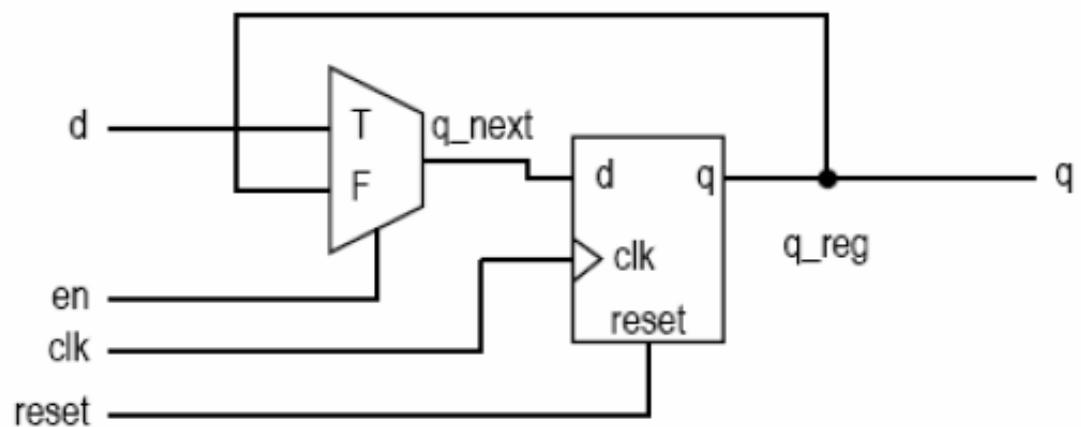


circuit



Design Examples: D FF with sync enable
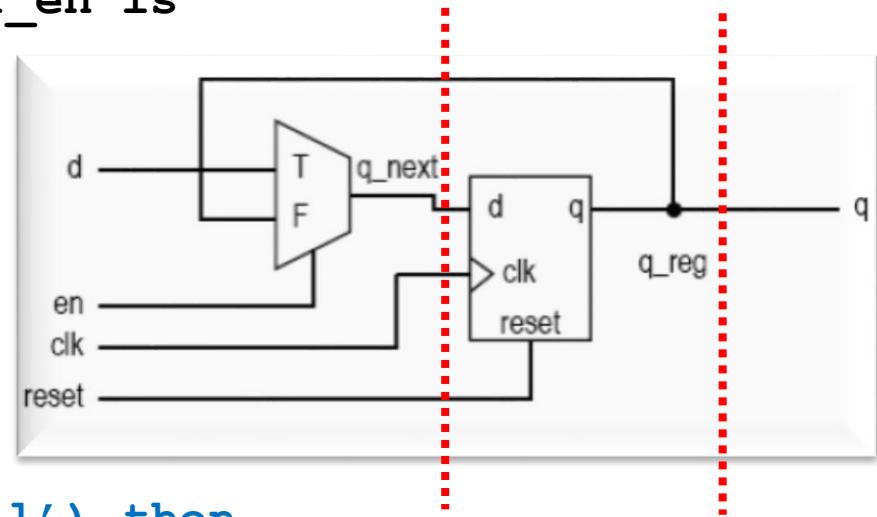
```
architecture two_seg_arch of dff_en is
signal q_reg:std_logic;
signal q_next:std_logic;
begin
-- D FF
process (clk, reset)
begin
  if (reset='1') then
    q_reg <= '0';
  elsif (clk'event and clk='1') then
    q_reg <= q_next;
  end if ;
end process;
-- next-state logic
q_next <= d when en ='1' else
          q_reg;
-- output logic
q <= q_reg;
end two_seg_arch;
```




**Multi-Segment
(at least two)
Recommended!**



Design Examples: Binary Counter

□ Binary Counter

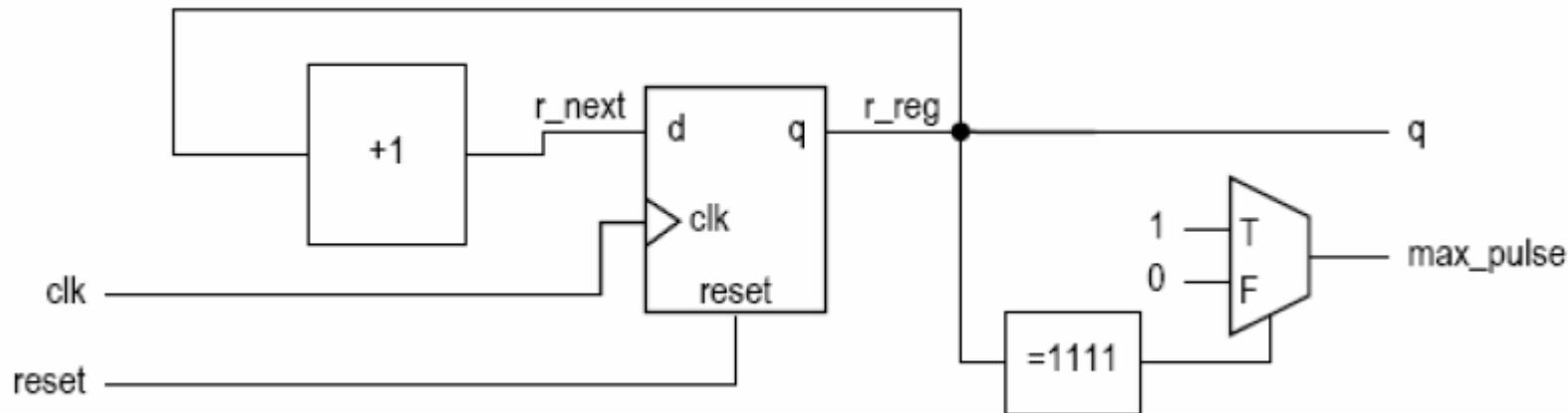- Circulates through a sequence that resembles the unsigned binary number
- Count from 0 to 15 and repeat
- Set a flag when counting to 15



Design Examples: Binary Counter

```
entity binary_counter4_pulse is
  port( clk, reset: in std_logic;
        max_pulse: out std_logic;
        q: out std_logic_vector (3 downto 0);
end binary_counter4_pulse ;
architecture two_seg_arch of binary_counter4_pulse is
  signal r_reg : unsigned (3 downto 0) ;
  signal r_next : unsigned (3 downto 0) ;
  process (clk, reset)
    begin
      if (reset='1') then r_reg <= ( others=> '0') ;
      elsif (clk'event and clk='1') then r_reg <= r_next;
      end if;
    end process;
    r_next <= r_reg + 1; -- incrementor
    q <= std_logic_vector(r_reg);
    max_pulse <= '1' when r_reg= "1111" else '0'; -- output
  end two_seg_arch;
```



Design Examples: Binary Counter

□ How to wrap around: 1111->0000

- Poor code ('Wrong' code)

bad: `r_next <= (r_reg + 1) mod 16`

□ In the `IEEE numeric_std` package, “+” on the `unsigned` data type is modeled after a **hardware adder**

□ Wrap around **automatically** when the addition result exceeds the range.

□ **Mod** operation may not be synthesized

Good: `r_next <= (r_reg + 1)`

How to wrap if we count from 0 to 9?



Outline

□ Inference of Basic Storage Element

□ Some Design Examples

- DFF with enable
- Register shifter
- Counter

□ Coding Style: Segment

□ Variables in Sequential Circuit

□ Poor Design Examples



Coding Style: Segment

□ One-segment

- Describe storage and combinational logic in one process
- May appear compact for certain simple circuit
- But it can be error-prone




*Is integration
always better???*



Segment: D FF with sync enable
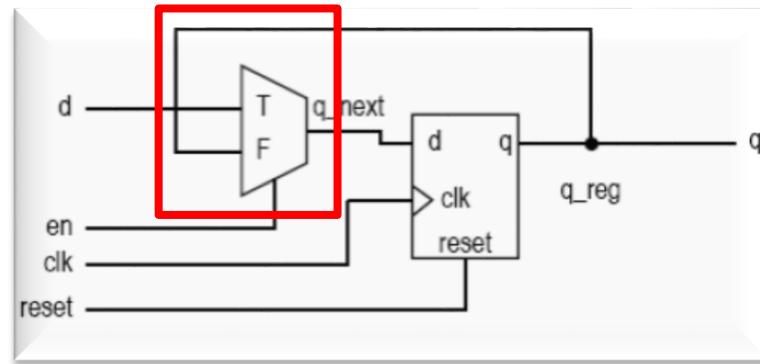
```
architecture one_seg_arch of dff_en is
begin
  process (clk,reset)
    begin
      if (reset='1') then
        q <= '0';
      elsif (clk'event and clk='1') then
        if (en='1') then
          q <= d;
        end if;
      end if;
    end process;
end one_seg_arch;
```




Segment: Binary Counter

```
architecture not_work_one_seg_glitch_arch
  of binary_counter4_pulse is
  signal r_reg: unsigned(3 downto 0);
begin
  process(clk,reset)
  begin
    if (reset='1') then
      r_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      r_reg <= r_reg + 1;
      if r_reg="1111" then
        max_pulse <= '1';
      else
        max_pulse <= '0';
      end if;
    end if;
  end process;
```

What will be
the circuit?



Segment: Binary Counter

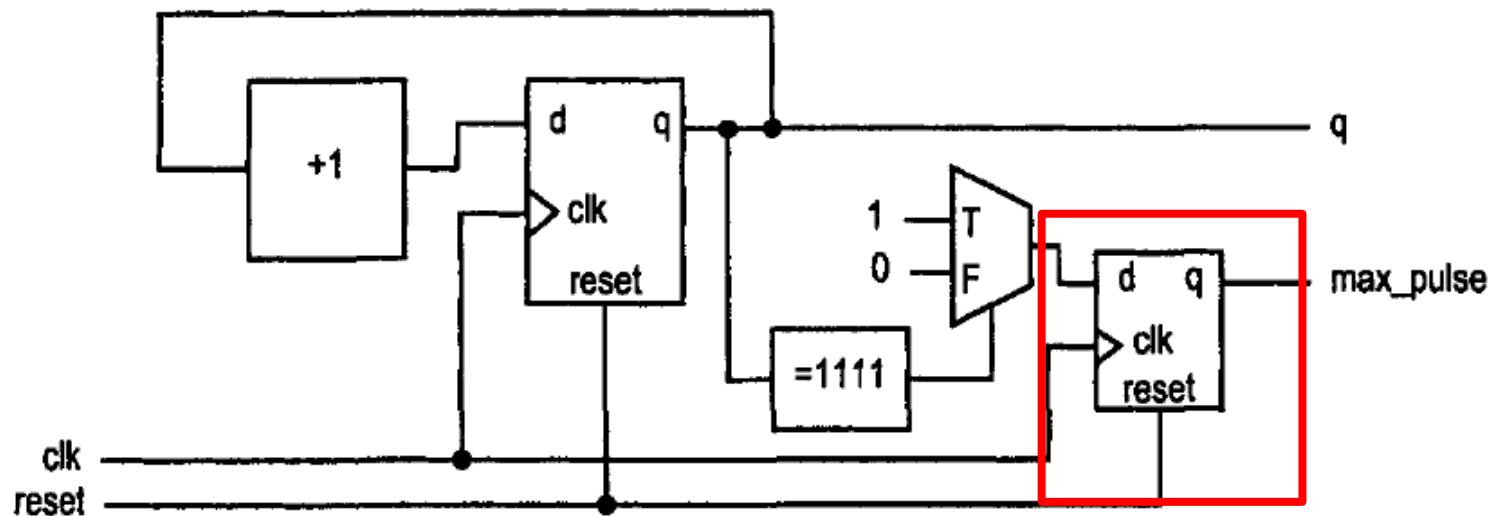

- A 1-bit register is inferred for the `max_pulse` signal.
- The register works as a buffer and *delays the output by one clock cycle*,
- and thus the `max_pulse` signal will be asserted when `r_reg="0000"`.



Segment: Summary

□ Two-segment code


- Separate storage segment from the rest
- Has a clear mapping to hardware component
- *Is preferred and recommended*

□ One-segment code

- Mix memory segment and next-state logic/output logic
- Can sometimes be more compact
- No clear hardware mapping
- Error prone



Segment: Summary

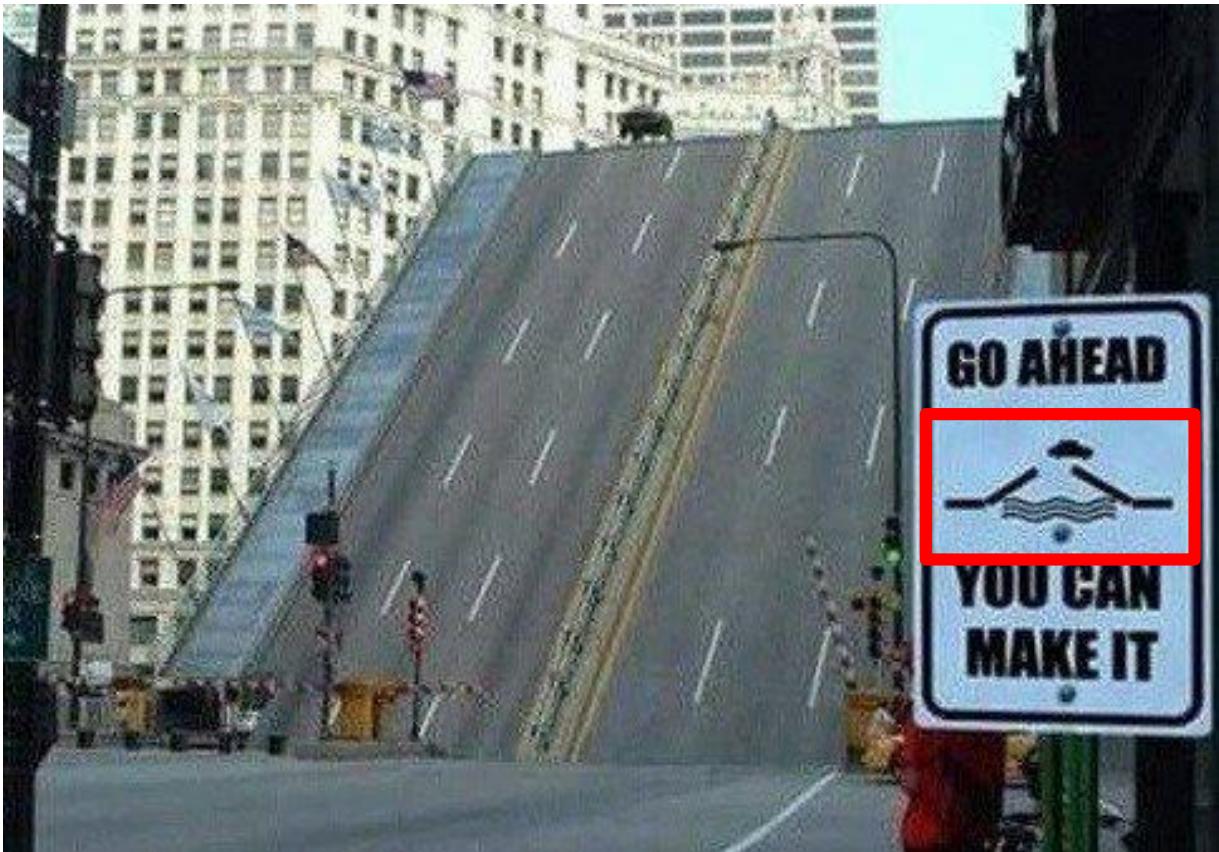

□ Keep the *hardware and the corresponding coding*

Go ahead, two-segment works!

are referred as registers



Outline

□ Inference of Basic Storage Element

□ Some Design Examples

- DFF with enable
- Register shifter
- Counter

□ Coding Style: Segment

□ Variables in Sequential Circuit

□ Poor Design Examples




Variables in Sequential Circuit

- Signals **always imply an FF** under `clk' event` and `clk='1'` condition
- When you don't want to infer an FF in a **one-segment process**
- Variable is **local** in a process and is not needed outside
- Variable may imply differently
 - Variable is used **after** it is assigned: get a value every time when the process is invoked
 - ***no register is inferred***
 - Variable is used **before** it is assigned: use the value from the previous process execution
 - ***FF or register need to be inferred***



Variables in Sequential Circuit: Example
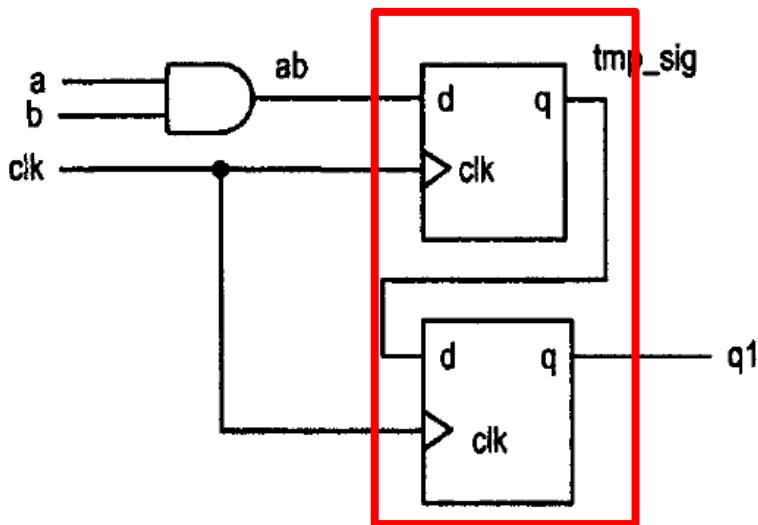
```
architecture arch of varaiable_ff_demo is
signal tmp_sig1: std_logic;
begin
process (clk)
begin
if (clk'event and clk='1') then
    tmp_sig1 <= a and b;
    q1 <= tmp_sig1;
end if ;
end process;
```




- Registers are inferred
- *q1* is one clock later than *tmp_sig1*



Variables in Sequential Circuit: Example
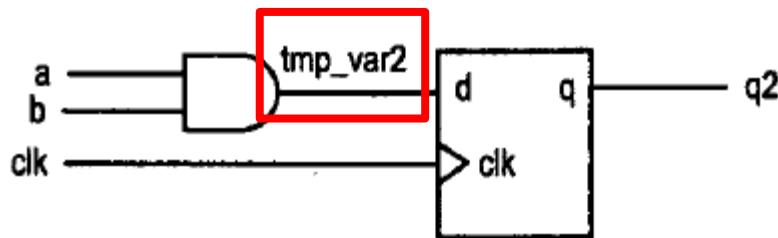
```
architecture arch of varaiable_ff_demo is
begin
  process (clk)
    variable tmp_var2: std_logic; -- declare in process
  begin
    if (clk'event and clk='1') then
      tmp_var2 := a and b; -- notice assignment format
      q1 <= tmp_var2;
    end if ;
  end process;
```




- Use variable
- *tmp_sig2* is used after it is assigned
- Just a hard wire, no Reg. is inferred



Variables in Sequential Circuit: Example
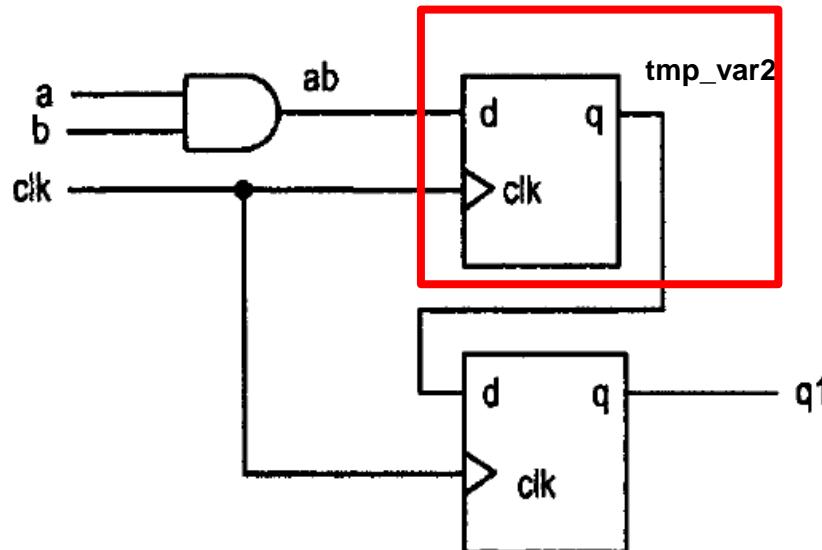
```
architecture arch of varaiable_ff_demo is
begin
  process (clk)
    variable tmp_var2: std_logic; -- declare in process
  begin
    if (clk'event and clk='1') then
      q1 <= tmp_var2;
      tmp_var2 := a and b; -- change the assignment order
    end if ;
  end process;
```



No Variables!



Outline

□ Inference of Basic Storage Element

□ Some Design Examples

- DFF with enable
- Register shifter
- Counter

□ Coding Style: Segment


□ Variables in Sequential Circuit

□ Poor Design Examples



Poor Design : Misuse of asynchronous reset

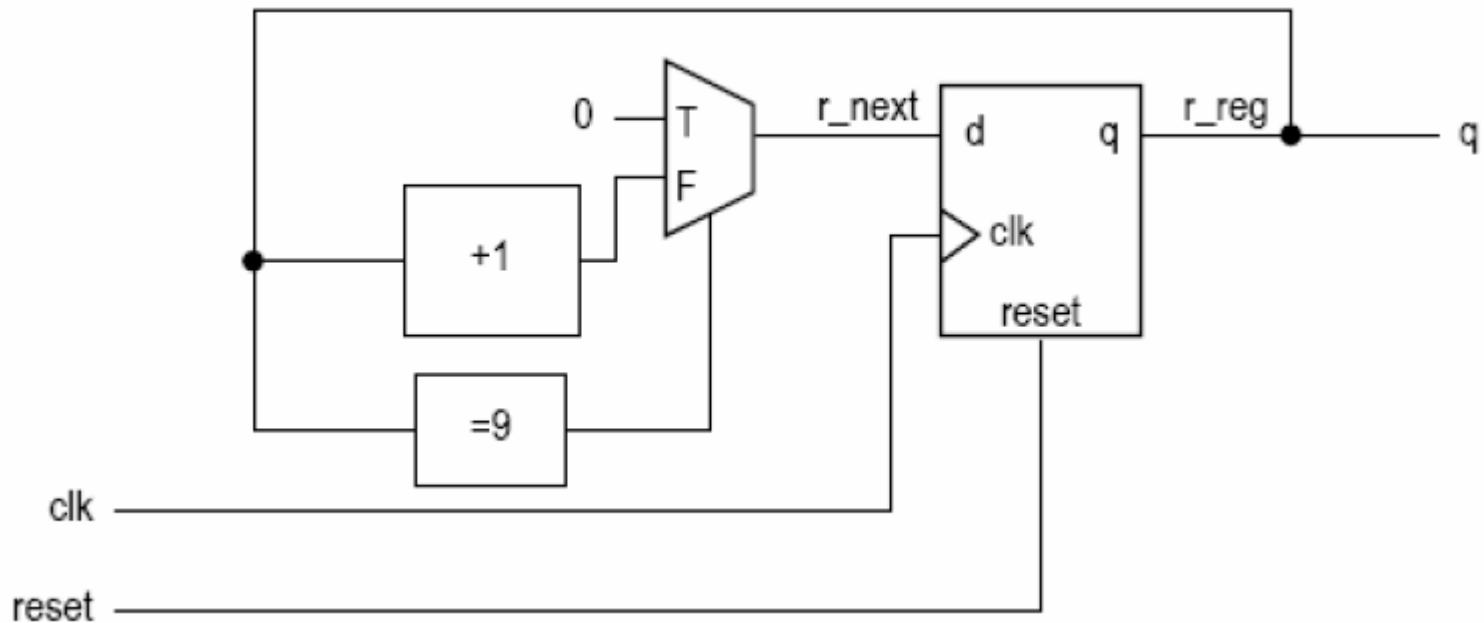□ Example: a mod-10 counter: 0,1,2 ...,7,8,9, 0,1,2..., 7,8,9,0



How to wrap from 9 to 0?





Poor Design : Misuse of asynchronous reset

```
entity mod10_counter is
  port(clk,reset: in std_logic; q:out std_logic_vector (3 downto 0));
end mod10_counter;
architecture poor_async_arch of mod10_counter is
  signal r_reg: unsigned (3 downto 0) ;
  signal r_next: unsigned (3 downto 0) ;
  signal async_clr: std_logic;
begin
  process (clk,async_clr)
    begin
      if (async_clr='1') then
        r_reg <= (others=>'0');
      elsif(clk'event and clk='1') then
        r_reg<=r_next;
      end if ;
    end process;
    r_next <= r_reg + 1;
    async_clr <='1' when (reset='1'or r_reg="1010") else '0';
    q <= std_logic_vector(r_reg);
  end poor_async_arch;
```




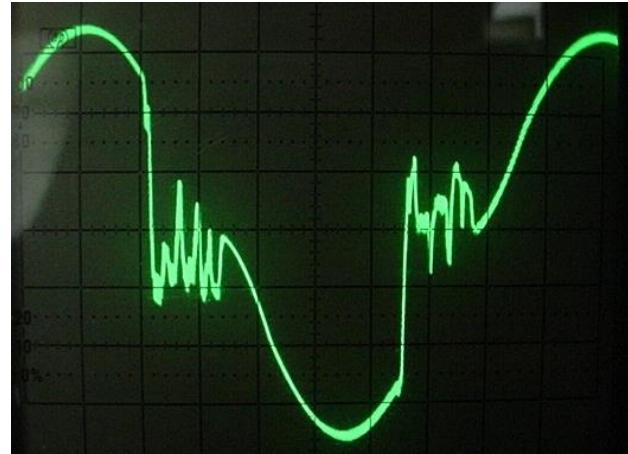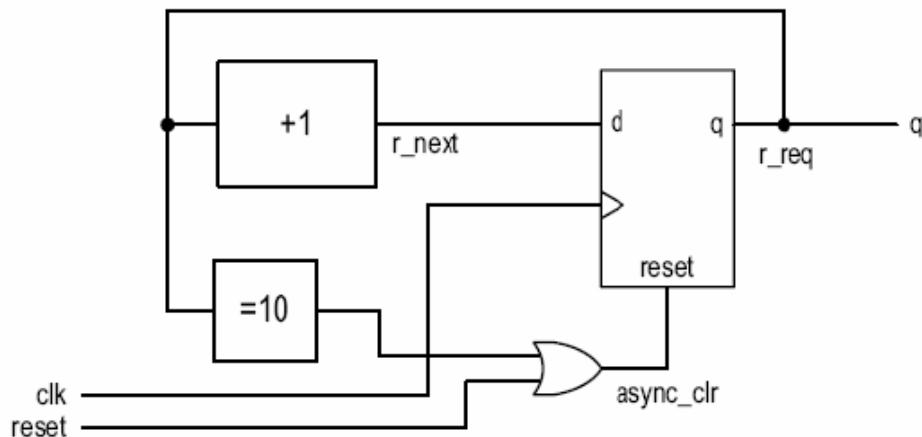Poor Design : Misuse of asynchronous reset



□ Problems

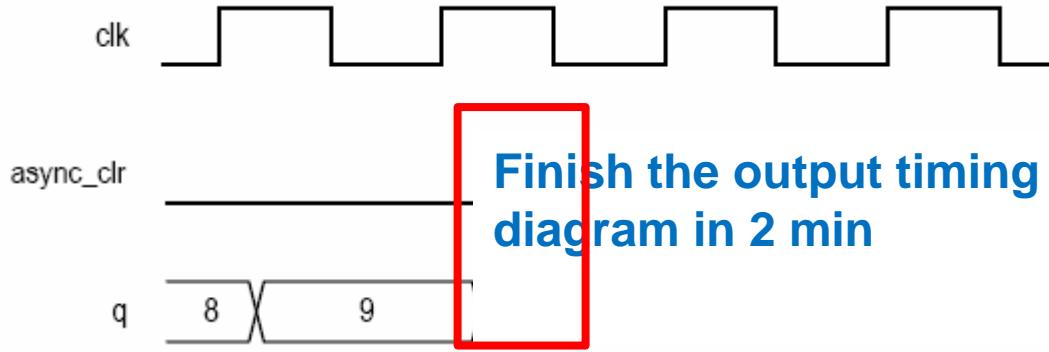- Glitch in counter: `r_req` goes to 10 and then reset, due to the delay of comparator
- **Glitches** in `async_clr` can reset the counter mistakenly




Poor Design : Misuse of asynchronous reset


□ Remedy

```
architecture two_seg of mod10_counter is
    signal r_reg: unsigned (3 downto 0) ;
    signal r_next: unsigned (3 downto 0) ;
begin
    process (clk,reset)
        begin
            if (reset = '1') then r_reg <= (others=>'0') ;
            elsif(clk'event and clk='1') then r_reg<=r_next;
            end if ;
        end process;
        r_next <= (others=>'0') when (r_reg=9) else r_reg+1;
        q <= std_logic_vector(r_reg);
    end two_seg;
```

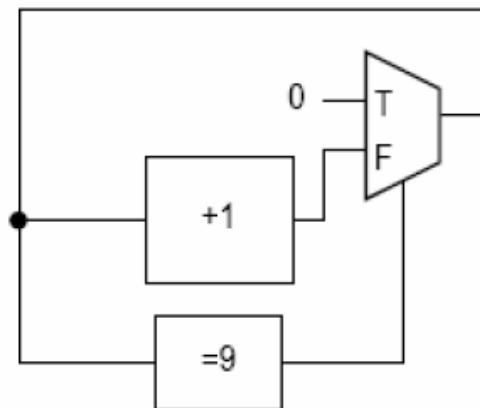**asynchronous reset should
ONLY be used for initialization!**



Poor Design : Misuse of derived clocks

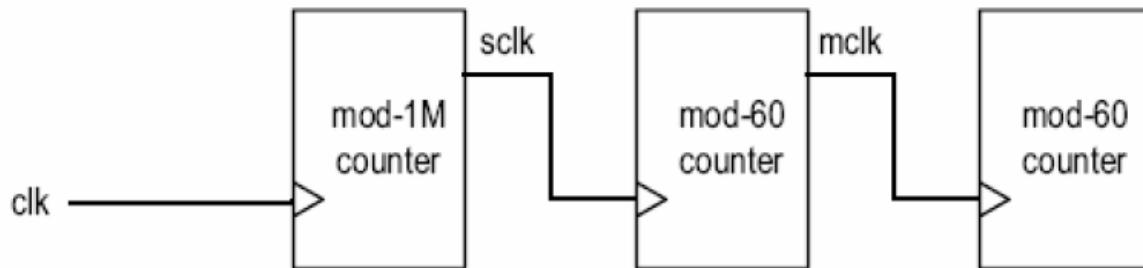

(a) Design with derived clock



Reading advice

RTL Hardware Design Using VHDL: P213-P254



Thanks

