 



Lab Assignment 2



Interfacing Keyboard with FPGA Board

Oskar Westman

elt13owe@student.lu.se

 

What happens when you press/release a key?

- **Key pressed = make code is generated.**
- **Key released = break code is generated.**

key	make	break
A	'1C'h	'F0'h '1C'h
B	'32'h	'F0'h '32'h
C	'21'h	'F0'h '21'h



How does the keyboard send data?



 


Figure 1: Key Board interface waveform

 

Scan codes


 
- Each key is assigned a unique scan code.



FPGA



  - Pressed key shows on FPGA -- 7 SEGEMENT DISPLAY



Demostration



- Check the reset condition, all display should be switched off at reset.
- Pressing "123456" one by one, the display should look the following:

Seven Segement Display

DISPLAY OFF			
			1
		1	2
	1	2	3
1	2	3	4
2	3	4	5
3	4	5	6

press (sw0) reset

press 1

press 2

press 3

press 4

press 5

press 6

Main Processes



- **Synchronizing Keyboard with FPGA.**
- **Detection of falling edge of keyboard Clock. (why?)**
- **Storing of relevant Scan Code from keyboard (meaning?).**
- **Display of 'numbers' keys on Seven Segment.**
- **Shift the previous key left and display the current number when the next number key is pressed.**

Why falling edge?



1.2 Reading Keyboard Scan Codes Through the PS/2 Interface on the Board

The keyboards provided in the lab has a USB interface, however, don't worry, we won't ask you to implement a USB host, which is a very complex design. In our case fortunately the FPGA board has a USB host (PIC microcontroller) implemented already. This USB host converts the keyboard interface to old PS/2 format interface, and we will design the controller for this interface.

The old PS/2 PC keyboard transmits data in a clocked serial format consisting of a start bit, 8 data bits with least significant bit (LSB) first, an odd parity bit and a stop bit. The clock signal is only active during data transmission. The generated clock frequency is usually in the range of 10 - 30 kHz. Each bit should be read on the falling edge of the clock.



 
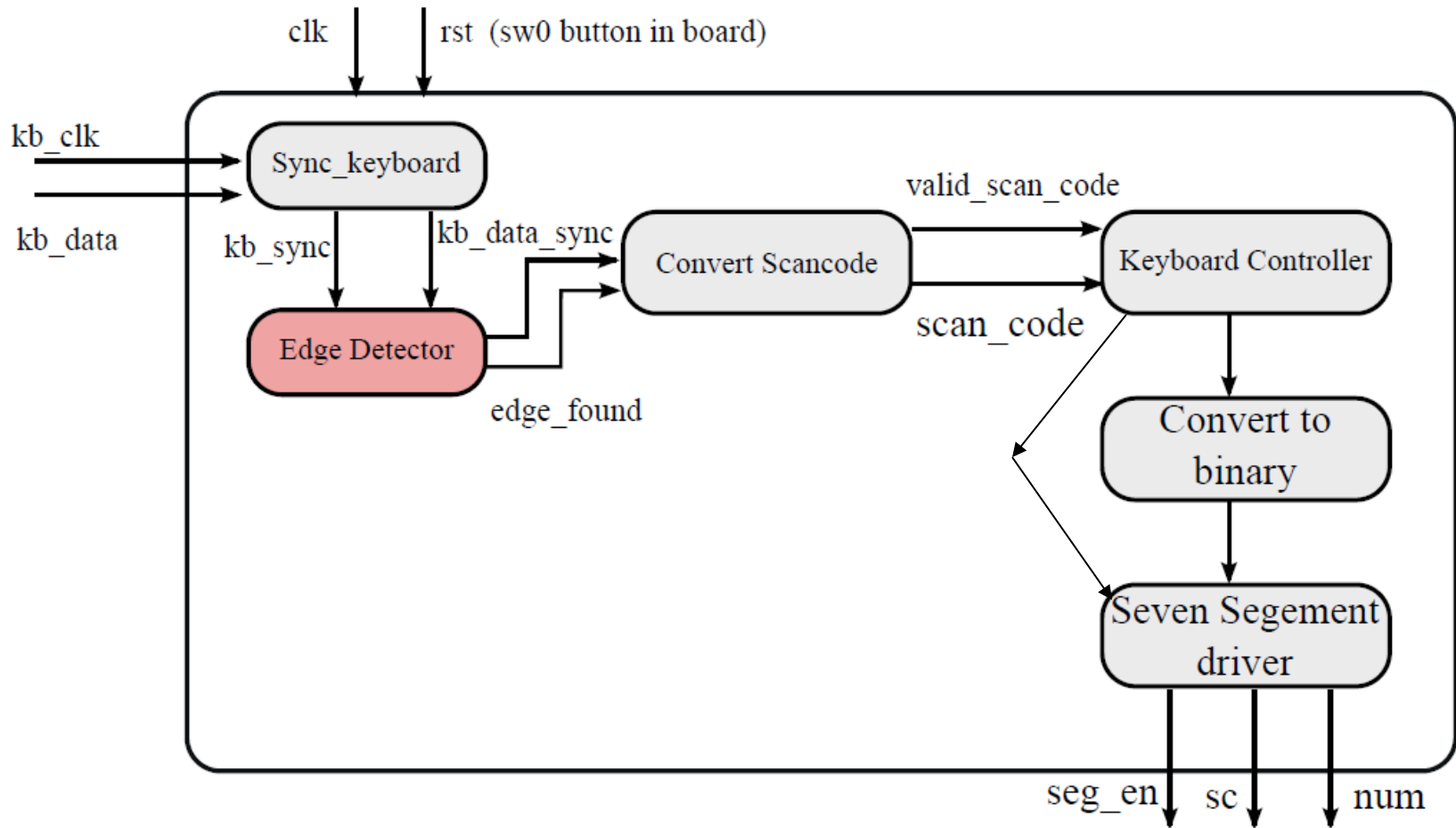


Figure 1: Key Board interface waveform

Tasks

 


Advice

 

- **Build your own test bench for each component and TEST IT!**
- **Work your way through the components, confirm function and continue.**
- **Document your work along, present to the TA.**
- **Bit-shift is a good operation in this lab. Read about it in the book or google it!**
- **NO LATCHES!**

VHDL File Lists

 

File Name

keyboard_top.vhd

sync_keyboard.vhd

edge_detector.vhd

convert_scancode.vhd

keybaord_ctrl.vhd

convert_to_binary.vhd

binary_to_sg.vhd

keyboard_top.xdc

tb_pkg.vhd

tb_keyboard.vhd

input.txt

Function

Top level integration file

Synchronize keyboard data

Edge detection circuit

Convert serial data to parallel

Keyboard controller

Convert scan code to binary

Seven segment driver

Pin mapping to FPGA board.

Required for some functions in testbench

test bench to drive stimulus

Keys to be sent to design via testbench.