

Introduction to Structured VLSI Design

EITF35

LAB 3

Simple ALU

Mojtaba Mahdavi

Mojtaba.Mahdavi@eit.lth.se



Introduction

- ❑ **Arithmetic Logic Unit (ALU)** is the fundamental building block of the CPU in a computer.
 - “Heart” of a processor
 - Each processor needs at least one ALU
- ❑ ALU is a digital circuit that performs:
 - Arithmetic operations (Add, Sub, . . .)
 - Logical operations (AND, OR, NOT)



Objective of Lab3

- ❑ Design a simple ALU to perform the following functions for its inputs (i.e. A, B):
 - Addition: $(A + B)$
 - Subtraction: $(A - B)$
 - Modulo 3: $(A \bmod 3)$

- ❑ It should support:
 - Sign/unsigned operations
 - Overflow detection





Inputs/Outputs of Design

Inputs:

- 8 bits for input operand
DIP Switches (SW7..SW0)
- 3 bits for control signals
Push buttons (BTNL, BTNC, CPU Reset)
- 50 MHz Clock


Outputs:

- 7-segment display

 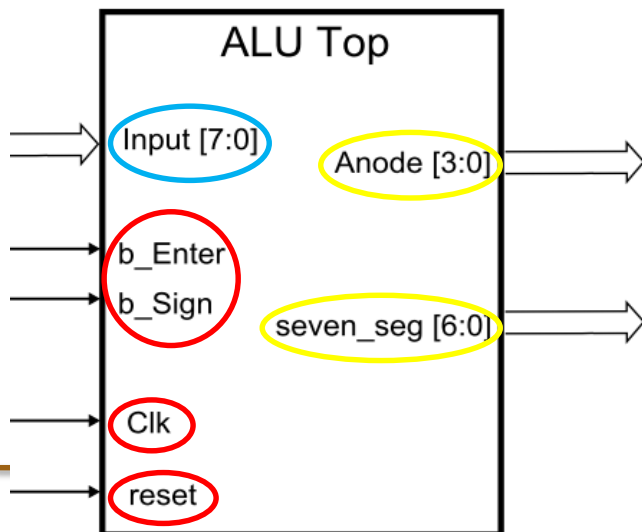


Top Module

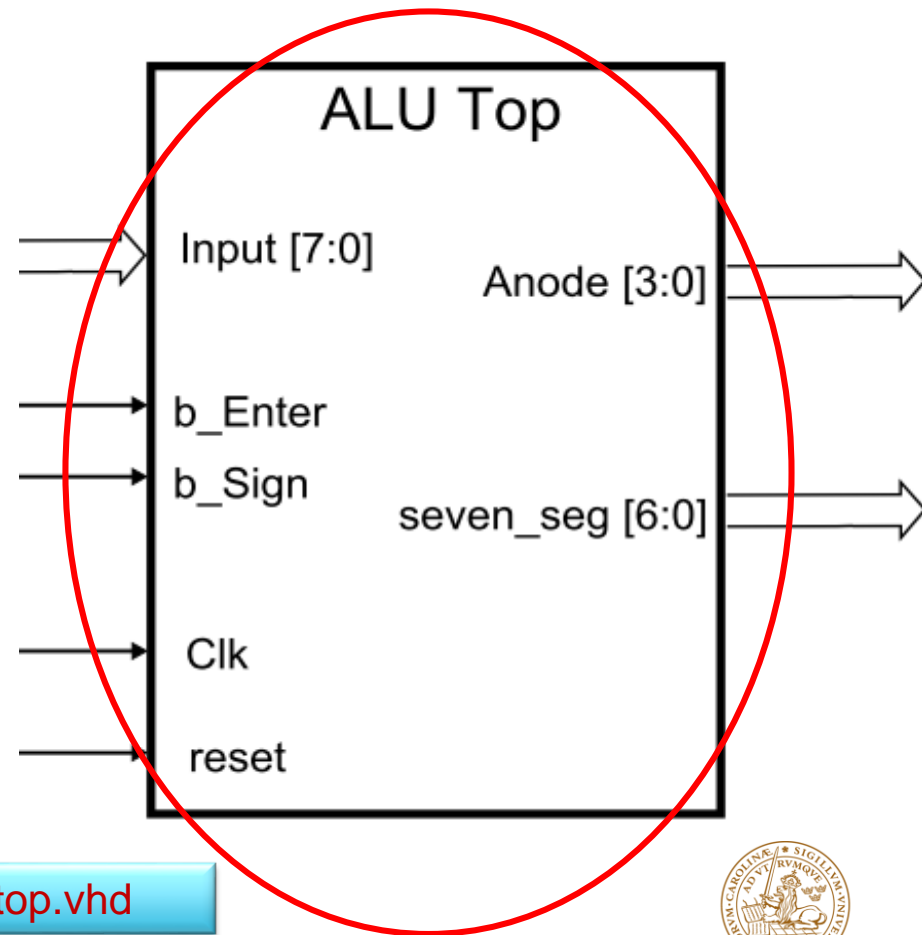- Generate a proper *.xdc* file based on the I/Os.
- Instantiate the *Debouncer* block in the top design.




ALU Architecture

ALU_ctrl.vhd

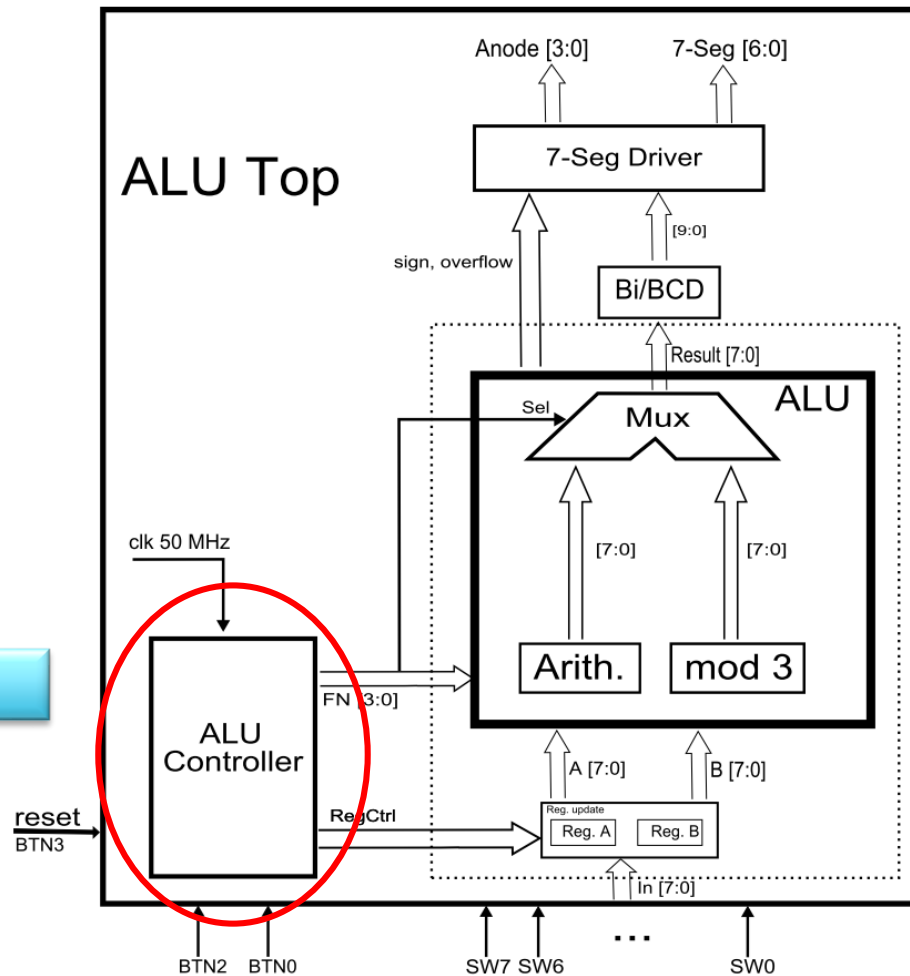


ALU Controller

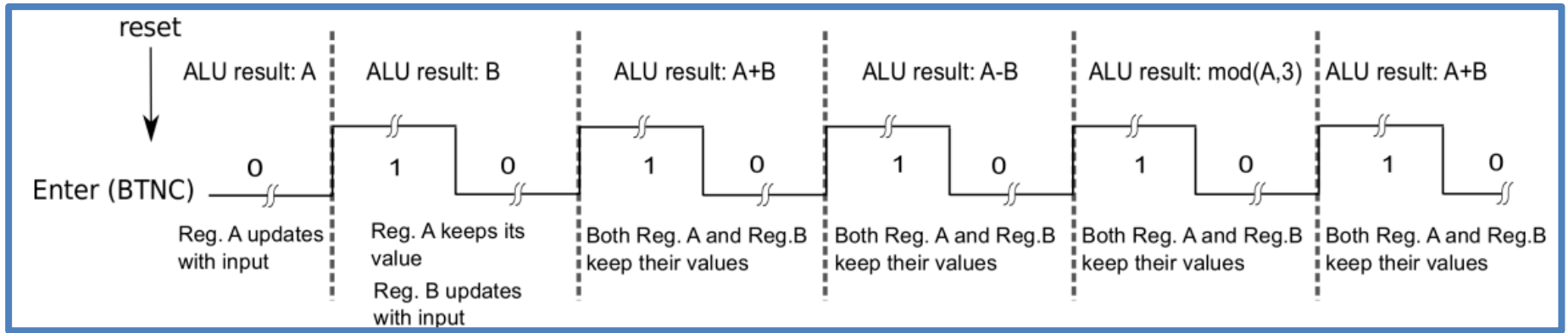

FN [3 : 0]	Operation
0000	Input A
0001	Input B
0010	Unsigned (A + B)
0011	Unsigned (A - B)
0100	Unsigned (A) mod 3
1010	Signed (A + B)
1011	Signed (A - B)
1100	Signed (A) mod 3



ALU Architecture

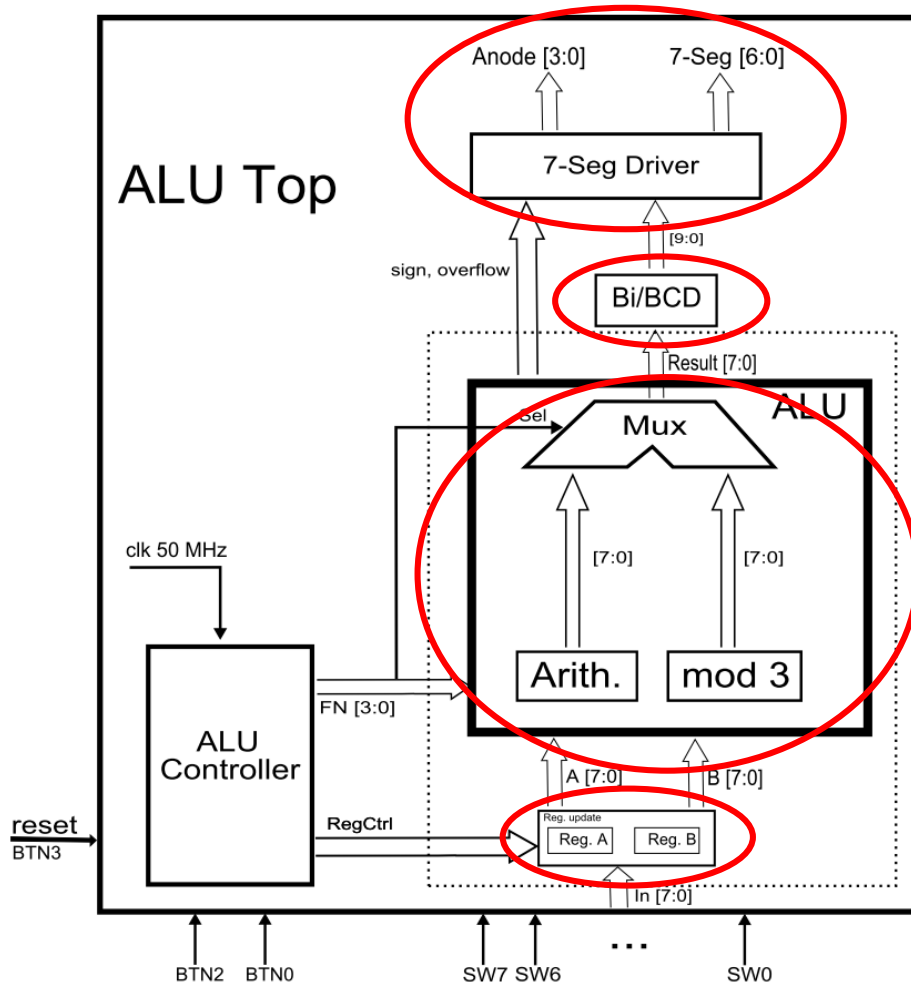

Similar Blocks in Lab 2
`7SegDriver.vhd`

`binary2BCD.vhd`

To do Arithmetic Operations
`ALU.vhd`

Separate Seq. & Comb. Logic
`regUpdate.vhd`



Lab Preparation

- Read the lab manual carefully to understand all the details.
- Read the checklist file and prepare the requirements of Lab 3.
- Read the *Modulo3.pdf* paper to design the modulo 3 operation.
- Design a hardware-friendly architecture for Binary to BCD conversion.



Some Notes

- Think about each block and its functionality before coding!
- Start early!
- Do the simulation as much as possible for your design and sub blocks.

