




LUND
UNIVERSITY

Introduction to Structured VLSI Design

How to Avoid Latches

MOHAMMAD ATTARI

 

LUND
UNIVERSITY

What is a latch?

- It is a kind of memory
 - An asynchronous storage element
 - Not controlled by the clock
- Why is it bad?
 - Timing issues
 - Race conditions
 - Combinatorial feedback

Example – 1-Bit Comparator

- Let's design a simple 1-bit comparator
- The following code looks innocent enough!

```
entity comp is
    port(A, B : in std_logic;
         AeqB : out std_logic);
end comp;

architecture behavior of comp is
begin
    process (A, B)
    begin
        if A = B then
            AeqB <= '1';
        end if;
    end process;
end behavior;
```

Example – 1-Bit Comparator (Latch)

- Let's design a simple 1-bit comparator
- The following code looks innocent enough!

```
entity comp is
    port(A, B : in std_logic;
         AeqB : out std_logic);
end comp;


architecture behavior of comp is
begin
    process (A, B)
    begin
        if A = B then
            AeqB <= '1';
        end if;
    end process;
end behavior;
```

- But is it?



 
Example – 1-Bit Comparator

- This is what we wanted:
 - A simple combinational logic comparator



 Example – 1-Bit Comparator (Latch)

- This is what we get:
 - A nasty feedback
 - Once the inputs are equal, the output will remain high forever!
 - Can you spot the memory?



Example – 1-Bit Comparator (Latch)

- But why?
 - We forgot to complete the if statement!
 - It implies **AeqB** must keep its old value if **A != B**

```
entity comp is
    port(A, B : in std_logic;
         AeqB : out std_logic);
end comp;
```

```
architecture behavior of comp is
begin
    process (A, B)
    begin
        if A = B then
            AeqB <= '1';
        end if;
    end process;
end behavior;
```

Where is my else?



Example – 1-Bit Comparator (Latch Free)

- How to rectify this?
 - Avoid incomplete conditionals in combinational logic (if, switch, ...)
- This is the correct design:

```
entity comp is
    port(A, B : in std_logic;
         AeqB : out std_logic);
end comp;

architecture behavior of comp is
begin
    process (A, B)
    begin
        if A = B then
            AeqB <= '1';
        else
            AeqB <= '0';
        end if;
    end process;
end behavior;
```

Here is my else clause!



- Yes!

