




LUND
UNIVERSITY

Introduction to Structured VLSI Design

Synthesizable VHDL Coding Styles

MOHAMMAD ATTARI

 

LUND
UNIVERSITY


Two Coding Styles

- There are 2 styles of writing synthesizable VHDL code
 - 1) One-process
 - 2) Two-process
- Which one is better?
- Let's consider two simple examples
 - A flipflop
 - A counter
- Let's do it using both styles
 - For simplicity libraries and reset signal are omitted

 Example 1, Flipflop – One-process Method

```
entity flipflop is
    port (clk : in std_logic;
          D : in std_logic;
          Q : out std_logic);
end flipflop;

architecture behavior of flipflop is
begin
    process (clk)
    begin
        if clk'event and clk = '1' then
            Q <= D;
        end if;
    end process;
end behavior;
```




Example 1, Flipflop – Two-process Method

```
entity flipflop is
    port(clk : in std_logic;
          D : in std_logic;
          Q : out std_logic);
end flipflop;

architecture behavior of flipflop is
    signal Q_next : std_logic;
begin
    process (clk)
    begin
        if clk'event and clk = '1' then
            Q <= Q_next;
        end if;
    end process;

     process (D)
    begin
        Q_next <= D;
    end process;
end behavior;
```



Example 1 Assessment

- Previous codes both synthesize into a flipflop
- But which one is preferred?
- To answer that let's design an up-counter


Example 2, Counter – One-process Method

```
entity up_counter is
    port(clk : in std_logic;
          count_out : out std_logic_vector(7 downto 0));
end up_counter;
```

```
architecture behavior of up_counter is
    signal count : std_logic_vector(7 downto 0);
begin
    process(clk)
    begin
        if clk'event and clk = '1' then
            count <= count + 1;
        end if;
    end process;

    count_out <= count;

end behavior;
```

 

Example 2, Counter – One-process Method

```
entity up_counter is
    port (clk : in std_logic;
          count_out : out std_logic_vector(7 downto 0));
end up_counter;
```


```
architecture behavior of up_counter is
    signal count : std_logic_vector(7 downto 0);
begin
```

```
    process (clk)
    begin
        if clk'event and clk = '1' then
            count <= count + 1;
        end if;
    end process;
```

```
    count_out <= count;
```

```
end behavior;
```

Combinational & sequential
are mixed

 


Example 2, Counter – Two-process Method

```
entity up_counter is
    port (clk : in std_logic;
          count_out : out std_logic_vector(7 downto 0));
end up_counter;
```

```
architecture behavior of up_counter is
    signal count_next, count : std_logic_vector(7 downto 0);
begin
    process (clk)
    begin
        if clk'event and clk = '1' then
            count <= count_next;
        end if;
    end process;

    process (count)
    begin
        count_next <= count + 1;
    end process;

    count_out <= count;
end behavior;
```

 


Example 2, Counter – Two-process Method

```
entity up_counter is
    port (clk : in std_logic;
          count_out : out std_logic_vector(7 downto 0));
end up_counter;
```

```
architecture behavior of up_counter is
    signal count_next, count : std_logic_vector(7 downto 0);
begin
    process (clk)
    begin
        if clk'event and clk = '1' then
            count <= count_next;
        end if;
    end process;
```

```
    process (count)
    begin
        count_next <= count + 1;
    end process;
```
 
```
    count_out <= count;
end behavior;
```



Example 2, Counter – Two-process Method

```
entity up_counter is
    port (clk : in std_logic;
          count_out : out std_logic_vector(7 downto 0));
end up_counter;
```


```
architecture behavior of up_counter is
    signal count_next, count : std_logic_vector(7 downto 0);
begin
```

```
    process (clk)
    begin
        if clk'event and clk = '1' then
            count <= count_next;
        end if;
    end process;
```

```
    process (count)
    begin
        count_next <= count + 1;
    end process;
```

```
    count_out <= count;
```

```
end behavior;
```

 


Assessment

- One-process style
 - Fewer lines of code
 - Less descriptive
- Two-process style
 - More verbose
 - Less susceptible to errors
 - Better modularity

Assessment

 - One-process style
 - Fewer lines of code
 - Less descriptive
- Two-process style
 - More verbose 🙄
 - Less susceptible to errors 😁
 - Better modularity 😁



You must use this
one in the course