



VHDL Examples



Example 1

Odd Parity Generator

--- This module has two inputs, one output and one process.
--- The clock input and the input_stream are the two inputs. Whenever the clock
--- goes high then there is a loop which checks for the odd parity by using
--- the xor logic. There is package anu which is used to declare the port
--- input_stream. One can change the value of m where it is declared as constant
--- and the input array can vary accordingly.

package anu **is**
constant m: **integer** :=8;
type input **is** array (0 to m-1) **of** bit;
end anu;

library ieee;
use ieee.std_logic_1164.all ;
use Work.anu.all;

entity Parity_Generator1 **is**
 port (input_stream : **in** input;
 clk : **in** std_logic ;
 parity :**out** bit);
end Parity_Generator1;



Example 1

Odd Parity Generator (cont'd)

```
architecture odd of Parity_Generator1 is
```

```
begin
```

```
    P1: process
```

```
        variable odd : bit ;
```

```
        begin
```

```
            wait until clk'event and clk = '1';  
            odd := '0';
```

```
                for l in 0 to m-1 loop
```

```
                    odd := odd xor input_stream (l);
```

```
                end loop;
```

```
                parity <= odd;
```

```
        end process;
```

```
end odd;
```



Example 1

Odd Parity Generator - Testbench

--- This structural code instantiate the ODD_PARITY_TB module to create a
--- testbench for the odd_parity_TB design. The processes in it are the ones
--- that create the clock and the input_stream. Explore the design in the
--- debugger by either adding to the testbench to provide stimulus for the
--- design or use assign statements in the simulator. If you want to change the
--- array width you will have to modify the a3.vhd code too by changing the
--- value of m.

```
-----  
entity ODD_PARITY_TB is  
end;  
library ieee;  
use ieee.std_logic_1164.all;  
use WORK.anu.all;
```

```
architecture OP_TB_ARCH of ODD_PARITY_TB is
```

```
component Parity_Generator1  
    port (input_stream : in input;  
          clk : in std_logic;  
          parity : out bit );  
end component;
```



Example 1

Odd Parity Generator – Testbench (cont'd)

```
signal input_stream : input;
signal clk :std_logic;
signal parity :bit ;
begin
U1: Parity_Generator1
    port map(
        input_stream,
        clk,
        parity => parity
    );

input1 : process (clk)

begin
    if clk <= 'U' then clk <= '0' after 1 ns;
    else clk <= not clk after 1 ns;
    end if;
end process;
```



Example 1

Odd Parity Generator – Testbench (cont'd)

```
input2: process (input_stream)
begin
    input_stream <= "10100110" after 1 ns,
                  "01111100" after 2 ns;
end process;
end OP_TB_ARCH;

configuration cfg_op of ODD_PARITY_TB is
for OP_TB_ARCH
end for;
end cfg_op;
```



Example 2

Pulse Generator

```
library IEEE;
use IEEE.std_logic_1164.all;

entity P_GENERATOR is
    port ( CLK      : in std_ulogic;
          RESET    : in std_ulogic;
          TRIG     : in std_ulogic;
          PULSE    : out std_ulogic);
end P_GENERATOR;

architecture STATE_MACHINE of P_GENERATOR is

    type PULSEGEN_STATE_TYPE is (IDLE, GEN_PULSE_A, GEN_PULSE_B,
                                END_PULSE, RETRIGGER); -- enumeration type
                                                    -- declaration.

    signal CURRENT_STATE, NEXT_STATE: PULSEGEN_STATE_TYPE;

    signal          COUNT : integer range 0 to 31;
    constant WIDTH : integer range 0 to 31 := 4;
```



Example 2

Pulse Generator (cont'd)

begin

STATE_MACH_PROC : **process** (CURRENT_STATE, TRIG, COUNT) -- sensitivity list.

begin

```
    case CURRENT_STATE is                -- case-when statement specifies the following set of
                                           -- statements to execute based on the value of
                                           -- CURRENT_SIGNAL
    when IDLE          =>                    if TRIG='1' then
                                           NEXT_STATE <= GEN_PULSE_A;
                                           end if;
    when GEN_PULSE_A =>                    if COUNT = WIDTH then
                                           NEXT_STATE <= END_PULSE;
                                           elsif TRIG='0' then
                                           NEXT_STATE <= GEN_PULSE_B;
                                           end if;
    when END_PULSE    =>                    if TRIG ='1' then
                                           NEXT_STATE <= IDLE;
                                           end if;
```




Example 2

Pulse Generator (cont'd)

```
when GEN_PULSE_B => if TRIG = '1' then
                                NEXT_STATE <= RETRIGGER;
                                elsif COUNT=WIDTH then
                                    NEXT_STATE <= IDLE;
                                end if;
when RETRIGGER => NEXT_STATE <= GEN_PULSE_A;
when OTHERS => NEXT_STATE <= NEXT_STATE;
end case;
end process STATE_MACH_PROC;
```



Example 2

Pulse Generator (cont'd)

```
PULSE_PROC : process (CLK, RESET)                                -- sensitivity list
```

```
begin
```

```
if RESET = '1' then
```

```
    PULSE          <= '0';  
    COUNT          <= 0;  
    CURRENT_STATE <= IDLE;
```

```
elsif (clk='1' and clk'event) then -- clk'event is event attribute of clk to  
                                        -- determine if a clock has transitioned
```

```
    CURRENT_STATE <= NEXT_STATE;
```

```
    case NEXT_STATE is
```

```
        when IDLE          => PULSE <= '0';  
                                COUNT <= 0;
```

```
        when GEN_PULSE_A  => PULSE <= '1';  
                                COUNT <= COUNT + 1;
```



Example 2

Pulse Generator (cont'd)

```
when END_PULSE          => PULSE <= '0';  
                        COUNT <= 0;  
  
when GEN_PULSE_B       => PULSE <= '1';  
                        COUNT <= COUNT + 1;  
  
when RETRIGGER         => COUNT <= 0;  
  
when OTHERS           => COUNT <= COUNT;  
  
    end case;  
end if;  
end process PULSE_PROC;  
  
end STATE_MACHINE;
```



Example 2

Pulse Generator - Testbench

```
entity STATE_MACHINE_TB is  
end STATE_MACHINE_TB;
```

```
library IEEE;  
use IEEE.std_logic_1164.all;
```

```
architecture ARC_STATE_MACHINE_TB of STATE_MACHINE_TB is
```

```
component P_GENERATOR
```

```
port (  
    CLK    : in std_ulogic;  
    RESET  : in std_ulogic;  
    TRIG   : in std_ulogic;  
    PULSE  : out std_ulogic);
```

```
end component;
```

```
signal          CLK    : std_ulogic;  
signal    RESET  : std_ulogic;  
signal    TRIG   : std_ulogic;  
signal          PULSE : std_ulogic;
```



Example 2

Pulse Generator – Testbench (cont'd)

```
begin
```

```
U1: P_GENERATOR
```

```
port map( CLK, RESET, TRIG, PULSE);
```

```
CREATE_CLOCK: process (clk)
```

```
begin
```

```
    if clk <= 'U' then clk <= '0' after 1 ns;
```

```
        else clk <= not clk after 1 ns;
```

```
    end if;
```

```
end process CREATE_CLOCK;
```

```
CREATE_PULSE: process (TRIG)
```

```
begin
```

```
    TRIG <= '0' after 10 ns,
```

```
        '1' after 15 ns,
```

```
        '0' after 20 ns;
```



Example 2

Pulse Generator – Testbench (cont'd)

```
end process CREATE_PULSE;
```

```
end ARC_STATE_MACHINE_TB;
```

```
configuration CFG_STATE_MACHINE of STATE_MACHINE_TB is
```

```
    for ARC_STATE_MACHINE_TB  
    end for;
```

```
end CFG_STATE_MACHINE;
```



Example 3

Priority Encoder

```
entity priority is
  port (I :          in bit_vector(7 downto 0);    --inputs to be prioritised
        A :          out bit_vector(2 downto 0);  --encoded output
        GS :         out bit);                  --group signal output
end priority;
```

```
architecture v1 of priority is
begin
  process (I)
  begin
    GS <= '1'; --set default outputs
    A <= "000";
    if I(7) = '1' then
      A <= "111";
    elsif I(6) = '1' then
      A <= "110";
    end if;
  end process;
end architecture v1;
```



Example 3

Priority Encoder (cont'd)

```
    elsif I(5) = '1' then
        A <= "101";
    elsif I(4) = '1' then
        A <= "100";
    elsif I(3) = '1' then
        A <= "011";
    elsif I(2) = '1' then
        A <= "010";
    elsif I(1) = '1' then
        A <= "001";
    elsif I(0) = '1' then
        A <= "000";
    else
        GS <= '0';
    end if;
end process;
end v1;
```




Example 4

Behavioral Model for 16 word, 8 bit RAM

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY ram16x8 IS
    PORT (address :          IN STD_LOGIC_VECTOR(3 DOWNTO 0);
          csbar, oebar, webar : IN STD_LOGIC;
          data :            INOUT STD_LOGIC_VECTOR(7 DOWNTO 0));
END ram16x8;

ARCHITECTURE version1 OF ram16x8 IS
    BEGIN
        PROCESS (address, csbar, oebar, webar, data)
            TYPE ram_array IS ARRAY (0 TO 15) OF BIT_VECTOR(7 DOWNTO 0);
            VARIABLE index : INTEGER := 0;
            VARIABLE ram_store : ram_array;

            BEGIN
                IF csbar = '0' THEN
```



Example 4

Behavioral Model for 16 word, 8 bit RAM (cont'd)

```
--calculate address as an integer
    index := 0;
    FOR i IN address'RANGE LOOP
        IF address(i) = '1' THEN
            index := index + 2**i;
        END IF;
    END LOOP;
IF rising_edge(webar) THEN
    --write to ram on rising edge of write pulse
    ram_store(index) := To_bitvector(data);
ELSIF oebar = '0' THEN
    data <= To_StdlogicVector(ram_store(index));
ELSE
    data <= "ZZZZZZZZ";
END IF;
ELSE
    data <= "ZZZZZZZZ";
END IF;
END PROCESS;
END version1;
```



Example 5

Incrementer - entity

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity incrementer is
  generic (width : integer := 8);
  port ( datain: in std_logic_vector(width-1 downto 0);
        control: in std_logic;
        dataout: out std_logic_vector(width-1 downto 0);
        flag: out std_logic);
end incrementer;
```



Example 5

Incrementer - architecture

architecture behv **of** incrementer **is**

signal dataout_int: std_logic_vector (width-1 downto 0);
begin

process (datain, control)
begin

if (control = '1') **then** -- increment
 dataout_int <= datain + '1';
else -- feedthrough
 dataout_int <= datain;
end if;

end process;

dataout <= dataout_int;

flag <= '1' when (control = '1' and datain = To_std_logic_vector(X"FF")) else '0';

end behv;



Example 5

Incrementer - Testbench

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
use IEEE.std_logic_arith.all;

entity tb_inc is
    generic (width : integer := 8);
end tb_inc;

architecture behv of tb_inc is

    -- define the internal signal which are connected to the UUT

    signal datain: std_logic_vector(width-1 downto 0);
    signal control: std_logic;
    signal dataout: std_logic_vector(width-1 downto 0);
    signal flag: std_logic;
```



Example 5

Incrementer – Testbench (cont'd)

-- component declaration : required to define the interface of

-- the instantiated component

component incrementer

generic (width : **integer**);

port (datain: **in** std_logic_vector(width-1 downto 0);

 control: **in** std_logic;

 dataout: **out** std_logic_vector(width-1 downto 0);

 flag: **out** std_logic);

end component;

begin

-- Process statement providing stimuli to UUT

P1: **process**

begin

wait for 2 ns;

 control <= '1'; -- increment mode

 loop1_260: **for** i **in** 0 to 259 **loop**

 datain <= conv_std_logic_vector(i, width);

wait for 10 ns;



Example 5

Incrementer – Testbench (cont'd)

```
end loop;
```

```
control <= '0'; -- feedthrough mode
```

```
loop2_260: for i in 0 to 259 loop
```

```
    datain <= conv_std_logic_vector(i, width);
```

```
    wait for 10 ns;
```

```
end loop;
```

```
end process;
```

----- Instantiating the component for testing

```
I1: incrementer generic map (width => width)
```

```
    port map (datain => datain, control => control, dataout => dataout, flag => flag);
```

```
end behv;
```



Example 5

Incrementer – Testbench (cont'd)

-- Configuration declaration to bind component declaration to entity-architecture

configuration CFG_top of tb_inc is

for behv

for I1: incrementer **use entity work**.incrementer(behv);

end for;

end for;

end CFG_top;



Example 6

Barrel Shifter - entity

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity bs_vhdl is

port (
    datain: in std_logic_vector(31 downto 0);
    direction: in std_logic;
    rotation : in std_logic;
    count: in std_logic_vector(4 downto 0);
    dataout: out std_logic_vector(31 downto 0));
end bs_vhdl;
```



Example 6

Barrel Shifter - architecture

architecture behv of bs_vhdl is

-- SHIFT LEFT/RIGHT FUNCTION

```
function barrel_shift(din: in std_logic_vector(31 downto 0);  
dir: in std_logic;  
cnt: in std_logic_vector(4 downto 0)) return std_logic_vector is  
begin  
  
  if (dir = '1') then  
    return std_logic_vector((SHR(unsigned(din), unsigned(cnt))));  
  else  
    return std_logic_vector((SHL(unsigned(din), unsigned(cnt))));  
  end if;  
end barrel_shift;
```



Example 6

Barrel Shifter – architecture (cont'd)

-- ROTATE LEFT/RIGHT FUNCTION

```
function barrel_rotate(din: in std_logic_vector(31 downto 0);  
dir: in std_logic;  
cnt: in std_logic_vector(4 downto 0)) return std_logic_vector is  
variable temp1, temp2: std_logic_vector(63 downto 0);
```

```
begin
```

```
case dir is
```

```
when '1' => -- rotate right cnt times
```

```
temp1 := din & din;
```

```
temp2 := std_logic_vector(SHR(unsigned(temp1),unsigned(cnt)));
```

```
return temp2(31 downto 0);
```



Example 6

Barrel Shifter – architecture (cont'd)

```
when others => -- rotate left cnt times  
temp1 := din & din;  
temp2 := std_logic_vector(SHL(unsigned(temp1),unsigned(cnt)));  
return temp2(63 downto 32);  
end case;
```

```
end barrel_rotate;
```

```
begin
```

```
P1: process (datain, direction, rotation, count)
```

```
begin
```

```
if (rotation = '0') then -- shift only
```

```
    dataout <= barrel_shift(datain, direction, count);
```

```
else -- rotate only
```

```
    dataout <= barrel_rotate(datain, direction, count);
```

```
end if;
```

```
end process;
```

```
end behv;
```



Example 6

Barrel Shifter – Testbench

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity tb_bs is
end tb_bs;

architecture behv of tb_bs is

-- Instantiating the UUT

component bs_vhdl
port (      datain: in std_logic_vector(31 downto 0);
        direction: in std_logic;
        rotation : in std_logic;
        count: in std_logic_vector(4 downto 0);
        dataout: out std_logic_vector(31 downto 0));
end component;
```



Example 6

Barrel Shifter – Testbench (cont'd)

-- Defining the signals connected to the UUT

```
signal datain: std_logic_vector(31 downto 0);  
signal direction: std_logic;  
signal rotation : std_logic;  
signal count: std_logic_vector(4 downto 0);  
signal dataout: std_logic_vector(31 downto 0);
```

begin

-- Instantiating the UUT

```
I1: bs_vhdl port map (datain => datain,  
direction => direction,  
rotation => rotation,  
count => count,  
dataout => dataout);
```



Example 6

Barrel Shifter – Testbench (cont'd)

-- Applying Stimuli

```
P1: process  
begin
```

```
wait for 2 ns;  
rotation <= '0'; -- shift mode  
datain <= To_std_logic_vector(X"AAAAAAAA");  
direction <= '0'; -- LEFT  
loop1: for i in 0 to 31 loop  
count <= conv_std_logic_vector(i, 5);  
wait for 10 ns;  
end loop;
```



Example 6

Barrel Shifter – Testbench (cont'd)

```
direction <= '1'; -- RIGHT
loop3: for i in 0 to 31 loop
count <= conv_std_logic_vector(i, 5);
wait for 10 ns;
end loop;
```

```
direction <= '1'; -- RIGHT
rotation <= '1'; -- barrel shift
datain <= To_std_logic_vector(X"55555555");
loop2: for i in 0 to 31 loop
count <= conv_std_logic_vector(i, 5);
wait for 10 ns;
end loop;
```

```
direction <= '0'; -- LEFT
loop4: for i in 0 to 31 loop
count <= conv_std_logic_vector(i, 5);
wait for 10 ns;
end loop;
```




Example 6

Barrel Shifter – Testbench (cont'd)

```
end process;  
end behv;
```

```
-- TOP LEVEL CONFIGURATION DECLARATION
```

```
configuration CFG_top of tb_bs is  
for behv  
for I1: bs_vhdl use entity work.bs_vhdl(behv);  
end for;  
end for;  
end CFG_top;
```



Example 7

BCD to 7-Seg Decoder – entity

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity DISPLAY_DECODER is
    port ( VALUE           : in bit_vector(3 downto 0); -- Bit 3 is MSB
          ZERO_BLANK      : in bit;
          DISPLAY          : out bit_vector(6 downto 0); -- 7 bit signal
          ZERO_BLANK_OUT  : out bit);
end DISPLAY_DECODER;
```



Example 7

BCD to 7-Seg Decoder – architecture

architecture BEHAVIOUR of DISPLAY_DECODER is

begin

process (VALUE, ZERO_BLANK) -- sensitivity list

begin

case VALUE is

-- case-when statement described how decode is

-- driven based on the value of the input.

when "0000" =>

if ZERO_BLANK='1' then

 DISPLAY <= "0000000";

 ZERO_BLANK_OUT <= '1';

else

 DISPLAY <= "1111110";

end if;

when "0001" =>

DISPLAY <= "0110000";

when "0010" =>

DISPLAY <= "1101101";



Example 7

BCD to 7-Seg Decoder – architecture (cont'd)

```
when "0011"    =>    DISPLAY <= "1111001";
when "0100"    =>    DISPLAY <= "0110011";
when "0101"    =>    DISPLAY <= "1011011";
when "0110"    =>    DISPLAY <= "1011111";
when "0111"    =>    DISPLAY <= "1110000";
when "1000"    =>    DISPLAY <= "1111111";
when OTHERS    =>    DISPLAY <= "1001111"; -- when others, an error
-- is specified
```

```
end case;
end process;
end BEHAVIOUR;
```



Example 7

BCD to 7-Seg Decoder – Testbench (cont'd)

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity DISPLAY_DECODER_TB is
end DISPLAY_DECODER_TB;

architecture ARC_DISPLAY_DECODER_TB of DISPLAY_DECODER_TB is

    signal          VALUE          : bit_vector(3 downto 0);
    signal ZERO_BLANK    : bit;
    signal DISPLAY      : bit_vector(6 downto 0);
    signal ZERO_BLANK_OUT : bit;

    component DISPLAY_DECODER
        port ( VALUE          : in bit_vector(3 downto 0);
              ZERO_BLANK    : in bit;
              DISPLAY        : out bit_vector(6 downto 0);
              ZERO_BLANK_OUT : out bit);
    end component;
```



Example 7

BCD to 7-Seg Decoder – Testbench (cont'd)

begin

INPUT_VALUES: **process**

begin

```
ZERO_BLANK    <= '1';  
VALUE         <= "0000";
```

wait for 5 ns;

```
ZERO_BLANK    <= '0';  
VALUE         <= "0000";
```

wait for 7 ns;

```
ZERO_BLANK    <= '1';  
VALUE         <= "0010";
```

wait for 12 ns;



Example 7

BCD to 7-Seg Decoder – Testbench (cont'd)

```
ZERO_BLANK    <= '0';  
  VALUE                                <= "0100";  
  
  wait for 12 ns;  
  
  ZERO_BLANK    <= '0';  
  VALUE                                <= "0110";  
  
  wait for 7 ns;  
  
end process INPUT_VALUES;  
  
U1: DISPLAY_DECODER  
  port map(VALUE, ZERO_BLANK, DISPLAY, ZERO_BLANK_OUT);  
  
end ARC_DISPLAY_DECODER_TB;
```



Example 7

BCD to 7-Seg Decoder – Testbench (cont'd)

configuration CFG_DISPLAY_DECODER **of** DISPLAY_DECODER_TB **is**

for ARC_DISPLAY_DECODER_TB

for U1:DISPLAY_DECODER **use entity**

work.DISPLAY_DECODER(BEHAVIOUR);

end for;

end for;

end CFG_DISPLAY_DECODER;



Example 8

Mealy Machine

```
Library IEEE;
use IEEE.std_logic_1164.all;

entity MEALY is      -- Mealy machine
  port (X, CLOCK: in STD_LOGIC;
        Z: out STD_LOGIC);
end;

architecture BEHAVIOR of MEALY is
  type STATE_TYPE is (S0, S1, S2, S3);
  signal CURRENT_STATE, NEXT_STATE: STATE_TYPE;
begin
```



Example 8

Mealy Machine (cont'd)

```
-- Process to hold combinational logic.  
COMBIN: process (CURRENT_STATE, X)  
begin  
  case CURRENT_STATE is  
    when S0 =>  
      if X = '0' then  
        Z <= '0';  
        NEXT_STATE <= S0;  
      elsif X = '1' then  
        Z <= '1';  
        NEXT_STATE <= S2;  
      else  
        Z <= 'U';  
        NEXT_STATE <= S0;  
      end if;
```



Example 8

Mealy Machine (cont'd)

```
when S1 =>
  if X = '0' then
    Z <= '0';
    NEXT_STATE <= S0;
  elsif X = '1' then
    Z <= '0';
    NEXT_STATE <= S2;
  else
    Z <= 'U';
    NEXT_STATE <= S0;
  end if;
when S2 =>
  if X = '0' then
    Z <= '1';
    NEXT_STATE <= S2;
  elsif X = '1' then
    Z <= '0';
    NEXT_STATE <= S3;
  else
```



Example 8

Mealy Machine (cont'd)

```
Z <= 'U';  
NEXT_STATE <= S0;  
end if;  
when S3 =>  
  if X = '0' then  
    Z <= '0';  
    NEXT_STATE <= S3;  
  elsif X = '1' then  
    Z <= '1';  
    NEXT_STATE <= S1;  
  else  
    Z <= 'U';  
    NEXT_STATE <= S0;  
  end if;  
end case;  
end process;
```



Example 8

Mealy Machine (cont'd)

```
-- Process to hold synchronous elements (flip-flops)
SYNCH: process
begin
    wait until CLOCK'event and CLOCK = '1';
    CURRENT_STATE <= NEXT_STATE;
end process;
end BEHAVIOR;
```



Example 8

Mealy Machine - Testbench

```
Library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity TB_MEALY is
```

```
end;
```

```
architecture TESTBENCH of TB_MEALY is
```

```
    signal CLK : std_logic;
```

```
    signal X   : std_logic;
```

```
    signal Z   : std_logic;
```

```
    component MEALY
```

```
        Port ( X, CLOCK: in STD_LOGIC;
```

```
              Z: out STD_LOGIC
```

```
        );
```

```
    end component;
```



Example 8

Mealy Machine - Testbench (cont'd)

```
begin
    UUT : MEALY
        Port Map (X, CLK, Z);

-- CLOCK STIMULI OF 100 NS TIME PERIOD
    CLOCK: process
        begin
            CLK <= '0', '1' after 50 ns;
                wait for 100 ns;
        end process;

-- X input STIMULI
    X_Stimuli: process
        begin
            X <= '0', '1' after 30 ns,
                'U' after 60 ns;
            wait for 90 ns;
        end process;
```



Example 8

Mealy Machine - Testbench (cont'd)

```
end TESTBENCH;
```

```
configuration CFG_TB_MEALY of TB_MEALY is  
  for TESTBENCH  
    for UUT : MEALY  
      end for;  
    end for;  
end;
```




Example 9

Moore Machine

```
Library IEEE;
use IEEE.std_logic_1164.all;

entity MOORE is          -- Moore machine
  port (X, CLOCK: in STD_LOGIC;
        Z: out STD_LOGIC);
end;

architecture BEHAVIOR of MOORE is
  type STATE_TYPE is (S0, S1, S2, S3);
  signal CURRENT_STATE, NEXT_STATE: STATE_TYPE;
begin

  -- Process to hold combinational logic
  COMBIN: process (CURRENT_STATE, X)
  begin
    case CURRENT_STATE is
```



Example 9

Moore Machine (cont'd)

```
when S0 =>
  Z <= '0';
  if X = '0' then
    NEXT_STATE <= S0;
  else
    NEXT_STATE <= S2;
  end if;
when S1 =>
  Z <= '1';
  if X = '0' then
    NEXT_STATE <= S0;
  else
    NEXT_STATE <= S2;
  end if;
when S2 =>
  Z <= '1';
  if X = '0' then
    NEXT_STATE <= S2;
  else
    NEXT_STATE <= S3;
  end if;
```



Example 9

Moore Machine (cont'd)

```
when S3 =>
  Z <= '0';
  if X = '0' then
    NEXT_STATE <= S3;
  else
    NEXT_STATE <= S1;
  end if;
end case;
end process;

-- Process to hold synchronous elements (flip-flops)
SYNCH: process
begin
  wait until CLOCK'event and CLOCK = '1';
  CURRENT_STATE <= NEXT_STATE;
end process;
end BEHAVIOR;
```



Example 9

Moore Machine - Testbench

```
Library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity TB_MOORE is
```

```
end;
```

```
architecture TESTBENCH of TB_MOORE is
```

```
    signal CLK : std_logic;
```

```
    signal X   : std_logic;
```

```
    signal Z   : std_logic;
```

```
    component MOORE
```

```
        Port (
```

```
            X, CLOCK: in STD_LOGIC;
```

```
            Z: out STD_LOGIC
```

```
        );
```

```
    end component;
```



Example 9

Moore Machine – Testbench (cont'd)

```
procedure check(signal Z : in std_logic;
                constant Expected : in std_logic;
                constant timepoint : in time) is
begin
    assert ( Z /= Expected OR timepoint /= now )
    report "Value on Z is OK"
    severity NOTE;
end;

begin
    UUT : MOORE
        Port Map (X, CLK, Z);

-- CLOCK STIMULI OF 100 NS TIME PERIOD

    CLOCK: process
    begin
        CLK <= '0', '1' after 50 ns;
        wait for 100 ns;
    end process;
```



Example 9

Moore Machine – Testbench (cont'd)

-- X input STIMULI

```
X_Stimuli: process
```

```
begin
```

```
    X <= '1', '0' after 1000 ns;
```

```
    wait for 2000 ns;
```

```
end process;
```

-- Assert Process

```
check(Z,'1', 50 ns);
```

```
check(Z,'0', 150 ns);
```

```
check(Z,'1', 250 ns);
```

```
check(Z,'0', 450 ns);
```

```
end TESTBENCH;
```



Example 9

Moore Machine – Testbench (cont'd)

```
configuration CFG_TB_MOORE of TB_MOORE is  
  for TESTBENCH  
    for UUT : MOORE  
      end for;  
  end for;  
end;
```