



**LUND**  
UNIVERSITY

# EITF35: Introduction to Structured VLSI Design

## Part 1.2.1: Finite State Machines

Liang Liu  
liang.liu@eit.lth.se



# Outline

## □ Why Digital?

- Advantages
- Some applications

## □ History & Roadmap

## □ Device Technology & Platforms

## □ **System Representation**

## □ Design Flow

## □ RTL Basics



# System Representation

## □ System

- SoC: a CPU chip ...

## □ Module

- Macro cell in a chip: ALU...

## □ Gate


- Basic logic block: xor, nor...

## □ Circuit


- Transistors

## □ Device

- Gate, source, drain

 


# View a Design in a Proper Way

 

Intel 4004 (2.3K transistors)

Full-custom


 


Intel Haswell (1.4B transistors)

?
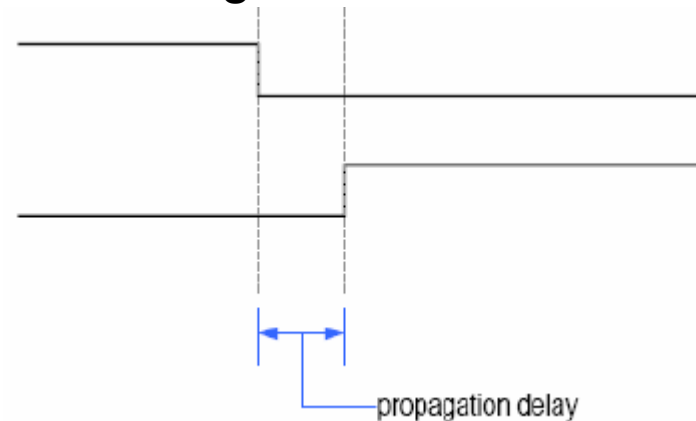 
## □ Abstraction: simplified model of a system


- Show the selected features accurate enough
- Ignore the others



# VLSI Design Flow
 
## □ Evolution of circuit design (Design Hierarchy)


- Full-custom  $\Rightarrow$  Design-automation
  - *Based on library cells and IPs*
  - *Top-down methodology*
- Design abstraction  $\Rightarrow$  “Black box” or “Model”
  - *Parameter simplification*
  - *Accurate enough to meet the requirement*



```
module HS65_GH_NAND2AX14 (Z, A, B);  
    output Z;  
    input A,B;  
    not U1 (INTERNAL1, B) ;  
    or #1 U2 (Z, A, INTERNAL1) ;  
    specify  
        (A ==> Z) = (0.1,0.1);  
        (B ==> Z) = (0.1,0.1);  
    endspecify  
endmodule // HS65_GH_NAND2AX14
```



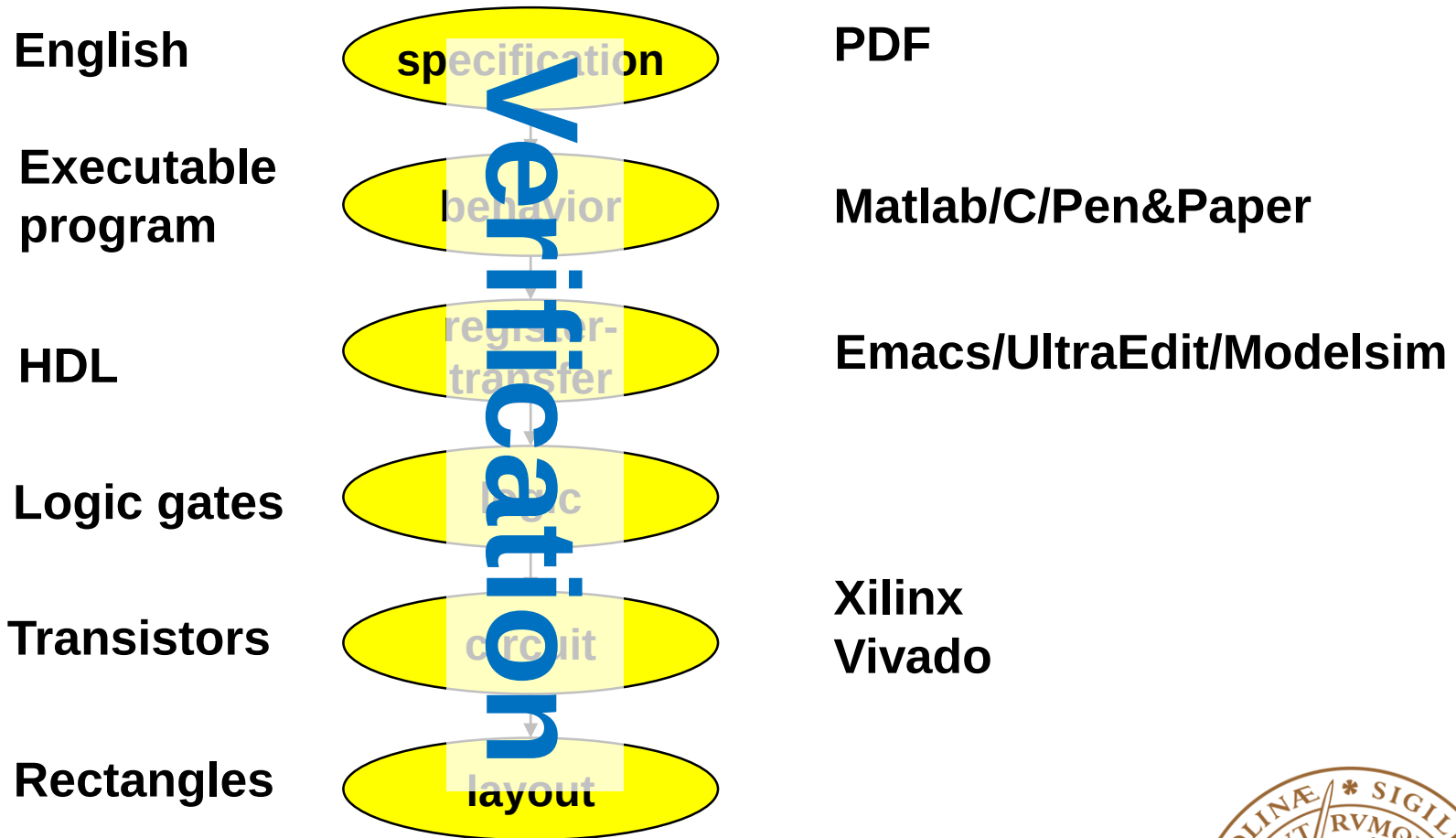
# VLSI Design Flow (This course): Summary



# ***Digital VLSI in 5 min***



# Overall VLSI Structure

 

```
IF (a>10)
    b = c + d;
ELSE
    b = c - d;
```

□ Scheduling / ordering / sequencing of operations

□ Mapping / allocation:

- Variables -> {Reg1, ... ,RegN}
- Operations -> {MUL, ADD, ALU, ... ,}


**We will implement something similar in this course**





# Two Basic Digital Components (What)

## Combinational Logic

 


Always:

$z \leq F(a, b, c);$

i.e. a function that is always evaluated when an input changes.  
Can be expressed by a truth table.

## Register

 

if clk' event and clk= '1' then  
 $Q \leq D;$

i.e. a stored variable,  
Edge triggered D Flip-Flop  
with enable.




# Timing (When)

Only if we guarantee to meet the **timing requirements**


... do the components guarantee to behave as intended.




# Combinational Logic Timing

 

 
- **Propagation delay:**  
After presenting new inputs  
Worst case delay before  
producing correct output



# Register timing

 


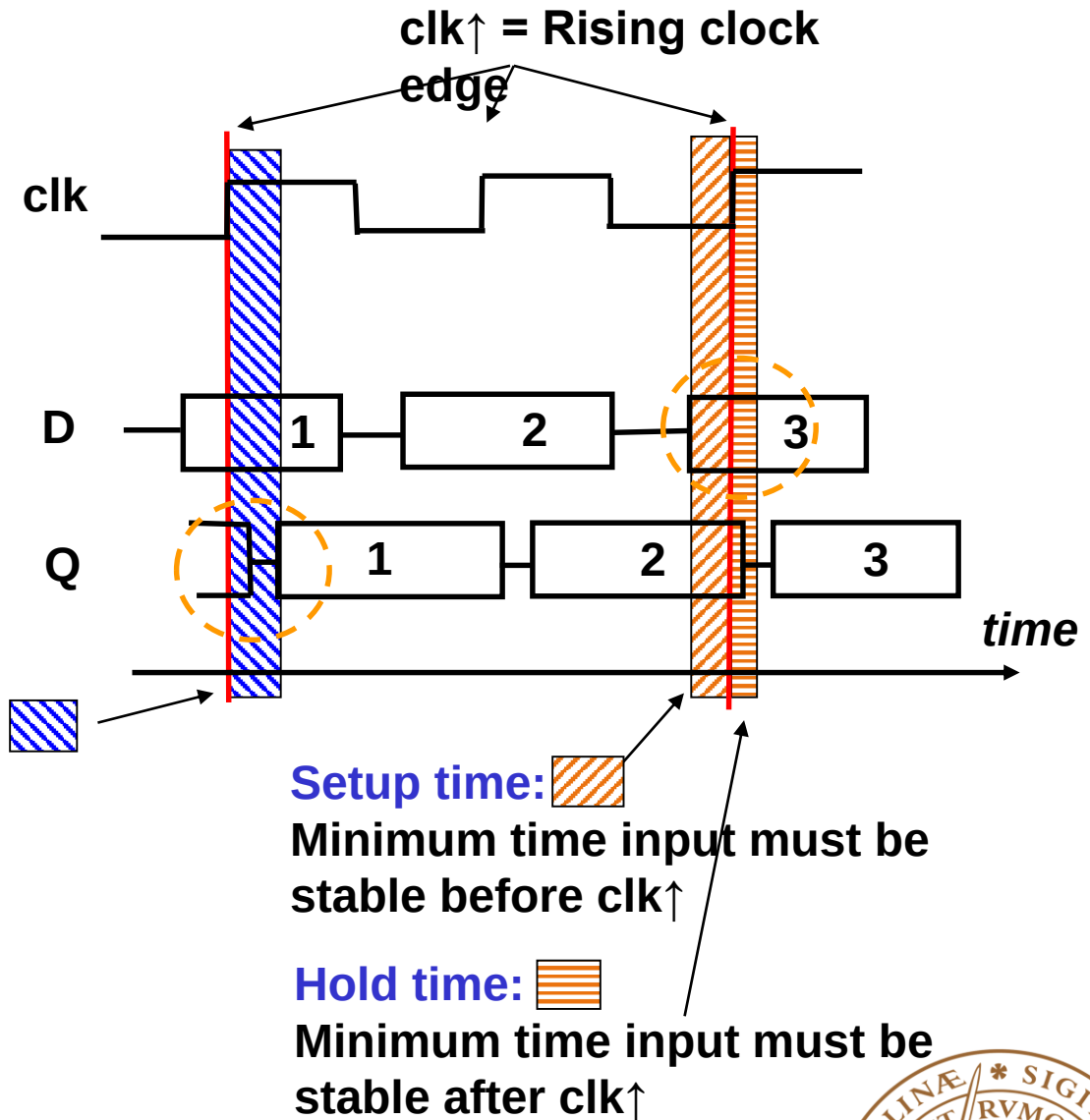**Propagation delay (clk\_to\_Q):**  
Worst case (maximum) delay after  $\text{clk}\uparrow$  before new output data is valid on Q.



# Clock Frequency (RTL)

□ What is the maximum clock frequency?

 

## Register

|                    |                    |       |
|--------------------|--------------------|-------|
| Propagation delay: | T <sub>ckl-Q</sub> | 250ps |
| Setup time:        | T <sub>su</sub>    | 200ps |
| Hold time:         | T <sub>h</sub>     | 100ps |

## AND-gate

|                    |                   |       |
|--------------------|-------------------|-------|
| Propagation delay: | T <sub>prop</sub> | 250ps |
|--------------------|-------------------|-------|

$$250 + 250 \times 3 + 200 = 1.2\text{ns}$$

$$f = 833\text{MHz}$$




# Critical path

- ...begin to explore the construction of digital systems with complex behavior

- Example:  $K = (A +_1 B) *_1 (C +_2 D *_2 E)$

- Combinational circuit:

 

# Outline

## □FSM Overview

## □FSM Representation

- examples


## □Moore vs. Mealy Machine

- from **circuits** perspective


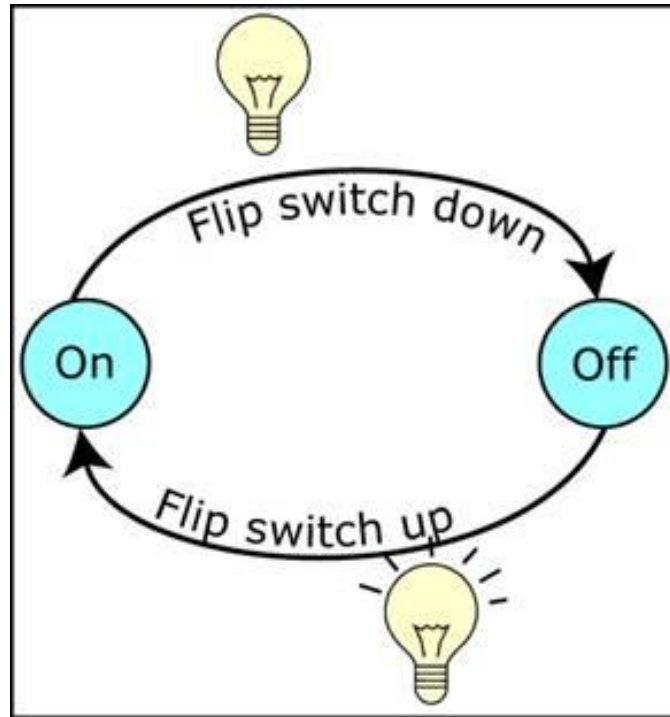
# FSM Overview

- Models for representing **sequential** circuits
- Used mainly as a **controller** in a large system







# How does a controller work in a system?




# Controller

 

# Controller

 


# The model can be used in many places

 

 
# Abstraction of state elements

- A FSM consists of several states. **Inputs** into the machine are combined with the **current state** of the machine to determine the new state or **next state** of the machine.
- Depending on the state of the machine, **outputs** are generated based on either the state or the state and inputs of the machine.


 
# Abstraction of state elements

- A FSM consists of several states. **Inputs** into the machine are combined with the **current state** of the machine to determine the new state or **next state** of the machine.
- Depending on the state of the machine, **outputs** are generated based on either the state or the state and inputs of the machine.
- Divide circuit into **combinational logic** and **state (registers)**



# Outline

- FSM Overview
- **FSM Representation**
- Moore vs. Mealy Outputs
- Exercise



# FSM Representation

- Can be represented using a state transition table which shows the *current state*, *input*, any *outputs*, and the *next state*.

| Current State \ Input | Input               |                    |      |                     |
|-----------------------|---------------------|--------------------|------|---------------------|
|                       | Input <sub>0</sub>  | Input <sub>1</sub> | .... | Input <sub>n</sub>  |
| State <sub>0</sub>    | Next State / Output |                    | .... | Next State / Output |
| State <sub>1</sub>    | ....                | ....               |      | ....                |
| ....                  | ....                | ....               |      | ....                |
| State <sub>n</sub>    | ....                | ....               |      | ....                |





# FSM Representation

- It can also be represented using a *state diagram* which has the same information as the state transition table.

- Mealy Output**


$Outputs = F(Inputs, Current\ state)$

$Next\ state = F(Inputs, Current\ state)$

- Moore Output**

$Outputs = F(Current\ state)$

 $Next\ state = F(Inputs, current\ state)$



# Example 1: A mod-4 synchronous counter

- ❑ **Function**: Counts from 0 to 3 and then repeats; Reset signal reset the counter to 0.
- ❑ It has a clock (*CLK*) and a *RESET* input.
- ❑ **Outputs** appear as a sequence of values of 2 bits (*q1 q0*)
- ❑ As the outputs are generated, a **new state** (*s1 s0*) is generated which takes on values of 00, 01, 10, and 11.



# State Transition Table of Mod-4 Counter

| Present state ( $S_t$ ) \ Input | <i>RESET</i> |       |
|---------------------------------|--------------|-------|
|                                 | 0            | 1     |
| <i>A</i> :00                    | 01/01        | 00/00 |
| <i>B</i> :01                    | 10/10        | 00/00 |
| <i>C</i> :10                    | 11/11        | 00/00 |
| <i>D</i> :11                    | 00/00        | 00/00 |


State  
Next

Output

**Clock?**


 
## State Transition Diagram for the Mod-4 Counter



## Use meaningful names for states



# Outline

- FSM Overview
- FSM Representation
- **Moore vs. Mealy Outputs**
- Exercise



# Mealy and Moore FSM

## A Method for Synthesizing Sequential Circuits

By GEORGE H. MEALY

(Manuscript received May 6, 1955)

*The theoretical basis of sequential circuit synthesis is developed, with particular reference to the work of D. A. Huffman and E. F. Moore. A new method of synthesis is developed which emphasizes formal procedures rather than the more familiar intuitive ones. Familiarity is assumed with the use of switching algebra in the synthesis of combinational circuits.*

### CONTENTS

|                                                             |      |
|-------------------------------------------------------------|------|
| 1. Introduction .....                                       | 1045 |
| 1.1 Foreword .....                                          | 1045 |
| 1.2 Introductory Remarks .....                              | 1046 |
| 2. A Model for Sequential Circuits .....                    | 1049 |
| 2.1 The Model .....                                         | 1049 |
| 2.2 State Diagrams .....                                    | 1051 |
| 3. Circuit Equivalence .....                                | 1053 |
| 3.1 Moore's Theory .....                                    | 1053 |
| 3.2 First Reduction Process .....                           | 1056 |
| 4. Development of the Method for Synchronous Circuits ..... | 1059 |
| 4.1 Introductory Remarks .....                              | 1059 |
| 4.2 Modification of First Reduction Process .....           | 1062 |
| 4.3 Second Reduction Process .....                          | 1063 |
| 4.4 Blank Entries; Uniqueness of Reduction .....            | 1065 |
| 4.5 Final Remarks; Summary of Method .....                  | 1065 |
| 5. The Method Applied to Asynchronous Circuits .....        | 1067 |
| 5.1 Introductory Remarks .....                              | 1067 |
| 5.2 Interpretation of the Model .....                       | 1067 |
| 5.3 Race Conditions; Coding of States .....                 | 1069 |
| 5.4 Huffman's Method .....                                  | 1072 |
| 5.5 Summary of Method .....                                 | 1072 |
| 6. Discussion .....                                         | 1077 |
| 7. Acknowledgements .....                                   | 1078 |
| 8. Selected Bibliography .....                              | 1078 |

### 1. INTRODUCTION

### GEDANKEN-EXPERIMENTS ON SEQUENTIAL MACHINES

Edward F. Moore

### INTRODUCTION

This paper is concerned with finite automata<sup>1</sup> from the experimental point of view. This does not mean that it reports the results of any experimentation on actual physical models, but rather it is concerned with what kinds of conclusions about the internal conditions of a finite machine it is possible to draw from external experiments. To emphasize the conceptual nature of these experiments, the word "gedanken-experiments" has been borrowed from the physicists for the title.

The sequential machines considered have a finite number of states, a finite number of possible input symbols, and a finite number of possible output symbols. The behavior of these machines is strictly deterministic (i.e., no random elements are permitted in the machines) in that the present state of a machine depends only on its previous input and previous state, and the present output depends only on the present state.

The point of view of this paper might also be extended to probabilistic machines (such as the noisy discrete channel of communication theory<sup>2</sup>), but this will not be attempted here.

### EXPERIMENTS


There will be two kinds of experiments considered in this paper. The first of these, called a simple experiment, is depicted in Figure 1.

<sup>1</sup>The term "finite" is used to distinguish these automata from Turing machines [considered in Turing's "On Computable Numbers, with an Application to the Entscheidungsproblem", Proc. Lond. Math. Soc., (1936) Vol. 24, pp. 230-265] which have an infinite tape, permitting them to have more complicated behavior than these automata.

<sup>2</sup>Defined in Shannon's "A Mathematical Theory of Communication", B.S.T.J. Vol. 27, p. 406.




# Output Timing: Moore

 

- ... a Moore machine is not able to produce  $A \rightarrow 1$  until the **next clock** when it enters s1



## Output Timing: Mealy


 


- When in s0, a Mealy machine may produce A->1 **immediately** in response to R->1





# Output Timing: Moore and Mealy

  

# Moore vs. Mealy

□ Detecting a pair of “1s” or “0s” and output “1”

 


Figure 3 State Diagram of Moore Machine

 


Figure 4 State Diagram of Mealy Machine



# Moore vs. Mealy (summary)

- A **Moore** machine produces glitch free outputs
  - Output change at the clock edge only
- A **Moore** machine produces outputs depending only on states, and this may allow using a higher-frequency clock
  - Less gate delay for the output combinational logic
- A **Mealy** machine can be specified using less states
  - Because it is capable of producing different outputs in a given state, (nm) possible outputs v.s. (n)
- A **Mealy** machine can be faster
  - Because an output may be produced immediately instead of at the next clock tick

**Suggestion: do NOT mix Mealy and Moore in one design (before getting experienced)**



?

