



LUND
UNIVERSITY

EITF35: Introduction to Structured VLSI Design

Part 2.1.1: Combinational circuit

Liang Liu
liang.liu@eit.lth.se




Why Called “Combinational” Circuits?

□ Combination

- In mathematics a combination is a way of selecting several things out of a larger group
- Select two fruits out of APPLE, PEAR, and ORANGE
- In a combination the **order** of elements is **irrelevant**

□ Combinational Circuits

 - *time-independent logic*, where the output is a pure function of the present input only.
- the **order** of inputs doesn't matter for the outputs.




Two basic components

□ Operands (Data type)

□ Operations



'Digital'- quantization

 

What does it mean?

00100000010010000110100100100001



What does it mean?

00100000010010000110100100100001


001000	00010	01000	0110100100100001
instruction	source	target	immediate
ADDI	2	8	26913

ADDI R8,R2,26913




Two basic components

□ Operands (Data type)

 

□ Operations

 

□ Check what is in the library!



Data Representation

□ Unsigned

- Unsigned integer: $\sum_{i=0}^{n-1} \text{bit}_i 2^i$

□ Signed (Two's complement)

- The result of **subtracting the number from 2^{N-1}**
- Inverting all bits and **adding 1**

$$\text{bit}_{n-1}(-2^{n-1}) + \sum_{i=0}^{n-2} \text{bit}_i 2^i$$

$$\underline{11110100}_2 = -12_{10}$$

Sign bit **2's complement**



8-bit Signed/Unsigned Integers

Signed integers	Signed overflow ↑		-128	1000 0000	
			-127	1000 0001	
			...	...	
				1111 1100	
				1111 1101	
			-2	1111 1110	
			-1	1111 1111	
			0	0000 0000	0
			1	0000 0001	1
			2	0000 0010	2
			3	0000 0011	3
			...	...	...
			126	0111 1110	126
			127	0111 1111	127
				1000 0000	128
				1000 0001	129
				...	...
				1111 1110	254
				1111 1111	255
		Signed overflow ↓			
					Unsigned integers
					Unsigned overflow ↓





Finite Word-Length Effect

□ Overflow

- Saturation

□ Quantization error

- Round
- Truncation

 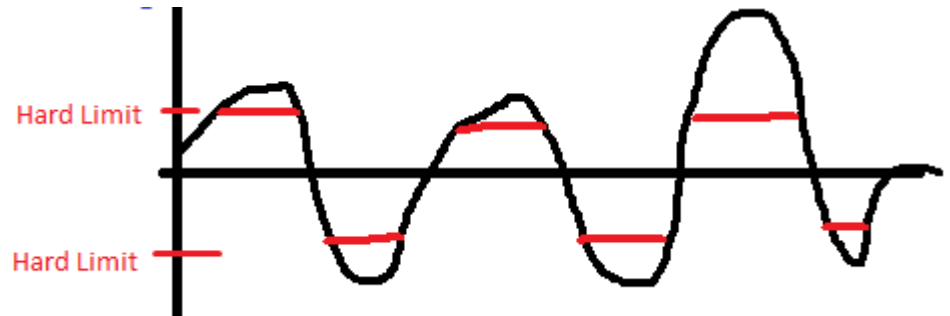

$$\text{round}(0.51)=1$$

$$\text{floor}(0.51)=0$$

$$\text{ceil}(0.49)=1$$

Will learn more in DSP-Design course





Fixed-Point Design

□ DSP algorithms

- Often developed in floating point
- Later mapped into **fixed point** for digital hardware realization


□ Fixed-point digital VLSI

  - Lower area
- Lower power
- Quantization error & small dynamic range




“Optimum” Word-Length

Range Analysis

 


“Optimum” Word-Length

 
- Range Analysis
- Fixed-point Simulation




(a) 12 bit.

 


(b) 13 bit.

 


(c) 14 bit.

 

(d) 15 bit.

 

(e) 16 bit.

 


(f) Single precision floating-point.




Hardware Consumption Analysis


- Complexity analysis
- Quick prototype

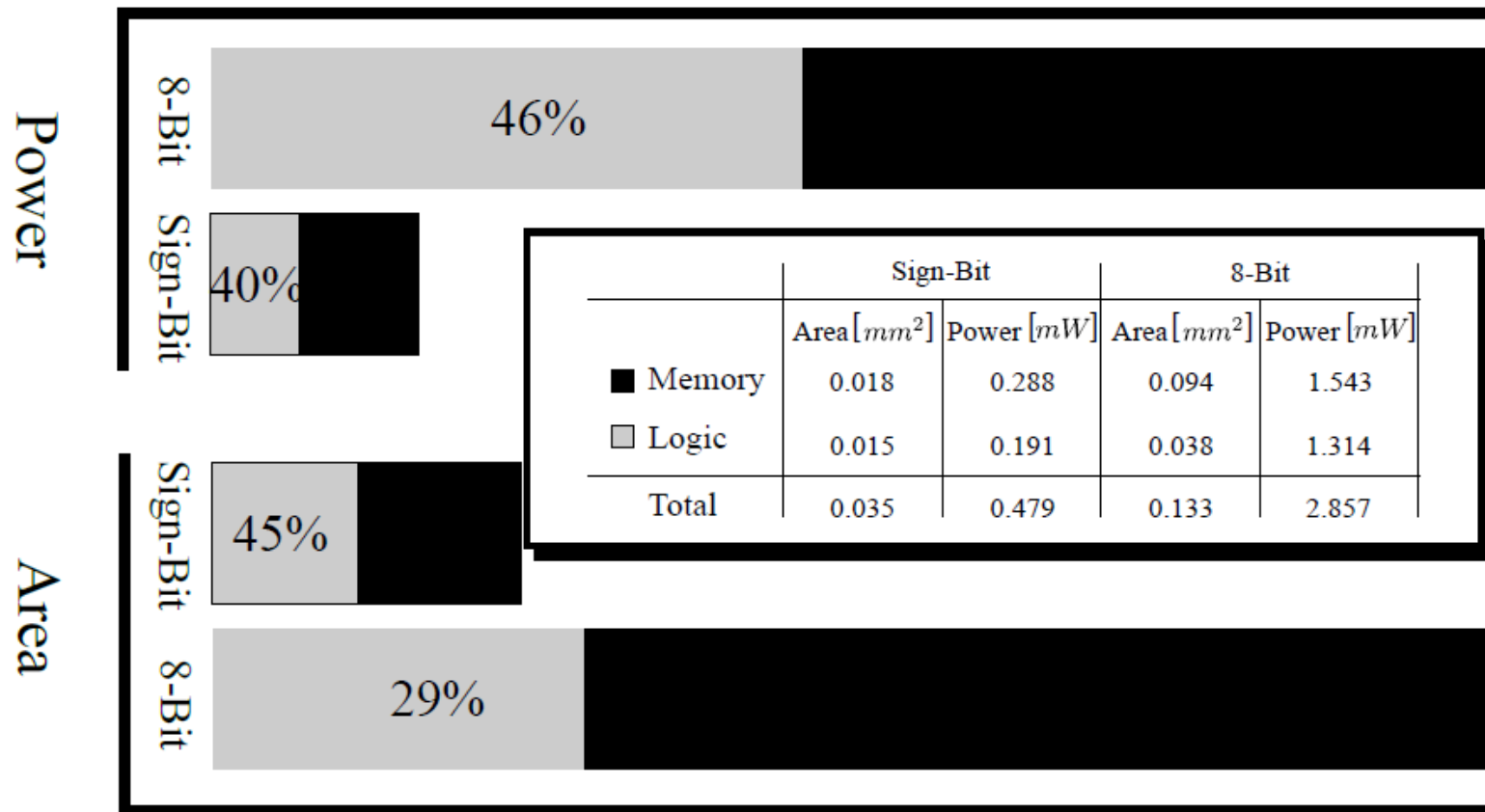

Where is the cost

 

Operation	Energy [pJ]
32 bit int ADD	0.1
32 bit float ADD	0.9
32 bit Register File	1
32 bit int MULT	3.1
32 bit float MULT	3.7
32 bit SRAM Cache	5
32 bit DRAM Memory	640

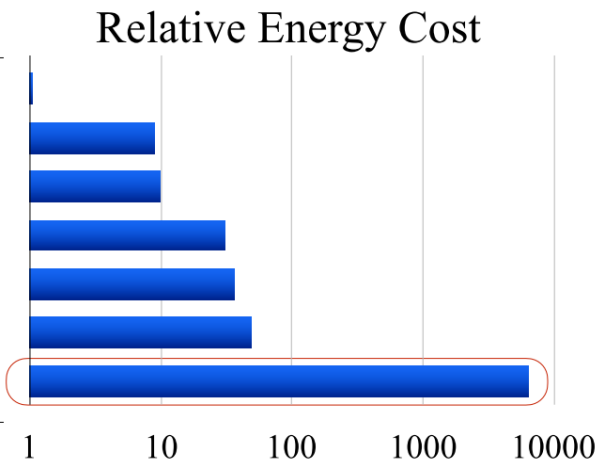

Source: Han Song, "Efficient Methods and Hardware for Deep Learning" & V. Sze et.al.
 "Efficient Processing of Deep Neural Networks: A Tutorial and Survey"



Design Trade-off

Implement the best HW realization. **Best??**



**Flexibility
Complexity**




- Processors
- FPGAs



**Low power
Low cost
Flexibility**



- Processors
- Dedicated HW

 

**Lower power
Lower cost**



- Dedicated HW
- Processors



Design Trade-off

Implement the best HW realization. **Best??**

Different applications, different demands...
Thus, "**just good enough**" is the best in engineering.

Try to find a **BALANCE** between effort and cost!




Overview

- Fixed-Point Representation
- **Add/Subtract**
- Multiplication
- Timing & Techniques to Reduce Delay



Add/Subtract (Binary)

 

■ The HW for sum/difference (S) does NOT care about signed/unsigned

■ Overflow

- Unsigned overflow = C_n
- Signed overflow = $C_n \oplus C_{n-1}$



Signed Overflow Example

4-Bit signed addition

$6 + 7 = 13$, outside $[-8..7]$

$$\begin{array}{r} 0110 \\ +0111 \\ \hline 1101 \end{array}$$

$C_4 = 0$
 $C_3 = 1$

$C_n \oplus C_{n-1} = C_4 \oplus C_3 = 0 \oplus 1 = 1 \Leftrightarrow$
Carry-outs different $\Leftrightarrow$ Signed overflow


Overflow Check in Hardware?




Overflow in Hardware

❑ Hardware does not take care of the overflow for you


- Unsigned

 

- Signed

 

Overflow in Hardware

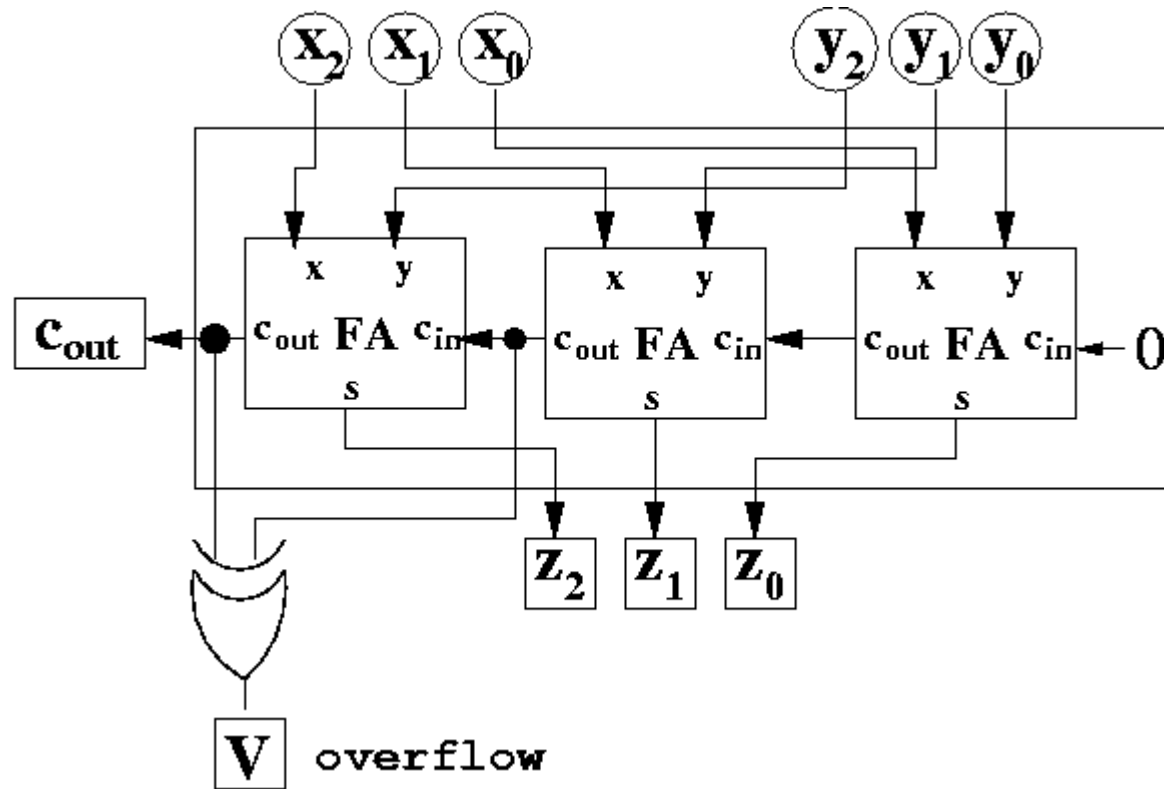

Saturation or wrap-around or 1 more bit



Two's Complement Signed Extension

□ To add two numbers, we should represent them with the **same number of bits**: **0100**+**11100**

- If we just pad with zeroes on the left:

4-bit

0100 (4)

1100 (-4)

8-bit

00000100 (still 4)

00001100 (12, not -4)

- Instead, replicate the MS bit -- **the sign bit**:

4-bit

0100 (4)

1100 (-4)

8-bit

00000100 (still 4)

11111100 (still -4)



Decimal Mark in Hardware

- Matlab aligns the decimal mark automatically

$$1.32 + 100.2343 = 101.5543$$

- Hardware **does NOT**

- Decimal mark is just a virtual concept

$$01.100 + 001.01 = ?$$

$$10001$$

- You need to align the decimal mark manually

$$001.100 + 001.010 = 010.110$$




Overview

Fixed-Point Representation

Add/Subtract

Multiplication

Timing & Techniques to Reduce Delay

 


Array Multiplier (unsigned)

1011 * 1110
0000 (*0 = zero)
+1011. (*1 = copy)
+1011.. (*1 = copy)
+1011... (*1 = copy)
10011010

Direct Mapping

- Horizontal** : partial product using AND
- Vertical** : shift-add of partial product

Multiplicand

 

Don't Forget ... Signed Multiplication

$$\begin{array}{r} 1\ 0\ 1\ 1 \\ 0\ 0\ 1\ 1 \\ \hline \end{array} \begin{array}{l} -5x \\ +3 \end{array}$$

?

$$\begin{array}{r} 1\ 1\ 1\ 1\ 0\ 0\ 0\ 1 \\ \hline \end{array} -15$$



Signed Multiplication

□ Either transform to multiply of non-negative integers:

- Record signs and negate any negative factors.
- Perform unsigned multiplication.
- Negate product if signs above differ.

$$\begin{array}{r}
 \text{abs}(-5)=5 \\
 \text{abs}(3)=3
 \end{array}
 \begin{array}{r}
 \begin{array}{cccc}
 0 & 1 & 0 & 1 \\
 0 & 0 & 1 & 1 \\
 \hline
 0 & 1 & 0 & 1 \\
 0 & 1 & 0 & 1 \\
 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 \\
 \hline
 0 & 0 & 0 & 1 & 1 & 1 & 1
 \end{array}
 \begin{array}{l}
 +5x \\
 +3 \\
 \\
 \\
 \\
 +15
 \end{array}
 \end{array}
 \begin{array}{l}
 \\
 \\
 \\
 -1*1*15=-15
 \end{array}$$



Signed Multiplication

□ Or directly perform signed multiplication:

- **Multiplier:** positive
- **Multiplicand:** positive or negative
- **Sign extend** the partial products when adding up

$$\begin{array}{r} 1011 \quad -5x \\ \underline{0011} \quad +3 \\ 11111011 \\ 1111011 \\ 000000 \\ \underline{00000} \\ 11110001 \quad -15 \end{array}$$





Multiplier in Xilinx FPGA


■ Embedded DSP48E1

- 25×18 embedded multipliers (**two's-complement multiplier**)
- Using Embedded Multipliers in Artix-7 FPGAs

  http://www.xilinx.com/support/documentation/user_guides/ug479_7Series_DSP48E1.pdf



Multiplier in Xilinx FPGA

 

Multiplier in Xilinx FPGA

USE_DSP48 Verilog Example

```
(* use_dsp48 = "yes" *) module test(clk, in1, in2, out1);
```

USE_DSP48 VHDL Example

```
attribute use_dsp48 : string;  
attribute use_dsp48 of P_reg : signal is "no"
```

```
architecture archi of use_dsp48_example is  
    signal s : std_logic_vector (7 downto 0);  
    attribute use_dsp48 : string;  
    attribute use_dsp48 of s : signal is "yes";  
begin  
    process (clk)  
    begin  
        if clk'event and clk = '1' then  
            s <= s + a;  
        end if;  
    end process;  
end archi;
```




Constant Multiplication

 Examples:

- **Twiddle factor** in FFTs
- **Constellation points** in wireless communication

$$y_j = \sum_{k=0}^{n-1} e^{-\frac{2\pi i}{n}jk} x_k$$



Software may be not smart enough to optimize

Designer should optimize that multiplications with a small constant is accomplished by **shifts & adds**

Some numerical examples:

*2 (*10₂): multiplicand << 1

*3 (*11₂): multiplicand << 1 + multiplicand

*5 (*101₂): multiplicand << 2 + multiplicand

*255 (*11111111₂): ?

multiplicand << 8 – multiplicand




Overview

- Fixed-Point Representation
- Add/Subtract
- Multiplication
- **Timing & Techniques to Reduce Delay**




Combinational Circuit Timing

□ Path delay = cell delay + net delay

 

 
$$\text{Path Delay} = 0.5 + 0.4 + 0.62 + 0.21 + 1.28 + 0.12 + 0.82 = 3.95 \text{ ns}$$




Combinational Circuit Timing

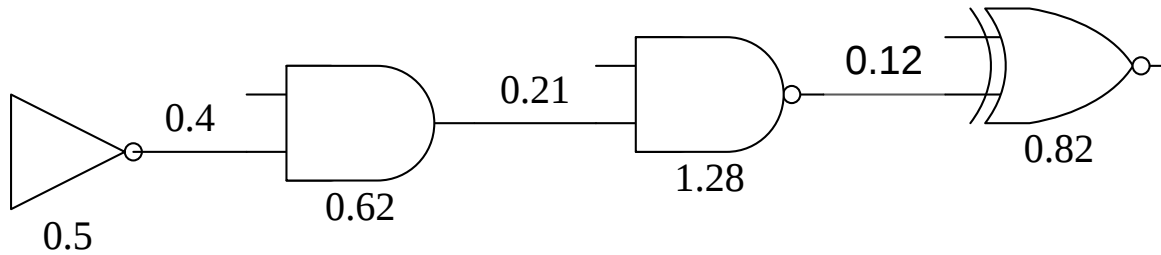□ **Path delay = cell delay + net delay**


 
$$\text{Path Delay} = 0.5 + 0.4 + 0.62 + 0.21 + 1.28 + 0.12 + 0.82 = 3.95 \text{ ns}$$




$$R = \rho \frac{L}{WH}$$

$$C_{ILD} = K_{ox} \epsilon_o \frac{WL}{X_{ox}}$$


$$C_{IMD} = K_{ox} \epsilon_o \frac{HL}{L_s}$$

Combinational Circuit Timing

□ Path delay = cell delay + net delay

 

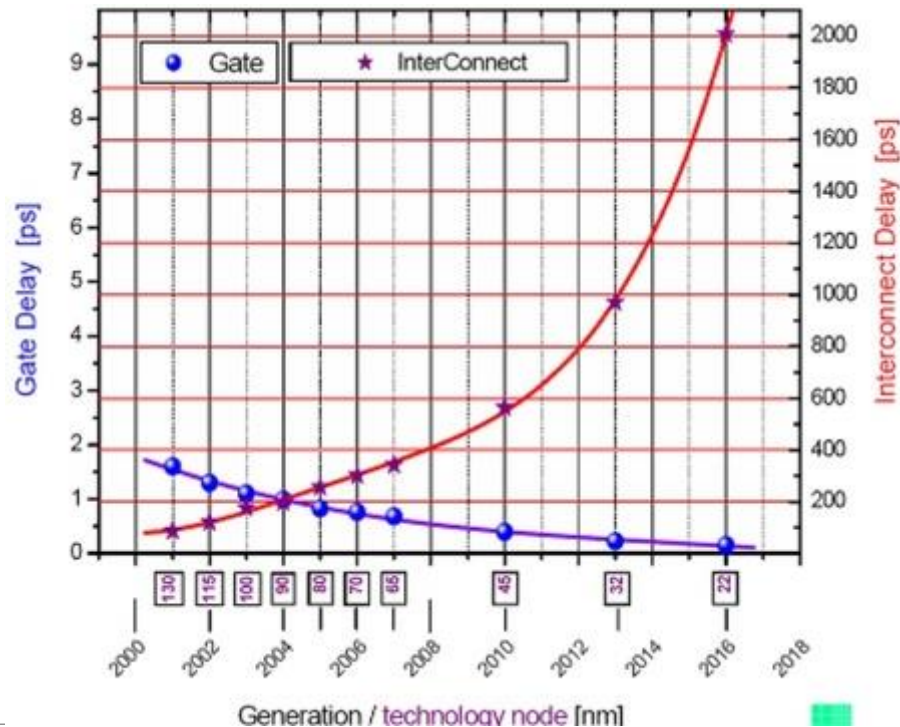
$$\text{Path Delay} = 0.5 + 0.4 + 0.62 + 0.21 + 1.28 + 0.12 + 0.82 = 3.95 \text{ ns}$$




Combinational Circuit Timing

□ Path delay = cell delay + net delay

 

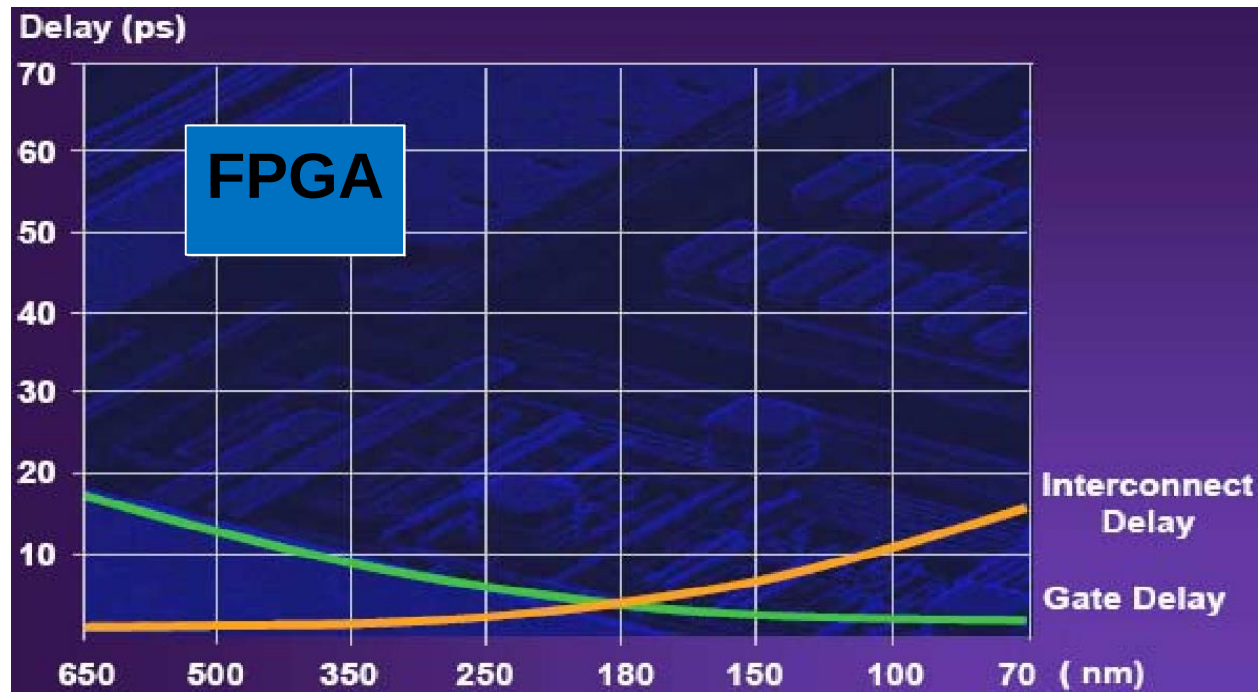
$$\text{Path Delay} = 0.5 + 0.4 + 0.62 + 0.21 + 1.28 + 0.12 + 0.82 = 3.95 \text{ ns}$$



Combinational Circuit Timing

□ Path delay = cell delay + net delay

 

$$\text{Path Delay} = 0.5 + 0.4 + 0.62 + 0.21 + 1.28 + 0.12 + 0.82 = 3.95 \text{ ns}$$


□ How to reduce processing delay

- Reduce cell delay? Standard-cell library (Digital-IC)
- Reduce net delay? Place & Route (Floor Plan)



Combinational Circuit Timing

□ Path delay = cell delay + net delay

 

$$\text{Path Delay} = 0.5 + 0.4 + 0.62 + 0.21 + 1.28 + 0.12 + 0.82 = 3.95 \text{ ns}$$


□ How to reduce processing delay

- Reduce cell delay? Standard-cell library (Digital-IC)
- Reduce net delay? Place & Route
- Or we can change the architecture



 Example1: Higher-Level Adder Chain

□ Calculate: $B = A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8$




Cascaded-Chain



Higher-Level
 
$$B = [(A_1 + A_2) + (A_3 + A_4)] + [(A_5 + A_6) + (A_7 + A_8)]$$



Thanks!

