

# Special instructions for home exam in

## EITF65 Digitalteknik

Dept. of Electrical and  
Information Technology  
Lund University

### 10.00 on August 26, 2021, until latest 12.00 on August 27.

- ▶ Hand-out of exam: at 10.00 on August 26 the exam will be available on the course web page for download. Use your own white sheets for writing solutions. Alternatively, a copy of the exam and empty sheets of paper can be picked up in boxes outside EIT (third floor in E-building) from 10.00.
- ▶ Hand-in of exam: During 10.00-12.00 on August 27 you can hand in your exam solutions at the department (third floor in E-building, hand-in boxes in stairwell). Alternatively, you can hand in by scanning your solutions and email them to the examiner on email address: thomas@eit.lth.se no later than 12.00! But you must then also send the original solutions and this first page with original signature by regular mail to the address below.<sup>1</sup> The exam will not be corrected until this is received.
- ▶ Exam contents: In the home exam there will be problems similar to a standard exam. The grading will require 25/35/45 points for grade 3/4/5, respectively, out of a total of 50. To get grade 5 you additionally need to be approved on an oral exam.
- ▶ Sign-up: You need to have signed up to take the exam.
- ▶ Help and assistance: You are allowed to use any written information you have access to and you are allowed to use computers and programming for computations. **You are not allowed to get assistance in any way from any other person to help you with your solutions.** This includes asking people to post information on forums, etc. It also includes assisting any other person doing the exam. To assure this, you have to formally sign such a statement.<sup>2</sup> **This first page with original signature must be handed in together with your solutions!**

Name:

Personal Code Number:

I solemnly declare that I have not used help from any other person in the process of preparing the exam solutions that I now hand in.

Signature:

Hand in this page with original signature!

<sup>1</sup>Address: Thomas Johansson, Dept. of EIT, Box 118, 22100 Lund, Sweden

<sup>2</sup>Overstepping the rules of help and assistance may lead to suspension from the university.





LUNDS  
UNIVERSITET

Electrical and Information Technology

# Exam in Digitalteknik, EITF65

26-27 augusti 2021

- ▶ Write your anonymous code and identifier, or personal number, on all papers you hand in.
- ▶ Start a new solution on a new sheet of paper. Use only one side of the sheet.
- ▶ The solutions must clearly show the line of reasoning.
- ▶ If asked for, the circuits for realizations should be drawn.
- ▶ You are allowed to use the course book and lecture notes.

Good Luck!

---

## Problem 1

Consider the following Boolean function in 5 variables given by its on-set and don't care set,

$$f^{-1}(1) = \{0, 3, 5, 7, 10, 15, 19, 21, 24, 28, 31\}$$

$$f^{-1}(-) = \{1, 2, 8, 11, 17, 23, 26, 30\}$$

Derive and write down all prime implicants and determine which of them are essential. Then express  $f$  in the minimal disjunctive form.

(10p)

---

## Problem 2

Consider the case where we have two binary inputs  $s_1$  and  $s_2$  and an output  $y$  in a discrete system. The output  $y(t)$  is 1 if and only if at least five of the six bits in

$$s_1(t), s_1(t-1), s_1(t-2), s_2(t), s_2(t-1), s_2(t-2)$$

are one. Assume that  $s_i(t) = 0$  if  $t < 0$ ,  $i = 1, 2$ . The following example gives inputs and the corresponding output sequence  $y(t)$  as follows,

$$s_1(t) = 11101111000101\dots$$

$$s_2(t) = 01110011001100\dots$$

$$y(t) = 00110001000000\dots$$

Construct a sequential circuit for the problem, using a minimum number of delay units (D-element). Construct the circuit using standard gates and make a picture of the full construction!


(10p)

---

---

### Problem 3

Consider the linear feedback shift register (LFSR) illustrated in Figure 3.1. Let the initial state be  $(u_0, u_1, \dots, u_4) = 01000$ , and let the sequence  $\mathbf{u}$  be generated as in the figure.

 

**Figure 3.1:** An LFSR generating the sequence  $\mathbf{u}$ .

- (a) Determine the  $D$ -transform of the sequence  $\mathbf{u}$ .
- (b) Determine the period of the sequence  $\mathbf{u}$ .
- (c) Find the shortest LFSR that can generate  $\mathbf{u}$ . Make a picture of this LFSR!
- (d) Assume that we add the sequence  $[01]^\infty$  (addition positionwise modulo 2) to the sequence  $\mathbf{u}$ . Determine the connection polynomial for the shortest LFSR that can generate this new sequence.

(1+2+3+4=10p)

---

### Problem 4

You are responsible for a digital construction handling four surveillance cameras connected to a monitor. Every camera has as input to the construction a sequence of 4-bit values  $\mathbf{u}_i(t)$ ,  $i = 0, \dots, 3$  at rate 1Mbit/s representing the image of that camera. Assume the notation  $\mathbf{u}_i(t) = (u_i^{(0)}(t), u_i^{(1)}(t), u_i^{(2)}(t), u_i^{(3)}(t))$ ,  $i = 0, \dots, 3$ .

Each camera has one more input signal  $v_i(t)$ ,  $i = 0, \dots, 3$ . If it is high (1) it indicates that the alarm, where the camera is located, is active. Your construction should work in such a way that if any alarm signal is high, then the image from that particular camera should be shown on the monitor. If there is no alarm signal high, then camera 0 should be displayed. The output in your construction should be a sequence of 4-bit values connected to the the monitor and one additional output, connected to a red lamp that will flash red when its signal is high. The lamp should flash when an alarm is active.

- (a) Construct a minimal combinatorial circuit  $K$  with  $v_i(t)$ ,  $i = 0, \dots, 3$  as input, and three outputs (Alarm,  $k_0, k_1$ ). The output Alarm is one if any alarm is active, and  $k_0, k_1$  is then the numerical representation of the camera where the alarm is active. If Alarm = 0 then  $(k_0, k_1) = (0, 0)$ . Use standard gates and make a picture of the circuit!
- (b) Now make a full construction, using components of type: multiplexer according to the data sheet in the appendix, 1 MHz clock, standard gates, delay units and the combinatorial circuit  $K$  from (a). Draw a picture of the construction in detail!

(2+8=10p)

---

## Problem 5

Let  $x_1(t), x_2(t)$  be two binary signals with  $t \in \mathbb{R}$ . If  $x_i(t) = 1$  during  $t_0 < t < t_1$  with  $x_i(t_0) = x_i(t_1) = 0$  then we call this a pulse. The length of pulses and the distance inbetween them are assumed to be much larger than the delay in a gate. Construct a minimal asynchronous sequential circuit where the output  $y(t)$  is  $y(t) = 1$  from the time when at least one pulse on each input signal has been detected, otherwise we should have  $y(t) = 0$ . The sequential circuit can be of Moore type. Realizera asynchronous sequential circuit using standard gates and make a detailed picture!

(10p)

---

**Good luck!**


**HCT157 QUAD 2 CHANNEL MULTIPLEXER**  
**HCT158 QUAD 2 CHANNEL MULTIPLEXER (INV.)**

- HIGH SPEED  
 $t_{PD} = 21 \text{ ns}$  (TYP.) AT  $V_{CC} = 5 \text{ V}$
- LOW POWER DISSIPATION  
 $I_{CC} = 4 \mu\text{A}$  (MAX.) AT  $T_A = 25^\circ\text{C}$
- COMPATIBLE WITH TTL OUTPUTS  
 $V_{IH} = 2 \text{ V}$  (MIN.)  $V_{IL} = 0.8 \text{ V}$  (MAX)
- OUTPUT DRIVE CAPABILITY  
10 LSTTL LOADS
- SYMMETRICAL OUTPUT IMPEDANCE  
 $|I_{OH}| = I_{OL} = 4 \text{ mA}$  (MIN.)
- BALANCED PROPAGATION DELAYS  
 $t_{PLH} = t_{PHL}$
- PIN AND FUNCTION COMPATIBLE  
WITH 54/74LS157/158

 **DESCRIPTION**


The M54/74HCT157 and the M54/74HCT158 are high speed CMOS QUAD 2-CHANNEL MULTIPLEXERS fabricated with silicon gate  $C^2$ MOS technology. They achieve the high speed operation similar to equivalent LSTTL while maintaining the CMOS low power dissipation.

These devices consist of four 2-input digital multiplexers with common select and strobe inputs. The HCT158 is an inverting multiplexer while the HCT157 is a non-inverting multiplexer. When the **STROBE** input is held High, selection of data is inhibited and all the outputs become Low in the M74HCT157 and High in the M74HCT158. The **SELECT** decoding determines whether the A or B inputs get routed to their corresponding Y outputs. All inputs are equipped with protection circuits against static discharge and transient excess voltage. M54/74HCT devices are designed to directly interface HSC<sup>2</sup>MOS systems with TTL and NMOS components. They are also plug in replacements for LSTTL devices giving a reduction of power consumption.




**PIN CONNECTIONS (top view)**

**HCT157**

 


**HCT158**

 


NC =  
No Internal  
Connection

## CHIP CARRIER

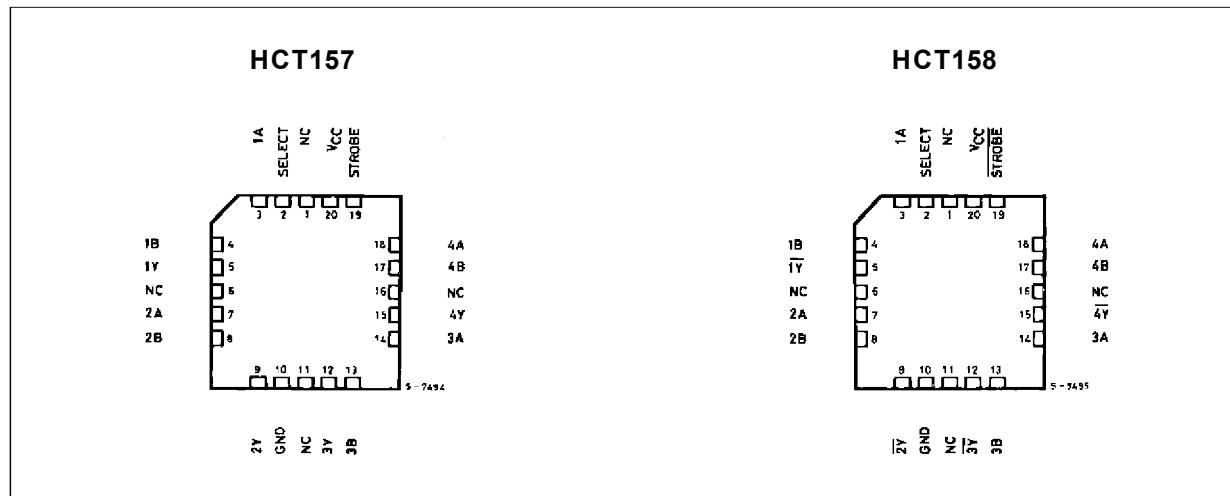

## INPUT AND OUTPUT EQUIVALENT CIRCUIT

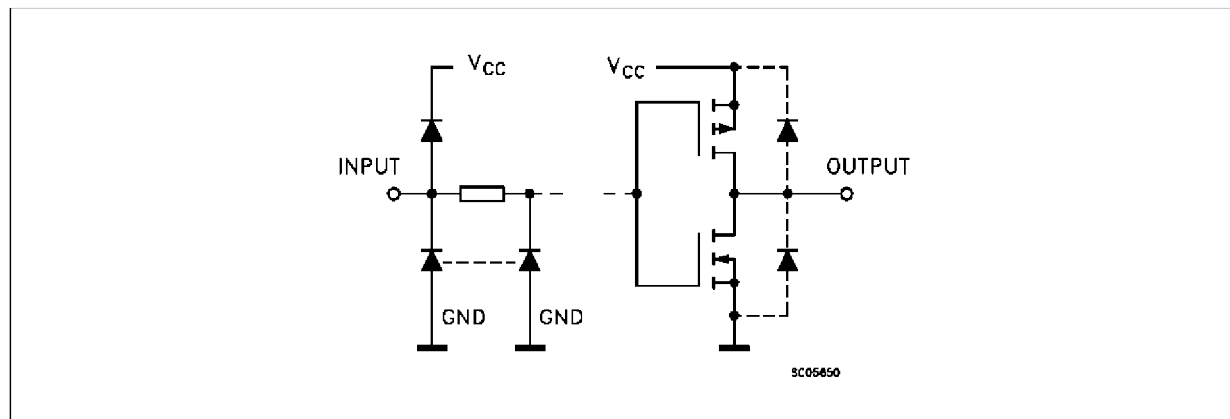

### PIN DESCRIPTION (for HCT157)

PIN No	SYMBOL	NAME AND FUNCTION
1	SELECT	Common Data Select Input
2, 5, 11, 14	1A to 4A	Data Inputs From Source A
3, 6, 10, 13	1B to 4B	Data Inputs From Source B
4, 7, 9, 12	1Y to 4Y	Multiplexer Output
15	STROBE	Strobe Input
8	GND	Ground (0V)
16	Vcc	Positive Supply Voltage

### PIN DESCRIPTION (for HCT158)

PIN No	SYMBOL	NAME AND FUNCTION
1	SELECT	Common Data Select Input
2, 5, 11, 14	1A to 4A	Data Inputs From Source A
3, 6, 10, 13	1B to 4B	Data Inputs From Source B
4, 7, 9, 12	1Y to 4Y	Multiplexer Output
15	STROBE	Strobe Input
8	GND	Ground (0V)
16	Vcc	Positive Supply Voltage




## TRUTH TABLE

INPUTS				OUTPUTS	
STROBE	SELECT	A	B	Y (HCT157)	Y (HCT158)
H	X	X	X	L	H
L	L	L	X	L	H
L	L	H	X	H	L
L	H	X	L	L	H
L	H	X	H	H	L

X: DON'T CARE

## IEC LOGIC SYMBOL

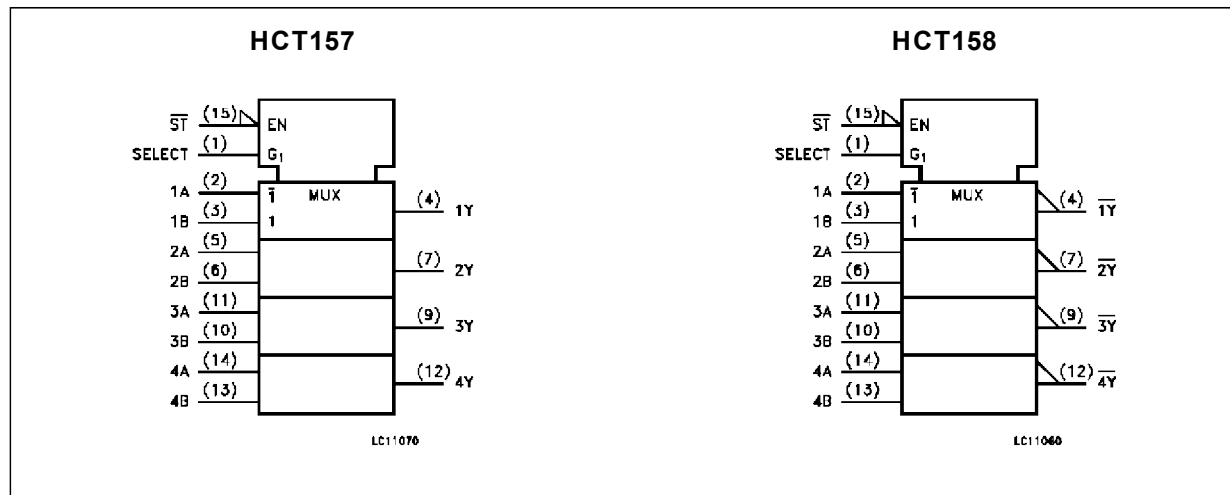

## LOGIC DIAGRAM

