

# Digitaltechnik

## Exercises for Digital Integrated Circuits

1. Make a truth table for the following circuits and set up the Boolean expression. Also draw an equivalent circuit using gates (AND, NAND, OR, NOR, NOT,...)

