



# Digitaltechnik EITF65

Lecture 12: Programmable Logic  
Standard Components  
CMOS Realizations

## Programmable Logic Array


A **PLA** (Programmable Logic Array) is a programmable circuit containing a two layer circuit with

- ▶  $n$  inputs and  $m$  outputs
- ▶ one **AND** area
- ▶ one **OR** area


The number of implicants is a measure of the size.

Mark the connections with a *plopp* (•)

# PLA

 

## Example: Detector (NBCD)

 

Assignment:

| $s$   | $q_0 q_1$ |
|-------|-----------|
| $s_0$ | 00        |
| $s_1$ | 01        |
| $s_2$ | 10        |
| $s_3$ | 11        |

Karnaugh maps:

| $q_1^+$ | 0 | 1 |
|---------|---|---|
| 00      | 0 | 0 |
| 01      | 1 | 0 |
| 11      | 0 | 0 |
| 10      | 1 | 1 |

| $q_2^+$ | 0 | 1 |
|---------|---|---|
| 00      | 1 | 0 |
| 01      | 0 | 0 |
| 11      | 1 | 0 |
| 10      | 0 | 1 |

| $u$ | 0 | 1 |
|-----|---|---|
| 00  | 0 | 0 |
| 01  | 0 | 0 |
| 11  | 0 | 1 |
| 10  | 0 | 0 |


Minimal functions:

$$u = q_1 q_2 x$$

$$q_1^+ = q_1 q_2' \vee q_1' q_2 x'$$

$$q_2^+ = q_1' q_2' x' \vee q_1 q_2 x' \vee q_1 q_2' x$$

## Example: Detector (Gray)

 

Assignment:

| $s$   | $q_0 q_1$ |
|-------|-----------|
| $s_0$ | 00        |
| $s_1$ | 01        |
| $s_2$ | 11        |
| $s_3$ | 10        |

Karnaugh maps:

| $q_1^+$ | 0 | 1 |
|---------|---|---|
| 00      | 0 | 0 |
| 01      | 1 | 0 |
| 11      | 1 | 1 |
| 10      | 0 | 0 |

| $q_2^+$ | 0 | 1 |
|---------|---|---|
| 00      | 1 | 0 |
| 01      | 1 | 0 |
| 11      | 1 | 0 |
| 10      | 1 | 0 |

| $u$ | 0 | 1 |
|-----|---|---|
| 00  | 0 | 0 |
| 01  | 0 | 0 |
| 11  | 0 | 0 |
| 10  | 0 | 1 |

Minimal functions:

$$u = q_1 q_2' x$$


$$q_1^+ = q_2 x' \vee q_1 q_2$$

$$q_2^+ = x'$$

# Multiplexer (Dataväljare)
 
## MUX

A **multiplexer**, or switch, is a circuit where  $L$  bits choose one of  $K = 2^L$  inputs.




The output is given by

$$y = x_{\phi(c_{L-1}, \dots, c_0)}$$

# Tri-state
 
## Tri-state

A tri-state buffer is a buffer with a control signal  $\varphi$ . If  $\varphi = 1$  the buffer is active, otherwise the output is high impedance (disconnected).




| $x$ | $\varphi$ | $y$            |
|-----|-----------|----------------|
| —   | 0         | High impedance |
| 0   | 1         | 0              |
| 1   | 1         | 1              |

# Demultiplexer (Avkodare)
 
## DeMUX

A **demultiplexer**, or decoder, is a circuit where  $L$  bits choose one of  $K = 2^L$  outputs.




The output is given by

$$y_i = \begin{cases} x, & \text{if } \phi(c_{L-1}, \dots, c_0) = i \\ 0, & \text{o.w.} \end{cases}$$



# Counter 74LS162A

 


| Pins            | Action  |
|-----------------|---|
| $P = P_3 - P_0$ | Parallel input  |
| $Q = Q_3 - Q_0$ | Parallel output; The state  |
| $\overline{SR}$ | Synchronous reset, active low<br>$Q \leftarrow 0$   |
| $\overline{PE}$ | Parallel enable (Load), active low<br>$Q \leftarrow P$  |
| CEP             | Count enable  |
| CET             | Count enable  |
| TC              | Terminal count output,<br>$TC = CET \wedge Q_3 \wedge Q_2' \wedge Q_1' \wedge Q_0$<br>Used for cascading counters |
| CP              | Clock   |

# Counter 74LS162A
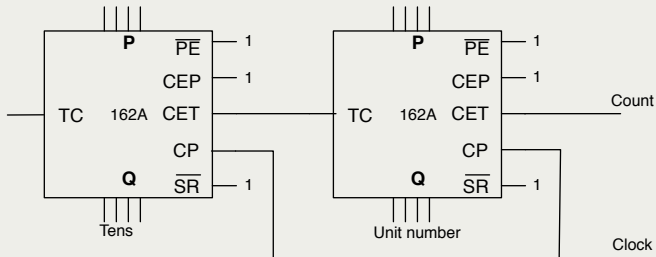
## Example: Cascade

Since  $TC = 1$  when  $Q = 9$  and  $CET = 1$ , this can be used to cascade several counters.

To build a modulo 100 counter cascade two modulo 10:




# Counter 74LS162A

## Example: Modulo 6 counter (Alt 1)

Construct a modulo 6 counter.

When  $Q = 5$  and  $CET = 1 \Rightarrow \overline{SR} = 0$  (Reset to zero).

 The new TC:  $TC_{\text{mod}6} = Q'_3 \wedge Q_2 \wedge Q'_1 \wedge Q_0 \wedge CET$




# Counter 74LS162A

## Example: Modulo 6 counter (Alt 2)

If the value of  $Q$  not important.

Use that  $Q = 9$  and  $CET = 1 \Rightarrow TC = 1$ ,

Then load  $Q \leftarrow 10 - 6 = 4$ .

 

# CMOS

---


- ▶ MOS: Metal Oxide Semiconductor (also MOSFET)
- ▶ CMOS: Complementary Metal Oxide Semiconductor
- ▶ CMOS was patented in 1963
- ▶ One of several ways to build digital circuits
- ▶ Attractive properties
  - ▶ Noise resistant
  - ▶ Very low static power consumption
  - ▶ Can fit into small area

# CMOS, P-type and N-type

---
 
## P-type

- ▶ Must have source connected to either  $V_{DD}$  or another P-type MOSFET
- ▶ Low resistance (conducting) between source (S) and drain (D) when input is low (0)
- ▶ High resistance between source and drain when input is high (1)
- ▶ Model as switch: Closed when gate (G) is low, open when gate is high




# CMOS, P-type and N-type

---
 
## N-type

- ▶ Must have source connected to either GND or another N-type MOSFET
- ▶ High resistance between source (S) and drain (D) when input is low (0)
- ▶ Low resistance (conducting) between source and drain when input is high (1)
- ▶ Model as switch: Closed when gate (G) is high, open when gate is low




# CMOS, Complementary design

---

- ▶ For each N-type, complement with a P-type transistor
- ▶ Connect input to gate of both transistors

 
⇒ Only one is open at a time ⇒ Very low power consumption when state is not switching






# CMOS, Gate

---

 

# CMOS, Gate

 


| $AB$ | OUT |
|------|-----|
| 00   | 1   |
| 01   | 1   |
| 10   | 1   |
| 11   | 0   |


NAND gate

# CMOS, Gate

---

 

# CMOS, Gate

 

| $AB$ | OUT |
|------|-----|
| 00   | 1   |
| 01   | 0   |
| 10   | 0   |
| 11   | 0   |

NOR gate

## Basic design rules (informal)

- ▶ For each input combination, there must be a path between OUT and either  $V_{DD}$  or GND.
- ▶ For each input combination, there must not be a short circuit between  $V_{DD}$  and GND.

If N-type are in series, then P-type must be in parallel. And vice versa.