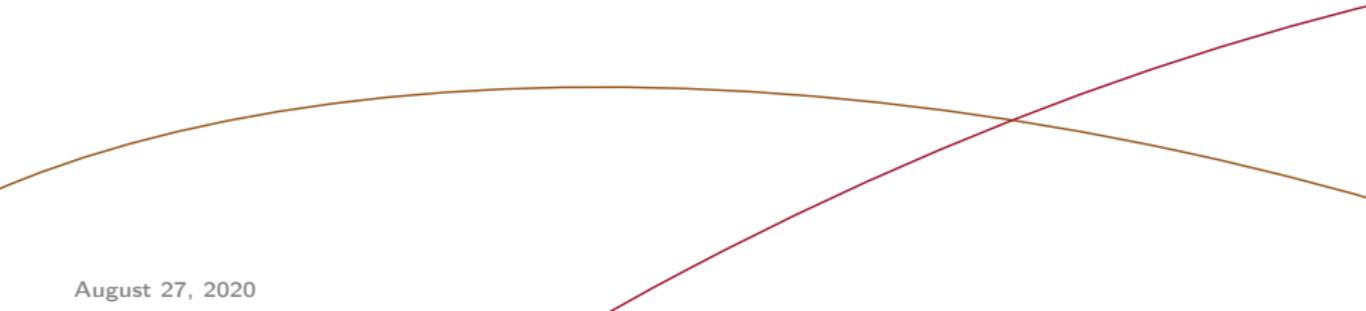




# Digitalteknik EITF65


Lecture 14: Linear Sequential Circuits, Part 2



# LFSR
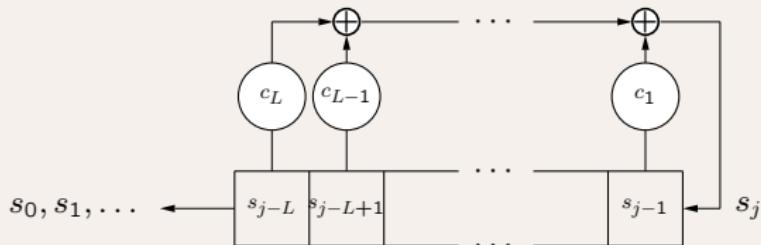
## Definition


A **linear feedback shift register (LFSR)** is a cascade of  $D$ -elements where the input is a linear function of the state variables.



# LFSR
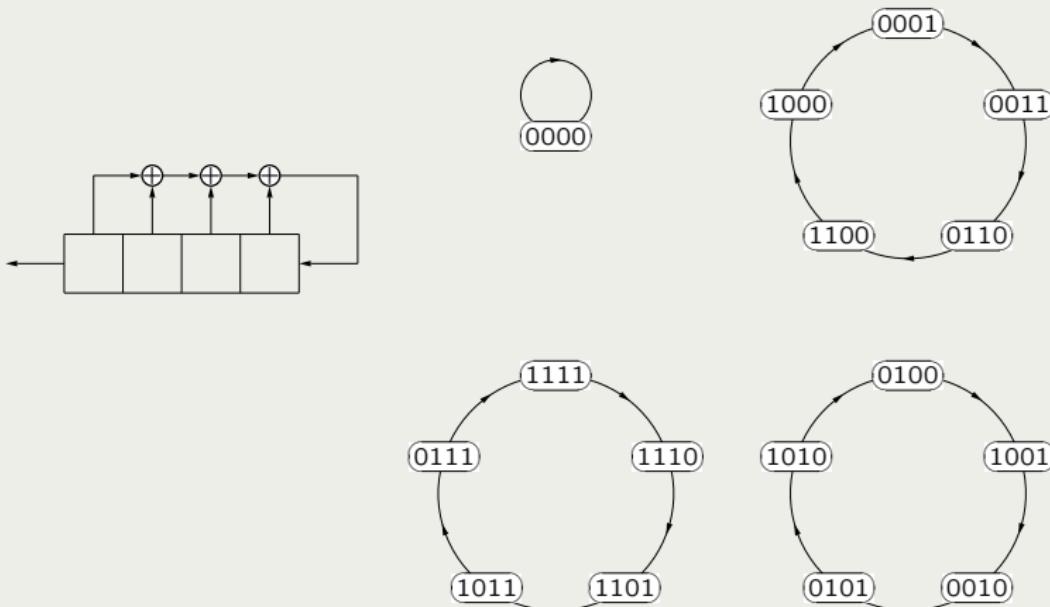
## Example


The following LFSR gives the state transition graph below.



# LFSR
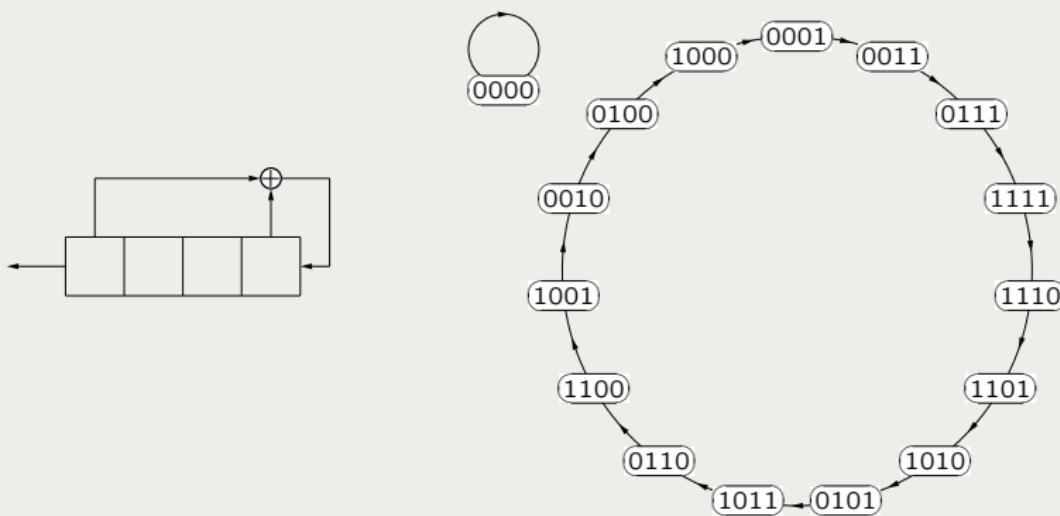
## Example

The following LFSR gives the state transition graph below.



# Maximal Length Sequence

---


## Definition

All LFSRs give separate cycles in the state transition graph. If all nonzero states are included in one cycle the output is called a **maximal length sequence**.

# LFSR

## Definition (Connection Polynomial)

The general form of an LFSR is given by:

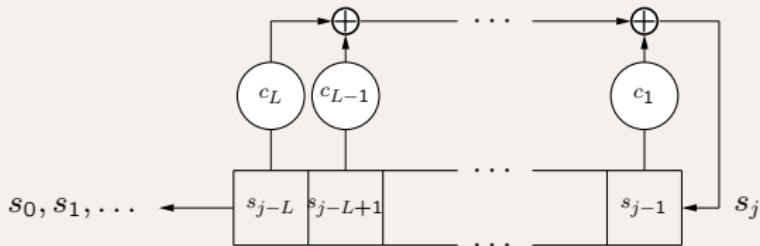

It is determined by  $\mathbf{c} = (1, c_1, \dots, c_L)$ . The  $\mathcal{D}$ -transform of  $\mathbf{c}$

$$C(D) = 1 \oplus \sum_{i=1}^L c_i D^i \stackrel{c_0=1}{=} \sum_{i=0}^L c_i D^i$$

is called the **connection polynomial** of the LFSR.

# Shift register recursion

---

## Theorem

The *shift register recursion* can be written as

$$\sum_{i=0}^L c_i s_{j-i} = 0, \quad j \geq L$$

where  $c_0 = 1$ .

## Shift register recursion

Proof.

For  $j \geq L$

$$s_j = c_L s_{j-L} \oplus c_{L-1} s_{j-L+1} \oplus \cdots \oplus c_1 s_{j-1} = \sum_{i=1}^L c_i s_{j-i}$$

or, equivalently,

$$s_j \oplus \sum_{i=1}^L c_i s_{j-i} = 0$$

With  $c_0 = 1$

$$c_0 s_j \oplus \sum_{i=1}^L c_i s_{j-i} = 0$$



# The LFSR theorem

---

## Theorem

An LFSR with connection polynomial  $C(D)$ ,  $\deg C(D) = L$ , can generate the sequence  $s$  if and only if  $S(D)$  can be written as

$$S(D) = \frac{P(D)}{C(D)}$$

where  $\deg P(D) < \deg C(D)$ .

See proof in course book.

## Euclid's algorithm

---

To find the shortest LFSR that generates a sequence  $s$  we delete common factors in the numerator and the denominator of the  $D$  transform  $S(D)$ .

Therefore, we need to find the greatest common divisor (gcd) of two polynomials. This can be done with Euclid's algorithm.

$$s = [1101001]^\infty$$

## Example

To find a minimal LFSR that generates  $s = [1101001]^\infty$ , consider the  $\mathcal{D}$ -transform

$$s(D) = \frac{1 \oplus D \oplus D^3 \oplus D^6}{1 \oplus D^7}$$


Use Euclid's algorithm to find common factors gives

$$\gcd(D^7 \oplus 1, D^6 \oplus D^3 \oplus D \oplus 1) = D^4 \oplus D^2 \oplus D \oplus 1$$

We get

$$s(D) = \frac{(1 \oplus D^2)(1 \oplus D \oplus D^2 \oplus D^4)}{(1 \oplus D \oplus D^3)(1 \oplus D \oplus D^2 \oplus D^4)} = \frac{1 \oplus D^2}{1 \oplus D \oplus D^3}$$

A minimal length LFSR:

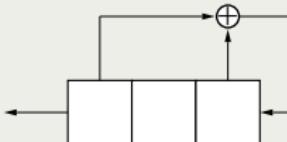

## Starting state ( $P(D) \rightarrow s$ )

---


To get the starting state we can also perform long division (series expansion) of (see next slide for derivation)

$$s(D) = \frac{1 \oplus D^2}{1 \oplus D \oplus D^3} = 1 \oplus D \oplus D^3 \oplus D^6 \oplus \dots$$

Hence,

$$s(D) = 1 \oplus D \oplus D^3 \oplus D^6 \oplus \dots \xrightarrow{\mathcal{D}^{-1}} \underbrace{110}_{\text{starting state}} 1001 \dots$$

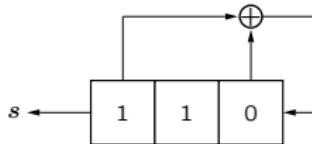The starting state is the first bits that are shifted out.



## Starting state ( $P(D) \rightarrow s$ )

---

Derivation of long division of  $S(D)$ .

$$\begin{array}{r} 1 \oplus D \quad \oplus D^3 \quad \oplus D^6 \oplus \dots \\ \hline 1 \oplus D \oplus D^3 \quad \boxed{1 \quad \oplus D^2} \\ 1 \oplus D \quad \oplus D^3 \\ \hline D \oplus D^2 \oplus D^3 \\ \hline D \oplus D^2 \quad \oplus D^4 \\ \hline D^3 \oplus D^4 \\ \hline D^3 \oplus D^4 \oplus D^6 \\ \hline D^6 \\ \hline D^6 \oplus D^7 \oplus D^9 \\ \hline D^7 \oplus D^9 \\ \hline \ddots \end{array}$$

## Starting state ( $s \rightarrow P(D)$ )

---

We can also derive  $P(D)$  from the starting state.

We know that

$$P(D) = S(D)C(D)$$

and if we know

$$C(D) = 1 \oplus D \oplus D^3$$

$$S(D) = 1 \oplus D \oplus \mathcal{O}(D^3)$$

where  $\mathcal{O}(D^3)$  represents all terms with degree 3 and higher.

Combining, we get


$$\begin{aligned} P(D) &= (1 \oplus D \oplus \mathcal{O}(D^3))(1 \oplus D \oplus D^3) \\ &= \underbrace{1 \oplus D^2}_{P(D)} \oplus \underbrace{\mathcal{O}(D^3)}_{=0} \end{aligned}$$

since  $\deg(P(D)) < \deg(C(D))$ .

# Observer canonical form
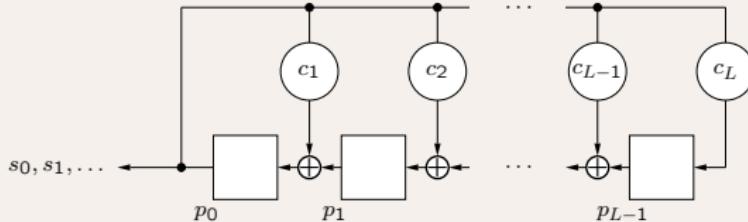
## OCF of LFSR

An LFSR is a linear sequential circuit in pseudo-controller canonical form. It can also be realized in observer canonical form.



To realize the sequence  $S(D)$  the starting state is

$$P(D) = S(D)C(D)$$


$$s(D) = \frac{1 \oplus D^2}{1 \oplus D \oplus D^3}$$

## Example

To generate the sequence  $s$  with  $\mathcal{D}$ -transform

$$s(D) = \frac{1 \oplus D^2}{1 \oplus D \oplus D^3}$$


we can use the circuit

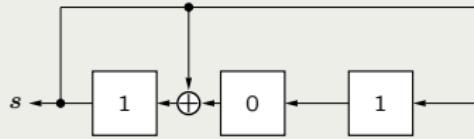

## State value

---

In this form the state is directly the remainder in the (long) division.

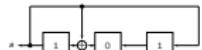  
1 0 1 =  $1 \oplus D^2$   
1 1 1 =  $1 \oplus D \oplus D^2$   
0 1 1 =  $D \oplus D^2$   
1 1 0 =  $1 \oplus D$   
0 0 1 =  $D^2$   
0 1 0 =  $D$   
1 0 0 = 1  
1 0 1 =  $1 \oplus D^2$

$$\begin{array}{r} 1 \oplus D \oplus D^3 \oplus D^6 \oplus \dots \\ \hline 1 \oplus D \oplus D^3 \\ 1 \oplus D \oplus D^3 \\ \hline D \oplus D^2 \oplus D^3 \\ D \oplus D^2 \oplus D^4 \\ \hline D^3 \oplus D^4 \\ D^3 \oplus D^4 \oplus D^6 \\ \hline D^6 \\ D^6 \oplus D^7 \oplus D^9 \\ \hline D^7 \oplus D^9 \end{array} = D(1 \oplus D \oplus D^2) = D^2(D \oplus D^2) = D^3(1 \oplus D) = D^4(D^2) = D^5(D) = D^6(1) = D^7(1 \oplus D^2)$$

# The period

---

The period  $T$  for a connection polynomial  $C(D)$  is defined as the smallest  $T > 0$  for which  $C(D)$  divides  $1 + D^T$ .

## Theorem

*The period for connection polynomial  $C(D)$  can be derived by the long division (series expansion) of  $\frac{1}{C(D)}$ . At the first occasion the remainder is  $D^k$  we get the period as  $T = k$ .*

# Period

## Example 7.7

To calculate the period for the connection polynomial

$$C(D) = 1 \oplus D \oplus D^3$$

we derive  $\frac{1}{C(D)}$ :

$$\begin{array}{r} 1 \oplus D \oplus D^2 \quad \oplus D^4 \oplus \dots \\ \hline 1 \oplus D \oplus D^3 | 1 \\ 1 \oplus D \quad \oplus D^3 \\ \hline D \quad \oplus D^3 \\ D \oplus D^2 \quad \oplus D^4 \\ \hline D^2 \oplus D^3 \oplus D^4 \\ D^2 \oplus D^3 \quad \oplus D^5 \\ \hline D^4 \oplus D^5 \\ D^4 \oplus D^5 \oplus D^7 \\ \hline D^7 \end{array}$$

Hence, the period is  $T = 7$ .

# The period

---

## Theorem

*The period for connection polynomial  $C(D)$  and the period of the sequence  $s$  with  $D$ -transform*

$$S(D) = \frac{P(D)}{C(D)}, \quad \text{where } \deg(P(D)) < \deg(C(D)),$$

*is the same if  $\gcd(P(D), C(D)) = 1$ .*