

High Speed Electronics 2019 – Exercise 3 Solutions

1. a)

$$\omega_T = \frac{g_m}{C_{gs}} = 2 * 10^{12} \text{ rad/s}$$

$$R = R_i + R_G = \frac{1}{1.4g_m} + R_G = 40.7\Omega$$

For f = 10GHz,

$$\omega = 2\pi f = 6.28 * 10^{10} \text{ rad/s}; \omega \ll \omega_T$$

$$F_{min} = 1 + 2\sqrt{\gamma} \frac{\omega}{\omega_T} = 1.06$$

$$NF = 10 \log(F) = 0.25 \text{ dB}$$

$$X_{opt} = \frac{1}{\omega C_{gs}} = 1592 \Omega$$

$$R_{opt} = \sqrt{R^2 + \frac{R}{\gamma g_m} \left(\frac{\omega_T}{\omega} \right)^2} = 1437 \Omega$$

For f = 94GHz,

$$\omega = 2\pi f = 0.6 * 10^{12} \text{ rad/s}; \omega \approx \omega_T$$

$$F_{min} = 1 + 2 \sqrt{R\gamma g_m \left(\frac{\omega}{\omega_T} \right)^2 + g_m^2 \gamma^2 R^2 \left(\frac{\omega}{\omega_T} \right)^4 + 2\gamma g_m R \left(\frac{\omega}{\omega_T} \right)^2} = 1.7$$

$$NF = 10 \log(F) = 2.3 \text{ dB}$$

$$X_{opt} = \frac{1}{\omega C_{gs}} = 167 \Omega$$

$$R_{opt} = \sqrt{R^2 + \frac{R}{\gamma g_m} \left(\frac{\omega_T}{\omega} \right)^2} = 156 \Omega$$

b) Assume $Z_s = R_s = 50 \Omega$

$$F = 1 + \frac{v_n^2 + |Z_s|^2 i_n^2 + 2\operatorname{Re}(v_n i_n^* Z_s^*)}{4kTR_s}$$

$$\begin{aligned} v_n^2 &= 4kT \left(R + \frac{\gamma}{g_m} (1 + (\omega RC)^2) \right) \\ i_n^2 &= \frac{4kT\gamma}{g_m} (\omega C_{gs})^2 \\ \operatorname{Re}(v_n i_n^*) &= \frac{4kT\gamma R}{g_m} (\omega C_{gs})^2 \end{aligned}$$

For $f = 10\text{GHz}$,

$$\begin{aligned} v_n^2 &= 363 \text{ kT} \\ i_n^2 &= 8 \cdot 10^{-5} \text{ kT} \\ \operatorname{Re}(v_n i_n^*) &= 3 \cdot 10^{-3} \text{ kT} \\ F &= 2.82 \\ NF &= 4.5 \text{ dB} \end{aligned}$$

For $f = 10\text{GHz}$,

$$\begin{aligned} v_n^2 &= 375 \text{ kT} \\ i_n^2 &= 7 \cdot 10^{-3} \text{ kT} \\ \operatorname{Re}(v_n i_n^*) &= 0.29 \text{ kT} \\ F &= 3.11 \\ NF &= 4.9 \text{ dB} \end{aligned}$$

c)

$$v_n^2 = 4kT \left(R + \frac{\gamma}{g_m} (1 + (\omega RC)^2) \right) \Delta f$$

Assuming very low frequency, $\omega RC \ll 1$


$$v_n^2 = 4kT \left(R + \frac{\gamma}{g_m} \right) \Delta f$$

At room temperature $T = 293 \text{ K}$,

$$v_n^2 = 1.5 \cdot 10^{-12} \text{ V}^2$$


Smallest possible signal $v_n = 1.2 \mu\text{V}$

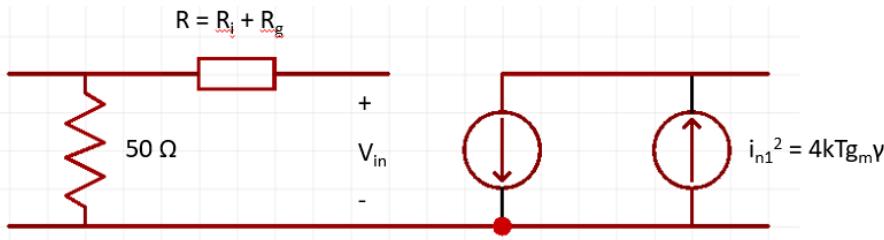d) Low frequency $\Delta f = 1 \text{ Hz}$. C_{gs} looks open. So we need to calculate v_n^2 , i_n^2 and $v_n i_n^*$. We also need to move all the noise sources outside the circuit:




i_{n1}^2 represent the noise due to drift/diffusion in the FET

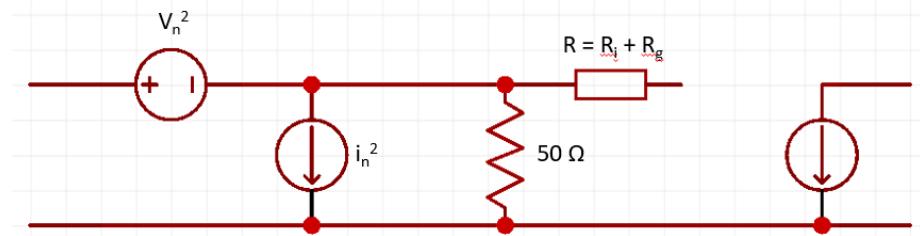The aim is to find v_n and i_n associated with the noise due to 50Ω resistor and the channel.




(i) To find i_n^2 , consider input open:

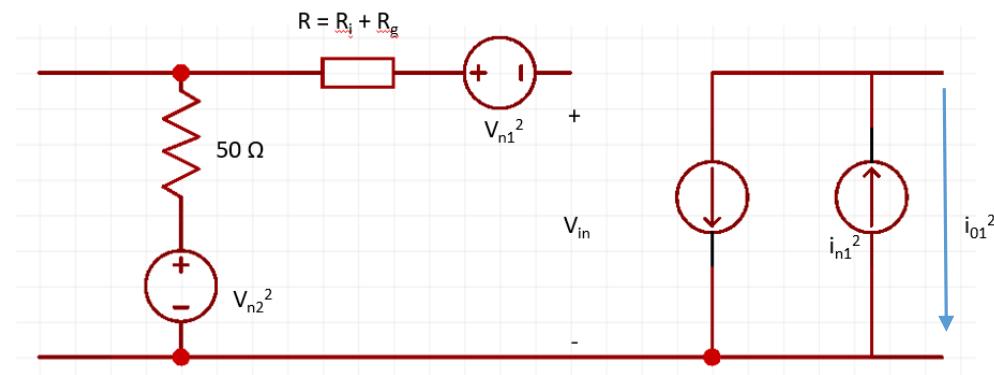

$$i_{01} = i_{n1} + (v_{n1} + v_{n2}) * g_m$$

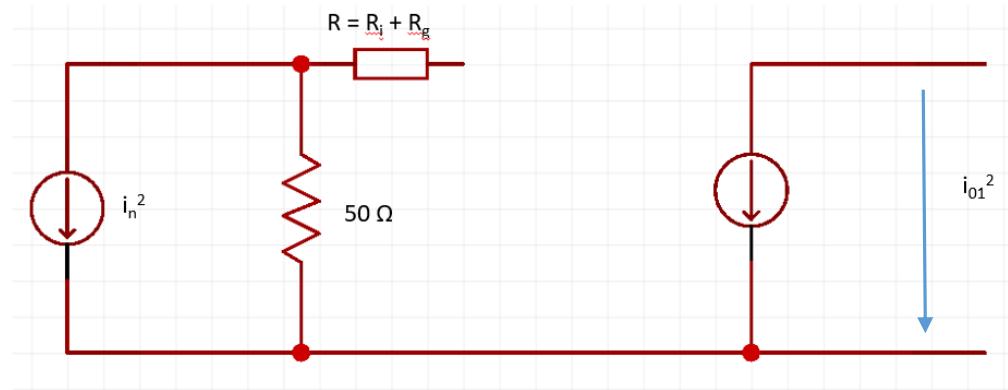Representing all the noise sources in the above circuit as i_n^2




$$i_{01} = g_m i_n * 50$$

Equating i_{01} from the above circuits:

$$i_n^2 = \frac{i_{n1}^2}{g_m^2 50^2} + \frac{v_{n1}^2 + v_{n2}^2}{50^2} \quad (\text{Assuming uncorrelated sources})$$


$$i_n^2 = 4kT \left(\frac{\gamma}{g_m * 50^2} + \frac{R + 50}{50^2} \right) = 0.23 kT$$

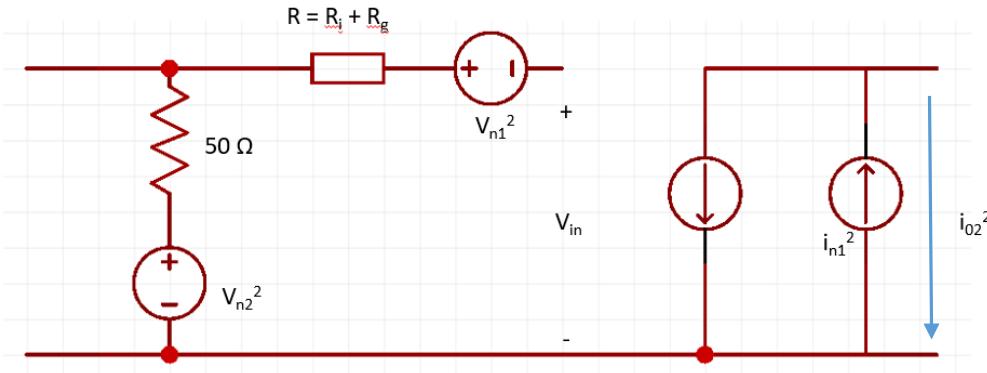(ii) To find v_n^2 , consider input shorted:



$$i_{02} = i_{n1} + v_{n1} g_m$$

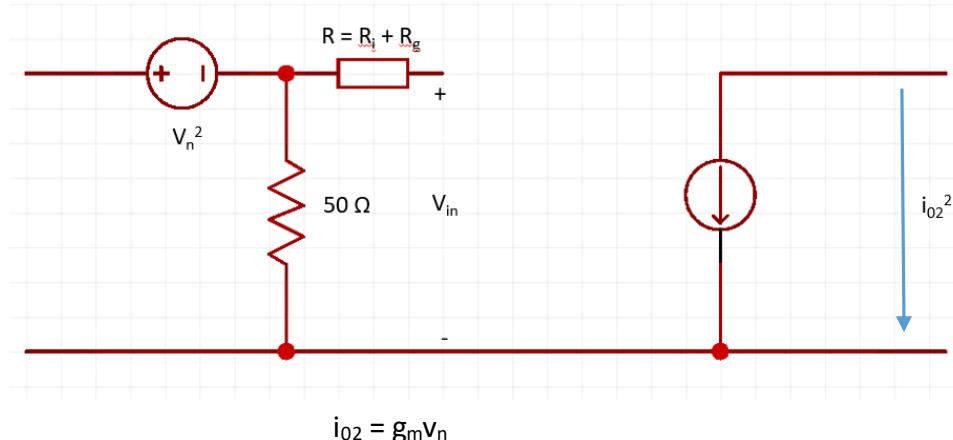Representing all the noise sources in the above circuit as v_n^2



$$i_{02} = g_m v_n$$

Equating i_{02} from the above circuits:

$$v_n^2 = v_{n1}^2 + \frac{i_{n1}^2}{g_m^2} = 4kT \left(R + \frac{\gamma}{g_m} \right) = 364 kT$$

$$v_n i_n^* = \frac{v_{n1}^2}{50} + \frac{i_{n1}^2}{g_m^2 * 50} = 4kT \left(\frac{R}{50} + \frac{\gamma}{g_m * 50} \right) = 7.3 kT$$

Thus the minimum noise figure for the device with a 50Ω resistance at the source is

$$F = 1 + \frac{v_n^2 + |Z_s|^2 i_n^2 + 2\operatorname{Re}(v_n i_n^* Z_s^*)}{4kT R_s} = 8.3$$

$$NF = 10 \log_{10} F = 9.2 dB$$

2. a-c) Gate capacitance normalized to areas is given by

$$\frac{1}{C_g} = \frac{1}{C_{ox}} + \frac{1}{C_q} + \frac{1}{C_c}$$

Thus, the gate capacitance per unit width for a gate length of $L_g = 20\text{nm}$

$$\frac{1}{C_g} = \left(\frac{1}{L_g C_{ox}} + \frac{1}{L_g C_q} + \frac{1}{L_g C_c} \right)$$

	m^*	ϵ_s	$L_g * C_{ox}$ (fF/ μ)	$L_g * C_q$ (fF/ μ)	$L_g * C_c$ (fF/ μ)	L_g (fF/ μ)
InAs	0.023	15.15	0.888	0.307	0.952	0.184
In _{0.53} Ga _{0.47} As	0.041	13.9	0.888	0.548	0.856	0.242
GaN	0.2	8.9	0.888	2.672	0.547	0.301

d)

$$I_{ds,sat} = \frac{qW2\sqrt{2m^*}}{3\pi^2 h^2} \left(\frac{qC'_{ox}}{C'_{ox} + \frac{C_q}{2}} \right)^{\frac{3}{2}} (V_{GS} - V_T)^{\frac{3}{2}}$$

Considering all the common terms as a constant and substituting

$$C'_{ox} = C_{ox} || C_c = \frac{C_{ox} C_c}{C_{ox} + C_c}$$

$$I_{ds,sat} = K \sqrt{2m^*} \left(\frac{1}{1 + \frac{C_q(C_{ox} + C_c)}{2C_{ox}C_c}} \right)^{\frac{3}{2}}$$

$$I_{ds,sat}(\text{GaN}) = 0.06\text{K}$$

$$I_{ds,sat}(\text{In}_{0.53}\text{Ga}_{0.47}\text{As}) = 0.137\text{K}$$

$$I_{ds,sat}(\text{InAs}) = 0.139\text{K}$$

Thus InAs has the highest saturation current given that there is no scattering.

$$3. \text{ a) } Y = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} j\omega C & -j\omega C \\ -j\omega C & j\omega C + R^{-1} \end{bmatrix}$$


$$\text{b) } Z = \frac{1}{Y_{11}Y_{22} - Y_{12}Y_{21}} \begin{bmatrix} Y_{22} & -Y_{21} \\ -Y_{12} & Y_{11} \end{bmatrix} = \begin{bmatrix} R + \frac{1}{j\omega C} & R \\ R & R \end{bmatrix}$$

c) The added parasitic network is connected in series to the given RC network, so the Z parameters of the full system are sum of Z parameters of individual networks.

$$Z_{total} = \begin{bmatrix} R + j\omega C & R \\ R & R \end{bmatrix} + \begin{bmatrix} R_G + R_{SD} & R_{SD} \\ R_{SD} & 2R_{SD} \end{bmatrix} = \begin{bmatrix} 4R + \frac{1}{j\omega C} & 2R \\ 2R & 3R \end{bmatrix}$$

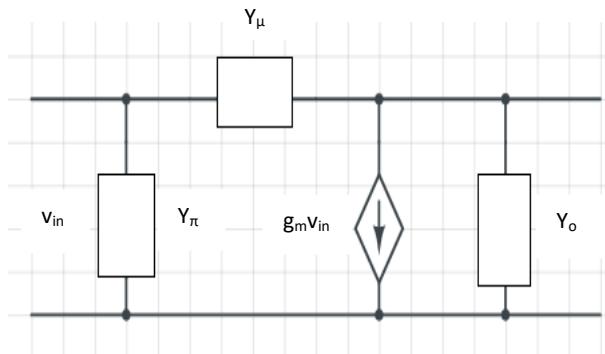d) It is easier to convert from Y parameters to the hybrid- π model. Now the total Y parameters of network including the parasitics is given by,

$$Y = \frac{1}{Z_{11}Z_{22} - Z_{12}Z_{21}} \begin{bmatrix} Z_{22} & -Z_{21} \\ -Z_{12} & Z_{11} \end{bmatrix} = \frac{1}{R \left(8R + \frac{3}{j\omega C} \right)} \begin{bmatrix} 3R & -2R \\ -2R & 4R + \frac{1}{j\omega C} \end{bmatrix}$$



The hybrid parameters are, $Y_\pi = Y_{11} + Y_{12} = \frac{1}{\left(8R + \frac{3}{j\omega C} \right)}$

$$Y_\mu = -Y_{12} = \frac{2}{\left(8R + \frac{3}{j\omega C} \right)}$$

$$Y_o = Y_{22} + Y_{12} = \frac{2R + \frac{1}{j\omega C}}{R \left(8R + \frac{3}{j\omega C} \right)}$$

$$g_m = Y_{21} - Y_{12} = 0$$