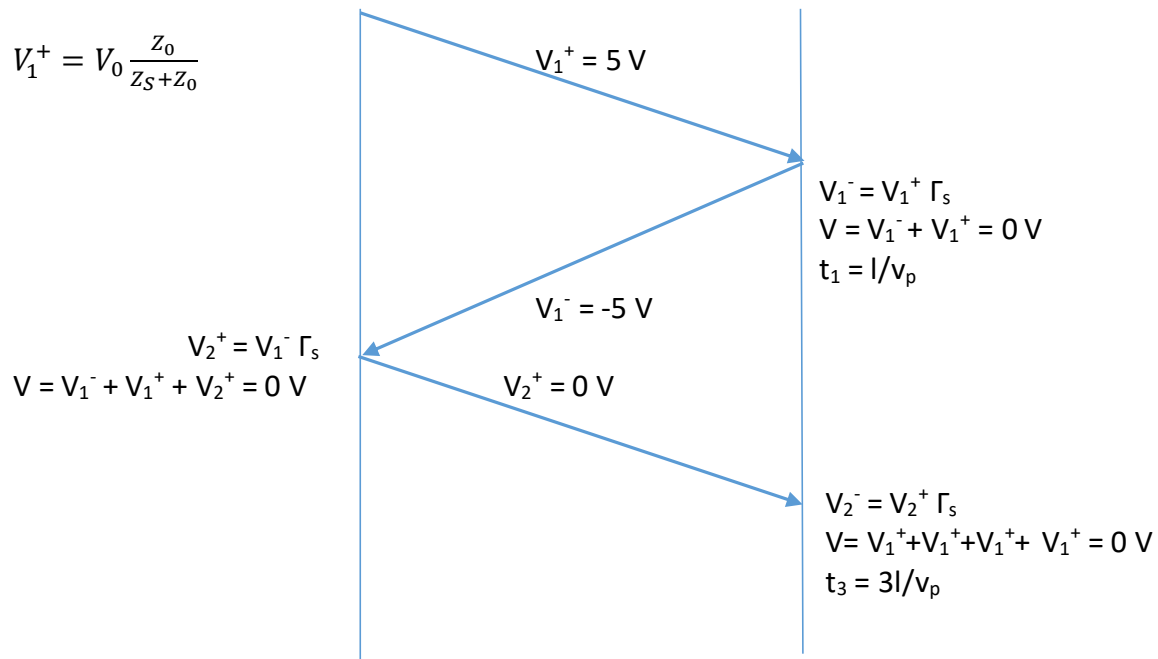


High Speed Electronics 2019-Exercise 4 solutions

1. $V_0 = 10 \text{ V}$
 $Z_s = 50 \Omega$
 $Z_L = 0 \Omega$

$$\Gamma_s = \frac{Z_s - Z_0}{Z_s + Z_0} = 0$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = -1$$



2. For an open line,

$$Z = -jZ_0 \frac{1}{\tan(\beta l)}$$

From the above equation, the length of the stub can be calculated as,

$$l = \frac{1}{\beta} \tan^{-1} \left(\frac{-jZ_0}{Z} \right)$$

$$\beta = \frac{\omega}{v_p} = \frac{2\pi f \sqrt{\epsilon_{eff}}}{c}$$

$$l = \frac{c}{2\pi f \sqrt{\epsilon_{eff}}} \tan^{-1} \left(\frac{-jZ_0}{Z} \right)$$

For a capacitance $C = 1\text{pF}$,

$$Z = \frac{1}{j\omega C} = -j16.7, \text{ Which gives, } l = 5.5\text{mm}$$

For an Inductor $L = 1\text{nH}$,

$$Z = j\omega L = j62.8, \text{ Which gives, } l = 3.9\text{mm}$$

3. $Z_0 = 50\Omega, Z_1 = 75\Omega$

a) Injection/Reflection co-efficient

$$\Gamma_s = \frac{Z_1 - Z_0}{Z_1 + Z_0} = 0.2$$

Transmission co-efficient

$$T = \frac{2Z_0}{Z_1 + Z_0} = 1.2$$

b) $V_0^- = V_0^+ \Gamma_s = 0.2V$ and $V_1^+ = V_0^+ T = 1.2V$

c)
$$P_{in} = \frac{1}{2} \frac{V_0^{+2}}{Z_0} = 0.01W$$

$$P_{avg} = \frac{1}{2} \frac{V_0^{+2}}{Z_0} (1 - \Gamma_s^2) = 0.009W$$


$$P_t = P_{in} \Gamma_s^2 = 0.0004W$$

$$P_{tr} = \frac{1}{2} \frac{V_1^{+2}}{Z_1} = 0.0096W$$


Energy is conserved because,

$$P_{in} - P_t = P_{tr} \text{ \& } P_{tr} = P_{avg}$$

4. General hybrid pi model

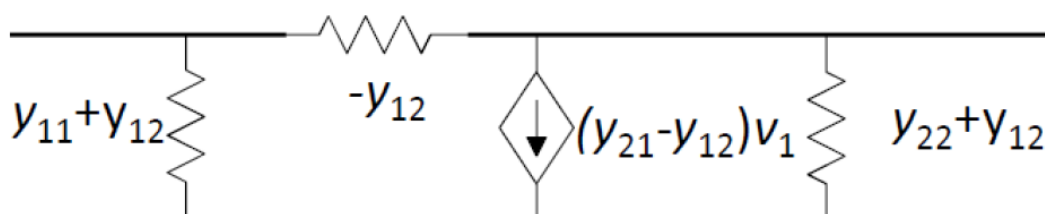

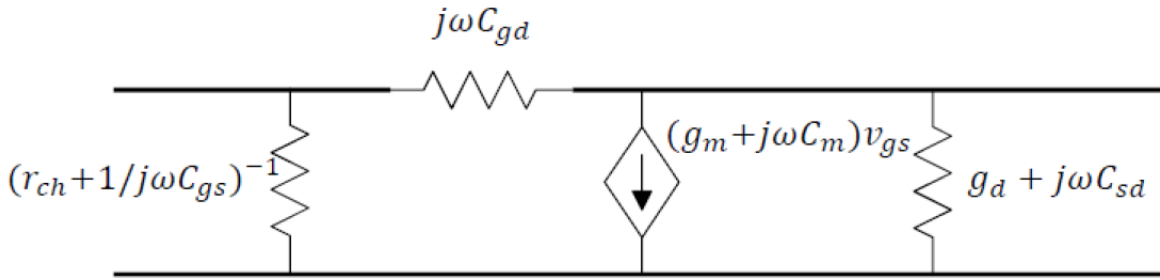The corresponding simplified NQS model ($R_S=R_D=R_G=0$)



f_{max} is the frequency at which $U=1$,

$$U = \frac{|y_{21} - y_{12}|^2}{4[Re(y_{11})Re(y_{22}) - Re(y_{12})Re(y_{21})]}$$

Miller capacitance C_m is the feedback capacitance between gate and drain. So assuming $C_m=0$, $y_{12}=0$

$$Re(y_{11}) = \frac{\omega^2 r_{ch}}{C_{gs}^2 + \omega^2 r_{ch}^2}$$

$$Re(y_{22}) = g_d$$

$$y_{21} - y_{12} = g_m (\text{since } C_m = 0)$$

$$Re(y_{12}) = 0$$

$$U = \frac{g_m^2 (C_{gs}^2 + \omega^2 r_{ch}^2)}{4\omega^2 r_{ch} g_d} = 1$$

$$f_{max} = \frac{g_m C_{gs}}{2\pi \sqrt{4r_{ch} g_d - r_{cg}^2 g_m^2}}$$

5. $f_T = \frac{g_m}{2\pi C_{gg}}$,

For $f_T > 1\text{THz}$, the minimum required g_m is, $g_m = 2\pi C_{gg} f_T = 10^{12} * 2\pi * C_{gg}$

From 1a, the calculated $C_{gg} = 0.23\text{fF}/\mu\text{m}$.

Best case: When parasitic capacitances are of, $C'_{gs} = C'_{gd} = 0.1\text{fF}/\mu\text{m}$,

The total capacitance including parasitics is, $C'_{gg} = C_{gg} + C'_{gs} + C'_{gd} = 0.43\text{fF}/\mu\text{m}$

The minimum $g_m=2.7\text{mS}/\mu\text{m}$

Worst case: When parasitics are of, $C'_{gs} = C'_{gd} = 0.5\text{fF}/\mu\text{m}$,

The total capacitance including parasitics is, $C'_{gg} = C_{gg} + C'_{gs} + C'_{gd} = 1.23\text{fF}/\mu\text{m}$

The minimum $g_m=7.72\text{mS}/\mu\text{m}$

Typical transconductances of quasi-ballistic FETs are 2-4mS/μm, thus it can be reached with the best-case condition considered. If the parasitic capacitances are too high, then it is not possible to achieve the desired transconductance for the given device.

6. De-normalizing the given parameters using the width W=10μm gives,

$$G_m = 20 \text{ mS}$$

$$G_d = 0.1 \text{ mS}$$

$$R_i = 30 \Omega$$

$$C_{gs} = 30 \text{ fF}$$

$$C_{gd} = 3 \text{ fF}$$

To find the y-parameters at f=60GHz

$$y_{11} = \left(R_i + \frac{1}{j\omega C_{gs}} \right)^{-1} + j\omega C_{gd} = 0.0034 + j0.0113 \text{ S}$$

$$\Omega y_{12} = -j\omega C_{gd} = -j0.00113 \text{ S}$$

$$y_{21} = g_m = 0.02 \text{ S}$$

$$y_{22} = g_d = 0.1 \text{ mS}$$

Rollett's stability factor,

$$K = \frac{2[\text{Re}(y_{11})\text{Re}(y_{22}) - \text{Re}(y_{12})\text{Re}(y_{21})]}{|y_{12}y_{21}|} = 0.0304$$

Maximum stable gain

$$MSG = \left| \frac{y_{21}}{y_{12}} \right| = 12.47 \text{ dB}$$

Maximum available gain,

$$MAG = \left| \frac{y_{21}}{y_{12}} \right| \left(k - \sqrt{k^2 - 1} \right)$$

The device is unstable at 60GHz as k<1. Therefore, MAG gives complex number. To stabilize the device, add a passive feedback that cancels the y₁₂

The gain after unilateralization is

$$U = \frac{|y_{21} - y_{12}|^2}{4[\text{Re}(y_{11})\text{Re}(y_{22}) - \text{Re}(y_{12})\text{Re}(y_{21})]} = 24.64 \text{ dB}$$