

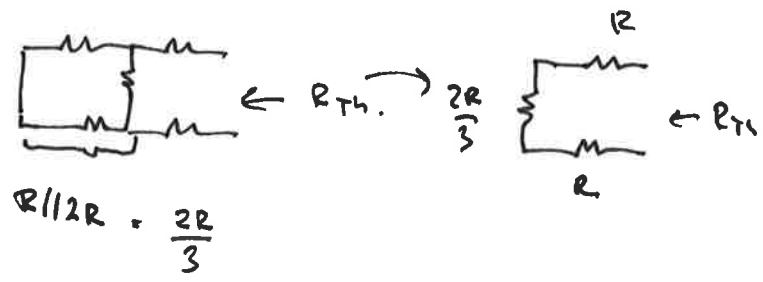


Sp. delung: $V_{TH} = \frac{R}{3R} \cdot V_0 = \frac{V_0}{3}$

R_{TH} : Nullstell V_0


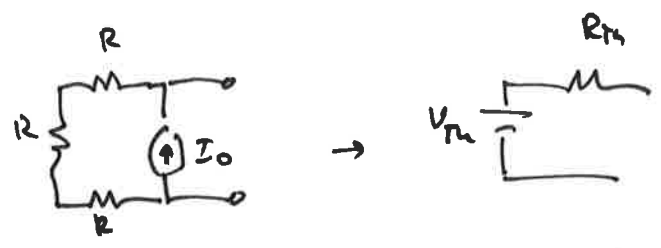


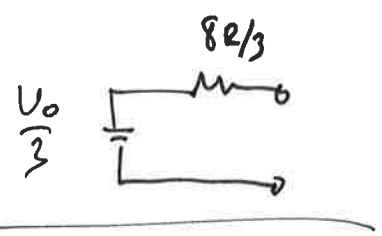
$R_{TH} = 2R + \frac{2R}{3} = \frac{8R}{3}$



V_{TH} : Spannung: $V_{TH} = I_0 \cdot 3R$

R_{TH} : Nullstell I_0
(Ausschalt!)

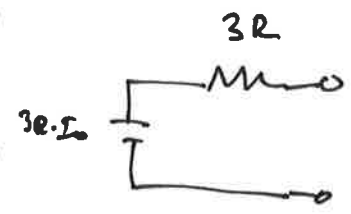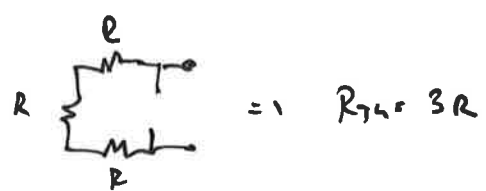

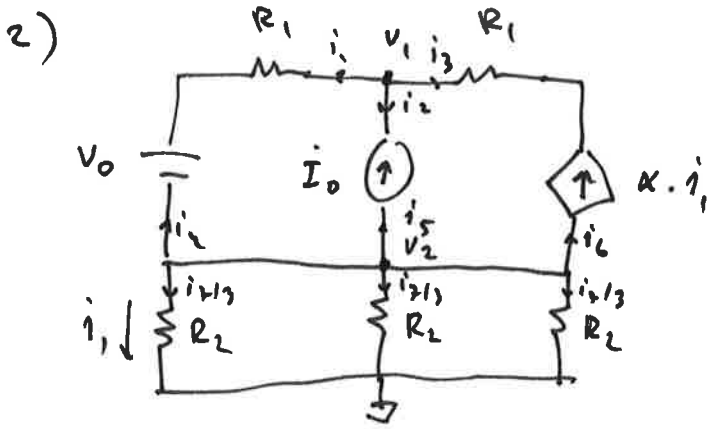

KCL nod 1) $i_1 + i_2 + i_3 = 0 \Rightarrow \frac{V_1 - V_0 - V_2}{R_1} - i_0 - \alpha \cdot i_1 = 0$


KCL nod 2) $i_4 + i_5 + i_6 + 3 \cdot \frac{i_3}{3} = 0 \Rightarrow \frac{V_2 + V_0 - V_1}{R_1} + i_0 + \alpha i_1 + \frac{V_2 \cdot 3}{R_2} = 0$

$i_1 = \frac{V_2}{R_2}$ Für eliminierung von i_1 .



1) $\frac{V_1}{R_1} - \frac{V_2}{R_1} - \frac{V_0}{R_1} - i_0 - \alpha \cdot \frac{V_2}{R_2} = 0 \Rightarrow \frac{1}{R_1} \cdot V_1 + \left(-\frac{1}{R_1} + \frac{\alpha}{R_2} \right) \cdot V_2 = i_0 + \frac{V_0}{R_1}$

2) $-\frac{V_1}{R_1} + \frac{V_2}{R_1} + \frac{V_2 \cdot 3}{R_2} + \frac{V_0}{R_1} + i_0 + \frac{\alpha V_2}{R_2} = 0 \Rightarrow \left(\frac{-1}{R_1} \right) \cdot V_1 + \left(\frac{1}{R_1} + \frac{3 + \alpha}{R_2} \right) \cdot V_2 = -i_0 - \frac{V_0}{R_1}$


3)

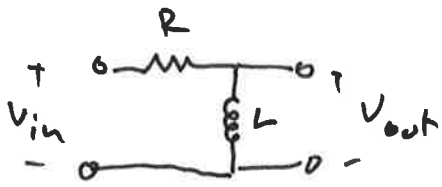
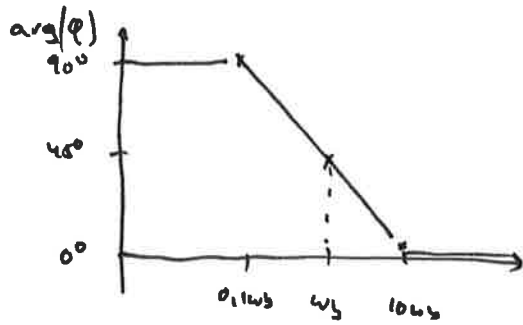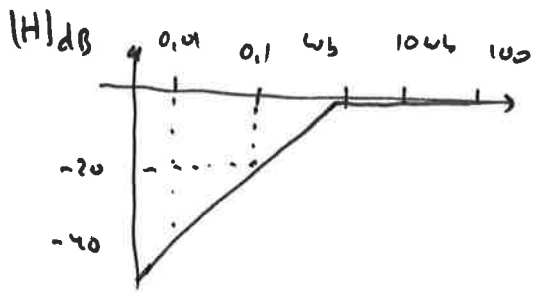
$$\omega_B = \frac{R}{L} = 1 \quad L = \frac{R}{\omega_B} = \frac{10^3}{10^6} = \underline{\underline{1 \text{ mH}}}$$




9)

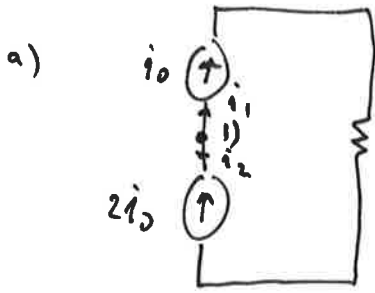


KCC på nod 1): $i_1 + i_2 = 0 \Rightarrow i_0 - 2i_0 = 0$ vilket ej kan uppfyllas! Kretsen skulle alltså brytas mot KCC.


b)

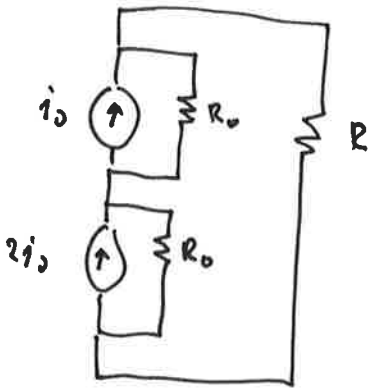

Superposition.

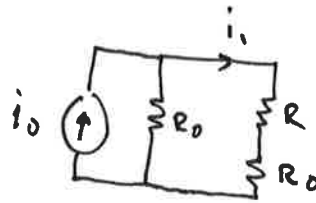

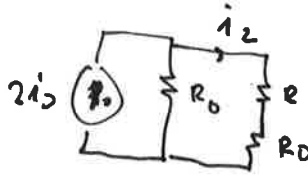
$$i_1 = i_0 \cdot \frac{R_0}{R + R_0 + R_0} = \frac{i_0}{2}$$




$$i_2 = 2i_0 \cdot \frac{R_0}{R + R_0 + R_0} = i_0$$

$$\rightarrow i_R = i_1 + i_2 = \underline{\underline{\frac{3i_0}{2}}}$$

5)

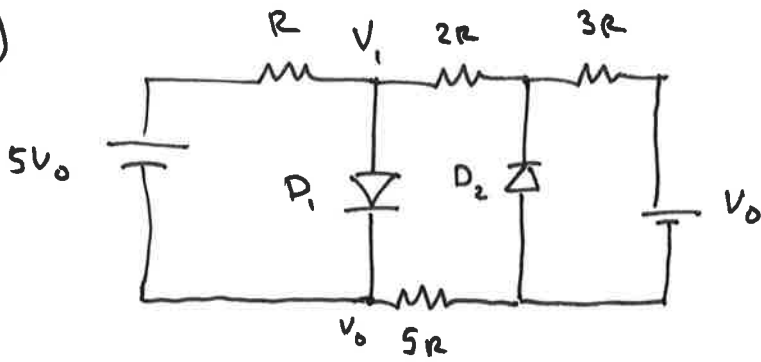

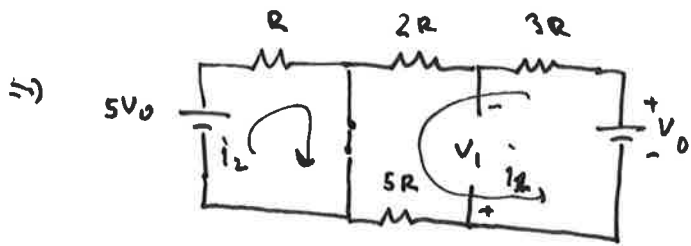$V_1 > V_0$, gissen att D_1 är framspänd! D_2 bör vara backspänd.



Ev superposition, eller KVL:


$$i_2 = \frac{V_0}{2R + 3R + 5R} = \frac{V_0}{10R} \quad (i_L = \frac{5V_0}{R})$$

Kontroll: D_1 : i_1 eller $i_2 > 0$ ok!

$$V_1 = 0 - (V_0 - i_1 \cdot 3R) = -V_0 + \frac{3V_0 R}{10R} = -V_0 \left(1 - \frac{3}{10}\right) < 0!$$

ok, D_2 backspänd!

6)

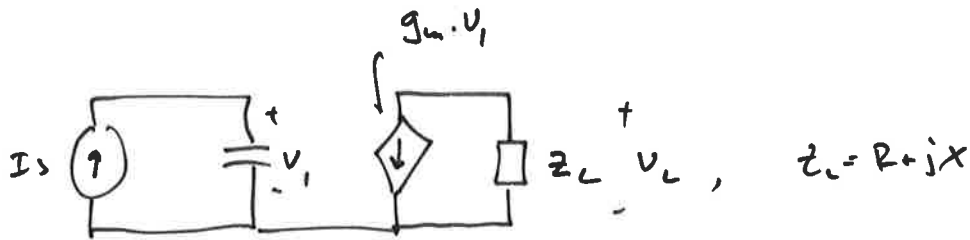

a) $V_L = -g_m \cdot V_1 \cdot z_L$
 $V_1 = \frac{I_s}{j\omega C}$ $\Rightarrow H = \frac{V_L}{I_s} = \frac{-g_m \cdot (R + jX)}{j\omega C} = \frac{g_m (-X + jR)}{\omega C}$

b) $H = \frac{g_m}{\omega C} \sqrt{X^2 + R^2} \cdot e^{j \arctan \frac{R}{X}}$

$\arctan(0) = 0 \Rightarrow \underline{R=0}$

Fasen
~~Delta~~ blir egentligen
~~arctan~~ $\pi = \arctan \frac{R}{|X|}$ di
~~kasen~~ $\text{imag } |H| \leq 0!$
 Villket ser en förskjutning pi
 π di exo.. Delta var inte
 viktigt menigen...

c) $|H|$ oberoende av ω ? R, C eller L?

$|H| = \frac{g_m}{\omega C} \sqrt{X^2 + R^2} = v \cdot l; R=0, X = \omega L \text{ (induktans!)}$
 $= \frac{g_m}{\omega C} (\omega L)^2 = \underline{\underline{\frac{g_m \cdot L}{C}}}$

Du ser $v \cdot l; z_L$ som en kondensator!