

Solutions to
Exam in
Analog IC Design

2007-10-20

Henrik Sjöland

$$1) \quad a) \quad R = R_D \cdot \frac{L}{W} \quad I = \frac{3V}{R} = \frac{3V \cdot W}{L \cdot R_D} \quad I_{max} = J \cdot W$$

$$I = I_{max} \Rightarrow \frac{3V \cdot W}{L \cdot R_D} = J \cdot W \Rightarrow L = \frac{3V}{R_D \cdot J}$$

$$\text{poly 1: } L_{\text{poly1}} = \frac{3V}{R_{sp} \cdot J_p} = \frac{3V}{6.52 \cdot 0.5 \text{ mA}/\mu\text{m}} = \frac{3}{6 \cdot 0.5 \cdot 10^{-3}} \mu\text{m} = \underline{1000 \mu\text{m}}$$

$$\text{poly 2: } L_{\text{poly2}} = \frac{3}{50 \cdot 0.3 \cdot 10^{-3}} \mu\text{m} = \underline{200 \mu\text{m}}$$

b) The length is chosen so that $I = I_{max} \Rightarrow I = J \cdot W$

$$\text{poly 1: } I = J_p \cdot W = 0.5 \text{ mA}/\mu\text{m} \cdot 1 \mu\text{m} = \underline{0.5 \text{ mA}}$$

$$\text{poly 2: } I = J_{p2} \cdot W = 0.3 \text{ mA}/\mu\text{m} \cdot 1 \mu\text{m} = \underline{0.3 \text{ mA}}$$


c) Poly 2 is best. Smallest size and least current.

$$2) \quad a) \quad I_{Dp} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_p (V_{GS} - V_{Tpp})^2 = \frac{1}{2} \cdot 40 \cdot 30 \cdot (-0.8 + 0.6)^2 \mu\text{A} = 24 \mu\text{A}$$

$$I_{Dn} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{IN} - V_{Tno})^2 = \frac{1}{2} \cdot 115 \cdot 10 \cdot (V_G - V_{Tno})^2 \mu\text{A}$$

$$I_{Dn} = I_{Dp} \Rightarrow V_{IN} - V_{Tno} = \sqrt{\frac{24}{\frac{1}{2} \cdot 115 \cdot 10}} = 0.204 \Rightarrow V_{IN} = 0.46 + 0.204 \text{ V} = \underline{0.66 \text{ V}}$$

b)

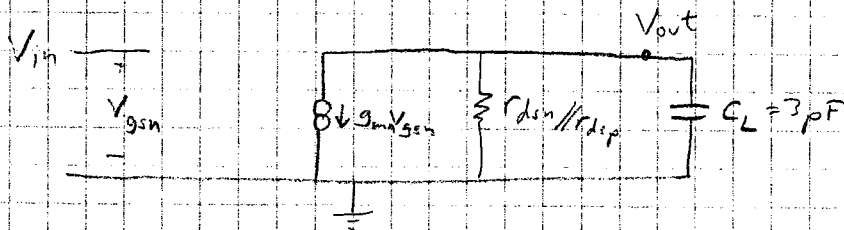


$$c) \quad g_{mn} = \frac{2I_D}{V_{ovn}} = \frac{48 \mu\text{A}}{0.204 \text{ V}} = 235 \mu\text{S} \quad r_{ds} = r_{dsp} = 55 \frac{\Omega}{\mu\text{m}} \cdot \frac{1 \mu\text{m}}{24 \mu\text{A}} = 2.3 \text{ M}\Omega$$

$$A_{v,dc} = -g_{mn} \cdot r_{ds} \parallel r_{dsp} = \underline{-270} \quad \omega_{-3dB} = \frac{1}{C_L \cdot r_{ds} \parallel r_{dsp}} = \underline{0.29 \text{ Mrad/s}} = \underline{46 \text{ kHz}}$$

$$\omega_{ta} = \frac{g_m}{C_L} = \underline{78 \text{ Mrad/s}} = \underline{12 \text{ MHz}}$$

3)

a)

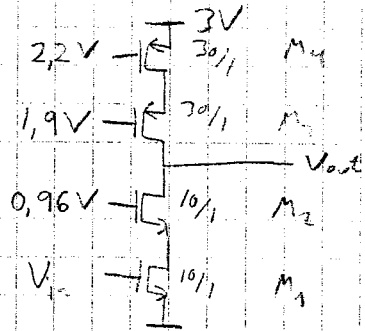

By choosing the same size of the transistors, and since they all have the same DC current, the overdrive will be the same $= 0,2V$.

At least $0,2V$ $V_{DS} = V_{ov}$ is needed to keep M_3 & M_4 in active region.

Therefore the gate voltage of M_3 should be at least $0,2V$ below that of M_4 . To give margin for body effect it is chosen $0,3V$ below, at $1,9V$. Same with $V_{G2} > V_{G1} + 0,3V$
 $V_{G2} = V_{G1} + 0,3V = 0,96V$ is chosen.

b)

$$R_o \approx g_{m2} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4}$$

$$g_{m2} = \frac{2I_D}{V_{ov2}} = 235 \mu S \quad g_{m3} = \frac{2I_D}{V_{ov}} = \frac{48 \mu A}{0,2V} = 240 \mu S$$

$$r_{o1} = r_{o2} = r_{o3} = r_{o4} = 2,3 M\Omega \quad (\text{from previous problem})$$

$$R_o \approx 235 \cdot 2,3 \cdot 2,3 M\Omega \parallel 240 \cdot 2,3 \cdot 2,3 M\Omega = 1,246 \Omega \parallel 1,274 \Omega = 0,636 \Omega$$

$$A_{v,dc} = -g_{m1} \cdot R_o = -235 \mu S \cdot 630 M\Omega = -235 \cdot 157 = -1,5 \cdot 10^5$$

c)

The output range is limited by M_2 and M_3 having to stay in the active regions:

$$V_{G2} - V_{tn} < V_{out} < V_{G3} - V_{tp} \Rightarrow 0,96 - 0,46 < V_{out} < 1,9 + 0,6 \Rightarrow$$

$$0,5V < V_{out} < 2,5V$$

(this is a slight underestimation, the body-effect will make the range slightly larger)

4)

a)

$$V_{ov} = V_{GS} - V_{th0} = 1 - 0,46 = 0,54 \text{ V}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2 = \frac{1}{2} \cdot 115 \cdot 10^{-6} \cdot 10 \cdot 0,54^2 = 168 \mu\text{A}$$

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2 \cdot 168 \mu\text{A}}{0,54 \text{ V}} = \underline{621 \mu\text{S}}$$

$$g_{ds} = \frac{1}{r_{ds}} = \frac{1}{55 \cdot \frac{1}{168 \cdot 10^{-6}}} = \frac{168}{55} \mu\text{S} = \underline{3,05 \mu\text{S}}$$

b)

$$V_t = V_{t0} + \gamma_n \left[\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right] =$$

$$= 0,46 \text{ V} + 0,58 \cdot \left[\sqrt{0,79 + 1} - \sqrt{0,79} \right] = 0,72 \text{ V}$$

$$V_{ov} = V_{GS} - V_t = 1 - 0,72 \text{ V} = 0,28 \text{ V}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2 = \frac{1}{2} \cdot 115 \cdot 10^{-6} \cdot 10 \cdot 0,28^2 = 45 \mu\text{A}$$

$$g_m = \frac{2I_D}{V_{ov}} = \frac{90 \mu\text{A}}{0,28 \text{ V}} = \underline{321 \mu\text{S}}$$

$$g_{ds} = \frac{1}{r_{ds}} = \frac{1}{55 \cdot \frac{1}{45 \cdot 10^{-6}}} = \frac{45}{55} \mu\text{S} = \underline{0,82 \mu\text{S}}$$

c)

$$V_{DS} = 0 \Rightarrow I_D = 0 \Rightarrow g_m = \frac{2I_D}{2V_{GS}} = 0 \quad (\text{deep triode})$$

$$g_{ds} = \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{V_{DS}=0} = g_{d0} = \mu_n C_{ox} \frac{W}{L} V_{ov} = 115 \cdot 10^{-6} \cdot 10 \cdot (2 - 0,46) =$$

$$= \underline{1,77 \text{ mS}}$$

1)

$$I_1 = I_{D5} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_5 (V_{GS5} - V_{tp0})^2 = 20 \mu \cdot 40 \cdot 0,2^2 = 32 \mu A$$

$$I_2 = I_{D5} \cdot \left(\frac{W}{L}\right)_7 / \left(\frac{W}{L}\right)_5 = 32 \mu A \cdot 5 = 160 \mu A$$

$$I_{TOT} = I_1 + I_2 = 192 \mu A$$

$$g_{m1} = \frac{2I_{D1}}{V_{ov1}} = \frac{I_2}{V_{ov6}} = \frac{32 \mu A}{0,2 V} = 160 \mu S$$

$$\omega_{t3} = \frac{g_{m1}}{C_c} = \frac{160 \cdot 10^{-6}}{1 \cdot 10^{-12}} = 160 \text{ Mrad/s} \quad (f_{t3} = \frac{160 M}{2\pi} = 25 \text{ MHz})$$

$$r_{ds4} = 55 \Omega \cdot \frac{1}{I_1/2} = \frac{55}{16} \text{ M}\Omega = 3,4 \text{ M}\Omega = r_{ds2}$$

$$A_{v1,dc} = g_{m1} \cdot r_{ds2} // r_{ds4} = 275$$

$$g_{m5} = \sqrt{2 I_{D5} \mu_n C_{ox} \left(\frac{W}{L}\right)_5} = \sqrt{2 \cdot 160 \mu \cdot 115 \mu \cdot 50} = 1,36 \text{ mS}$$

$$r_{ds5} = r_{ds7} = \frac{55 \cdot 1}{160 \cdot 10^{-6}} = 344 \text{ k}\Omega$$

$$A_{v2,dc} = g_{m5} \cdot r_{ds5} // r_{ds7} = 234$$

$$A_{v,dc} = A_{v1,dc} \cdot A_{v2,dc} = 275 \cdot 234 = 64 \cdot 10^3$$

$$SR_L = \pm \frac{I_1}{C_c} = \pm \frac{32 \mu A}{1 \text{ pF}} = \pm 32 \text{ V/\mu s} \quad (\text{input stage limited})$$

$$SR_R = \frac{I_2}{C_c + C_L} = \frac{160 \mu A}{3 \text{ pF}} = 53 \text{ V/\mu s} \quad (\text{output stage not limiting})$$

b)

$$P_2 \approx - \frac{g_{m5}}{C_L} = - \frac{1,36 \text{ m}}{2 \text{ p}} = -680 \text{ Mrad/s}$$

$$Z = \frac{1}{\left(\frac{1}{g_{m5}} - P_2\right) C_c} = \frac{1}{(735 - 2000) \cdot 1 \cdot 10^{-12}} = 790 \text{ Mrad/s}$$

$$\varphi_m = 90^\circ - \arctan\left(\frac{160}{680}\right) + \arctan\left(\frac{160}{790}\right) = 90^\circ - 13,2^\circ + 11^\circ = 88^\circ$$

As C_L increases p_2 will drop, $\varphi_m = 60^\circ$ reached when

$$\arctan\left(\frac{160 \text{ m}}{P_2}\right) = (90^\circ - 60^\circ) + 11^\circ = 41^\circ \Rightarrow P_2 = -184 \text{ Mrad/s}$$

$$P_2 \approx - \frac{g_{m5}}{C_L} \Rightarrow C_L \approx - \frac{g_{m5}}{P_2} = - \frac{1,36 \text{ m}}{-184 \text{ M}} = 7,4 \text{ pF}$$