

Solutions to  
Exam in  
Integrated Radio Electronics

March 2004

Henrik Sjöland

1.

$$L = \frac{37,5 \cdot \mu_0 \cdot n^2 \cdot a^2}{22r - 14a}$$

$$n=1 \Rightarrow r=a=50 \mu\text{m} \Rightarrow L = \frac{37,5 \cdot 4\pi \cdot 10^{-7} \cdot 1^2 \cdot (50 \mu\text{m})^2}{8 \cdot 50 \mu\text{m}} = 0,29 \text{ nH}$$

$$n=2 \Rightarrow r=60 \mu\text{m}, a=55 \mu\text{m} \Rightarrow L = \frac{37,5 \cdot 4\pi \cdot 10^{-7} \cdot 2^2 \cdot (55 \mu\text{m})^2}{22 \cdot 60 \mu\text{m} - 14 \cdot 55 \mu\text{m}} = 1,0 \text{ nH}$$

$$n=4 \Rightarrow r=80 \mu\text{m}, a=65 \mu\text{m} \Rightarrow L = \frac{37,5 \cdot 4\pi \cdot 10^{-7} \cdot 4^2 \cdot (65 \mu\text{m})^2}{22 \cdot 80 \mu\text{m} - 14 \cdot 65 \mu\text{m}} = 3,7 \text{ nH}$$

$$n=8 \Rightarrow r=120 \mu\text{m}, a=85 \mu\text{m} \Rightarrow L = \frac{37,5 \cdot 4\pi \cdot 10^{-7} \cdot 8^2 \cdot (85 \mu\text{m})^2}{22 \cdot 120 \mu\text{m} - 14 \cdot 85 \mu\text{m}} = 15 \text{ nH}$$

b)

$$f_s = \frac{1}{2\pi \sqrt{L C_{ox}/2}}, \quad C_{ox} = W \cdot l \cdot \frac{\epsilon_{ox}}{t_{ox}}, \quad l = 8 \cdot n \cdot a$$

$$n=1 \Rightarrow l = 8 \cdot 1 \cdot 50 \mu\text{m} = 400 \mu\text{m}, \quad C_{ox} = 8 \mu\text{m} \cdot 400 \mu\text{m} \cdot \frac{8,85 \cdot 10^{-12} \cdot 3,9}{5 \mu\text{m}} = 22 \text{ fF} \Rightarrow$$

$$f_s = \frac{1}{2\pi \sqrt{0,29 \text{ nH} \cdot 22 \text{ fF}/2}} = 89 \text{ GHz}$$

$$n=2 \Rightarrow l = 8 \cdot 2 \cdot 55 \mu\text{m} = 880 \mu\text{m}, \quad C_{ox} = 8 \mu\text{m} \cdot 880 \mu\text{m} \cdot \frac{8,85 \cdot 10^{-12} \cdot 3,9}{5 \mu\text{m}} = 48 \text{ fF} \Rightarrow$$

$$f_s = \frac{1}{2\pi \sqrt{1,0 \text{ nH} \cdot 48 \text{ fF}/2}} = 32 \text{ GHz}$$

$$n=4 \Rightarrow l = 8 \cdot 4 \cdot 65 \mu\text{m} = 2080 \mu\text{m}, \quad C_{ox} = 8 \mu\text{m} \cdot 2080 \mu\text{m} \cdot \frac{8,85 \cdot 10^{-12} \cdot 3,9}{5 \mu\text{m}} = 115 \text{ fF} \Rightarrow$$

$$f_s = \frac{1}{2\pi \sqrt{3,7 \text{ nH} \cdot 115 \text{ fF}/2}} = 11 \text{ GHz}$$

$$n=8 \Rightarrow l = 8 \cdot 8 \cdot 85 \mu\text{m} = 5440 \mu\text{m}, \quad C_{ox} = 8 \mu\text{m} \cdot 5440 \mu\text{m} \cdot \frac{8,85 \cdot 10^{-12} \cdot 3,9}{5 \mu\text{m}} = 301 \text{ fF} \Rightarrow$$

$$f_s = \frac{1}{2\pi \sqrt{15 \text{ nH} \cdot 301 \text{ fF}/2}} = 3,3 \text{ GHz}$$

c)

$$Q = \frac{W L}{R_s}, \quad R_s = \frac{l \rho}{W \delta (1 - e^{-l/\delta})}, \quad \delta = \sqrt{\frac{2\rho}{\omega \mu_0}} = \sqrt{\frac{2 \cdot 27 \cdot 10^{-9}}{2\pi \cdot 2 \cdot 10^9 \cdot 4\pi \cdot 10^{-7}}} = 1,85 \mu\text{m}$$


$$R_s = l \cdot \frac{27 \cdot 10^{-9}}{8 \cdot 10^{-6} \cdot 1,85 \cdot 10^{-6} \cdot (1 - e^{-2/1,85})} = l \cdot 2,76 \text{ k}\Omega$$

$$n=1 \Rightarrow R_s = 400 \mu\text{m} \cdot 2,76 \text{ k}\Omega/\mu\text{m} = 1,1 \Omega, \quad Q = \frac{2\pi \cdot 2 \cdot 10^9 \cdot 0,29 \cdot 10^{-9}}{1,1} = 3,3$$

$$n=2 \Rightarrow R_s = 880 \mu\text{m} \cdot 2,76 \text{ k}\Omega/\mu\text{m} = 2,4 \Omega, \quad Q = \frac{2\pi \cdot 2 \cdot 10^9 \cdot 1,0 \cdot 10^{-9}}{2,4} = 5,2$$

$$n=4 \Rightarrow R_s = 2080 \mu\text{m} \cdot 2,76 \text{ k}\Omega/\mu\text{m} = 5,7 \Omega, \quad Q = \frac{2\pi \cdot 2 \cdot 10^9 \cdot 3,7 \cdot 10^{-9}}{5,7} = 8,2$$
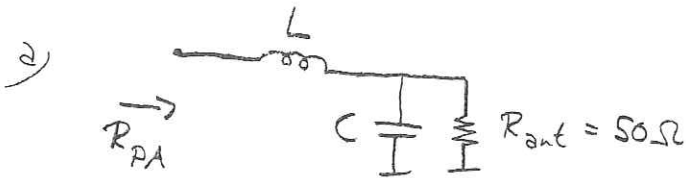
$$n=8 \Rightarrow R_s = 5440 \mu\text{m} \cdot 2,76 \text{ k}\Omega/\mu\text{m} = 15 \Omega, \quad Q = \frac{2\pi \cdot 2 \cdot 10^9 \cdot 15 \cdot 10^{-9}}{15} = 13$$



$$Q = \sqrt{\frac{R_{ant}}{R_{PA}} - 1} = \sqrt{\frac{50}{5,0} - 1} = 3,0$$

$$Q = \omega_0 R_{ant} C \Rightarrow C = \frac{Q}{\omega_0 R_{ant}} = \frac{3}{2\pi \cdot 2 \cdot 10^9 \cdot 50} = 4,8 \text{ pF}$$

$$L = \frac{1}{\omega_0^2 C} = \frac{1}{(2\pi \cdot 2 \cdot 10^9)^2 \cdot 4,8 \cdot 10^{-12}} = 1,3 \text{ nH}$$

b)  $R_{ant} = 30 \Omega$

$$Q = \omega_0 R_{ant} C = 1,8$$

$$R_{PA} = \frac{R_{ant}}{Q^2 + 1} = \frac{30}{1,8^2 + 1} = 7,1 \Omega$$

$R_{ant} = 100 \Omega$

$$Q = \omega_0 R_{ant} C = 6$$

$$R_{PA} = \frac{R_{ant}}{Q^2 + 1} = \frac{100}{6^2 + 1} = 2,7 \Omega$$

c)  $R_{ant} = 30 \Omega$

$$V_{PA} = 4V_{PP} \Rightarrow I_{PA} = \frac{4V_{PP}}{7,1 \Omega} = 560 \text{ mA}_{PP} < 800 \text{ mA} \Rightarrow \text{voltage limited}$$

$$P = \frac{V_{PA, pk}^2}{2R_{PA}} = \frac{(2V_P)^2}{2 \cdot 7,1} = 0,28 \text{ W}$$

$R_{ant} = 50 \Omega$

$$V_{PA} = 4V_{PP} \Rightarrow I_{PA} = \frac{4V_{PP}}{5 \Omega} = 800 \text{ mA}_{PP} \Rightarrow \text{limited in voltage and current simultaneously. (optimum power)}$$

$$P = \frac{V_{PA, pk}^2}{2R_{PA}} = \frac{2^2}{2 \cdot 5} = 0,40 \text{ W}$$

$R_{ant} = 100 \Omega$

$$V_{PA} = 4V_{PP} \Rightarrow I_{PA} = \frac{4V_{PP}}{2,7 \Omega} = 1,5 \text{ A} > 800 \text{ mA} \Rightarrow \text{current limited}$$

$$(\Rightarrow V_{PA} = 800 \text{ mA}_{PP} \cdot 2,7 \Omega = 2,16 \text{ V}_{PP})$$

$$P = I_{PA, pk}^2 \cdot R_{PA} / 2 = 0,4^2 \cdot \frac{2,7}{2} = 0,22 \text{ W}$$

3

$$a) R_L = \omega_0 L Q = 2\pi \cdot 1,8 \cdot 10^9 \cdot 8 \cdot 10^{-9} \cdot 12 = 1,09 \text{ k}\Omega \quad (\text{per side})$$

$$P_{sig} = 2 \cdot \frac{V_{sig}^2}{2R_L} = \frac{V_{sig}^2}{1,09 \text{ k}\Omega}$$

$$L(\Delta f) = 10 \cdot \log \left[ \frac{2FkT}{P_{sig}} \cdot \left( \frac{f_0}{2Q \cdot \Delta f} \right)^2 \right] = -138 \text{ dBc/Hz} @ 3 \text{ MHz } \Delta f \Rightarrow$$

$$P_{sig} = \frac{2FkT}{10^{-13,8}} \cdot \left( \frac{f_0}{2Q \cdot \Delta f} \right)^2 = \frac{2 \cdot 3 \cdot 4,2 \cdot 10^{-21}}{10^{-13,8}} \cdot \left( \frac{1800}{2 \cdot 12 \cdot 3} \right)^2 = 1,0 \text{ mW} \Rightarrow$$

$$V_{sig} = \sqrt{1,0 \text{ mW} \cdot 1,09 \text{ k}\Omega} = 1,04 \text{ V}$$

$$0,5 \text{ V margin} \Rightarrow V_{dd} = 1,04 + 0,5 = 1,54 \text{ V} \Rightarrow \text{choose } V_{dd} = 1,6 \text{ V}$$

$$V_{sig} = I_{dc} \cdot \frac{2}{\pi} \cdot R_L \Rightarrow I_{dc} = \frac{1,04 \text{ V} \cdot \pi}{2 \cdot 1,09 \text{ k}\Omega} = 1,5 \text{ mA}$$

b) Varactor

$$f_{high} = 1,8 \text{ GHz} + 7\% = 1,93 \text{ GHz} \quad f_{low} = 1,8 \text{ GHz} - 7\% = 1,67 \text{ GHz}$$

$$C_{tot \max} = \frac{1}{(2\pi)^2 L f_{low}^2} = 1,14 \text{ pF/side} \quad C_{tot \min} = \frac{1}{(2\pi)^2 L f_{high}^2} = 0,85 \text{ pF/side}$$

$$C_{var \max} - C_{var \min} = C_{tot \max} - C_{tot \min} = 1,14 \text{ pF} - 0,85 \text{ pF} = 0,29 \text{ pF}$$

$$\frac{C_{var \max}}{C_{var \min}} = 2 \Rightarrow C_{var \max} \left(1 - \frac{1}{2}\right) = 0,29 \text{ pF} \Rightarrow C_{var \max} = 0,58 \text{ pF}$$

$$C_{var \max} = WL(C_{ox} + 2WC_{gdo}) \Rightarrow W = \frac{C_{var \max}}{LC_{ox} + 2C_{gdo}} = \frac{580}{0,4 \cdot 4,6 + 2 \cdot 0,21} \text{ }\mu\text{m} = 256 \text{ }\mu\text{m}$$

$$C_{rest} = C_{tot \max} - C_{var \max} = 1,14 - 0,58 = 0,56 \text{ pF}$$

$$C_{ind, par} = \frac{1}{(2\pi)^2 L f_s^2} = \frac{1}{(2\pi)^2 \cdot 8 \cdot 10^9 \cdot (4 \text{ GHz})^2} = 0,20 \text{ pF} \quad (\text{parasitics of inductor})$$

$$C_{transistor, par} = C_{rest} - C_{ind, par} = 0,36 \text{ pF}$$

$$C_{transistor, par} = C_{gs} + C_{db} + 4C_{gd} = \frac{2}{3}WL(C_{ox} + WC_{gdo}) + \frac{W}{2} \cdot 1,1 \cdot C_{jn} + 4WC_{gd} =$$

$$= W(\text{ }\mu\text{m}) \cdot \left( \frac{2}{3} \cdot 0,4 \cdot 4,6 + 0,21 + 0,55 \cdot 0,93 + 4 \cdot 0,21 \right) \text{ fF} = W \cdot 2,8 \text{ fF/}\mu\text{m} \Rightarrow$$

$$W = 360 \text{ fF} / 2,8 \text{ fF/}\mu\text{m} = 130 \text{ }\mu\text{m}$$

$$\underline{\text{Tail transistor}}: W = L \cdot \frac{2I_d}{\mu C_{ox} V_{od}^2} = 0,4 \cdot \frac{2 \cdot 1,5 \text{ mA}}{110 \mu\text{m} \cdot 0,25^2} \text{ }\mu\text{m} = 175 \text{ }\mu\text{m}$$

$$V_{bias} = V_{T_0} + V_{od} = 0,70 \text{ V}$$

$$g) g_{m, startup} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \sqrt{2 \cdot 110 \cdot 10^{-6} \cdot \frac{130}{0,4} \cdot \frac{1,5 \text{ mA}}{2}} = 7,3 \text{ mS}$$

$$A_{L, startup} = g_{m, startup} \cdot R_L = 7,3 \text{ mS} \cdot 1,09 \text{ k}\Omega = 8 > 3 \quad \underline{OK}$$

$$A_{L, startup} = 8, \quad V_{bias} = 0,70 \text{ V}$$

Results:  $V_{dd} = 1,6 \text{ V}$ ,  $I_{dc} = 1,5 \text{ mA}$ ,  $W_{var} = 256 \text{ }\mu\text{m}$ ,  $W_{sw} = 130 \text{ }\mu\text{m}$ ,  $W_{tail} = 175 \text{ }\mu\text{m}$

4. a)

$$Q_{in} = \frac{1}{2\omega_0 R_s C_{gs}} \Rightarrow C_{gs} = \frac{1}{2\omega_0 R_s Q_{in}} = \frac{1}{2 \cdot 2\pi \cdot 1,575 \cdot 10^9 \cdot 50 \cdot 1,5} = 670 \text{ fF}$$

$$C_{gs} = W C_{gdo} + \frac{2}{3} W L C_{ox} \Rightarrow W = \frac{C_{gs}}{C_{gdo} + \frac{2}{3} L C_{ox}} = \frac{670}{0,21 + \frac{2}{3} \cdot 0,4 \cdot 4,60} = 470 \text{ } \mu\text{m}$$

$$I_d = \frac{1}{2} \mu C_{ox} \frac{W}{L} V_{od}^2 \Rightarrow V_{od} = \sqrt{\frac{2I_d}{\mu C_{ox} \frac{W}{L}}} = \sqrt{\frac{2 \cdot 1,5 \text{ mA}}{110 \cdot 10^{-6} \cdot \frac{470}{0,4}}} = 152 \text{ mV}$$

$$g_m = \frac{2I_d}{V_{od}} = \frac{3 \text{ mA}}{152 \text{ mV}} = 19,7 \text{ mS}$$

$$R_{in} = g_m \frac{L_s}{C_{gs}} \Rightarrow L_s = \frac{R_{in} C_{gs}}{g_m} = \frac{50 \cdot 670 \cdot 10^{-15}}{19,7 \cdot 10^{-3}} = 1,7 \text{ nH}$$

$$L_g = \frac{1}{\omega_0^2 C_{gs}} - L_s = 13,5 \text{ nH}$$

$$V_g = V_{r_s} + V_{od} = 652 \text{ mV}$$

$$F = 1 + \frac{(\delta/5) \cdot (Q^2 + 1) + \delta/4}{R_s Q^2 g_m} = 1 + \frac{(2,8/5) \cdot 3,25 + 1,4/4}{50 \cdot 2,8 \cdot 19,7 \cdot 10^{-3}} = 1,98 = 3,0 \text{ dB}$$

$$V_{G, \text{cascode}} = V_{s, \text{cascode}} + V_t + V_{od} = V_{od} + 0,3 \text{ V} + V_t + V_{od} = 1,1 \text{ V}$$

b)  $C_{d, \text{cascode}} = C_{db, \text{cascode}} + C_{dg, \text{cascode}}$

$$C_{db, \text{cascode}} = \frac{C_{db0}}{(1 + V_{dd}/V_t)^{m_j}} = \frac{\frac{W}{2} \cdot 1,1 \cdot 0,93 \text{ fF}}{(1 + 2/0,69)^{0,31}} = 158 \text{ fF}$$

$$C_{dg, \text{cascode}} = W \cdot C_{gdo} = 470 \cdot 0,21 \text{ fF} = 99 \text{ fF}$$

$$C_L = 150 \text{ fF} \Rightarrow C_{\text{except coil}} = 158 + 150 + 99 = 407 \text{ fF}$$

$$R_L = \omega_0 L \cdot Q \sim L \cdot \frac{1}{\sqrt{L}} \sim \sqrt{L} \Rightarrow \text{higher } L \text{ is better}$$

choose max L that gives sufficient frequency:

$$C_{\text{tot}} = \frac{1}{\omega_0^2 L}, \quad C_{\text{tot}} = C_{\text{except coil}} + C_{\text{coil}} = 407 \text{ fF} + \frac{1}{\omega_s^2 L} \Rightarrow$$

$$\frac{1}{\omega_0^2 L} = \frac{1}{\omega_s^2 L} + 407 \text{ fF} \Rightarrow \frac{1}{\omega_0^2 L} = \frac{L}{(20 \text{ Hz}/\text{H} \cdot 2\pi)^2} + 407 \text{ f} \Rightarrow$$

$$L^2 + 407 \text{ f} \cdot (20 \cdot 2\pi)^2 L - \frac{(20 \cdot 2\pi)^2}{(2\pi \cdot 1,575 \cdot 10^9)^2} = 0 \Rightarrow L = -3,2 \text{ nH} \pm \sqrt{(3,2)^2 + 1,61 \cdot 10^{-16}} =$$

$$= 9,9 \text{ nH} \Rightarrow Q_L = \frac{20}{\sqrt{9,9}} = 6,36, \quad f_s = \frac{20 \text{ GHz}}{9,9} = 2,02 \text{ GHz}$$

(check:  $C_{\text{coil}} = \frac{1}{\omega_s^2 L} = 627 \text{ fF} \Rightarrow C_{\text{tot}} = 407 + 627 = 1,03 \text{ pF} \Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}} = 1,575 \text{ GHz}$  ok)

$$A_v = 2Q_{in} g_m R_L = 2 \cdot 1,5 \cdot 19,7 \cdot 10^{-3} \cdot 6,36 \cdot 2\pi \cdot 1,575 \cdot 10^9 \cdot 9,9 \cdot 10^{-9} =$$

$$= 37 = 31 \text{ dB}$$

5. a)  $0,2V$  in  $\omega$  (cc)  $\Rightarrow$  choose  $V_{od, in} = 0,22$

$$g_{m, in} = \frac{2I_d}{V_{od}} = \frac{1mA}{0,22V} = 4,5mS$$

$$A_v = \frac{2}{\pi} \cdot g_m R_L \Rightarrow R_L = \frac{A_v}{\frac{2}{\pi} \cdot g_m} > \frac{1,78}{\frac{2}{\pi} \cdot 4,5m} = 0,62 k\Omega$$

$$V_{R_L} = I_{R_L} \cdot R_L = 0,15m \cdot 0,62k = 0,31V$$

$\nearrow$  neglect that  $V_{out} > V_{R_L}$ .  
Due to non-linearities.  
Assume pure 1F sinusoid.

$$V_{in} = 0,2V \Rightarrow V_{out} = 0,2 \cdot 1,78 = 0,36V$$

$$I_d = \frac{1}{2} \mu C_{ox} \frac{W}{L} V_{od}^2 \Rightarrow W = L \cdot \frac{2I_d}{\mu C_{ox} V_{od}^2} = 0,4\mu m \cdot \frac{1m}{110\mu \cdot 0,22^2} = 75\mu m$$

$$V_{G, in} = V_{to} + V_{od} = 0,72V$$

switches

$$\sqrt{2} V_{od, sw} = \sin(0,15 \cdot 90^\circ) \cdot 1V_{pk} = (V_{L1} = 1V_{pk, diff}) \Rightarrow V_{od, sw} = 0,16V$$

$$W_{sw} = L \cdot \frac{2I_d}{\mu C_{ox} V_{od, sw}^2} = 0,4\mu m \cdot \frac{0,5m}{110\mu \cdot 0,16^2} = 71\mu m$$

choose LO-bias voltage

$$\text{largest input voltage} \Rightarrow V_{od, in, max} = 0,2V + 0,22V = 0,42V$$

$$\text{at zero-crossing } V_{od, sw, max} = V_{od, in, max} \sqrt{\frac{W_{in}}{2W_{sw}}} = 0,31V$$

$$\Rightarrow V_{LO, bias} > 0,42 + 0,31 + V_T = 1,23V, \text{ choose } 1,25V$$

$$V_{LO, pk, high} = 1,25 + 0,5 = 1,75V$$

$$V_{IF, pk, low} = V_{dd} - 2V_{out} = 2 - 2 \cdot 0,36 = 1,28V$$

} diff =  $0,47V < 0,50 = V_T$   
 $\Rightarrow$  OK, small margin..

$\Rightarrow$  no switch transistor or input transistor will enter triode either at LO peak or zero-crossing  $\Rightarrow$  OK.

b)  $C_{in} = 2 \cdot C_{gs, in} + C_{routing} = 2 \cdot W_{in} \left( \frac{2}{3} LC_{ox} + C_{do} \right) + 50fF =$   
 $= 2 \cdot 75 \left( \frac{2}{3} \cdot 0,4 \cdot 4,6 + 0,21 \right) + 50 = 266 fF > 150 fF$

$$\omega_0 = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{9,9n \cdot (627 + 523)f}} = 1,492 GHz$$

$$\text{Frequency shift} = 1,575 GHz - 1,492 GHz = 83 MHz = 5\%$$

Result: The center frequency has moved 5% downwards.