


Solutions to
Written Exam in
Integrated Radio Electronics (ET1170)

2009-03-11

Henrik Sjöland


1.

a)

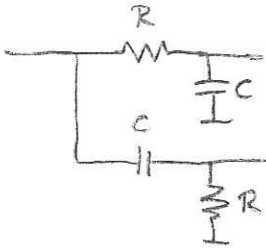

$$R = 200 \Omega$$
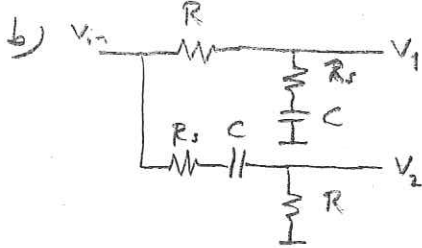
$$C = \frac{1}{2\pi f R} = \frac{1}{2\pi \cdot 5 \cdot 10^9 \cdot 200} = 159 \text{ fF}$$



$$V_1 = \frac{R_s + \frac{1}{sC}}{R + R_s + \frac{1}{sC}}$$

$$V_2 = \frac{R}{R + R_s + \frac{1}{sC}}$$

$$\frac{V_1}{V_2} = \frac{R_s + \frac{1}{sC}}{R} = \frac{10 + \frac{1}{j2\pi \cdot 5 \cdot 10^9 \cdot 159 \cdot 10^{-12}}}{200} = \frac{10 - j200}{200} = -j + 0,05 =$$

$$\left| \frac{V_1}{V_2} \right| = \sqrt{1^2 + 0,05^2} = 1,00125 \Rightarrow \text{amplitude error} = 0,125 \%$$

$$\arg\left(\frac{V_1}{V_2}\right) = -90^\circ + \arctan(0,05) = -90^\circ + 2,86^\circ \Rightarrow \text{phase error} = 2,86^\circ$$

c) $\epsilon = 0,00125$ before $\Rightarrow \epsilon = 0,00025$ after suppression

$$\Delta\phi = 2,86^\circ = 0,050 \text{ rad}$$

$$IRR = \frac{4}{\epsilon^2 + (\Delta\phi)^2} = \frac{4}{(0,00025)^2 + (0,050)^2} = 1,6 \cdot 10^3 = 32 \text{ dB}$$

$$2. \quad a. \quad R_g = \frac{1}{3} \cdot R_D \cdot \frac{W_{tot}}{L} \cdot \frac{1}{(\pi f_{in,par})^2} = \frac{1}{3} \cdot 6 \cdot \frac{100}{0,4} \cdot \frac{1}{64} = 7,8 \Omega$$

$$b. \quad R_{ndt} = \frac{l}{W \cdot \sigma \cdot \delta (1 - e^{-t/\delta})} \quad , \quad \delta = \sqrt{\frac{2}{W \rho_0 \sigma}}$$

$$\delta = \sqrt{\frac{2 \cdot 2,7 \cdot 10^{-8}}{2\pi \cdot 1,575 \cdot 10^9 \cdot 47 \cdot 10^{-7}}} = 2,08 \mu\text{m}$$

$$R_{ndt} = \frac{150 \cdot 10^{-6} \cdot 2,7 \cdot 10^{-8}}{10 \cdot 10^{-6} \cdot 2,08 \cdot 10^{-6} \cdot (1 - e^{-0,925/2,08})} = 0,54 \Omega$$

$$c. \quad NF_{no,par} = 2 \text{ dB} \Rightarrow F_{no,par} = 1,585$$

With parasitics:

$$F_{par} \approx F_{no,par} + \frac{R_{ndt} + R_s}{50 \Omega} = 1,585 + \frac{8,3}{50} = 1,747$$

$$NF_{pw} = 10 \cdot \log F_{pw} = 2,43 \text{ dB} < 2,5 \text{ dB} \Rightarrow$$

It still meets the specification

3. a Capacitances / side:

$$C_{\text{trans}} = C_{gs1} + 4C_{gd1} + C_{db1} = \frac{2}{3}WL C_{ox} + 5WC_{gd0} + \\ + \frac{w}{2} \cdot 1,2 \mu\text{m} \cdot C_{jn} \cdot \frac{1}{(1 + v_{dd}/V_{j1})^{m_j}} + 1,2 \mu\text{m} \cdot 8 C_{j\text{sp}} \cdot \frac{1}{(1 + v_{dd}/V_{sw})^{m_{sw}}} = \\ = 98 \text{ fF} + 84 \text{ fF} + 29 \text{ fF} + 2 \text{ fF} = 213 \text{ fF}$$

$$C_{\text{ind}} = \frac{1}{\omega_s^2 \cdot L} = \frac{1}{(2\pi \cdot 8 \cdot 10^9)^2 \cdot 5 \cdot 10^{-9}} = 79 \text{ fF}$$

$$C_{\text{var, max}} = WL C_{ox} + 2C_{sv} = 300 \cdot 0,5 \cdot 4,60 + 2 \cdot 300 \cdot 0,21 \text{ fF} = 816 \text{ fF}$$

$$C_{\text{var, min}} = C_{\text{var, max}} / 2,5 = 326 \text{ fF}$$

$$C_{\text{tot, max}} = C_{\text{trans}} + C_{\text{ind}} + C_{\text{load}} + C_{\text{var, max}} = 213 + 79 + 100 + 816 \text{ fF} = 1,2 \text{ pF}$$

$$C_{\text{tot, min}} = C_{\text{trans}} + C_{\text{ind}} + C_{\text{load}} + C_{\text{var, min}} = 718 \text{ fF}$$

Tuning range:

$$f_{\text{min}} = \frac{1}{2\pi \sqrt{L \cdot C_{\text{tot, max}}}} = 2,05 \text{ GHz}, \quad f_{\text{max}} = \frac{1}{2\pi \sqrt{L \cdot C_{\text{tot, min}}}} = 2,66 \text{ GHz}$$

b. First calculate parallel resistances:

$$R_{p, \text{ind}} = \omega L Q_{\text{ind}} = 644 \Omega @ f_{\text{min}}, \quad 836 \Omega @ f_{\text{max}}$$

$$R_{p, \text{trans}} = \frac{Q_{\text{trans}}}{\omega C_{\text{trans}}} = \frac{20}{2\pi f \cdot 213 \cdot 10^{-15}} = 7,3 \text{ k}\Omega @ f_{\text{min}}, \quad 5,6 \text{ k}\Omega @ f_{\text{max}}$$

$$R_{p, \text{var}} = \frac{Q_{\text{var}}}{\omega C_{\text{var}}} = \frac{30}{\omega_{\text{min}} \cdot C_{\text{var, max}}} = 2,85 \text{ k}\Omega @ f_{\text{min}}, \quad 5,5 \text{ k}\Omega @ f_{\text{max}}$$

$$R_{p, \text{load}} : Q_{\text{load}} = \frac{1}{\omega R_{\text{load}} C_{\text{load}}} = 155 @ f_{\text{min}}, \quad 120 @ f_{\text{max}}$$

$$R_{p, \text{load}} = \frac{Q_{\text{load}}}{\omega C_{\text{load}}} = 120 \text{ k}\Omega @ f_{\text{min}}, \quad 72 \text{ k}\Omega @ f_{\text{max}}$$


$$R_{p, \text{tot}} = \frac{1}{\frac{1}{R_{p, \text{ind}}} + \frac{1}{R_{p, \text{trans}}} + \frac{1}{R_{p, \text{var}}} + \frac{1}{R_{p, \text{load}}}} = 488 \Omega @ f_{\text{min}}, \quad 637 \Omega @ f_{\text{max}}$$

$$Q_{\text{tot}} = \frac{R_{p, \text{tot}}}{\omega L} = 7,58 @ f_{\text{min}}, \quad 7,62 @ f_{\text{max}}$$

c. $V_o = I_{\text{BIAS}} \cdot \frac{2}{\pi} \cdot R_{p, \text{tot}} = 2 \cdot 10^{-3} \cdot \frac{2}{\pi} \cdot 488 = 0,62 \text{ V}_{\text{pk}} / \text{side} @ f_{\text{min}}$

— " — $= 2 \cdot 10^{-3} \cdot \frac{2}{\pi} \cdot 637 = 0,81 \text{ V}_{\text{pk}} / \text{side} @ f_{\text{max}}$

4.

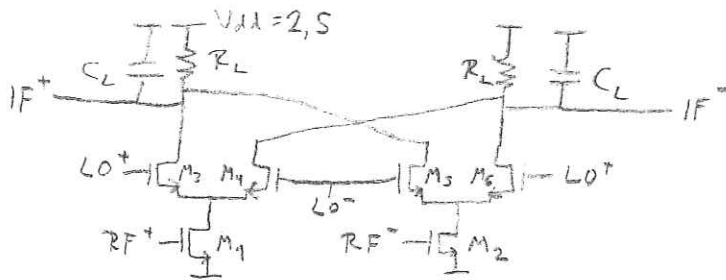

$$ICP \geq 200 \text{ mV}/\text{side} \Rightarrow V_{ov1,2} \geq 200 \text{ mV}, \text{ set } V_{ov1,2} = 250 \text{ mV}$$

$$I_{DC} \leq 5 \text{ mA}, \text{ set } I_{D1} = I_{D2} = 2,5 \text{ mA}$$

$$g_{m1} = \frac{2I_{D1}}{V_{ov1}} = \frac{5 \text{ m}}{0,25} = 20 \text{ mS}$$

$$A_{cv} = g_{m1} \cdot \frac{2}{\pi} \cdot R_L = 6 \text{ dB} = 2 \Rightarrow R_L = 157 \Omega$$

$$F = 1 + \frac{\gamma}{g_m \cdot 50 \Omega} \cdot 2 = 1 + \frac{1,5}{20 \text{ m} \cdot 50} \cdot 2 = 4 = 6 \text{ dB} < 8 \text{ dB} \text{ OK}$$

$$V_{ov,sw,bal} = \frac{1}{\sqrt{2}} \cdot V_{Lo}^{0,8V} \cdot \sin(90^\circ \cdot 0,25) = 216 \text{ mV}$$

$$W_{3,4,5,6} = W_{sw} = L_{sw} \cdot \frac{2I_d}{\mu C_{ox} V_{ov,sw,bal}^2} = 0,4 \mu\text{m} \cdot \frac{2,5 \text{ m}}{115 \mu \cdot 0,108^2} = 186 \mu\text{m}$$

$$W_{1,2} = L_{1,2} \cdot \frac{2I_d}{\mu C_{ox} V_{ov1,2}^2} = 0,4 \mu\text{m} \cdot \frac{5 \text{ m}}{115 \cdot 10^{-6} \cdot 0,25^2} = 278 \mu\text{m}$$

$$V_{G1,2} = V_{th0} + V_{ov1,2} = 0,48 + 0,25 = 0,73 \text{ V}$$

$$V_{S,sw,min} = V_{G,sw} - V_E - 2 \cdot V_{ov,sw,bal} > V_{ov1,2} + V_{in,max} \Rightarrow M_{1,2} \text{ i saturation.}$$

$$V_{G,sw} > V_{ov1,2} + V_{in,max} + V_E + 2 \cdot V_{ov,sw,bal} = 0,25 + 0,2 + 0,48 + 2 \cdot 0,216 =$$

$$= 1,36 \text{ V}, \text{ choose } 1,5 \text{ V to give margin for body effect}$$

$$M_{sw} \text{ in saturation} \Rightarrow V_{out} > V_{G,sw} + \hat{V}_{Lo} - V_E = 1,42 \text{ V}$$



$$V_{out,min} = V_{DD} - \frac{I_{AC}}{2} \cdot R_L - A_{cv} \cdot V_{in,max} = 2,5 - 2,5 \cdot 157 - 2 \cdot 0,2 = 1,7 \text{ V}$$

\Rightarrow OK

$$C_{L,trans} < 2 \cdot \frac{1}{2} W_{sw} \cdot 1,2 \mu\text{m} \cdot C_{jn} = 0,2 \text{ pF} \text{ (almost negligible)}$$

$$C_{L,bt} = \frac{1}{2\pi \cdot BW \cdot R_L} = 6,75 \text{ pF}$$

$$\text{Choose } C_L = 6,6 \text{ pF}$$

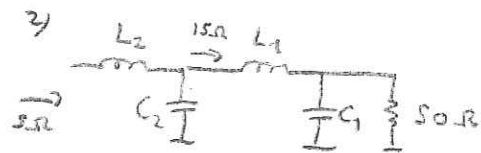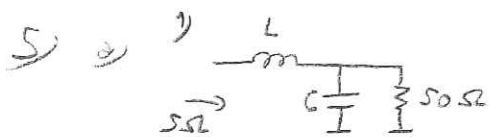

$$1: Q = \sqrt{\frac{50}{5} - 1} = 3 \quad L = \frac{QR_{in}}{\omega_0} = \frac{3 \cdot 5}{2\pi \cdot 2 \cdot 10^9} = 1,19 \text{ nH}$$

$$C = \frac{Q}{\omega_0 R_L} = \frac{3}{2\pi \cdot 2 \cdot 10^9 \cdot 50} = 4,78 \text{ pF}$$

$$2: Q_1 = \sqrt{\frac{50}{15} - 1} = 1,53 \quad L_1 = \frac{Q_1 R_L}{\omega_0} = \frac{1,53 \cdot 15}{2\pi \cdot 2 \cdot 10^9} = 1,83 \text{ nH}$$

$$C_1 = \frac{Q_1}{\omega_0 R_L} = \frac{1,53}{2\pi \cdot 2 \cdot 10^9 \cdot 50} = 2,44 \text{ pF}$$

$$Q_2 = \sqrt{\frac{15}{5} - 1} = 1,41 \quad L_2 = \frac{Q_2 R_{in}}{\omega_0} = \frac{1,41 \cdot 5}{2\pi \cdot 2 \cdot 10^9} = 0,56 \text{ nH}$$

$$C_2 = \frac{Q_2}{\omega_0 R_L} = \frac{1,41}{2\pi \cdot 2 \cdot 10^9 \cdot 15} = 7,5 \text{ pF}$$

b) 1: $Z_{in} = j\omega L + R_L \parallel \frac{1}{j\omega C}$

2: $Z_{in} = j\omega L_2 + \frac{1}{j\omega C_2} \parallel (j\omega L_1 + (\frac{1}{j\omega C_1} \parallel R_L)) = j\omega L_2 + \frac{1}{j\omega C_2 + \frac{1}{j\omega L_1 + \frac{1}{j\omega C_1 + \frac{1}{R_L}}}}$

$f = 1,6 \text{ GHz} \quad f = 2,5 \text{ GHz}$

1: $Z_{in} = 7,4 - j5,8 \Omega \quad 3,3 + j6,3 \Omega$

2: $Z_{in} = 4,5 - j3,2 \Omega \quad 6,7 + j0,5 \Omega$

Result: Matching circuit 2 is closer to 5 Ohm, best.

c) Voltage limit $2V_{rms} \Rightarrow i_{max} = \min\left(\frac{V_{limit}}{|Z_{in}|}, i_{max}\right)$

$P_{max} = i_{max}^2 \cdot \text{Re}(Z_{in})$ (ideal: $i_{max} = 0,4 \text{ Arms} \Rightarrow P_{max} = 5 \cdot 0,4^2 = 0,8 \text{ W}_{rms}$)

$f = 1,6 \text{ GHz}$

$f = 2,5 \text{ GHz}$

1: $|Z_{in}| = 9,4 \Omega$
 $i_{max} = 0,21 \text{ Arms}$
 $P_{max} = 0,34 \text{ W}_{rms}$

$|Z_{in}| = 7,1 \Omega$
 $i_{max} = 0,28 \text{ Arms}$
 $P_{max} = 0,26 \text{ W}_{rms}$

2: $|Z_{in}| = 5,5 \Omega$
 $i_{max} = 0,36 \text{ Arms}$
 $P_{max} = 0,59 \text{ W}_{rms}$

$|Z_{in}| = 6,72 \Omega$
 $i_{max} = 0,30 \text{ Arms}$
 $P_{max} = 0,59 \text{ W}_{rms}$

Circuit 2 is superior, about 2 times more power!