

Solutions to
Written Exam in
Integrated Radio Electronics (ETI 170)

2010-03-10

Henrik Sjöland

1 a, b, c


$$Q = \frac{\omega L}{R_s} \quad , \quad f_s = \frac{1}{2\pi\sqrt{LC_p/2}} \quad , \quad R_p = R_s(Q^2 + 1)$$

	Q	f_s	R_p
A	10,5	16,6 GHz	165 Ω
B	12,6	13,5 GHz	396 Ω
C	9,0	11,25 GHz	564 Ω

d. For large tuning range inductor A is best, since it has smallest L and highest f_s .

e. For low power inductor C is best, since it has highest R_p

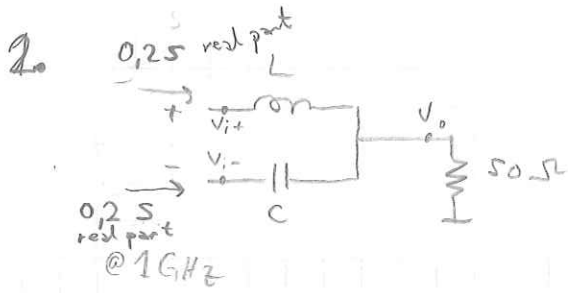f. For low phase noise without considering power, inductor A is best as it has the highest Q/L ratio.



$$\begin{aligned} \text{a)} \quad & (V_{i+} - V_o) \frac{1}{j\omega L} + (V_{i-} - V_o) j\omega C - V_o \cdot \frac{1}{R} = 0 \Rightarrow \\ & V_{i+} \cdot \frac{1}{j\omega L} + V_{i-} \cdot j\omega C = V_o \left(\frac{1}{R} + \frac{1}{j\omega L} + j\omega C \right) \Rightarrow \\ & V_{i+} \cdot \frac{1}{\omega L} - V_{i-} \cdot \omega C = jV_o \left(\frac{1}{R} + \frac{1}{\omega L} + j\omega C \right) \quad , \text{ vid resonans: } \omega C = \frac{1}{\omega L} \Rightarrow \\ & \omega C (V_{i+} - V_{i-}) = jV_o \cdot \frac{1}{R} \Rightarrow \\ & V_o = j\omega RC (V_{i-} - V_{i+}) \quad , V_{i+} = -V_{i-} \Rightarrow V_o = 2j\omega RC V_{i-} = -2j\omega RC V_{i+} \end{aligned}$$

$$\begin{aligned} i_+ &= (V_{i+} - V_o) \frac{1}{j\omega L} = V_{i+} (1 + 2j\omega RC) \cdot (-j\omega C) \Rightarrow \\ Y_+ &= \frac{i_+}{V_{i+}} = -j\omega C + 2\omega^2 RC^2 = \frac{1}{j\omega L} + 2R \frac{C}{L} \\ i_- &= (V_{i-} - V_o) \cdot j\omega C = V_{i-} (1 - 2j\omega RC) \cdot j\omega C \Rightarrow \\ Y_- &= \frac{i_-}{V_{i-}} = j\omega C + 2\omega^2 RC^2 = j\omega C + 2R \frac{C}{L} \end{aligned}$$

$$\begin{aligned} 2 \cdot 50 \cdot \frac{C}{L} &= \frac{1}{S} \Rightarrow \frac{C}{L} = \frac{1}{500} \\ \frac{1}{\sqrt{LC}} &= 2\pi \cdot 16 \text{ Hz} \Rightarrow LC = 2,53 \cdot 10^{-20} \end{aligned} \quad \left. \begin{aligned} & LC \cdot \frac{C}{L} = C^2 = \frac{1}{500^2} = 2,53 \cdot 10^{-20} \Rightarrow \\ & C = 7 \text{ pF}, L = 3,6 \text{ nH} \end{aligned} \right\}$$

b)

$$Y_+ = -j0,044 + 0,2 \text{ S}$$

shunt capacitor:

$$Y_s = j\omega C = j0,044 \Rightarrow$$

$$C = \frac{0,044}{\omega} = 7 \text{ pF}$$


$$Y_- = +j0,044 + 0,2 \text{ S}$$

shunt inductor:

$$Y_s = -\frac{j}{\omega L} = -j0,044 \Rightarrow$$

$$L = \frac{1}{\omega \cdot 0,044} = 3,6 \text{ nH}$$

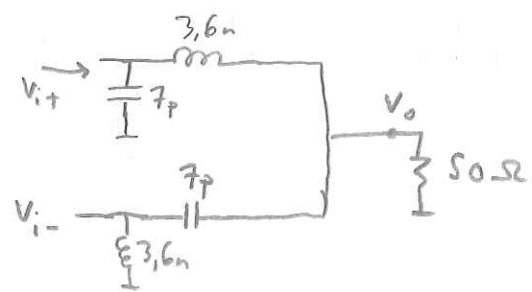That is the shunt component has the same values as the series ones.



3.

In active region. ($V_{GS} > V_T$, $V_{DS} > V_{GS} - V_T$)

$$C_{gs} = \frac{2}{3} C_{ox} \cdot WL = \frac{2}{3} \cdot 14 \cdot 100 \cdot 0,2 \text{ fF} = 187 \text{ fF}$$

$$C_{gd} = W \cdot C_{ox} / w = 100 \cdot 0,07 \text{ fF} = 7 \text{ fF}$$

$$r_g = \frac{1}{3} \cdot R_{sp} \cdot \frac{W}{L} \cdot \frac{1}{(n \cdot C_{gs})^2} = \frac{1}{3} \cdot 7,5 \cdot \frac{100}{0,2} \cdot \frac{1}{20^2} = 3,1 \Omega$$

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 = \frac{1}{2} \cdot 400 \mu \cdot \frac{100}{0,2} \cdot (0,5 - 0,3)^2 = 4,0 \text{ mA}$$

$$g_m = \frac{2I_D}{V_{ov}} = \frac{8,0 \text{ mA}}{0,2 \text{ V}} = 40 \text{ mS}$$

$$f_T = \frac{g_m}{C_{gs}} \cdot \frac{1}{2\pi} = \frac{40 \text{ m}}{187 \cdot 10^{-15} \cdot 2\pi} = 34 \text{ GHz}$$

$$f_{max} = \frac{1}{2\pi} \cdot \frac{1}{2} \sqrt{\frac{2\pi f_T}{r_g C_{gd}}} = 250 \text{ GHz}$$

$$g_{ds} = \frac{I_D}{L} \cdot \left| \frac{dx_{ch}}{dV_{DS}} \right| = \frac{4 \text{ mA}}{0,2 \mu\text{m}} \cdot 0,08 \mu\text{m/V} = 1,6 \text{ mS}$$

$$A_v = \frac{g_m}{g_{ds}} = \frac{40}{1,6} = 25$$

$$C_{ddb0} = \frac{W}{2} \cdot D_{gs} \cdot 1,0 \text{ fF} = 50 \cdot 0,4 \cdot 1,0 \text{ fF} = 20 \text{ fF}$$

$$\overline{i_{nd}^2} = 4kT g_m \Delta f = 1,67 \cdot 10^{-20} \cdot 1,5 \cdot 40 \cdot 10^{-3} \cdot 1 \cdot 10^6 \text{ A}^2 = 1,0 \cdot 10^{-15} \text{ A}^2$$

$$g_g = \frac{\omega^2 C_{gs}^2}{5 g_{d0}} = \frac{(2\pi \cdot 3 \cdot 10^9 \cdot 187 \cdot 10^{-15})^2}{5 \cdot 40 \cdot 10^{-3}} = 6,2 \cdot 10^{-5}$$

$$\overline{i_{ng}^2} = 4kT g_g \Delta f = 1,67 \cdot 10^{-20} \cdot 3 \cdot 6,2 \cdot 10^{-5} \cdot 1 \cdot 10^6 \text{ A}^2 = 3,1 \cdot 10^{-18} \text{ A}^2$$

4.

$$a) \quad d_{\text{avg}} = 80 \mu\text{m} \quad d_{\text{out}} = 92 \mu\text{m} \quad n = 2$$

$$L \approx 9,375 \cdot \mu_0 \cdot n^2 \frac{d_{\text{avg}}^2}{11 d_{\text{out}} - 7 d_{\text{avg}}} = 0,67 \text{ nH}$$

$$\text{Length} = n \cdot 4 \cdot d_{\text{avg}} = 640 \mu\text{m}$$

$$\delta = \sqrt{\frac{2}{\omega \mu_0 \sigma}} = \sqrt{\frac{2}{2\pi \cdot 10 \cdot 10^9 \cdot 4\pi \cdot 10^{-7} \cdot 59,6 \cdot 10^6}} = 0,65 \mu\text{m}$$

$$R_s \approx \frac{\text{Length}}{W \cdot \sigma \cdot \delta (1 - e^{-L/\delta})} = \frac{640 \mu}{8 \cdot 10^{-6} \cdot 59,6 \cdot 10^6 \cdot 0,65 \mu \cdot (1 - e^{-210,65})} = 2,16 \Omega$$

$$Q = \frac{\omega L}{R_s} = \frac{10 \cdot 10^9 \cdot 2\pi \cdot 0,67 \cdot 10^{-9}}{2,16} = 19,5$$

$$C_{\text{par}} = \frac{\text{Length} \cdot W}{D} \cdot \epsilon_0 \epsilon_r = \frac{640 \mu \cdot 8 \mu}{3,5 \mu} \cdot 8,85 \cdot 10^{-12} \cdot 4 = 52 \text{ fF}$$

$$f_s = \frac{1}{2\pi \sqrt{L C_{\text{par}}/2}} = 38 \text{ GHz}$$

$$b) \quad 2R_1 = \left(\frac{300 \mu \cdot 100 \mu}{100 \mu} \right)^{-1} \cdot 5 \Omega \text{ cm} = 166 \Omega \Rightarrow R_1 = 83 \Omega$$

$$C_{\text{par, no shield}} = C_{\text{par}} \cdot \frac{3,5}{4} = 46 \text{ fF}$$

$$f_{s, \text{no shield}} = \frac{1}{2\pi \sqrt{L C_{\text{par, no shield}}/2}} = 40,5 \text{ GHz}$$

Transform both resistors to parallel:

$$Q_1 = \frac{1}{\omega R_1 C_{\text{par, no shield}}/2} = \frac{1}{2\pi \cdot 10 \cdot 10^9 \cdot 33 \cdot 23 \cdot 10^{-15}} = 8,3$$

$$R_{p1} = R_1 \cdot (Q_1^2 + 1) = 83 \cdot (8,3^2 + 1) = 5,8 \text{ k}\Omega$$

$$R_{p2} = R_s \cdot (Q_{\text{shield}}^2 + 1) = 2,16 \cdot (19,5^2 + 1) = 823 \Omega$$

$$R_p = R_{p1} \parallel R_{p2} = 720 \Omega$$

$$Q_{\text{no shield}} = \frac{R_p}{\omega L} = \frac{720}{2\pi \cdot 10 \cdot 10^9 \cdot 0,67 \cdot 10^{-9}} = 17,1$$

Result: Q reduced from 19,5 to 17,1 at 10 GHz, and f_s increased from 38 GHz to 40,5 by removing shield

5. First neglect inductor losses & r_g & find parameters so that F is low:

Max current = 10 mA \Rightarrow 5 mA / side

ICP > -13 dBm \Rightarrow -16 dBm / side $50 \Omega \Rightarrow 50$ mV

Choose $Q = 2$ & $V_{ov} = 0,25$ V ($V_{ov} > 2Q \cdot V_{in}$ OK)

$$g_m = \frac{2I_D}{V_{ov}} = \frac{10 \text{ mA}}{0,25} = 40 \text{ mS}$$

$$C_T = \frac{1}{2\omega_0 R_s Q} = \frac{1}{2 \cdot 2\pi \cdot 5 \cdot 10^9 \cdot 50 \cdot 2} = 160 \text{ fF}$$

$$L_s = \frac{R_{in} \cdot C_T}{g_m} = \frac{50 \cdot 160 \cdot 10^{-15}}{40 \cdot 10^{-3}} = 0,2 \text{ nH}$$

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} V_{ov}^2 \Rightarrow W = L \cdot \frac{2I_D}{\mu C_{ox} V_{ov}^2} = 0,2 \mu\text{m} \cdot \frac{10 \text{ mA}}{400 \mu \cdot 0,25^2} = 80 \mu\text{m}$$

$$C_{gs} = \frac{2}{3} W L C_{ox} = \frac{2}{3} \cdot 80 \cdot 0,2 \cdot 14 \text{ fF} = 150 \text{ fF}$$

$$P = \frac{C_{gs}}{C_T} = \frac{150}{160} = 0,94$$

$$F = 1 + \frac{(5/50)(Q^2+1) \cdot P^2 + 2/4}{P_s Q^2 g_m} = 1 + \frac{0,8 \cdot 5 \cdot 0,94^2 + 0,5}{50 \cdot 4 \cdot 40 \cdot 10^{-3}} = 1,50 = 1,8 \text{ dB}$$

seems OK \Rightarrow Continue:

$$L_g = \frac{1}{\omega_0^2 C_T} - L_s = 6,33 \text{ nH} - 0,2 \text{ nH} = 6,1 \text{ nH} \quad \text{Too large!}$$

$$R_{L_g+L_s} = \frac{\omega_0(L_g+L_s)}{Q_L} = \frac{199}{14} = 14 \Omega$$

Too large

$$F_{L_{gs}} = 1,50 + \frac{14}{50} + \frac{0,4}{50} = 1,79 = 2,5 \text{ dB} \quad \text{with cascode } 2,7 \text{ dB, too much!}$$

Reduce Q from 2 to 1,4 to reduce L_g . Keep V_{ov}

$$g_m = 40 \text{ mS} \quad C_T = 0,23 \text{ pF} \quad L_s = 0,29 \text{ nH}$$

$$L = 0,2 \mu\text{m} \quad W = 80 \mu\text{m} \quad C_{gs} = 0,15 \text{ pF} \Rightarrow P = 0,65$$

$$F = 1,38 = 1,4 \text{ dB} \quad L_g = 4,1 \text{ nH} \quad R_{L_g+L_s} = 9,9 \Omega$$

< 5 nH OK

$$F_{L_{gs}} = 1,38 + \frac{9,9}{50} + \frac{0,4}{50} = 1,586 = 2,0 \text{ dB} \quad F_{tot} = 2,0 + 0,2 = 2,2 \text{ dB} < 2,5 \text{ dB}$$

↑ cascode

OK

$$A_v = 2Q g_m R_L \Rightarrow R_L = \frac{A_v}{2Q g_m} = \frac{10}{2 \cdot 1,4 \cdot 40 \cdot 10^{-3}} = 90 \Omega$$

S continued.

Try snth load inductor for load:

$$R_p = \omega_0 L Q = 2\pi \cdot 5 \cdot 10^9 \cdot 5 \cdot 10^{-9} \cdot 14 = 2,2 \text{ k}\Omega$$

Load with 94Ω in parallel to get 90Ω in total

$$C_{\text{tot}} = \frac{1}{\omega_0^2 L} = 200 \text{ fF}$$

$$C_{\text{drain, cascade}} < W \cdot \frac{1}{2} \cdot 0,4 \cdot 1,0 \text{ fF} = 80 \cdot \frac{1}{2} \cdot 0,4 \cdot 1,0 \text{ fF} = 16 \text{ fF}$$

$$\text{Result: } L_{\text{load}} = S_{\text{nth}}, R_{\text{Load}} = 94\Omega, C_{\text{Load}} = 200 - 16 \text{ fF} = 0,19 \text{ pF}$$

$$V_{G1} = V_t + V_{ov} = 0,3 + 0,25 = 0,55 \text{ V}$$

$$V_{G2} = V_t + 2V_{ov, \text{max}} + 0,1 \text{ V} = 0,3 + 2 \cdot (0,25 + V_{in, \text{max}} \cdot 2\Omega) + 0,1 = 1,2 \text{ V}$$

$$V_{out, \text{max}} = V_{in, \text{max}} \cdot A_v = 0,05 \text{ V} \cdot 10 = 0,5 \text{ V}$$

$$V_{DD} = V_{G2} - V_t + V_{out, \text{max}} = 1,2 - 0,3 + 0,5 = 1,4 \text{ V} \text{ is required}$$

(should be OK to exceed 1,2V slightly, thanks to cascade)

$$r_g = \frac{1}{3} \frac{W}{L} \cdot R_{sp} \cdot \frac{1}{n \cdot f_{sig}} \Rightarrow n_{f_{sig}} = \sqrt{\frac{1}{3} \frac{W}{L} \frac{R_{sp}}{r_g}} = \sqrt{\frac{1}{3} \cdot \frac{80}{0,2} \cdot \frac{7,5}{0,4}} = 50$$

50 gates if contacted on one side

(if contacted on both sides, 25 is enough.)

$$\text{Results: } W_{1,2} = 80 \mu\text{m} \quad L_{1,2} = 0,2 \mu\text{m}$$

$$L_s = 0,3 \text{ nH} \quad L_g = 4,1 \text{ nH} \quad L_{\text{Load}} = 5 \text{ nH}$$

$$R_{\text{Load}} = 94\Omega \quad C_{\text{Load}} = 0,19 \text{ pF}$$

$$V_{G1} = 0,55 \text{ V} \quad V_{G2} = 1,2 \text{ V} \quad V_{DD} = 1,4 \text{ V}$$