 


# Examination in Integrated A/D and D/A Converters, ETI220


14.00-19.00, Friday, August 27, 2010
 
## I. Basic questions about converters

- If we sample a time span of 10ms and obtain  $2^{15}$  samples, what is the highest frequency we can resolve?
- Explain what we intend with spectrum folding, and why it is a major concern in convert design. Can it also be used intentionally?
- What are the major noise sources limiting the SNR of an A/D converter?
- What does this figure describe?




- Looking at the fft response of an A/D converter, how can we determine whether the energy present in a given bin is due to noise or distortion?
- What kind of converter typically displays this kind of SNR vs. the amplitude of the input signal?




 II. Specific questions about converters


- Describe a pipeline A/D converter, and explain in detail how a 1.5b pipeline A/D converter stage works.
- What kind of converter is this? Explain how it works and derive its transfer function. Explain the role of  $C_A$ , and why  $C_A$  can be regarded as a critical component.



 
- A diode-bridge is shown below on the left. Explain how it works. On the right we see an improved version – explain how it works, and why it is an improvement.




 
- Below you see a Delta-Sigma modulator. Find the signal transfer function  $STF=V/U$ , the quantization-noise transfer function  $NTF=V/E$ , and show that  $X_2$  is independent of  $U$ . What is the order of this modulator?



 e) Explain what conversion is implemented by the circuit below, and how it works.



  f) Below you see a charge-transfer Sample & Hold circuit, with the (single-ended) circuits for noise analysis during Sample and during Hold. Assume that the amplifier noise is  $v_{n,op}^2 = 4kT\gamma'/g_m$ , the amplifier gain  $A = \omega_T/s$  and  $\omega_T = g_m/C_L$ . Find the total noise at the output of the amplifier caused by both switches and amplifier, accounting for both Sample and Hold phases.



g) In the next page you see a sinusoid quantized with some resolution, together with its fft. The frequency of the sinusoid is  $(3/1024) \cdot 2\text{MHz}$ , the sampling frequency is  $2\text{MHz}$ , and the simulation time is  $512\mu\text{s}$ .

We notice that the quantization noise power is not distributed evenly in all bins – in fact, every other bin does not contain noise at all (notice that a level close to  $-300\text{dB}$  is practically zero). Explain why this is so (by the way, the same effect would be noticed if the signal frequency was  $(5/1024) \cdot 2\text{MHz}$ , or  $(7/1024) \cdot 2\text{MHz}$ , etc). Hint: the sinusoid has a DC level of exactly zero, and the reference voltages are  $V_{\text{ref}}$  and  $-V_{\text{ref}}$ , i.e. symmetrical around zero.

