

Examination of Integrated A/D and D/A Converters

14.00-19.00, Friday, Dec 14, 2007


I. Basic questions about A/D converters

- a) Assuming the quantization error ε_Q is distributed from $-\Delta/2$ to $+\Delta/2$ (where Δ is the quantization step) with uniform probability $p(\varepsilon_Q)$, write the expressions of the error power P_Q and the *rms* error voltage V_Q as functions of Δ (remember that P_Q is given by the integration

$$P_Q = \int_{-\infty}^{\infty} \varepsilon_Q^2 \cdot p(\varepsilon_Q) d\varepsilon_Q$$

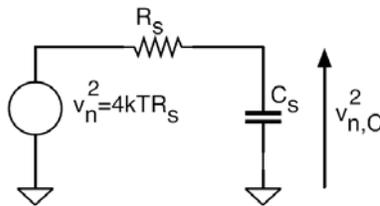- b) Express the *rms* voltage of a full-scale sinusoidal input signal in terms of the quantization step Δ for an n -bit A/D converter.
- c) Write the expression of the *rms* signal-to-quantization noise ratio (SNR) as a function of n , when the input signal is a full-scale sinusoid.
- d) Does bandwidth over which the quantization noise is spread depend on the sampling frequency f_s ? If so, express their relation. Furthermore, what conditions should be satisfied in order to assume that the quantization noise has a white spectral density?
- e) What is the Nyquist bandwidth of an A/D converter, and what is its relation with the sampling frequency f_s ? What happens when the bandwidth of the input signal is larger than the Nyquist bandwidth?
- f) Another fundamental limit in the SNR of A/D converters is set by thermal noise. For the circuit below, show that the thermal noise power P_C across capacitance C_S is independent of R_S , and derive its expression using the integration

$$P_C = \int_0^{\infty} v_{n,C}^2(f) df$$




- g) Yet another limit in the SNR of A/D converters is set by “jitter”. What do we mean by that? Explain qualitatively why the impact of jitter grows with the frequency of the input signal.

II. Basic questions about D/A converters

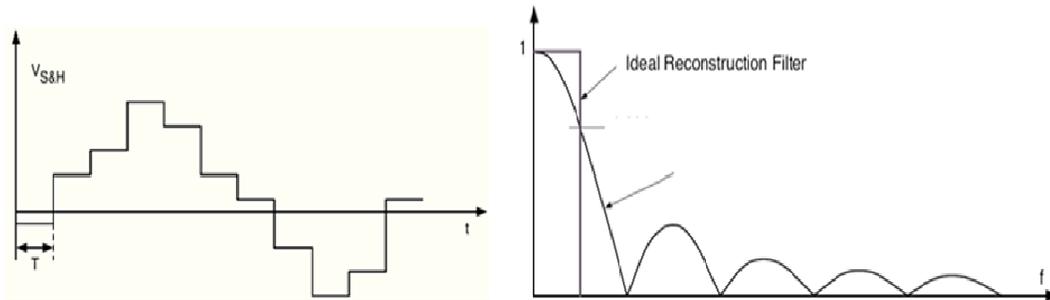- a) The signal waveform after the sample-and-hold (S&H) of a D/A converter is shown on the left, and the amplitude response of the ideal and the real S&H are shown on the right. Remembering that the transfer function of the real S&H is

$$H_{S\&H}(s) = \frac{1 - e^{-sT}}{s\tau}$$

where $T=1/f_s$ (f_s = sampling frequency) and τ is a suitable gain factor. Derive an expression for the amplitude of $H_{S\&H}(j\omega)$, and find the frequencies at which $H_{S\&H}(j\omega)$ is null. How much has $H_{S\&H}(j\omega)$ dropped at the Nyquist frequency, compared to its low-frequency value?




- b) Why is a reconstruction filter usually needed after a D/A converter? In what way does it help to have a large ratio of f_s to f_B , where f_B is the signal bandwidth?

III. Basic questions about $\Sigma\Delta$ converters


- What are the key ideas behind $\Sigma\Delta$ converters? What are the main advantages of $\Sigma\Delta$ converters over Nyquist converters?
- Why is it difficult to replace a full-flash converter with a $\Sigma\Delta$ converter?
- What particular implementation of a $\Sigma\Delta$ converter is intrinsically linear (excluding second-order effects)?
- What is the purpose of the “dynamic element matching” technique?

VI. Specific questions about converters

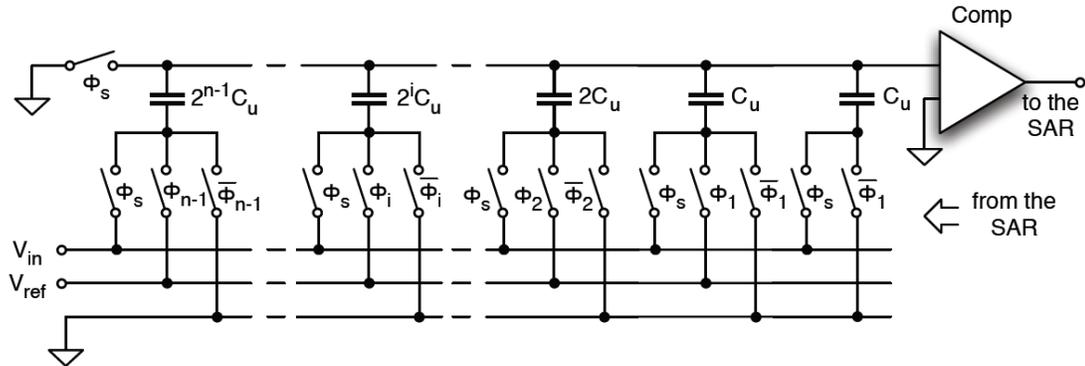
- a) What kind of converter is the one below? Explain how it works, and how sampling frequency and clock frequency are related



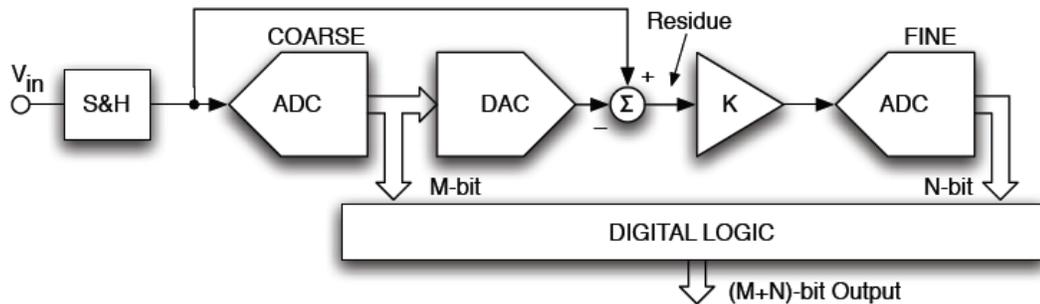
- b) What kind of converter is the one below? Explain how it works, how sampling frequency and clock frequency are related, and why it is often an attractive alternative to a flash converter.



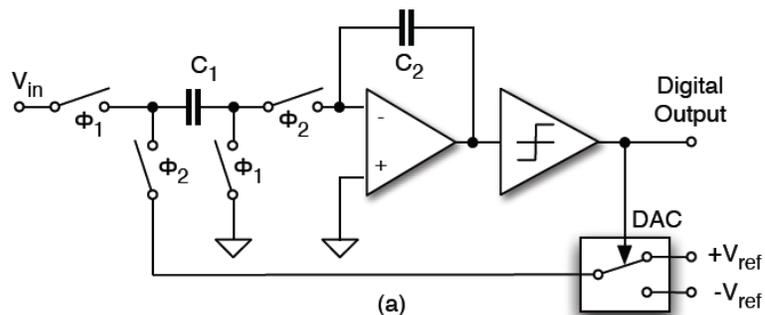- c) What kind of converter is the one below? Explain the operations of the various blocks.



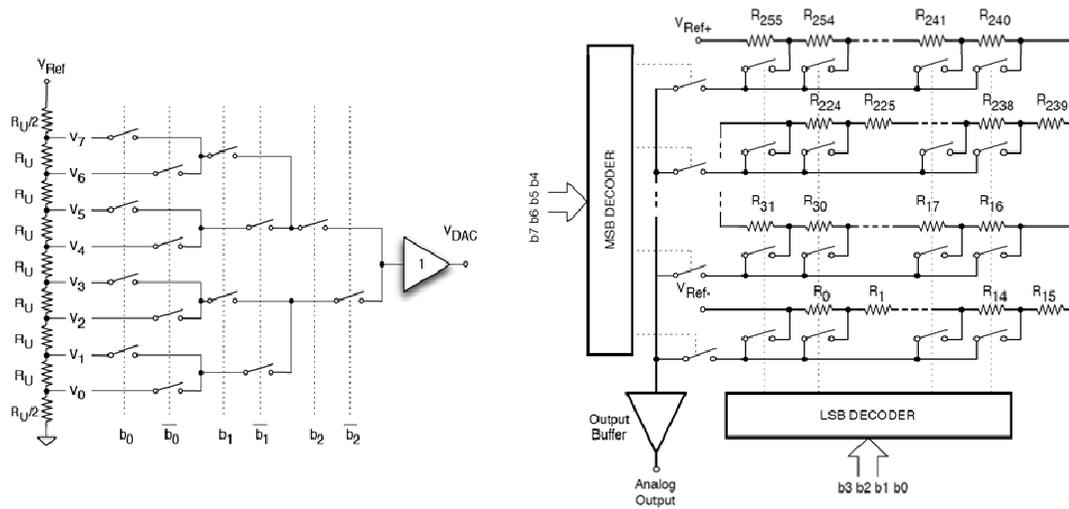- d) We see below the most straightforward implementation of a resistive-ladder D/A converter (left). What is its main drawback, and how is it alleviated by the alternative implementation to the right?



- e) Why is it not a good idea to implement the current sources in a current-based D/A converter as simple current mirrors? Are there better alternatives?
- f) What might be the use of the circuit below? Where is it used?

