

Analog Electronics

Crash course part 1

Bertil Larsson

Electro- and Information Technology







Layout

- Feedback using the nullor (e.g. ideal amplifier)
- Transistor (bipolar and FET)
- Linearization of the transistor (small signal model)
- Implementation (one, two or three amplifying stages)
- Asymptotic gain model

Fundamentals



- Why use feedback?
- Why do we want negative feedback?

Nullor circuits

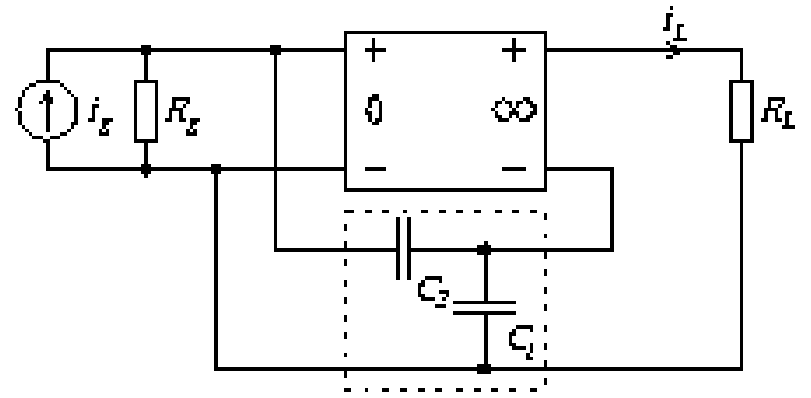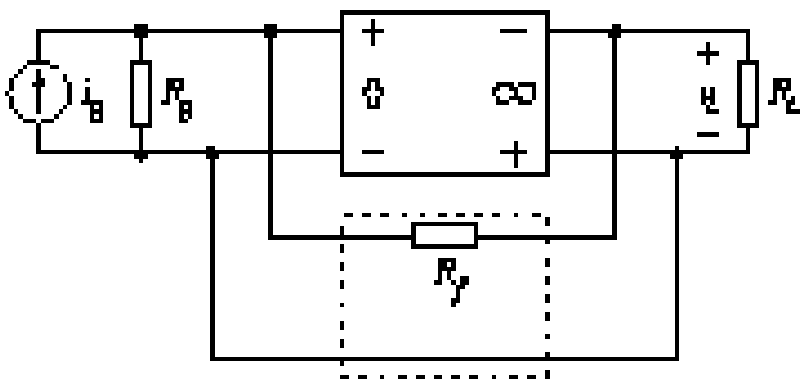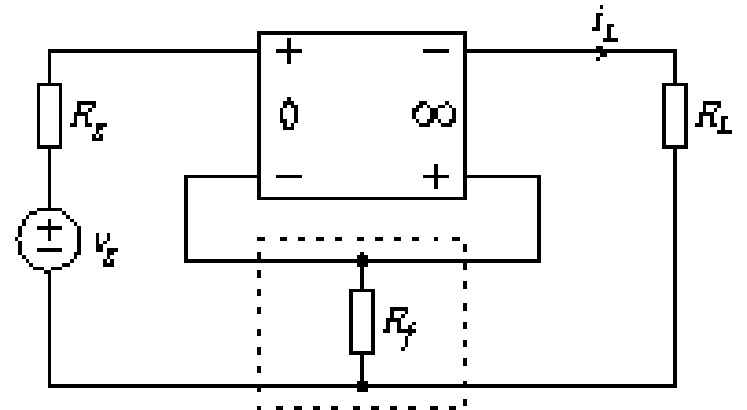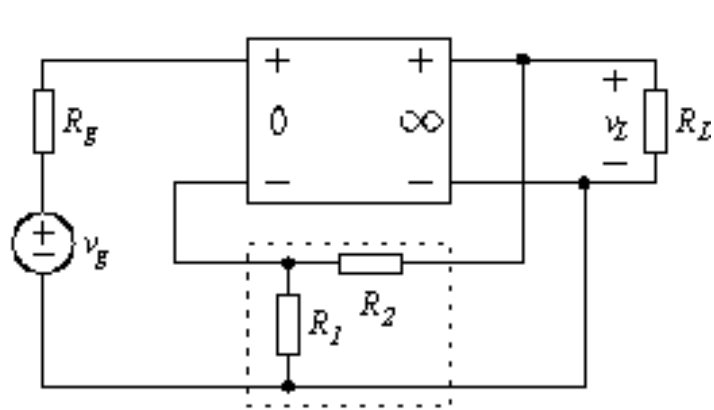


Output

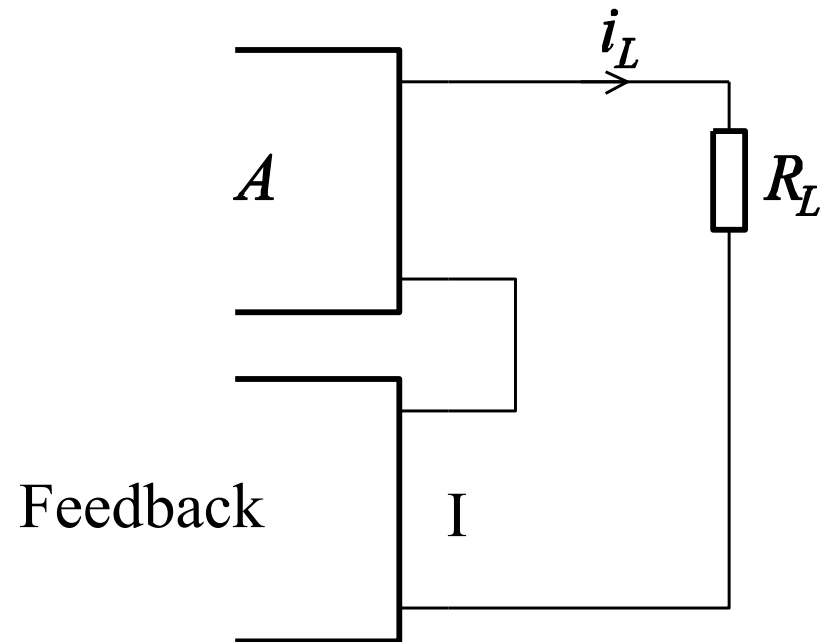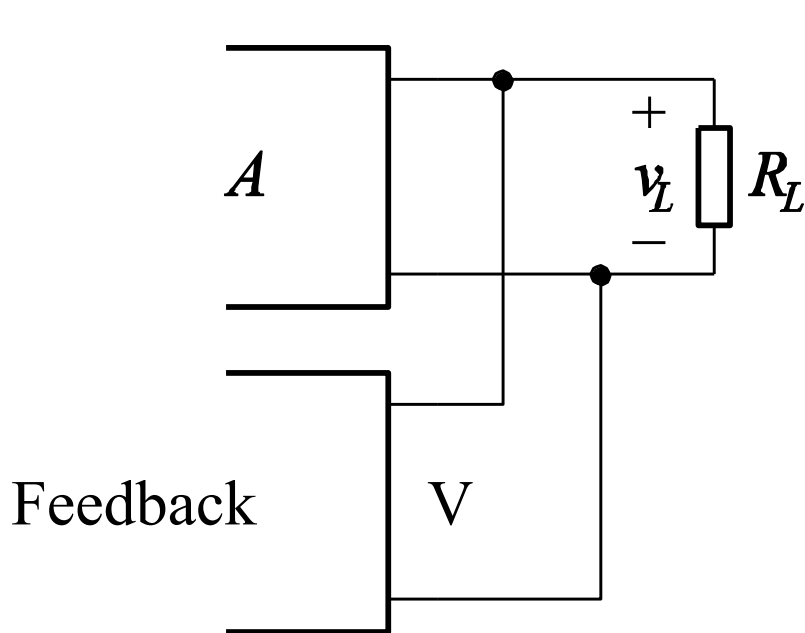- Load voltage is measured in parallel with the load
 - ▶ "shunt"-measure
- Load current is measured in series with the load




Input

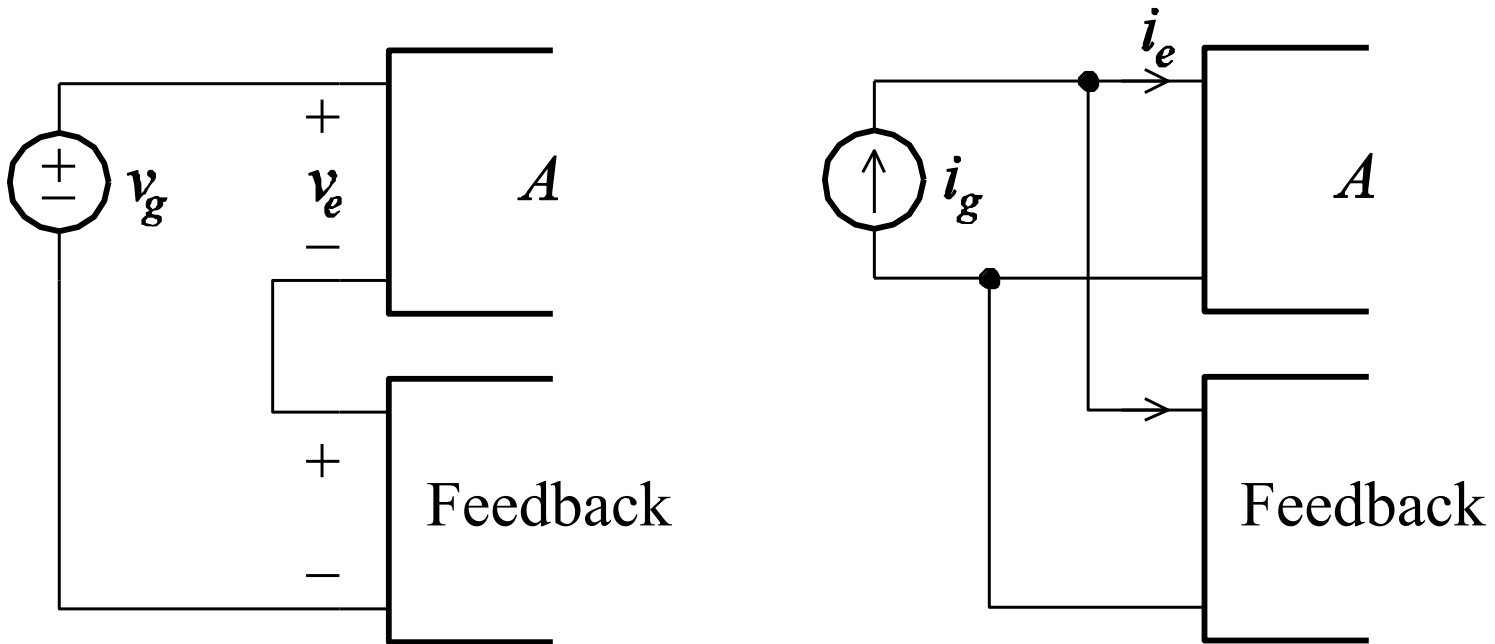- Voltage is added in series to the source signal
- Current is added in parallel to the source signal




Amplifying elements

- BJT

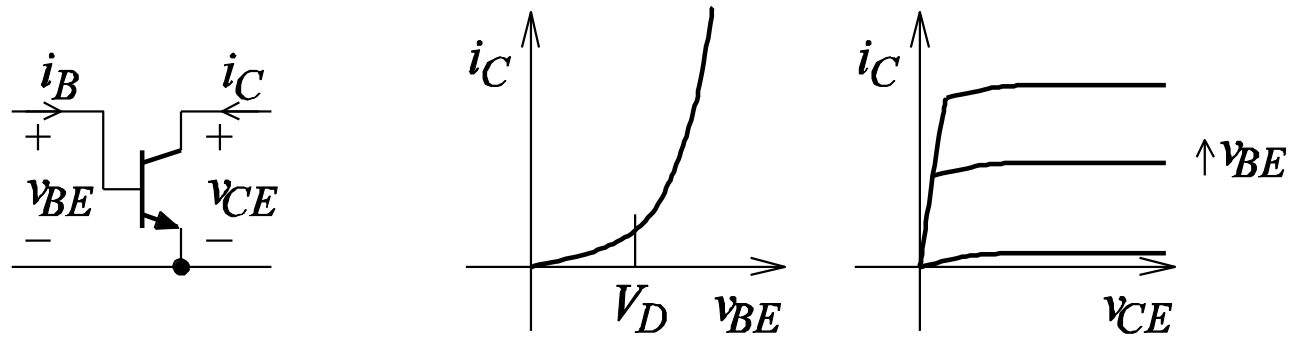


- FET

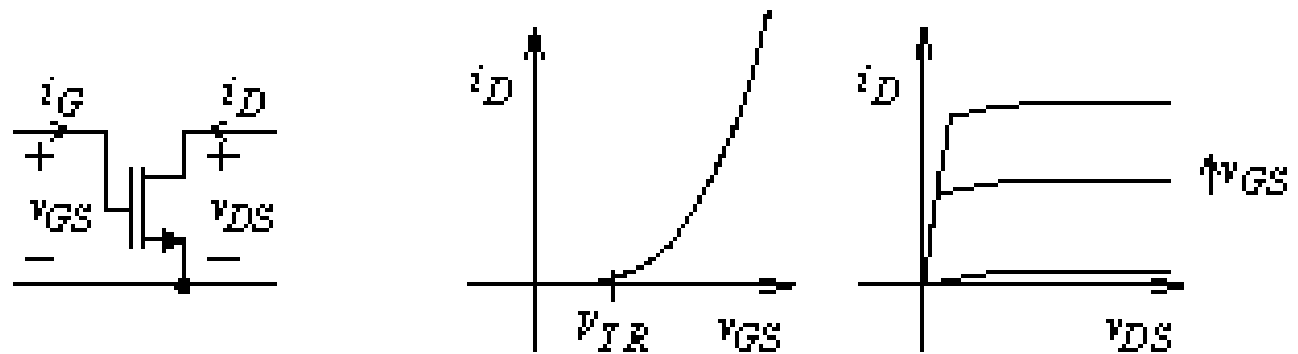

- Both have a non linear relation between input and output signal


Graphs for BJT

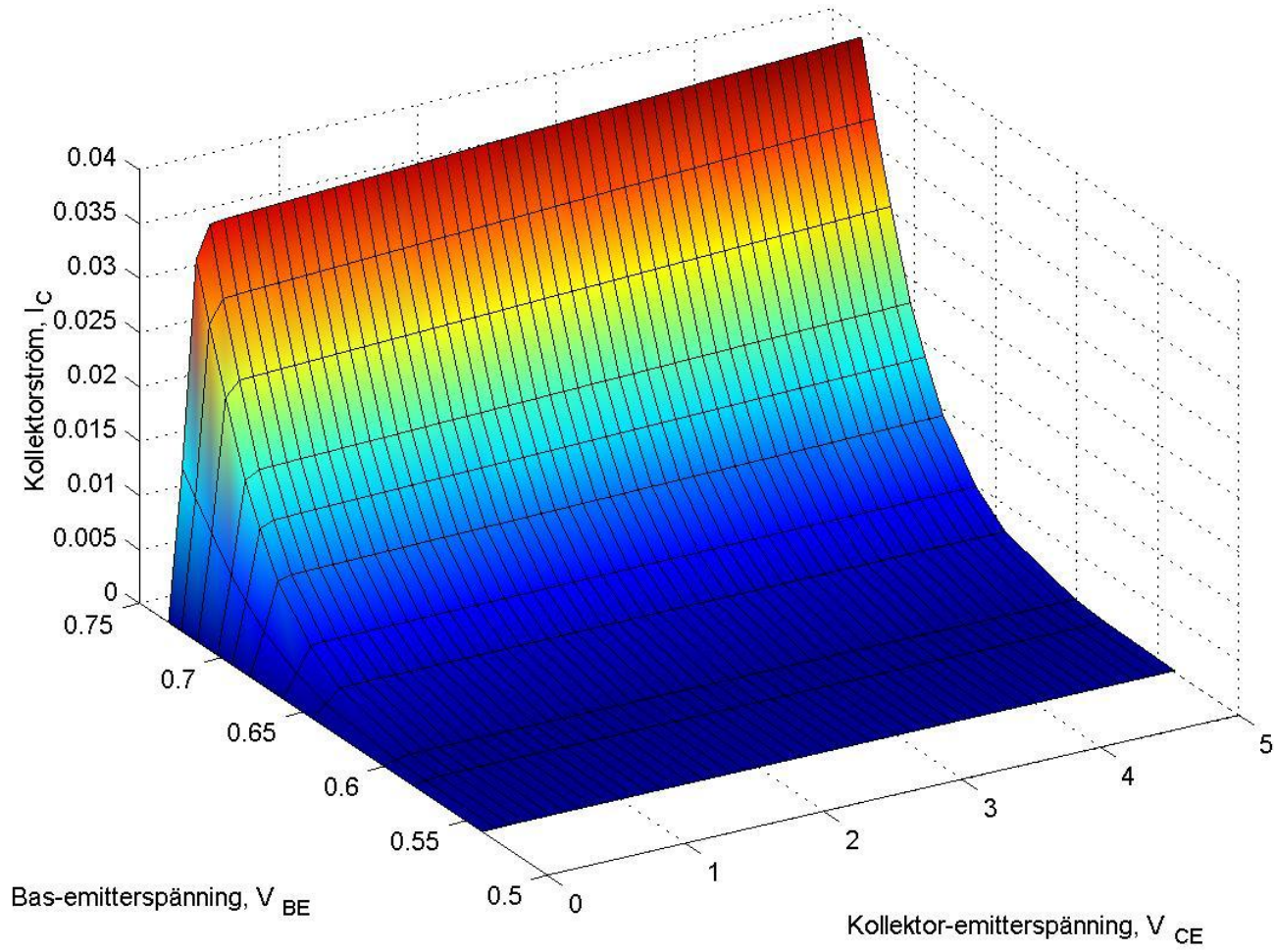


Implementation

- Transimpedance amplifier


Nullor

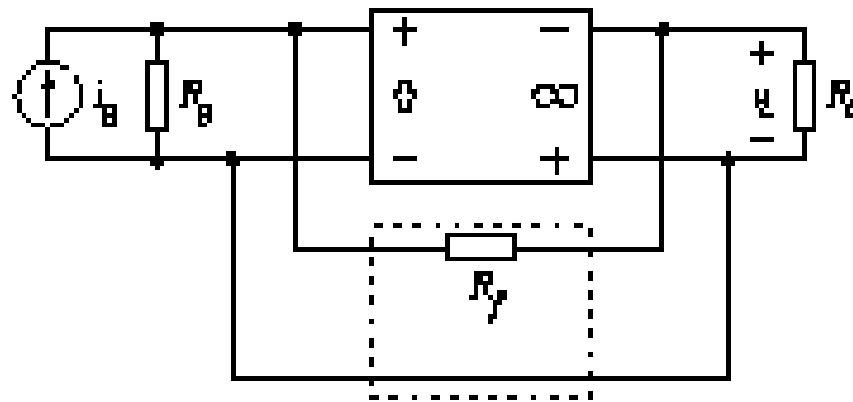

CE-stage

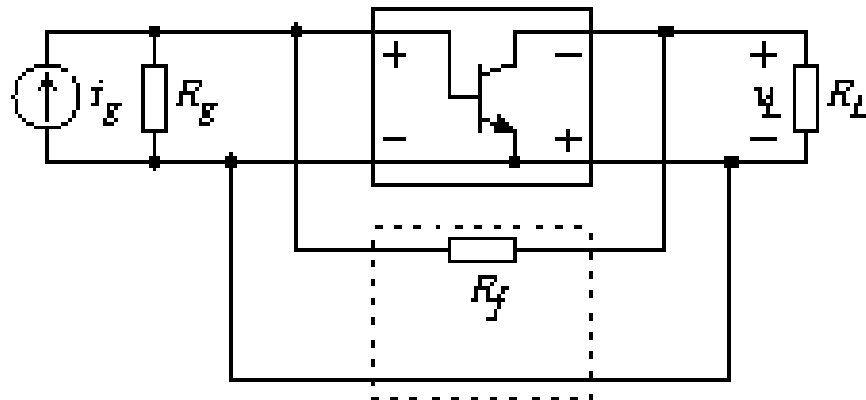

Bias is necessary

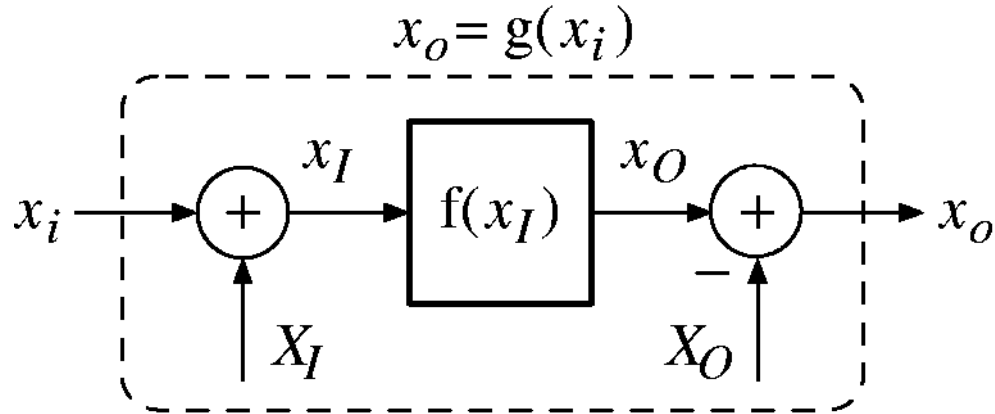


- For small x_i

$$g(x_i) = A \cdot x_i$$


- Note
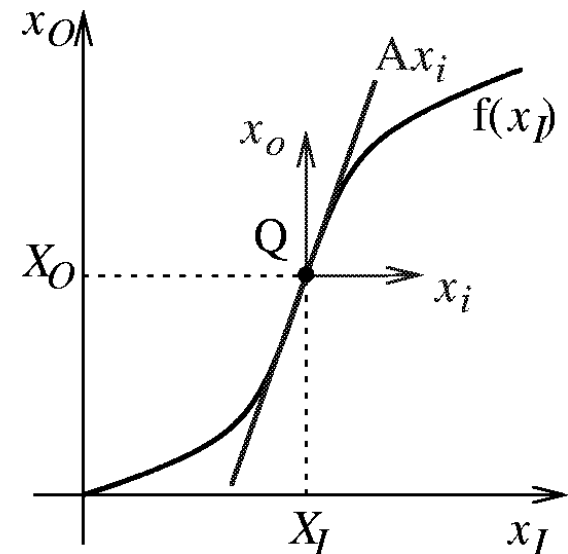
$$\underbrace{x_I}_{\text{Total}} = \underbrace{x_i}_{\text{Signal}} + \underbrace{X_I}_{\text{Bias}}$$




Transistor models

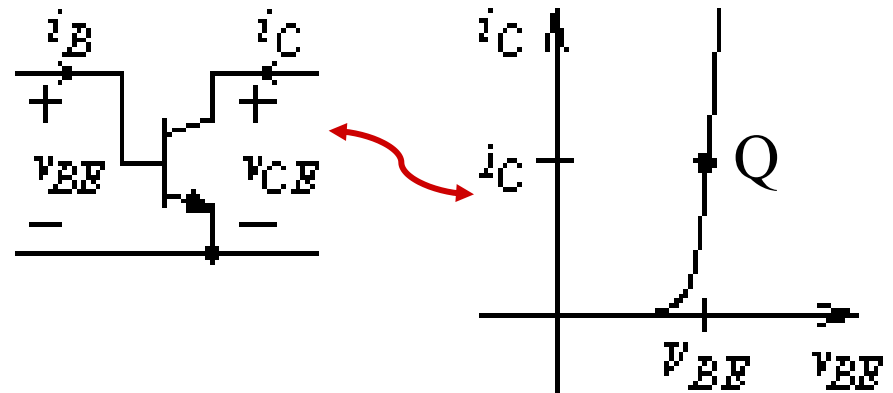- Large signal model
 - ▶ Non linear equations
 - ▶ Bias point
 - ▶ Sets the linear model
- Small signal model
 - ▶ Linear equations
 - ▶ Loop gain



$$g_m, r_\pi, r_o$$

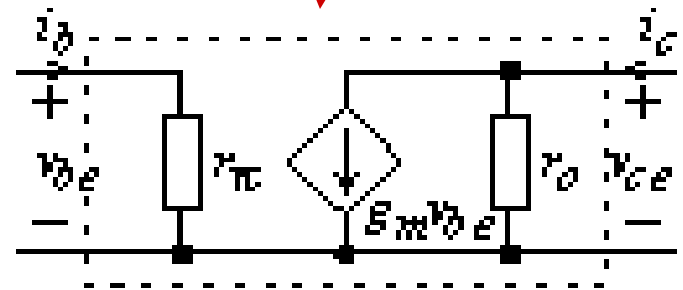

2 minuter

- Suppose you know I_C for a BJT
 - ▶ What is g_m ?
 - ▶ What is r_π ?


Superposition model

- Relation of load and source signal

$$\begin{cases} Q_i = \xi Q_g + \beta Q_c \\ Q_L = A_{t0} Q_g + v Q_c \\ Q_c = A Q_i \end{cases}$$

$$A_t = \frac{Q_L}{Q_g} = A_{t0} + \frac{\xi v A}{1 - A\beta}$$

← Loop gain

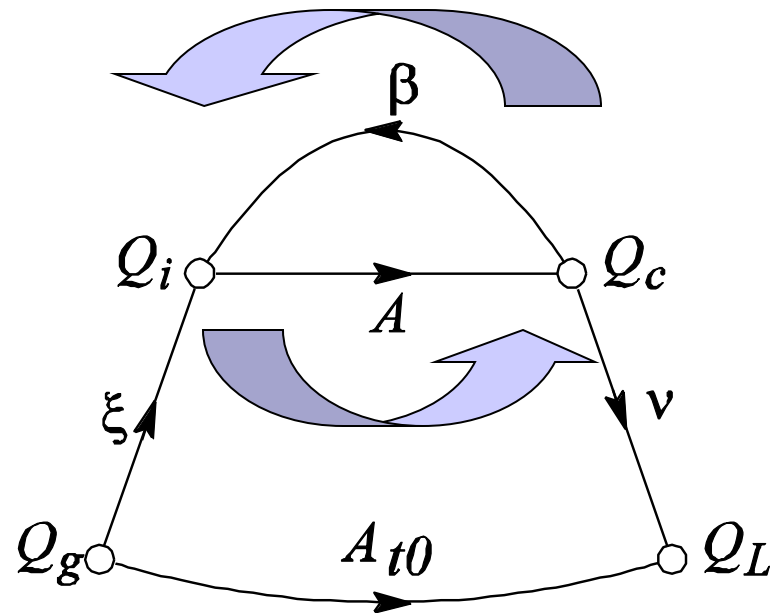

How to calculate A_t

$$A_t = \frac{1}{\beta} \frac{\xi v A \beta}{1 - A \beta} + A_{t0} \frac{1 - A \beta}{1 - A \beta} = A_{t\infty} \frac{-A \beta}{1 - A \beta} + A_{t0} \frac{1}{1 - A \beta}$$

Discrepancy factor Neglect

- $A_{t\infty}$ is set by the nullor circuit

$$A_t \approx A_{t\infty} \frac{-A \beta}{1 - A \beta}$$

Calculate loopgain $A\beta$



- Identify the "natural" A and β

- ▶ Feedback

$$\beta = \frac{v_1}{i_{c2}} \Big|_{v_s=0}$$


- ▶ Controlled sources gain

$$A = \frac{i_{c2}}{v_1}$$

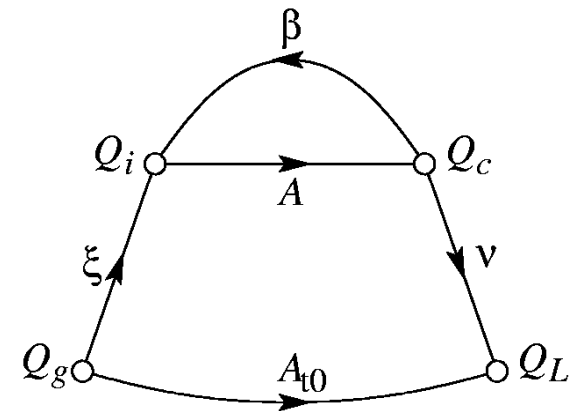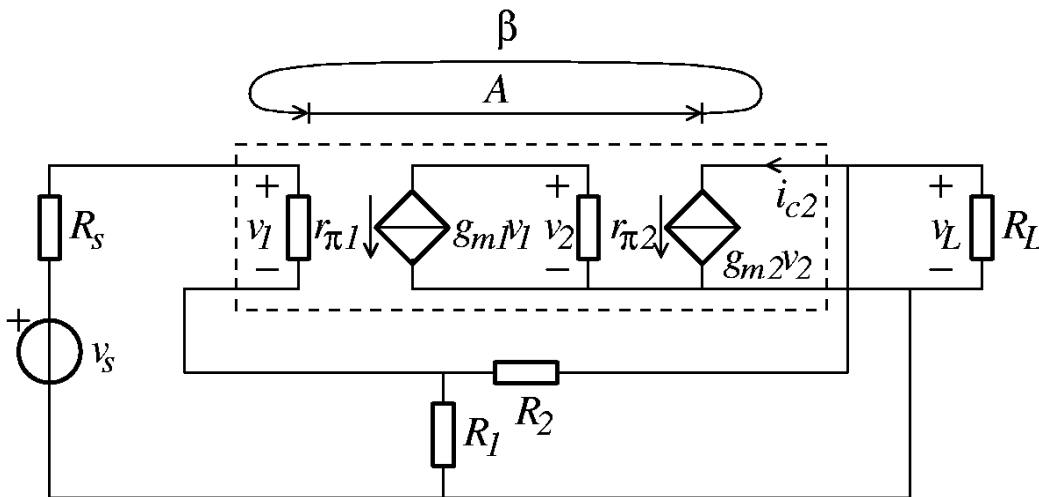


Amplifying stages

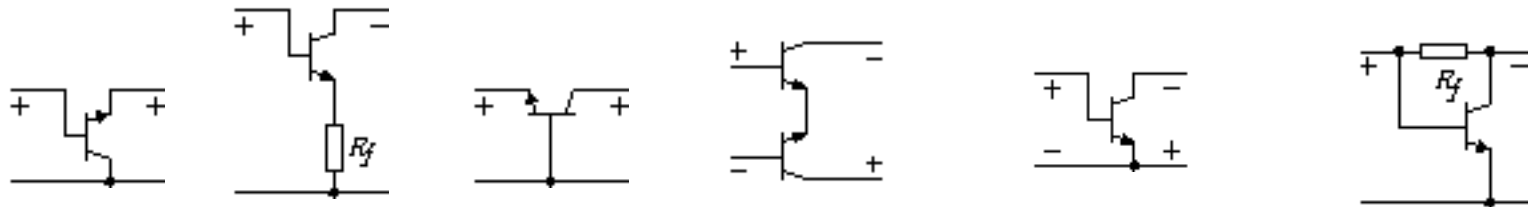- CE-steg negative transfer no feedback
- AS-steg neg./pos. transfer no feedback
- CC-steg positive transfer feedback
- CB-steg positive transfer feedback
- Series-stage negative transfer feedback
- Shunt-stage negative transfer feedback



2 minuter

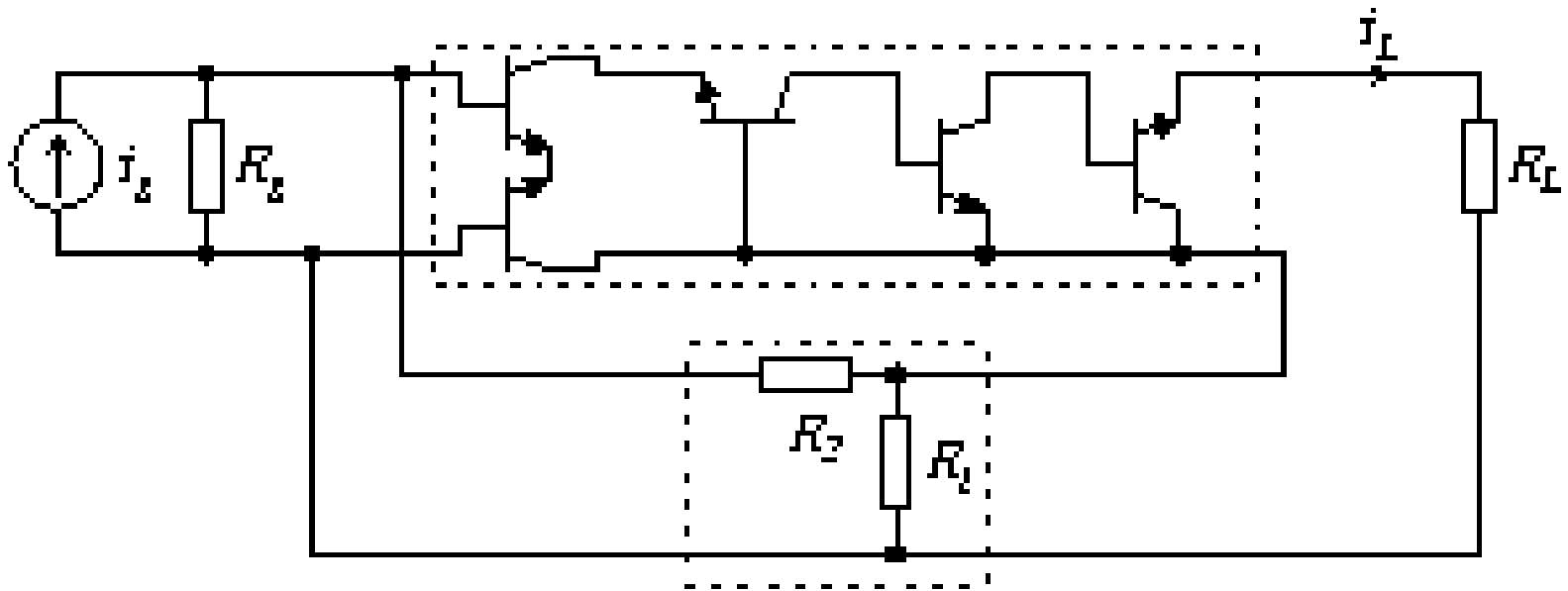
- Identify amplifying stages for the current amplifier and name them
- Check for negative feedback



Antiseries stage

- Small-signal model for the AS-stage is very similar to the hybrid- π -model for CE-stage
- No connection between in- and output
- Parameters of the model

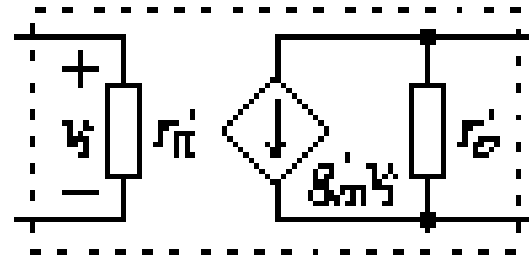- ▶ Transconductance g_m'
- ▶ Input impedance r_π'
- ▶ Output impedance r_o'



- In this course we neglect r_o' if nothing else is stated!

Time to get going

- You are to design a 2-stage $V \rightarrow I$ amplifier
- Which stages do you choose? Motivate!
- Theoretical, what is the maximum loop gain?
 - ▶ Assume you have BJT transistors at hand
- Which bias current influence $A\beta$?