

Crash course part 2

Frequency compensation



Agenda

- Frequency dependance
- Feedback amplifiers
- Frequency dependance of the Transistor
- Frequency Compensation
- Phantom Zero


- Examples

poles and zeros

- In general a transfer function can be written as:

$$H(s) = k \frac{\left(1 - \frac{s}{n_1}\right) \left(1 - \frac{s}{n_2}\right) \cdots \left(1 - \frac{s}{n_m}\right)}{\left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) \cdots \left(1 - \frac{s}{p_n}\right)}$$

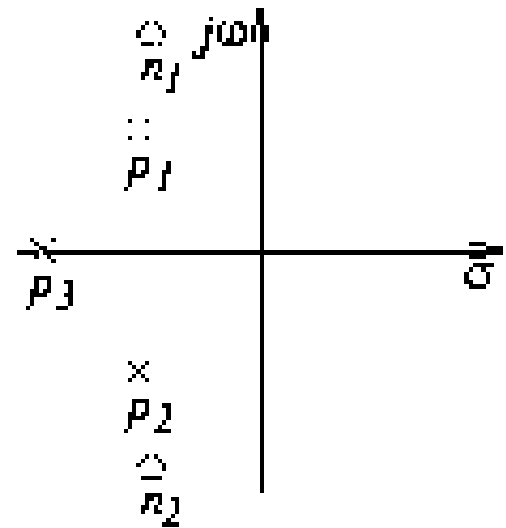- n_1, n_2, \dots, n_m are zeros
- p_1, p_2, \dots, p_n are poles
- poles and zeros are shown in the s-plane
- poles are drawn as \times
- zeros as \circ









System with one pole

Pole placement

Magnitude

Step response

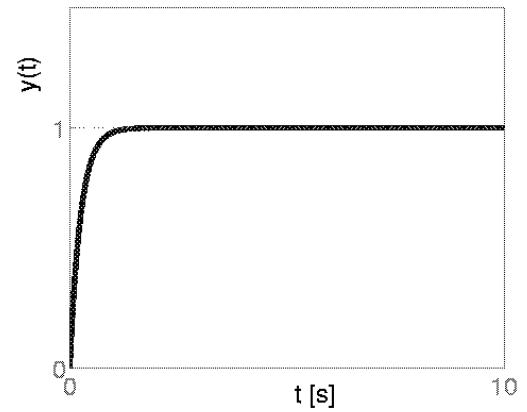
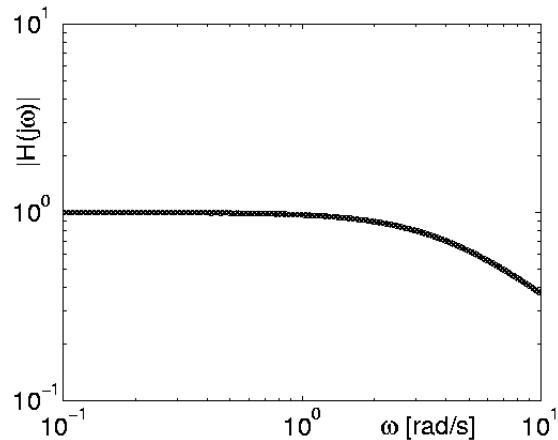
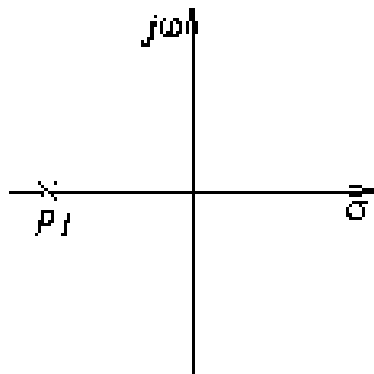
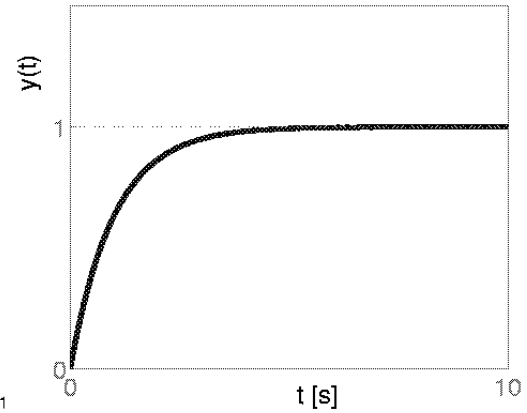
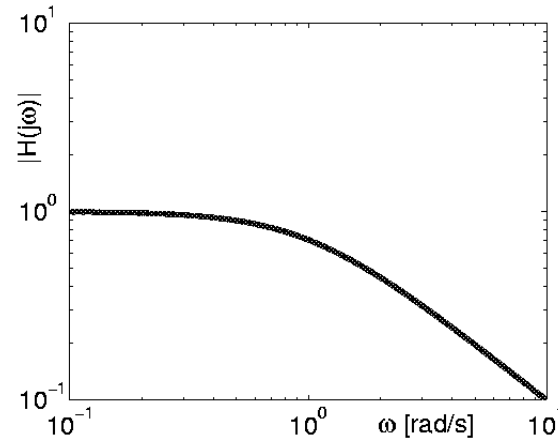
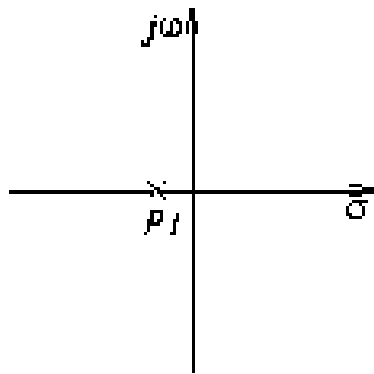


System with complex pole pair

Pole placement



Magnitude

Step response

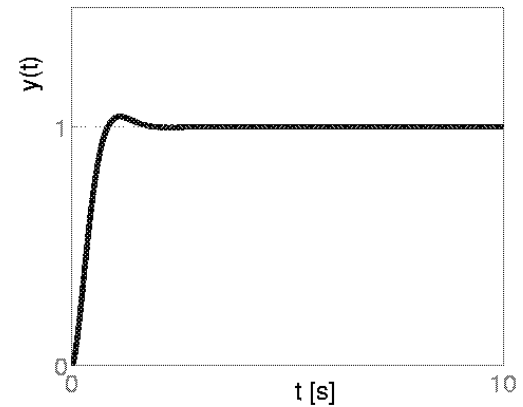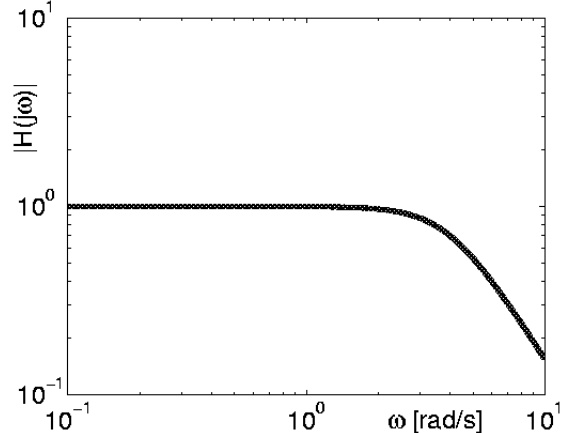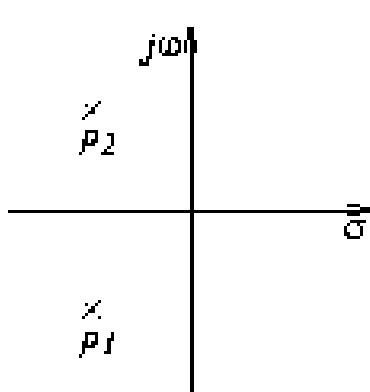
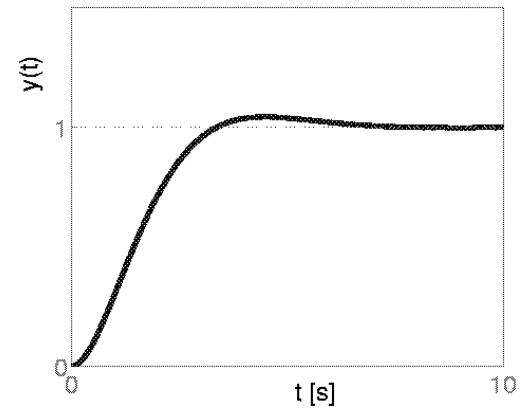
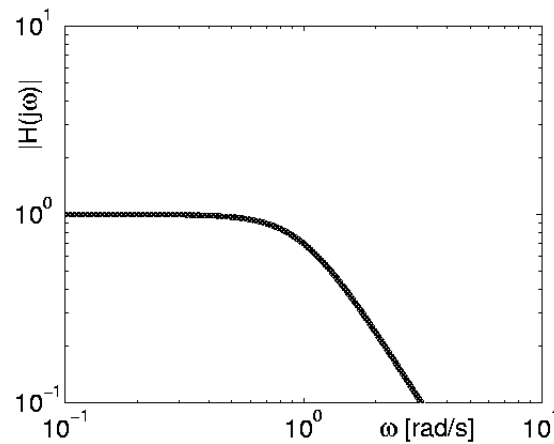
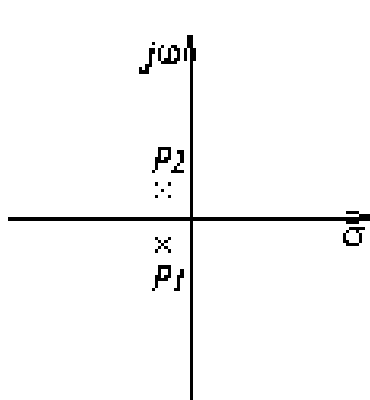


Complex poles close to $j\omega$ -axis

Pole placement

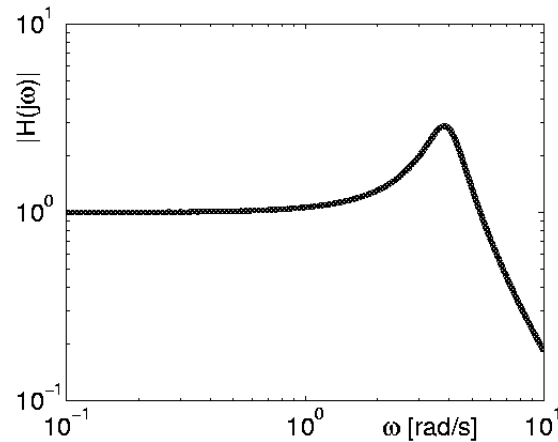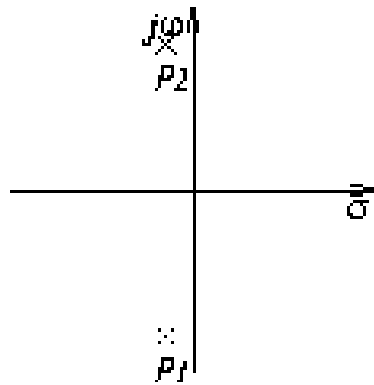

Step response

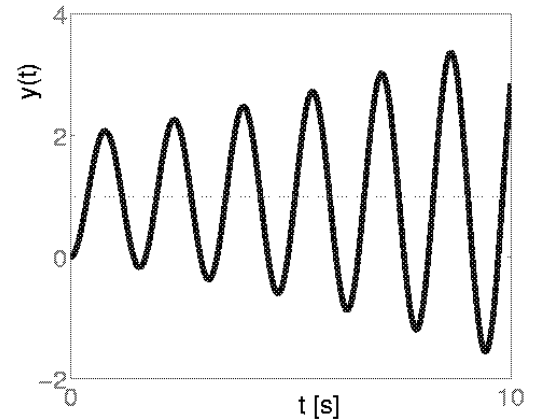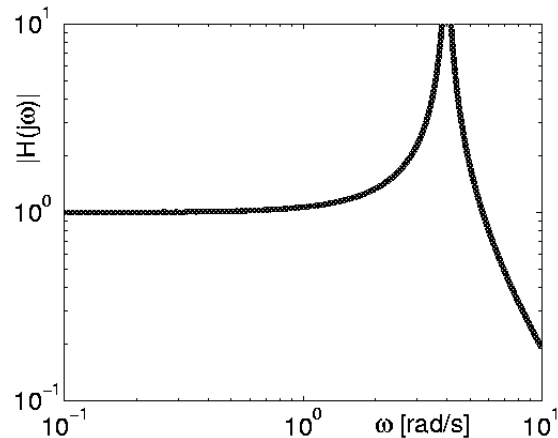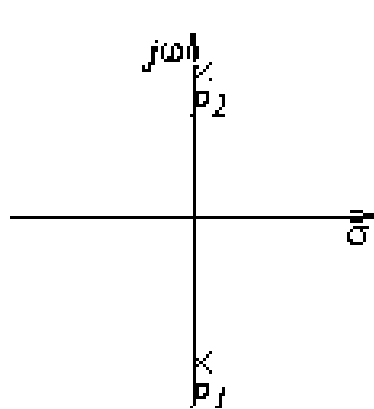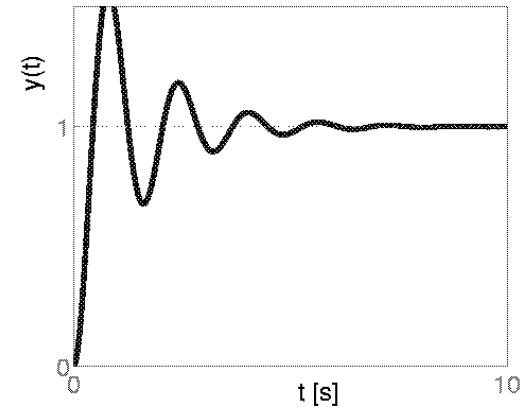

Discrepancy factor, frequency dependence


- Discrepancy factor can be written as:

$$\frac{-A\beta(s)}{1-A\beta(s)} = \frac{-A\beta(0)\frac{N(s)}{P(s)}}{1-A\beta(0)\frac{N(s)}{P(s)}} = \frac{-A\beta(0)N(s)}{P(s)-A\beta(0)N(s)}$$

- Interpretation of the above:
 - ▶ zeros in $A\beta(s)$ is zeros in A_t
 - ▶ Roots of equation $P(s) - A\beta(0)N(s) = 0$ are poles in A_t
 - ▶ The system poles depends on the loop gain $A\beta(0)$
- $P(s) - A\beta(0)N(s)$ is called the characteristic polynome


Root locus

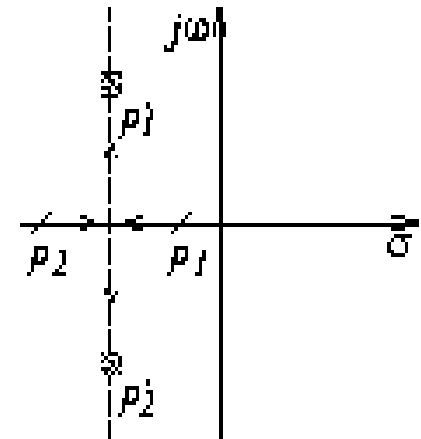- Root locus is a graphical representation of how the system poles moves with increasing $A\beta(0)$
 - ▶ Arrows in root locus shows increasing $A\beta(0)$
- Loop poles are p_1, p_2, \dots, p_n
- System poles are p'_1, p'_2, \dots, p'_n



High frequency model for BJT

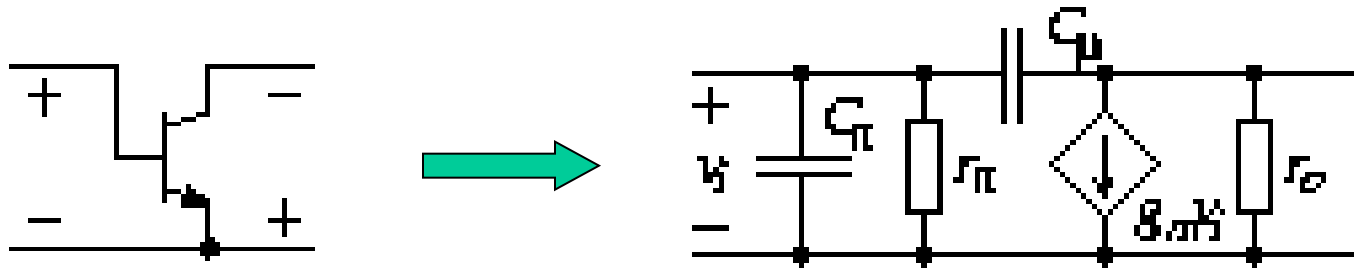
- Capacitances are included in the hybrid- π -model
- C_{π} capacitance between base and emitter
- C_{μ} capacitance between base and collector




- C_{μ} is much less than C_{π} and is assumed to have no importance in our calculations.
- C_{μ} (and r_o) are neglected if not stated otherwise!

Transit frequency f_T

- At very high frequencies the CE-stage has no gain
- f_T is the frequency when $|H(s)| = |i_o/i_i| = 1$ for a current driven CE-stage with a short circuit at the output

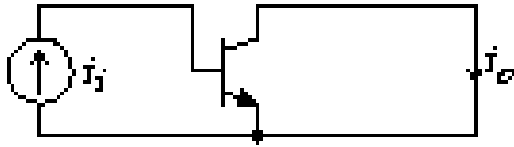



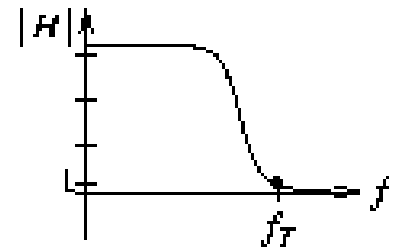
$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$



- f_T varies heavily between different types of transistors
- 1N26 $f_T \sim 1\text{kHz}$ but today there are transistors having $f_T > 50\text{GHz}$

Maximal flat magnitude

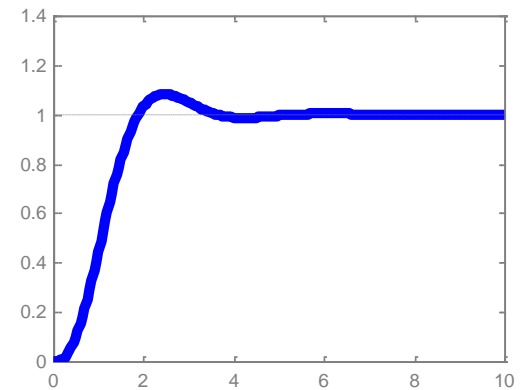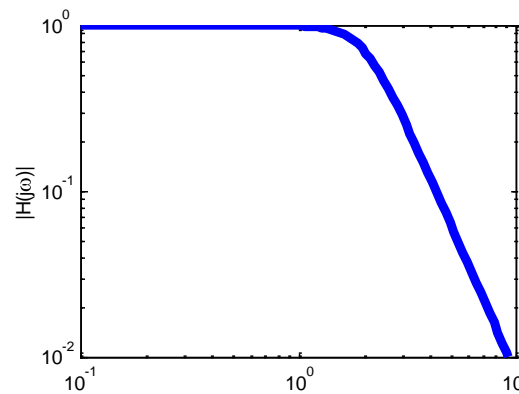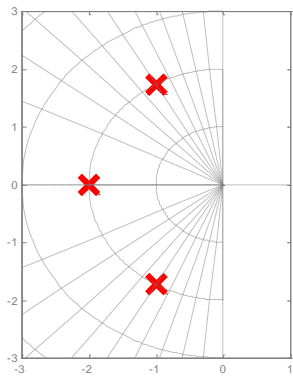- Often you want to have constant gain for all signal frequencies
- This is equal to having the system poles in Butterworth position
- They are located on a half circle equally spaced in left half plane



Loop-gain-Poles-product (LP-product)

- The characteristic polynomial for a system having two loop poles and no loop zeroes is:

$$P(s) - A\beta(0)N(s) = s^2 - (p_1 + p_2)s + [1 - A\beta(0)]p_1p_2$$

- The same system with poles in Butterworth position is:

$$P(s) - A\beta(0)N(s) = s^2 - (p_a + p_b)s + \omega_0^2$$

- Identifying:
- $\omega_0^2 = |[1 - A\beta(0)]p_1p_2|$
- ω_0 is the maximum **possible** bandwidth for the system.

LP-product definition

- The LP-product for a system with two loop poles:

$$LP_2 = \left| \mathbf{I} - A\beta(0) \overline{p_1 p_2} \right|$$

- In general the LP-product is:

$$LP = \left| \mathbf{I} - A\beta(0) \overline{\prod_{\forall n} p_n} \right|$$

- With the poles in Butterworth position the band width is, ω_0 :

$$\omega_0 = \sqrt[n]{LP} = \sqrt[n]{\left| \mathbf{I} - A\beta(0) \overline{\prod_{\forall n} p_n} \right|}$$

Poles in Butterworth

- Poles in Butterworth is found from:

$$s^n + a_1 s^{n-1} + \dots + a_n = 0 \text{ där } |a_n| = \omega_0^n$$


- Location for the poles are (2:nd and 3:rd order)

- ▶ 2:nd order $-\omega_0 \frac{1}{\sqrt{2}} \left(\pm j \right)$
- ▶ 3:rd order $-\omega_0, -\omega_0 \frac{1}{2} \left(\pm j\sqrt{3} \right)$



Flow chart for band width estimation

- Calculate the LP-product
- Estimate the band width
- Choose the location of the system poles (Butterworth) for estimated band width
- Calculate the sum of the loop poles and the sum of the system poles
- Check that the loop poles are dominant
- If a non-dominant pole exists remove the most negative one and re-calculate
- Finished

Phantom zero, graphical interpretation

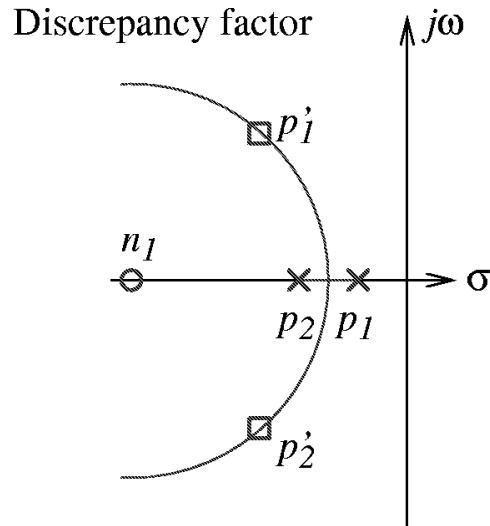

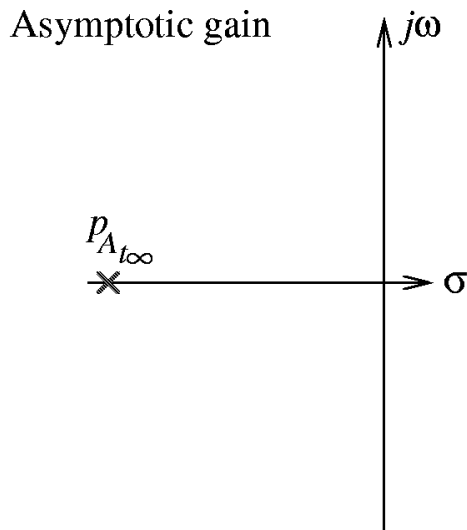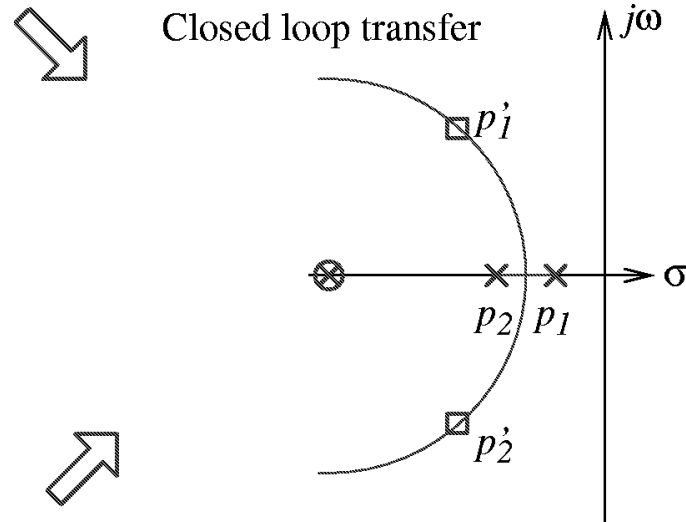$A_{t\infty}$ is made frequency independent



Where to put the phantom zero (2:nd order)

- Identification of s-terms gives
 - ▶ $p_1 + p_2 + \frac{\omega_0^2}{n} = p'_1 + p'_2$, $|A\beta(0)| \gg 1$

- Place the zero at $n = \frac{-\omega_0^2}{-(p'_1 + p'_2) + p_1 + p_2}$

- System poles sum

▶	<u>Characteristics</u>	$p'_1 + p'_2$	
	Butterworth	$-\sqrt{2}\omega_0$	← MFMM
	Bessel	$-1.73\omega_0$	
	Real double polee	$-2\omega_0$	

Implementation of phantom zero

- β should increase for higher frequencies

$$\beta(s) = \beta(0) \left(1 - \frac{s}{n} \right)$$

- Three places to put a phantom zero in β
 - ▶ In the feedback net
 - ▶ At the amplifiers output
 - ▶ At the amplifiers input