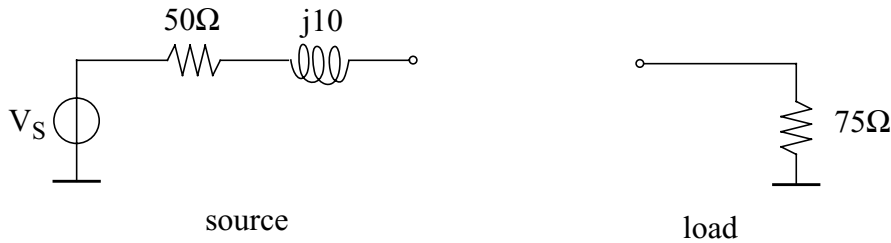



## Solutions exercise 3 (RLC-circuits & amplifiers)
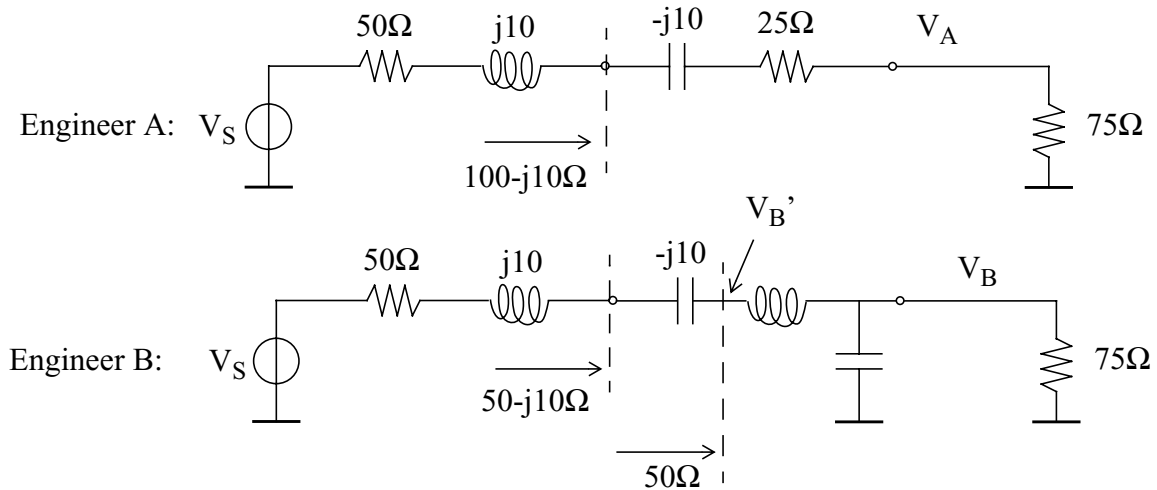
### 1. Problem 4.1

The source and the load in the figure are to be matched for maximum power transfer.



Two engineers come up with two different solutions:



$$\frac{P_A}{P_B} = \frac{V_A^2}{V_B^2} = \frac{(V_A/V_S)^2}{(V_B'/V_S)^2 \cdot (V_B/V_B')^2} = \frac{(1/2)^2}{(1/2)^2 \cdot 75/50} = \frac{50}{75} = \frac{2}{3}$$

In solution A the load seen by the source is  $100-j10\Omega$ , instead of the optimal  $50-j10\Omega$  of solution B. Furthermore, signal power is wasted in the extra  $25\Omega$  resistor. One third of the power is lost in A, compared to the optimal solution in B. (The series connected capacitor and inductor of B can be combined in just one component).


## 2. Problem 4.2 with extension

Given:

$$R_L = 50\Omega \quad P = 1W \Rightarrow \hat{V}_L = \sqrt{2 \cdot P \cdot R_L} = 10V$$

$$f = 1\text{GHz} \quad \hat{V}_{prim} = \frac{6.3}{2}V \Rightarrow R_{prim} = 50\Omega \cdot \left(\frac{6.3}{2 \cdot 10}\right)^2 = 5.0\Omega$$

### a. L-match

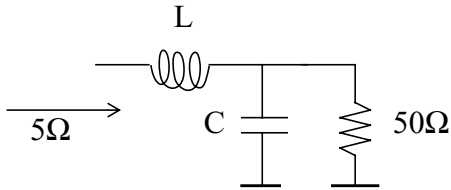


$$R_{prim} = \frac{50\Omega}{Q^2 + 1} \Rightarrow Q = 3$$

$$C = \frac{Q}{\omega R_L} = 9.5\text{pF}$$

$$L = \frac{1}{C\omega^2} = 2.65\text{nH}$$

$$\hat{I}_L = \frac{\hat{V}_{prim}}{R_{prim}} = 0.63\text{A}$$

### b. Pi-match

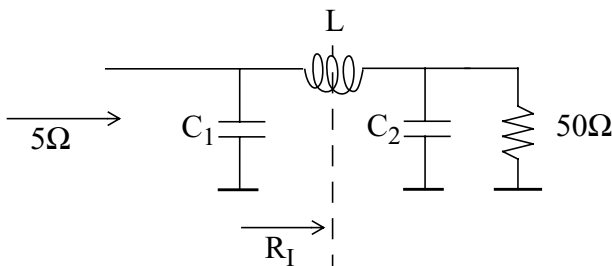

$$Q = 10$$

$$R_I \approx \frac{(\sqrt{R_{prim}} + \sqrt{R_L})^2}{Q^2} = 0.866\Omega$$

$$L = \frac{Q \cdot R_I}{\omega} = 1.4\text{nH}$$


$$Q_{left} = \sqrt{\frac{R_{prim}}{R_I} - 1} = \sqrt{\frac{5.0}{0.866} - 1} = 2.18 \quad Q_{right} = \sqrt{\frac{R_L}{R_I} - 1} = \sqrt{\frac{50}{0.866} - 1} = 7.53$$

$$Q = Q_{left} + Q_{right} = 9.7 \approx 10 \Rightarrow \text{close enough}$$

$$C_1 = \frac{Q_{left}}{\omega R_{prim}} = 70\text{pF} \quad C_2 = \frac{Q_{right}}{\omega R_L} = 24\text{pF}$$

$$\hat{I}_L = Q_{right} \cdot \frac{\hat{V}_L}{R_L} = 7.5 \cdot \frac{10}{50} = 1.5\text{A}$$

**c. T-match**

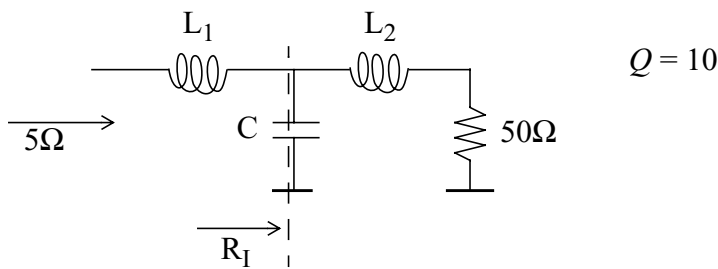


$$R_I = 300\Omega \Rightarrow Q = Q_{left} + Q_{right} = 7.68 + 2.24 = 9.92 \Rightarrow \text{close enough}$$

$$C = \frac{Q}{\omega R_I} = 52\text{pF} \quad L_1 = \frac{Q_{left} \cdot R_{prim}}{\omega} = 6.1\text{nH} \quad L_2 = \frac{Q_{right} \cdot R_L}{\omega} = 18\text{nH}$$

$$\hat{I}_{L_1} = \frac{\hat{V}_{prim}}{R_{prim}} = 0.63\text{A} \quad \hat{I}_{L_2} = \frac{\hat{V}_L}{R_L} = 0.20\text{A}$$

**d. Capacitive tap**

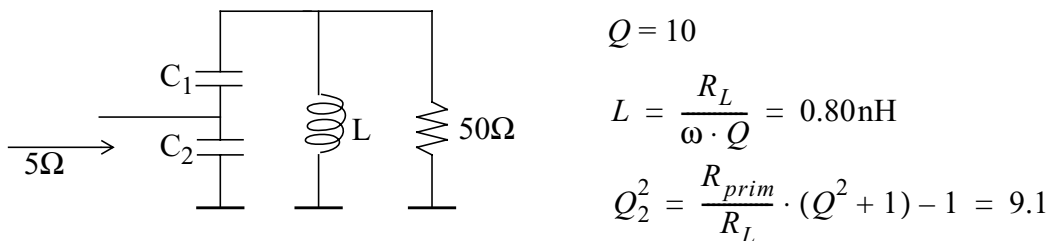

$$Q = 10$$

$$L = \frac{R_L}{\omega \cdot Q} = 0.80\text{nH}$$

$$Q_2^2 = \frac{R_{prim}}{R_L} \cdot (Q^2 + 1) - 1 = 9.1$$


$$C_2 = \frac{Q_2}{\omega \cdot R_L} = 9.6\text{pF} \quad C_1 = C_2 \cdot \frac{Q_2^2 + 1}{Q \cdot Q_2 - Q_2^2} = 4.2\text{pF}$$

$$\hat{I}_L = \frac{\hat{V}_L}{\omega \cdot L} = 2.0\text{A}$$

**e. Which solutions are integratable?**

All solutions have component values that are compatible with integration, but the large current levels may be a problem. Also the low intermediate resistance in (b) is a problem, since the series resistances in the components must be much smaller. Best suited for integration is (a).

### 3. Problem 4.5

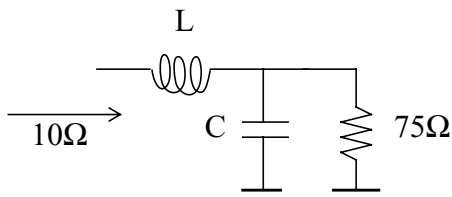


$$f_0 = 150\text{MHz}$$

$$Q = \sqrt{\frac{75}{10}} - 1 = 2.55$$

$$L = \frac{Q \cdot R_{prim}}{\omega_0} = 27\text{nH}$$

$$C = \frac{Q}{\omega_0 \cdot R_L} = 36\text{pF}$$

### 4. Problem 4.6

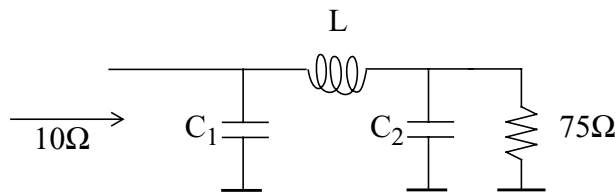


$$f_0 = 150\text{MHz}$$

$$BW = 15\text{MHz} \Rightarrow Q = \frac{BW}{f_0} = 10$$


$$R_I = 1.3\Omega \Rightarrow Q = Q_{left} + Q_{right} = 2.6 + 7.5 = 10.1 \Rightarrow \text{close enough}$$

$$L = \frac{Q \cdot R_I}{\omega_0} = 13.8\text{nH} \quad C_1 = \frac{Q_{left}}{\omega_0 R_{prim}} = 276\text{pF} \quad C_2 = \frac{Q_{right}}{\omega_0 R_L} = 106\text{pF}$$

### 5. Problem 8.5

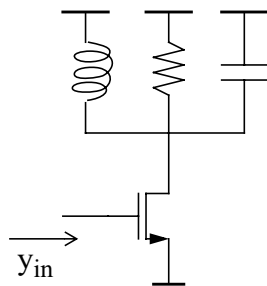

Small signal equivalent:

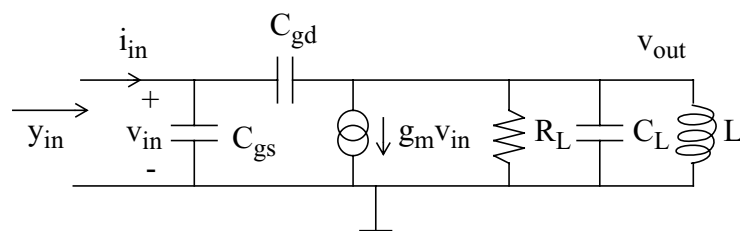

The negative real part of  $y_{in}$  occurs due to  $C_{gd}$  and the load being inductive at some frequencies. To simplify the calculations, assume  $C_{gd} \ll C_L$ , so that the influence of  $C_{gd}$  on the voltage gain can be disregarded:

$$v_{out} = -v_{in} \cdot g_m \cdot Z_L \Rightarrow A_v = -g_m \cdot Z_L$$

$$\text{Miller} \Rightarrow i_{in} = v_{in}(1 - A_v) \cdot sC_{gd} + sC_{gs} = v_{in} \cdot (1 + g_m Z_L) \cdot sC_{gd} + sC_{gs}$$

$$y_{in} = i_{in}/v_{in} = sC_{gd} \cdot (1 + g_m Z_L) + sC_{gs} = s(C_{gs} + C_{gd}) + sC_{gd} \cdot g_m Z_L$$

$$\text{The real part is due to the term} \quad sC_{gd} \cdot g_m Z_L = j\omega C_{gd} \cdot g_m Z_L$$

$$Z_L = \frac{1}{\frac{1}{R} + j\omega C_L + \frac{1}{j\omega L}} = \frac{1}{\frac{1}{R} + j\left(\omega C_L - \frac{1}{\omega L}\right)} = \frac{\frac{1}{R} - j\left(\omega C_L - \frac{1}{\omega L}\right)}{\left(\frac{1}{R}\right)^2 + \left(\omega C_L - \frac{1}{\omega L}\right)^2}$$

$$\text{Re}(y_{in}) = \text{Re}(j\omega C_{gd} \cdot g_m Z_L) = g_m \omega C_{gd} \cdot \frac{\omega C_L - \frac{1}{\omega L}}{\left(\frac{1}{R}\right)^2 + \left(\omega C_L - \frac{1}{\omega L}\right)^2} < 0 \Rightarrow \omega C_L < \frac{1}{\omega L}$$

$$\Rightarrow \omega < \frac{1}{\sqrt{L \cdot C_L}} = 2\pi \cdot f_0$$


The real part is negative below the resonance frequency.

Two solutions:

1. Minimize  $C_{gd}$  since  $y_{in}$  is proportional to  $C_{gd}$ . For example by cascoding or neutralization.
2. Make sure that  $\text{Re}(y_{gen}) > -\text{Re}(y_{in})$ , that is drive with low impedance.

## 6. Problem 8.7

a.

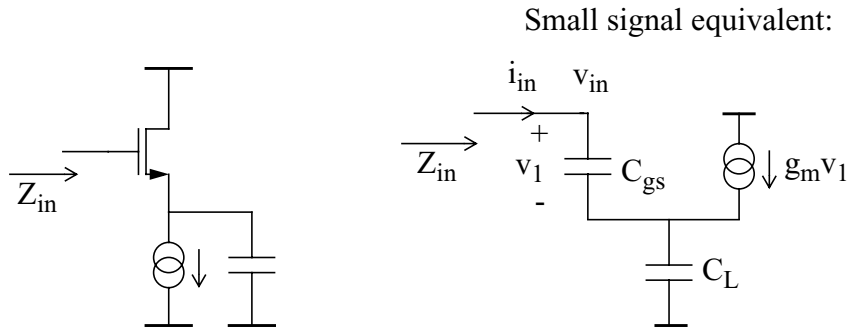

$$\begin{cases} g_m(v_{in} - v_{out}) + (v_{in} - v_{out})sC_{gs} - v_{out}sC_L = 0 \Rightarrow v_{in}(g_m + sC_{gs}) = v_{out}(g_m + sC_{gs} + sC_L) \\ i_{in} = (v_{in} - v_{out})sC_{gs} \end{cases}$$

$$i_{in} = \left( v_{in} - v_{in} \cdot \frac{g_m + sC_{gs}}{g_m + sC_{gs} + sC_L} \right) sC_{gs} = v_{in} \cdot \left( 1 - \frac{g_m + sC_{gs}}{g_m + sC_{gs} + sC_L} \right) sC_{gs}$$

$$\Rightarrow Z_{in} = \frac{v_{in}}{i_{in}} = \frac{g_m + s(C_{gs} + C_L)}{s^2 C_L C_{gs}} = -\frac{g_m + j\omega(C_{gs} + C_L)}{\omega^2 C_{gs} C_L} \Rightarrow \text{Re}(Z_{in}) = -\frac{g_m}{\omega^2 C_{gs} C_L}$$

b. As can be seen from (a) all  $C_L$  gives a negative  $\text{Re}(Z_{in})$  !

c. One way is to put a resistor  $R_p$  from the input to signal ground. If  $1/R_p > -1/\text{Re}(Y_{in})$ ,  $\text{Re}(Z_{in})$  will be positive.

$$Y_{in} = \frac{1}{Z_{in}} = -\frac{\omega^2 C_{gs} C_L}{g_m + j\omega(C_{gs} + C_L)} = -\frac{\omega^2 C_{gs} C_L (g_m - j\omega(C_{gs} + C_L))}{g_m^2 + \omega^2 (C_{gs} + C_L)^2}$$

$$\text{Re}(Y_{in}) = -\frac{g_m \omega^2 C_{gs} C_L}{g_m^2 + \omega^2 (C_{gs} + C_L)^2}$$

$$R_p < -\frac{1}{\text{Re}(Y_{in})} = \frac{g_m^2 + \omega^2 (C_{gs} + C_L)^2}{g_m \omega^2 C_{gs} C_L} = \frac{g_m}{\omega^2 C_{gs} C_L} + \frac{1}{g_m} \cdot \frac{(C_{gs} + C_L)^2}{C_{gs} C_L}$$

To get a positive real part at all frequencies:  $R_p < \frac{1}{g_m} \cdot \frac{(C_{gs} + C_L)^2}{C_{gs} C_L}$

## 7. Design problem

Max input signal = 0.15V(peak) => Set  $V_{gs} - V_t = 0.2V$  to avoid input clipping.  
Frequency = 1GHz, Bandwidth = 200MHz => Q=5

Test if 20nH inductor, which has a Q of 5 can be used:

$$R_{pL} = \omega L Q = 630 \Omega$$

$$A_v = g_m R_{pL} = 10 \Rightarrow g_m = 16 \text{mS}$$

$$g_m = \frac{2I_d}{V_{gs} - V_t} \Rightarrow I_d = 1.6 \text{mA}$$

$$\frac{W}{L} = \frac{I_d}{\mu C_{ox} (V_{gs} - V_t)^2} = 362, L = 0.4 \mu\text{m} \Rightarrow W = 145 \mu\text{m}$$

$$C_{db} = C_{jn} \cdot \frac{W}{2} \cdot 0.6 = 0.93 \cdot 72.5 \cdot 0.6 \text{fF} = 40 \text{fF} \quad (\text{fingered transistor layout})$$

$$C_{dg} = C_{gd0} \cdot W = 0.21 \cdot 145 \text{fF} = 30 \text{fF}$$

$$C_{dtot} = C_{db} + C_{dg} = 70 \text{fF}$$

Total capacitance needed to resonate with L at 1GHz:  $C_{tot} = \frac{1}{\omega_0^2 \cdot L} = 1.27 \text{pF}$

$$C = C_{tot} - C_{dtot} - C_L = 1.1 \text{pF} \quad (\text{In practice also correction for inductor parasitics needed})$$

The choice of inductance was fine (everything worked out to reasonable values).

It remains to choose  $V_{G1}$  and  $V_{G2}$ :

$$V_{G1} = V_t + 0.2 = 0.72 \text{V}$$

$$V_{G2} = V_t + 2V_{odmax} + 0.2 \text{V margin} = 0.52 + 2(0.2 + 0.15) + 0.2 = 1.42 \text{V}$$

$$\text{Maximum output signal swing: } v_{dd} - (1.42 - V_t) = 2.1 \text{V}$$

The amplifier can handle 2.1V(peak). It would have been sufficient with  $A_v V_{inmax} = 1.5 \text{V(peak)}$ .

This is OK, and the design is thereby successfully finished.