

# DSP Design

## Pipelining & Parallel Processing cont.

**Steffen Malkowsky**



# Repetition

- **DSP algorithms are non-terminating** = repeatedly execute same code
- **Iteration** = all operations are executed once
- **Iteration period** = time to perform one iteration
- **Sampling rate (throughput)** = number of samples per second
- **Latency** = time difference between output sample and corresponding input sample (how long before producing output samples)

**Block Diagram** - close to actual hardware – interconnected functional blocks, potentially with delay elements between blocks

**DFG** - Capture the data-driven nature of a DSP system, intra-iteration and inter-iteration constraints, nodes are computations (functions, subtasks), edges are data paths, very general description. Difference from block diagram: Hardware not allocated, scheduled in DFG.

# Repetition

- **Critical path** - the combinational path with maximum total execution time
- **Loop (=cycle)** - a path beginning and ending at same node
- **Loop bound for loop**


$$\frac{T_j}{W_j} \text{ loop computation time}$$

$$W_j \text{ number of delays in loop}$$

- **Iteration Bound** - maximum of all loop bounds

$$T_{\infty} = \max_{l \in L} \left\{ \frac{t_l}{w_l} \right\}$$

 
It is the lower bound on execution time for DFG (assuming only pipelining, retiming, unfolding)


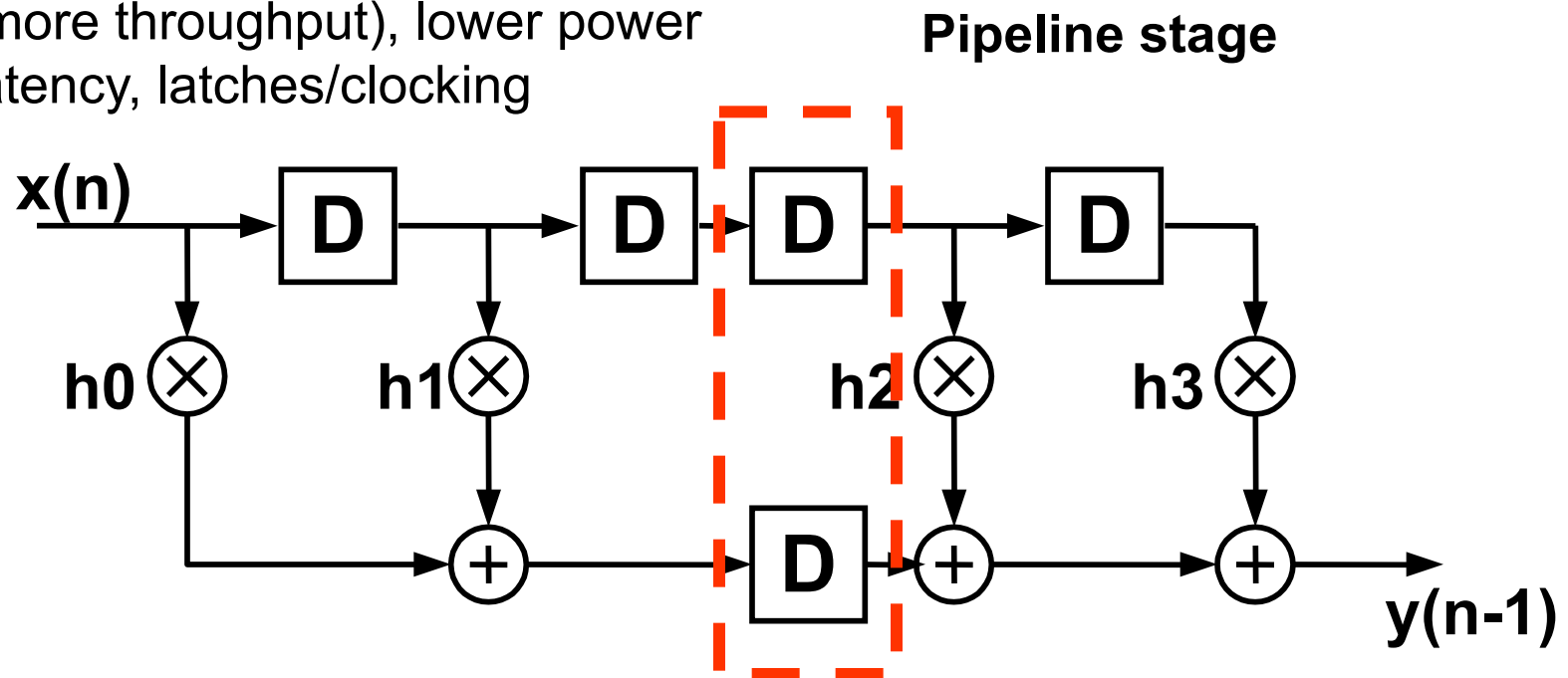
# Repetition

**Pipelining** - insert delay elements to reduce critical path length, In an  $M$ -level pipelined system, the number of delay elements in any path from input to output is  $(M-1)$  greater than that in the same path in the original sequential circuit


- + Faster (more throughput), lower power
- Added latency, latches/clocking




# Repetition

- Pipelining** - insert delay elements to reduce critical path length. In an  $M$ -level pipelined system, the number of delay elements in any path from input to output is  $(M-1)$  greater than that in the same path in the original sequential circuit

Sequential (critical path):

 


Pipelined: (critical path when  $M=3$ )

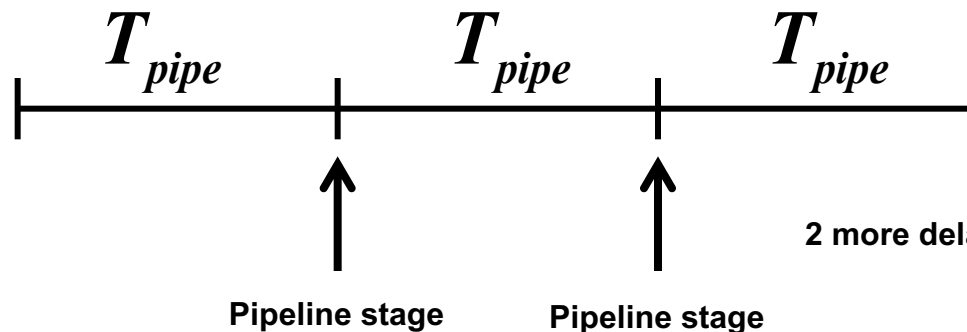

2 more delays in path [ $M-1=(3-1) = 2$ ]

# Repetition: Feedforward Cutsets

 


$$T_{\text{critical}} = 3 \Rightarrow 5 \Rightarrow 4 \Rightarrow 6$$

## Feedforward cutset


Must place delays  
on all edges in the  
cutset

# Repetition: Feedforward Cutsets

 

$$T_{\text{critical}} = 3 \Leftrightarrow 4 \Leftrightarrow 5 \Leftrightarrow 6$$

Not a  
Feedforward cutset


 


**Pipelining not possible**

**Let's continue...**




# Pipelining (cont.)

  

We said that the critical path could be cut in half by introducing pipelining.

Is that always true??
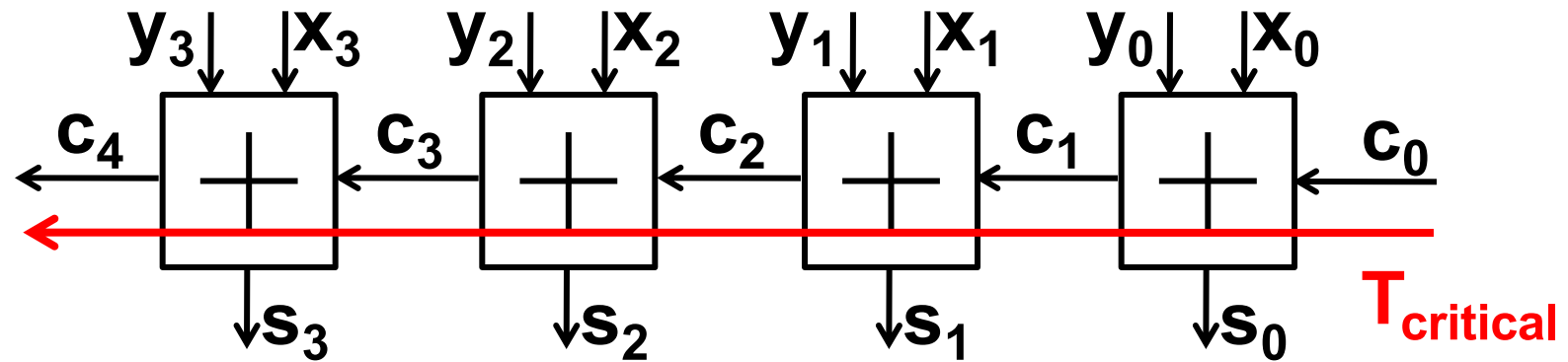
## Example: Pipelining when ripple-carry adders




Assume the delay in calculating the sum,  $S_{delay}$ , is equal to calculating the carry,  $C_{delay}$ .

What is the critical path?

$$4 \times C_{delay}$$

# Example: Pipelining when ripple-carry adders


Let's add a stage

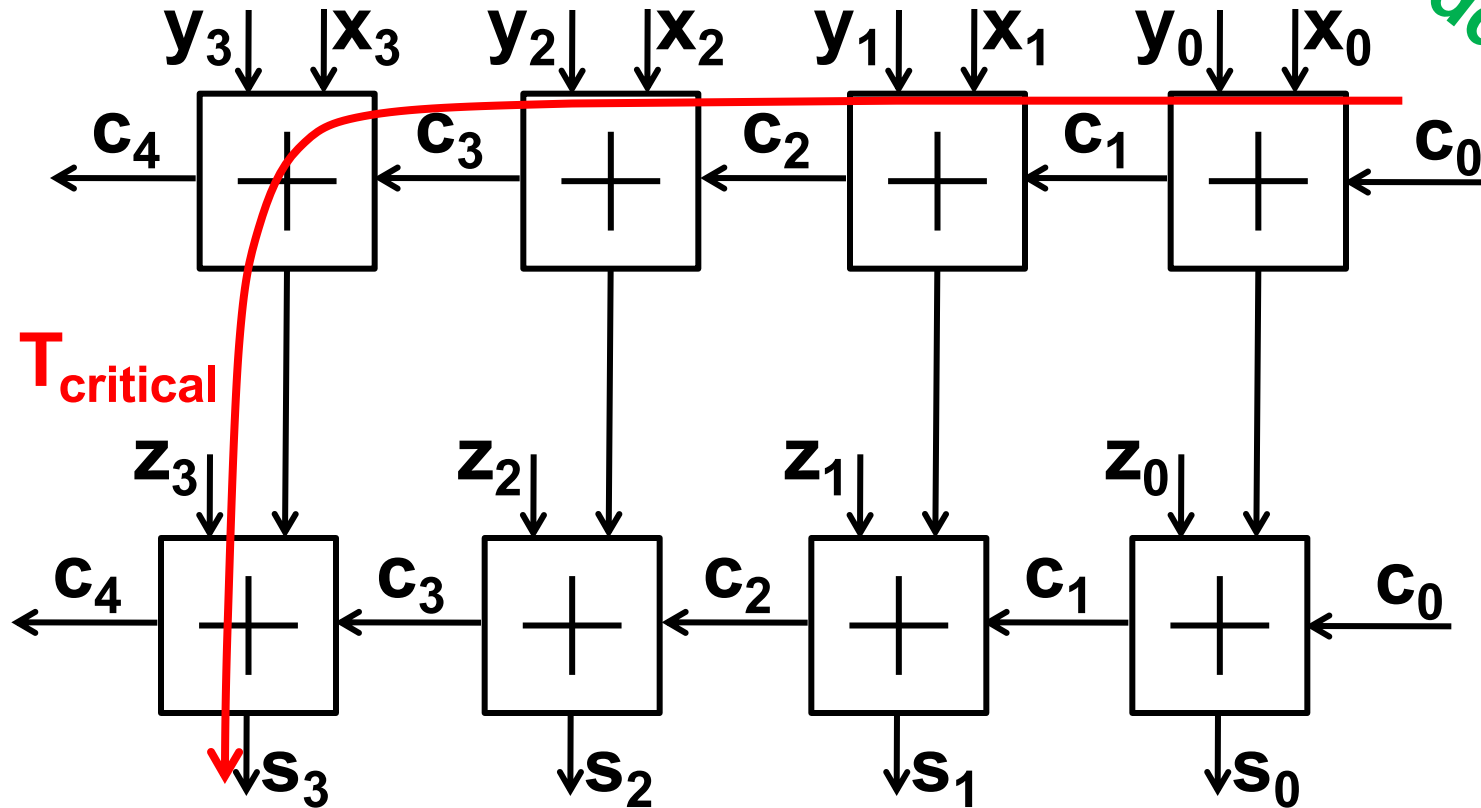

What is the critical path now?

$$4 \times C_{delay} + S_{delay} \approx 5 \times C_{delay}$$

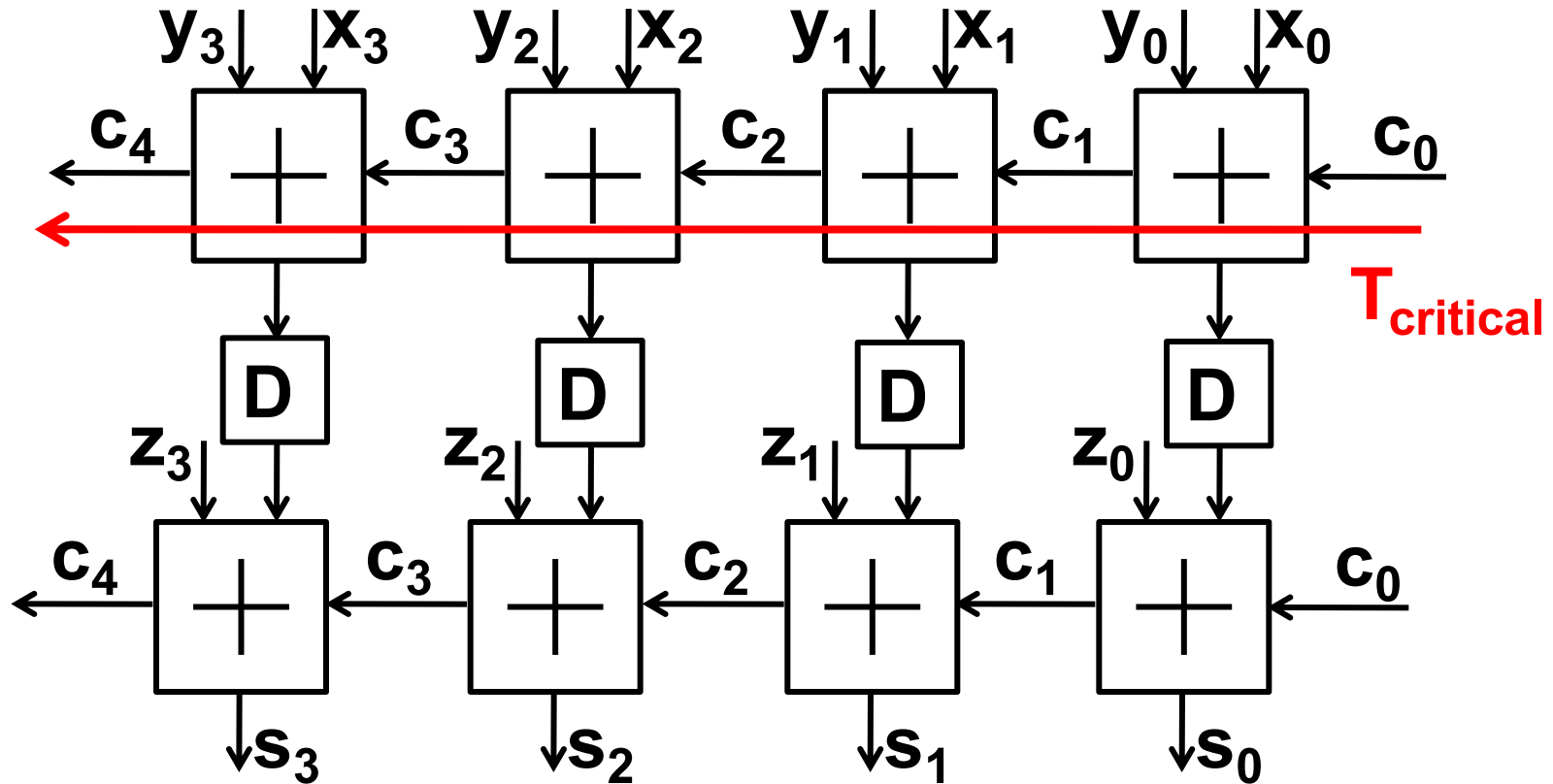
# Example: Pipelining when ripple-carry adders



What is the critical path now?

$$4 \times C_{delay}$$

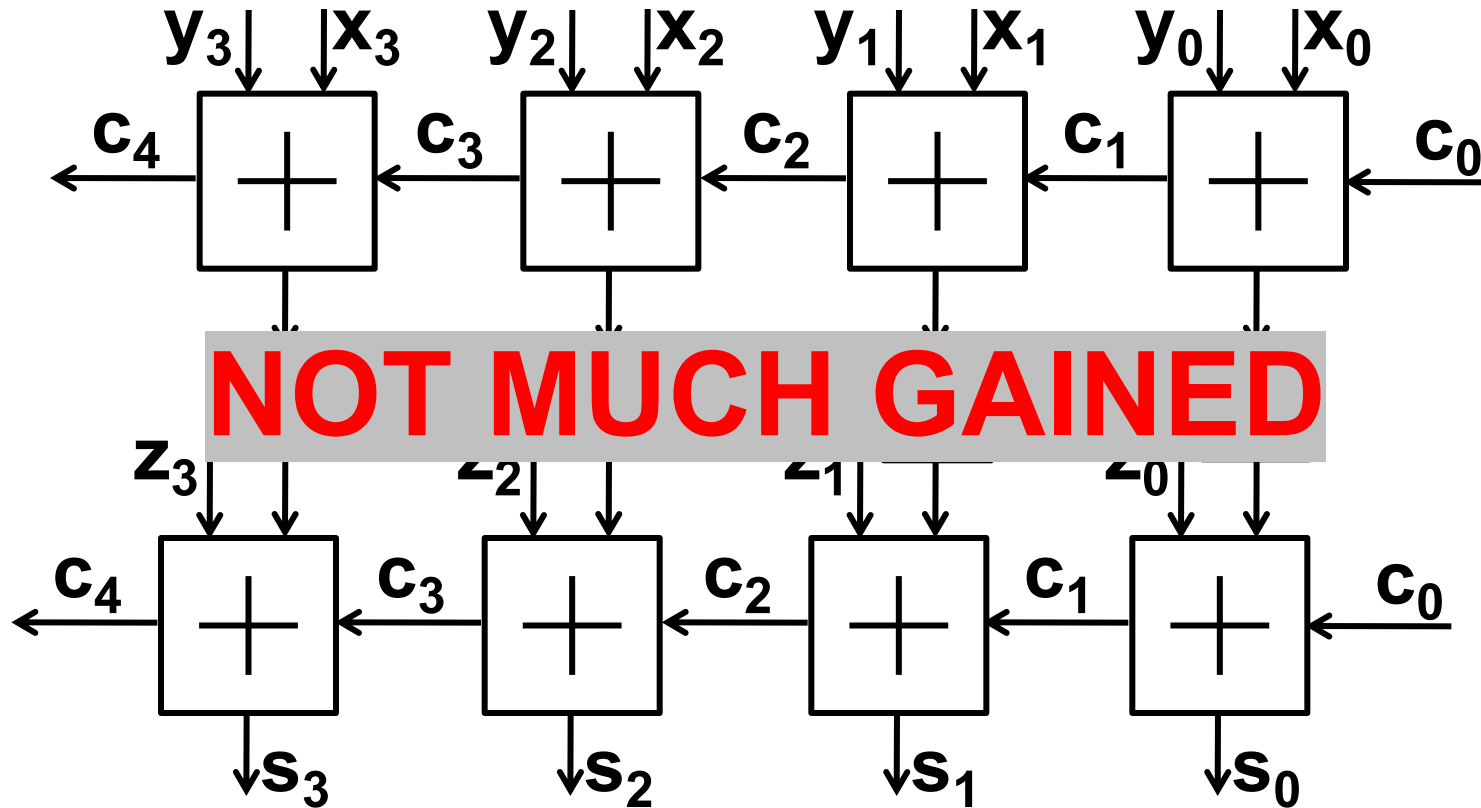
# Example: Pipelining when ripple-carry adders



What is the critical path now?

$$4 \times C_{\text{delay}}$$
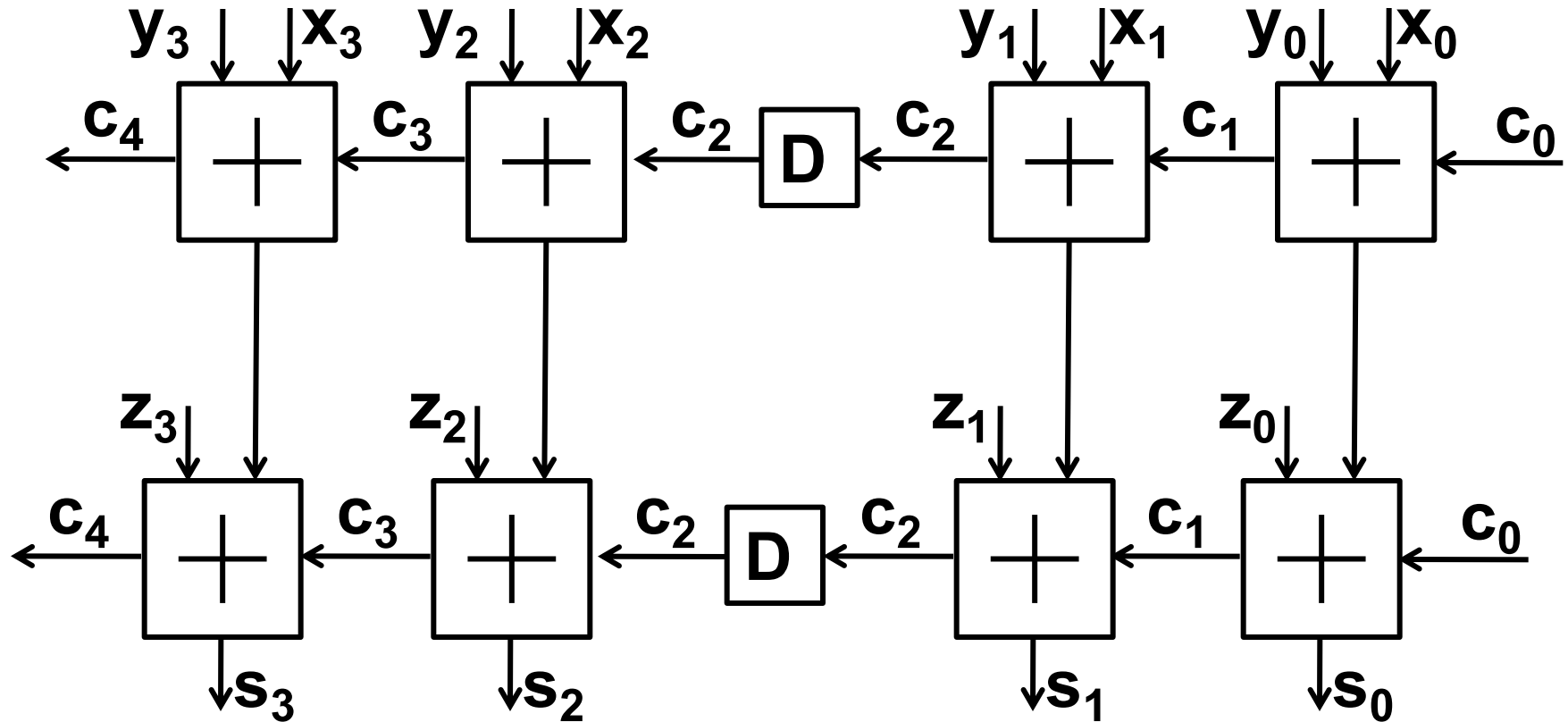
## Example: Pipelining when ripple-carry adders



What is the critical path now?

**Possible??**


# Conclusion

**The result depends on the structure of the used blocks, e.g. type of adder (ripple-carry, carry save, carry look-ahead,...).**

**We have to understand how the blocks work and if the critical paths are independent or if there is a relationship.**
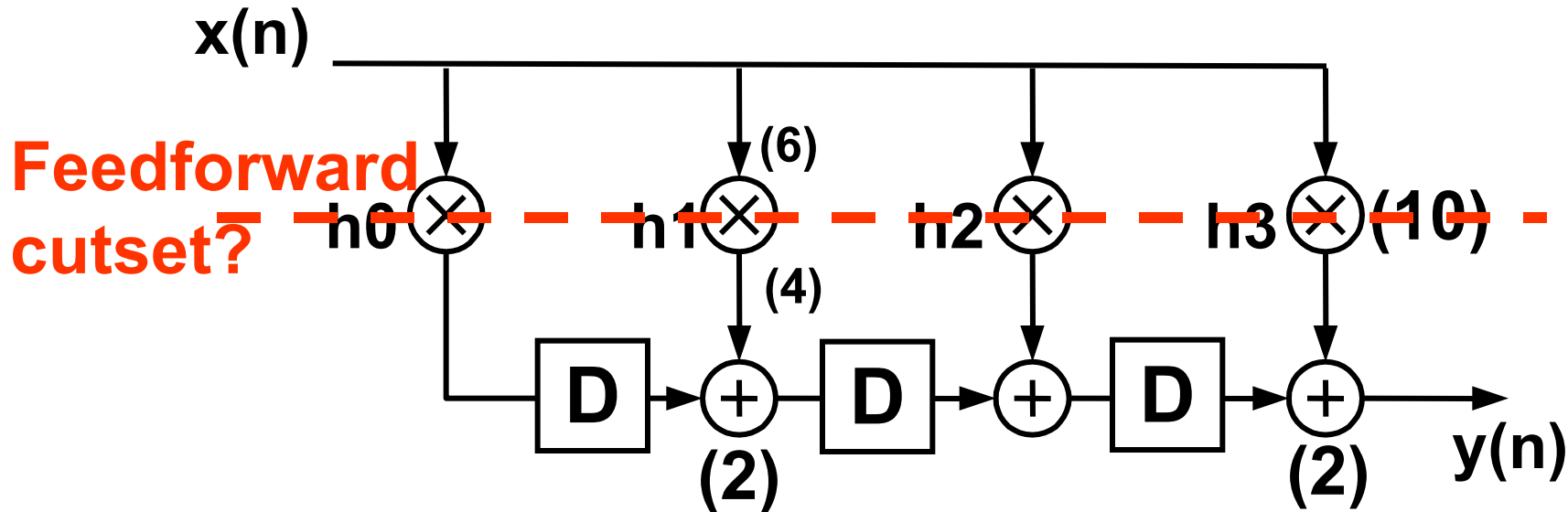
# Fine-Grain pipelining


- Let  $T_M=10$  units and  $T_A=2$  units. If the multiplier is broken into 2 smaller units with processing times of 6 units and 4 units, respectively (by placing the latches on the horizontal cutset across the multiplier), then the desired clock period can be achieved as  $(T_M+T_A)/2$






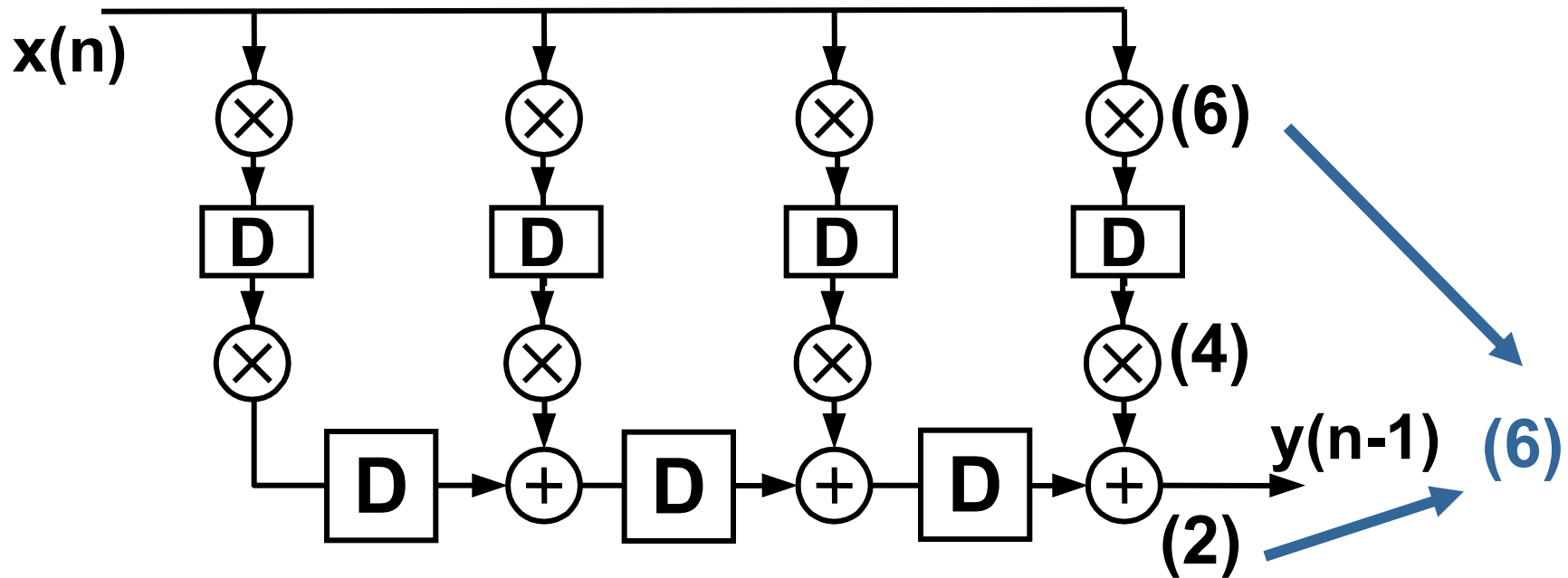
# Fine-Grain pielinging

- Equal paths. We get a more balanced design.
- A fine-grain pipelined version of the 3-tap data-broadcast FIR filter is shown below.



 
 
# Pipelining to Reduce Switching Activity

In chained operations there will be spurious transitions.





*Results from PhD student Rakesh Gangarajaiah*

# Synchronous Pipelining

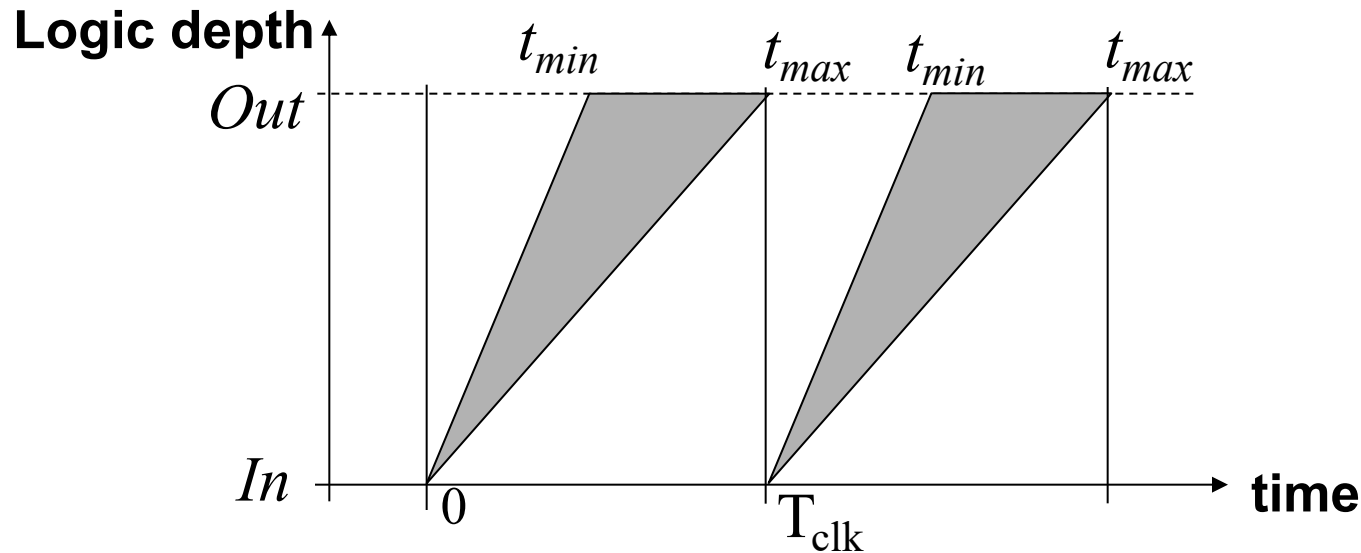 

# Wave Pipelining

 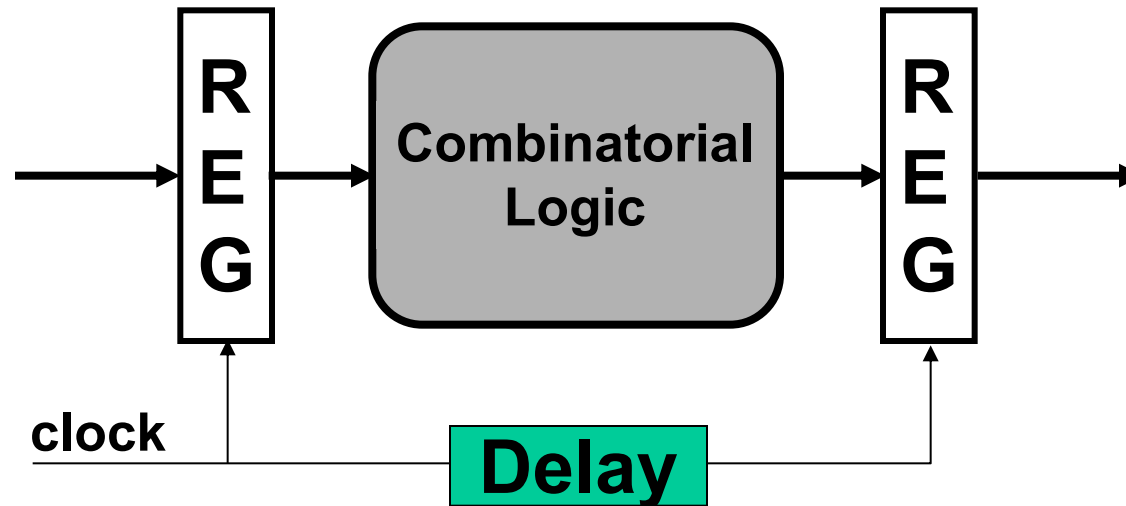

New input data is applied before the previous computation is done.


$$T_{clk} < T_{critical\ path}$$

# Wave pipelining: Pros and cons?


- + shorter  $T_{clk}$
- extensive simulation
- tedious design
- hard to verify
- lack of tools

# Parallel Processing

# Parallel Processing

 

$k=0,1,2,3...$

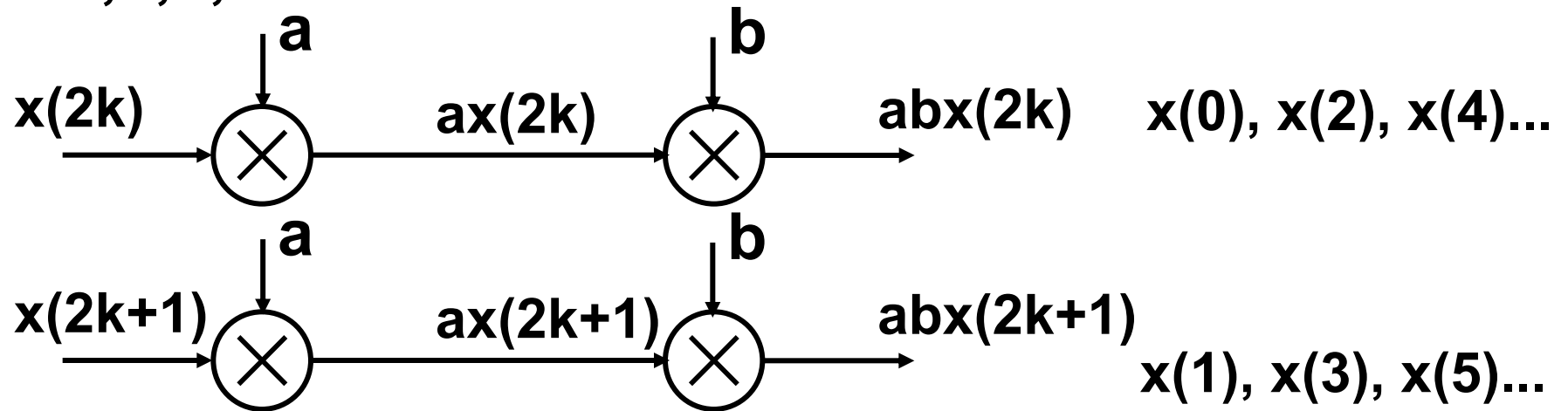

Two samples are processed in parallel

- double throughput

or

- lower power consumption due to reduced  $V_{DD}$


# Parallel Processing

- Parallel processing and pipelining techniques are duals of each other: **if a computation can be pipelined, it can also be processed in parallel.** Both of them exploit concurrency available in the computation in different ways.
- How to design a Parallel FIR system?
  - Consider a single-input single-output (SISO) FIR filter:
    - $y(n)=ax(n)+bx(n-1)+cx(n-2)$
  - Convert the SISO system into an MIMO (multiple-input multiple-output) system in order to obtain a parallel processing structure
    - To get a parallel system with 3 inputs per clock cycle

$$y(3k)=ax(3k)+bx(3k-1)+cx(3k-2)$$

$$y(3k+1)=ax(3k+1)+bx(3k)+cx(3k-1)$$

$$y(3k+2)=ax(3k+2)+bx(3k+1)+cx(3k)$$

 


Parallel processing system is also called **block processing**, and the number of inputs processed in a clock cycle is referred to as the **block size**



 
# Parallel Processing (cont'd)

- For example:

When block size is 2, 1 delay element = 2 sampling delays




 When block size is 10, 1 delay element = 10 sampling delays


 
## Ex. Parallel 3-Tap FIR

$$\begin{array}{l} \text{HW} \times 2 \\ \rightarrow \end{array} \left\{ \begin{array}{l} y(n) = b_0 x(n) + b_1 x(n-1) + b_2 x(n-2) \\ y(n+1) = b_0 x(n+1) + b_1 x(n) + b_2 x(n-1) \end{array} \right.$$




**$n$  changed to  $2k$**

$$\left\{ \begin{array}{l} y(2k) = b_0 x(2k) + b_1 x(2k-1) + b_2 x(2k-2) \\ y(2k+1) = b_0 x(2k+1) + b_1 x(2k) + b_2 x(2k-1) \end{array} \right.$$
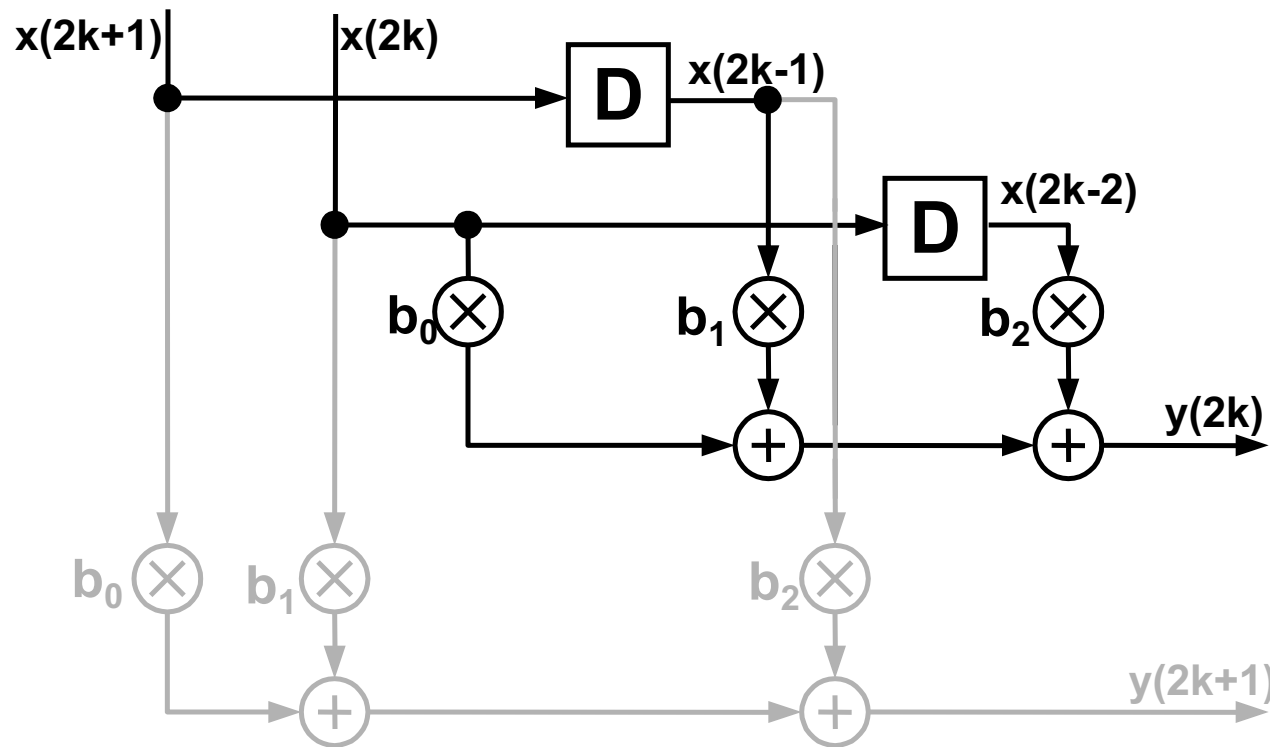
# Parallel 3-Tap (2)

$$\begin{cases} y(2k) = b_0x(2k) + b_1x(2k-1) + b_2x(2k-2) \\ y(2k+1) = b_0x(2k+1) + b_1x(2k) + b_2x(2k-1) \end{cases}$$




**k=0** 
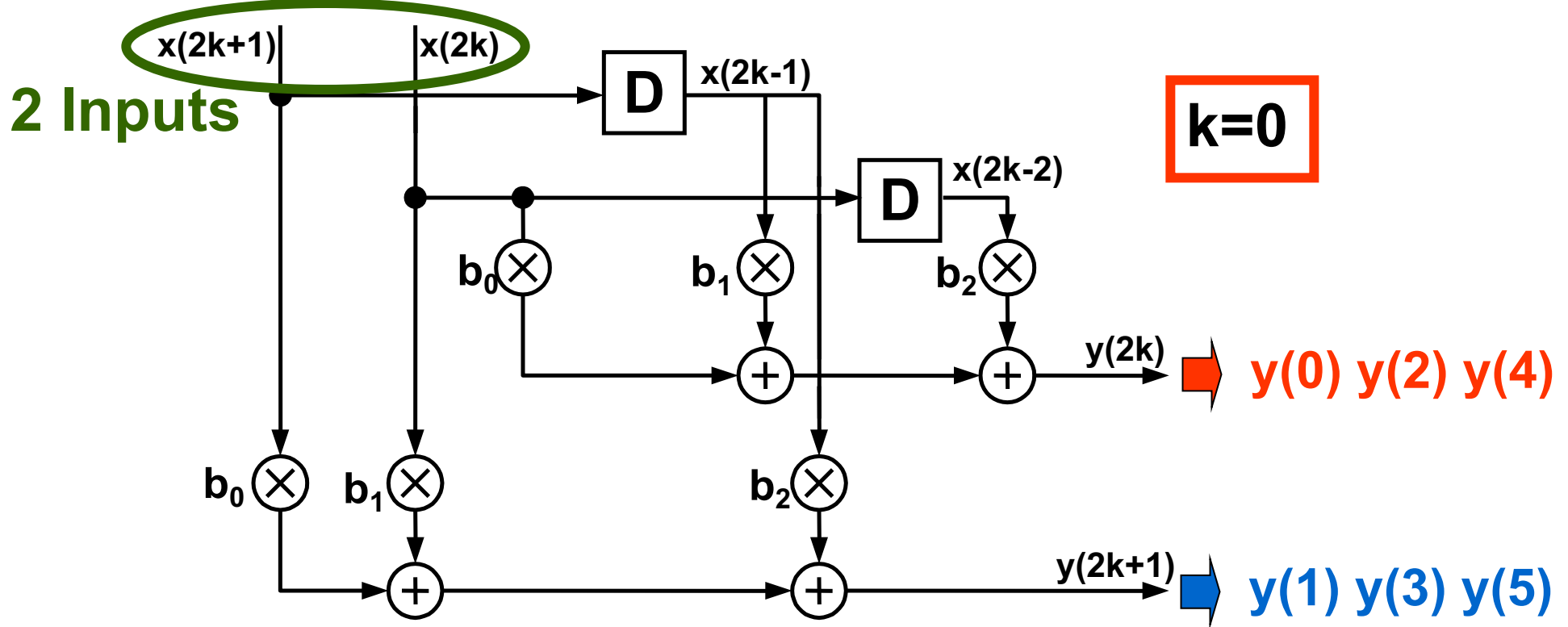
# Parallel 3-Tap (3)


$x(5)$   $x(4)$   
 $x(3)$   $x(2)$   
 $x(1)$   $x(0)$

$$\begin{cases} y(0) = b_0 x(0) + b_1 x(-1) + b_2 x(-2) \\ y(1) = b_0 x(1) + b_1 x(0) + b_2 x(-1) \end{cases}$$



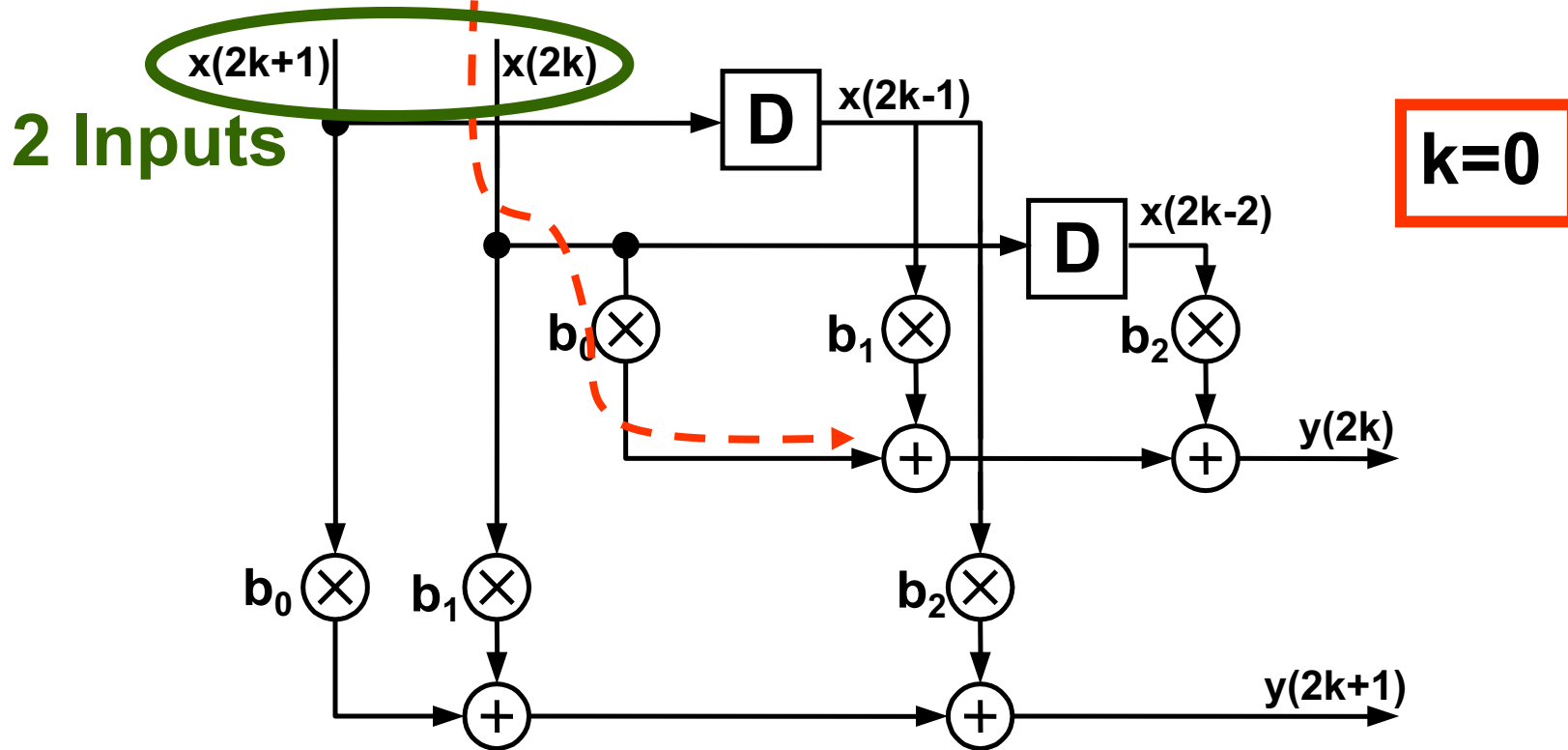
# Parallel 3-Tap (4)

$$\begin{cases} y(0) = b_0 x(0) + b_1 x(-1) + b_2 x(-2) \\ y(1) = b_0 x(1) + b_1 x(0) + b_2 x(-1) \end{cases}$$



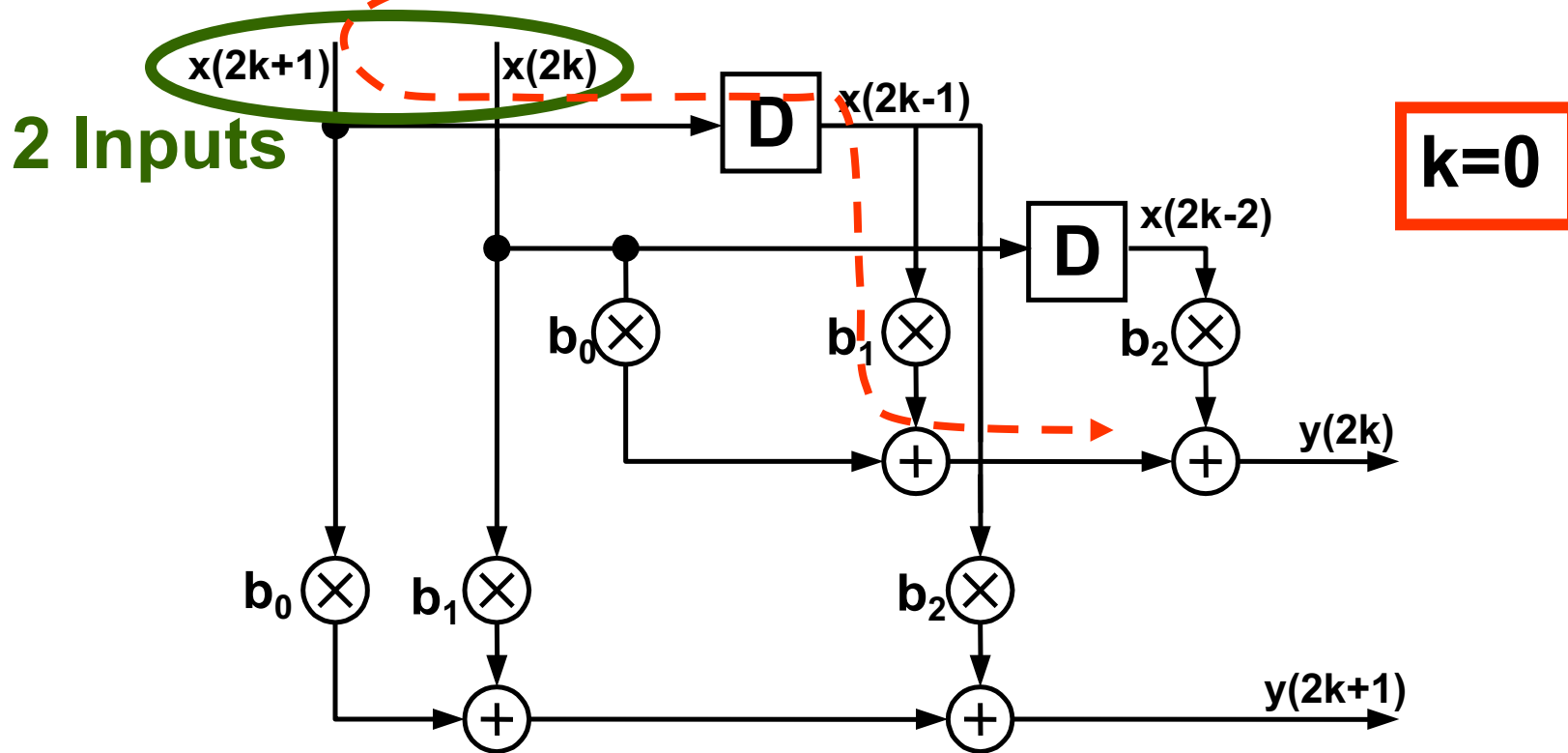
# Parallel 3-Tap (4)

$$\begin{cases} y(0) = b_0 x(0) + b_1 x(-1) + b_2 x(-2) \\ y(1) = \cancel{b_0 x(1)} + b_1 x(0) + b_2 x(-1) \end{cases}$$



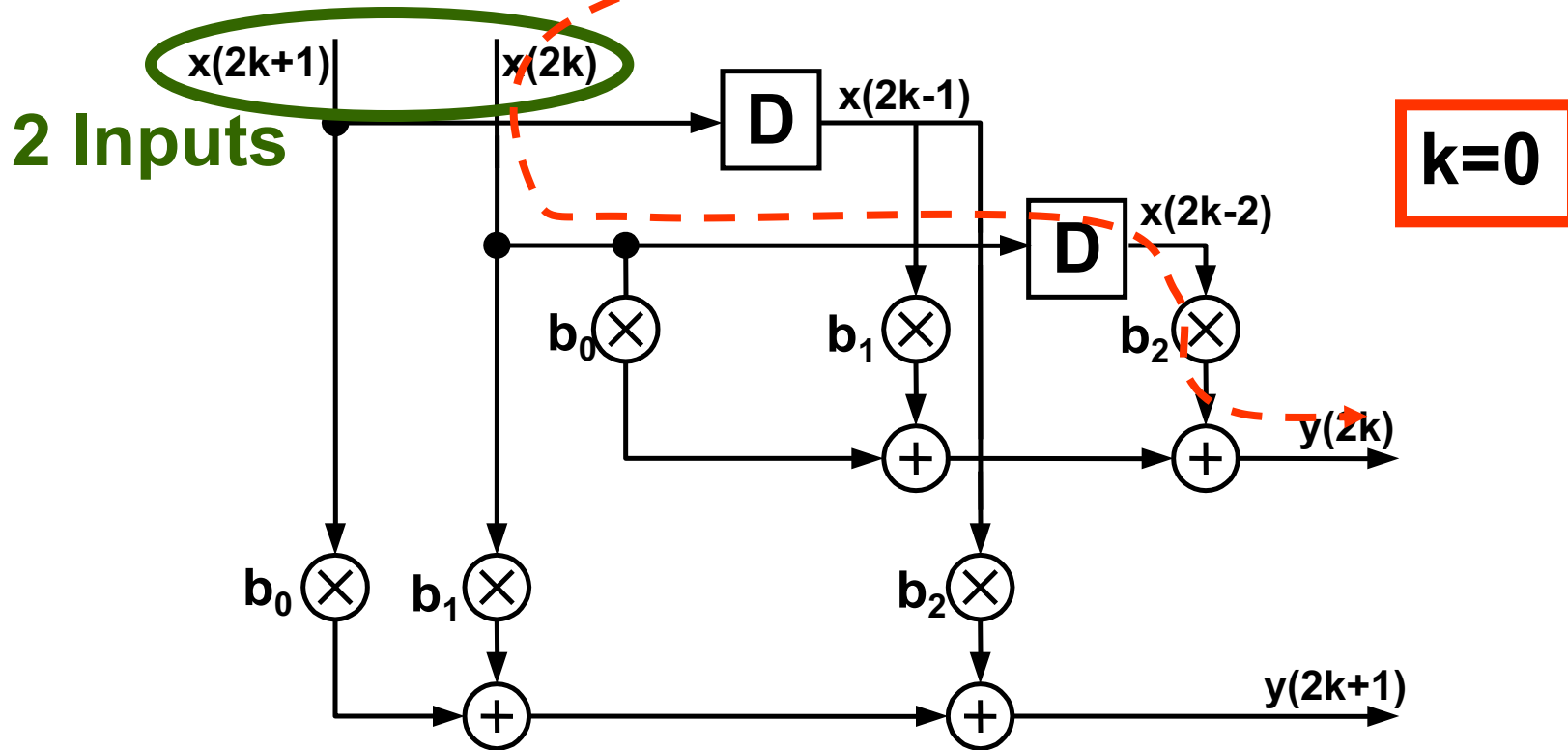
# Parallel 3-Tap (4)

$$\begin{cases} y(0) = b_0 x(0) + b_1 x(-1) + b_2 x(-2) \\ y(1) = b_0 x(1) + b_1 x(0) + b_2 x(-1) \end{cases}$$


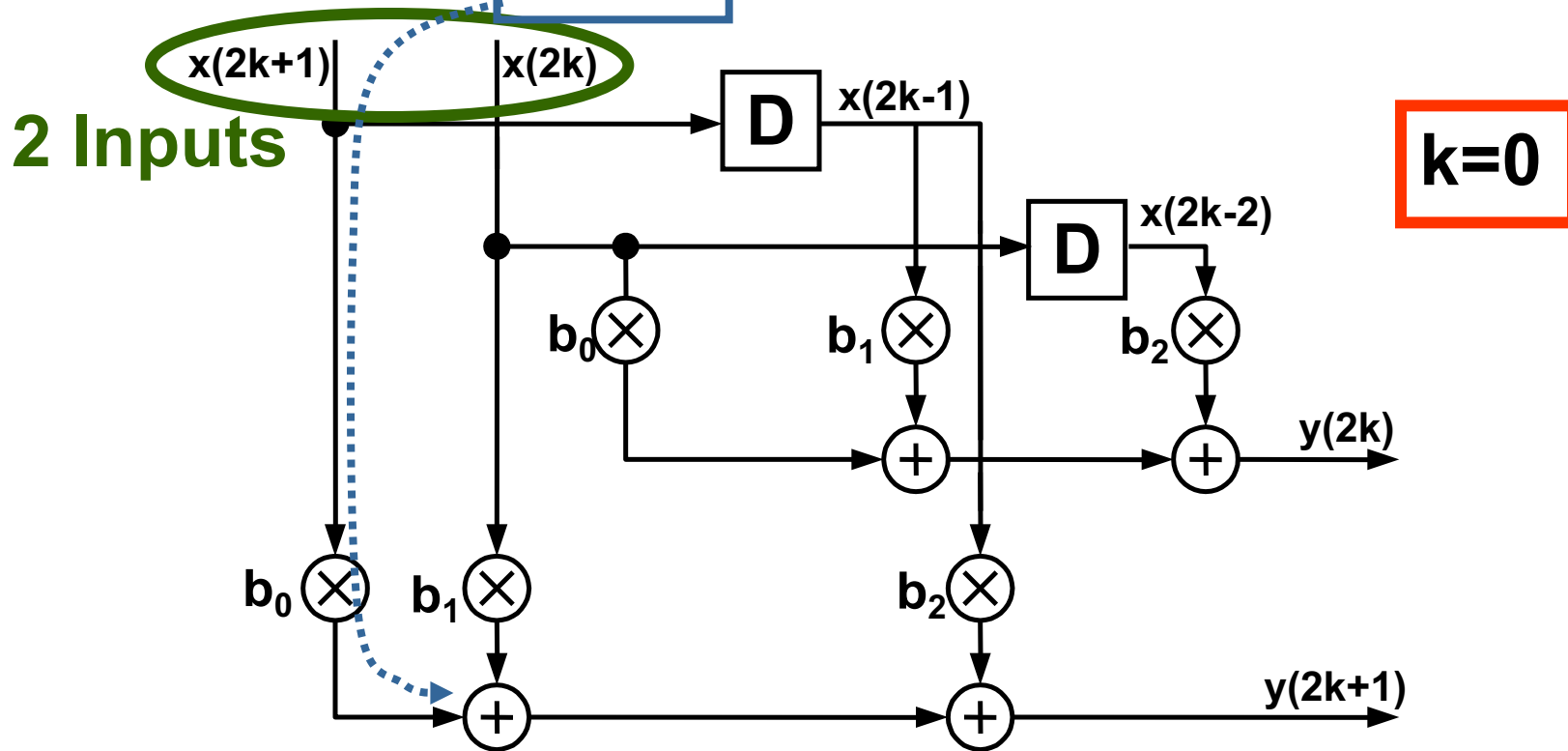
# Parallel 3-Tap (5)


$$\begin{cases} y(0) = b_0 x(0) + b_1 x(-1) + b_2 x(-2) \\ y(1) = b_0 x(1) + b_1 x(0) + b_2 x(-1) \end{cases}$$





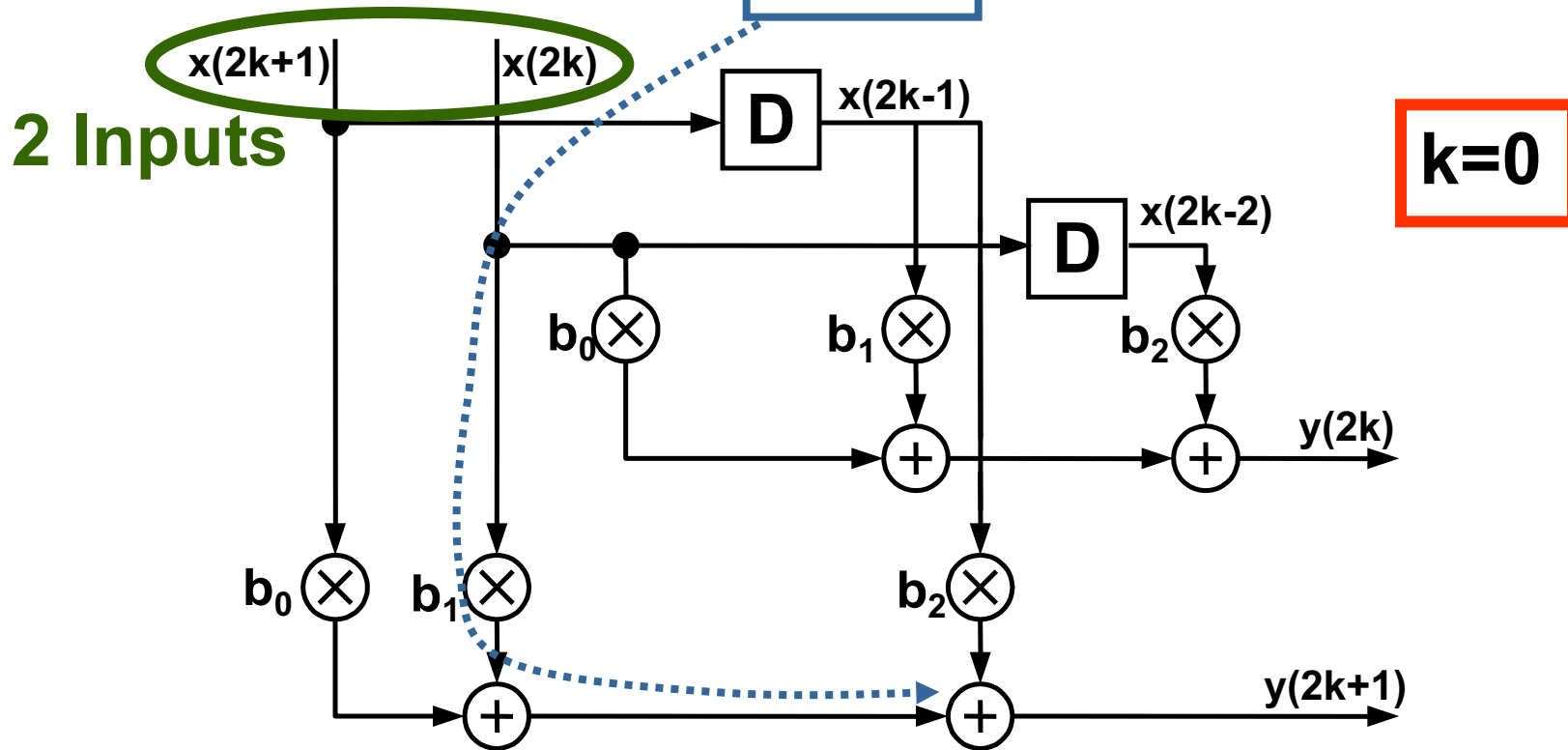
# Parallel 3-Tap (5)

$$\begin{cases} y(0) = b_0 x(0) + b_1 x(-1) + b_2 x(-2) \\ y(1) = b_0 x(1) + b_1 x(0) + b_2 x(-1) \end{cases}$$


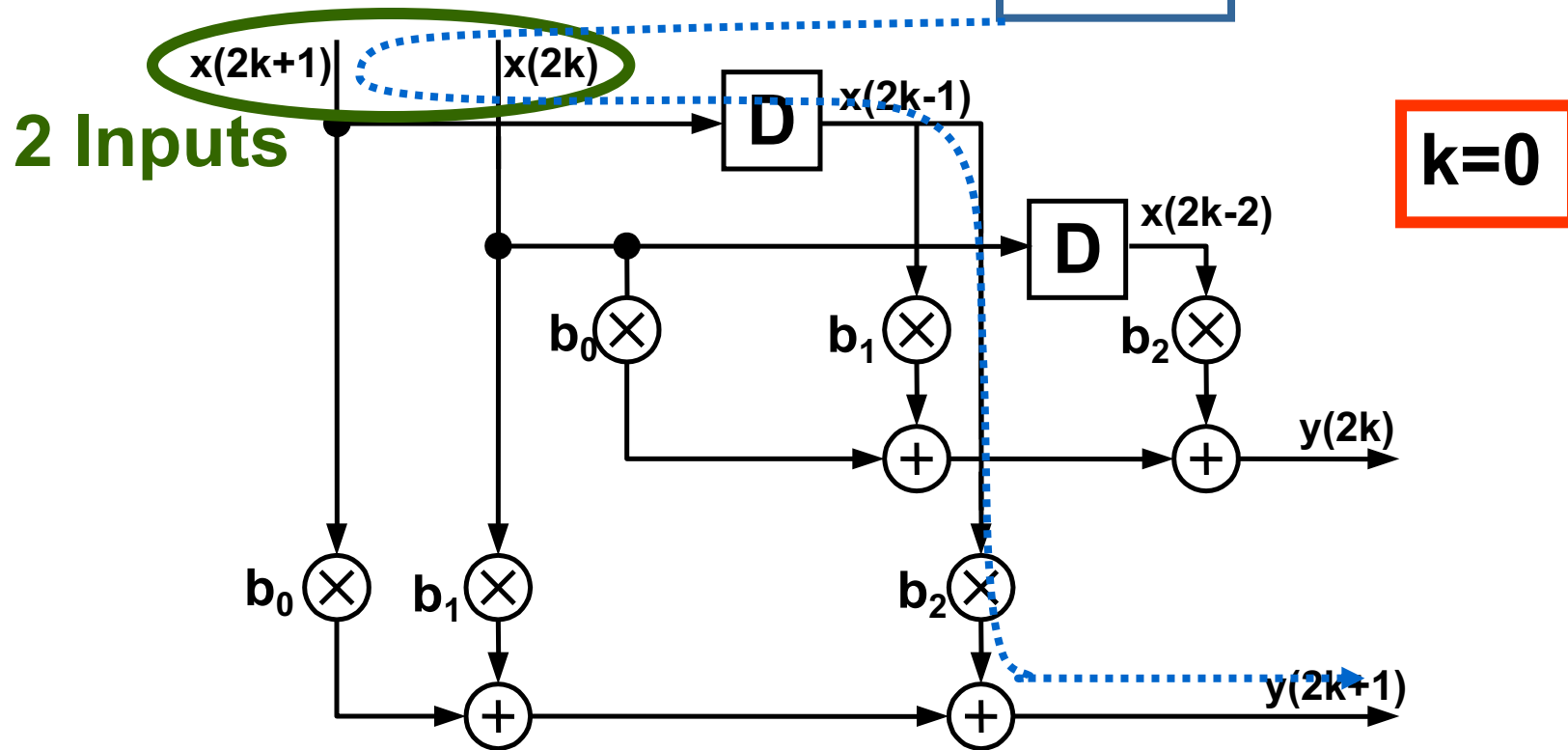
# Parallel 3-Tap (5)

$$\begin{cases} y(0) = b_0 x(0) + b_1 x(-1) + b_2 x(-2) \\ y(1) = b_0 x(1) + b_1 x(0) + b_2 x(-1) \end{cases}$$



## Parallel Processing (cont'd)

- Note: The critical path of the block (or parallel) processing system remains unchanged. But since  $L$  samples are processed in 1 clock cycle, the iteration (or sample) period is given by the following equations:

$$T_{clock} \geq T_M + 2T_A \quad \text{for a 3-tap FIR filter}$$


$$T_{iteration} = T_{sample} = \frac{T_{clock}}{L}$$

- So, it is important to understand that in a parallel system

$$T_{sample} \neq T_{clock}, \text{ whereas in a pipelined system } T_{sample} = T_{clock}$$
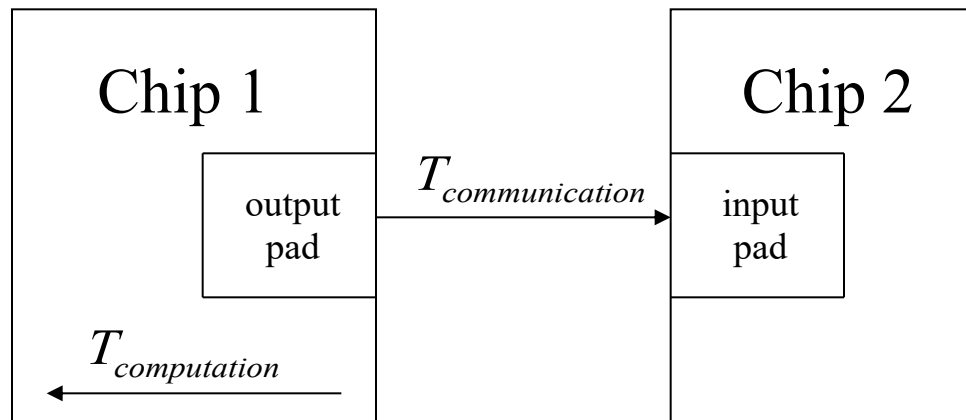
# Parallel Processing (cont'd)

- Why use parallel processing when pipelining can be used equally well?
  - Consider the following chip set: when the critical path is less than the I/O bound (output-pad delay plus input-pad delay and the wire delay between the two chips), we say this system is **communication bounded**
  - So, we know that pipelining can be used only to the extent such that the critical path computation time is limited by the communication (or I/O) bound. Once this is reached, pipelining can no longer increase the speed



## Parallel Processing (cont'd)


- So, in such cases, pipelining can be combined with parallel processing to further increase the speed of the DSP system
- By combining parallel processing (block size:  $L$ ) and pipelining (pipelining stage:  $M$ ), the sample period can be reduced to:

$$T_{iteration} = T_{sample} = \frac{T_{clock}}{L \cdot M}$$


- Parallel processing can also be used for reduction of power consumption while using slow clocks

# Parallel Processing- Converters

- **A serial-to-parallel converter**

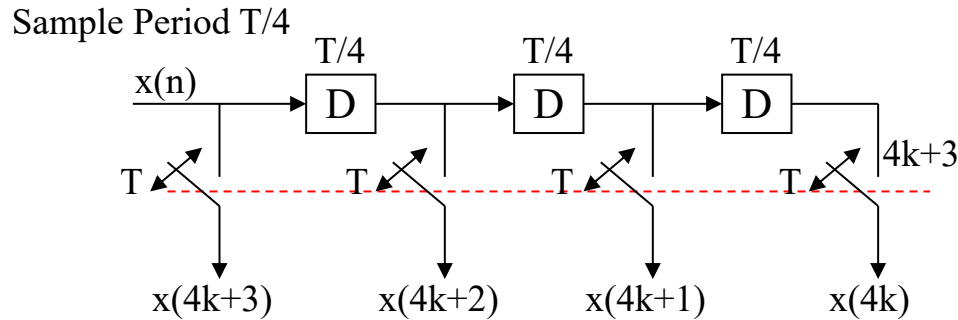

- **A parallel-to-serial converter**

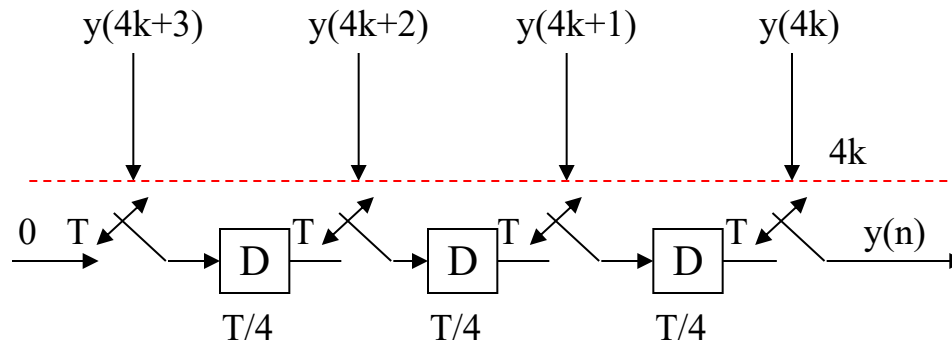

# Pipelining and Parallel Processing for Low Power



# Power Dissipation

**Two measures are important**

- **Peak power (sets dimensions)**

$$P_{\text{peak}} = V_{\text{DD}} \times I_{\text{DDmax}}$$

- **Average power (battery and cooling)**


$$P_{\text{av}} = \frac{V_{\text{DD}}}{T} \int_0^T i_{\text{DD}}(t) dt$$

**or rather "the energy".**



 
# Power consumption in CMOS

Gaining more  
importance with  
technology scaling


 
$$P_{\text{total}} = P_{\text{dynamic}} + P_{\text{short-circuit}} + P_{\text{static}}$$



The one we will look at  
and reduce with  
pipelining and  
parallelism

# CMOS Power Consumption


$$\begin{aligned} P_{\text{tot}} &= P_{\text{dynamic}} + P_{\text{short-circuit}} + P_{\text{static}} = \\ &= \alpha f C_L V_{\text{DD}}^2 + V_{\text{DD}} I_{\text{sc}} + I_{\text{leakage}} V_{\text{DD}} \end{aligned}$$

$\alpha$  = probability for switching


$$C_L = C_{\text{charge}}$$
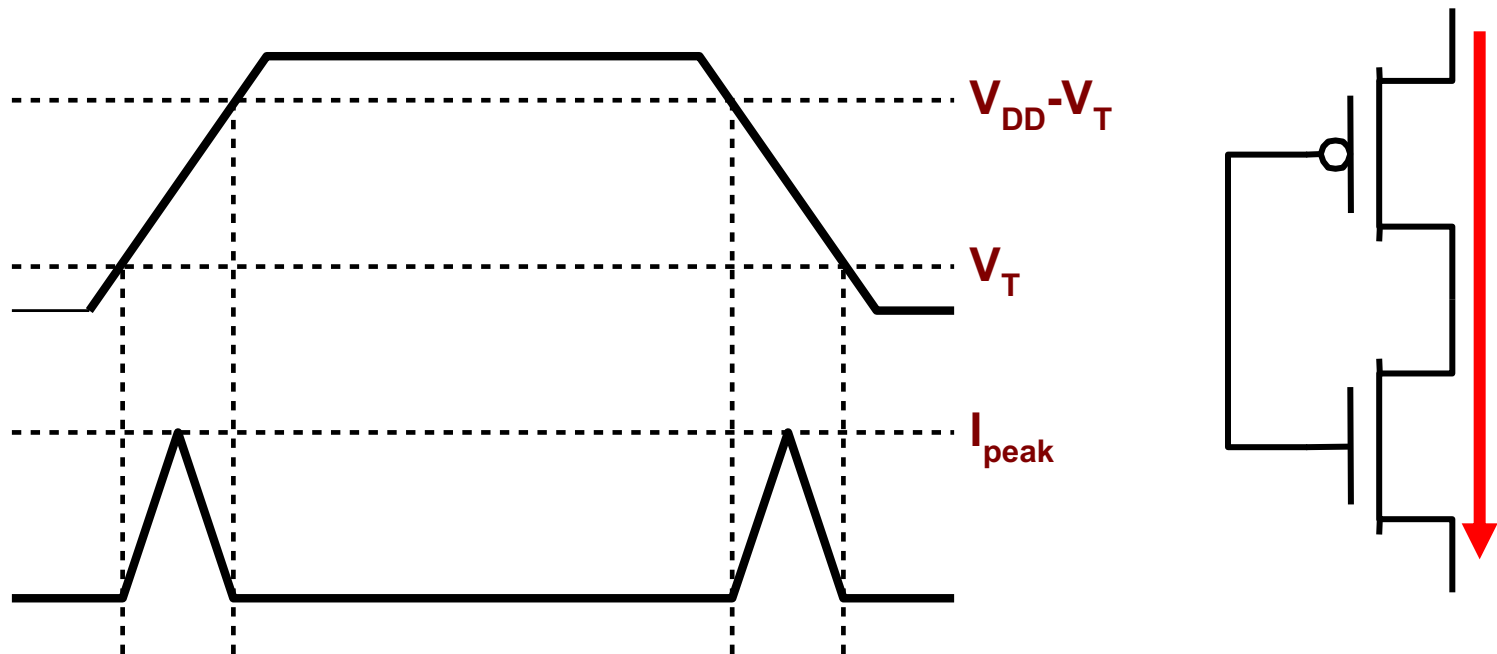
# Short Circuit - Current Spikes

Current peak when both N- and PMOS are open


 
# Static Power Consumption due to leakage current



Drain Leakage

$I_{leakage}$

Subthreshold  
Current


$$P_{stat} = I_{leakage} \times V_{DD}$$

$I_{leakage}$  increases  
with decreasing  $V_T$
 
# $V_T$ Scaling: $V_T$ and $I_{OFF}$ Trade-off

Performance vs  
Leakage:


$V_T \downarrow \Rightarrow I_{OFF} \uparrow$



$\Rightarrow$  As  $V_T$  decreases, sub-threshold leakage increases
 
# Dynamic Power Consumption

Assumed that  $V_{\text{swing}} = V_{\text{DD}}$



Energy charged in a capacitor

$$E_C = CV^2/2 = C_L V_{DD}^2/2$$

Energy  $E_C$  is also discharged, i.e.

$$E_{\text{tot}} = C_L V_{DD}^2$$

Power consumption

$$P = C_L V_{DD}^2 f (=C_{\text{tot}} V_0^2 f)$$



Since squared most efficient to reduce P

# Reduce...

## Capacitances

- Transistor/Gate C
- Load C
- Interconnects, more and more important
- External

## Activity

## Frequency

Power supply – squared so most efficient

**...without reducing performance?.**

# Propagation Delay in CMOS


$$T_{pd} = \frac{C_L \cdot V_{DD}}{k(V_{DD} - V_T)^2}, \quad k \propto \mu, \frac{W}{L}, C_{ox}$$

if  $V_{DD} \gg V_T$

$$T_{pd} = \frac{C_L}{kV_{DD}} = \frac{1}{f} \Rightarrow \text{proportional to } \frac{f}{V_{DD}}$$



# Pipelining, *power consumption*

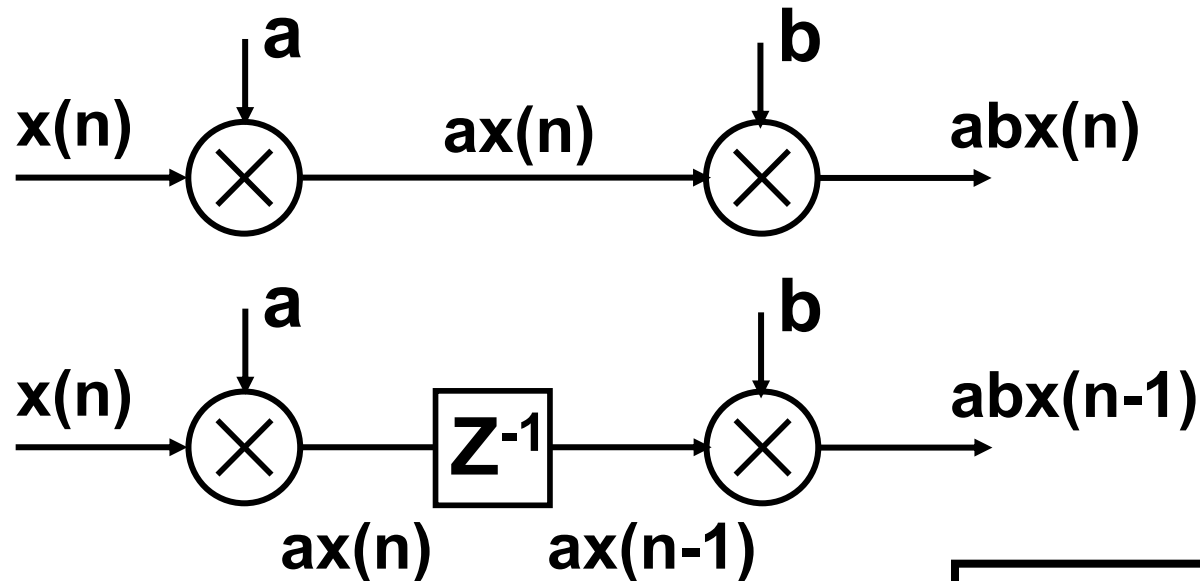

**Critical path cut in half**

- double  $f \Rightarrow$  double throughput

or


- same  $f \Rightarrow$  double time for mult  $\Rightarrow$  reduced  $V_{DD}$

$$P = f C V_{DD}^2$$

# Reduction of Critical Path

Propagation delay of the original filter and the pipelined filter

Sequential (critical path):

 

Pipelined: (critical path when M=3)



# Pipelining, *power consumption*

- The power consumption in original architecture

$$P_{seq} = f C_L V_{DD}^2$$

- The supply voltage can be reduced to  $\beta V_{DD}$ , ( $0 < \beta < 1$ ).  
Hence, the power consumption of the pipelined filter is:

$$P_{pipe} = f C_L (\beta V_{DD})^2 = \beta^2 P_{seq}$$

# Pipelining

Propagation delays of the sequential and the pipelined architecture:

$$T_{seq} = \frac{C_L \cdot V_{DD}}{k(V_{DD} - V_T)^2}, \quad T_{pip} = \frac{(C_L/M) \cdot \beta V_{DD}}{k(\beta V_{DD} - V_T)^2}$$


The capacitance in each stage has been reduced.

Since the same  $f$  is maintained  $\Rightarrow T_{seq} = T_{pipe}$

$$M(\beta V_{DD} - V_T)^2 = \beta(V_{DD} - V_T)^2$$
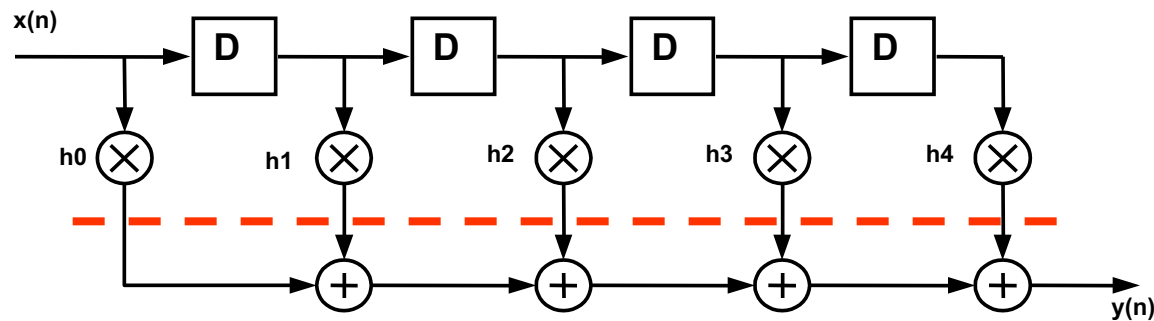
# Pipelining

$$M(\beta V_{DD} - V_T)^2 = \beta(V_{DD} - V_T)^2$$




$$T_{add} = 1$$

$$T_{mult} = 3$$

$$M = ?$$
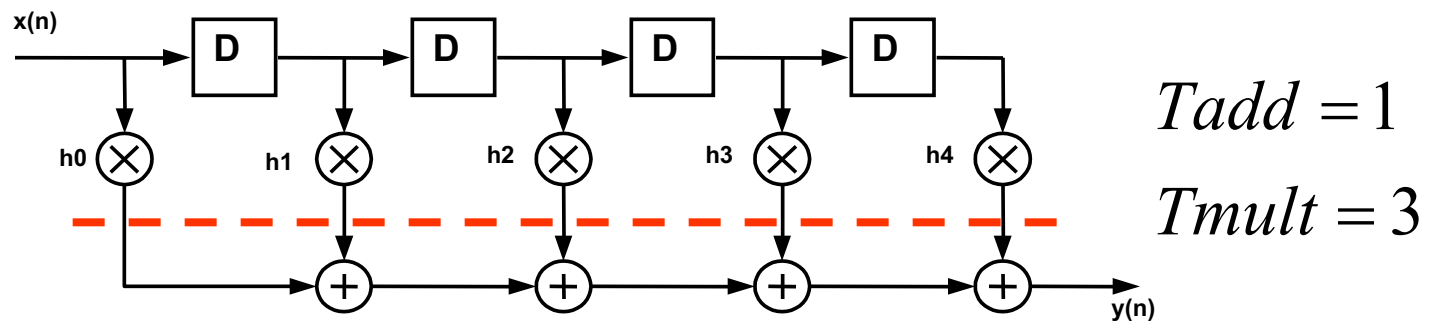
# Pipelining

$$M(\beta V_{DD} - V_T)^2 = \beta(V_{DD} - V_T)^2$$



$$T_{original} = T_{mult} + 4T_{add} = 7t.u.$$

$$T_{Pipelined} = 4T_{add} = 4t.u.$$





$$M = \frac{7}{4}$$

If  $M$  doesn't divide the critical path evenly you have to use the "real  $M$ ",  
i.e. how big is the actual reduction of the critical path.

# Example: simple datapath

$$P = f C V^2$$

**C = the total switched capacitance**

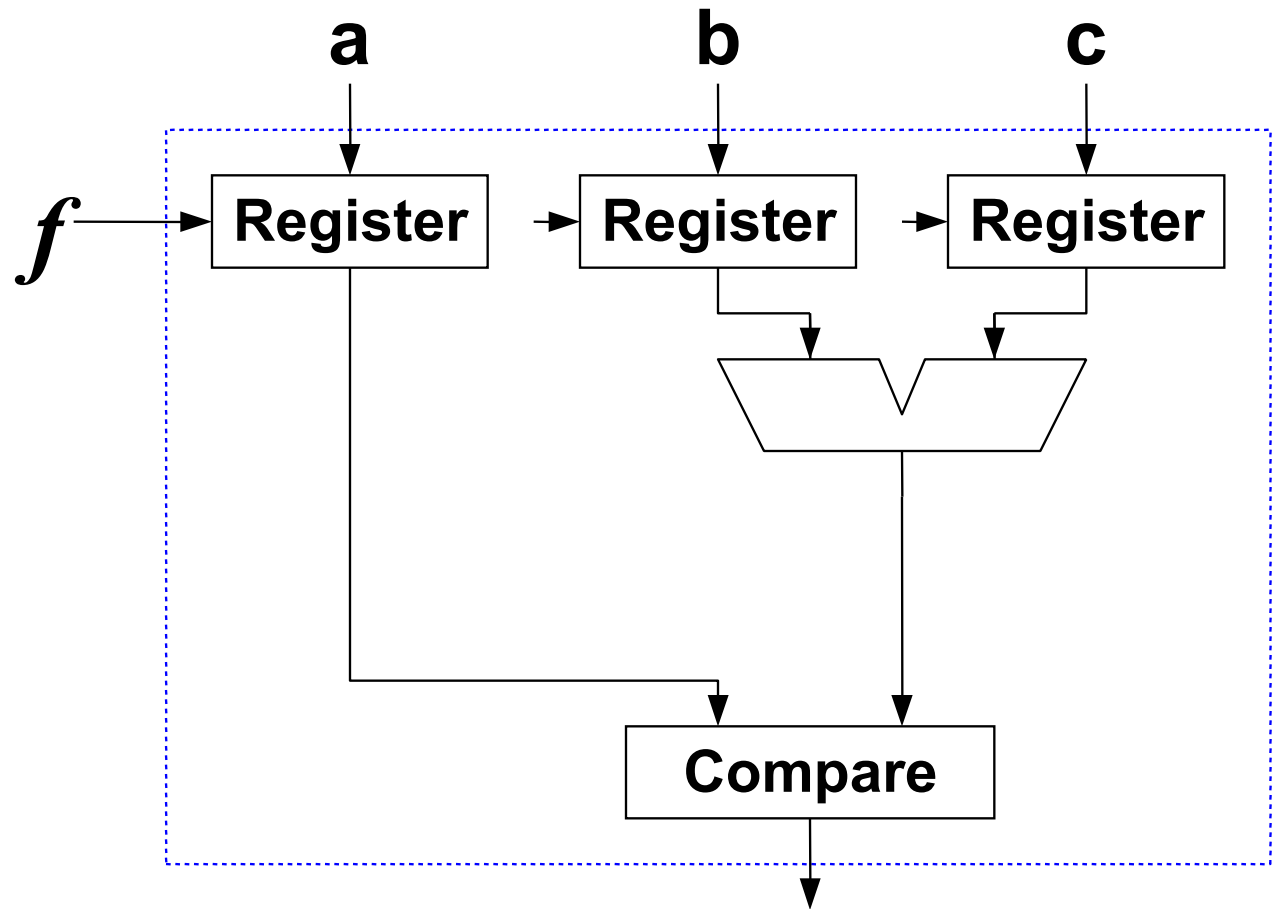 


# Pipelining

Increased C due to register

$\beta$


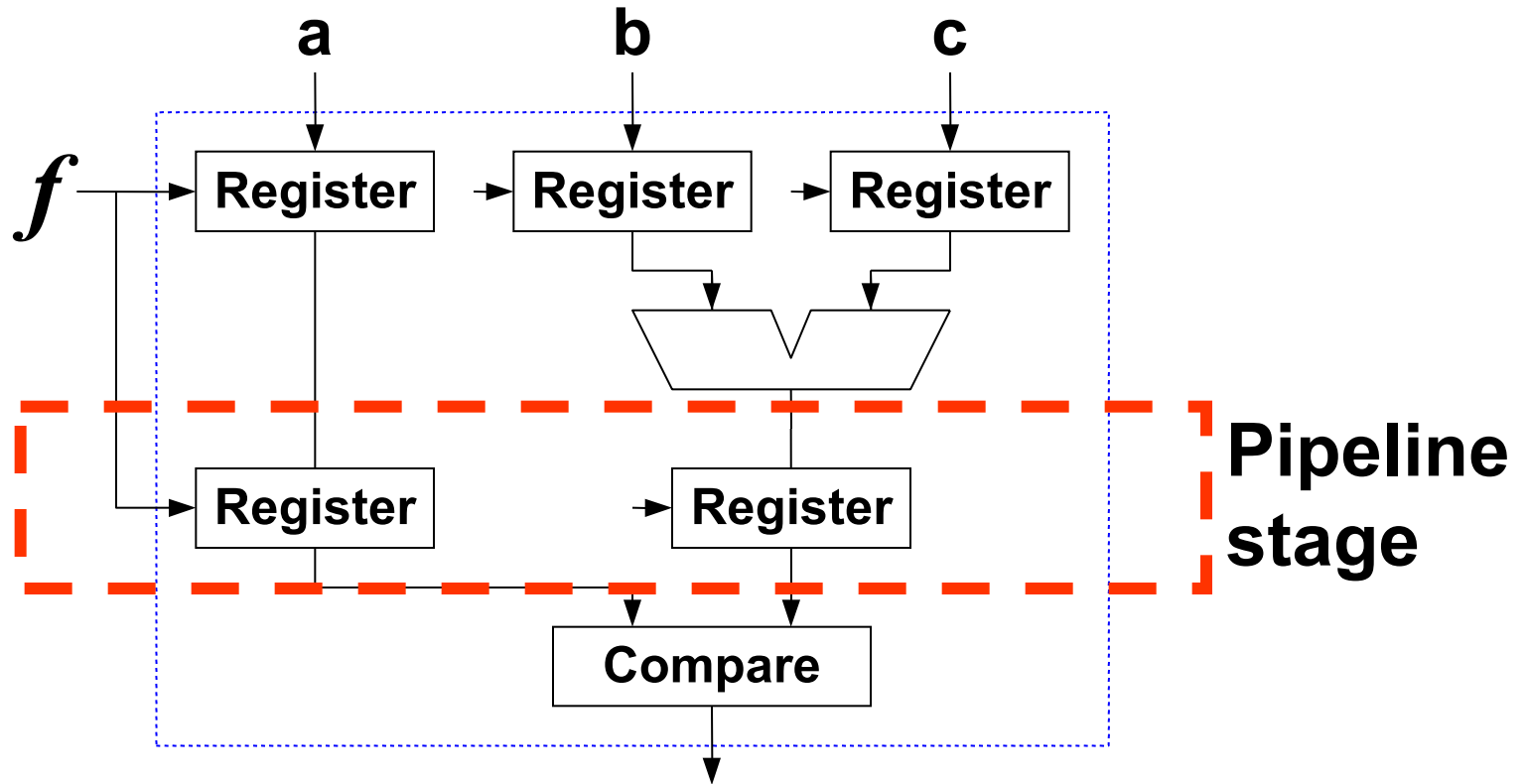
$$P_{pipe} = f \times 1.1C \times (0.58V)^2 = 0.37P$$





# Power in sub- $V_T$ with Pipelining

AMA = Addition-Multiplication-Addition

  

MT = Multiplication Tree


 


Figure 6.6.: Energy per cycle vs  $V_{DD}$  @ max freq. for the two designs corresponding to the pipelines

**Power decreases up to a point and then increase due to increased overhead.**

From PhD thesis *Design Space Exploration of Digital Circuits for Ultra-low Energy Dissipation* by Yasser Sherazi, January 2014

# Parallel Processing

 

Two samples are processed in parallel

- same  $f$  but two samples  $\Rightarrow$  double throughput

or


- reduce  $f$  and two samples  $\Rightarrow$  same throughput and reduced  $V_{DD}$

# Parallel Processing for Low Power

- Total capacitance,  $C$ , is increased by  $L$
- To maintain the same sample rate  
 $f$  is reduced by  $1/L$
- $f$  reduced  $\Rightarrow V_{DD}$  can be reduced

# Parallel Processing


$k=0,1,2,3\dots$

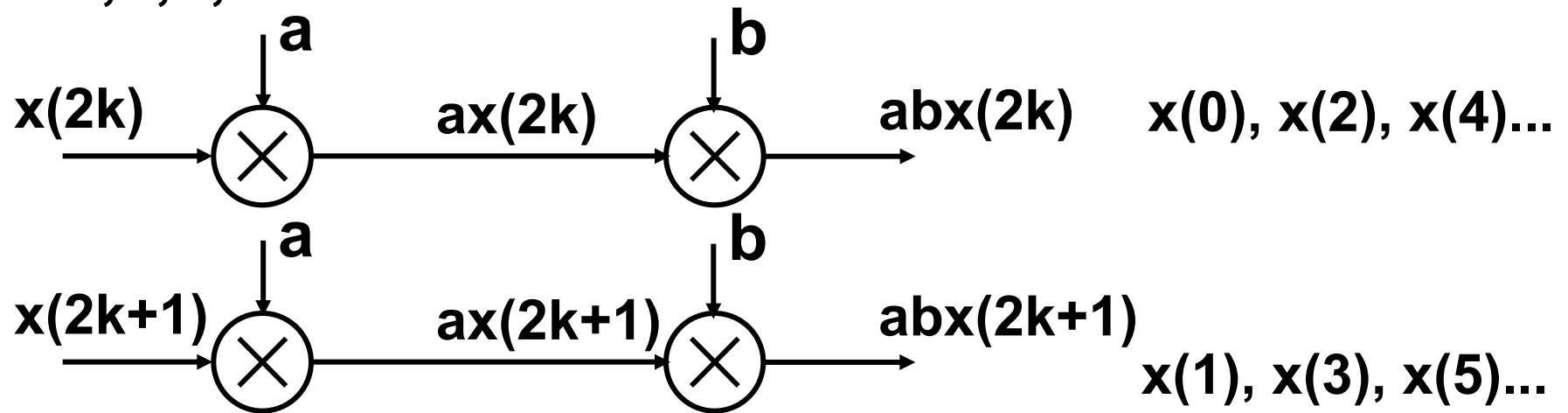


$$P_{para} = \cancel{L} C_L \frac{f}{\cancel{L}} (\beta V_{DD})^2 =$$

# Parallel Processing for Low Power

Sequential (critical path):

 


Parallel: (critical path when  $L=3$ )

 

Propagation delay of the L-parallel system is given by
 
$$T_{par} = L \cdot T_{seq} \Rightarrow \frac{C_L \cdot \beta V_{DD}}{k(\beta V_{DD} - V_T)^2} = L \frac{C_L \cdot V_{DD}}{k(V_{DD} - V_T)^2}$$




$$L(\beta V_{DD} - V_T)^2 = \beta(V_{DD} - V_T)^2$$

# Parallel Processing

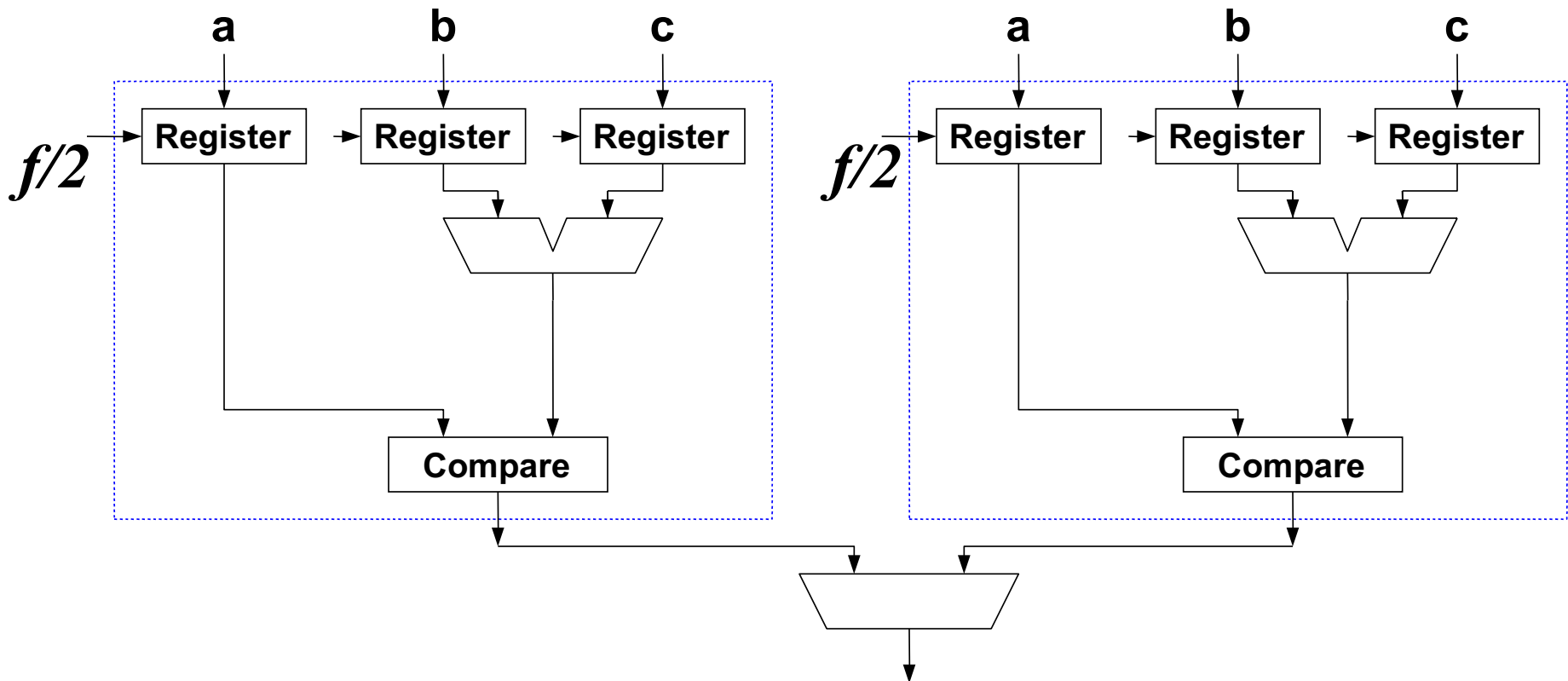2.15 due to mux


$\beta$

$$P_{par} = 0.5f \times 2.15C \times (0.58V)^2 = 0.36P$$


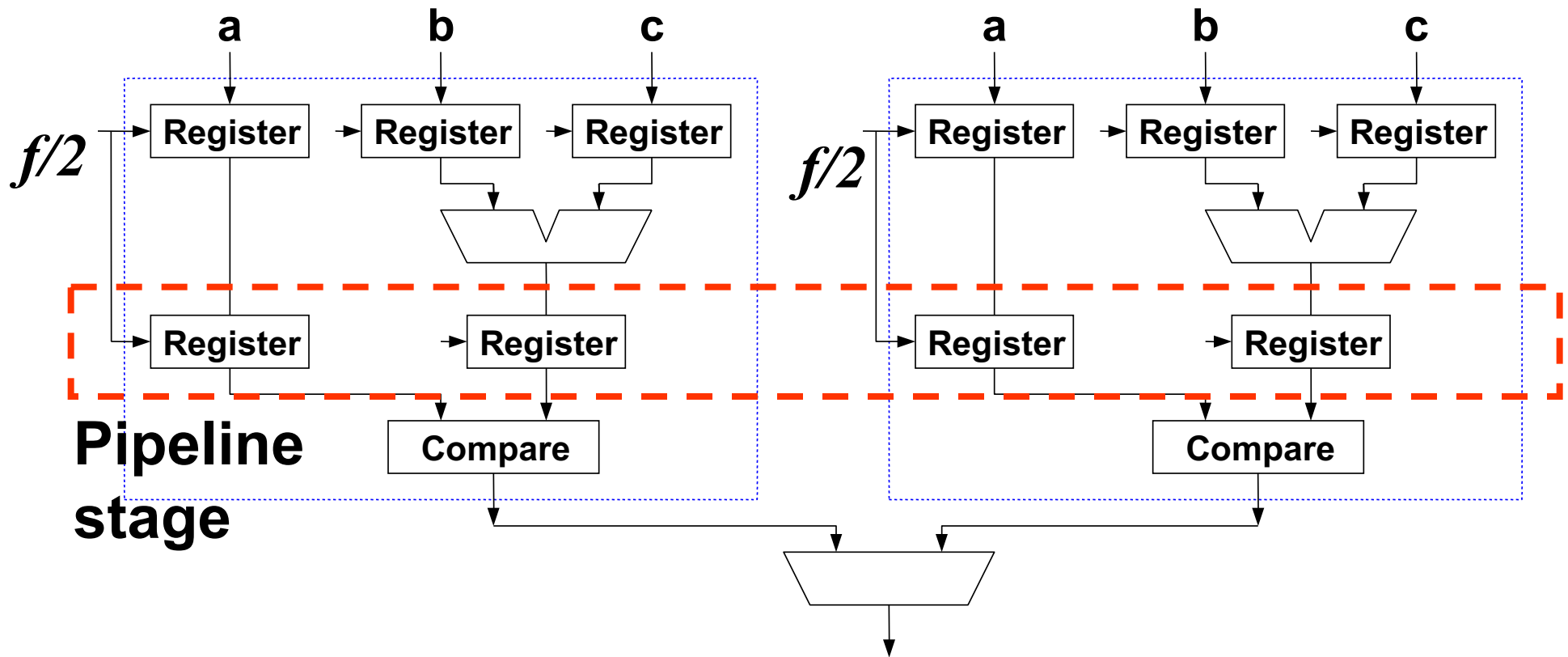
# Parallel Processing and Pipelining

$$P_{par,pipe} = 0.5f \times 2.35C \times (0.4V)^2 = 0.19P$$





# Summary - The Effect of Pipelining and Parallelization

We have seen that the power can be significantly reduced in a system using pipelining and parallelization.

Pipelining only


$$P_{pipe} = f \times 1.1C \times (0.58V)^2 = 0.37P$$

Parallelization only

$$P_{par} = 0.5f \times 2.15C \times (0.58V)^2 = 0.36P$$

Pipe- and Parallelization
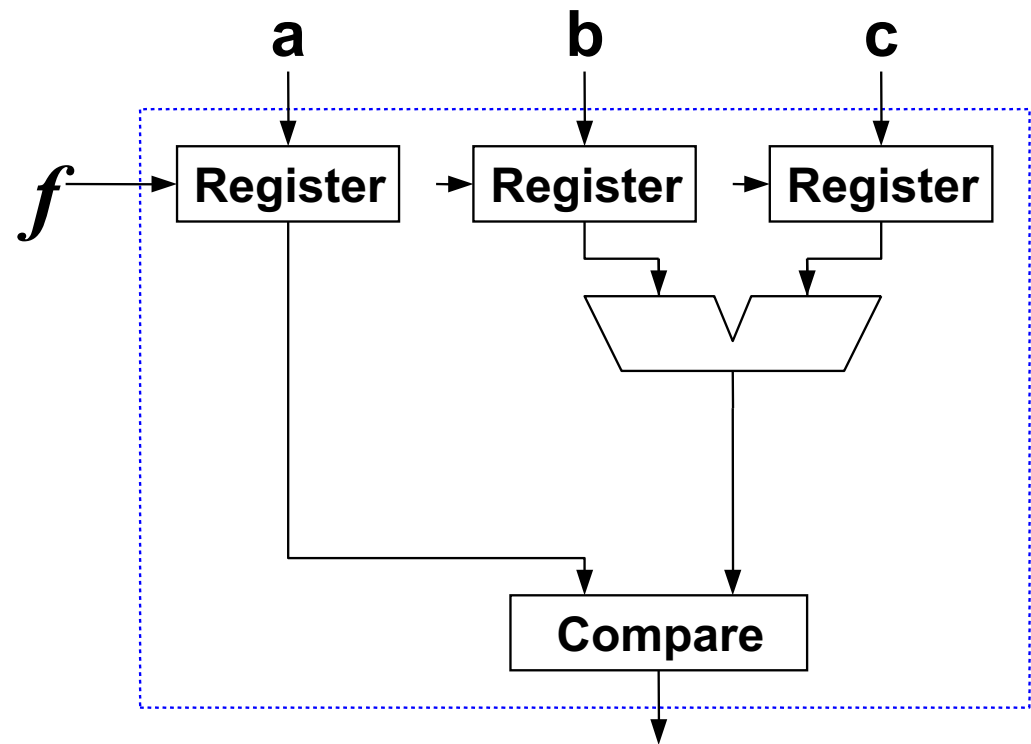
$$P_{par,pipe} = 0.5f \times 2.35C \times (0.4V)^2 = 0.19P$$



# End of Lecture 4