

# DSP Design – Lecture 5

## Retiming

**Dr. Fredrik Edman**

**fredrik.edman@eit.lth.se**



# Repetition

- **Critical path** - the combinational path with maximum total execution time
- **Loop (=cycle)** - a path beginning and ending at same node
- **Loop bound for loop**


$$\frac{T_j}{W_j} \text{ loop computation time}$$

$W_j$  number of delays in loop

- **Iteration Bound** - maximum of all loop bounds



$$T_{\infty} = \max_{l \in L} \left\{ \frac{t_l}{w_l} \right\}$$

 It is the lower bound on execution time for DFG (assuming only pipelining, retiming, unfolding)




# Fine-Grain pielinging

Repetition

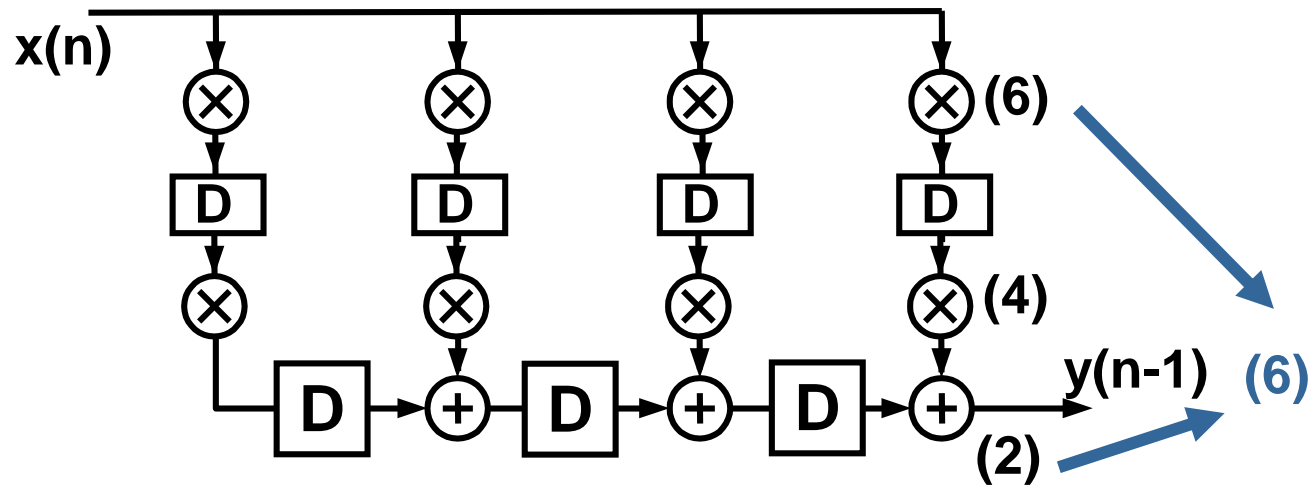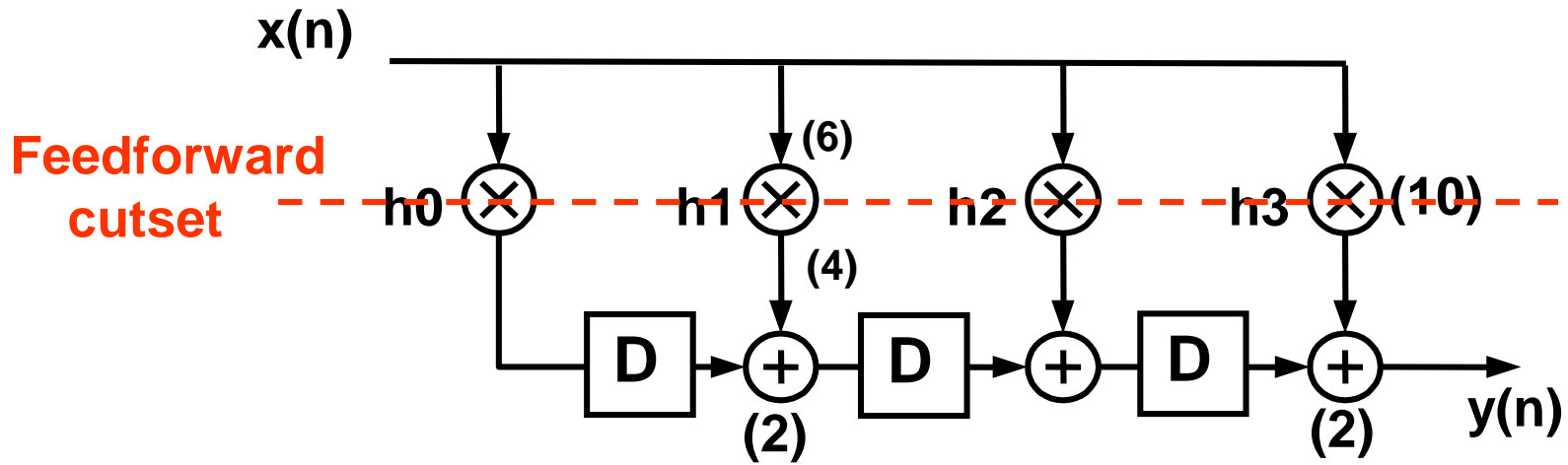


# Parallel Processing

Repetition

 


$k=0,1,2,3...$

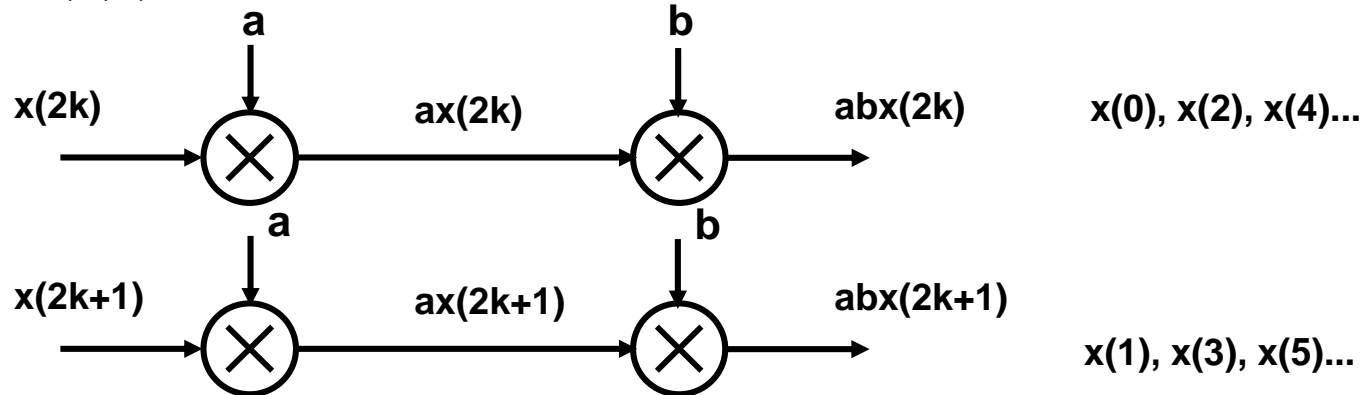

Two samples are processed in parallel => double throughput or lower power consumption due to reduced  $V_{DD}$

 When block size is 2, 1 delay element = 2 sampling delays



# Power Consumption

- The power consumption in original architecture

$$P_{seq} = f C_L V_{DD}^2$$

- The supply voltage can be reduced to  $\beta V_{DD}$ , ( $0 < \beta < 1$ ).  
Hence, the power consumption of the pipelined filter is:

$$P_{pipe} = f C_L (\beta V_{DD})^2 = \beta^2 P_{seq}$$

$$P_{para} = LC_L \frac{f}{L} (\beta V_{DD})^2 = \beta^2 \cdot P_{seq}$$

Repetition

# The Effect of Pipelining and Parallelization

Repetition

We have seen that the power can be significantly reduced in a system using pipelining and parallelization.

$$P = f C V^2$$

**Pipelining only**


$$P_{pipe} = f \times 1.1C \times (0.58V)^2 = 0.37P$$

**Parallelization only**

$$P_{par} = 0.5f \times 2.15C \times (0.58V)^2 = 0.36P$$

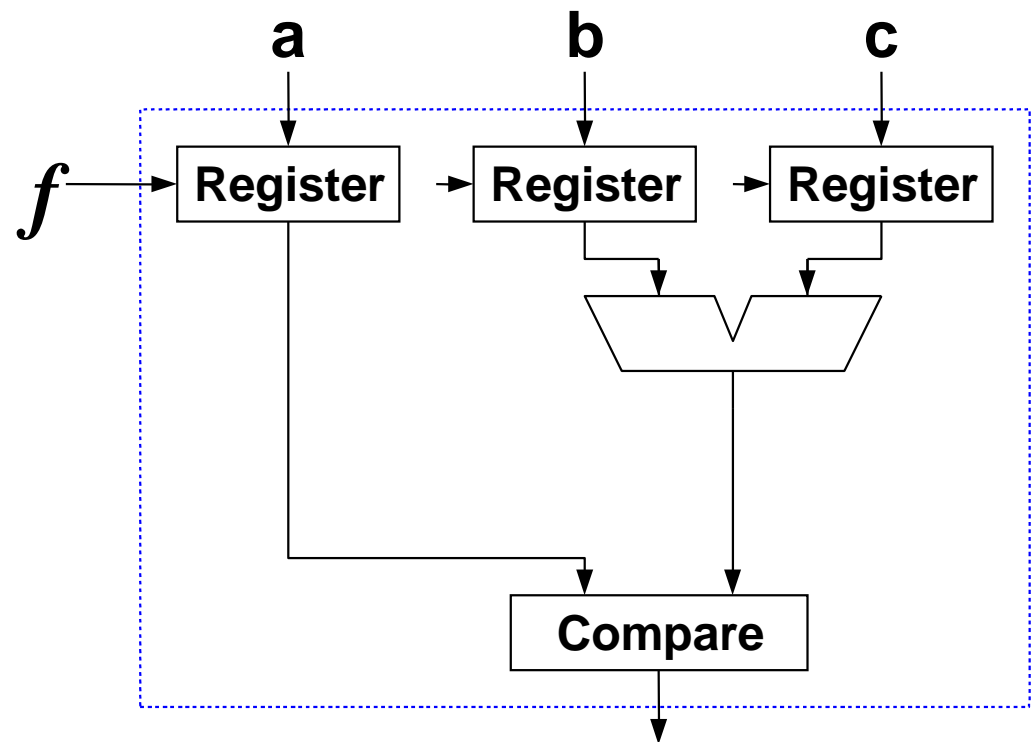**Pipe- and Parallelization**

$$P_{par,pipe} = 0.5f \times 2.35C \times (0.4V)^2 = 0.19P$$



# Retiming

## Chapter 4.



## What is retiming?

*Retiming is a transformation technique used to change the location of delay elements in a circuit without affecting the characteristics of the circuit.*

*Retiming is the technique of moving the structural location of latches or registers in a digital circuit to improve its performance, area, and/or power characteristics in such a way that preserves its functional behaviour at its outputs.*


### **Can be used for:**

- *Reducing the clock period*
- *Reducing the number of registers*
- *Reducing the power consumption*
- *Logic synthesis (not in this course)*

The lower bound on the clock period of the circuit can be achieved by retiming the circuit.



## Retiming is about moving delays!

 

**Delays can be moved from ALL inputs to ALL outputs**

**Reduce Critical Path**

- faster
- reduced power consumption

**Reduced number of Register**


# Retiming

$$\text{Loop bound} = \frac{T_j}{W_j} \begin{matrix} \text{loop computation time} \\ \text{number of delays in} \\ \text{the loop} \end{matrix}$$



Retiming does not change

- delay in loop
- the iteration bound
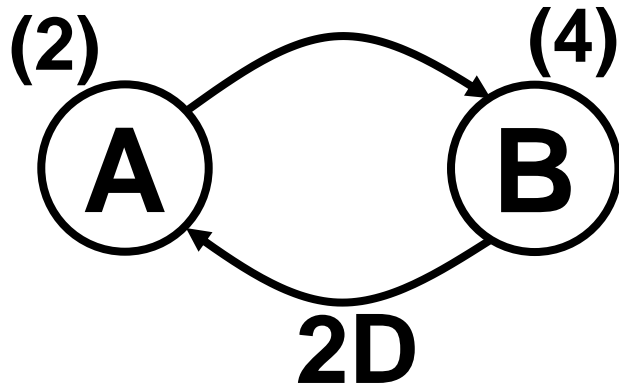
$$T_\infty = \max_{l \in L} \left\{ \frac{t_l}{w_l} \right\}$$



  Critical path = 6  
 Loop bound =  $6/2 = 3$



Critical path = 4  
 Loop bound =  $6/2 = 3$

...but it changes the critical path!




# Overview Retiming

- **Cutset retiming and pipelining** (visual retiming)
- **Systolic transformation**
- **Retiming Formulation**
- **Retiming for clock period minimization**

# Ex. Cutset Retiming


$$T_A = 2 \text{ t.u.}$$

$$T_M = 4 \text{ t.u.}$$

  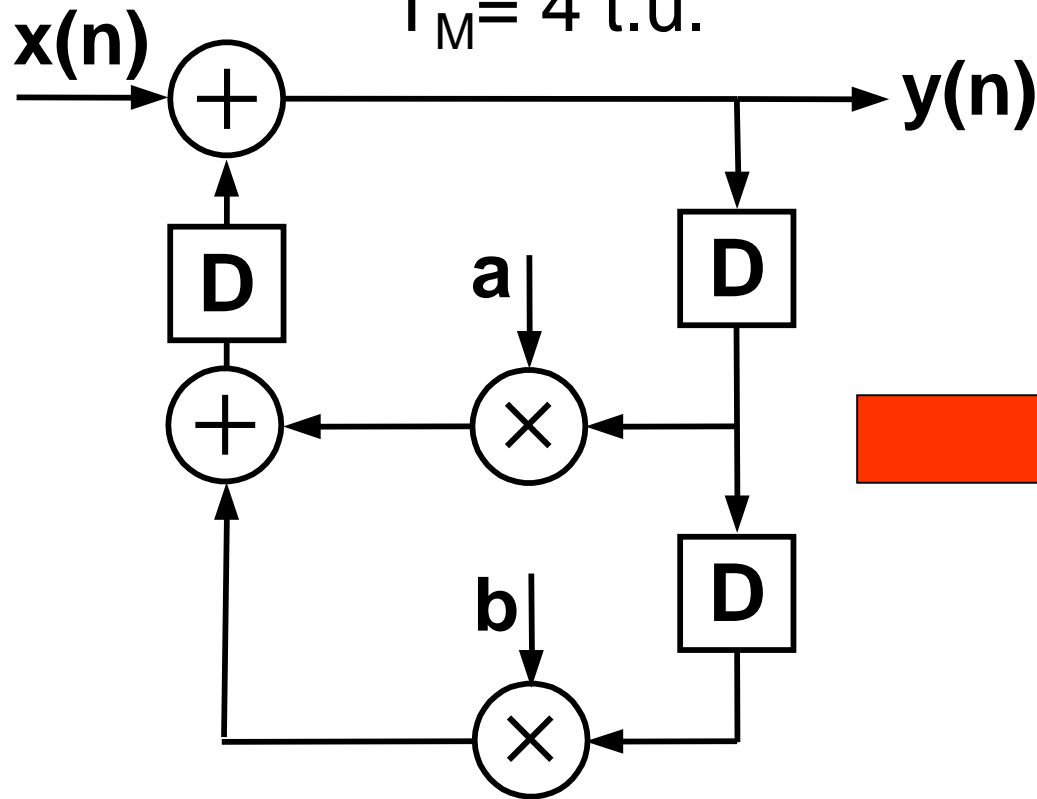

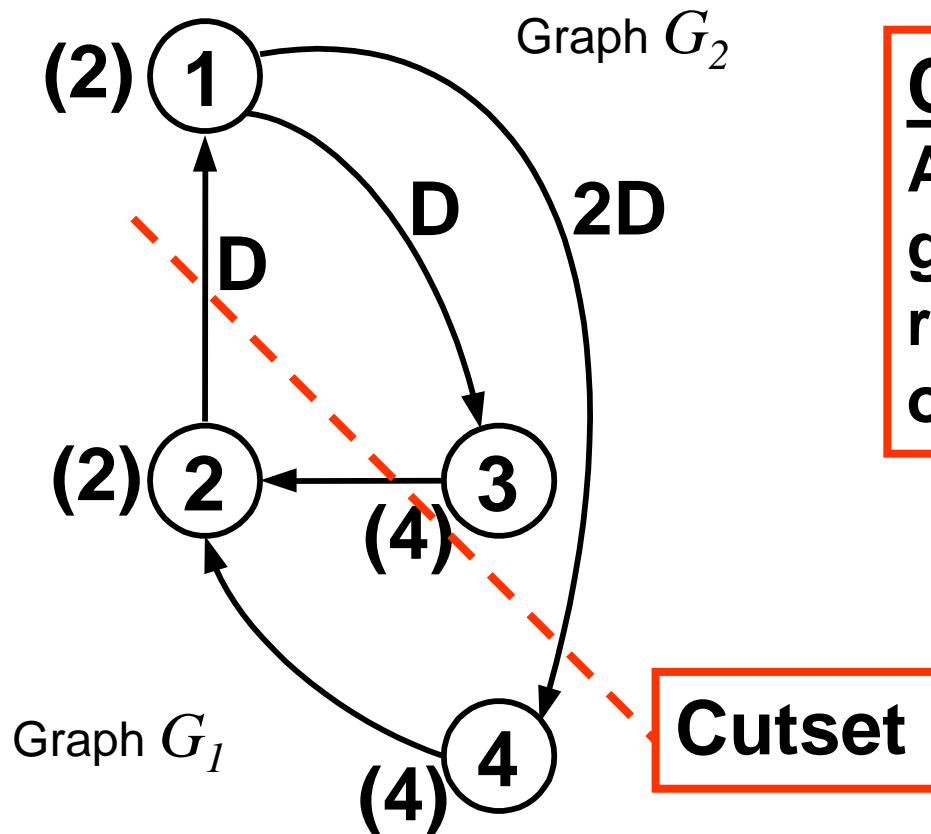
# Ex. Cutset Retiming

**Cutset:** A set of edges that if removed, or cut, results in two disjoint graphs.



 
## Cutset Retiming

Add  $k$  delays to edges going one way and remove  $k$  delays from ones going the other.



 
# Ex. Cutset Retiming

**Cutset Retiming:** Add delays to edges going one way and remove from edges going the other.



# Ex. Node Cutset Retiming

Node Retiming: Cutset around one node.

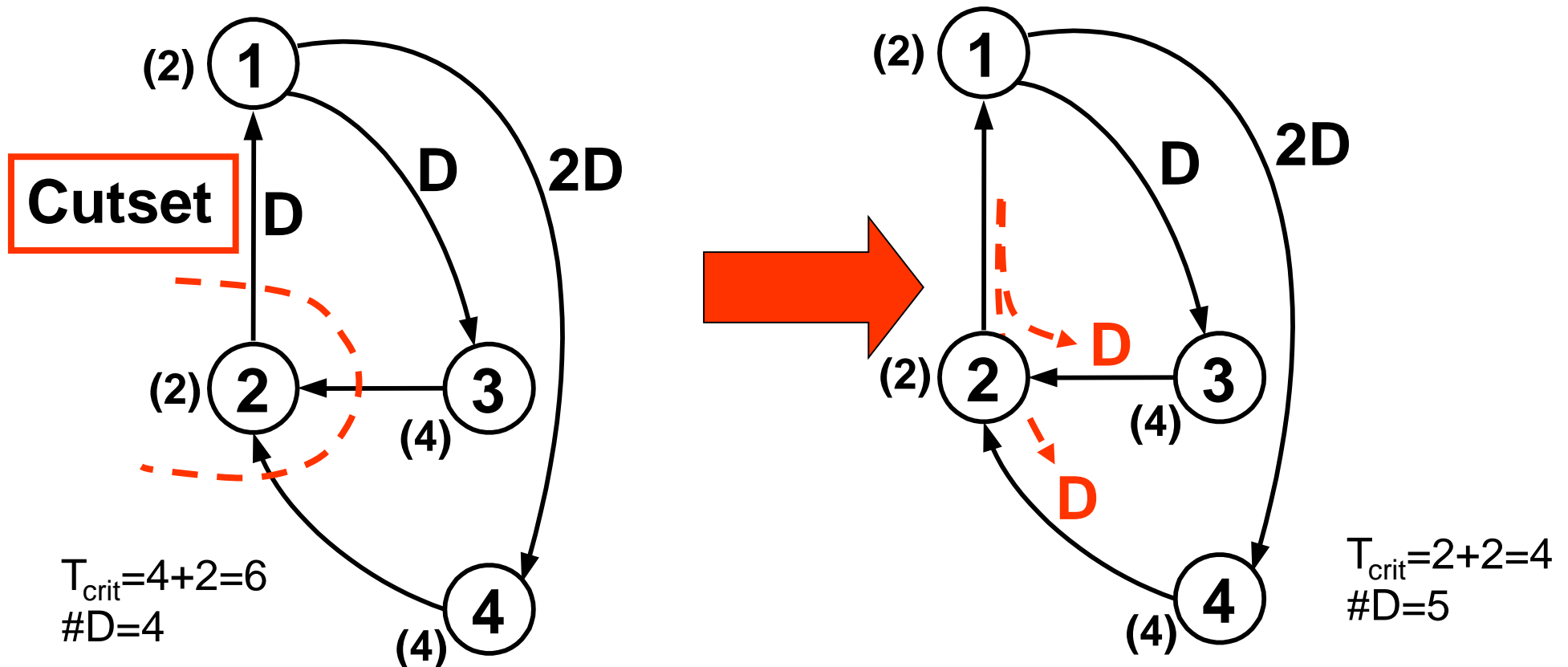


# Pipelining

- **Pipelining is a special case of cutset retiming where there are no edges in the cutset from  $G_2$  to  $G_1$ , i.e., pipelining applies to graphs without loops.**
- **Retiming is a generalization of pipelining**
- **Pipelining is equivalent to introducing delays at the input followed by retiming**


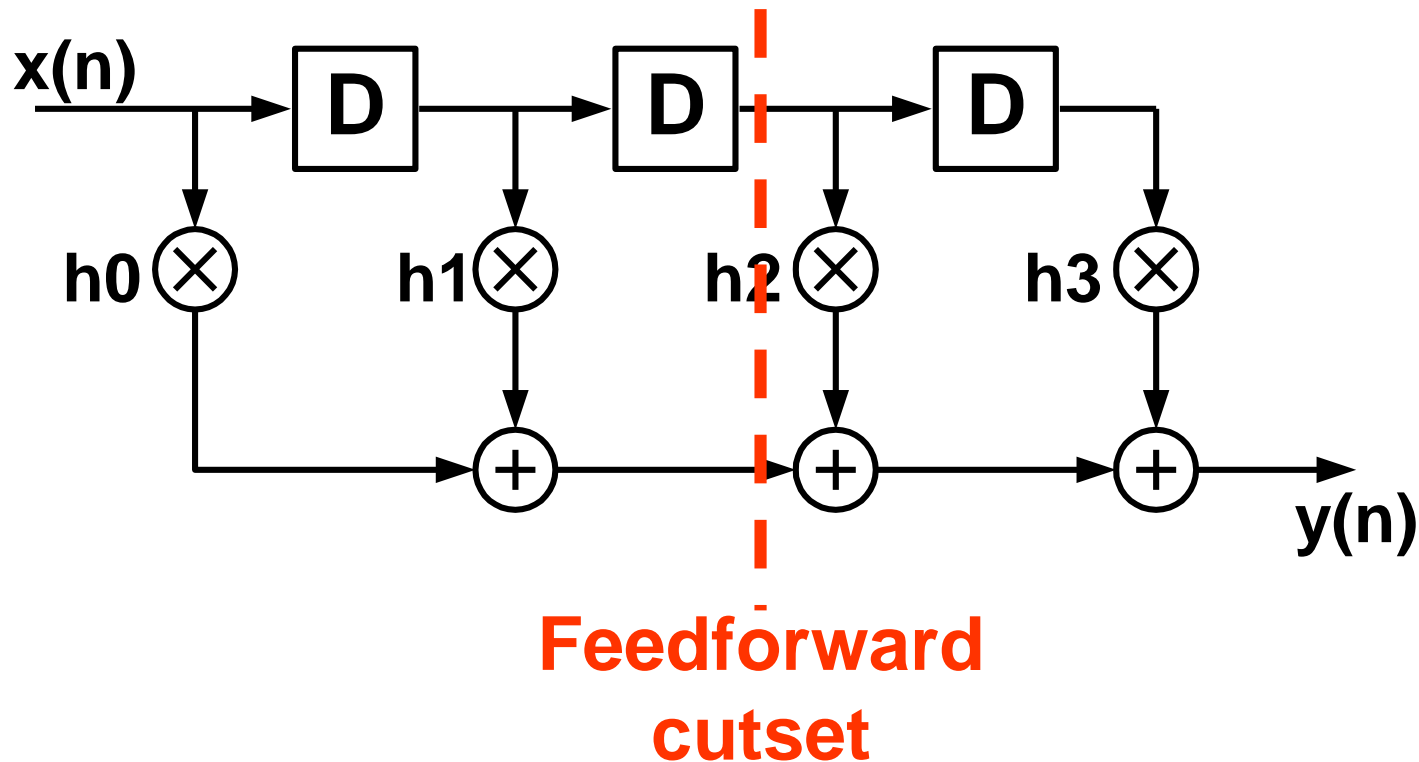
# Pipelining – Feedforward Cutset


Pipelining is a special case of cutset retiming:  
Placing delays at feedforward cutsets.



# Overview Retiming

- **Cutset retiming and pipelining**
- **Systolic transformation**
- **Retiming Formulation**
- **Retiming for clock period minimization**

# Systolic Transformation

 

Eliminating global broadcasting


# Overview Retiming

- **Cutset retiming and pipelining**
- **Systolic transformation**
- **Retiming Formulation**
- **Retiming for clock period minimization**

# Retiming Formulation

$\omega(e)$  = weight of edge  $e$  = # of delays


$r(x)$  = retiming values

 

$$\omega_r(e) = \omega(e) + r(V) - r(U)$$

**Valid retiming if all  $\omega_r(e) \geq 0$  for all edges!**

# Retiming Formulation for a Node

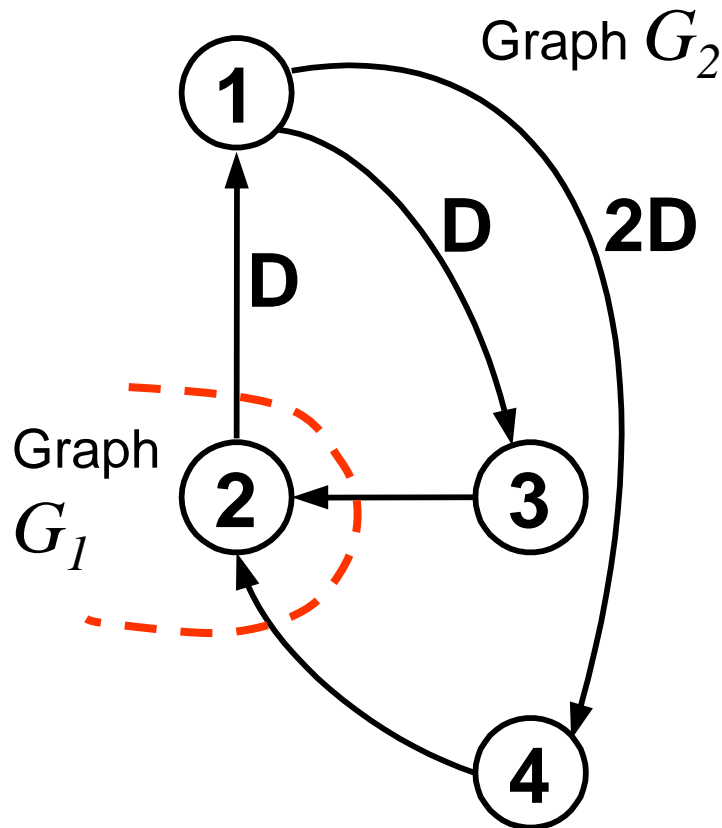


Each node in  $G_1$  has retiming value  $j$  and each node in  $G_2$  has retiming value  $j+k$

Any value  $j$  results in the same retimed graph.

Valid retiming only if all  $\omega_r(e) \geq 0$

# Node Retiming with Formulation

Original weights ( $\omega(e)$ )

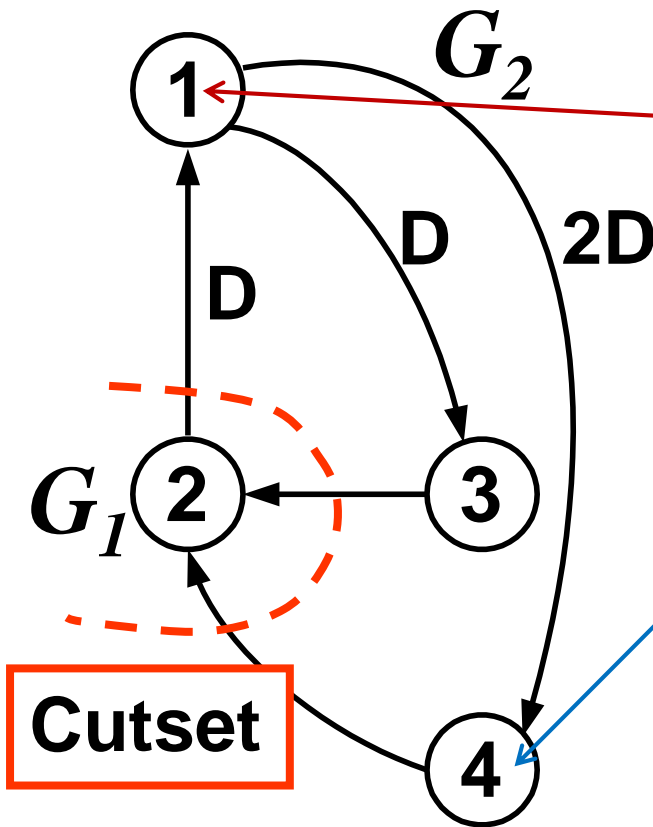

$$1 \rightarrow 3 = 1$$

$$1 \rightarrow 4 = 2$$

$$2 \rightarrow 1 = 1$$

$$3 \rightarrow 2 = 0$$

$$4 \rightarrow 2 = 0$$

Choose any retiming values

$$G_2 = 0 \Leftrightarrow r(1) = r(3) = r(4) = 0$$

$$G_1 = 1 \Leftrightarrow r(2) = 1$$

# Node Retiming with Formulation

## Original weights

$$1 \rightarrow 3 = 1$$

$$1 \rightarrow 4 = 2$$

$$2 \rightarrow 1 = 1$$

$$3 \rightarrow 2 = 0$$

$$4 \rightarrow 2 = 0$$

$$\omega_r(e) = \omega(e) + \underset{\text{Receive}}{r(V)} - \underset{\text{Send}}{r(U)}$$

$$1 \rightarrow 3 = 1 + 0 - 0 = 1$$

$$1 \rightarrow 4 = 2 + 0 - 0 = 2$$

$$2 \rightarrow 1 = 1 + 0 - 1 = 0$$

$$3 \rightarrow 2 = 0 + 1 - 0 = 1$$

$$4 \rightarrow 2 = 0 + 1 - 0 = 1$$

## Retiming values

$$r(1)=0, r(2)=1, r(3)=0 \text{ and } r(4)=0$$



# Node Retiming with Formulation (3)

## Retimed weights

$$1 \rightarrow 3 = 1$$


$$1 \rightarrow 4 = 2$$

$$2 \rightarrow 1 = 0$$

$$3 \rightarrow 2 = 1$$


$$4 \rightarrow 2 = 1$$

Retimed Graph

 

## Algorithm for clock period minimization in 4.4.2

# Node Retiming with Formulation (3)

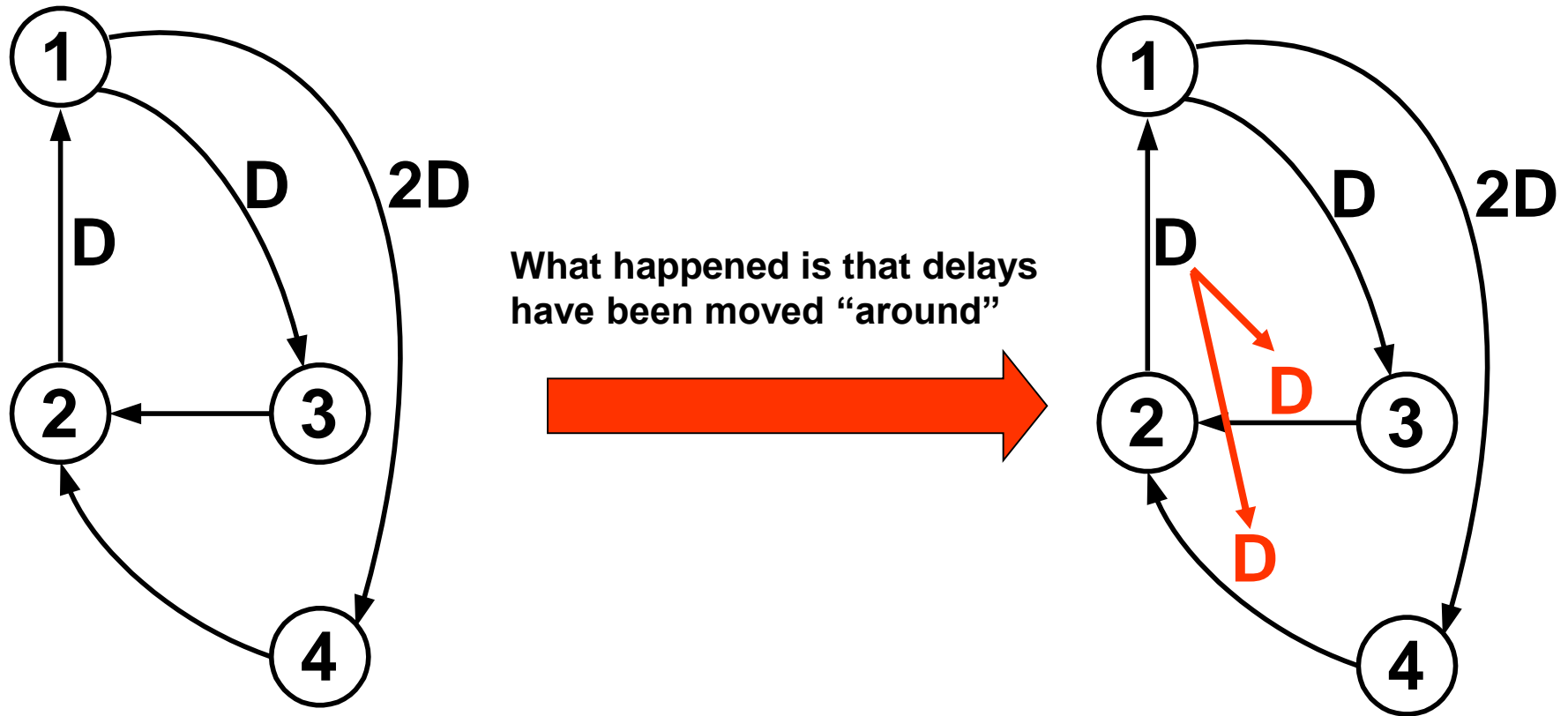

# Overview Retiming

- **Cutset retiming and pipelining**
- **Systolic transformation**
- **Retiming Formulation**
- **Retiming for clock period minimization**

## Retiming for Minimizing Clock Period

- Note that retiming will NOT alter the iteration bound  $T_\infty$ .
- Iteration bound is the theoretical minimum clock period to execute the algorithm.
- Let edge  $e$  connect node  $u$  to node  $v$ . If the node computing time  $t(u) + t(v) > T_\infty$ , then clock period  $T > T_\infty$ . For such an edge, we require that  $w_r(e) \geq 1$ .
- In other words, for any possible critical path in the DFG that is larger than  $T_\infty$ , we require  $w_r(e) \geq 1$ .

Formula: Retiming for Minimizing Clock Period

(1) Check that  $t(u) + t(v) \geq T_\infty$  then

$$w_r(e) \geq 0 \text{ if } t(u)+t(v)=T_\infty$$


$$w_r(e) \geq 1 \text{ if } t(u)+t(v)>T_\infty$$

(2) Solve  $w_r(e_{uv}) = w(e) + r(v) - r(u)$

(3) Check that the retime values are valid!
 
# Ex. Retiming for Minimizing Clock Period

Check that  $t(u) + t(v) \geq T_\infty$  then  
 $w_r(e) \geq 0$  if  $t(u)+t(v)=T_\infty$   
 $w_r(e) \geq 1$  if  $t(u)+t(v)>T_\infty$



$$T_\infty = 2$$

$$w_r(e_{21}) \geq 0, \text{ since } t(2)+t(1) = 2 = T_\infty.$$

$$w_r(e_{13}) \geq 1, \text{ since } t(1)+t(3) = 3 > T_\infty.$$

$$w_r(e_{14}) \geq 1, \text{ since } t(1)+t(4) = 3 > T_\infty.$$

$$w_r(e_{32}) \geq 1, \text{ since } t(3)+t(2) = 3 > T_\infty.$$

$$w_r(e_{42}) \geq 1, \text{ since } t(4)+t(2) = 3 > T_\infty.$$

Use eq.  $w_r(e_{uv}) = w(e) + r(v) - r(u)$  then

$$w(e_{21}) + r(1) - r(2) = 1 + r(1) - r(2) \geq 0$$

$$w(e_{13}) + r(3) - r(1) = 1 + r(3) - r(1) \geq 1$$

$$w(e_{14}) + r(4) - r(1) = 2 + r(4) - r(1) \geq 1$$

$$w(e_{32}) + r(2) - r(3) = 0 + r(2) - r(3) \geq 1$$

$$w(e_{42}) + r(2) - r(4) = 0 + r(2) - r(4) \geq 1$$

## Ex. Retiming for Minimizing Clock Period

- Since the retimed graph  $G_r$  remain the same if all node retiming values are added by the same constant. We thus can set  $r(1) = 0$ .
- The inequalities then become:
  - $1 - r(2) \geq 0$  or  $r(2) \leq 1$
  - $1 + r(3) \geq 1$  or  $r(3) \geq 0$
  - $2 + r(4) \geq 1$  or  $r(4) \geq -1$
  - $r(2) - r(3) \geq 1$  or  $r(3) \leq r(2) - 1$
  - $r(2) - r(4) \geq 1$  or  $r(2) \geq r(4) + 1$
- Since
  - $1 \geq r(2) \geq r(3) + 1 \geq 0 + 1 = +1$
  - one must have  $r(2) = +1$ .
- This implies  $r(3) \leq 0$ .  
But we also have  $r(3) \geq 0$ .  
Hence  $r(3) = 0$ .
- These leave  $-1 \leq r(4) \leq 0$ .
- Hence the two sets of solutions are:

$$r(0) = r(3) = 0, r(2) = +1, \text{ and } r(4) = 0 \text{ or } (-1).$$

**However for larger systems...**

# Solving a Systems of Inequalities

Given a systems of inequalities:

$$r(i) - r(j) \leq k; 1 \leq i, j \leq N$$

Construct a constraint graph:

1. Map each  $r(i)$  to node  $i$ . Add a node  $N+1$ .
2. For each inequality  $r(i) - r(j) \leq k$ , draw an edge  $e_{ji}$  such that  $w(e_{ji}) = k$ .
3. Draw  $N$  edges  $e_{N+1,i} = 0$ .

The system of inequalities has a solution if and only if the constraint graph contains **no negative cycles**

If a solution exists, one solution is where  $r_i$  is the minimum length path from the node  $N+1$  to the node  $i$ .

Shortest path algorithms: (Appendix A)

Bellman-Ford algorithm

Floyd-Warshall algorithm

**See chapter 4.4.2**

## Drawbacks with Retiming

- The state encoding of the circuit may be destroyed, making testing and verification more difficult.
- Some retimed circuits may require complicated initialization logic to have the circuit start in a special initial state.
- Retiming changes the circuit's topology which have consequences in other logical and physical synthesis steps that make design closure more difficult.




# Time Scaling using Slow Down and Retiming


- **A slow down process is often used in combination with the cutset retiming process**
  - **Replace each delay in a DFG with N delays**
  - **N-slow DFG N-1**
  - **Null operations (or 0 samples) must be interleaved to preserve the functionality**
 
# Time Scaling (Slow Down)

- Transform each delay element (register)  $D$  to  $ND$   
Reduce the sample frequency by  $N$ -fold to slow down the computation  $N$  times.



 
- In slow down the clock cycle time remains unchanged. Only the sampling time is increased.



**This provides opportunity for retiming, and interleaving.**

# Slow Down by k

Replace each D by kD

 


Clock	
0	A0 → B0
1	A1 → B1
2	A2 → B2

$$T_{\text{clk}} = 2t.u.$$

$$T_{\text{iter}} = 2t.u.$$

After 2-slow transformation

 

Clock	
0	A0 → B0
1	
2	A1 → B1
3	
4	A2 → B2


$$T_{\text{clk}} = 2t.u.$$

$$T_{\text{iter}} = 2 \times 2t.u. = 4t.u.$$

- Input new samples every alternate cycles.
- null operations account for odd clock cycles.
- Hardware utilized only 50% time

# Retiming Example: 3-stage Lattice Filter

## Loop Bounds

 


$$T_{L1} = \frac{3T_{Add} + 2T_{Mult}}{1}$$

$$T_{L3} = \frac{5T_{Add} + T_{Mult}}{3}$$

$$T_{L2} = \frac{5T_{Add} + 2T_{Mult}}{2}$$

# Example: 3-stage Lattice Filter


## Iteration Bound

 

$$T_{\infty} = \max\{T_{L1}, T_{L2}, T_{L3}, \dots\} = \frac{3T_{Add} + 2T_{Mult}}{1}$$

# Example: 3-stage Lattice Filter

## Critical Path

 


**Critical Path = (N+1) Adders + 2 Mult**

**N = Number of Stages**


# Example: 3-stage Lattice Filter

## Cutset Retiming

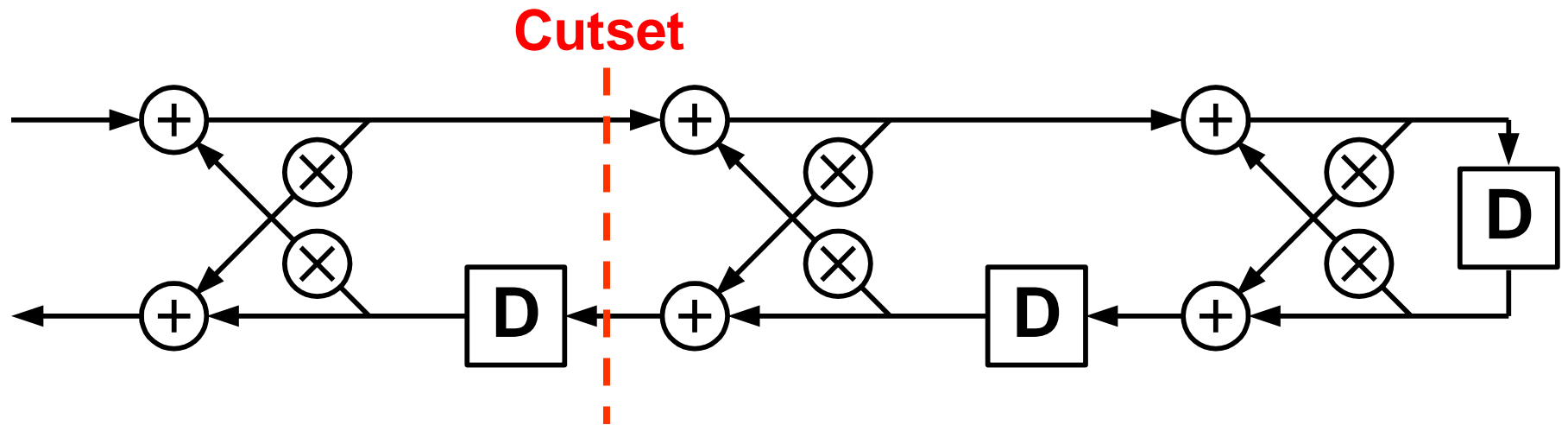

# Example: 3-stage Lattice Filter

## Cutset Retiming

 

**Critical Path = 4 Adders + 4 Mult**  
**Independent of  $N$  = nr. of stages in filter**

**compared to**


**Original Critical Path =  $(N+1)$  Adders + 2 Mult**




**Worse for Low  $N$ . Trade-off depends on  $T_M$  and  $T_A$**


 
# Compare: Cutset Retiming of a 4-stage Lattice Filter




Move every second delay

 

Critical Path = 4Adders + 4Mult

 
# Compare: Cutset Retiming of a 5-stage Lattice Filter



**Critical Path = 4Adders + 4Mult**

# Example: 3-stage Lattice Filter

## Cutset Retiming with Slowdown

 


**Critical Path =  $(N+1)$  Adders + 2 Mult**

**N = Number of Stages**

# Example: 3-stage Lattice Filter

## Slowdown by factor 2

 


Critical Path has not changed. Same  $f_{clk}$ .

Insertion of 0 samples to preserve behavior!

$x_0 \ x_0 \ x_1 \ x_1 \ x_2 \ x_2 \ x_3 \ x_3 \ . \ . \ .$  or  
 $x_0 \ 0 \ x_1 \ 0 \ x_2 \ 0 \ x_3 \ 0 \ . \ . \ .$

# Example: 3-stage Lattice Filter


## Slowdown by factor 2

 

Add delays on Edges in one direction  
and remove in the other

# Example: 3-stage Lattice Filter


## Slowdown by factor 2

 

**Critical Path = 2 Adders + 2 Mult**

**But requires twice the number of clock cycles**

# Register Minimization

 

- **Register Sharing**

When a node has multiple fan-out with different number of delays, the registers can be shared so that only the branch with max. # of delays will be needed.

- Register reduction through node delay transfer from multiple input edges to output edges (e.g.  $r(v) > 0$ )
- Should be done only when clock cycle constraint (if any) is not violated.

## Algorithm for register minimization in 4.4.3

# End of Retiming