

DSP Design – Lecture 7

Unfolding cont. & Folding

Dr. Fredrik Edman

fredrik.edman@eit.lth.se



Unfolding of Switches

- The following assumptions are made when unfolding an edge $U \rightarrow V$ containing a switch :
 - The wordlength W is a multiple of the unfolding factor J , i.e. $W = W'J$.
 - All edges into and out of the switch have no delays.


- If so, an edge $U \rightarrow V$ can be unfolded as:

- Write the switching instance as

$$Wl + u = J(W'l + \lfloor u/J \rfloor) + (u \% J)$$

- Draw an edge from the node $U_{u \% J} \Rightarrow V_{u \% J}$,

 which is switched at time instance $(W'l + \lfloor u/J \rfloor)$.




Unfolding (cont.)

Chapter 5




What about Switches with Delays?

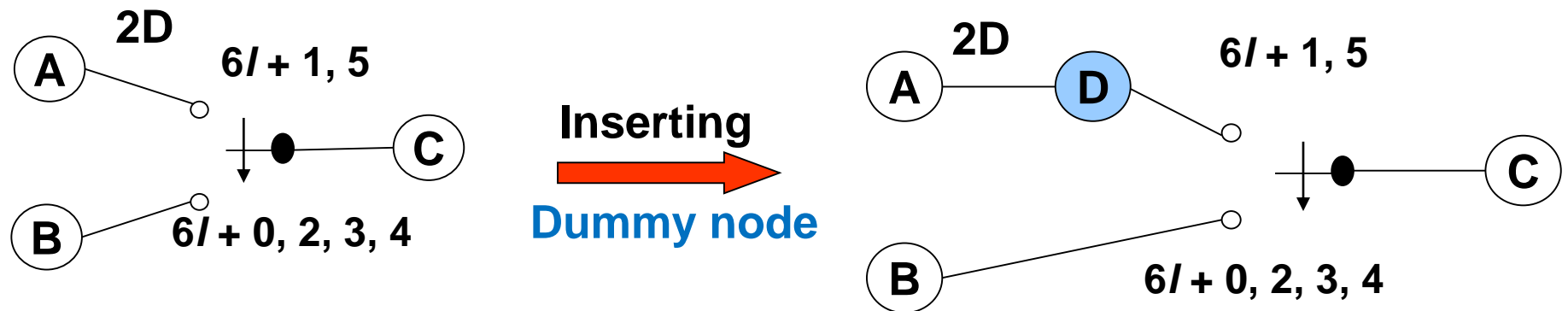Unfolding a DFG containing an edge having a switch and a positive number of delays is done by introducing a dummy node.




After unfolding remove the dummy node!

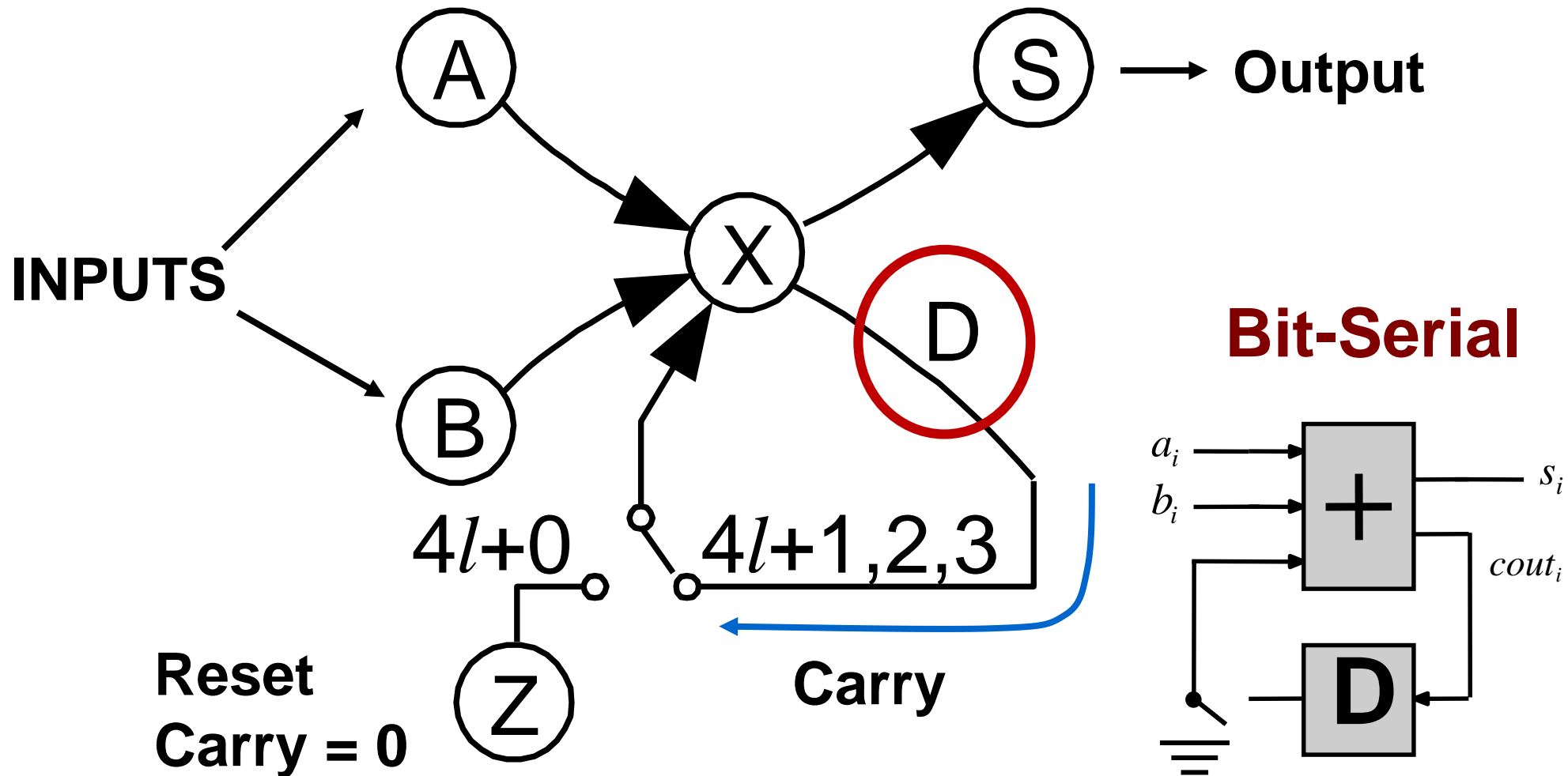
Example: How to Unfold a Bit-serial Adder



 Example: How to Unfold a Bit-serial Adder




Unfold Bit-serial Addder, J=2

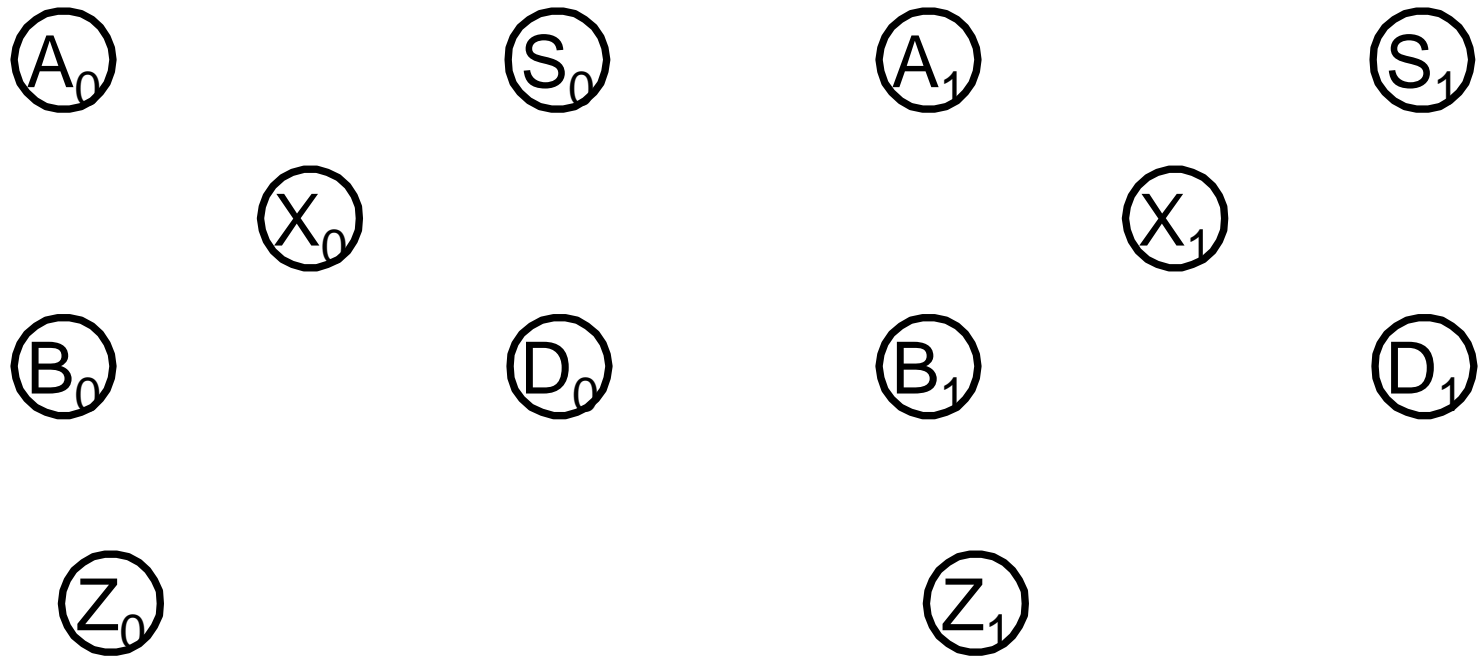

For each node U in the original DFG, draw J nodes $U_0, U_1, U_2, \dots, U_{J-1}$


Unfold Bit-serial Adder, $J=2$

 

For each edge $U \rightarrow V$ with w delays in the original DFG,
 draw the J edges $U_i \rightarrow V_{(i+w)\%J}$ with
 $\lfloor (i+w)/J \rfloor$ delays for $i = 0, 1, \dots, J-1$

If edge has $w=0 \Rightarrow U_i \rightarrow V_i$ with $\mathbf{0}$ delays


Unfold Bit-serial Adder, $J=2$

 

For each edge $U \rightarrow V$ with w delays in the original DFG,
 draw the J edges $U_i \rightarrow V_{(i+w)\%J}$ with
 $\lfloor (i+w)/J \rfloor$ delays for $i = 0, 1, \dots, J-1$

$X \Rightarrow D$ for $i=0 \Rightarrow X_0 \rightarrow D_1$ with **0** delays and $X \Rightarrow D$ for $i=1 \Rightarrow X_1 \rightarrow D_0$ with **1** delays


Unfold the Switch, J=2

 

Write the switching instance as

$$Wl + u = J(W'l + \lfloor u/J \rfloor) + (u \% J)$$

Unfold the Switch, J=2

 

$Z \Leftrightarrow X$

$4l+0 \rightarrow 2(2l+0)+0$

$Z_0 \rightarrow X_0$ at time $2l+0$

$D \Leftrightarrow X$


$4l+1 \rightarrow 2(2l+0)+1$

$4l+2 \rightarrow 2(2l+1)+0$

$4l+3 \rightarrow 2(2l+1)+1$

$D_0 \rightarrow X_0$ at time $2l+1$

Unfold the Switch, J=2

 

$$\underline{Z \Rightarrow X}$$

$$4l+0 \rightarrow 2(2l+0)+0$$

$Z_0 \rightarrow X_0$ at time $2l+0$

$$\underline{D \Rightarrow X}$$

$$4l+1 \rightarrow 2(2l+0)+1$$


$$4l+2 \rightarrow 2(2l+1)+0$$

$$4l+3 \rightarrow 2(2l+1)+1$$

$D_0 \rightarrow X_0$ at time $2l+1$

$D_1 \rightarrow X_1$ at time $2l+0, 1$
i.e. always closed

Unfold the Switch, $J=2$

 


$Z_0 \rightarrow X_0$ at time $2l+0$

$D_0 \rightarrow X_0$ at time $2l+1$

$D_1 \rightarrow X_1$ at time $2l+0, 1$
i.e. *always closed*

Remove Dead and Dummy Nodes

 


$Z_0 \rightarrow X_0$ at time $2l+0$

$D_0 \rightarrow X_0$ at time $2l+1$

$D_1 \rightarrow X_1$ at time $2l+0, 1$
i.e. always closed


The Digit Serial Addder

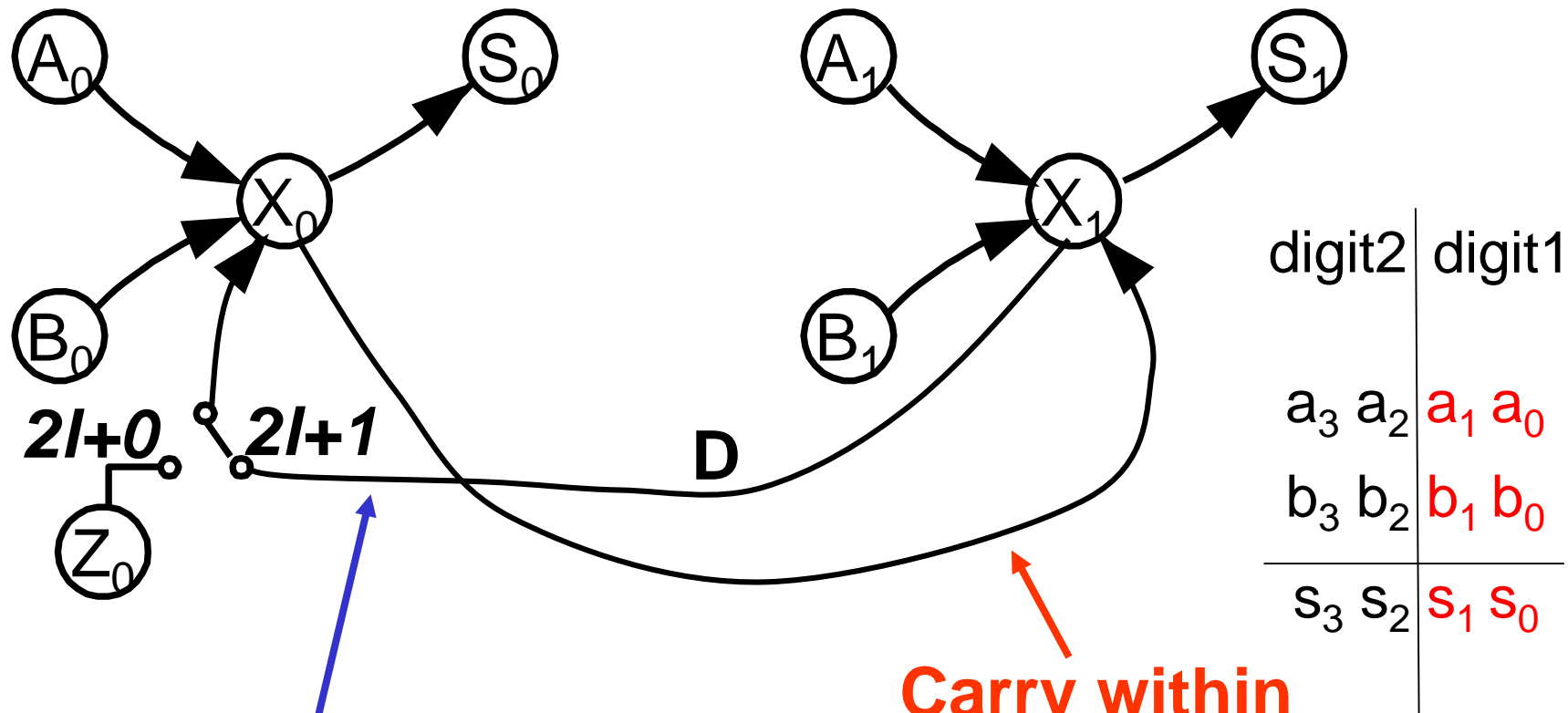

Carry next iteration
 $D=1$


Carry within iteration

Fully Parallel Adder, i.e. $J=4$

 

For each node U in the original DFG, draw J nodes $U_0, U_1, U_2, \dots, U_{J-1}$
 For each edge $U \rightarrow V$ with w delays in the original DFG,
 draw the J edges $U_i \rightarrow V_{(i+w)\%J}$ with $\lfloor (i+w)/J \rfloor$ delays for $i = 0, 1, \dots, J-1$


Unfold the Switch, J=4

 

Write the switching instance as

$$Wl + u = J(W'l + \lfloor u/J \rfloor) + (u \% J)$$


Unfold the Switch, J=4

 

Only 1 time instance 0, i.e. fully parallel

$Z_0 \rightarrow X_0, D_1 \rightarrow X_1, D_2 \rightarrow X_2$ and $D_3 \rightarrow X_3$


Bit-parallel Adder

 


Only 1 time instance 0, i.e. fully parallel

$Z_0 \rightarrow X_0, D_1 \rightarrow X_1, D_2 \rightarrow X_2$ and $D_3 \rightarrow X_3$

Bit-parallel Adder

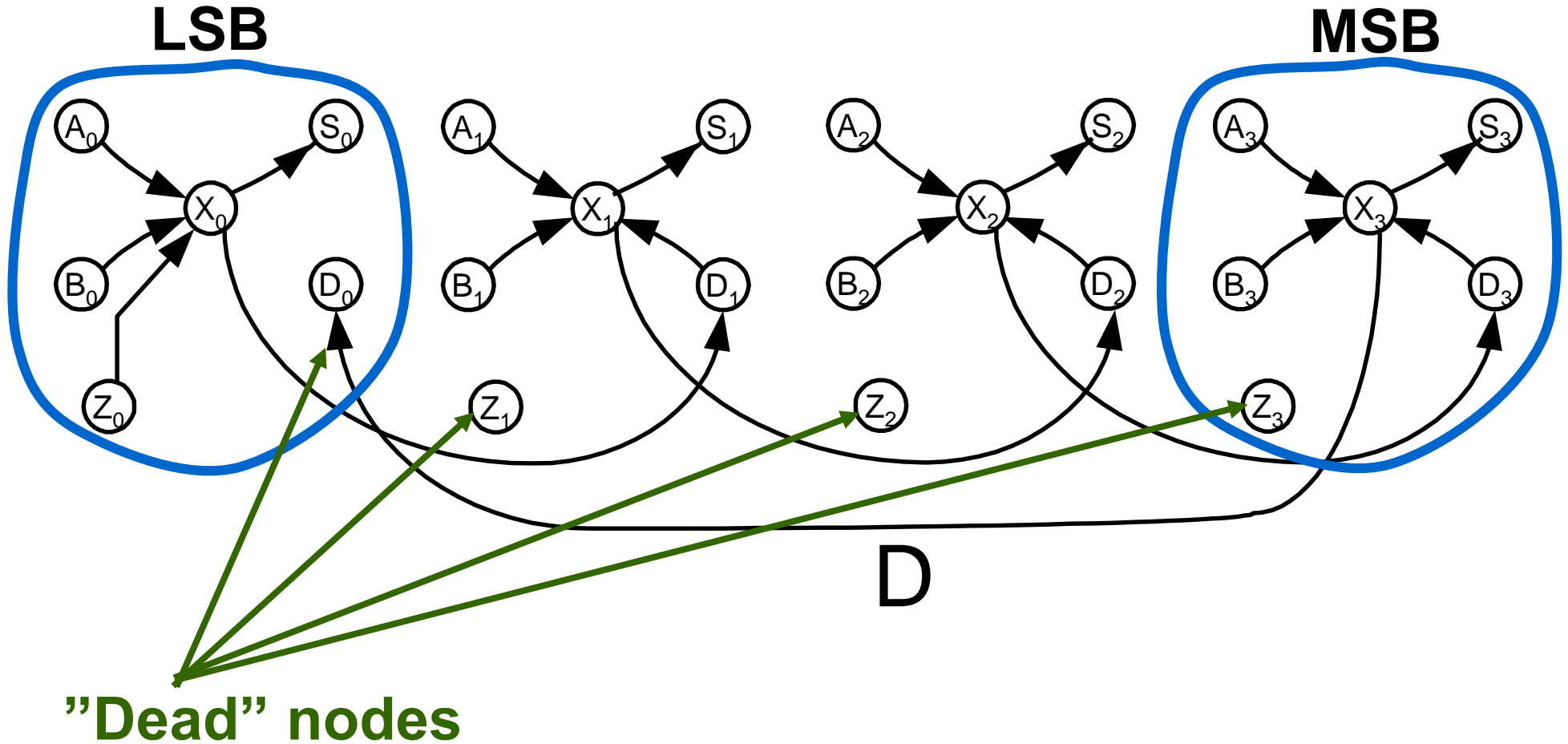

Remove "Dead" and Dummy Nodes

 


"Dead" nodes
can be removed

Dummy nodes
can be removed

Bit-parallel Adder

 Carry from MSB as overflow or if to be used as a 4-bit module



Switch if to be used as a 4-bit module
Carry $\neq 0$


Carry Ripple Adder

$$\begin{array}{r}
 a_3 \ a_2 \ a_1 \ a_0 \\
 b_3 \ b_2 \ b_1 \ b_0 \\
 \hline
 s_3 \ s_2 \ s_1 \ s_0
 \end{array}$$

If Wordlength is not a multiple of J

- **determine** $L=lcm\{W,J\}$, lcm = least common multiple
- **replace switching instance** $Wl+u$ **with** L/W **instances**
 $Ll+u+wW$, for $w=0..L/W-1$
i.e. the switching periodicity has been changed
from W **to** L
- **perform the unfolding as previously**
- **identify the correspondence between original instances and expanded instances**

 Example: Unfold Bit-serial Adder by $J=3$



Wordlength $W=4$ not a multiple of the the unfolding factor $J=3$.

Determine


$$L = \text{lcm}\{W, J\} = \text{lcm}\{4, 3\} = 12$$

Replace

$$Wl+u \text{ with } Ll+u+wW$$

for $w = 0$ to $L/W-1$

 Example: Unfold Bit-serial Adder by $J=3$



Replace


$Wl+u$ with $Ll+u+wW$
for $w=0$ to $L/W-1$

$4l+0$ is now equivalent to
 $12l+0$, $12l+4$ and $12l+8$


and so on...

Unfold as for the regular case.

 Example: Unfold Bit-serial Adder by $J=3$



 Example: Unfold Bit-serial Adder by $J=3$



Write the switching instance as

$$Wl + u = J(W'l + \lfloor u/J \rfloor) + (u \% J)$$


$$12l+0 = 3(4l+0)+0 \quad Z_0 \rightarrow X_0$$

$$12l+4 = 3(4l+1)+1 \quad Z_1 \rightarrow X_1$$


$$12l+8 = 3(4l+2)+2 \quad Z_2 \rightarrow X_2$$

Draw an edge from node $U_{u \% J} \Rightarrow V_{u \% J}$,
 which is switched at time instance
 $(W'l + \lfloor u/J \rfloor)$

 Example: Unfold Bit-serial Adder by $J=3$



Example: Unfold Bit-serial Adder by J=3

 

Write the switching instance as

$$Wl + u = J(W'l + \lfloor u/J \rfloor) + (u\%J)$$

$$12l+1 = 3(4l+0)+1$$

$$12l+2 = 3(4l+0)+2$$

$$12l+3 = 3(4l+1)+0 \quad D_0 \rightarrow X_0$$

$$12l+5 = 3(4l+1)+2$$

$$12l+6 = 3(4l+2)+0 \quad D_0 \rightarrow X_0$$


$$12l+7 = 3(4l+2)+1$$

$$12l+9 = 3(4l+3)+0 \quad D_0 \rightarrow X_0$$


$$12l+10 = 3(4l+3)+1$$

$$12l+11 = 3(4l+3)+2$$

 Example: Unfold Bit-serial Adder by $J=3$



Example: Unfold Bit-serial Adder by J=3

 

Write the switching instance as

$$Wl + u = J(W'l + \lfloor u/J \rfloor) + (u \% J)$$

$$12l+1 = 3(4l+0)+1 \quad D_1 \rightarrow X_1$$

$$12l+2 = 3(4l+0)+2$$

$$12l+3 = 3(4l+1)+0$$

$$12l+5 = 3(4l+1)+2$$

$$12l+6 = 3(4l+2)+0$$


$$12l+7 = 3(4l+2)+1 \quad D_1 \rightarrow X_1$$

$$12l+9 = 3(4l+3)+0$$


$$12l+10 = 3(4l+3)+1 \quad D_1 \rightarrow X_1$$

$$12l+11 = 3(4l+3)+2$$

 Example: Unfold Bit-serial Adder by $J=3$



Example: Unfold Bit-serial Adder by J=3

 


Write the switching instance as

$$Wl + u = J(W'l + \lfloor u/J \rfloor) + (u\%J)$$

$12l+1 =$	$3(4l+0)+1$	
$12l+2 =$	$3(4l+0)+2$	$D_2 \rightarrow X_2$
$12l+3 =$	$3(4l+1)+0$	
$12l+5 =$	$3(4l+1)+2$	$D_2 \rightarrow X_2$
$12l+6 =$	$3(4l+2)+0$	
$12l+7 =$	$3(4l+2)+1$	
$12l+9 =$	$3(4l+3)+0$	
$12l+10 =$	$3(4l+3)+1$	
$12l+11 =$	$3(4l+3)+2$	$D_2 \rightarrow X_2$

 Example: Unfold Bit-serial Adder by $J=3$



c_3	c_2	c_1	c_0	a_3	a_2	a_1	a_0
d_3	d_2	d_1	d_0	b_3	b_2	b_1	b_0
s'_3	s'_2	s'_1	s'_0	s_3	s_2	s_1	s_0


End of Unfolding

Folding

Chapter 6

What is folding??

Folding is the "Inverse" of Unfolding

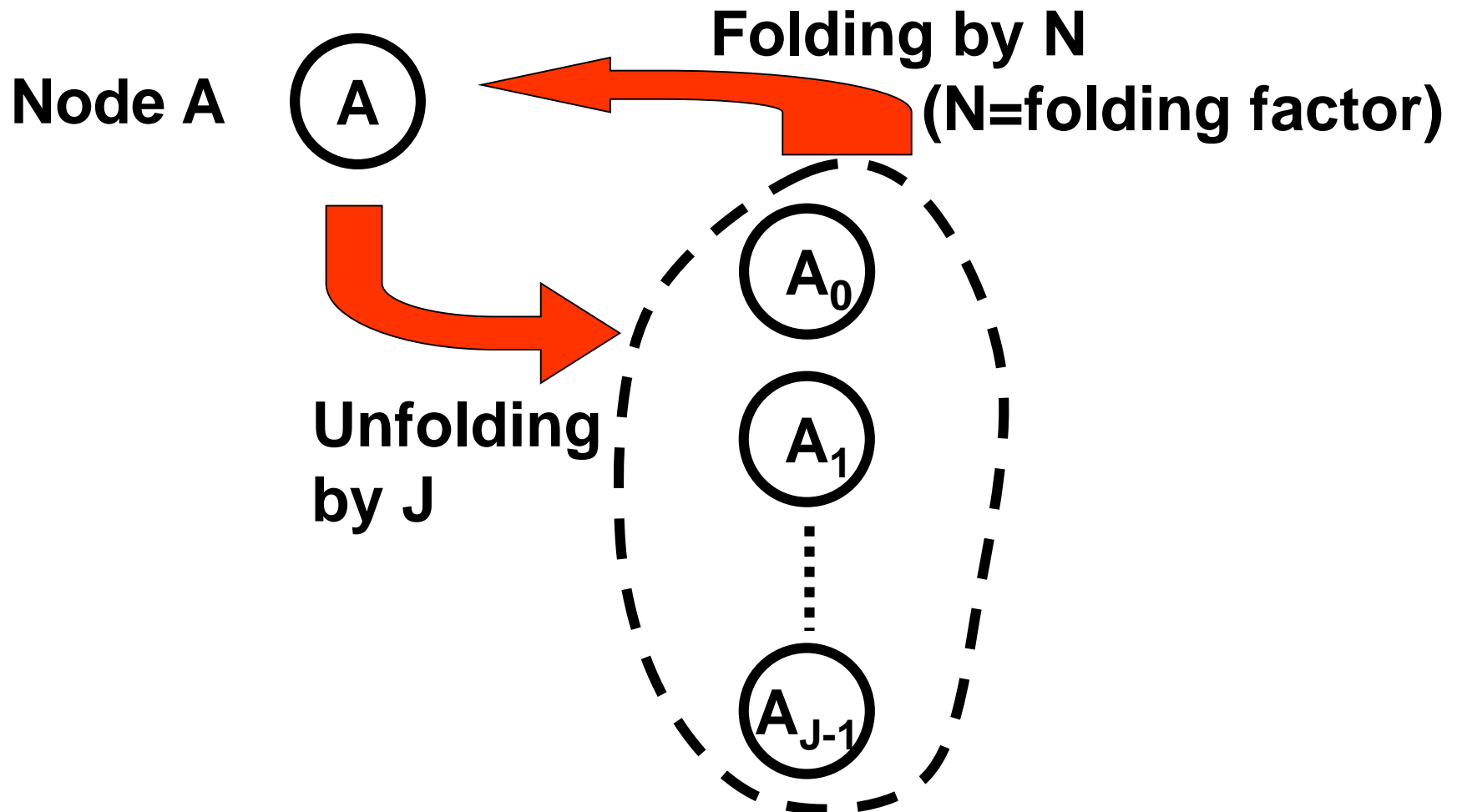



Folding?

- Used to minimize silicon area (trading area for time)!
- A way to systematically determine the control circuits in DSP architectures by folding transformation, where multiple algorithm operations are time-multiplexed to a single functional unit.
- Use for synthesis of DSP architectures that can be operated at single or multiple clocks.
- Use to reduce the number of hardware functional units (FUs) such as adders and mults by a factor of N at the expense of increasing computation time by a factor of N .

But Folding lead to an architecture that uses a large number of registers and thus a register minimization technique needs sometime to be applied.

Hardware Mapped vs. Time multiplexed
  
$$FIR : y(n) = \sum_{k=0}^{N-1} h(k)x(n-k)$$




1 sample/cc
N fixed multipliers
N-1 adders


N cc/sample
1 generalized multiplier
1 adders
1 coefficient memory
+ control

Hardware Mapped vs. Time multiplexed/Microcoded

Biquad Filter

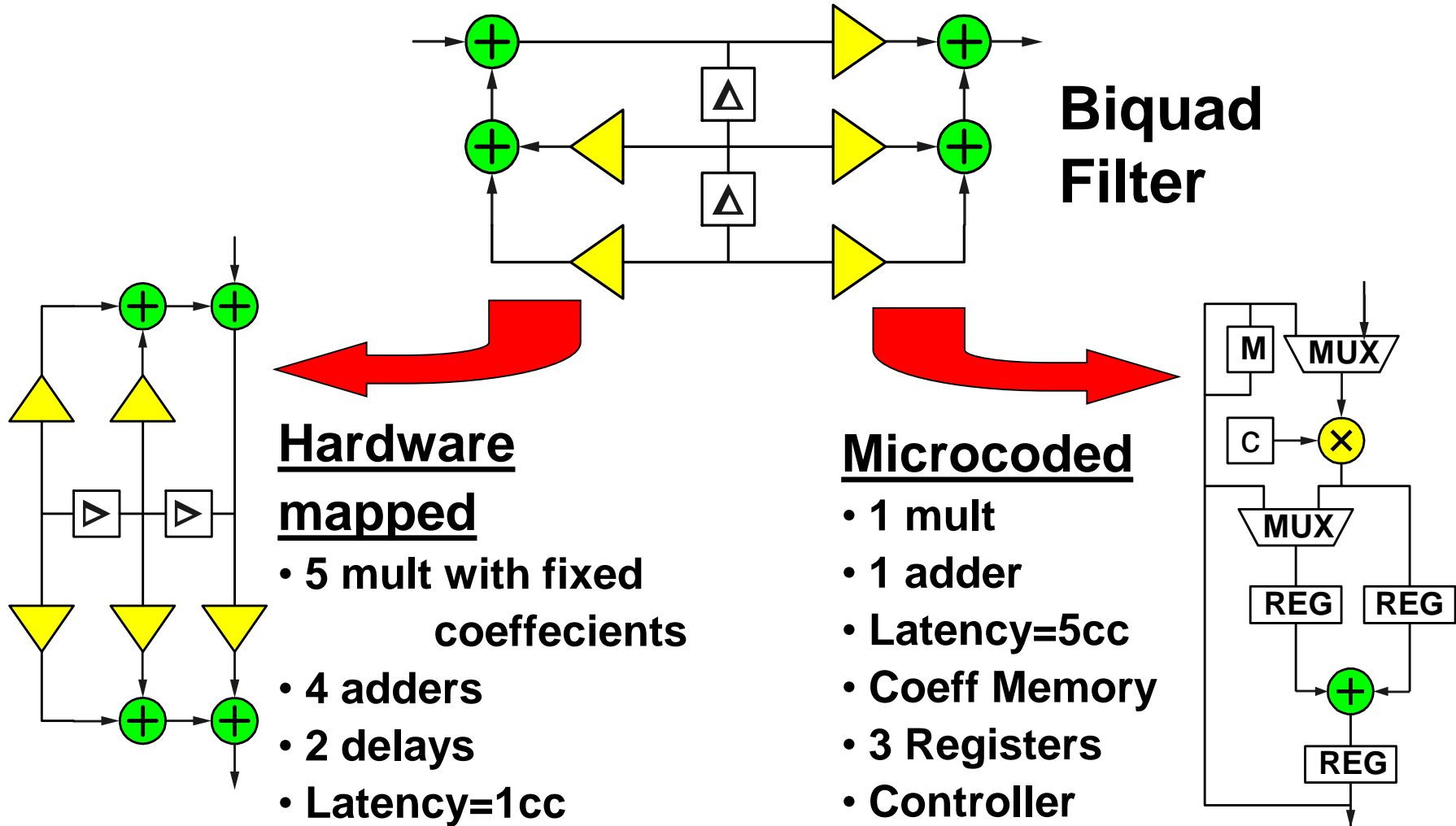


Folding – Time-shared Architecture

 


Folding is a technique to reduce the silicon area by time-multiplexing many operations into single functional units.

- The right figure shows a 2 times folded architecture where 2 additions are folded, or time-multiplexed, to a single adder
- Folding introduces registers/storage
- Computation time increased, e.g. one output sample every 2 cc (one input signal consumed every 2cc)


Folding Example – A more detailed look!
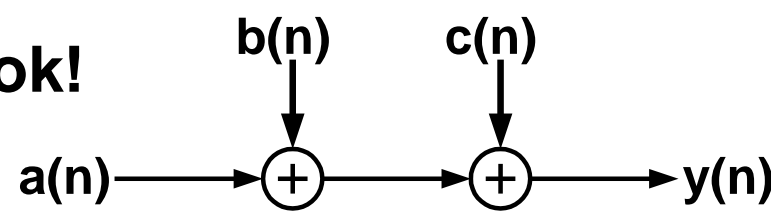
$$y(n) = a(n) + b(n) + c(n)$$

  
 
Cycle 0




Cycle 1




Cycle 2



Cycle 3

 

Control Unit

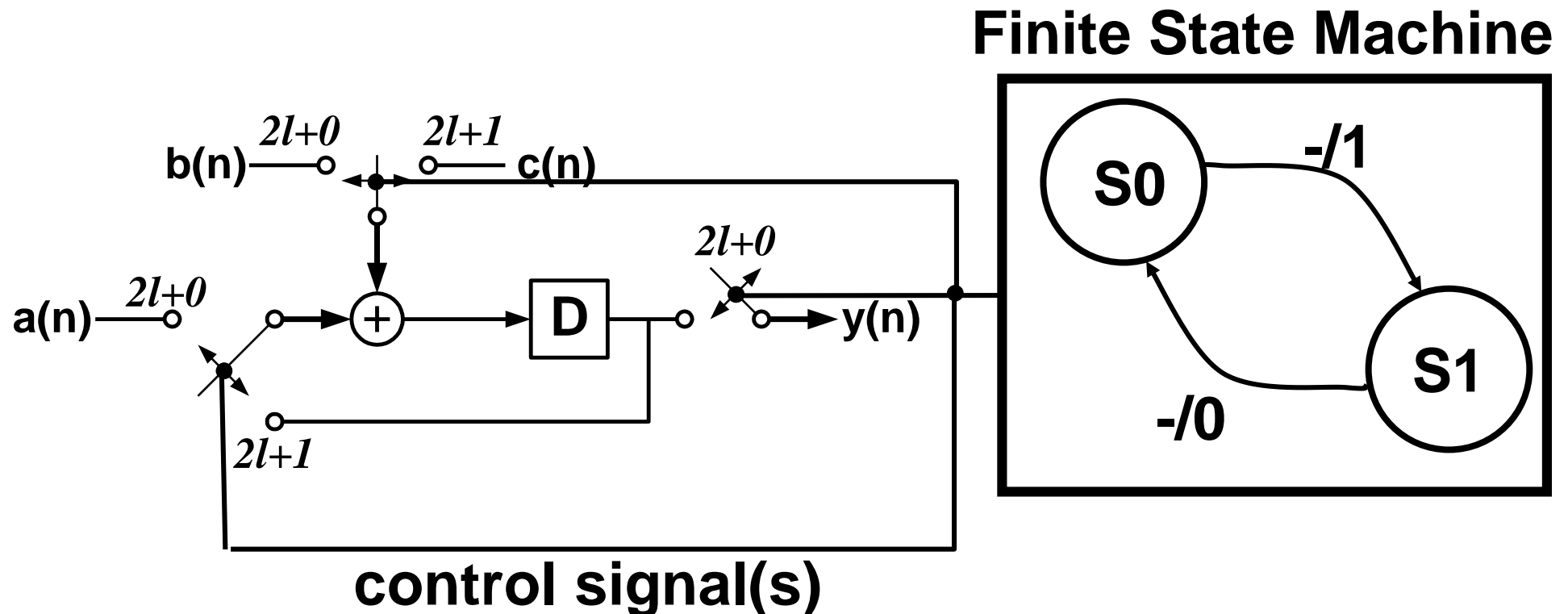


Control units can be complex in large systems!

Folding



- Reduce hardware by N-folding
- $T_{\text{computation}}$ increased by N \Leftrightarrow Latency
- Extremes
 - Fully parallel
 - Time multiplexed = 1 unit per algorithmic operation
- Folding \Leftrightarrow
 - extra registers, i.e. extra storage
 - a more complex control unit
 - more latency

Folding Transformation

 N=folding factor
Nr. of operations
folded to a single
unit




$l = \text{iteration}$

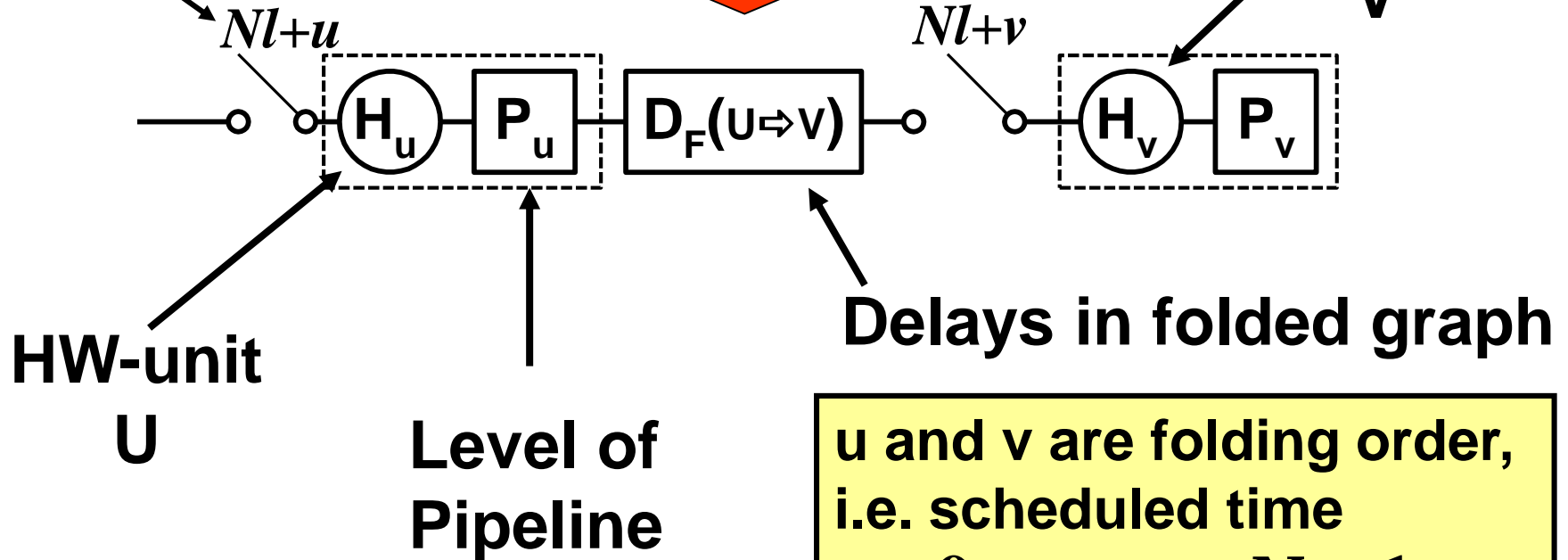 

u and v are folding order,
i.e. scheduled time

$$0 \leq u, v \leq N - 1$$

Folding Transformation

 

- H_u is pipelined by P_u stages and its output is available at $Nl + u + P_u$.
- Edge $U \rightarrow V$ has $w(e)$ delays \Rightarrow the l -th iteration of U is used by $(l + w(e))$ th iteration of node V , which is executed at $N(l + w(e)) + v$.

So, the result should be stored for :

$$D_F(U \rightarrow V) = [N(l + w(e)) + v] - [Nl + P_u + u]$$

$$\Rightarrow D_F(U \rightarrow V) = Nw(e) - P_u + v - u \quad \underline{\text{(independent of } l)}$$

Folding Set

- A folding set is an ordered set of operations to be executed on the same functional unit.
- The folding set are typically obtained from a scheduling and allocation algorithm (ref. Appendix B)
- The folding set represents underlying folding transformation
- Each set contain N entries, N=folding factor.

Folding order: 0 1 2 (... N-1)

$$S_1 = \{A_1, 0, A_2\}$$


A_1 belongs to folding set S_1 with folding order 0

N=3


↑
Null operation

$$(S_1 | 0)$$

Ex. Folding of Biquad filter

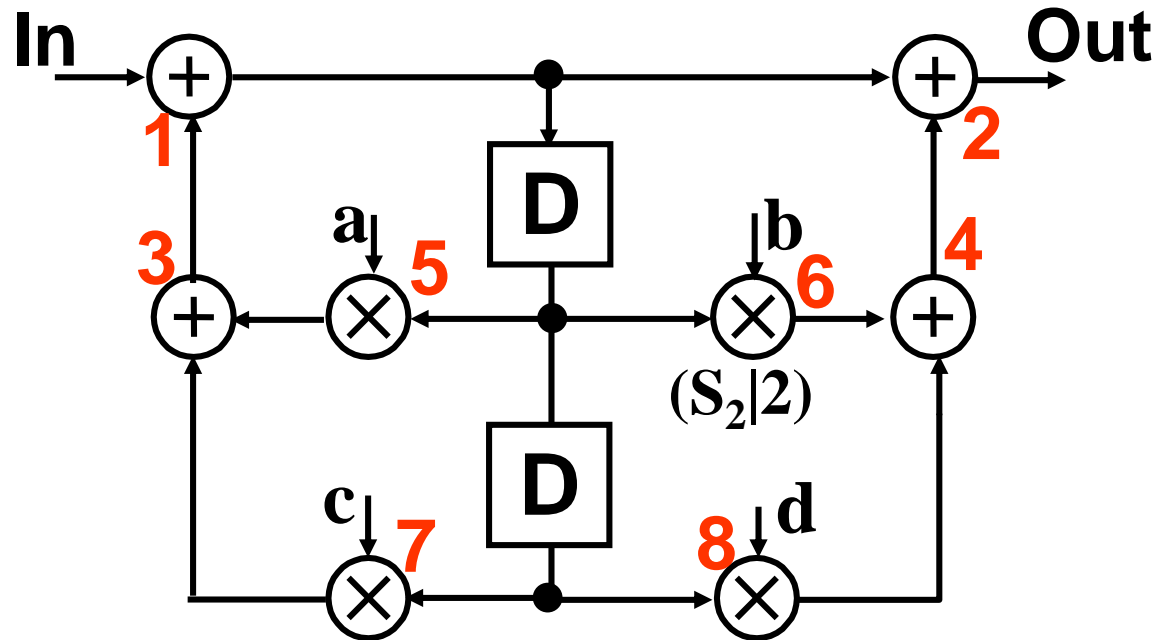

Ex. Folding of Biquad filter

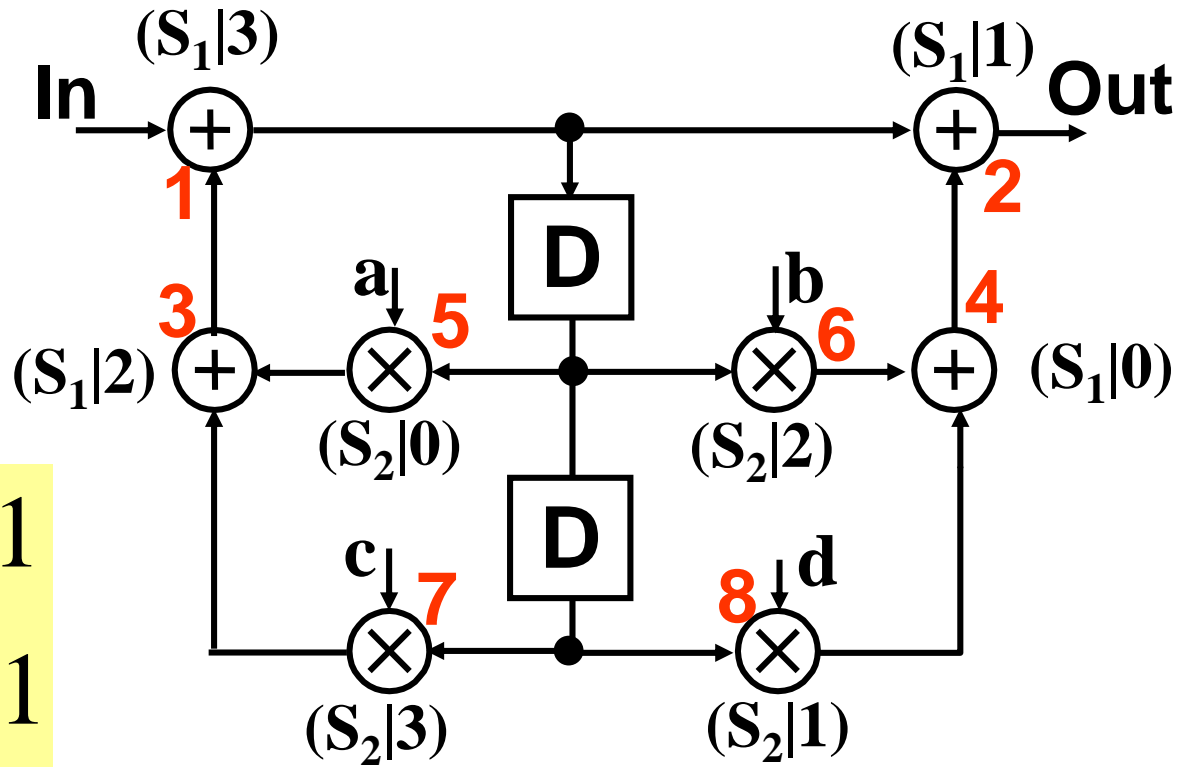

$$T_{adder} = 1$$

$$P_{adder} = 1$$

$$T_{mult} = 2$$

$$P_{mult} = 2$$

Additions

$$S_1 = \{4, 2, 3, 1\}$$

Multiplication

$$S_2 = \{5, 8, 6, 7\}$$


Folding of Biquad filter, N=4

$$D_F(U \rightarrow V) = Nw(e) - P_u + v - u$$

receive
send


A delay between two edges can not be negative!

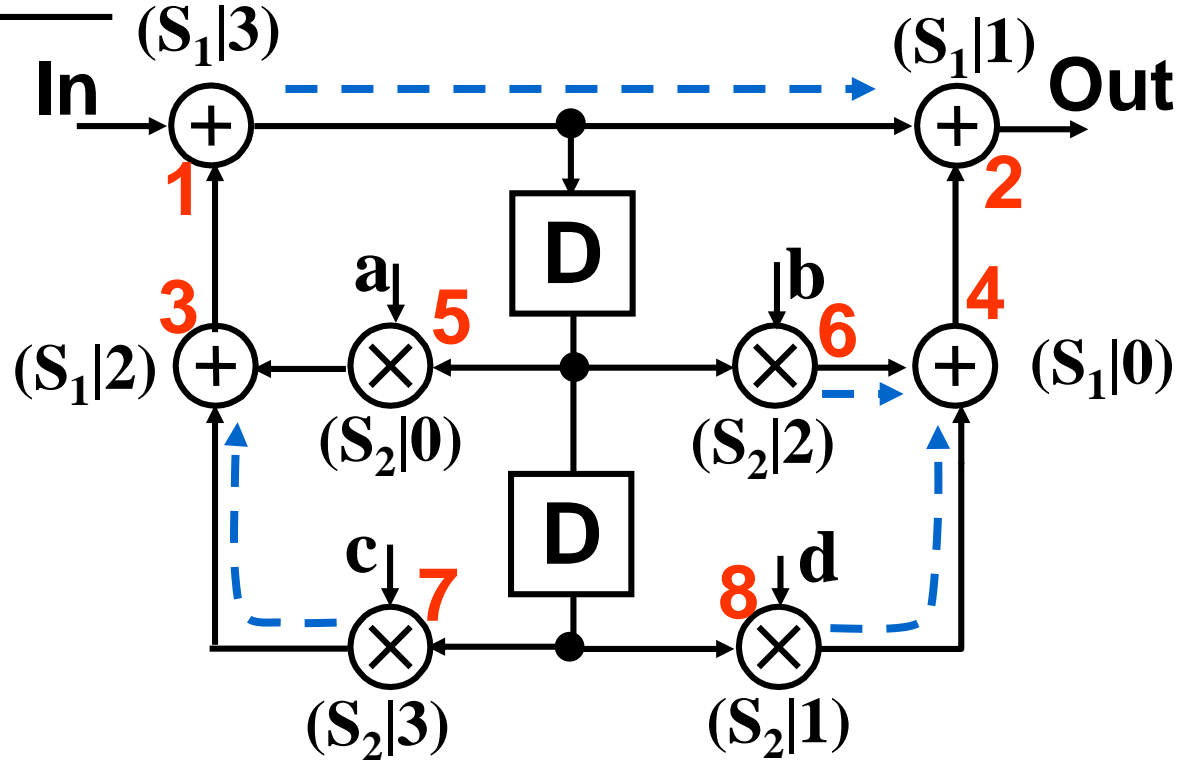- $D_F(1 \rightarrow 2) = -3$
- $D_F(1 \rightarrow 5) = 0$
- $D_F(1 \rightarrow 6) = 2$
- $D_F(1 \rightarrow 7) = 7$
- $D_F(1 \rightarrow 8) = 5$
- $D_F(3 \rightarrow 1) = 0$
- $D_F(4 \rightarrow 2) = 0$
- $D_F(5 \rightarrow 3) = 0$
- $D_F(6 \rightarrow 4) = -4$
- $D_F(7 \rightarrow 3) = -3$
- $D_F(8 \rightarrow 4) = -3$




$D_F(U \rightarrow V) < 0 \Rightarrow$ Not Valid folding


Retiming: Folding of Biquad filter, N=4

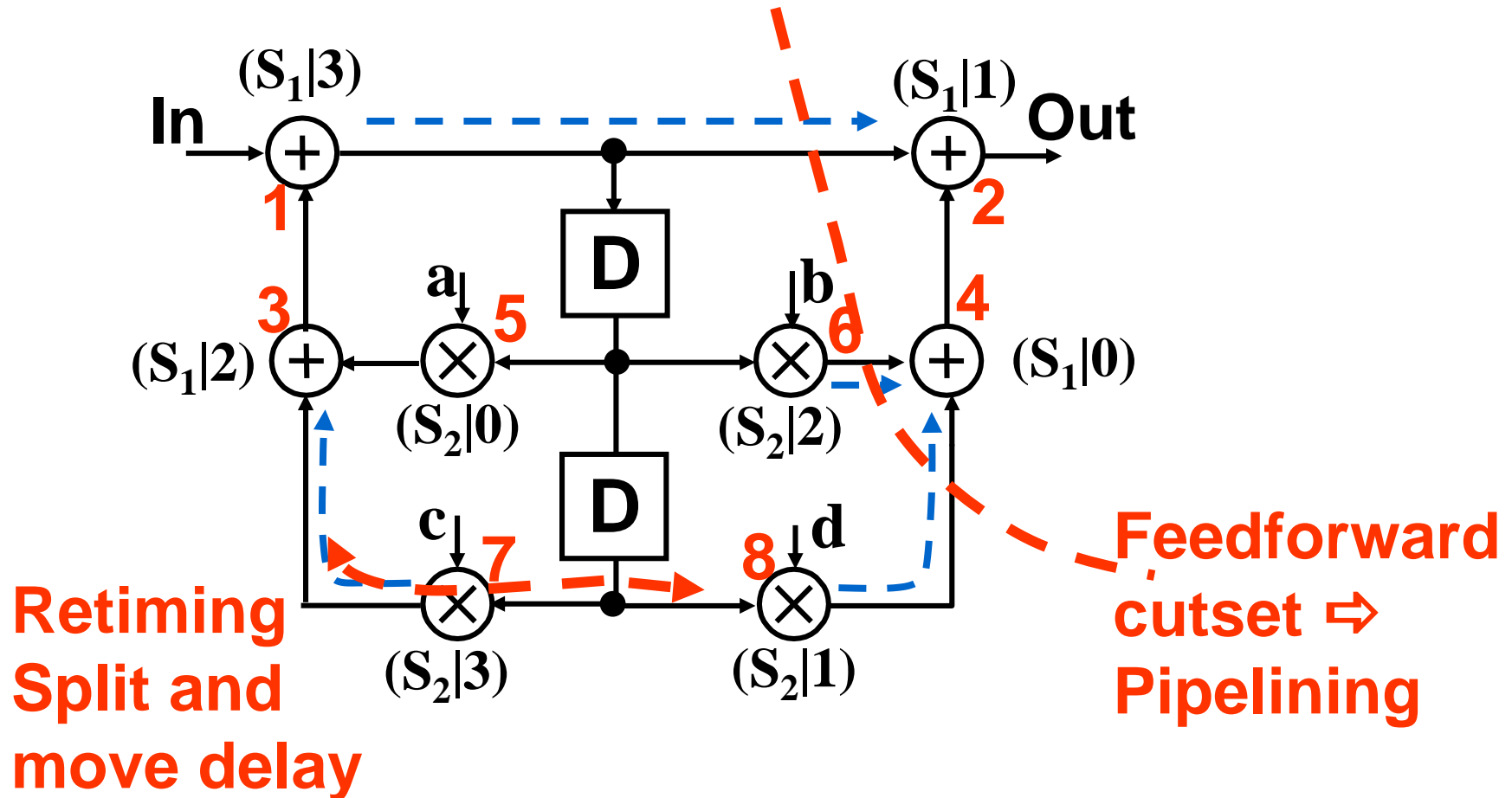

Folding of retimed Biquad filter

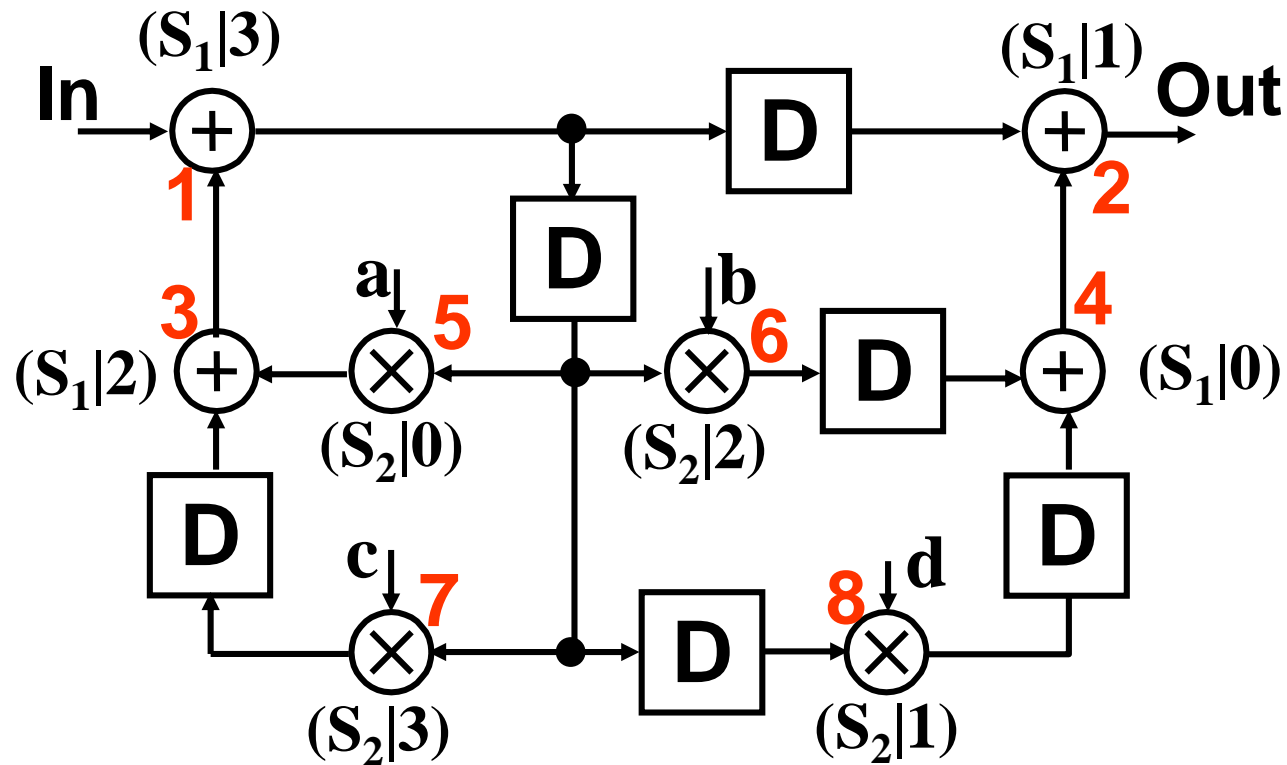

Systematic way of: Retiming for Folding

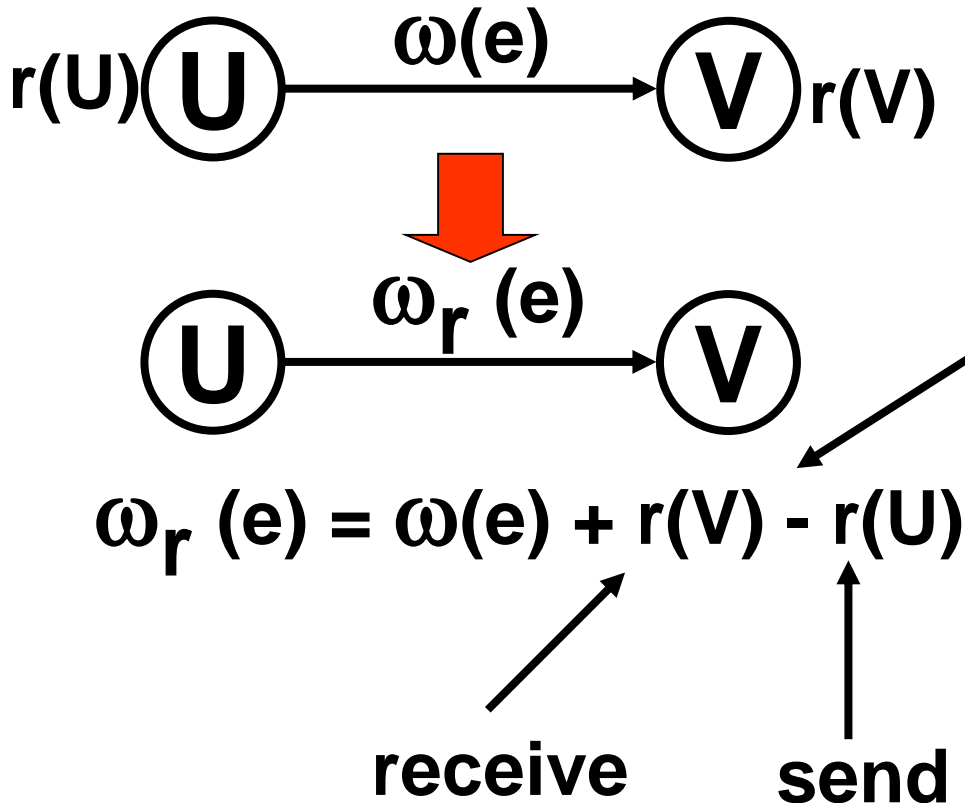

If $D'_F(U \rightarrow V)$ is the folded delays of the edge $U \rightarrow V$ for the retimed graph then $D'_F(U \rightarrow V) \geq 0 \Leftrightarrow$

$$Nw_r(e) - P_U + v - u \geq 0$$

$$\Rightarrow N(w(e) + r(V) - r(U)) - P_U + v - u \geq 0$$

$$\Rightarrow N(r(U) - r(V)) \leq \underline{Nw(e) - P_U + v - u}$$

$$\Rightarrow r(U) - r(V) \leq D_F(U \rightarrow V) / N$$


$$\Rightarrow r(U) - r(V) \leq \lfloor D_F(U \rightarrow V) / N \rfloor$$

\Rightarrow (floor since retiming values are integers)

Then solve the the system of inequalities!

Folding of retimed Biquad filter,

N=4

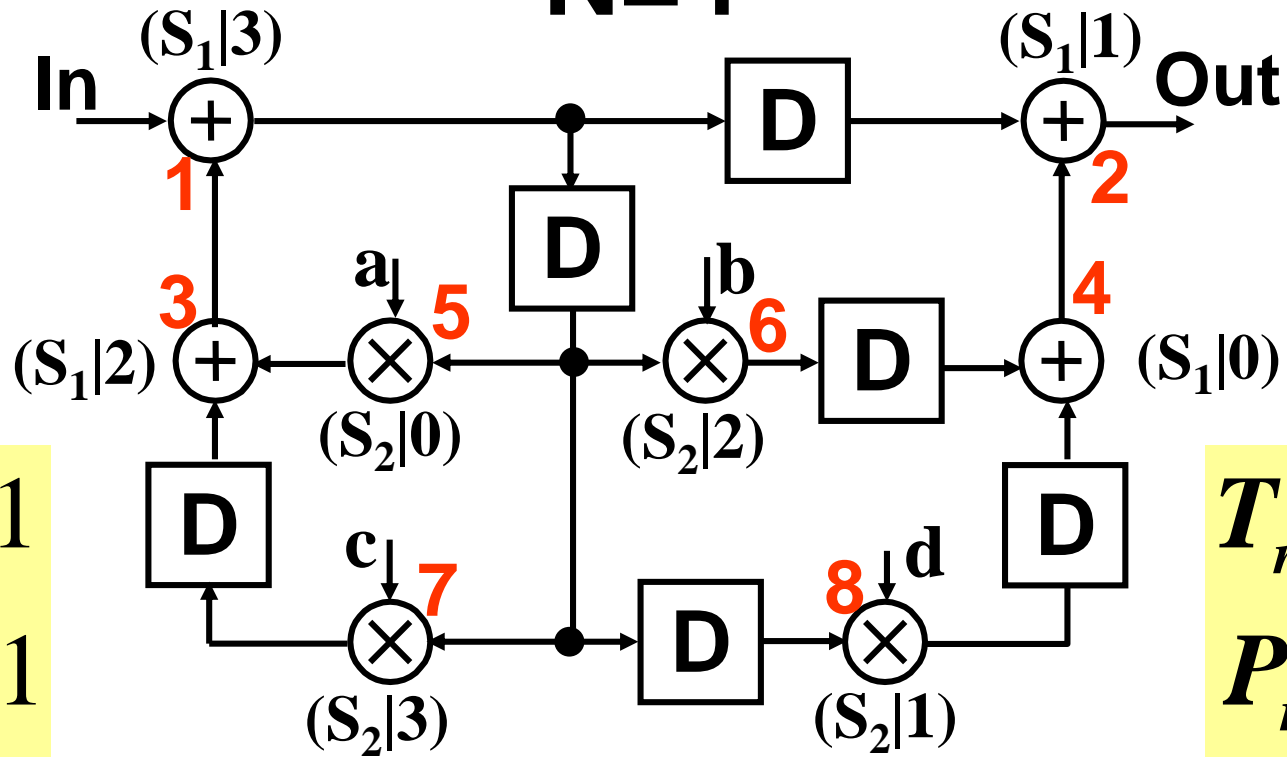

$T_{adder} = 1$
 $P_{adder} = 1$

$T_{mult} = 2$
 $P_{mult} = 2$

Additions

Multiplication

$S_1 = \{4, 2, 3, 1\}$

$S_2 = \{5, 8, 6, 7\}$

Folding of retimed Biquad filter,


N=4

receive

send

$$D_F(U \rightarrow V) = Nw(e) - P_u + v - u$$

- $D_F(1 \rightarrow 2) = 4(1) - 1 + 1 - 3 = 1$
- $D_F(1 \rightarrow 5) = 4(1) - 1 + 0 - 3 = 0$
- $D_F(1 \rightarrow 6) = 4(1) - 1 + 2 - 3 = 2$
- $D_F(1 \rightarrow 7) = 4(1) - 1 + 3 - 3 = 3$
- $D_F(1 \rightarrow 8) = 4(2) - 1 + 1 - 3 = 5$
- $D_F(3 \rightarrow 1) = 4(0) - 1 + 3 - 2 = 0$
- $D_F(4 \rightarrow 2) = 4(0) - 1 + 1 - 0 = 0$
- $D_F(5 \rightarrow 3) = 4(0) - 2 + 2 - 0 = 0$
- $D_F(6 \rightarrow 4) = 4(1) - 2 + 0 - 2 = 0$
- $D_F(7 \rightarrow 3) = 4(1) - 2 + 2 - 3 = 1$
- $D_F(8 \rightarrow 4) = 4(1) - 2 + 0 - 1 = 1$

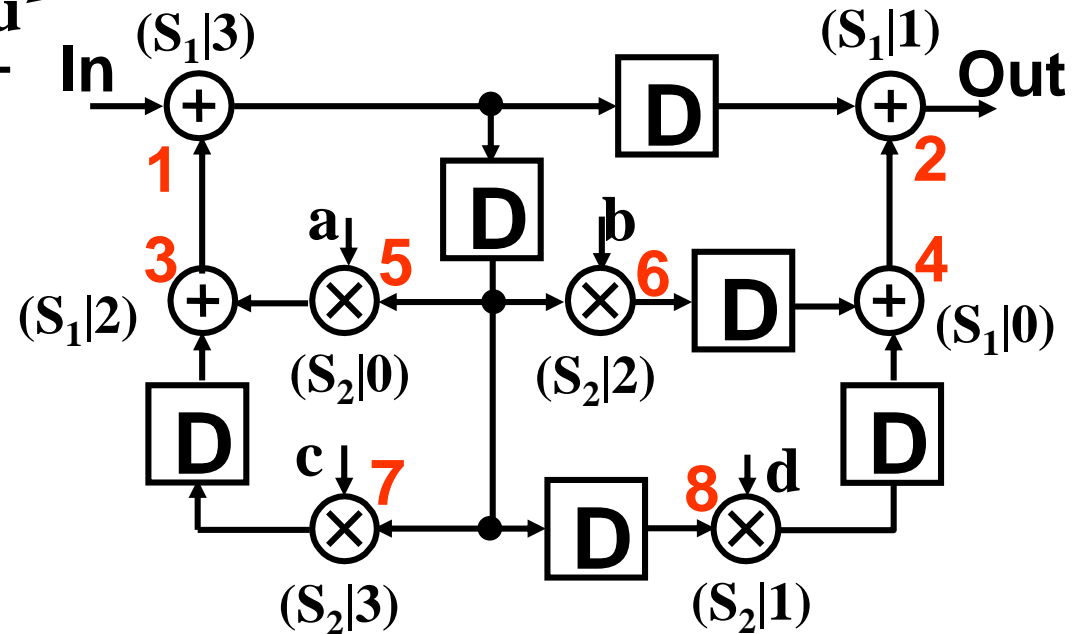

Valid folding

$$D_F(U \rightarrow V) \geq 0$$

Folding of retimed Biquad filter,

N=4


receive

send

$$P_{adder} = 1$$

$$D_F(U \rightarrow V) = Nw(e) - P_u + v - u$$

- $D_F(1 \rightarrow 2) = 4(1) - 1 + 1 - 3 = 1$
- $D_F(1 \rightarrow 5) = 4(1) - 1 + 0 - 3 = 0$
- $D_F(1 \rightarrow 6) = 4(1) - 1 + 2 - 3 = 2$
- $D_F(1 \rightarrow 7) = 4(1) - 1 + 3 - 3 = 3$
- $D_F(1 \rightarrow 8) = 4(2) - 1 + 1 - 3 = 5$
- $D_F(3 \rightarrow 1) = 4(0) - 1 + 3 - 2 = 0$
- $D_F(4 \rightarrow 2) = 4(0) - 1 + 1 - 0 = 0$
- $D_F(5 \rightarrow 3) = 4(0) - 2 + 2 - 0 = 0$
- $D_F(6 \rightarrow 4) = 4(1) - 2 + 0 - 2 = 0$
- $D_F(7 \rightarrow 3) = 4(1) - 2 + 2 - 3 = 1$
- $D_F(8 \rightarrow 4) = 4(1) - 2 + 0 - 1 = 1$

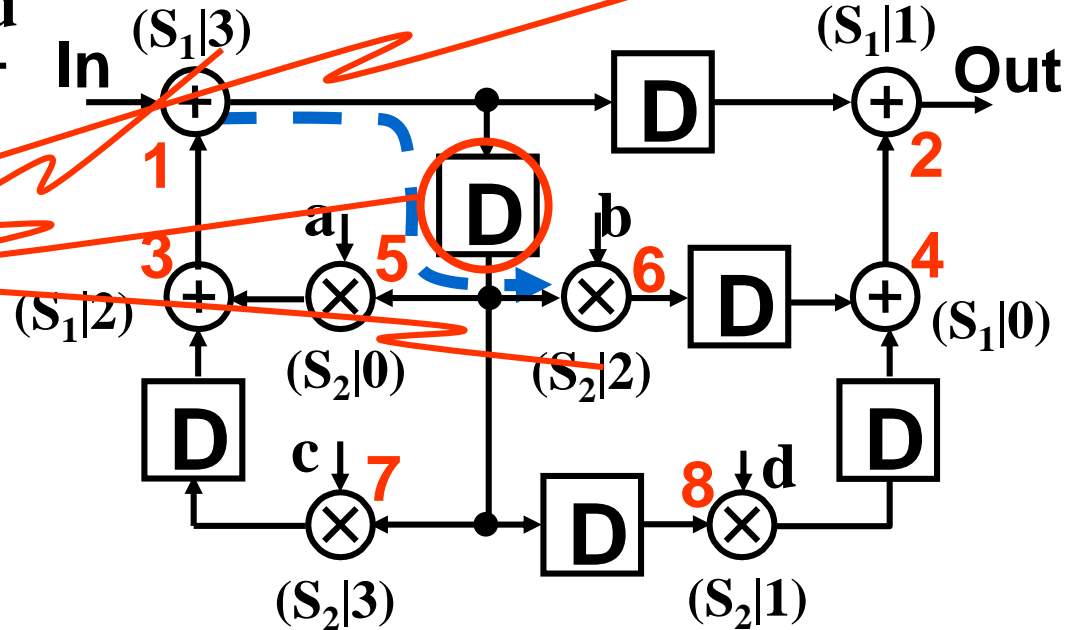


Valid folding

$$D_F(U \rightarrow V) \geq 0$$

Folding of retimed Biquad filter,

N=4

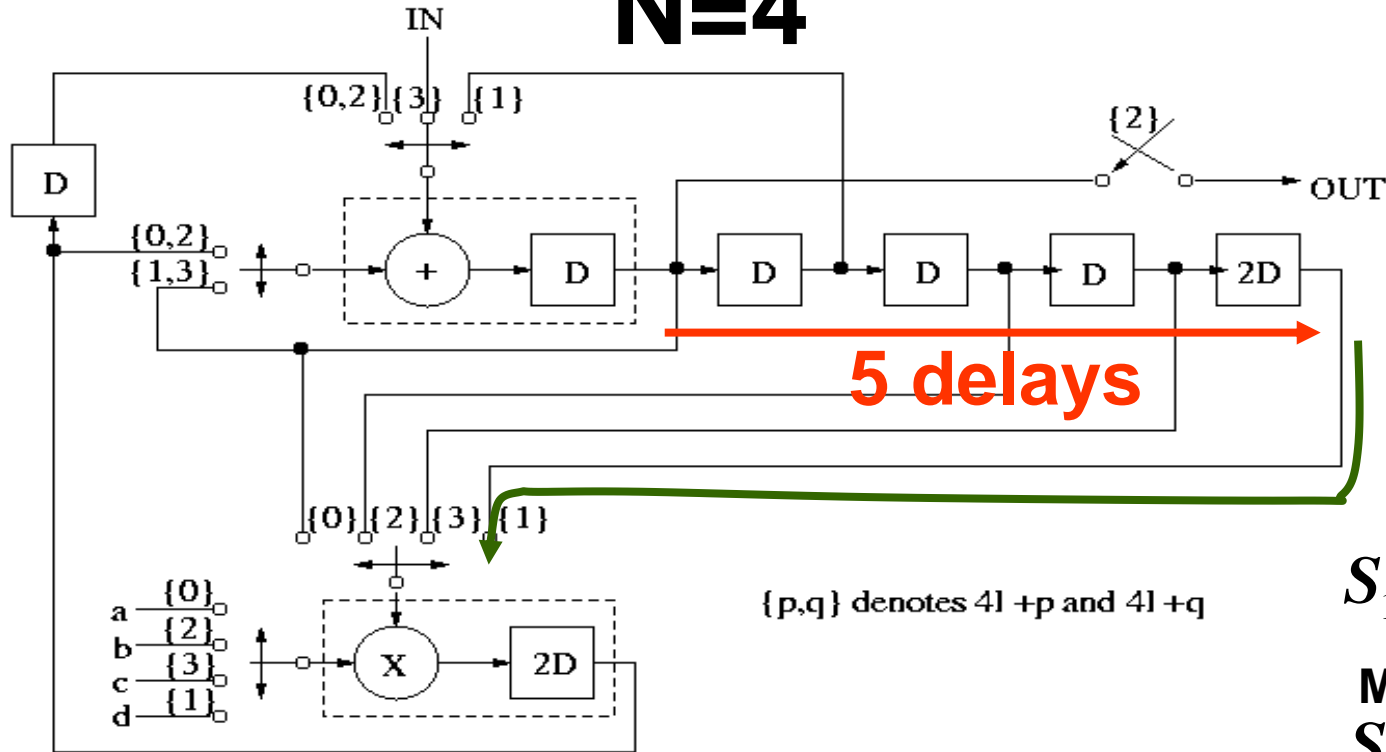

{p,q} denotes $4l + p$ and $4l + q$

Additions

$$S_1 = \{4, 2, 3, 1\}$$

Multiplication


$$S_2 = \{5, 8, 6, 7\}$$

$$D_F(U \rightarrow V) = Nw(e) - P_u + v - u$$

$$D_F(1 \rightarrow 8) = 4(2) - 1 + 1 - 3 = 5 \Rightarrow \text{path from add to mult with } 5D$$

Node 8 has folding order 1 \Rightarrow switch close at 1

Folding of retimed Biquad filter

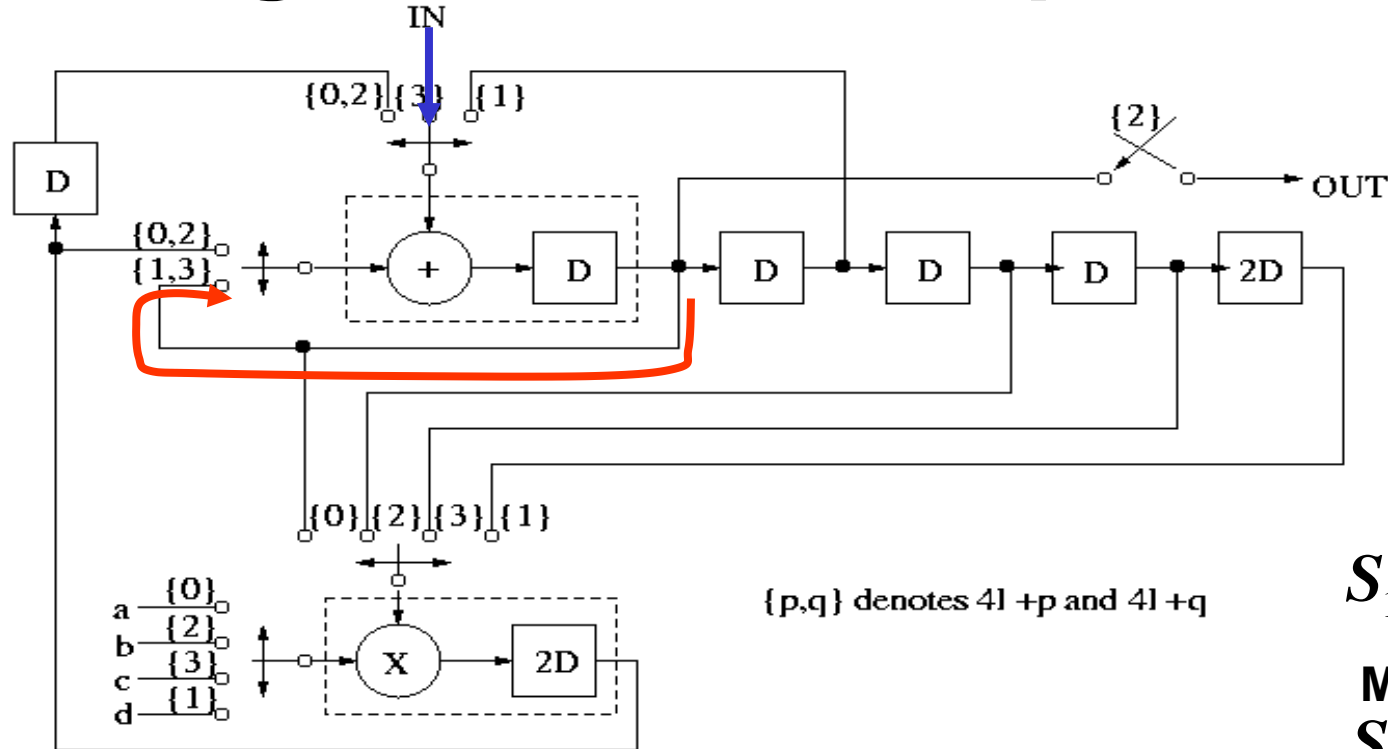

Additions
 $S_1 = \{4,2,3,1\}$


Multiplication
 $S_2 = \{5,8,6,7\}$

$D_F(3 \rightarrow 1) = 4(0) - 1 + 3 - 2 = 0 \Rightarrow$ path from add to add with $0D$

Node 1 has folding order 3 \Rightarrow switch close at 3 \rightarrow

Node 1 is also connected to the input \rightarrow

Folding of retimed Biquad filter

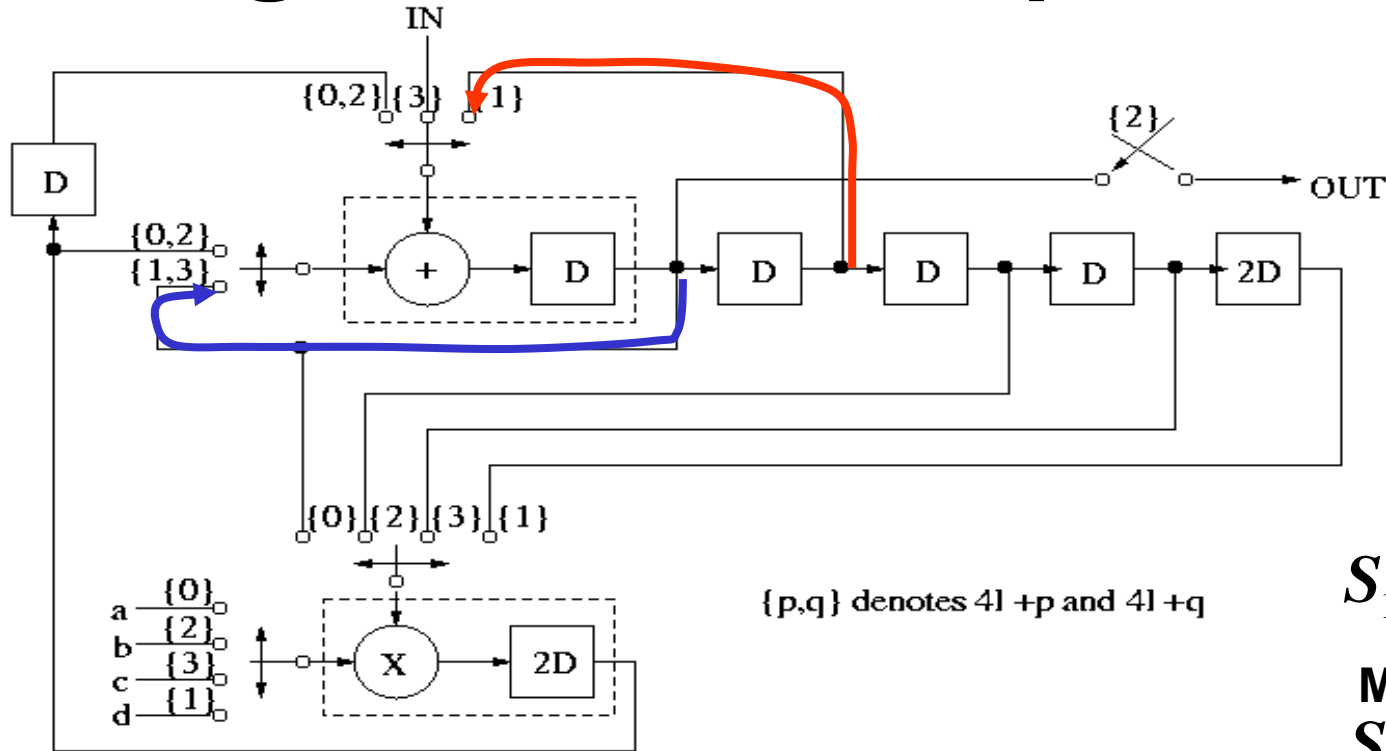

Additions

$$S_1 = \{4, 2, 3, 1\}$$

Multiplication

$$S_2 = \{5, 8, 6, 7\}$$

Execution of node 2 (input from node 1 and 4) :

$$D_F(1 \rightarrow 2) = 4(1) - 1 + 1 - 3 = 1 \Rightarrow \text{path from add to add with 1D}$$

Node 2 has folding order 1 \Rightarrow switch close at 1 \rightarrow

$$D_F(4 \rightarrow 2) = 4(0) - 1 + 1 - 0 = 0 \Rightarrow \text{path from add to add with 0D} \rightarrow$$

End of Lecture