



LUND UNIVERSITY

Exercises in DSP Design 2016

&

Exam from 2005-12-12

Exam from 2004-12-13

Some helpful equations

- Retiming:

$$\omega_r(e) = \omega(e) + r(V) - r(U)$$

- Folding:

$$D_F(U \rightarrow V) = Nw(e) - P_u + v - u$$

- Unfolding:

$$U_i \rightarrow V_{(i+w)\%J}, \quad \lfloor (i+w)/J \rfloor \text{ delays for } i = 0, \dots, J-1$$

- Unfolding of switch:

Switching instance

$$Wl + u = J(W'l + \lfloor u/J \rfloor) + (u\%J)$$

Edge:

$$U_{u\%J} \rightarrow V_{u\%J}$$

If the wordlength is not a multiple of J , determine

$$L = \text{lcm}\{W, J\}$$

Replace $Wl + u$ with the L/W instances

$$Ll + u + wW, \quad \text{for } w = 0, \dots, L/W - 1$$

- Pipelining:

$$T_{\text{seq}} = \frac{C_{\text{ch}} \cdot V_{\text{dd}}}{k(V_{\text{dd}} - V_{\text{t}})^2}, \quad T_{\text{pip}} = \frac{(C_{\text{ch}}/M) \cdot \beta V_{\text{dd}}}{k(\beta V_{\text{dd}} - V_{\text{t}})^2}$$

- Parallel processing:

$$T_{\text{par}} = L \cdot T_{\text{seq}} = \frac{C_{\text{ch}} \cdot \beta V_{\text{dd}}}{k(\beta V_{\text{dd}} - V_{\text{t}})^2}$$

Assignments

1. Short Questions

- (a) List 3 architectural technologies that are used to implement Digital Signal Processing. Differentiate them in terms of performance, energy consumption, programmability and development time.
- (b) What are FPGAs and ASICs? How are they different from each other?
- (c) Describe/explain the following
 - FFT.
 - FIR filter.
 - IIR filter.
- (d) Cut-off frequency in a digital filter.

2. A digital word has a wordlength of 6 bits.

- (a) What is the resolution if $V_{\max} = 1$ V?
- (b) What is the dynamic range if $V_{\text{LSB}} = 0.1$ V?

3. Express the following 2's complement numbers in decimal notation.

- 0010.1101
- 1011.0011

- (a) Truncation at the binary point results in ...?
- (b) What is the difference to rounding?
- (c) Explain the term DC error.
- (d) Apply sign extension to the numbers above.

4. Add the following three numbers in two steps, first carry out $\nu = \nu_1 + \nu_2$, then $\nu + \nu_3$. Use 5 bits in 2's complement notation for $\nu_1 = 0.6875$, $\nu_2 = 0.8125$, and $\nu_3 = -0.5625$.

5. Describe the concept of safe scaling.

- (a) What is the safe scaling factor if $\mathbf{h} = [0.1, -0.3, 0.7, -0.3, 0.1]$?
- (b) Draw an architecture that uses the property of \mathbf{h} .
- (c) What is the complexity reduction compared to a direct implementation?
- (d) Consider another impulse response $\mathbf{g} = [0.1, 0.5, 0, -0.5, -0.1]$. Modify the previous architecture to cope with \mathbf{g} .

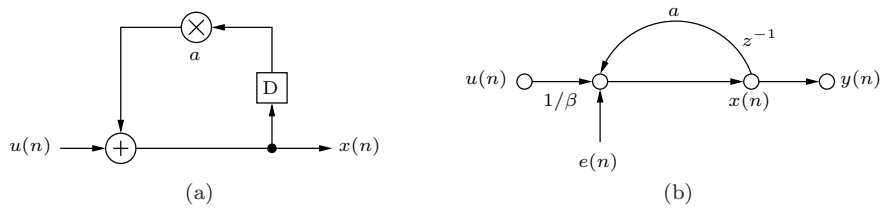


Figure 1: A first order all-pole IIR filter (a) and its scaled signal graph (b).

6. What is the maximum output at $x(n)$ if we have a single feedback section ($|a| < 1$) as shown in Figure 1(a) and $u(n)$ is the step function. What can we do to avoid internal overflows?

If the introduced error $e(n)$ is uniformly distributed white noise and uncorrelated to all other signals

- Calculate the intervals for round-off and truncation errors of $e(n)$.
- What is the mean and variance for the above two types of quantization errors?
- Calculate the SQNR for rounding and truncation.

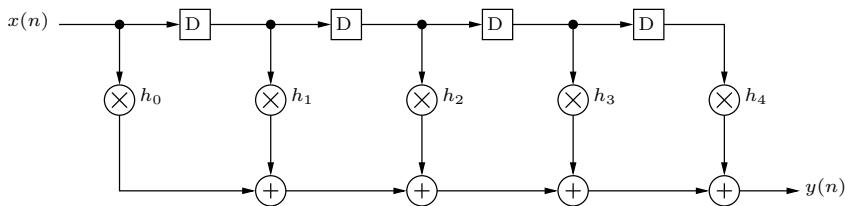


Figure 2: A 5-tap FIR filter in direct form.

7. Consider the 5-tap FIR filter in Figure 2 in the time domain.
- Transpose the filter using the SFG.
 - Show that the functionality is not altered between direct and transposed form.
 - Introduce a one-stage pipeline and show the functionality.

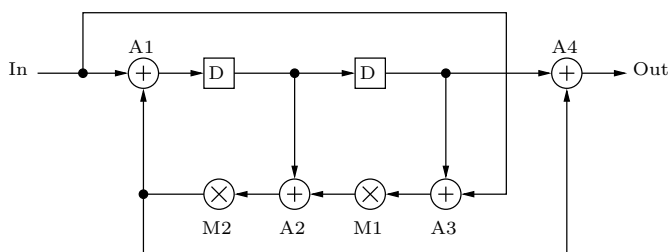


Figure 3: An IIR filter structure.

8. For the digital filter in Figure 3:
- Define the iteration bound and explain its meaning.

- (b) Find the iteration bound of the filter. Assume that a multiplication requires 2 t.u. and an add operation 1 t.u.
- (c) Transpose the filter.

9. Consider the lattice filter in Figure 4.

- (a) What is the iteration bound expressed in T_{add} and T_{mult} ?
- (b) What is the critical path?

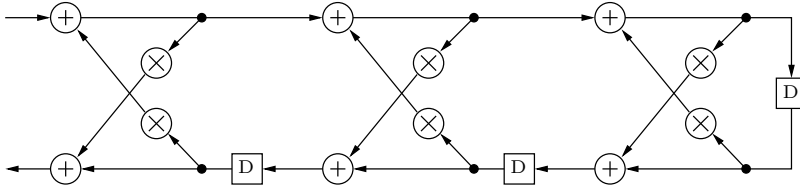


Figure 4: Lattice filter.

10. In Figure 5, calculate the critical path and the iteration bound.

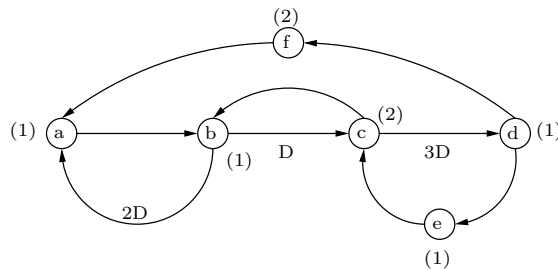


Figure 5: A DFG with node computation times.

11. † Consider the graph shown in Figure 6. Assume that T_{add} and T_{mult} are 1 t.u. and 2 t.u. .

- (a) Compute the iteration bound according to the LPM-algorithm.
- (b) The LPM algorithm is more suitable for calculation using a computer program. Construct a program (MATLAB, C, ...) and verify it by calculating the iteration bound for the graph in Figure 6

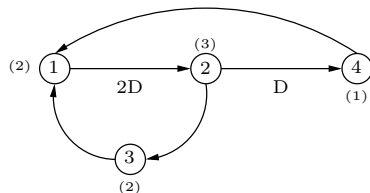


Figure 6: A DFG with node computation times.

12. † Consider the DFG in Figure 8 and assume the computation time for each node to be T .

- (a) What is the maximum achievable sample rate?

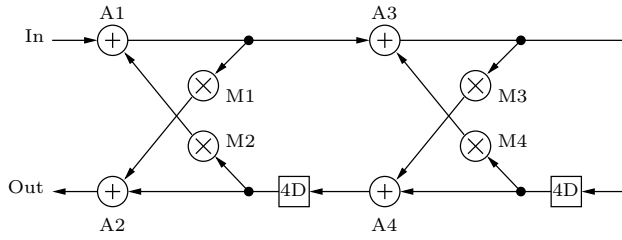


Figure 7: A 4-level pipelined all-pass 8th order IIR filter.

- (b) Place feedforward registers at appropriate feedforward cutsets such that the sample rate will be approximately equal to $1/T$. Count the number of registers.
- (c) You only got 4 pipeline registers available. What is the achievable sample rate now?

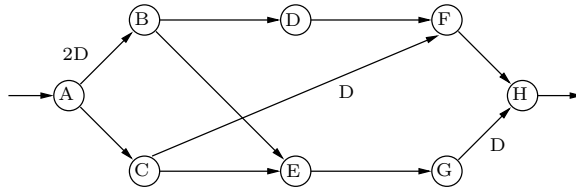


Figure 8: A DFG.

13. † Consider the IIR filter in Figure 9. Assume T_{mult} 2 t.u. and T_{add} 1 t.u.
- (a) Calculate the critical path.
- (b) Pipeline the filter to reduce the critical path to 3 t.u.

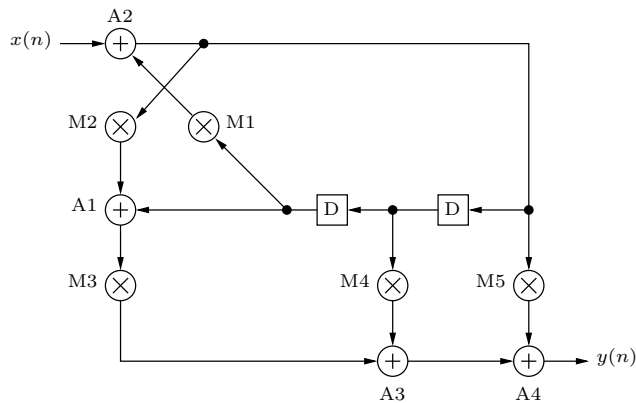


Figure 9: Digital IIR filter.

14. † A direct form implementation of the FIR filter is expressed as

$$y(n) = ax(n) + bx(n-2) + cx(n-3).$$

Assume the time for one multiply-add operation is T .

- (a) Pipeline this filter such that the clock period is approximately T .

- (b) Draw a block filter for a block size of 3. Pipeline this filter such that the clock period is T . What is the sample rate of the system?
- (c) Pipeline the filter in (b) such that the clock period is $T/2$. Show the cutset and label the outputs. What is the sample rate now?

15. † A recursive filter is defined by

$$x(n) = ax(n-2) + u(n).$$

- (a) Pipeline this multiply-add operator by 2 stages by first breaking up the multiply-add operation into 2 components and by redistributing the delay elements in the loop.
- (b) Interleave the computation from above with

$$y(n) = by(n-2) + v(n)$$

using the same hardware. Now pipeline the multiply-add operation by 4 stages. Show all the circuits needed for this implementation.

16. Name the different sources of power consumption in digital CMOS circuits. Elaborate on the influence of technology scaling on these sources?
17. Consider a 5-tap FIR filter

$$y(n) = \sum_{k=0}^4 h_k x(n-k)$$

Assume a multiplier delay of 3 t.u. and an adder delay of 1 t.u.

- (a) Pipeline along 1 cutset in the direct form to reduce the critical path. You should achieve the minimum T_{crit} .
- (b) Assume that $V_{\text{dd}} = 3 \text{ V}$ and $V_{\text{t}} = 0.4 \text{ V}$. What is the power consumption of the pipelined filter as a percentage of the original filter (power ratio)?

18. † Two implementations of an 8-tap FIR filter are shown in Figure 10. Assume the critical path of a multiplier to be twice that of an adder, that is, $T_{\text{mult}} = 2T_{\text{add}}$. Therefore, the charging capacitance of a multiplier is twice that of an adder. The critical path of the direct form structure in Figure 10(a) is $T_{\text{mult}} + 7T_{\text{add}} = 9T_{\text{add}}$. The structure in Figure 10(b) can be operated with a lower supply voltage to meet the clock period or sampling period constraint of $9T_{\text{add}}$. Thus, the structure in Figure 10(b) can be used to reduce power consumption. Assume that the structure in Figure 10(a) is operated with a supply voltage of 4 V. Assume the technology threshold voltage to be 0.5 V. The supply must be greater than 1.2 V to achieve the acceptable noise margin. What is the minimum supply voltage at which the structure shown in Figure 10(b) can be operated to achieve the desired sampling period of $9T_{\text{add}}$? Calculate the percentage of reduction in power consumption for this structure as compared with the one from Figure 10(a). Neglect the propagation delay and capacitance of delay elements in calculation of the critical path or power consumption.

19. † A datapath has a total capacitance of C_{tot} . This datapath is pipelined by M levels. Let C_{latch} represent the total capacitance of the latches used for 1 pipelining stage. The pipelined system is operated with lower supply voltage to reduce the power consumption. Assume both systems are operated at same

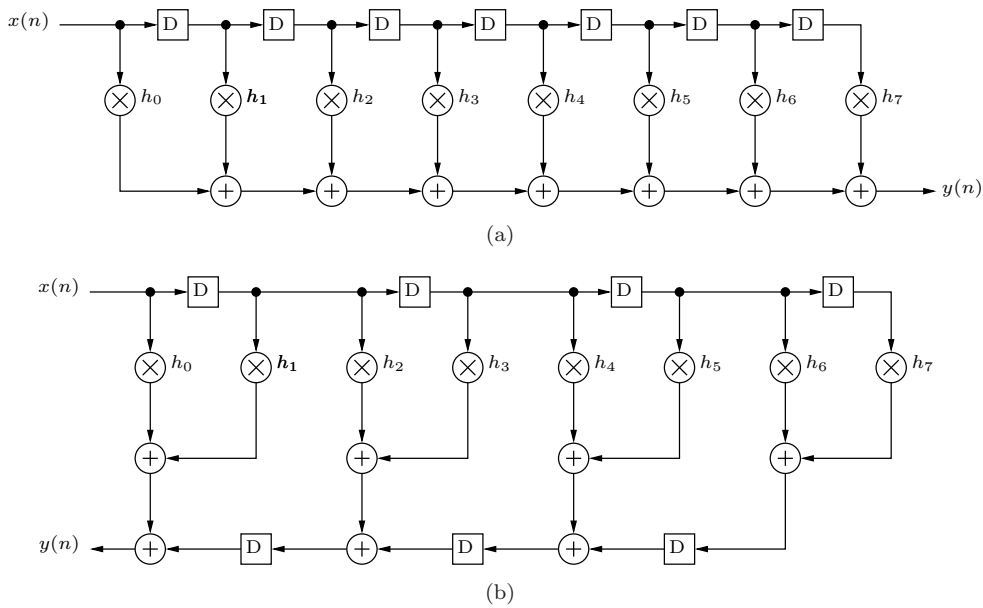


Figure 10: Two implementations of an 8-tap FIR filter.

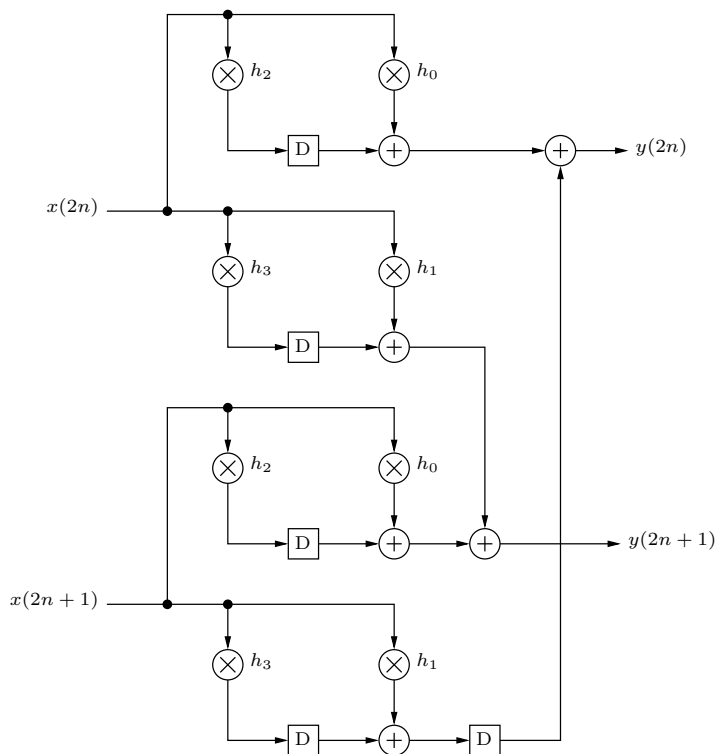


Figure 11: Decomposed 4-tap FIR filter.

speed and assume the propagation delay of the latch to be negligible. Let $C_{\text{tot}} = 10C_{\text{latch}}$, $V_{\text{dd}} = 4 \text{ V}$, and $V_t = 0.6 \text{ V}$. Calculate the power consumption of the pipelined system as a percentage of that of the sequential systems for different values of M . What is the optimal M for least power consumption?

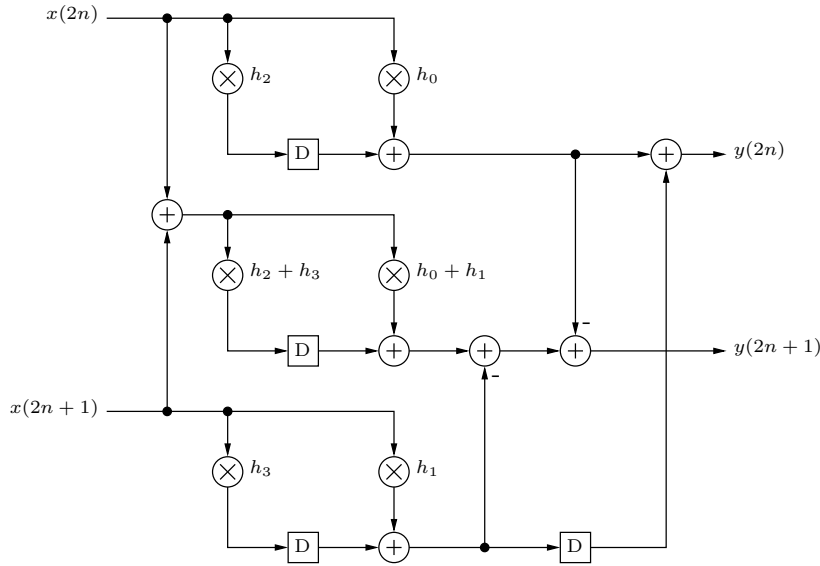


Figure 12: Fast FIR implementation of a 4-tap FIR filter.

20. † Calculate the power reduction of a computation if it is pipelined by 4 stages and processed using a block structure with block size 4, but is operated with the same sample rate as the original system. Assume that the original system was operated at a supply voltage of 5 V, and assume the threshold voltage of the CMOS process to be 0.4 V. Calculate the power consumption of the parallel-pipelined system as compared with the original system. What is the operating supply voltage of the parallel-pipelined system?
21. For the two 4-tap FIR filters in Figure 11 (decomposed form) and Figure 12 (fast FIR) show that their output sequence is the same as the sequence of the original filter.
- What is the complexity per sample compared to the original filter?
 - What is the critical path compared to the original filter, both direct and transposed form?
 - What happens with the complexity when the filter length is increased?
22. † Express the 2-parallel filter algorithm

$$Y_0 = X_0 H_0 + z^{-2} X_1 H_1$$

$$Y_1 = X_0 H_0 + X_1 H_1 - (X_0 - X_1)(H_0 - H_1)$$

in terms of a post-processing matrix, a diagonal matrix, and a pre-processing matrix. Obtain another 2-parallel structure using the transpose of this formulation.

23. Consider a 5-tap FIR filter defined by the transfer function

$$H(z) = a + bz^{-1} + bz^{-3} + cz^{-4} + cz^{-5}.$$

Design a filter with minimum number of multipliers. Design a 2-parallel filter using the fast FIR approach which also uses a minimum number of multipliers.

24. † Consider the wave digital filter shown in Figure 13. Assume that $T_{\text{mult}} = 20$ ns and $T_{\text{add}} = 8$ ns.

- (a) Calculate the iteration bound.
- (b) Calculate the critical path.
- (c) Pipeline and/or retime the filter to achieve a critical path equal to the iteration bound.

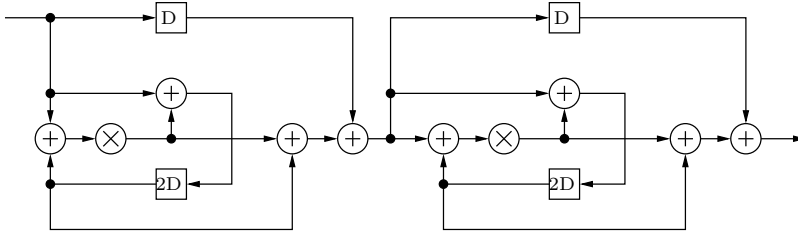


Figure 13: A wave digital filter structure.

25. † Consider the DFG in Figure 14.
 - (a) What is the maximum sample rate?
 - (b) What is the fundamental limit of the sample rate?
 - (c) Retime to minimize the clock period.

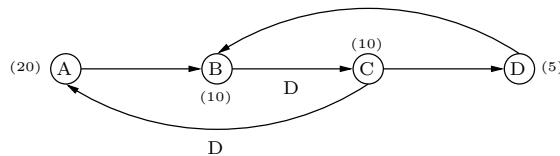


Figure 14: A DFG with node computation times.

26. † Recall the 8th-order IIR filter from Figure 7. Assume that $T_{\text{mult}} = 2$ ns and $T_{\text{add}} = 1$ ns.
 - (a) Calculate the iteration bound.
 - (b) Calculate the critical path.
 - (c) Pipeline and/or retime the filter to achieve a critical path of 2 ns.
27. † Interblock pipelining of recursive DFGs.
 - (a) Retime the system in Figure 15(a) to achieve interblock pipelining, that is, each interblock communicating edge should have at least one delay element.
 - (b) To obtain interblock pipelining for the system shown in Figure 15(b), use an appropriate slow-down approach and then use retiming. What is the hardware utilization efficiency of this system?
28. Recall the FFT algorithm.
 - (a) How many non-trivial twiddle factors has an 8-point FFT?
 - (b) Elaborate on hardware-mapped, pipelined, and time-multiplexed implementations of this algorithm.
 - (c) Describe the concept of bit-reversed addressing.

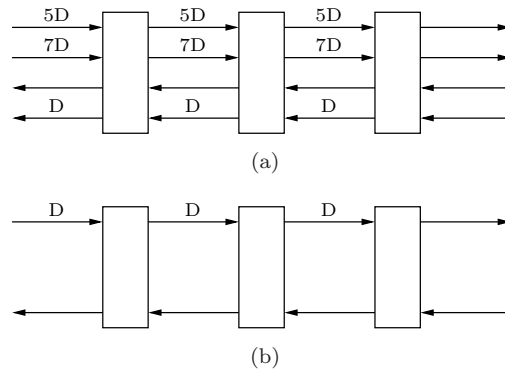


Figure 15: Two recursive DFGs.

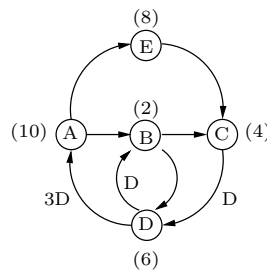


Figure 16: A DFG with node computation times.

29. There are two sequences x and y with length N and M , respectively. How many points are needed to represent the frequency response of their convolution.
30. † The DFG in Figure 16 is subject to unfolding. The numbers in parentheses are the computation times of the nodes.
- What is the iteration bound of this DFG? What is the actual iteration period?
 - Retime this DFG to minimize the iteration period. What is the actual iteration period of the retimed DFG?
 - Unfold both the original and the retimed DFG by a factor of 2. What are their iteration periods?

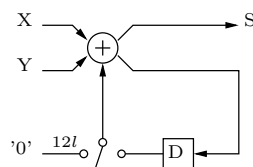


Figure 17: Bit-serial adder.

31. † Unfold the bit-serial adder with wordlength 12 in Figure 17 by factors 4 and 5 to obtain the corresponding digit-serial adders.
32. Consider the 2-section biquad filter shown in Figure 18. Assume a folding factor $N = 5$, a multiplier which is pipelined by two stages, and an adder which is pipelined by one stage.

- (a) Perform retiming for folding.
 (b) Draw the folded architecture with the following folding sets:

$$S_{M1} = \{M2, M1, M3, M6, M7\}$$

$$S_{M2} = \{M4, -, M5, M8, M9\}$$

$$S_{A1} = \{A4, -, A1, A2, A3\}$$

$$S_{A2} = \{A5, A6, A7, A8, -\}$$

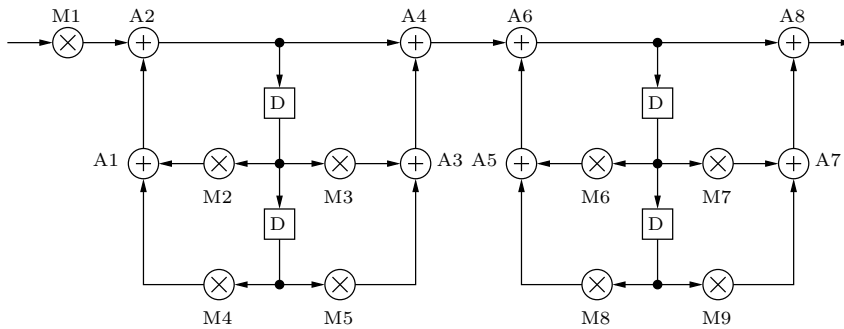


Figure 18: Biquad filter with 2 sections.

33. Recall the lattice filter from Figure 7 with a folding factor $N = 2$.

- (a) Retime for folding.
 (b) Fold the retimed graph.
 (c) Minimize the number of registers by lifetime analysis.

$$S_{M1} = \{M2, M1\}$$

$$S_{M2} = \{M3, M4\}$$

$$S_{A1} = \{A1, A2\}$$

$$S_{A2} = \{A4, A3\}$$

34. Consider the digital filter in Figure 19.

- (a) Fold this architecture with folding factor 4 using the folding set

$$S_A = \{A4, A3, A2, A1\}$$

$$S_M = \{M1, M3, M2, -\}$$

Multipliers and adders are pipelined by 2 and 1 stages, respectively. Preprocess the DFG for folding by pipelining/retiming if necessary.

- (b) Draw the folded architecture and show the switching instances.
 (c) Make a lifetime chart and find the lowest number of registers needed.
 (d) What are the advantages and disadvantages with folding?

35. Fold the digital filter from Figure 3 with a folding factor $N = 4$ using the provided folding set. Assume the multiplier to be pipelined by 2 stages and the adder by 1 stage, that is, a multiplier requires 2 t.u. and an adder 1 t.u.

- (a) Preprocess the DFG for folding by pipelining if necessary.

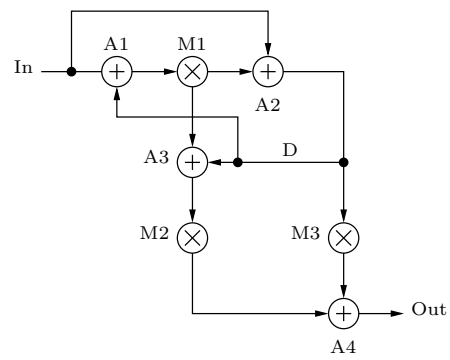


Figure 19: An IIR filter structure.

(b) Draw the folded architecture and show the switching instances.

$$S_A = \{A1, A2, A3, A4\}$$

$$S_M = \{-, -, M2, M1\}$$

Exam from 2004-12-13

- Consider the lattice filter in Figure 20. Assume that an addition takes 1 t.u. and a multiplication 2 t.u.
 - What is the critical path of this architecture?
 - What is the formal definition of the iteration bound and what does it mean? Determine the iteration bound of this algorithm.
 - What can you do to improve the architecture so it achieves the iteration bound? (3 approaches)
 - Draw the improved architecture that results in minimum overhead.

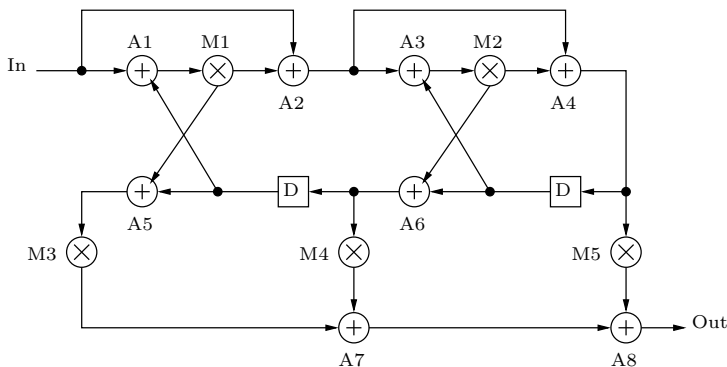


Figure 20: The lattice filter for problem 1.

- A 6th-order orthogonal filter is shown in Figure 21. All operations (R) are CORDIC rotation operations. Each rotation takes T t.u.
 - Determine the iteration bound and the critical path of this filter.
 - Improve the filter to achieve a critical path of $2T$ t.u. Show all the cutset locations used for retiming explicitly.

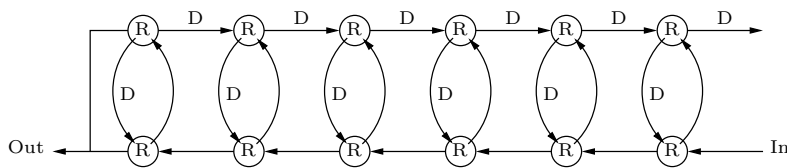


Figure 21: A 6th-order orthogonal filter.

3. From a specification you should design 2 FIR filter architectures. The filter has 8 taps computed by MATLAB's `fir1` function resulting in

$$\mathbf{h} = [0.0136, 0.0557, 0.1655, 0.2652, 0.2652, 0.1655, 0.0557, 0.0136]$$

A multiplier has a propagation delay of 3 ns and an adder of 1 ns. The delay introduced by the registers is neglected. Furthermore, you can assume that all signals are $-1 \leq x < 1$.

- Calculate the values of the coefficients when a wordlength of 8 bits and truncation are used.
 - The coefficients have certain properties which can be used to reduce the algorithmic strength and increase the precision of the calculation for a given number of bits. Describe such possibilities.
 - To avoid overflow we can either scale the input signals or allow for an increased internal dynamic range. Describe one internal and one external way to ensure avoidance of overflow.
 - Design a filter architecture for a sampling rate greater than 300 Msamples/s. Motivate your choice of architecture by comparing with alternative architectures.
 - In another application, we have a lower requirement on the sampling rate (> 30 Msamples/s). Propose another architecture that uses the relaxed requirement to reduce the area.
4. Shown in Figure 22 are the probability distributions of the quantization error for two common quantization schemes. Assume that $\Delta = 2^{-(w-1)}$, where w is the desired wordlength. Assign the names of the schemes and fill in the number on the respective axes in terms of Δ . Calculate mean values and variances for both schemes.

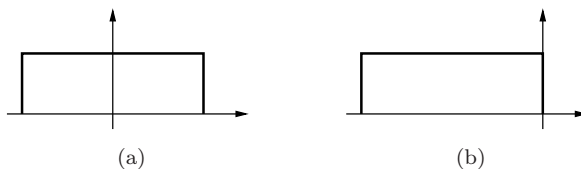


Figure 22: Two probability distributions for quantization schemes.

5. Consider the system in Figure 23.
- Unfold the system 2 times and draw the new system.
 - Change the switching instances from $4l$ to $3l$ and unfold again. Note that the instance $3l + 3$ becomes obsolete.
 - Which are the advantages and disadvantages of the unfolded systems compared to the original one?
6. Consider the FIR filter in Figure 24. The time required for a multiply operation is $4T$ and addition takes T . Assume that $V_{dd} = 5$ V, $V_t = 0.6$ V, $C_{add} = C$, and $C_{mult} = 4C$.
- Transpose the filter and describe the transformation process.
 - Pipeline the transposed filter to achieve a critical path of $\leq 4T$ and compare the power consumption of the pipelined filter with the non-pipelined version.

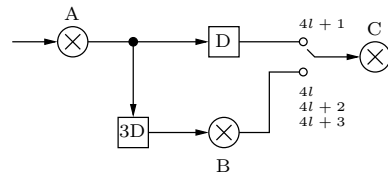


Figure 23: The DFG for problem 5.

- (c) Parallelize the transposed filter 2 times and compare the power consumption of the parallel filter with the two previous ones. Note that the number of registers should be the same as in the original filter.

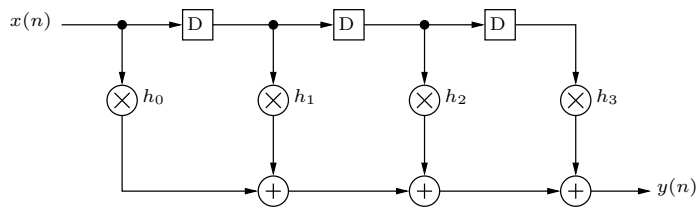


Figure 24: A 4-tap FIR filter in direct form.

7. Consider the digital filter in Figure 25.

- (a) Fold the architecture with folding factor 3 using the folding set

$$S_A = \{A3, A5, -\} \quad \text{and} \quad \{A4, A1, A2\}$$

$$S_M = \{M2, M1, M3\}$$

Assume the multiplier to be pipelined by two stages and the adder by one stage. Preprocess the DFG for folding by pipelining/retiming if necessary.

- (b) Draw the folded architecture and show the switching instances.
 (c) Make a lifetime chart and find the lowest number of registers needed.
 (d) What are the advantages and disadvantages with folding?

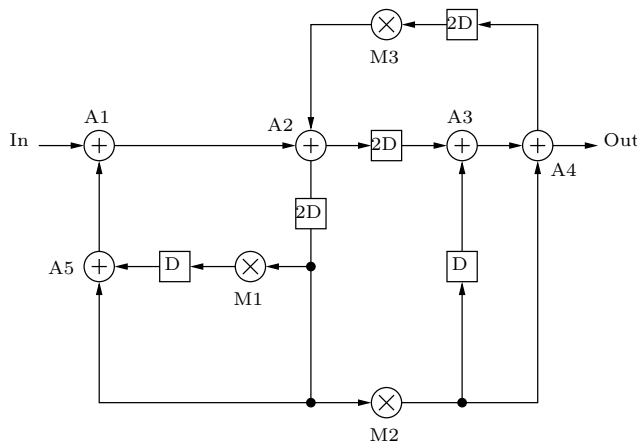


Figure 25: The IIR filter for problem 7.

Exam from 2005-12-12

1. Consider the digital filter in Figure 26, where a multiplication takes 2 t.u. and an addition takes 1 t.u. The units' capacitances are proportional to their execution times.

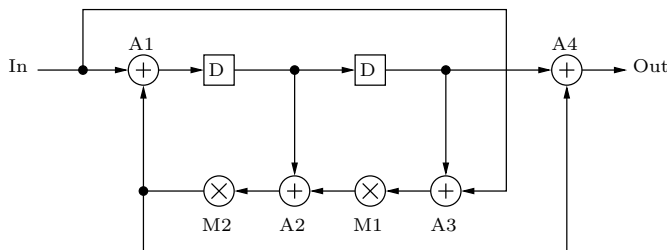


Figure 26: .

- (a) Determine iteration bound and critical path of this filter. Pipeline and/or retime to achieve a critical path equal to T_∞ .
 - (b) Describe the concept of supply voltage scaling. What is the achievable power reduction due to this scaling? Assume $V_{dd} = 1.8$ V and $V_t = 0.6$ V.
2. Unfold the DFG in Figure 27 by a factor $J = 3$.

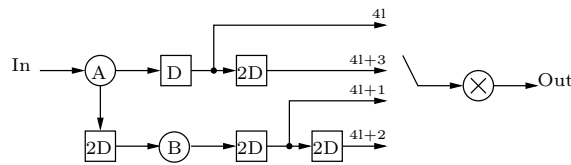


Figure 27: .

3. Consider a 7-tap linear-phase FIR filter. Additions and multiplications require 2 ns and 4 ns, respectively.
 - (a) Given a coefficient wordlength of 8 bits in 2's complement notation. How do you guarantee to use the given number range $[-1, 1)$ as efficient as possible. Show with a number example.
 - (b) Draw an area-efficient architecture that fulfills the filter's sample rate requirement of ≥ 90 Msamples/s. Motivate your choice by comparing to other possible architectures.
 - (c) Now the sample rate only has to be ≥ 20 Msamples/s. Draw and explain another area-efficient architecture that fulfills the new requirement.

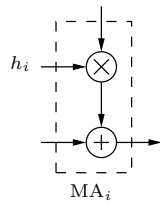


Figure 28: .

- (d) Figure 28 shows a multiply-add operation that involves coefficient h_i . This block is to be used for a general 6-tap FIR filter. Draw a hardware-mapped architecture that uses MA_i and assign the corresponding labels i .
- (e) Fold the filter given that only three such multiply-add units are available. Each multiply-add unit is 1-stage pipelined. Derive a folding set by assuming that operation MA_i is processed in unit $S_{\lfloor i/N \rfloor}$ at times $(i + 1) \% N$.
- (f) What is the sample rate of the folded architecture? Compare to the original architecture from (3d).
4. Consider a 16-point FFT as in Figure 29, where the complex arithmetic unit adder/subtractor has a delay $T_{\text{add}} = 1$ ns and the multiplier $T_{\text{mult}} = 3$ ns. The input and coefficient wordlengths are both 8 bits in 2's complement notation in the range $[-1, 1)$. Furthermore, the inputs are limited to $\pm \frac{1}{\sqrt{2}}$.

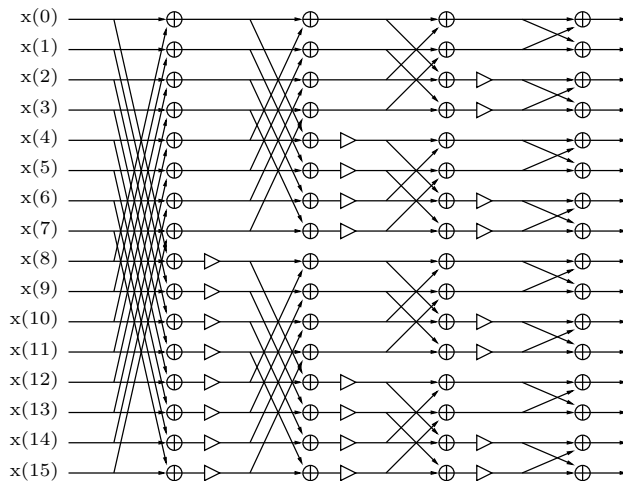


Figure 29: .

- (a) Label the outputs top to bottom in Figure 29. How is this addressing mode called?
- (b) What is the critical path? Pipeline the structure to achieve $T_{\text{crit}} = 4$ ns.
- (c) How much does the wordlength need to be increased to avoid overflow?
- (d) Figure 30 shows a pipeline FFT structure, where each R2 BF block consists of a radix-2 butterfly unit and a multiplier. Now consider a 1024-point FFT. How many R2 BF stages do we need?

- (e) Assume the input data arrives in natural order, that is, $x(0), x(1), \dots$. What is the memory requirement (in number of samples) for each stage? Explain the functionality of the architecture.

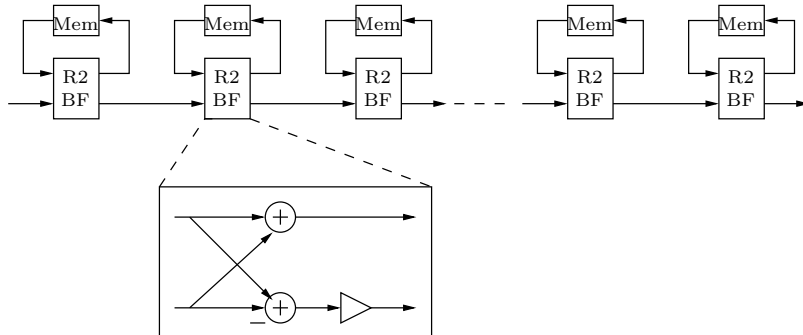


Figure 30: .

5. The filter in Figure 31 is subject to folding. The pipeline stages for adder and multiplication units are 1 and 2, respectively. Assume a folding factor of $N = 6$ and the following folding sets:

$$S_A = \{A1, -, -, A2, A3, -\}$$

$$S_M = \{-, M2, M3, -, M1, -\}$$

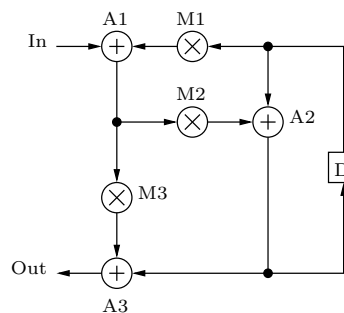


Figure 31: .

- What is the iteration bound of this filter?
- Preprocess the filter to carry out folding.
- Draw the folded architecture.
- Determine the minimum number of registers needed and show the corresponding allocation table.
- Redraw the register-minimized architecture.

